

CHAPTER-3

MEASUREMENT OF VOLTAGE & CURRENT


01. Ans: (b)

Sol: In the question For a **full wave rectifier** rms = average value

$$= 100\text{v}$$

04. Ans: (d)

Sol:

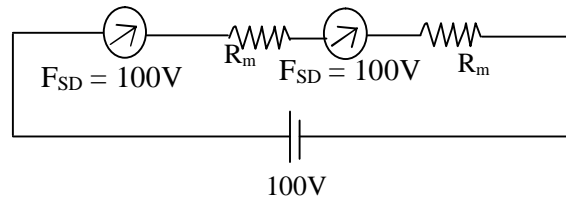

The two voltmeters are connected in series so the current is same so both the voltmeters indicate equal readings because they have same internal resistances.

05. Ans: (b)

Sol: PMMC instrument has linear scale


FSD – 0.1 mA

$$\frac{1}{2} \text{ FSD} - 0.05 \text{ mA}$$

Two mark questions

43. Ans: (c)

Sol:

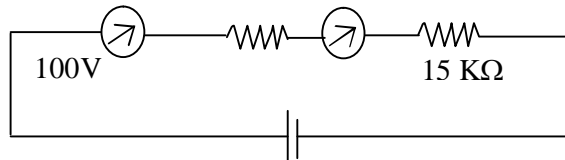

Resistance of meter A is $100 \times 100 = 10,000 = 10 \text{ K}\Omega$

Total Resistance = $R_A + R_B = 10\text{K}\Omega + 15\text{K}\Omega = 25\text{K}\Omega$

Voltmeter A reading is 100v for a resistance of 10KΩ by voltage division the voltmeter

B reading is 150v for a resistance of 15 kΩ

Total voltage = $100\text{v} + 150\text{v} = 250 \text{ volts}$

45. Ans: (d)

Sol: $u(t) = 5 + 10 \cos (314 + 30^\circ)$

MI instrument reads RMS value & it is used for both A.C & D.C


$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}} = \frac{10}{\sqrt{2}} = 5\sqrt{2}$$

$$\text{Voltmeter reading} = \sqrt{5^2 + (5\sqrt{2})^2} = \sqrt{75} \text{ V}$$

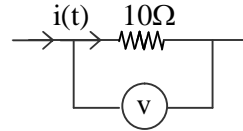47. Ans: (a)



Sol: PMMC instrument measure average value

$$\frac{12 \times 10 + 5 \times 10}{2} = \frac{120 + 50}{2} = \frac{170}{2} = 85 \text{ volts}$$



48. Ans:(c)

Sol:

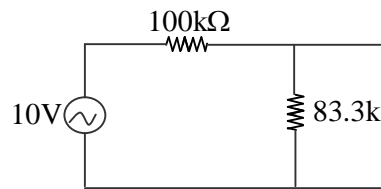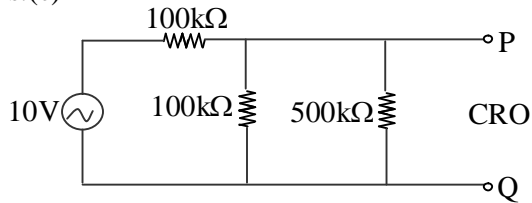

By Voltage division

$$V_{83.3k\Omega} = \frac{10 \times 83.3K}{100K + 83.3K}$$

$$= 4.54 \text{ Volts}$$

49. Ans: (a)

Sol: N = 100

$$l = 10\text{mm} \quad b = 20 \text{ mm}$$

$$B = 200 \text{ mT} \quad \theta = 90^\circ$$

$$I = 50 \text{ mA}$$

$$T_d = BINA$$

$$= 200 \times 10^{-3} \times 50 \times 10^{-3} \times 100 \times 10 \times 10^{-3} \times 20 \times 10^{-3}$$

$$= 200 \times 10^{-6} \text{ N-m}$$

$$= 200 \mu\text{N-m}$$

50. Ans: (b)

Sol: $T_d = 240 \mu\text{Nm}$ $\theta = 120^\circ$ $I = 10\text{A}$

$$\frac{dL}{d\theta} = ?$$

$$T_d = \frac{1}{2} I^2 \frac{dL}{d\theta}$$

$$\frac{dL}{d\theta} = \frac{2T_d}{I^2} = \frac{2 \times 240 \times 10^{-6}}{10^2} = 4.8 \mu\text{H/rad}$$

53. Ans: (b)

$$\begin{aligned} \text{Sol: } S_{AC\ H(w)} &= \frac{R_{V\ H(w)}}{V_{rms}\ FSD} \\ &= \frac{0.45 \frac{V_{rms\ FSD}}{I_{DC\ FSD}}}{V_{rms\ FSD}} = 0.45 \times \frac{1}{I_{DC\ FSD}} \\ &= 0.45 S_{DC} \end{aligned}$$

54. Ans: (c)

$$\begin{aligned} \text{Sol: } S_{V(H\omega)} &= 0.45 S_{DC} \\ &= 0.45 \times 10k\ \Omega/V = 4.5k\ \Omega/V \end{aligned}$$

55. Ans: (c)

Previous IES questions

01. Ans: (b)

$$\begin{aligned} \text{Sol: } (0-150)V \quad G.A.E &= 1\% \\ 150 \times \frac{1}{100} &= 1.5V \\ 75 \times \frac{x}{100} = 1.5 &\Rightarrow x = \frac{100 \times 1.5}{75} = 2\% \end{aligned}$$

12. Ans: (a)

$$\begin{aligned} \text{Sol: } I &= 3 + 4\sqrt{2} \sin 314t \\ \text{Pmmc instrument used only for D.C so } I &= 3A \end{aligned}$$

13. Ans: (c)

$$\begin{aligned} \text{Sol: } \text{Given } V &= 8V \\ S &= \frac{2k\Omega}{V} \text{ for } 10V \text{ scale meter:} \\ \Rightarrow R_V &= 2 \times 10 \Rightarrow 20\ k\Omega \\ \text{Before inserting meter} \\ I &= \frac{8}{1k\Omega} \Rightarrow 8mA \\ \text{After inserting meter} \\ R_V \parallel 1k\Omega &= 0.9523\ k\Omega \\ \therefore V &= 8 \times 10^{-3} \times 0.9523 \\ &= 7.62\ V \end{aligned}$$

16. Ans: (b)

$$\begin{aligned} \text{Sol: } I &= 2 + 4 \sin 314t \\ \text{Hot wire instrument are used for both A.C \& D.C \& measures RMS values.} \end{aligned}$$

$$\begin{aligned} I_{rms} &= \frac{I_m}{\sqrt{2}} = \frac{4}{\sqrt{2}} = 2\sqrt{2} \\ I &= \sqrt{2^2 + (2\sqrt{2})^2} = 2\sqrt{3} = 3.46A \end{aligned}$$

17. Ans: (d)

Sol: (0-250)V G.A.E 1%
For 100V L.E----?

$$250 \times \frac{1}{100} = 2.5 \text{ V}$$

$$100 \times \frac{x}{100} = 2.5 \Rightarrow x = \frac{2.5 \times 100}{100} = 2.5\%$$

21. Ans: (b)

Sol: M.I instrument $T_d \propto I^2$, spring control
1 mA -----100V $T_C \propto \theta$

0.5 mA-----?

All the instruments are current measuring instruments

$$\frac{V_1^2}{V_2^2} = \frac{I_1^2}{I_2^2}$$

$$\frac{V_1}{V_2} = \frac{I_1}{I_2} \Rightarrow \frac{100}{V_2} = \frac{1 \times 10^{-3}}{0.5 \times 10^{-3}} \Rightarrow V_2 = 100 \times 0.5 = 50 \text{ V}$$

23. Ans: (a)

Sol: (0-200) V G.A.E = 1%
50 V ----- L.E = ?

$$200 \times \frac{1}{100} = 2 \text{ Volts}$$

$$50 \times \frac{x}{100} = 2 \Rightarrow x = \frac{2 \times 100}{50} = 4\%$$

34. Ans: (c)

Sol: A rectifier instrument measures rms value
meter reads \rightarrow 100V
But indicating \rightarrow 111V

35. Ans: (b)

Sol: $R_{sh} = 0.55 \Omega$ $R_m = 5 \Omega$ $I_m = 1 \text{ mA}$

$$R_{sh} = \frac{R_m}{m-1} \Rightarrow m-1 = \frac{5}{0.55}$$

$$m = \frac{5}{0.55} + 1$$

$$\frac{I}{I_m} = 10.09$$

$$I = 10.09 \times 1 \times 10^{-3} \\ = 10.09 \text{ mA.}$$

39. Ans: (a)

Sol: PMMC will read only DC values. Sol the voltmeter reading is oscillates around zero

Previous Gate questions

03. Ans: (d)

Sol: In Pmmc instrument the current passes through Spring & the coil, when one of the spring is snap it will be an open circuit i.e $I = 0$

07. Ans: (d)

Sol: sensitivity = $1000\Omega/\text{volt}$

Full scale value = 100V


Half full scale value = 50V

$$I = \frac{V}{R} \quad \text{sensitivity} = \frac{1}{I_{f.s.d}}$$

$$I_{f.s.d} = \frac{1}{1000} = 0.1\text{mA}$$

$$I = \frac{50}{1000 \times 100} = 0.5\text{mA}$$

09. Ans: (a)

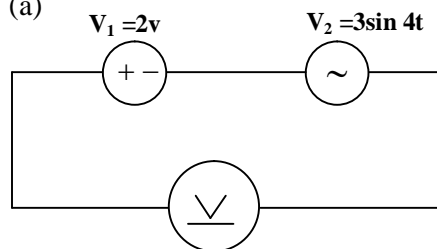Sol:

Pmmc instruments are used to measure D.C only so voltmeter reads only 2V

10. Ans: (a)

Sol: Voltmeter F.S.D = 10V

$S_V = 1000\Omega/\text{volt}$

$R_m = 1000 \times 10 = 10\text{ k}\Omega$


By voltage division

For $10\text{K}\Omega$ _____ 5V

For $50\text{K}\Omega$ _____ 25V


So supply voltage

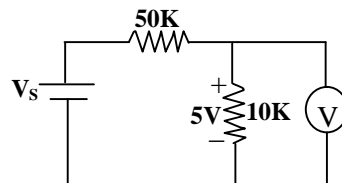$V_s = 5 + 25 = 30\text{ V}$ (\because KVL)




11. Ans: (b)

Sol:

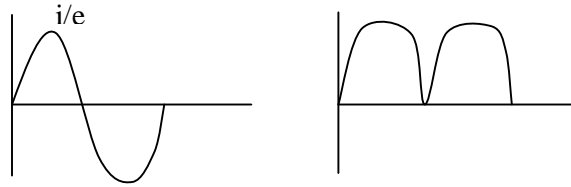

Form factor = 1.11

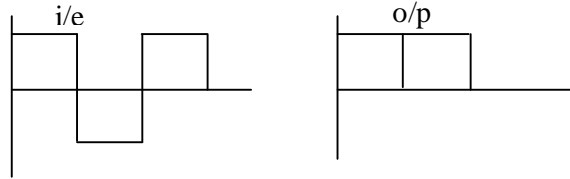

$$\text{Form factor} = \frac{1}{1.11}$$

12. Ans: (c)

Sol: $I_1 = 100 \text{ mA}$

$I_2 = 99 \text{ mA}$

Accuracy = 1%


$I_3 = ?$

By KCL

$I_1 + (-I_2) = I_3$

$100\text{mA} \pm 1\% - 99\text{mA} \pm 1\% = I_3$

$I_3 = 1\text{mA} \pm 2\%$

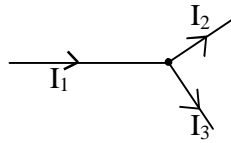

15. Ans: (c)

Sol: $L = 10 + 3\theta - \frac{\theta^2}{4} \mu\text{H}$

$$\frac{dL}{d\theta} = 0 + 3 - \frac{2\theta}{4} \mu\text{H} = 3 - \frac{\theta}{2} \mu\text{H}$$

$$K = 25 \times 10^{-6} \text{ N-m/rad}$$

$$I = 5\text{A}$$

$$T_d = \frac{1}{2} I^2 \frac{dL}{d\theta} \quad T_c = K\theta$$

$$T_d = T_c$$

$$\theta = \frac{1}{k} \frac{1}{2} I^2 \frac{dL}{d\theta}$$

$$\theta = \frac{5^2 \times (3 - \frac{\theta}{2}) \times 10^{-6}}{2 \times 25 \times 10^{-6}}$$



$$2\theta + \frac{\theta}{2} = 3$$

$$\theta = \frac{6}{5} = 1.2 \text{ rad}$$

17. Ans; (c)

Sol: Under Forward bias diode resistance is Zero

Under Reverse bias diode resistance is ∞

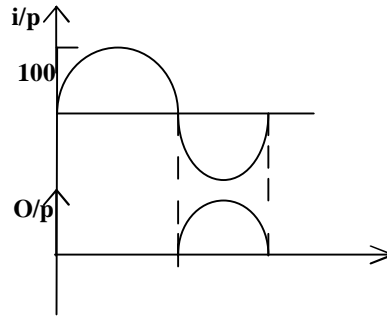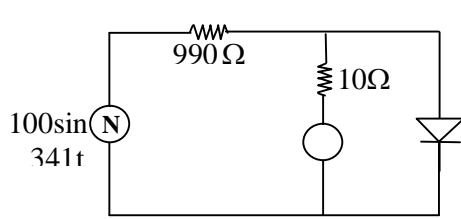

$$V_{10\Omega} = \frac{-10 \times \frac{100}{\pi}}{990 + 10} = \frac{1}{\pi}$$

$$I = \frac{-V}{R}$$

$$= \frac{1}{\pi} = \frac{1}{10\pi}$$

$$= -31.84 \text{ mA}$$

18. Ans: (a)

Sol: $N = 100$ $l = 10 \text{ mm}$ $b = 20 \text{ mm}$

$\theta = 90^\circ$ $B = 200 \text{ mT}$ $I = 50 \text{ mA}$

$T_d = BINA$

$$= 200 \times 10^{-3} \times 50 \times 10^{-3} \times 100 \times 10 \times 10^{-3} \times 20 \times 10^{-3}$$

$$= 200 \mu\text{Nm}$$

21. Ans: (b)

Sol: $S_V = 500 \Omega/V$


F.S.D = 100V

$R_m = 500 \times 100 = 50 \text{ K}\Omega$

Voltmeter reading = 20 v

In parallel branches voltage is same

So $R_x = 50 \text{ k}\Omega$

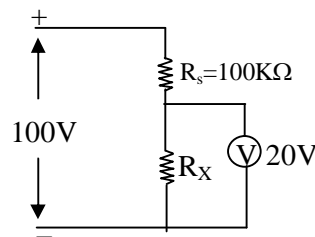

22. Ans: (c)

Sol: Input Ac rms = 100 v, $I = 1 \text{ mA}$

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$$

$$V_m = 100\sqrt{2} \text{ volts}$$

For a full wave rectifier

$$V_{\text{dc}} = \frac{2V_m}{\pi} = \frac{2 \times 100\sqrt{2}}{\pi} = 90.063 \text{ volts}$$

Applying KVL

$$90.063 = R_s (1 \times 10^{-3}) + 100 (1 \times 10^{-3})$$

$$R_s = \frac{90.063 - 0.1}{10^{-3}} = 89.96 \text{ k}\Omega$$

23. Ans: (c)

$$\text{Sol: } I = \left[-6 \sin 100\Lambda t + 6\sqrt{2} \cos(300t + \sqrt{2}) + 6\sqrt{2} \right] \text{A}$$

$$\sqrt{\left(\frac{-6}{\sqrt{2}}\right)^2 + \left(\frac{6\sqrt{2}}{\sqrt{2}}\right)^2 + (6\sqrt{2})^2} = \sqrt{126}$$

24. Ans: (a)

$$\text{Sol: } R_{\text{sh}} = \frac{R_m}{m-1} = \frac{100 \times 10^{-3} / 2}{\frac{10}{2} - 1}$$

$$R_{\text{sh}} = \frac{50 \times 10^{-3}}{4} = 12.5 \text{ m}\Omega \text{ (Ans : a)}$$

25. Ans: (b)

$$\text{Sol: } R_m = 100\Omega \quad I_{f.s} = 1 \text{ mA}$$

$$R_{\text{se}} = R_m (m-1)$$

$$= R_m \left(\frac{V}{V_m} - 1 \right)$$

$$= 100 \left(\frac{10}{0.1} - 1 \right) = 9900\Omega$$

$$= 9.9 \text{ k}\Omega.$$