

CHAPTER – 4 MEASUREMENT OF RESISTANCE

One Mark Questions

02. Ans: (d)

Sol: There are three meters

(i). Meter one having a sensitivity $S = 1000\Omega/v$
Resistance offered $R_v = \text{sensitivity} \times \text{voltage range}$
 $R_v = 1000 \times 100 = 100k\Omega$

(ii). Meter two having a sensitivity $S = 20,000\Omega/v$
 $R_v = 20,000 \times 100 = 2M\Omega$

(iii) Meter three is an Electronic meter

Meters two and three having high sensitivity less loading effect
Meter one has less sensitivity more loading effect

Two Marks Questions

30. Ans: (b)

Sol:


The given circuit is

Sensitivity (S) = 20,000Ω/v

$R_v = S \times \text{voltage range}$

$R_v = 20,000 \times 1$

$R_v = 20k\Omega$

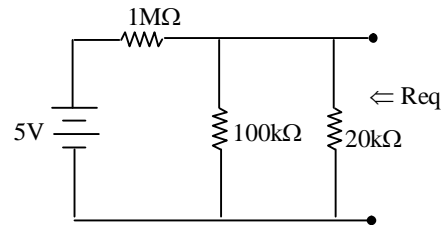

$$\text{From the circuit } R_{eq} = \frac{100 \times 10^3 \times 20 \times 10^3}{100 \times 10^3 + 20 \times 10^3} + 1 \times 10^6$$

$$R_{eq} = 1016.66\Omega$$

From voltage division rule

$$V_m = 5 \times \frac{100}{100 + 1019.6} = 0.45V$$

31. Ans: (d)

Sol: Voltage across the 500kΩ resistor is exactly 10V

Sensitivity of voltmeter 20kΩ/V

The readings indicated on its 50V and 5V range?



Voltage across V_{AB} by voltage division rule

$$V_{AB} = \frac{500}{500 + 500} \times 20$$

$$V_{AB} = 10V$$

Reading indicated on 50V range is

$$R_v = S \times \text{voltage range}$$

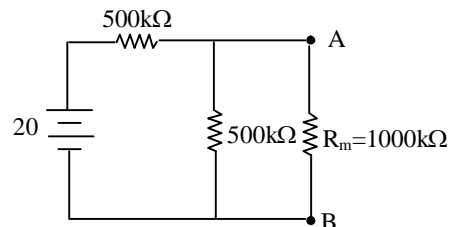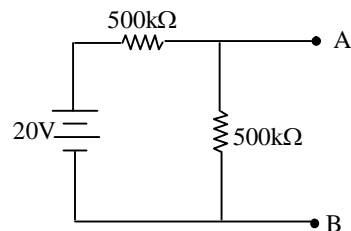

$$R_v = 20 \times 10^3 \times 50 = 1000 \text{ k}\Omega$$

R_v connected across 'AB'

$$R_{eq} = \frac{500 \times 1000}{500 + 1000} = 333.3 \Omega$$

$$V = 20 \times \frac{333.3}{500 + 333.3} = 8 \text{ V}$$

Reading indicated on '5V' range is

$$R_v = S \times \text{voltage range}$$

$$R_v = 20 \times 10^3 \times 5 = 100 \text{ k}\Omega$$

$$R_{eq} = \frac{500 \times 100}{500 + 100} = 83.33 \Omega$$

$$V = 20 \times \frac{83.33}{500 + 83.33} = 2.86 \text{ V}$$

32. Ans: (a)

Sol:

Voltmeter reads 60V on 100V full scale

Ammeter reads 0.8A on 1 A full scale

Both meters are having guaranteed accuracy error 1% of full scale

$$V_m = 60 \text{ V} \quad I_m = 0.8 \text{ A}$$

Voltmeter, G.A.E = 1% of full scale voltage

$$= \frac{1}{100} \times 100 = 1$$

$$\% \text{ Limiting error} = \frac{\text{G.A.E}}{V_m} \times 100$$

$$= \frac{1}{60} \times 100 = 1.66\%$$

Ammeter, G.A.E = 1% of full scale current

$$= \frac{1}{100} \times 1 = 0.01$$

$$\% \text{ limiting error} = \frac{\text{G.A.E}}{I_m} \times 100$$

$$= \frac{0.01}{0.8} \times 100 = 1.25\%$$

$$\text{Resistance } R = \frac{V_m(\pm \text{L.E})}{I_m(\pm \text{L.E})}$$

$$R = \frac{60(\pm 1.66\%)}{0.8(\pm 1.25\%)}$$

$$R = 75(\pm 2.91\%)$$

$$\% \text{L.E} = 2.91\%$$

33. Ans: (b)

Sol:


From the given data

$$\text{Total } R_{se} = 2020 \Omega$$

$$L = 0.3H$$

The meter read correctly at dc as well as at 50Hz ac

We have connect a capacitor of value

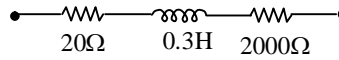

$$C = \frac{0.41 \times L_m}{(R_{se})^2}$$

$$C = \frac{0.41 \times 0.3}{(2020)^2} 40.$$

$$C = 0.0314 \mu F$$

36. Ans: (b)

Sol:

$$\text{Ratio arms } \left(\frac{P}{Q} \right) = \frac{1000}{100} = 10 \Omega$$

Standard resistance arms $S_1 = 1000, S_2 = 100, S_3 = 10, S_4 = 1 \Omega$

Bridge under balanced condition

$$\frac{R}{S} = \frac{P}{Q}$$

$$R = \left(\frac{P}{Q} \right) S_{\text{variable}}$$

$$\text{Unknown resistance } R_1 = 10 \times S_1$$

$$= 10 \times 1000 = 10000 \Omega$$

$$R_2 = 10 \times 100 = 1000 \Omega$$

$$R_3 = 10 \times 10 = 100 \Omega$$

$$R_4 = 10 \times 1 = 10 \Omega$$

The minimum value of unknown resistance is $R_4 = 10 \Omega$

The maximum value is obtained by adding '4' unknown values corresponding to each 'S'

$$R = 10000 + 1000 + 100 + 10$$


$$R = 11110 \Omega$$

40. Ans: (a)

Sol:

$$S = 0.5 \text{ M}\Omega$$

$$R_g = R_h = 10 \text{ K}\Omega$$

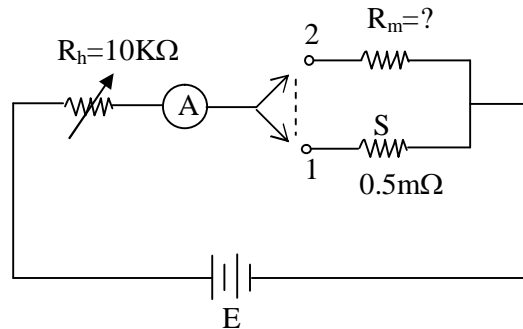

- (i) With standard resistor, 41 divisions
 No. of divisions \propto current flowing through the meter

$$41 \propto \frac{E}{0.5 \times 10^6 + 10 \times 10^3} \text{ ----- (i)} \quad [\because \text{switch at positions}]$$

- (ii) With unknown resistance, 51 divisions

$$51 \propto \frac{E}{R_m + 10K\Omega} \text{ ----- (ii)}$$

divide $\frac{(ii)}{(i)}$ them we get R_m

$$\frac{51}{41} = \frac{E}{R_m + 10 \times 10^3} \times \frac{0.5 \times 10^6 + 10 \times 10^3}{E}$$

$$R_m = 0.4 \text{ M}\Omega$$

41. Ans: (a)

Sol: Resistance of unknown resistance required for balance is

$$R = (P/Q)S = \left(\frac{1000}{1000}\right) \times 200 = 2000\Omega$$

In the actual bridge $R = 2005\Omega$

The deviation from balance condition is $\Delta R = 2005 - 2000$

$$\Delta R = 5\Omega$$

$$\text{Thevenine source generator emf } E_0 = E \left[\frac{R}{R+S} - \frac{P}{P+Q} \right]$$

$$= 5 \left[\frac{2005}{2005+200} - \frac{1000}{1000+100} \right]$$

$$= 1.0307 \times 10^{-3} \text{ V}$$

Internal resistance of bridge looking into terminals b & d

$$R_0 = \frac{R_s}{R+S} + \frac{PQ}{P+Q}$$


$$R_0 = \frac{2005 \times 200}{2005+200} + \frac{1000 \times 100}{1000+100} = 272.8\Omega$$

$$\text{Hence the current through the galvanometer } I_g = \frac{E_0}{R_0 + G}$$

$$I_g = \frac{1.0307 \times 10^{-3}}{272.8 + 100} = 2.77 \mu\text{A}$$

$$\text{Deflection of galvanometer } \theta = S_i \times I_g = 10 \times 2.77 = 27.7 \text{ mm}$$
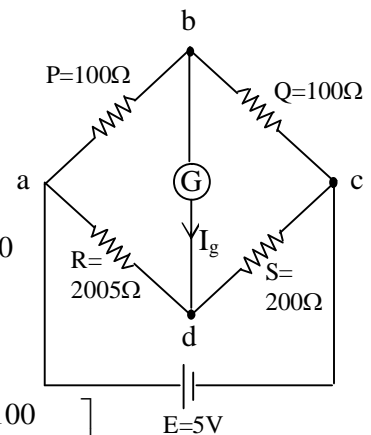
$$\text{Sensitivity of bridge } S_B = \frac{\theta}{\Delta R} = \frac{27.7}{5} = 5.54 \text{ mm}/\Omega$$



42. Ans: (a)

Sol: Each arm having a guaranteed accuracy error of $\pm 0.05\%$
 Standard arm has a guaranteed accuracy of $\pm 0.1\%$
 Ratio arms of both are set at 1000Ω
 Bridge is balanced with standard arm adjusted to determine the upper and lower limits of unknown resistance?

$$\begin{aligned} \text{Value of unknown resistance } R &= \left(\frac{P}{Q}\right) \times S \\ &= \frac{1000}{1000} \times 3154 \\ &= 3154\Omega \end{aligned}$$

% error in determination of R

$$\begin{aligned} R &= \frac{1000(\pm 0.05\%)}{1000(\pm 0.05\%)} \times 3154(\pm 0.1\%) \\ R &= 3154 \pm [0.05\% + 0.05\% + 0.1\%] \\ &= 3154 \pm 0.2\% \end{aligned}$$

The upper and lower limits of unknown resistance is 3091 to 3217 Ω

43. Ans: (a)

Sol: Given that
 $P = 1k\Omega$, $R = 1k\Omega$
 $S = 5k\Omega$, $G = 100\Omega$
 Thevenin's voltage $E_0 = 24mV$

$$I_g = 13.6\mu A$$

From circuit find thevenin equivalent circuit.

$$R_0 = \frac{RS}{R+S} + \frac{PQ}{P+Q}$$

$$I_0 = \frac{E_0}{R_0 + G}$$




$$R_0 + G = \frac{24 \times 10^{-3}}{13.6 \times 10^{-6}} = 1764.70$$

$$R_0 = 1764.7 - 100 = 1665\Omega$$

$$R_0 = \frac{1000 \times 5000}{1000 + 5000} + \frac{1000 \times Q}{1000 + Q}$$

$$\frac{1000Q}{1000 + Q} = 8317$$

$$Q = 4.95k\Omega$$

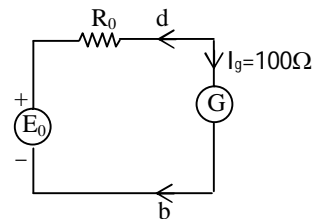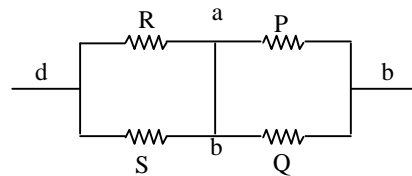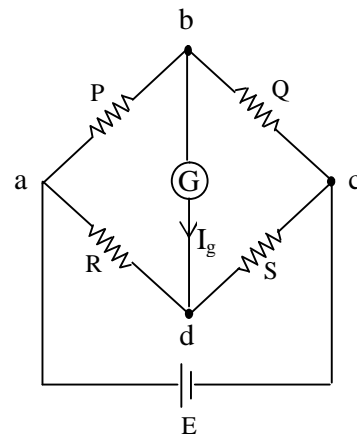

44. Ans: (a)

Sol:


$$S = 100.03 \times 10^6 \Omega$$

$$p = 100.31 \Omega \quad P = 100.24$$

$$q = 200 \Omega \quad Q = 200 \Omega$$

$$r = 100 \times 10^{-6} \Omega$$
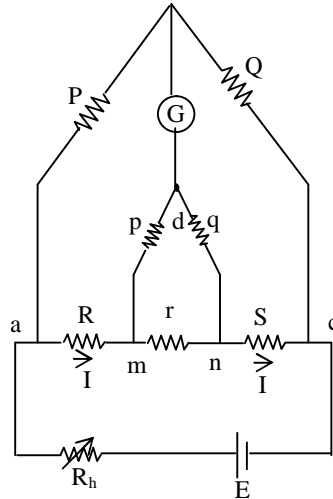
$$R = \frac{P}{Q} \cdot S + \frac{qr}{p+q+r} \left[\frac{P}{Q} - \frac{p}{q} \right]$$



$$R = \frac{100.24}{200} \times 100.03 \times 10^6 + \frac{200 \times 100 \times 10^{-6}}{100.31 + 200 + 100 \times 10^{-6}} \left[\frac{100.24}{200} - \frac{100.31}{200} \right]$$

$$R = 49.97 \times 10^6 \Omega$$

45. Ans:

Sol:

Given that

$$C = 600 \text{ pF}$$

$$V = 250 \text{ V} \quad v = 92 \text{ V}$$

$$\text{Insulation resistance } R = \frac{0.43 \times t}{C \log_{10} \left(\frac{V}{v} \right)}$$

$$R = \frac{0.434 \times 60}{600 \times 10^{-12} \times \log_{10} \left(\frac{250}{92} \right)}$$

$$R = 9.99 \times 10^{10}$$


$$R = 100 \times 10^9 \Omega$$

PREVIOUS IES SOLUTIONS

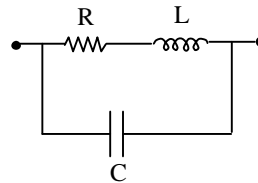01. Ans: (b)

Sol: The given circuit is
Equivalent impedance Z_{eq}

$$Z_1 = R + j\omega L, \quad Z_2 = \frac{1}{j\omega C}$$



$$Z_{eq} = \frac{Z_1 Z_2}{Z_1 + Z_2} \Rightarrow \frac{\left(\frac{1}{j\omega C}\right)(R + j\omega L)}{\left(R + j\omega L + \frac{1}{j\omega C}\right)}$$

$$Z = \frac{R + j\omega(L - \omega^2 L^2 C - CR^2)}{1 + \omega^2 C^2 R^2 - 2\omega^2 LC + \omega^4 L^2 C^2}$$

Effective reactance

$$X_{eff} = \frac{\omega\{L(1 - \omega^2 LC) - CR^2\}}{1 + \omega^2 C^2 R^2 - 2\omega^2 LC + \omega^4 L^2 C^2}$$

Since X_{eff} is small, we have; $\omega^2 LC \ll 1$
So, $\omega^2 LC$ can be neglected

$$\therefore X_{eff} = \frac{\omega(L - CR^2)}{1 + \omega^2 C(CR^2 - 2L)}$$

If the resistance is non-inductive, then

$$L - CR^2 = 0 \Rightarrow R = \sqrt{L/C}$$

02. Ans: (b)

Sol:

$$V_A = 10 \left[\frac{10}{20 + 10} \right]$$


$$V_A = 3.33 \text{ V}$$

$$V_B = 10 \left(\frac{20}{20 + 10} \right)$$

$$V_B = 6.66 \text{ V}$$

$$V_B - V_A = 6.66 - 3.33 = 3.33 \text{ V}$$

The reading of voltmeter is 3.33V

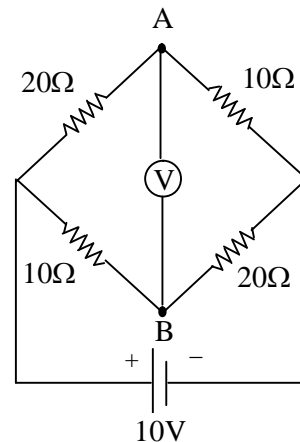

03. Ans: (a)

Sol:

For accuracy = 99%, voltage across the meter should be 49.5V

$$V_S = 50 \text{ V}, \quad V_m = 49.5 \text{ V}$$

$$V_m = V_S \times \frac{R}{100k + R}$$

$$\frac{R}{100k + R} = \frac{49.5}{50}$$

$$R = 0.99(100 \times 10^3 + R)$$

$$R = 99000 + 0.99R$$

$$0.01R = 9900$$

$$R = 990000$$

$$R = 10 \text{ M}\Omega$$

04. Ans: (b)

Sol:

Total current $I = I_1 + I_2$

$I_1 = 150 \pm 1A$ $I_2 = 250 \pm 2A$

Limits of error are given as standard

Deviations $d_1 = 1$ $d_2 = 2$ $n = 2$ $\sigma = 2$

$$\sigma = \sqrt{\frac{d_1^2 + d_2^2}{n - 1}}$$

$$\sigma = \sqrt{\frac{(1)^2 + (2)^2}{1}} = 2.236$$

$$\sigma = 2.24$$

$$I = 400 \pm 2.24$$

06. Ans: (a)

Sol:

$V = 10.14V,$ $I = 5.07mA$

$$\text{Resistance } R = \frac{V}{I} = \frac{10.14}{5.07 \times 10^{-3}} = 2k\Omega$$

07. Ans: (c)

Sol:

Given that $R_m = 100\Omega$ $I_{FSD} = 1mA$


From the circuit

$V = V_{se} + V_m$ $V = 10$

$V_{se} = V - V_m$

$1 \times 10^{-3}R = 10 - 1 \times 10^{-3} \times 100$

$R = 9900\Omega$

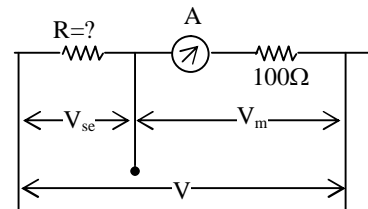

PREVIOUS GATE QUESTIONS

One Mark Questions:

2. GATE-EE -2001

Ans (a)

Sol:

$R_1 = 10\Omega \pm 5\%$ $R_2 = 5\Omega \pm 10\%$

R_1 Ranges $\rightarrow 10 \times \pm \frac{5}{100} \Rightarrow \pm 0.5 \rightarrow R_1 (10.5 - 9.5)$

R_2 Ranges $\rightarrow 5 \times \pm \frac{10}{100} \Rightarrow \pm 0.5 \rightarrow R_2 (5.5 - 4.5)$

For Parallel combination $\frac{10.5 \times 5.5}{10.5 + 5.5}$ and $\frac{9.5 \times 4.5}{9.5 + 4.5}$
 $= 3.60\Omega$ and 3.05Ω

Two Marks Questions:

03. GATE, IN – 1996

Ans : (b)

Sol : From the circuit the bridge is under balanced condition when

$$\frac{X_C}{R} = 1 \Rightarrow X_C = R \text{ then}$$

Voltmeter reading is

$$V = V_s \left[\frac{R}{R + R} \right]$$

$$V = 10 \left[\frac{R}{2R} \right] = 5V$$

04. GATE – IN – 2003

Ans : (a)

Sol : The output resistance obtained by using Thevenin's equivalent resistance by putting voltage source is zero

$$R_{12} = \frac{20 \times 10^3 \times 30 \times 10^3}{20 \times 10^3 + 30 \times 10^3} + \frac{25 \times 10^3 \times 25 \times 10^3}{25 \times 10^3 + 25 \times 10^3} = 24.5 K\Omega$$

06. GATE – IN – 2005

Ans:(d)


Sol: The ammeter resistance = 0.01Ω Voltmeter resistance = 2000Ω

True value of resistance

$$(R_L)_t = \frac{\text{voltmeter reading}}{\text{ammeter reading}}$$

$$(R_L)_t = \frac{180}{2} = 90\Omega$$
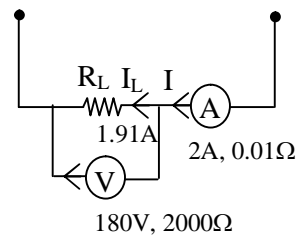
$$\begin{aligned} I_L &= I - \frac{V}{R_m} \\ &= 2 - \frac{180}{2000} \\ &= 1.91 \text{ Amp} \end{aligned}$$



From the circuit measured value

$$(R_L)_m = \frac{180}{1.91} = 94.24\Omega$$

$$\begin{aligned} \% \text{ error} &= \frac{(R_L)_m - (R_L)_t}{(R_L)_t} \times 100 \\ &= \frac{94.24 - 90}{90} \times 100 = 4.71\% \end{aligned}$$