

Bridge measurement of R, L, C

LEVEL-2:

01. Ans: (c)

Hint: Instrument sensitivity = $\frac{\text{Change in deflection}}{\text{Change in resistance}}$

$$= \frac{3}{6} \text{ mm}/\Omega$$

$$= 0.5 \text{ mm/ohm}$$

02. Ans: (d)

Hint: With R_x disconnected, the full scale current

$$I_m = \frac{E}{R_1 + R_m}$$

Given that the new current $I_{\text{New}} = SI_m \rightarrow (1)$

The New current can be obtained as

$$I_T = \frac{E}{R_1 + \frac{R_m R_x}{R_m + R_x}}$$

From current division rule,

$$I_{\text{New}} = \frac{E}{R_1 + \frac{R_m R_x}{R_m + R_x}} \left[\frac{R_x}{R_m + R_x} \right]$$

$$= \frac{ER_x}{R_1(R_m + R_x) + R_m R_x}$$

From (1)

$$\frac{ER_x}{R_1(R_m + R_x) + R_m R_x} = \frac{R_x}{R_x + R_p} \left[\frac{E}{R_1 + R_m} \right]$$


$$R_x(R_1 + R_m) + R_p(R_1 + R_m) = R_1 R_m + R_1 R_x + R_m R_x$$

$$R_p = \frac{R_1 R_m}{R_1 + R_m}$$

03. Ans: (d)

Hint: Given data $Z_1 = 450 \Omega$

$$Z_2 = (300 - j600)\Omega$$

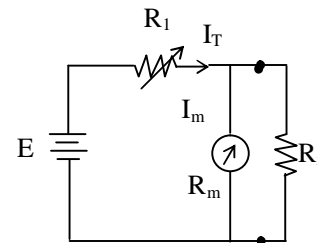

$$Z_3 = (200 + j 100)\Omega$$

Under balance $Z_1 Z_3 = Z_2 Z_4$

$$450 (200 + j100) = (300 - j600)Z_4$$

$$\frac{450 \times (200 + j100)(300 + j600)}{(300)^2 + (600)^2} = Z_4$$

$$\frac{450 \times 10^4 (2 + j)(3 + 6j)}{450 \times 10^3} = Z_4$$

$$10[6 + 15j - 6] = Z_4$$

$$\therefore Z_4 = (0 + j150)\Omega$$

04. Ans: (d)

Hint: The given bridge is wein's bridge.

under balance

$$R_4 \left[R_1 \frac{1}{j\omega C_1} \right] = R_2 \left[\frac{R_3}{j\omega C_3 R_3 + 1} \right]$$

$$R_1 R_4 (j\omega C_3 R_3 + 1) + \frac{R_4}{j\omega C_1} [j\omega C_3 R_3 + 1] = R_2 R_3$$

Compare real and imaginary terms

$$\omega R_1 R_4 C_3 R_3 - \frac{R_4}{\omega C_1} = 0$$

$$\omega = \frac{1}{\sqrt{C_1 C_3 R_1 R_3}}$$

If $R_1 = R_3 = R$ and $C_1 = C_3 = C$

$$\omega = \frac{1}{RC}$$

And real part,

$$R_1 R_4 + \frac{R_4 C_3 R_3}{C_1} = R_2 R_3$$

$$\Rightarrow R_4 \left[R_1 + \frac{C_3 R_3}{C_1} \right] = R_2 R_3$$

If $R_1 = R_3$ and $C_1 = C_3$

$$R_4 [R_3 + R_3] = R_2 R_3$$

$$\Rightarrow R_2 = 2R_4$$

05. Ans: (a)

Hint: under balanced condition,

$$Z_x \left[\frac{4000}{j\omega 0.05\mu \times 4000 + 1} \right] = 2000 \times 750$$

$$Z_x = \frac{750}{2} (1 + j\omega \times 10^{-3})$$

$$R_x + j\omega L_x = 375 + j75 \times 10^{-3} \omega$$

Compare real and imaginary terms

$$R_x = 375\Omega \text{ and } L_x = 75\text{mH}$$


06. Ans: (d)

Hint: The given bridge is unbalanced bridge

$$V_b = 10 \times \frac{10}{30} = 3.33 \text{ V}$$

$$V_a = 20 \times \frac{10}{30} = 6.66 \text{ V}$$
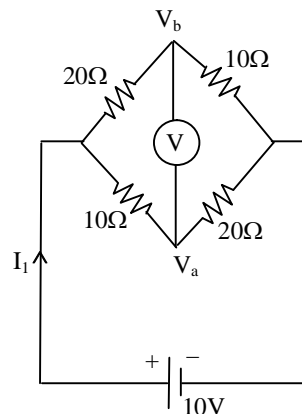
$$\begin{aligned} \text{Voltmeter reading} &= V_a - V_b \\ &= 6.66 - 3.33 \\ &= 3.33 \text{ V} \end{aligned}$$



10. Ans: (b)

$$\text{Given } \frac{X_c}{R} = 1$$

$$\text{Volt meter reading} = V_{ab} = V_a - V_b$$

$$V_a = \frac{10 \times R}{R + R} = 5\text{V}$$

$$V_b = \frac{10 \times X_c}{X_c + R} = \frac{10}{1 + \frac{R}{X_c}} = \frac{10}{2} = 5\text{V}$$

$$\therefore \text{ Voltmeter reading } V_{ab} = 0\text{V}$$

11. Ans: (a)

$$\text{Sol: } V_{ab} = V_a - V_b = \frac{30 \times 10}{30} - \frac{30 \times 2}{10} = 4$$

$$\text{Energy stored in capacitor} = \frac{1}{2} C V_{ab}^2 = \frac{1}{2} \times 1 \times 10^{-6} \times 4^2 = 8\mu\text{J}$$

12. Ans: (d)

Sol : Take $I = I_1 + I_2$
 $I_1 =$ inner loop current and $I_2 =$ outer loop current
 from KVL.

$$-V_s + 2 + 2 \times 10^3 I_2 = 0 \rightarrow (1)$$

$$\text{and } -V_s + 5 \times 10^3 I_1 = 0 \rightarrow (2)$$

Given $V_0 = 0$, therefore voltage across $4K\Omega$ is equal to voltage across $2 K\Omega$.

$$4 \times 10^3 I_1 = 2 \times 10^3 I_2$$

$$I_2 = 2I_1 \rightarrow (3)$$

By solving (1), (2) and (3)

$$I_1 = 2\text{mA}, I_2 = 4\text{mA}$$

$$\therefore I = 6\text{mA}$$

13. Ans: (a)

Sol :

$$\text{Given } V_1 = \sqrt{2} \cos 1000t \quad V$$

$$V_2 = 2 \cos(1000 + 45^\circ) \text{ and } V_d = 0$$

V_1 is the voltage across the resistor $R = 100\Omega$, since $V_d = 0$

$$\therefore I_2 = \frac{V_1}{R} = \frac{\sqrt{2} \cos 1000t}{100}$$

V_2 is the voltage across the impedance Z_x .

$$V_2 = 2 \cos(1000t + 45^\circ)$$

$$I_2 = \sqrt{2} \times 10^{-2} \cos 1000t$$

Here V_2 leads the current I_2 with the phase angle 45° .

Hence the element is inductor with some resistance.

$$\begin{aligned} \text{Now } R &= \frac{V_2 \cos 45^\circ}{I_2} \\ &= \frac{2}{\sqrt{2} \times 10^{-2}} \times \frac{1}{\sqrt{2}} = 100 \Omega \end{aligned}$$

$$\text{and } X_L = \frac{V_2 \sin 45^\circ}{I_2} = \frac{2}{\sqrt{2} \times 10^{-2}} \times \frac{1}{\sqrt{2}}$$

$$X_L = 100\Omega \text{ and } L = \frac{100}{1000} = 100 \text{ mH}$$

14. Ans: (c)

Sol :

$$\text{The voltage across } R_2 \text{ is } = \frac{ER_2}{R_1 + R_2} = \frac{E}{2}$$

$$\text{Therefore voltage across } R_1 \text{ is also } \frac{E}{2}.$$

$$\text{Now } \frac{E}{2} = IR_3 + V$$

$$\therefore I = \frac{E - 2V}{2R}$$

$$\text{and } \frac{E}{2} = IR_4$$

$$\frac{E}{2} = \left(\frac{E - 2V}{2R} \right) (R + \Delta R)$$

$$R + \Delta R = \frac{ER}{E - 2V}$$

$$\therefore \Delta R = \frac{2VR}{E - 2V}$$

15. Ans: (b)

Sol :

Under balanced condition

$$(X_C || 10K\Omega)Z = 500 \times 1K\Omega$$

$$\frac{10^4 Z}{1 + j\omega 100 \times 10^{-9} \times 10^4} = 5 \times 10^5$$

$$Z = 50[1 + j\omega 50 \times 10^{-3}]$$

$$= 50 + j\omega 50 \times 10^{-3}$$

16.

Ans: (d)

Sol: Voltage across the 500kΩ resistor is exactly 10V


Sensitivity of voltmeter 20kΩ/V

The readings indicated on its 50V and 5V range?

Voltage across V_{AB} by voltage division rule

$$V_{AB} = \frac{500}{500 + 500} \times 20$$

$$V_{AB} = 10V$$

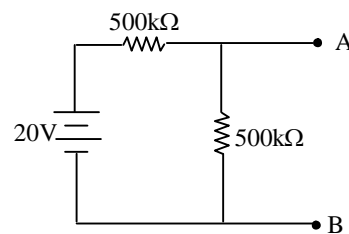

Reading indicated on 50V range is

$$R_m = S \times \text{voltage range}$$

$$R_m = 20 \times 10^3 \times 50 = 1000 \text{ k}\Omega$$

R_m connected across 'AB'

$$R_{eq} = \frac{500 \times 1000}{500 + 1000} = 333.3\Omega$$

$$V = 20 \times \frac{333.3}{500 + 333.3} = 8V$$


Reading indicated on '5V' range is

$$R_m = S \times \text{voltage range}$$

$$R_m = 20 \times 10^3 \times 5 = 100k\Omega$$

$$R_{eq} = \frac{500 \times 100}{500 + 100} = 83.33\Omega$$
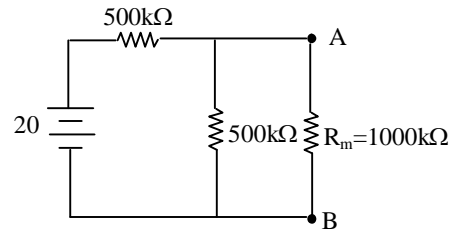
$$V = 20 \times \frac{83.33}{500 + 83.33} = 2.86V$$



17. Ans (a)

Sol: $41 = E / (0.5M\Omega + 10K\Omega)$ and

$$51 = E / (R_m + 10K\Omega)$$

Take ratio then R_m value is $0.4M\Omega$

18.

Ans: (a)

Sol: Each arm having a guaranteed accuracy error of $\pm 0.5\%$

Standard arm has a guaranteed accuracy of $\pm 1\%$

Ratio arms of are both set at 1000Ω

Bridge is balanced with standard arm adjusted to determine the upper and lower limits of unknown resistance?

$$\text{Value of unknown resistance } R = \left(\frac{P}{Q}\right) \times S$$

$$= \frac{1000}{1000} \times 3154$$

$$= 3154\Omega$$

% error in determination of R

$$R = \frac{1000(\pm 0.5\%)}{1000(\pm 0.5\%)} \times 3154(\pm 1\%)$$

$$R = 3154 \pm [0.5\% + 0.5\% + 1\%]$$

$$= 3154 \pm 2\%$$

The upper and lower limits of unknown resistance is 3091 to 3217 Ω

19.

Ans: (a)


Sol: Given that

$$P = 1k\Omega, \quad R = 1k\Omega$$

$$S = 5k\Omega, \quad G = 100\Omega$$

Thevenine voltage $E_0 = 24mV$

$$I_g = 13.6\mu A$$

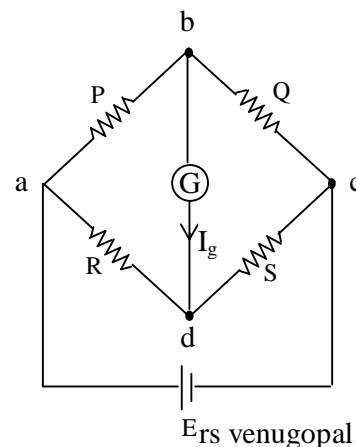

All the best

Ers venugopal

From circuit find thevenin equivalent circuit.

$$R_0 = \frac{RS}{R+S} + \frac{PQ}{P+Q}$$

$$I_0 = \frac{E_0}{R_0 + G}$$


$$R_0 + G = \frac{24 \times 10^{-3}}{13.6 \times 10^{-6}} = 1764.70$$

$$R_0 = 1764.7 - 100 = 1665 \Omega$$

$$R_0 = \frac{1000 \times 5000}{1000 + 5000} + \frac{1000 \times Q}{1000 + Q}$$

$$\frac{1000Q}{1000 + Q} = 8317$$

$$Q = 4.95 \text{ k}\Omega$$

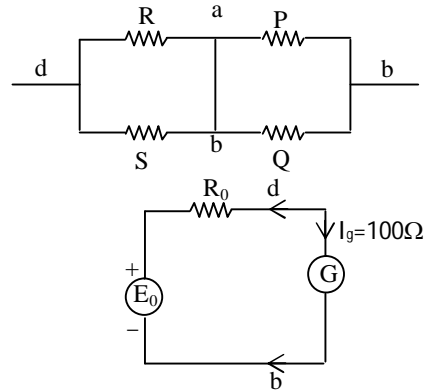

20.

Ans: (a)


Sol: $S = 100.03 \times 10^6 \Omega$

$$p = 100.31 \Omega \quad P = 100.24$$

$$q = 200 \Omega \quad Q = 200 \Omega$$

$$r = 100 \times 10^{-6} \Omega$$
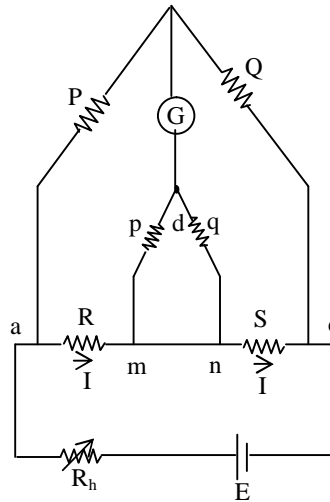
$$R = \frac{P}{Q} \cdot S + \frac{qr}{p+q+r} \left[\frac{P}{Q} - \frac{p}{q} \right]$$



$$R = \frac{100.24}{200} \times 100.03 \times 10^{-6} + \frac{200 \times 100 \times 10^{-6}}{100.31 + 200 + 100 \times 10^{-6}} \left[\frac{100.24}{200} - \frac{100.31}{200} \right]$$

$$R = 49.97 \times 10^{-6} \Omega$$

21.

Ans: Given that

Sol: $C = 600\text{pF}$ $V = 250\text{V}$ $v = 92\text{V}$

$$\text{Insulation resistance } R = \frac{0.43 \times t}{C \log_{10} \left(\frac{V}{v} \right)}$$

$$R = \frac{0.434 \times 60}{600 \times 10^{-12} \times \log_{10} \left(\frac{250}{92} \right)}$$

$$R = 9.99 \times 10^{10}$$

$$R = 100 \times 10^9 \Omega$$