

CHAPTER-5

POTENTIOMETERS & Instrument Transformer

10. Ans: (b)

Sol: Measurement of reactance of a coil by using

Polar type ac potentiometer

Given that $I = 12 \angle 13.8^\circ$, $V = 27.8 \angle 29.7^\circ$

$$Z = \frac{V}{I} \angle \theta_C - \theta_S$$

Reactance $X = Z \sin(\theta_C - \theta_S)$, Where $\theta_C = 29.7^\circ$, $\theta_S = 13.8^\circ$

$$Z = \frac{27.8}{12} \angle 29.7 - 13.8$$

$$Z = 2.31 \angle 15.9^\circ$$

Reactance $X = 2.31 \sin(29.7 - 13.8)$

$$X = 0.632 \Omega$$

11. Ans: (b)

Sol: The voltage read by potentiometer is 1.2V

The voltmeter reads 0.6V with $20,000 \Omega/V$ on 5V range

Input resistance $R_V = S_{DC} \times \text{voltage}$

$$R_V = 20,000 \times 5$$

$$R_V = 1,00,000 \Omega$$

12. Ans: (a)

Sol: Given that

Working current $I_w = 10 \text{mA}$

Dial resistor having 15 steps of 10Ω each

i.e. = 150Ω

slide wire resistance is = 10Ω

Total resistance = $150 + 10 = 160 \Omega$

Range of voltage = $I_w \times R_{\text{total}}$

$$= 10 \times 10^{-3} \times 160 = 1.6 \text{V}$$

Resolution: slide wire provide with 100 divisions and since the total resistance of slide wire (10Ω) corresponding to a voltage drop of ($10 \text{mA} \times 10 \Omega = 0.1 \text{V}$), each division of

slide wire corresponds to = $\frac{0.1}{100} = 0.001$

With certainly the reading upto $\frac{1}{5}$ of scale division

Then resolution is $\frac{1}{5} \times 0.001 = 0.2 \text{mV}$

13. Ans: (a)


Sol: For the voltage division $\left(\frac{V_0}{V_{in}}\right)$ is independent of frequency, the impedance ratio should also be independent of frequency

$$\begin{aligned} \frac{Z_1}{Z_2} &= \frac{R_1 \frac{1}{j\omega C_1}}{R_1 + \frac{1}{j\omega C_1}} \times \frac{R_2 + \frac{1}{j\omega C_2}}{R_2 \times \frac{1}{j\omega C_2}} \\ &= \frac{R_1}{1 + j\omega C_1 R_1} \times \frac{1 + j\omega C_2 R_2}{R_2} \\ &= \frac{R_1}{R_2} \cdot \frac{1 + j\omega C_2 R_2}{1 + j\omega C_1 R_1} \Rightarrow C_2 R_2 = C_1 R_1 \\ C_1 &= \frac{C_1 R_1}{R_2} = \frac{1 \times 10^{-6} \times 10}{1 \times 10^3} = 10 \mu\text{F} \end{aligned}$$

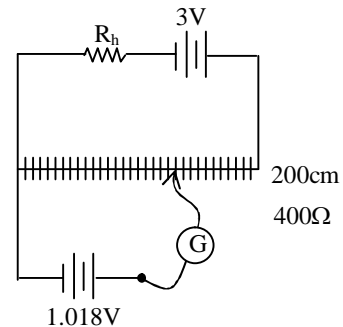15. Ans: (a)

Sol: Given that,

Working battery is 3V
 Slide wire is 400Ω
 Length L = 200 cm
 Let 1cm = 2Ω
 Standard cell voltage is 1.018V
 Sliding contact at 101.8cm
 Sliding contact resistance = 2 × 101.8 = 203.6Ω
 Current through the slide wire is



$$\begin{aligned} 1.018\text{V} &= I_w \times 203.6 \\ I_w &= 5 \times 10^{-3} \\ I_w &= \frac{E}{R_h + 400} \Rightarrow R_h + 400 = \frac{3}{5 \times 10^{-3}} = 600 \\ R_h &= 600 - 400 = 200\Omega \end{aligned}$$

16. Ans: (a)

Sol: Resistance of unknown resistor $R = \frac{V_R}{V_S} S = \frac{0.4221}{1.0235} \times 0.1 = 0.041208\Omega$

Current through the resistor = $\frac{V_S}{S} = \frac{1.0235}{0.1} = 10.235\text{A}$

Power loss in unknown resistance = $I^2 R = (10.235)^2 \times 0.041208 = 4.316\text{W}$

17. Ans: (b)

Sol: Voltage drop per unit length = $\frac{1.45}{50} = 0.029\text{V/cm}$

Voltage drop across 75 cm length = $0.029 \times 75 = 2.175\text{V}$

Current through resistor = $\frac{2.175}{0.1} = 21.75\text{A}$

27. Ans: (a)

Sol: Given that

$$f = 50\text{Hz}, \quad N_2 = 500$$

$$I_s = 5\text{A}, \quad R = 1\Omega$$

Magnetizing turns = 200AT

Bar primary = 1turn

$$I_0 = 200 \times 1$$

$$I_0 = 200\text{A}$$

About α, δ nothing is mentioned neglect

$$\text{Phase angle error } \theta = \frac{I_0 \cos(\alpha + \delta)}{nI_s} \quad \text{rad}$$

$$\theta = \frac{I_0}{nI_s} \times \frac{180}{\pi} \quad \text{degrees}$$

$$\theta = \frac{200 \times 180}{500 \times \pi \times 5} = 4.6 \text{ degrees}$$

28. Ans: b

Sol: The flux in the CT core is

$$\text{emf } E_2 = 4.44 \times f \times \phi_m \times N_2$$

$$\phi_m = \frac{E_2}{4.44 \times f \times N_2} = \frac{5 \times 1}{4.44 \times 50 \times 500} = 45 \mu\text{Wb}$$

29. Ans: (a)

Sol: Under balanced condition

$$I_w = \frac{E}{R_h + R_{\text{slide}}}$$

$$= \frac{3.2}{200 + 200 + 2800} = 1 \times 10^{-3} \text{ A}$$

Then,

$$E_x = I_w \times 200 = 2 \times 10^{-3} \times 200 = 200\text{mV}$$

30. Ans:(c)

Sol:

Before reversing of V_x

$$I = 0.2 \times 10^{-3} \text{ A}$$

$$-V_x - IR_m - 1\text{V} = 0$$

$$V_x = -(0.2 \times 10^{-3} \times R - 1) \text{-----(1)}$$


After reversing of V_x

$$I = 3.8 \times 10^{-3} \text{ A}$$

$$V_x = 3.8 \times 10^{-3} \times R - 1 \text{----- (2)}$$

Equating (1) & (2)
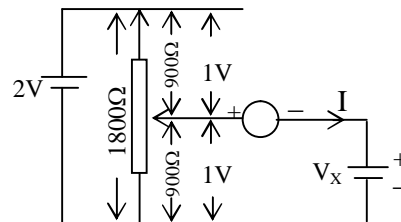
$$-[0.2 \times 10^{-3} R - 1] = [3.8 \times 10^{-3} \times R - 1]$$



$$R = \frac{2}{4 \times 10^{-3}} = 500\Omega$$

From (2) $V_x = 3.8 \times 10^{-3} \times 500 - 1$
 $V_x = 0.9V$

31. Ans:(a)

Sol: from the circuit

$$V = -\frac{R_f}{R} \times V_i = -\frac{15 \times 10^3}{10 \times 10^3} \times 1V = -1.5V$$

32. Ans(a)

Sol:

E_x balances at 10 m 18cm

i.e 10.18m = 10.18Ω


$E_x = I_w \times$ resistance of slid wire at balance

$$I_w = \frac{1.018}{10.18} = 0.1A$$

$$I_w = \frac{E}{R_{sc} + 11}$$

$$R_{se} + 11 = \frac{2}{0.1}$$

$$R_{se} = 20 - 11 = 9\Omega$$

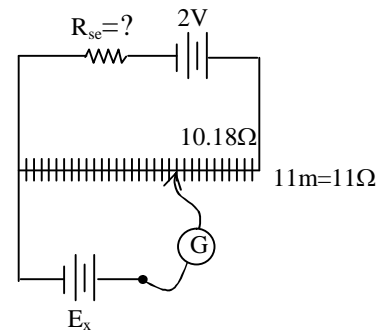

33. Ans(d)

$I_g = 10\mu A, E_u = ?$

Write KVL for loop 1

$$-1.6 + (100 + 500) I_w + 1000(I_w + I_g) = 0$$


$$1600I_w + 1000I_g = 1.6$$

$$I_w = \frac{1.6 - 10 \times 10^{-3}}{1600} = 9.9375 \times 10^{-4}A.$$

Write KVL for loop 2

$$-E_u + 100 \times 10 \times 10^{-6} + 1000(10 \times 10^{-6} + 9.9375 \times 10^{-4}) = 0$$

$$E_u = 1.00475$$

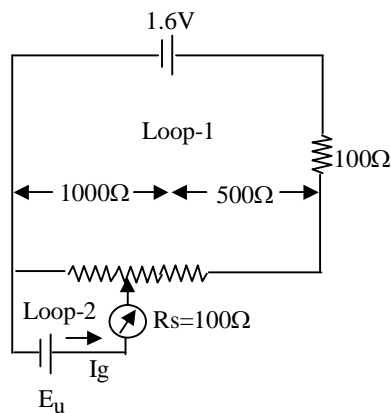


34. Ans: (b)

Sol: Given data $I_w = 10\text{mA}$, $R_g + R_1 = 100\Omega$

The unknown resistance 'X' can be obtained as

$$I_w = \frac{3}{X + 250}$$
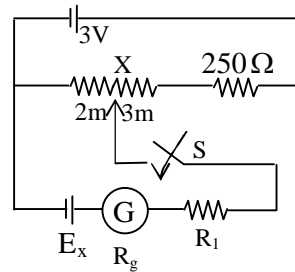
$$X = \frac{3}{10 \times 10^{-3}} - 250 = 50\Omega$$



The sliding contact differentiates the unknown resistance into 20Ω and 30Ω .

Now find out true E_x value

$$E_x = \text{drop across } 20\Omega \text{ resistor} = 20 \times 10 \times 10^{-3} = 0.2 \text{ V}$$

But the galvanometer can only detect current greater than $10\mu\text{A}$.

Now the error is nothing but voltage drop across $R_g + R_1$.

$$I_g (R_g + R_1) = 10 \times 10^{-6} (100) = 1\text{mV}$$

$$\text{percentage error} = \frac{1 \times 10^{-3}}{0.2} \times 100 = 0.5$$

37. Ans: (a)

Sol :

$$\text{Sol: Nominal ratio } K_n = \frac{200}{1} = 200$$

Since no turns compensation nominal ratio = turns ratio (n)

$$\text{Actual ratio } R = \frac{I_p}{I_s} = \frac{100}{0.495} = 202.02$$

$$\begin{aligned} \text{Ratio error} &= \frac{K_n - R}{R} \times 100 \\ &= \frac{200 - 202.02}{202.02} \times 100 \\ &= -0.99\% \end{aligned}$$

$$\approx -1.0\%$$