

CHAPTER-5

BRIDGE MEASUREMENT, MEASUREMENT OF INDUCTANCE & CAPACITANCE

Two Marks Questions

33. Ans: (a)

Sol: Given data

$$r_2 = 32.7\Omega$$

$$L_2 = 47.8\text{mH}$$

$$R = 1.36\Omega$$

Under Balance conditions

$$Z_1 Z_4 = Z_2 Z_3$$

$$Z_1 = R_1 + r_1 + j\omega L_1$$

$$Z_2 = 100\Omega$$

$$Z_4 = 100\Omega$$

$$Z_3 = r_2 + j\omega L_2$$

$$(R_1 + r_1 + j\omega L_1) \times 100 = 100(r_2 + j\omega L_2)$$

Compare real part & img part

$$R_1 + r_1 = r_2$$

$$j\omega L_1 = j\omega L_2$$

$$L_1 = L_2$$

$$1.36 + r_1 = 32.7 \quad L_1 = 47.8\text{mH}$$

$$r_1 = 31.34\Omega$$

34. Ans: (b)

Sol: Given data

$$R_2 = 400\Omega \quad R_3 = 600\Omega$$

$$R_4 = 1000\Omega \quad C_4 = 0.5\mu\text{F}$$

$$f = 1000\text{HZ}$$

$$Z_1 Z_4 = Z_2 Z_3$$

$$Z_1 = Y_4 Z_2 Z_3$$

$$Z_2 = R_2, \quad Z_3 = R_3, \quad Y_4 = \frac{1}{R_4} + j\omega C_4$$

$$Z_1 = R_1 + j\omega L_1$$

$$(R_1 + j\omega L_1) = \left(\frac{1}{R_4} + j\omega C_4\right) R_2 R_3$$


$$R_1 + j\omega L_1 = \frac{R_2 R_3}{R_4} + j\omega C_4 R_2 R_3$$

Compare Real parts & img parts

$$R_1 = \frac{R_2 R_3}{R_4} \quad \omega L_1 = \omega C_4 R_2 R_3$$

$$L_1 = C_4 R_2 R_3$$
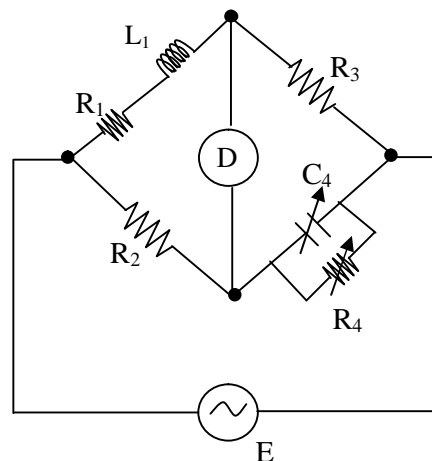
$$R_1 = \frac{400 \times 600}{1000} \quad L_1 = 0.5 \times 10^{-6} \times 400 \times 600$$



$$R_1 = 240\Omega \quad L_1 = 0.12H$$

$$Q = \frac{\omega L_1}{R_1} = \frac{2\pi \times 1000 \times 0.12}{240} = 3.14$$

35. Ans: (d)


Sol: Voltmeter reading

$$V = V_{ab} - V_{ad}$$

$$= I_1 \times 20 - I_2 \times 10$$

$$= \frac{10}{20 + 10} \times 20 - \frac{10 \times 10}{10 + 20}$$
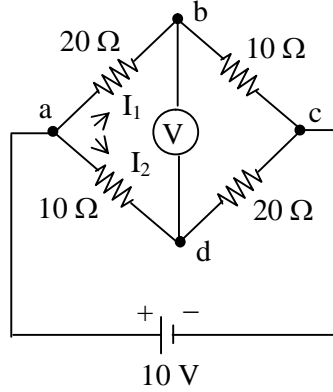
$$V = \frac{10}{30} (20 - 10) = \frac{100}{30} = 3.33V$$



37. Ans: (a)

Sol: For the $Z_1 = 200\angle 30^\circ$ $Z_2 = 150\angle 0^\circ$ $Z_3 = 230\Omega\angle -40^\circ$


Under balanced condition

$$Z_1 Z_4 = Z_2 Z_3$$

$$200\angle 30^\circ Z_4 = 150 \times 230\angle 0^\circ - 40^\circ$$

$$Z_4 = \frac{150 \times 230}{200} \angle -70^\circ$$

$$= 172.5 \angle -70^\circ$$

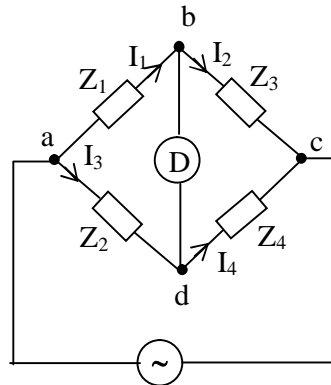

38. Ans: (c)

Sol: ab R in series with inductance


ad → pure resistance

bc → pure resistance

what about cd

cd should consists of a variable resistance in series or parallel with a variable capacitance.

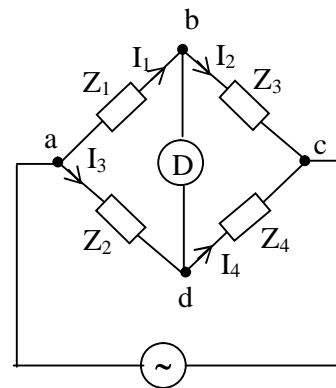
Parallel → Maxwell Inductance – capacitance bridge



Previous IES question

02. Ans: (a)

Sol:

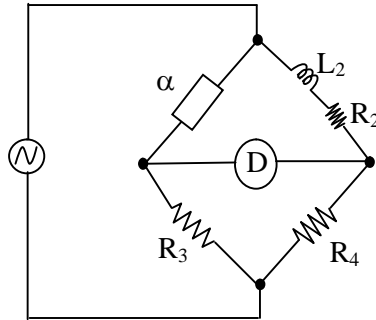

X = self inductance having resistance, Maxwell's inductance bridge

03. Ans: (b)

Sol:
$$Q = \frac{\omega L_1}{R_1} = \frac{\omega C_4 R_2 R_3}{R_2 R_3 / R_4} = \omega C_4 R_4 = \omega CR$$

Take Maxwell Inductance – capacitance Bridge


04. Ans: (b)

Sol:
$$Z_1 = 100 \angle 30^\circ$$

$$Z_2 = 150 \angle 0^\circ$$

$$Z_3 = 250 \angle -40^\circ$$

$$Z_4 = ?$$

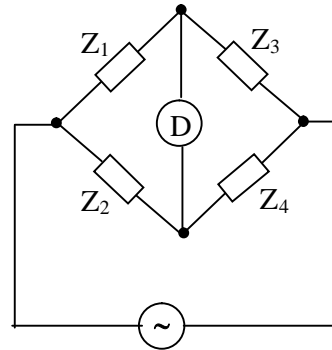

Under balance condition

$$Z_1 Z_4 = Z_2 Z_3$$


$$100 \angle 30^\circ Z_4 = 150 \angle 0^\circ \times 250 \angle -40^\circ$$

$$Z_4 = 375 \angle -40^\circ - 30^\circ$$

$$Z_4 = 375 \angle -70^\circ \Omega$$

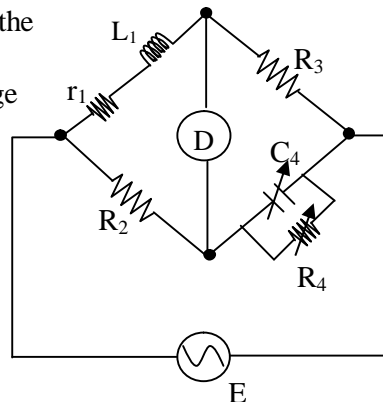06. Ans: (c)

Sol: Given data $R_1 = R_2 R_3 / R_4$ $L_1 = R_2 R_3 C_4$
 R_1 & L_1 are unknown quantities what are the variable parameters i.e. C_4 & R_4
 eg: Maxwell Inductance – capacitance bridge




07. Ans: (c)

Sol: Under balance condition

$$200 \angle 30^\circ \times Z_4 = 250 \angle -40^\circ \times 150 \angle 0^\circ$$

$$= 187.5 \angle -70^\circ$$

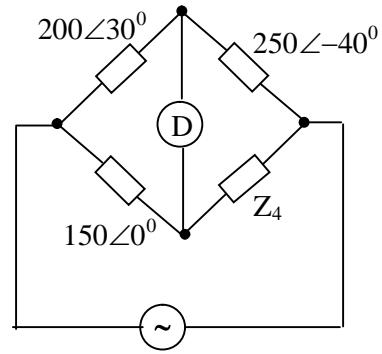

14. Ans: (a)

Sol: $Z_1 = Z_2 Z_3 / Z_4$

$$Z_2 = \pm 1\% \quad Z_3 = \pm 1\% \quad Z_4 = \pm 3\%$$

$$\text{Uncertainty} = \sqrt{(\pm 1)^2 + (\pm 1)^2 + (\pm 3)^2}$$

$$= \sqrt{1 + 1 + 9} = \sqrt{11} \%$$

15. Ans: (b)

Sol: Balanced condition

$$\left(R_1 + \frac{1}{j\omega C_1} \right) R_s = (R + j\omega L) \frac{1}{j\omega C_s}$$

$$R_1 R_s - \frac{jR_s}{\omega C_1} = \frac{-jR}{\omega C_s} + \frac{\omega L}{\omega C_s}$$


Compare real parts & img parts

$$R_1 R_s = \frac{L}{C_s}$$

$$R_1 = \frac{L}{R_s C_s} \quad L = R_1 R_s C_s$$

$$\frac{R_s}{\omega C_1} = \frac{R}{\omega C_s}$$

$$R = \frac{R_s C_s}{C_1}$$

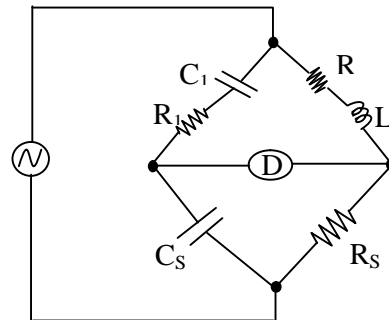

16. Ans: (a)

Sol: $C_s = 0.5 \mu F$

$R_s = 1000 \Omega$


Under balanced condition similar to Maxwell's Inductance capacitance bridge

$$L_x = C_s R_2 R_3 \quad R_x = \frac{R_2 R_3}{R_s}$$

$$= 0.5 \times 10^{-6} \times 1000 \times 1000$$

$$= \frac{1000 \times 1000}{1000} = 1000 \Omega$$

$$= 0.5 \text{ H}$$

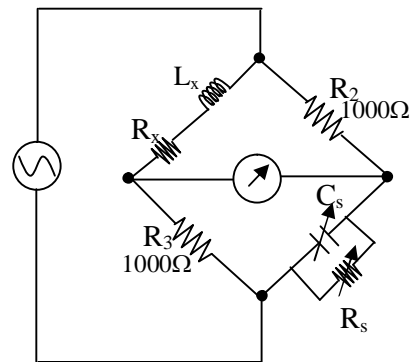

20. Ans: (d)


Sol: At balance

$$\left(\frac{1}{j\omega c_b}\right)(R_x + j\omega L_x) = \left(R_c - \frac{j}{\omega c_c}\right) R_a$$

$$\frac{-R_x j}{\omega c_b} + \frac{L_x}{c_b} = R_c R_a - \frac{j R_a}{\omega c_c}$$

$$\frac{R_x}{\omega c_b} = \frac{R_a}{\omega c_c} \Rightarrow \frac{R_a c_b}{c_c}$$

$$L_x = R_c R_a R_b$$

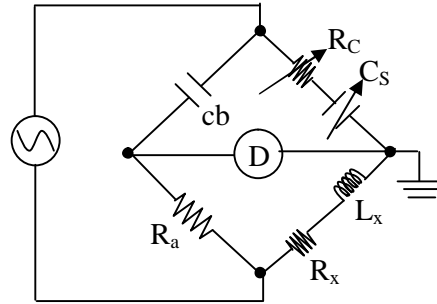

22. Ans: (a)

Sol: $Z_1 Z_x = Z_2 Z_3$ $Z_x = Y_1 Z_2 Z_3$

$$Y_1 = \frac{1}{R_1} + j\omega c_1$$

$$z_2 = R_2 \quad z_3 = \frac{-j}{\omega c_3}, \quad z_4 = R_x \frac{j}{\omega c_x}$$

$$\left(R_x - \frac{j}{\omega c_x}\right) = R_2 \frac{-j}{\omega c_3} \times \left(\frac{1}{R_1} + j\omega c_1\right)$$


$$R_x - \frac{j}{\omega c_x} = \frac{-R_2 j}{\omega c_3 R_1} + \frac{\omega c_1 R_1}{\omega c_3}$$

Compare real part & img part

$$R_x = \frac{\omega c_1 R_2}{\omega c_3} = \frac{c_1 R_2}{c_3}$$

$$R_x = \frac{c_1 R_2}{c_3} \Rightarrow \frac{1}{\omega c_x} = \frac{+R_2}{\omega c_3 R_1}$$

$$c_x = \frac{c_3 R_1}{R_2}$$

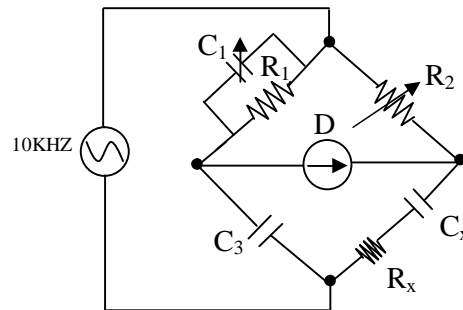

23. Ans: (b)

Sol: $f = \frac{1}{2\pi\sqrt{L(c + c_s)}}$

$c_s \rightarrow$ self - capacitance

$$500 \times 10^3 = \frac{1}{2\pi\sqrt{L(c + 36 \times 10^{-12})}} \dots\dots\dots (1)$$

$$250 \times 10^3 = \frac{1}{2\pi\sqrt{L(c + 160 \times 10^{-12})}} \dots\dots\dots (2)$$

Dividing equation (1) by equation (2)

$$2 = \sqrt{\frac{c + 160 \times 10^{-12}}{c + 36 \times 10^{-12}}}$$

$$4 = \frac{c + 160 \times 10^{-12}}{c + 36 \times 10^{-12}}$$

$$4c + 144 \times 10^{-12} = c + 160 \times 10^{-12}$$

$$3c = 16 \times 10^{-12}$$

$$c = 5.33 \text{ pF}$$

24. Ans: (c)


Sol: $c_1 = 150 \pm 2.4 \text{ } \mu\text{F}$ $c_2 = 120 \pm 1.5 \text{ } \mu\text{F}$

$$\begin{aligned} \text{parallel } c_{\text{eq}} &= c_1 + c_2 \\ &= 150 \pm 2.4 + 120 \pm 1.5 \\ &= 270 \pm 3.9 \end{aligned}$$

Limiting error = 3.9 μF

25. Ans: (b)

Sol:

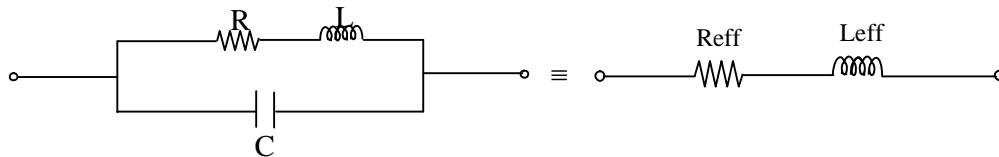

$$Z = \frac{\left(\frac{1}{j\omega c}\right)(R + j\omega L)}{R + j\omega L + \frac{1}{j\omega c}}$$

$$= \frac{R + j\omega(L - \omega^2 L^2 c - cR^2)}{1 + \omega^2 c^2 R^2 - 2\omega^2 Lc + \omega^4 L^2 c^2}$$

Since these inductance & capacitance of a resistor are very small is value therefore $\omega^2 Lc \ll 1$ & $\omega^4 L^2 c^2 \ll 1$

$$Z = \frac{R + j\omega(L - cR^2)}{1 + \omega^2 c(cR^2 - 2L)}$$

effective inductive

$$L_{\text{eff}} = \frac{L - cR^2}{1 + \omega^2 c(cR^2 - 2L)}$$

for the resistor to be non inductive

$$L - cR^2 = 0 \qquad L = cR^2$$

27. Ans: (a)

Sol:

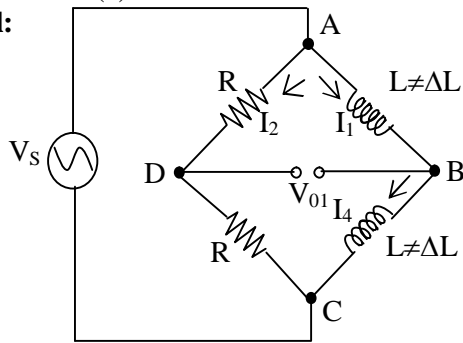


Fig.1

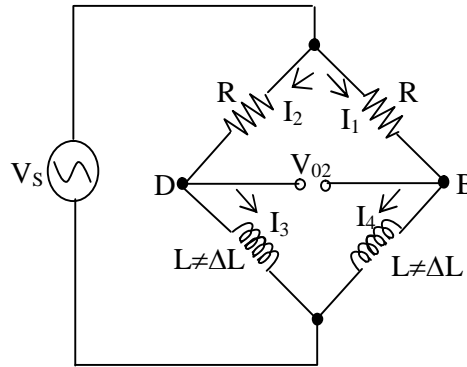


Fig.2

from fig. (1)

$$V = V_{AB} - V_{AB}$$

$$= I_1(L \pm \Delta L) - I_2 R$$

$$= \frac{V_s j\omega(L \pm \Delta L)}{j\omega(L \pm \Delta L + L \pm \Delta L)} - \frac{V_s}{R + R} \times R = \frac{V_s(L \pm \Delta L)}{2L} - \frac{V_s}{2R} \times R$$

$$= \frac{V_s}{2} \left[1 + \frac{\Delta L}{L} - 1 \right]$$

$$= \frac{V_s}{2} \times \frac{\Delta L}{L} = \frac{V_s}{2} \times 0.1 = 0.05 V_s$$

from fig. (2)

$$V = I_1 R - I_2 R$$

$$= \frac{V_s}{R + j\omega(L \mp \Delta L)} \times R - \frac{V_s \times R}{R + j\omega(L \pm \Delta L)}$$

$$= V_s R \left[\frac{R + j\omega(L \pm \Delta L) - (R + j\omega)(L \mp \Delta L)}{[(R + j\omega)(L \mp \Delta L)] - R + j\omega(L \pm \Delta L)} \right]$$

$$= V_s R \frac{2j\omega\Delta L}{(R + j\omega)(L \mp \Delta L)(R + j\omega)(L \pm \Delta L)}$$

$$= V_{01} = V_{02}$$

29. Ans: (a)

Sol: $Z_1 Z_x = Z_2 Z_3$ $Z_x = Y_1 Z_2 Z_3$


$$\left(R_x - \frac{1}{\omega c_x} \right) = R_2 \frac{1}{j\omega c_3} \times \left(\frac{1}{R_1} + j\omega c_1 \right)$$

$$R_x - \frac{j}{\omega c_x} = \frac{R_2}{j\omega c_3 R_1} + \frac{R_2 c_1}{c_3}$$

Compare two equations

$$R_x = \frac{R_2 c_1}{c_3} \quad \frac{1}{\omega c_x} = \frac{-R_2}{\omega c_3 R_1}$$

$$c_x = \frac{c_3 R_1}{R_2}$$

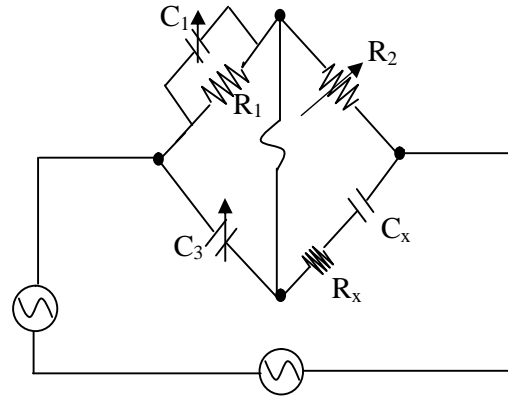

41. Ans: (c)

Sol: $\frac{1}{2}(\Delta c)V^2 = Fv$ displacement so

$$\Delta c = \frac{2 \times \text{force} \times \text{displacement}}{V^2} \quad V = 12 \text{ KV}$$

$$= \frac{2 \times 0.006 \times 1.5 \times 10^{-12}}{12 \times 10^{-3} \times 12 \times 10^3} \quad F = 0.006 \text{ N}$$

$$d = 1.5 \text{ mm} \\ = 0.125 \times 10^{-12} \text{ F} = 0.125 \text{ pF}$$

Previous gate questions

02. Ans: (a)

Sol: $V = V_{CA} - v_{CD}$


$$I = \frac{V_s}{R(1+x)+R}$$

$$= I_1 R(1+x) - I_2 R$$

$$= \frac{V_s}{R(1+x)+R} R(1+x) - \frac{V_s}{R+R(1+x)} \times R$$

$$= \frac{V_s [R(1+x) - R]}{2R + Rx} = V_s \frac{Rx}{R(2+x)}$$

$$V = IR_x$$

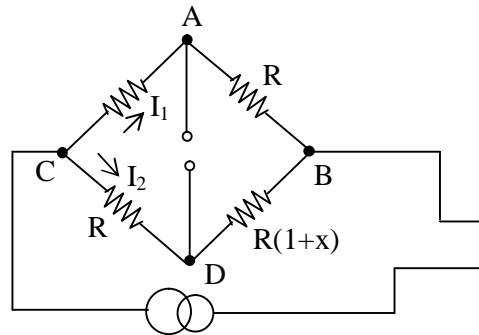

$$I_1 = I_3$$

$$I_2 = I_4$$