

CHAPTER-6

EXTENSION OF INSTRUMENT RANGES

01. Ans: (b)

Sol: $I_m = 1\text{mA} = 1 \times 10^{-3}\text{A}$, $R_m = 100\ \Omega$

$I = 5\text{A}$ $R_{sh} = ?$

$$R_{sh} = \frac{R_m}{m-1} \quad \text{Where } m = \frac{I}{I_m}$$

$$= \frac{100}{\frac{5}{10^{-3}} - 1} = \frac{100}{5000-1} = \frac{100}{4999} = \frac{1}{49.99}\ \Omega$$

02. Ans: (a)

Sol: $I_m = 1\text{mA} = 1 \times 10^{-3}\text{A}$, $R_m = 100\ \Omega$, $V = 100\text{V}$

$$V_m = I_m R_m = 1 \times 10^{-3} \times 100 = 0.1\text{V}$$

$$R_{se} = R_m (m-1) = 100 \left(\frac{V}{V_m} - 1 \right) = 100 \left(\frac{100}{0.1} - 1 \right)$$

$$= 100 (1000-1) = 99900$$

$$= 99.9\text{K}\Omega$$

03. Ans: (a)

Sol: The shunt Resistance is used for a milli-Ammeter to extend the range & to reduce the resistance of the instrument

04. Ans: (d)

Sol: The Internal resistance of a practical Ammeter in the range of “Hundreds of ohms”

05. Ans: (a)

Sol: Similarly for an milli ammeter the range is in ohms

06. Ans: (b)

Sol: Similarly for an micro Ammeter the range is in kilo ohms

Note: The Internal resistance of

- (1) Ideal Ammeter -----Zero
- (2) Ideal voltmeter ----- infinity
- (3) Ideal Current source ----- infinity
- (4) Ideal voltage Source ----- Zero.

07. Ans: (a)

Sol: $I = 50\ \mu\text{A}$

$$\text{Sensitivity} = \frac{1}{I} = \frac{1}{50 \times 10^{-6}} = \frac{10^6}{50} = \frac{10^4}{50}$$

$$= 20\ \text{K}\Omega/\text{V}$$

08. Ans: (c)

Sol: To reduce the Temperature error the resistance is made up of manganin.

09. Ans: (d)

Sol: A Ayrton shunt or universal shunt is used to make the D'Arsonal galvanometer into multi range Ammeter.

10. Ans: (a)

Sol: $R_{m1} = 100\Omega$, $P_1 = 0.1\text{mW}$
 $R_{m2} = 200\Omega$ $P_2 = ?$
 $P_1 = I_1^2 R_{m1}$

$$I_1 = \sqrt{\frac{0.1 \times 10^{-3}}{100}} = \frac{0.01}{10} = 1\text{mA}$$

$$P = I_1^2 R_{m2} = (1 \times 10^{-3})^2 \times 200 = 0.2\text{mW}$$

11. Ans: (b)

Sol: $I_m = 1\text{mA}$, $R_m = 100\Omega$ $I = 1\text{A}$

$$R_{sh} = \frac{R_m}{m-1} = \frac{100}{\frac{1}{10^{-3}} - 1} = \frac{100}{999} = 0.1001\Omega$$

12. Ans: (c)

Sol: $I_m = 1 \times 10^{-3}\text{A}$ $R_m = 100\Omega$ $V = 10\text{V}$

$$R_{se} = R_m(m-1) = 100 \left(\frac{10}{10^{-3} \times 100} - 1 \right) = 9900\Omega$$

13. Ans: (b)

Sol: $I_m = 1\text{mA}$ $R_m = 100\Omega$ $I = 100\text{mA}$

$$R_{sh} = \frac{R_m}{m-1} = \frac{100}{\frac{100 \times 10^{-3}}{10^{-3}} - 1} = \frac{100}{99} = 1.01\Omega$$

14. Ans: (b)

Sol: $R_m = 1000\Omega$ $m = 50$

$$R_{sh} = \frac{R_m}{m-1} = \frac{1000}{50-1} = 20.408\Omega$$

15. Ans: (a)

Sol: The most widely used material for resistors to get precision are

(i) Manganin (ii) Constantan (iii) Nickel Chromium Alloys

17. Ans: (d)

Sol: Shunts are used to extend the range of Ammeter or galvanometer upto 100Amps only & to measure high currents C.T'S are used.


Multipliers are used to extend the range of the voltmeter upto 1KV & to measure high voltages P.T's are used

18. Ans:(a)

Sol: The Purpose of Shunt in an Ammeter is to by pass the current

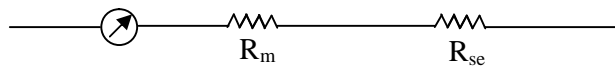19. Ans:(a)

Sol: The multiplier & meter coil are connected in series to a voltmeter



20. Ans: (c)

Sol: The loading effect is across a 2mΩ resistor only since $I \propto 1/R$



21. Ans: (a)

Sol: $R_m = 1000\Omega$ $I_m = 1\text{mA}$ $I = 3I_m$

$$R_{sh} = \frac{R_m}{m-1} = \frac{1000}{\frac{3I_m}{I_m} - 1} = 500\Omega$$

22. Ans: (b)

Sol:

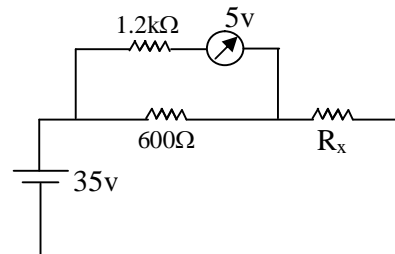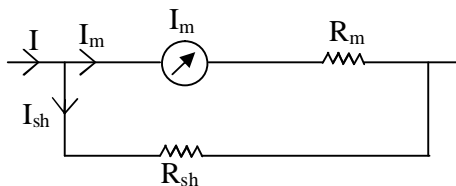

$R_{sh} = 0.02\Omega$ $R_m = 100\Omega$ $V_m = 500\text{mV}$

Voltage across parallel paths will be same

$$I_m R_m = I_{sh} R_{sh}$$

$$500 \times 10^{-3} = I_{sh} (0.02)$$

$$I_{sh} = \frac{500 \times 10^{-3}}{0.02} = 25\text{A}$$

23. Ans: (d)

Sol: By KVL

Voltage across $R_x \Omega = 35 - 5 = 30\text{V}$

1.2 KΩ & 600Ω are in parallel

$$R_{eq} = \frac{1.2 \times 10^3 \times 600}{1.2 \times 10^3 + 600} = 400\Omega$$

So voltage across 400Ω is 5V

By voltage division

$$30 = 35 \cdot \frac{R_x}{R_x + 400}$$

$$R_x = 2400\Omega = 2.4K\Omega$$

25. Ans: (d)

Sol: Swamping resistance is connected in series with the meter because to reduce the temperature error in shunt resistance.

27. Ans: (a)

Sol: $K = 0.14 \times 10^{-6} \text{ N.m/rad}$, $\theta = \frac{\pi}{2} \text{ rad}$, $l \times d = 15\text{mm} \times 12\text{mm}$

$$B = 1.8 \times 10^{-3} \text{ wb/m}^2 \quad I = 5\text{mA}$$

$$K\theta = BINA$$

$$N = \frac{K\theta}{BIA} = \frac{0.14 \times 10^{-6} \times 3.14/2}{1.8 \times 10^{-3} \times 5 \times 10^{-3} \times 15 \times 12 \times 10^{-6}}$$

$$N = 135.67 \cong 136$$

28. Ans: (a)

Sol: $I_m = 10\text{mA}$ $V_m = 100\text{mV}$ $I = 100\text{A}$

$$R_{sh} = \frac{R_m}{m-1} = \frac{100 \times 10^{-3} / 10 \times 10^{-3}}{\frac{100}{10 \times 10^{-3}} - 1} = \frac{10}{9999}$$

$$R_{sh} = 0.001\Omega$$

29. Ans: (a)

Sol: $R_{se} = R_m(m-1) = \frac{100 \times 10^{-3}}{10 \times 10^{-3}} \left(\frac{1000}{100 \times 10^{-3}} - 1 \right) = 10(9999)$

$$99.99K\Omega \cong 100K\Omega$$

Previous IES Questions

01. Ans: (d)

Sol: $25A \pm 1\% \rightarrow 25 \times \frac{1}{100} = 0.25A \rightarrow \text{G.A.E}$

$$5A \times \frac{x\%}{100} = 0.25 \Rightarrow \% x = \frac{0.25 \times 100}{5} = 5\%$$

02. Ans: (c)

Sol: $S_v = 20000\Omega/V$ (0–100V) $V = 1000V$
($V_m = 100V$)

$$R_m = 20000 \times 100 = 2 \times 10^6\Omega = 2M\Omega$$

$$R_{se} = R_m(m-1)$$


$$2 \times 10^6 \left(\frac{1000}{100} - 1 \right) = 18 \text{M}\Omega$$

03. Ans: (a)

$$\text{Sol: } R_{m1} = \frac{V_m}{I_m} = \frac{100}{5 \times 10^{-3}} = 20 \text{K}\Omega$$

$$Sv_2 = 250\Omega/V \quad R_{m2} = 250 \times 100 = 25 \text{K}\Omega$$

$$R_{m3} = 15 \text{K}\Omega$$

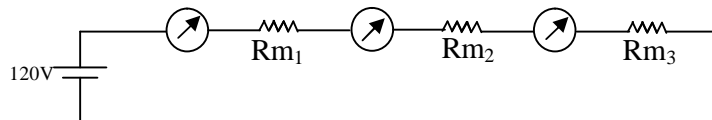

By voltage division

$$V_{m1} = 120 \times \frac{20 \text{K}\Omega}{20 \text{K} + 25 \text{K} + 15 \text{K}} = 120 \times \frac{20 \text{K}}{60 \text{K}} = 40 \text{V}$$

$$V_{m2} = 120 \times \frac{25 \text{K}\Omega}{60 \text{K}\Omega} = 50 \text{V}$$

$$V_{m3} = 120 \times \frac{15 \text{K}\Omega}{60 \text{K}\Omega} = 30 \text{V}$$

Previous Gate Questions

01. Ans: (c)

$$\text{Sol: } I_m = 100 \mu\text{A} \quad R_m = 100 \Omega \quad I = 500 \mu\text{A}$$

$$R_{sh} = \frac{R_m}{m-1} = \frac{100}{\frac{500 \times 10^{-6}}{100 \times 10^{-6}} - 1} = \frac{100}{4} = 25 \Omega$$

02. Ans: (d)

$$\text{Sol: } R_m = 50 \Omega \quad I_m = 50 \mu\text{A} \quad I = 1 \text{mA}$$

$$R_{sh} = \frac{R_m}{m-1} = \frac{50}{\frac{1 \times 10^{-3}}{50 \times 10^{-6}} - 1} = \frac{50}{19} = 2.63 \Omega$$

03. Ans: (c)

$$\text{Sol: } R_m = 0.1 \Omega \quad I_m = 100 \text{A} \quad I = 500 \text{A}$$

$$R_{sh} = \frac{R_m}{m-1} = \frac{0.1}{\frac{500}{100} - 1} = \frac{0.1}{4} = 0.025 \Omega$$