

CHAPTER-7 POTENTIOMETERS

Two Mark Questions

10. Ans: (b)

Sol: Measurement of reactance of a coil by using
Polar type ac potentiometer

Given that $I = 12 \angle 13.8^\circ$, $V = 27.8 \angle 29.7^\circ$

$$Z = \frac{V}{I} \angle \theta_C - \theta_S$$

Reactance $X = Z \sin(\theta_C - \theta_S)$, Where $\theta_C = 29.7^\circ$, $\theta_S = 13.8^\circ$

$$Z = \frac{27.8}{12} \angle 29.7^\circ - 13.8^\circ$$

$$Z = 2.31 \angle 15.9^\circ$$

Reactance $X = 2.31 \sin(29.7 - 13.8)$

$$X = 0.632 \Omega$$

11. Ans: (b)

Sol: The voltage read by potentiometer is 1.2V

The voltmeter reads 0.6V with $20,000 \Omega/V$ on 5V range

Input resistance $R_V = S_{DC} \times \text{voltage}$

$$R_V = 20,000 \times 5$$

$$R_V = 1,00,000 \Omega$$

12. Ans: (a)

Sol: Given that

Working current $I_w = 10 \text{mA}$

Dial resistor having 15 steps of 10Ω each

i.e. = 150Ω

slide wire resistance is = 10Ω

Total resistance = $150 + 10 = 160 \Omega$

Range of voltage = $I_w \times R_{\text{total}}$

$$= 10 \times 10^{-3} \times 160 = 1.6 \text{V}$$

Resolution: slide wire provide with 100 divisions and since the total resistance of slide wire (10Ω) corresponding to a voltage drop of ($10 \text{mA} \times 10 \Omega = 0.1 \text{V}$), each division of

slide wire corresponds to = $\frac{0.1}{100} = 0.001$

With certainly the reading upto $\frac{1}{5}$ of scale division

Then resolution is $\frac{1}{5} \times 0.001 = 0.2 \text{mV}$

13. Ans: (a)


Sol: For the voltage division $\left(\frac{V_0}{V_{in}}\right)$ is independent of frequency, the impedance ratio should also be independent of frequency

$$\begin{aligned} \frac{Z_1}{Z_2} &= \frac{R_1 \frac{1}{j\omega C_1}}{R_1 + \frac{1}{j\omega C_1}} \times \frac{R_2 + \frac{1}{j\omega C_2}}{R_2 \times \frac{1}{j\omega C_2}} \\ &= \frac{R_1}{1 + j\omega C_1 R_1} \times \frac{1 + j\omega C_2 R_2}{R_2} \\ &= \frac{R_1}{R_2} \cdot \frac{1 + j\omega C_2 R_2}{1 + j\omega C_1 R_1} \Rightarrow C_2 R_2 = C_1 R_1 \\ C_1 &= \frac{C_1 R_1}{R_2} = \frac{1 \times 10^{-6} \times 10}{1 \times 10^3} = 10 \mu\text{F} \end{aligned}$$

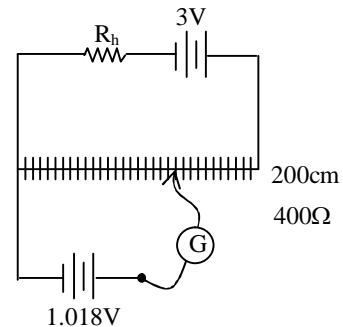15. Ans: (a)

Sol: Given that,

Working battery is 3V
 Slide wire is 400Ω
 Length L = 200 cm
 Let 10cm = 2Ω
 Standard cell voltage is 1.018V
 Sliding contact at 101.8cm
 Sliding contact resistance = 2 × 101.8 = 203.6Ω
 Current through the slide wire is



$$\begin{aligned} 1.018\text{V} &= I_w \times 203.6 \\ I_w &= 5 \times 10^{-3} \\ I_w &= \frac{E}{R_h + 400} \Rightarrow R_h + 400 = \frac{3}{5 \times 10^{-3}} = 600 \\ R_h &= 600 - 400 = 200\Omega \end{aligned}$$

16. Ans: (a)

Sol:

$$\begin{aligned} \text{Resistance of unknown resistor } R &= \frac{V_R}{V_S} S = \frac{0.4221}{1.0235} \times 0.1 = 0.041208\Omega \\ \text{Current through the resistor} &= \frac{V_S}{S} = \frac{1.0235}{0.1} = 10.235\text{A} \\ \text{Power loss in unknown resistance} &= I^2 R = (10.235)^2 \times 0.041208 = 4.316\text{W} \end{aligned}$$

17. Ans: (b)

Sol:

$$\begin{aligned} \text{Voltage drop per unit length} &= \frac{1.45}{50} = 0.029\text{V/cm} \\ \text{Voltage drop across 75 cm length} &= 0.029 \times 75 = 2.175\text{V} \\ \text{Current through resistor} &= \frac{2.175}{0.1} = 21.75\text{A} \end{aligned}$$

PREVIOUS IES QUESTIONS

03. Ans: (c)

Sol: Voltage drop per unit length = $\frac{1.45}{50} = 0.029\text{V/cm}$
 Voltage drop across 70 cm length = $0.029 \times 70 = 2.03\text{V}$
 \therefore Current through resistor = $\frac{2.03}{1} = 2.03\text{A}$

PREVIOUS GATE QUESTIONS

One Mark Questions:

02. (GATE-EE-1994)

Sol: Standard cell e.m.f = 1.18V
 And balanced at 600 mm
 \therefore Working current $I_w = \frac{1.18\text{V}}{600 \times 10^{-3}} = 1.967 \times 10^{-3}\text{A}$
 Test cell balanced at 680 mm
 $680 \times I_w = \text{test cell voltage (V)}$
 $\therefore V = 680 \times 1.96 \times 10^{-3} = 1.34\text{V}$

Two Marks Questions

06. GATE – IN – 1996

Ans: (a)

Sol: Under balanced condition

$$I_w = \frac{E}{R_h + R_{slide}}$$


$$= \frac{3.2}{200 + 200 + 2800} = 1 \times 10^{-3}\text{A}$$
 Then,

$$E_x = I_w \times 200 = 2 \times 10^{-3} \times 200 = 200\text{mV}$$

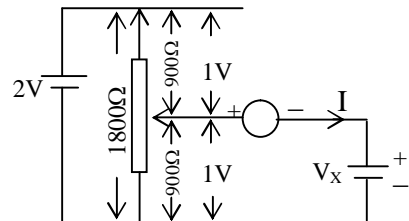07. GATE ,IN– 2003

Ans:(c)

Sol: Before reversing of V_x
 $I = 0.2 \times 10^{-3}\text{A}$
 $-V_x - IR_m - 1\text{v} = 0$
 $V_x = -(0.2 \times 10^{-3} \times R - 1) \dots\dots\dots(1)$
 After reversing of V_x
 $I = 3.8 \times 10^{-3}\text{A}$
 $V_x = 3.8 \times 10^{-3} \times R - 1 \dots\dots\dots(2)$
 Equating (1) & (2)



$$-\left[0.2 \times 10^{-3} R - 1\right] = \left[3.8 \times 10^{-3} \times R - 1\right]$$

$$R = \frac{2}{4 \times 10^{-3}} = 500 \Omega$$

From (2) $V_x = 3.8 \times 10^{-3} \times 500 - 1$
 $V_x = 0.9V$

08. GATE – IN – 2004

Ans:(a)

Sol: from the circuit

$$V = -\frac{R_f}{R} \times V_i = -\frac{15 \times 10^3}{10 \times 10^3} \times 1V = -1.5V$$

09. GATE – IN – 2004

Ans(a)

Sol:

E_x balances at 10 m 18cm

i.e 10.18m = 10.18Ω


$E_x = I_w \times$ resistance of slid wire at balance

$$I_w = \frac{1.018}{10.18} = 0.1A$$

$$I_w = \frac{E}{R_{sc} + 11}$$

$$R_{se} + 11 = \frac{2}{0.1}$$

$$R_{se} = 20 - 11 = 9\Omega$$

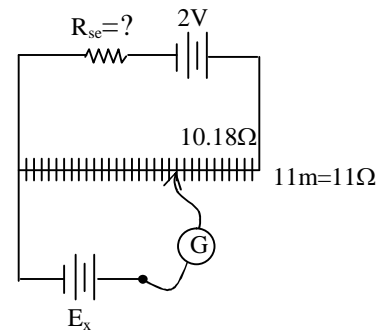

10. GATE – IN – 2006

Ans:(c)

Sol:

Voltage across 1000Ω resistance on slide wire by

Using voltage division = $1.6 \times \frac{1000}{1000 + 500 + 100} = 1V$

Apply KVL

$$E_v = I_g R_s + 1V$$

$$E_v = 10 \times 10^{-6} \times 100 + 1$$

$$E_v = 1.001V$$