

**ELECTRICAL  
AND  
ELECTRONICS  
MEASUREMENTS  
2012**



22/4/12  
(6 to 8)

1. Error Analysis
2. Basic Instruments
  - M-C type
    - PMMC
    - EMMC
  - M-I type
    - Attraction
    - Repulsion
3. Extension Range of Basic Instruments
4. Electro static Voltmeters
5. Thermal Instruments
6. Rectifier Type Instruments
  - H-Wave Rectifier
  - Full Wave "
7. Measurement of 'R', 'L' & 'C'
  - Dc Bridges
  - Ac Bridges
8.  $\phi$  - meter
9. Potentiometer
10. Measurement of Power
11. Measurement of Energy
12. Measurement of power factor, Unknown Frequency
13. DVM'S
14. CRO
15. Instrument Transformers.

Error Analysis : Error ( $E$ )

$$E = A_m - A_t$$

$\downarrow$  Measured Value  
 $\downarrow$  True Value  
 +ve ( $A_m > A_t$ )  
 -ve ( $A_m < A_t$ )

Static error  
Independent of time  
Dynamic error

the error which is independent of time  $\rightarrow$  Static error  
 the error which changes wrt time  $\rightarrow$  Dynamic error

Correction factor : The Value which we are added / subtracted from the "measured Quantity" in order to get true value.

$$C.F = -E$$

Relative Static error :-

\* % Relative Static Error =  $\left( \frac{A_m - A_t}{A_t} \right) \times 100$

\* Determines Quality of the Instrument

23/4/12  
(2 to 5:30)

Limiting Error : \* It is specified by the Manufacturer Range of Error

\* It give will the Range of operation (or) Error

\* the Limiting error is always wrt true Value

\* the other names are Tolerance and Uncertainty

Range  $\rightarrow$  Full scale value  
(0-10)A % LE

- A  $\pm 2\%$
- B  $\pm 1\%$
- C  $\pm 0.5\%$
- D  $\pm 0.01\%$

True value  
2A  $\rightarrow$

A:  $2 \times \frac{\pm 2}{100} = \pm 0.04$

$2 \pm 0.04$   $\rightarrow$  Measured Value

$\Rightarrow 1.96 - 2.04$

B:  $2 \times \frac{\pm 1}{100} = \pm 0.02$

$= 1.98 - 2.02$


? 'C' is the best & we should not choose 'D'.

\* In laboratories, experiments are performed repeatedly to cancel the positive errors and Negative errors so as to get the Accurate Value

\* Basic Characteristics of Instruments :

(Accuracy, Precision, Linearity, Sensitivity, Dead Time, Dead zone Resolution).

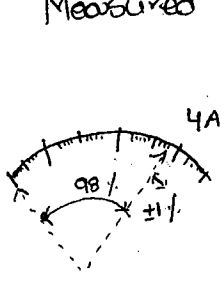Accuracy: the Accuracy indicates the degree of closeness of Measured Quantity to true Value.



A	±1%	→ High Accurate	± Indicates Deviation from true Value
B	±99%	→ 3rd "	
C	98%	→ 2nd high "	Normal Indicates Deflection from Initial
D	1%	→ 4 3rd "	

G.A.E.: (Guaranteed Accuracy Error)

It is specified by Manufacturer. It is a Constant error seen by the Instrument. Because it is respect to Full Scale Value.

(0-10)A     % G.A.E = ± 1%

$$\text{G.A.E} = \frac{10 \times \pm 1}{100} = \pm 0.1 \text{ \% LE}$$

1A ± 0.1     →  $1 \times \frac{x}{100} = 0.1 \Rightarrow 10\%$

2A ± 0.1     →  $2 \times \frac{x}{100} = 0.1 \Rightarrow 5\%$

5A ± 0.1     →  $5 \times \frac{x}{100} = 0.1 \Rightarrow 2\%$

9A ± 0.1     →  $9 \times \frac{x}{100} = 0.1 \Rightarrow 1.1\%$

As the pointer reaches to "Full Scale Value", the Error % LE decreases but the "Guaranteed Accuracy" is Constant. Bcz the "% LE" is wrt "true Value" and "G.A.E" wrt "Full Scale Value".

1. A (0-10)A Ammeter with a G.A.E of ± 1%. If we measure a true value of 2.5 A. % LE is —

$$2.5 \text{ A} \pm \frac{10 \times \pm 1}{100} = \pm 0.1$$

$$2.5 \pm 0.1 \rightarrow 2.5 \times \frac{x}{100} = 0.1$$

$$\Rightarrow x = \frac{0.1 \times 100}{2.5} = 4\%$$

2. A (0-10) A Ammeter with G.A.E error of 98%. If we measure a true value of 2.5 Amp. Then % Limiting error is .

$$10 \times \frac{\pm 2}{100} = \pm 0.2$$

$$98\% \rightarrow \pm 2\% \quad 2.5 \pm 0.2 \rightarrow 2.5 \left( \frac{\pm 0.2}{2.5} \right) = \pm 8\%$$

(Deflection) (Deviation)

$$x = \frac{0.2 \times 100}{2.5}$$

$$= \pm 8\%$$

3. A (0-10) A Ammeter with GAE error of  $\pm 1\%$  of reading. If we measure a true value of 2.5 A. Then % LE is

$$10 \times \frac{\pm 1}{100} = \pm 0.1\% \text{ "of reading"} \rightarrow$$

with true value

$$\rightarrow \text{Limiting error}$$

Precision: The Most repeatable Value (or) Reproducible Value out of set of records is known as precision

'A' is Accurate & precise Instrument.

'B' is precise Instrument

\* "Accurate Instrument" may be "precise" but "precise" will not confirm "Any Accuracy".

Be prefer Always Accurate as well as precise Instrument.



A <sub>L</sub> = 2A	
A	B
1.9	1.5
1.5	1.5
1.9	1.9
1.9	1.5
1.5	1.9
1.9	1.5
A & P	P

Linearity: the o/p follows the i/p with linear relation / equation is called Linearity.

In most of the meters, the responsible quantity is current. So, current causes a force on the pointer to deflect. (Electrical to force then force to angular deflection)

$$\theta \propto I \quad (\text{Linear})$$

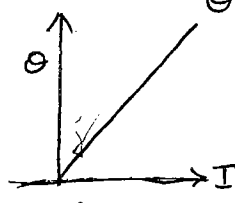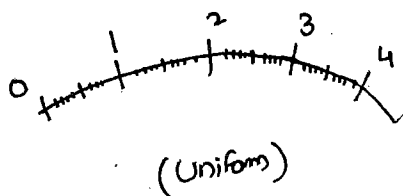
$$\theta \propto I^2 \quad (\text{Non-linear})$$



\* I  
PC  
ma  
TO  
arr  
\* Be  
that  
we  
\*\*  
\* Ser  
Be  
So

\* For  
and  
\* For  
the  
I

78 / IF  
% Limiting

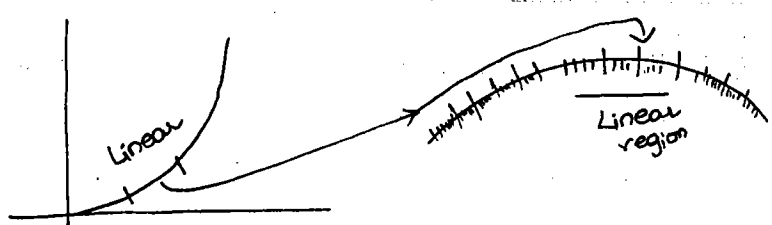

\* We have to choose a meter so that it reads the pointer reading is in Linear region so that Accuracy is maintained.

To measure 17A, we have to choose (0-20)A among (0-100)A, (0-20)A, (0-30)A meters

\* Be\* prefer always the instrument in such a way that the pointer should enter "Linear region" so that we may not lose "Accuracy"


\*\* Sensitivity:- (s):

Be prefer always "high Sensitive" Instruments High Sensitive  
Low "  
~~Medium~~ "  
So that we may not lose "Accuracy"

$$S = \frac{\text{Change in o/p}}{\text{Unit change in I/p}}$$


$$S = \frac{\Delta o/p}{\Delta I/p} = \text{slope of the } = \tan \theta$$

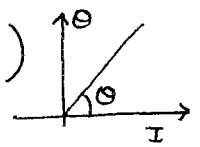\* For perfect linear Instruments, Sensitivity is Constant and is equal to 1 (as  $\theta = 45^\circ$ ,  $\tan \theta = 1$ )




For PMMC, Sensitivity = 1 (Linear)

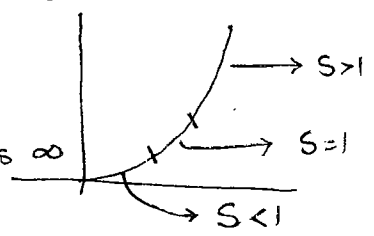\* For Non-linear Instruments, the Sensitivity will Vary through out the Scale.



Ideal voltmeter Int. Resist is  $\infty$

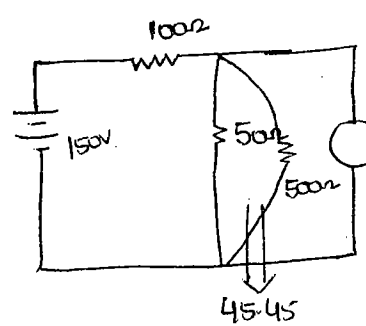

$$V_{AB} = \frac{150 \times 50}{150} = 50V$$

$$V_m = \frac{150 \times 45.45}{145.45}$$

Suppose 'S' is increased to 100k $\Omega$  then equivalent will become 49.99

2.2

% of  
% LEIS

} →

due

error

educable

precision

$V_L = 2A$

A B

7 1.5

5 1.5

1 1.9

7 1.5

1.9

1.5

P

ear

arity

on the


en

2)

inear)



mped

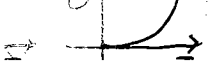

\* If Sensitivity is increased, then Accuracy will also be increased.



\* We can manufacture Int. Resistance  $\propto$  meter won't work as open ckt exist & flows  
 \* Be prefer "high Sensitivity" Instruments so increase "Accuracy"  
 24/4/12 (11 to 1)  
 A (0-10)V Volt the allowable C Reading.

Units  $S = \frac{\Omega/V}{V/\Omega} = \frac{1}{I} = \frac{1}{I_{FSD}} \therefore S = \frac{1}{I_{FSD}}$

" $I_{FSD}$  is the max. allowable current that meter will damage"

Pb: Two 100V Voltmeters with sensitivities of 10 & 20  $k\Omega/V$  respectively are connected in series. What is the max. voltage that we can measure with this series combination.

A (0-1) m Resistance

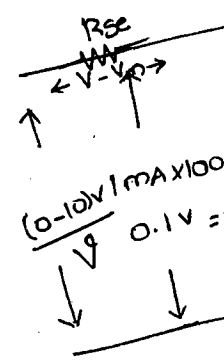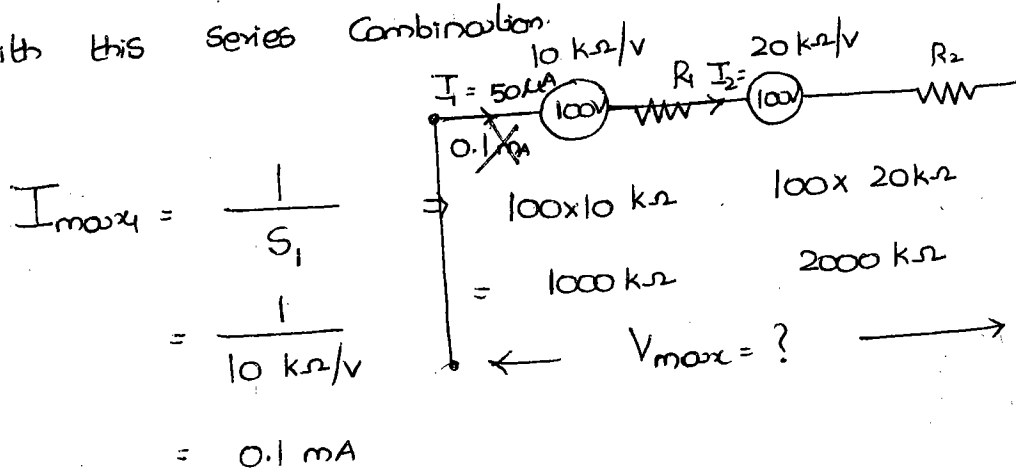

$I_{max1} = \frac{1}{S_1} = \frac{1}{10 k\Omega/V} = 0.1 mA$

$I_{max2} = \frac{1}{S_2} = \frac{1}{20 k\Omega/V} = 50 \mu A$

Among  $I_{max1}$ ,  $I_{max2}$ , we have to allow 50  $\mu A$  only otherwise  $V_2$  will be damaged

So,  $I_1 = 50 \mu A$

$V_{max} = (50 \mu A) (3000) k\Omega = 150 V$

So,

\*



24/4/12 (11 to 1)

1. A (0-10)V Voltmeter with a sensitivity of  $10 \text{ k}\Omega/\text{V}$  find the allowable current through voltmeter at half full scale Reading.

$$S = 10 \text{ k}\Omega/\text{V}$$

$$10 \times 10^3 \Omega/\text{V}$$

$$S = \frac{1}{I_{FS}} \times V_{FS}$$


$$I_{SD} = \frac{1}{10 \times 10^3}$$

$$= 10^{-4} \text{ A } = 0.1 \text{ mA}$$

∴ At half full scale =  $5 \times 10^{-4} \text{ A}$

$$\frac{0.1 \text{ mA}}{2} = 0.05 \text{ mA}$$

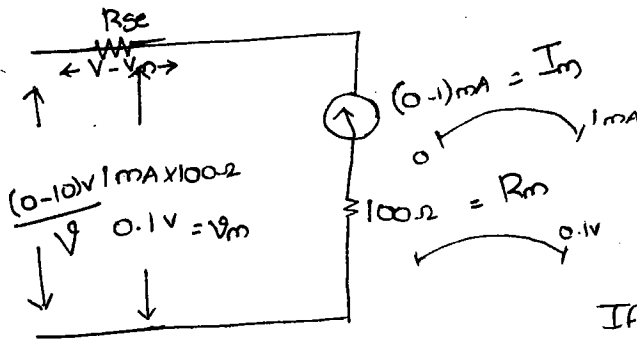
2. A (0-1) mA linear instrument with an internal resistance of  $100 \Omega$  is to be converted into (0-10) V.



But if we have to design for (0-10) V

If we apply 10V, meter damages. as the allowable is

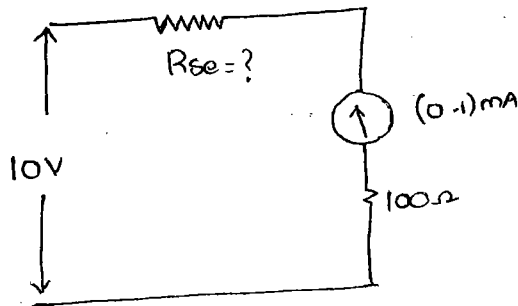So, a resistance in series have to be added.



$$I = \frac{V}{R}$$

$$1 \text{ mA} = \frac{10}{R_{se} + 100 \Omega}$$

$$\Rightarrow (R_{se} + 100) 10^{-3} = 10$$

$$R_{se} 10^{-3} + 0.1 = 10$$

$$\Rightarrow R_{se} = \frac{9.9}{10^{-3}} = 9.9 \text{ k}\Omega$$

\* We can manufacture only ammeters and it can be converted into voltmeter.

If we want to read for 20V, again calculate  $R_{se}$  and change it

As Current is Same

$$\Rightarrow \frac{V - V_m}{R_{se}} = \frac{V_m}{R_m} \Rightarrow \frac{R_{se}}{V - V_m} = \frac{R_m}{V_m}$$

Voltmeter  $\rightarrow$  
$$R_{se} = \left( \frac{V - V_m}{V_m} \right) R_m = \left( \frac{V}{V_m} - 1 \right) R_m$$


$$= (m - 1) R_m \quad \left( m = \frac{V}{V_m} \right)$$

$V \uparrow \leftrightarrow R_{se} \uparrow$

Other Way: 
$$R_{se} = \left( \frac{10}{0.1} - 1 \right) 100$$

$$= 9.9 \text{ k}\Omega$$

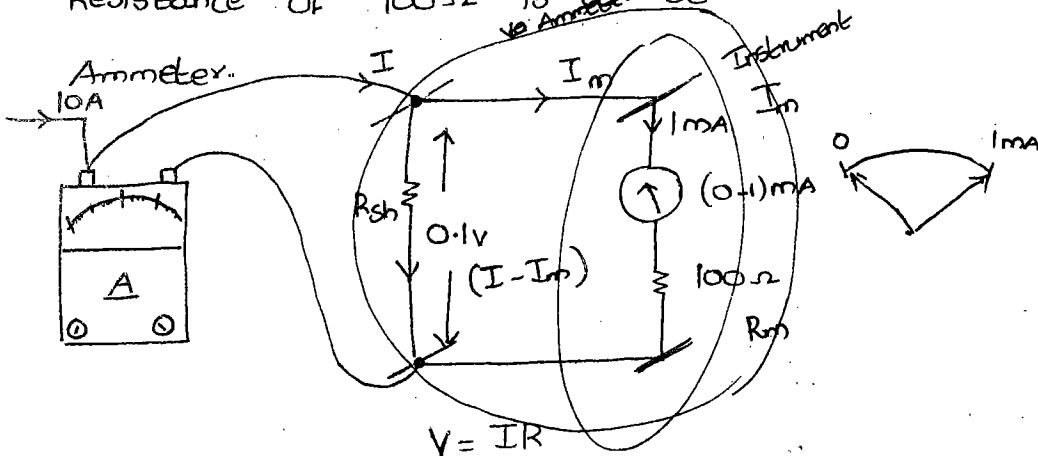3. A (0-1) mA linear Instrument with an Internal Resistance of  $100 \Omega$  is to be converted into (0-10) A



$$V = IR$$

$$R = \frac{V}{I} = \frac{0.1V}{10A}$$

$$\Rightarrow \frac{R_{sh} \parallel 100}{R_{sh} + 100} = 0.01$$

$I \uparrow, R_{sh} \downarrow$

$$R_{sh}(100) = 0.01 R_{sh} + 1$$

$$\Rightarrow R_{sh}(99.99) = 1 \Rightarrow R_{sh} = 0.01 \Omega$$

\* Voltage is same

$$R_{sh}(I - I_m) = I_m R_m$$

$$\Rightarrow R_{sh} = \left( \frac{I_m}{I - I_m} \right) R_m$$

Ideal Voltmeter,  
Int. Res  $\rightarrow \infty$   
Ideal Ammeter,  
Int. Res  $\rightarrow 0$

$$R_{sh} = \frac{R_m}{\left( \frac{I}{I_m} - 1 \right)}$$

Am Voltmeter

\* We can manufacture them but

they don't work

\* In always  
\* In always

\* Inx Voltme

Note 1:

1. By Will
2. By instr
3. I Curve
4. T
5. T

6. /

Volt

7. /

8. /

Since

9. /

ins

10. /

but

will

11. /

\* In Voltmeter, we have series Ntack inside. So, we always connect in || (Voltage division)

\* In Ammeter, we have parallel Ntack inside. So, we always connect in Series (Current division)

High currents bypassed through shunt Resistance

$$-1) R_m$$

$$\left( m = \frac{V}{V_m} \right)$$

\* Instrument is a part of meter. In Ammeter, Voltmeter Instruments are same.

Note 1: (Summary)

1. By connecting high Resistance in Series with an instrument will become Voltmeter
2. By connecting low Resistance across / parallel to the instrument will become Ammeter
3. In both the meters, the responsible quantity is Current

4. The Value of  $R_{se} = R_m \left( \frac{V}{V_m} - 1 \right)$

5. The Value of  $R_{sh} = \frac{R_m}{\left( \frac{I}{I_m} - 1 \right)}$

6. As we are increasing the Voltage Range,  $R_{se}$  Value increases

7. As the Current Range increases,  $R_{sh}$  Value decreases

8. Voltmeters are to be always connected in || since inside voltmeter series ckt there

9. Ammeters are to be connected in Series. Since, inside ammeter parallel ckt there

10. Ideal Voltmeters, Ammeters can be manufactured but they should not be manufactured, as current will not enter and it will not work

11. Instrument is a part of Meter

0-10A

0-10

em but

Dead Time:

Ammeters  $\Theta \propto I$

In all electrical instruments, the responsible quantity is Current.

Voltmeters  $\Theta \propto I \propto V$

In case of Current measurement We cannot directly measure Voltage

$\Theta \propto I$  In case of Voltage measurement,  $\Theta \propto I \propto V \Rightarrow \Theta \propto V$

Note 1: In all electronic instruments, the responsible quantity is Voltage (Bcz pulse counting is there, pulse is nothing but Voltage pulse)

\* All electrical instruments are energy converters which converts electrical energy to Mech. energy  
 \* All electronic meters are not energy converters. So,

these are fast response instruments when compared to electrical instruments since there is no energy conversion.

\* If we use electrical instruments for low values it will not deflect and if electronic instruments for high values they damage



\* The time taken by the instrument to move the pointer from its initial position is called Dead time

\* The Main reason for dead time is Inertia


\* All instruments will experience both transient as well as steady state. Initially transient, finally reaches to steady state

Dead zone: The minimum input beyond which the response will come is called Dead zone other name is threshold

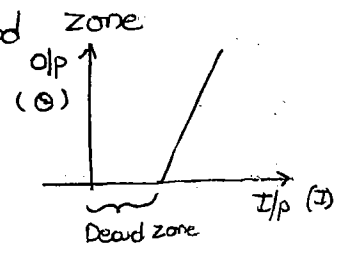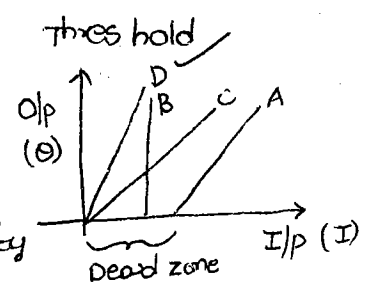Among C, D. D is best bcz of high sensitivity



1. A the Reading

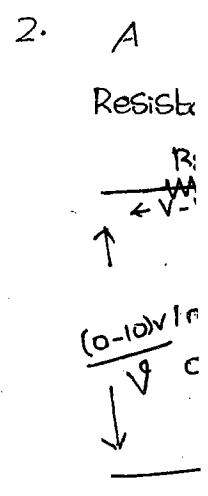

Sc

\* Ca

Rec

Resolution :- (R) :- The Smallest output that we can detect with certainty (or) clarity is called Resolution (or) the Smallest change in I/p that we can detect with certainty clarity. We prefer always High Resolution Instruments. As the Resolution increases, Clarity increases so that we may not lose Accuracy.

$$R = \frac{\text{Full scale Value}}{\text{Total No. of divisions}}$$

If No. of divisions increases, Resolution also increases.

Types of Errors :-

1. Gross Error
2. Systematic Error
3. Random Error

Instrumental  
 Environmental  
 Observational

\* All Human Negligence errors comes under Gross Error while taking errors (varies from one person to person)

\* Instrumental errors — (due to Manufacturing defects, ageing, loading error also come under this)

\* Environmental errors — (due to temp. changes in environment)

\* Observational errors — parallax errors

→ Common for all

\* Random errors — There is no particular reason for occurring of these errors. Suddenly, the error will come and disappear.

\* All the instruments will offer Random errors. The Random errors may be +ve (or) -ve. We can solve these errors by using Mathematical tool.

\* The Random errors can be solved by using Mathematical tool statistics like mean, mode and standard deviation.

Statistics

$$s.d = \sigma = \sqrt{\frac{d_1^2 + d_2^2 + \dots + d_n^2}{n-1}}$$

like Arithmetic

Random Error Analysis:

Suppose (0-150) V, 0.1 Voltmeter taken and true Value  $A_t = 100V$ . Measure 50 times

- 99.7 - 1
- 99.8 - 4
- 99.9 - 12
- 100 - 19
- 100.2 - 3
- 100.3 - 1


$d_{10}^2$

2/35

930

2

True  
Met

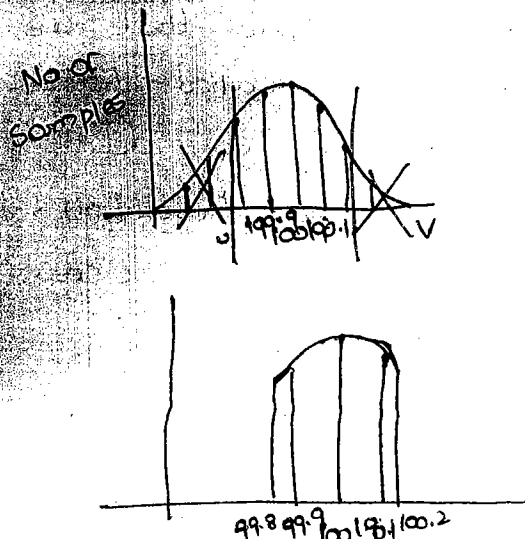

Probable error =  $\pm 0.6745 \sigma$

$$S.D = \sqrt{\frac{d_1^2 + d_2^2 + \dots + d_n^2}{(n-1)}}$$

$n \leq 20$   
 $n \geq 20$

Eliminate high

Note: 1. Let  $R_1 = (100 \pm 4) \Omega$ ,  $R_2 = (50 \pm 2) \Omega$   
 $R_1 + R_2 = (150 \pm 6) \Omega$ ,  $(R_1 - R_2) = (50 \pm 6) \Omega$

Met

In case of Addition & Subtraction, the absolute errors will be added up

2. Let  $R_1 = 50 \pm 6 \%$ ,  $R_2 = 10 \pm 3 \%$   
 $R_1 \times R_2 = 500 \pm 9 \%$ ,  $\frac{R_1}{R_2} = 5 \pm 9 \%$

In case of Multiplication & division, the % errors will be added up

$$R_1 \times R_2 = 5000 \pm (2 \times 3\% + 1 \times 6\%) = 5000 \pm 12\%$$

\* Two resistors  $R_1$  &  $R_2$  connected in ||, the values of  $R_1$  &  $R_2$  are  $(100 \pm 0.1) \Omega$ ,  $R_2 = (50 \pm 0.05) \Omega$ . Then calculate total uncertainty in the combined resistor.

(33.33  
2)

$$\Rightarrow \frac{R_1 R_2}{R_1 + R_2} = \frac{(100 \pm 0.1)(50 \pm 0.05)}{(100 \pm 0.1) + (50 \pm 0.05)}$$

$$100 \times \frac{x}{100} = 0.1$$

$$x = 0.1\%$$

$$50 \times \frac{x}{100} = 0.05$$

$$x = 0.1\%$$

$$150 \times \frac{x}{100} = 0.15$$

$$= \frac{(100 \pm 0.1)(50 \pm 0.1\%)}{(150 \pm 0.15)}$$

$$= \frac{(5000 \pm (0.2)\%)}{(150 \pm 0.15)}$$

$$(5000 \pm (0.2)\%)/150 = 33.333 \pm$$

$20 \times \frac{1}{100}$   
 $\Rightarrow 2$

True  $\times \frac{x}{100} = \text{tolerance} = (33.333 + 0.099) \Omega$

(9)

Method 2:

$$R_{eq} = \frac{R_1 + R_2}{R_1 + R_2}$$

$$\frac{\Delta R_{eq}}{R_{eq}} = \frac{\Delta R_1}{R_1} + \frac{\Delta R_2}{R_2} + \frac{\Delta (R_1 + R_2)}{(R_1 + R_2)}$$

$$\frac{\Delta R_{eq}}{33.33} = \frac{0.1}{100} + \frac{0.05}{50} + \frac{0.15}{150}$$

$$= 0.001 + 0.001 + 0.001 = 0.003$$

$$\Delta R_{eq} = 33.33 \times 0.003 = 0.1 \Omega$$

$$\therefore (33.33 + 0.1) \Omega$$

Method 3:

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$


$$R_{eq} = 33.33 \Omega \quad \text{extreme high}$$

$$R_{eq} = \frac{(100 + 0.1) \times (50 + 0.05)}{(100 - 0.1) + (50 - 0.05)} \quad \text{extreme low}$$

$$= 33.43 \Omega \quad \text{extreme low}$$

$$R_{eq} = \frac{(100 - 0.1)(50 - 0.05)}{(100 + 0.1) + (50 + 0.05)} \quad \text{extreme high}$$

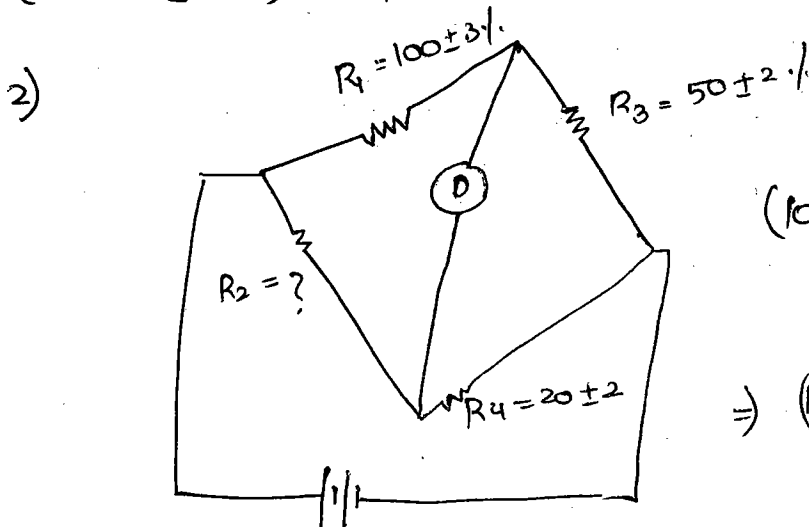on careful examination of above two answers  
 $(33.33 \pm 0.1) \Omega$  is the answer



$$(100 \pm 3\%) (20 \pm 2\%) = (50 \pm 2\%)^2$$

$$\Rightarrow (100 \pm 3\%) (20 \pm 10\%) = (50 \pm 2\%)^2$$

$$\Rightarrow \frac{(20 \pm 10\%)^2}{(50 \pm 2\%)^2} = 2$$

$$x = 40 \pm 15\% \Rightarrow (20 \pm 15\%)^2 = 2$$

$$20 \times \frac{x}{100} = 2$$

$$\Rightarrow x = 10\%$$

$$33.333 \pm 0.3\%$$

3) The following ten readings were observed while measuring a voltage.

- 1 → 41.7
- 2 → 42
- 3 → 41.8
- 4 → 42
- 5 → 42.1
- 6 → 41.9
- 7 → 42.5
- 8 → 42
- 9 → 41.9
- 10 → 41.8

Find the probable error

Probable error =  $\pm 0.6745 \sigma$

$$\sigma = \sqrt{\frac{d_1^2 + d_2^2 + \dots + d_n^2}{n-1}}$$

Avg = 41.97

$d_1 = 41.7 - 41.97 = -0.27$

$d_2 = 42 - 41.97 = 0.03$

$d_3 = 41.8 - 41.97 = -0.17$

$d_4 = 42 - 41.97 = 0.03$

$d_5 = 42.1 - 41.97 = 0.13$

$d_6 = 41.9 - 41.97 = -0.07$

$d_7 = 42.5 - 41.97 = 0.53$

$d_8 = 42 - 41.97 = 0.03$

$d_9 = 41.9 - 41.97 = -0.07$

$d_{10} = 41.8 - 41.97 = -0.17$

$$\sigma = \sqrt{\frac{d_1^2 + d_2^2 + \dots + d_{10}^2}{9}}$$

= 0.22135

Probable error =

$\pm 0.6745 \times 0.22135$

=  $\pm 0.14930$

$\therefore 41.97 \pm 0.14930$

Resolution

with

Smaller

Clarity

As it

we

Types

\* A

while

\* {

\*

\* }

\* F

for

and

\* All

Random

errors

\* the

by

mean

25/41

Random

and



will


4. The limiting errors of a 4-dial resistance box

are Units:  $\pm 0.2\%$

Tens:  $\pm 0.1\%$

Hundreds:  $\pm 0.05\%$

Thousands:  $\pm 0.02\%$

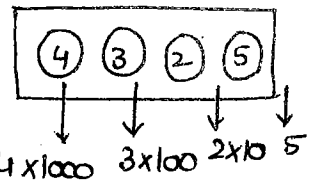

The Value of Resistance  $\odot$  in the dial box is 4325  $\Omega$ . Find the total limiting error in the resistance

$$4000 \times \frac{0.02}{1000} + 300 \times \frac{0.05}{100} + 20 \times \frac{0.1}{100} + 5 \times \frac{0.2}{100}$$

$$= \pm 0.1043\% \rightarrow 0.8 + 0.15 + 0.02 + 0.01$$

$$4325 \times \frac{0.1043}{100} = 0.98$$

$$\Rightarrow (4325 \pm 0.98)$$

$$4325 \times \frac{x}{100} = 0.98 \Rightarrow x = 0.0226\%$$

5. A 3 $\phi$  power is measured by using two wattmeter method. one of the wattmeter reading is 50 W with an Accuracy error of  $\pm 0.5\%$ . And the second wattmeter reading is 125 W with an Accuracy error of  $\pm 1.5\%$  of reading. Both the wattmeters are having a full scale reading of 150 W. Then the total power in 3 $\phi$  ckt.

$$(50 \pm 0.5\%)$$

$$(125 \pm 1.5\%)$$

$$150 \times \frac{0.5}{100} = \pm 0.75$$

$$50 \text{ W} \pm 0.75$$

$$\Rightarrow \frac{50 \times 2}{100} = 0.75 \Rightarrow x = \pm 1.5\%$$

$$125 \times \pm 1.5$$

$$125 \pm 2.25$$

$\Rightarrow$

$$\Rightarrow 175 \pm$$

$$50 \pm 0.25$$

$$125 \pm 1.875$$

$$50 \times \frac{0.5}{100} = 0.25$$

$$125 \times \frac{1.5}{100} = 1.875$$


$$175 \pm 2.125$$

Given direct Error of reading  $\rightarrow$  LE

but  
= Current  
as to

after

10 k $\Omega$ /V,  
res. then  
measure

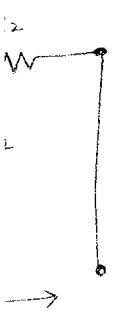

ultao  
ed

$$150W \begin{cases} W_1 = 50 \\ W_2 = 125 \end{cases}$$

$$50 \times \frac{1.5}{100} = 0.75$$

$$150 \times \frac{0.5}{100}$$

$$50 \pm 0.75$$

$$125 \times \frac{1.5}{100} = 1.875$$

$$125 \pm 1.875$$

$$\Rightarrow 175 \pm 2.625$$


$$\Rightarrow 175 \times \frac{2.625}{100} = 2.625$$

$$x = 1.5 \%$$

$$\therefore A: 175 \pm 1.5 \%$$

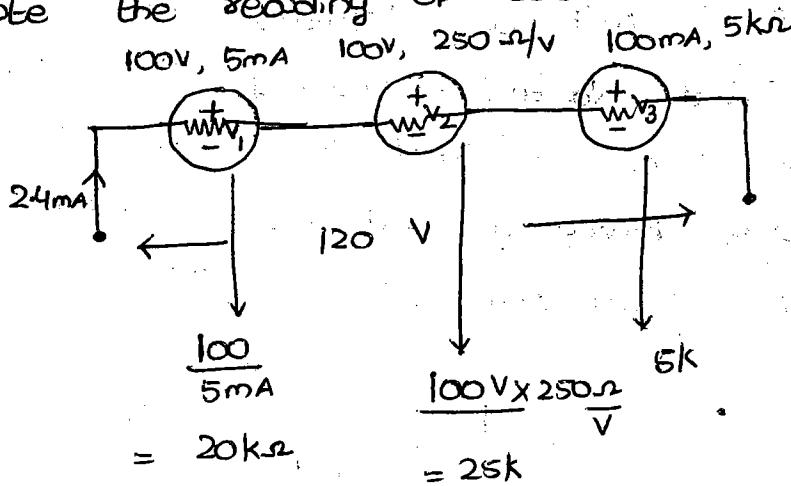- 6) Three Voltmeters are Connected in Series across 120 V DC supply. They are 1) 100V, and 5 mA  
2) 100V and 250  $\Omega/V$   
3) 100 mA and 5 k $\Omega$

Then estimate the reading of each Voltmeter.



$$\Rightarrow \text{Eq. Resistance} = 50k$$

$$I = \frac{120}{50k} = 2.4 \text{ mA}$$

$$\text{I Voltmeter} = 2.4 \text{ mA} \times 20k = 48 \text{ V}$$


$$\text{II Voltmeter} = 2.4 \text{ mA} \times 25k = 60 \text{ V}$$

$$\text{III " " } = 2.4 \text{ mA} \times 5k = 12 \text{ V}$$

7. A  
diver.  
of  
the

8. A  
x,  
coil  
of  
re  
80  
the

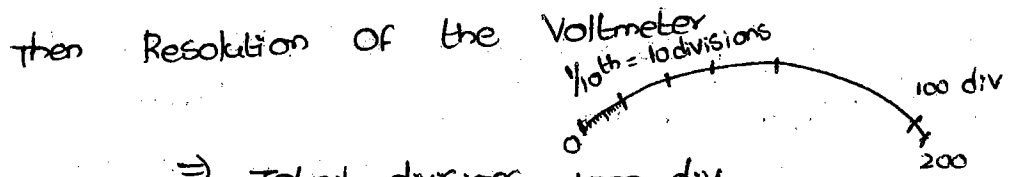7. A Moving Coil Voltmeter has uniform scale with 100 divisions with a full scale reading of 200V and  $\frac{1}{10}$ th of the scale division can be measured very accurately.



$\Rightarrow$  Total divisions = 1000 div

$\Rightarrow$  Resolution =  $\frac{200}{1000}$  (=  $\frac{\text{Full Scale Value}}{\text{No. of divisions}}$ )  
= 0.2

8. A Variable 'W' is measured with three <sup>other</sup> variables x, y, z as  $W = \frac{xy}{z}$ . The variables are measured with three meters with accuracies of  $\pm 0.5\%$  of reading,  $\pm 0.1\%$  of full scale and  $\pm 0.1\%$  of full scale and  $\pm 0.1\%$  of full scale. The actual readings of three meters are 80, 20 & 50 with 100 being full scale for 3 meters then find total uncertainty in measurement will be

$\Rightarrow$   $80 \times \pm \frac{0.5}{100} = \frac{4}{10} = \pm 0.4$   
 $20 \pm 0.1\%$   
 $50 \pm 0.05\%$   
 $50 \times \frac{0.1}{100} = 0.05$

$\Rightarrow W = \frac{(80 \pm 0.5\%)(20 \pm 0.1\%)}{(50 \pm 0.1\%)}$

$80 \times \frac{0.5}{100} = 0.4$

$\Rightarrow x = \frac{4}{8}$

= 0.5

$50 \times \frac{0.1}{100} = 0.05$

$x = \frac{0.5}{5}$

= 0.1

$X = 80 \pm 0.5\%$

$Y = 20 * L^{\Rightarrow} 20 \times \frac{0.1}{100} \Rightarrow 1 \Rightarrow x = 1\%$

$Z = 50 \pm 1.5\%$

=  $\left( \frac{80 \times 20}{50} \right) + \left( \frac{+5.5}{\pm 1.5} \right)$

$\pm 7\%$

0.75  
5  
across  
2/v  
n  
eter.  
skn  
↓

26/4/22 (11 to 1)  
 9. The power factor is measured by using three meters, they are Ammeter, Voltmeter and Wattmeter. The Ammeter reads as 2.5 A on 5A (Full scale Reading). The Voltmeter reads as 115V on 250V (Full scale Reading) and the power as 220W on 500W Wattmeter. The Ammeter and Voltmeter are having a GAE of  $\pm 0.5\%$  of full scale deflection and the Wattmeter has GAE of  $\pm 1\%$  of Full scale deflection. Then calculate the uncertainty in Power-factor will be —

10. A  
 Eq.  
 Vol  
 the  
 I  
 <

Sol:

$$I = 5 \times \frac{0.5}{100} = 0.025$$

$$V = 250 \times \frac{0.5}{100} = 1.25$$

$$W = 500 \times \frac{1}{100} = 5$$

Sol:

$$P = VI \cos \phi$$

$$PF = \cos \phi = \frac{P}{VI}$$

Watt
Ammeter

	FSV		At				
$\pm 0.5\%$	5A	← I →	2.5	± 0.025			
	250V	← V →	115V	± 1.25			
$\pm 1\%$	500W	← W →	220W	± 5			

$$5 \times \frac{0.5}{100} = 0.025$$

$$2.5 \times \frac{2}{100} = 0.025 = \pm 1\%$$

$$115 \times \frac{2}{100} = 1.25 = \pm 1.086\%$$

$$220 \times \frac{2}{100} = 5 = \pm 2.27\%$$


$$\Rightarrow PF = \frac{220}{115 \times 2.5} = \pm 4.358\%$$

$$\Rightarrow \underline{A} = 0.76 \pm 4.358$$

$$Error = \frac{\% GAE}{100} \times FSV = \text{True Value} \times \frac{\% LE}{100}$$

eters. They  
ter reads  
ads as  
as 220W  
are  
and  
deflection.  
will be —

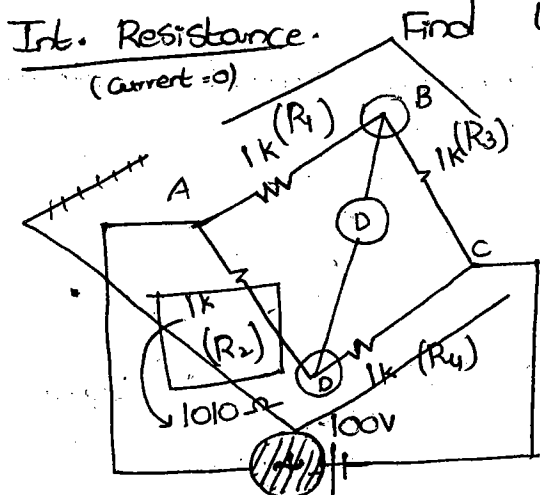10. A Wheatstone Bridge is balanced with all 4 resistances equal to  $1k\Omega$  each. The Bridge Supply Voltage is 100V. The Value of one of the resistance is changed to  $1010\Omega$ . (So, Voltage Division rule is applied) The o/p is measured with Voltage measuring device of  $\infty$  Int. Resistance. Find the bridge Sensitivity



$$S = \frac{\text{change in o/p}}{\text{change in I/p}}$$

$$= \frac{e}{10}$$

change in o/p =  $e - 0 = e$

$$e = V_B - V_D$$

$V_B \rightarrow$  It is nothing but total voltage - drop across AB

$$V_D = 100 - V_{AD} \quad \quad \quad = 100 - V_{AB}$$

$$e = 100 - V_{AB} - 100 + V_{AD}$$

$$= V_{AD} - V_{AB}$$

$$V_{AD} = 100 \times \frac{1010}{1010 + 1000} = 50.2487V$$

$$V_{AB} = 100 \times \frac{1000}{1000 + 1000} = 50V$$

$$e = 0.2487$$


$$\Rightarrow S = \frac{0.248}{10} = 0.0248 = 25 \text{ mV}/\Omega$$

0.25 =  $\pm 1\%$   
=  $\pm 1.086\%$   
=  $\pm 2.272\%$

$$\frac{\Delta LE}{100}$$
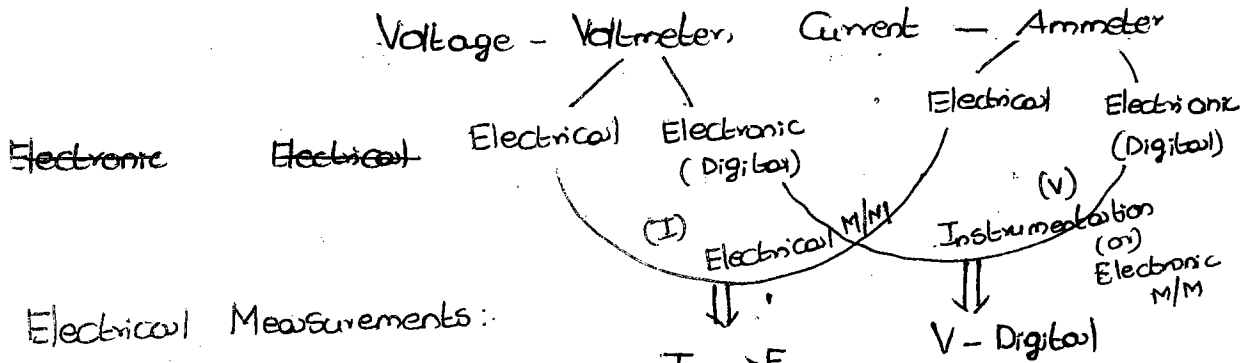
## Unit - II

Basic Instruments: The Instruments which are used for the measurement of basic quantities are called Basic Instruments.



Electrical Measurements:


In all electrical Instruments,  $I \rightarrow F$ .  
 The responsible quantity is current and it is converted into force.

There are mainly 4 effects that convert current into force are:

- a) Magnetic Effect
- b) Thermal effect
- c) Electrostatic effect
- d) Induction effect

$$F = BIL \sin \theta$$

↓  
Lorentz's law

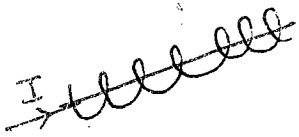

Any meter (i.e., almost all meters) come under the above four

\* Basically there are three forces will develop in all electrical Instruments

- a) Deflecting force / torque ( $T_d$ )
- b) Controlling force / torque ( $T_c$ )
- c) Damping force

a) This is the force reqd to move the pointer from its initial position by using any one of the effect. But because of this force, the pointer continuously rotate in the meter which is undesirable so that we need one more force which is opposite in direction. This force is called control torque.

27/4/12  
(11601)

b) Controlling Torque: This is the force which is opposite in direction to the deflection torque. When  $T_d = T_c$ , pointer will come to steady state. But before coming to the steady state, the pointer will make so many oscillations which is undesirable so that we need one more force to reduce the no. of oscillations at steady state is called Damping Torque.

c) Damping Torque: It is the force reqd to reduce the no. of oscillations at steady state.

\* Functions of Controlling Torque:

- It will provide a proportional output to the input
- When the I/p has been removed, the pointer should back to initial position.

Actually, the damping force will make to reduce the speed of the pointer so that the no. of oscillations will be reduced at steady state.

\* At steady state only two forces: deflection, Controlling

\* When pointer comes to rest position from steady state only one force: Controlling Torque

Ⓟ A PMMC instrument is spring controlled, the control spring stiffness decreased by  $0.04\%$  /  $^{\circ}$  rise in temp and strength of the magnet decreased by  $0.02\%$  per degree rise in temp. The rise in temp of  $10^{\circ}\text{C}$ , the new deflection.

$T_c$	$1^{\circ}\text{C}$	$10^{\circ}\text{C}$	$T_c \downarrow 0.4\%$	$\uparrow 0.4\%$
Stiffness of Spring	$0.04\% \downarrow$	$0.4\%$	$0.2\% \downarrow$	$0.2\%$
Strength of Magnet	$0.02\% \downarrow$	$0.2\%$	$0.2\% \downarrow$	$0.2\%$

$F = BIL \sin \theta$

$\theta \rightarrow 0.2\%$

Mechanism for producing  $T_d$ : (Magnetic Effect)


i) Force b/w Permanent Magnet & Current carrying coil:

$\theta = \frac{BINA}{k}$


$0.2\% \uparrow$        $\downarrow 0.2\%$

$0.4\% \uparrow$        $0.4\% \downarrow$

21/4/12  
(11 to 1)

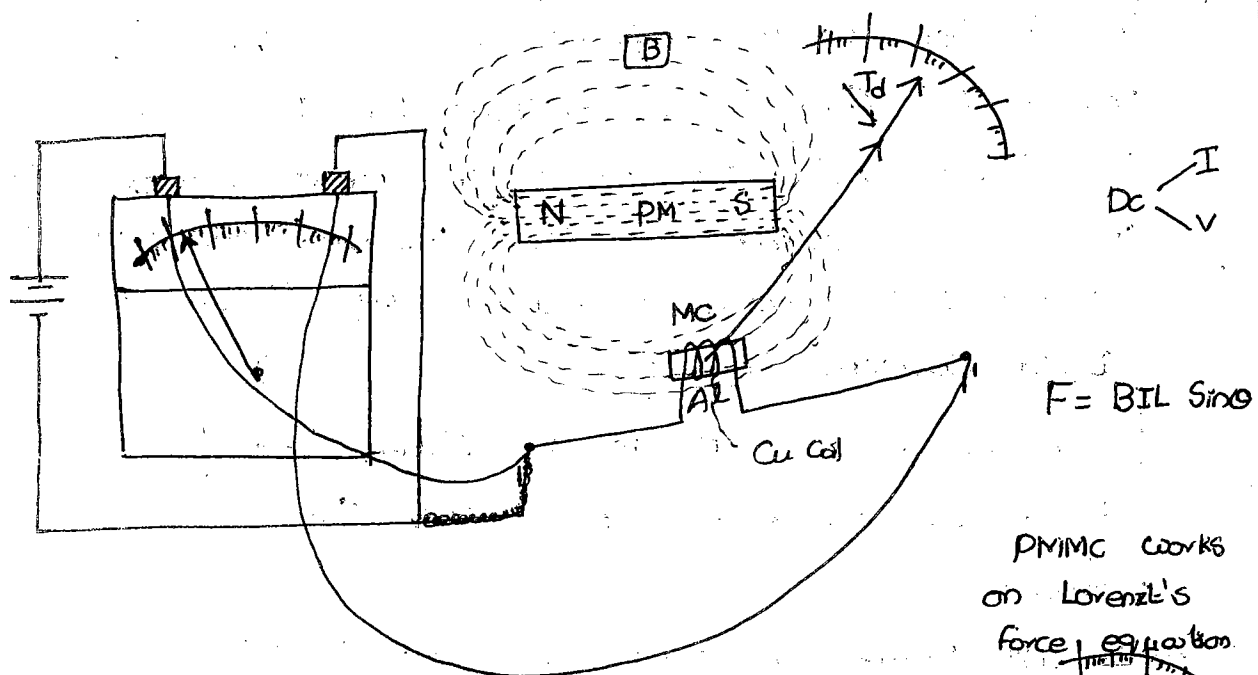


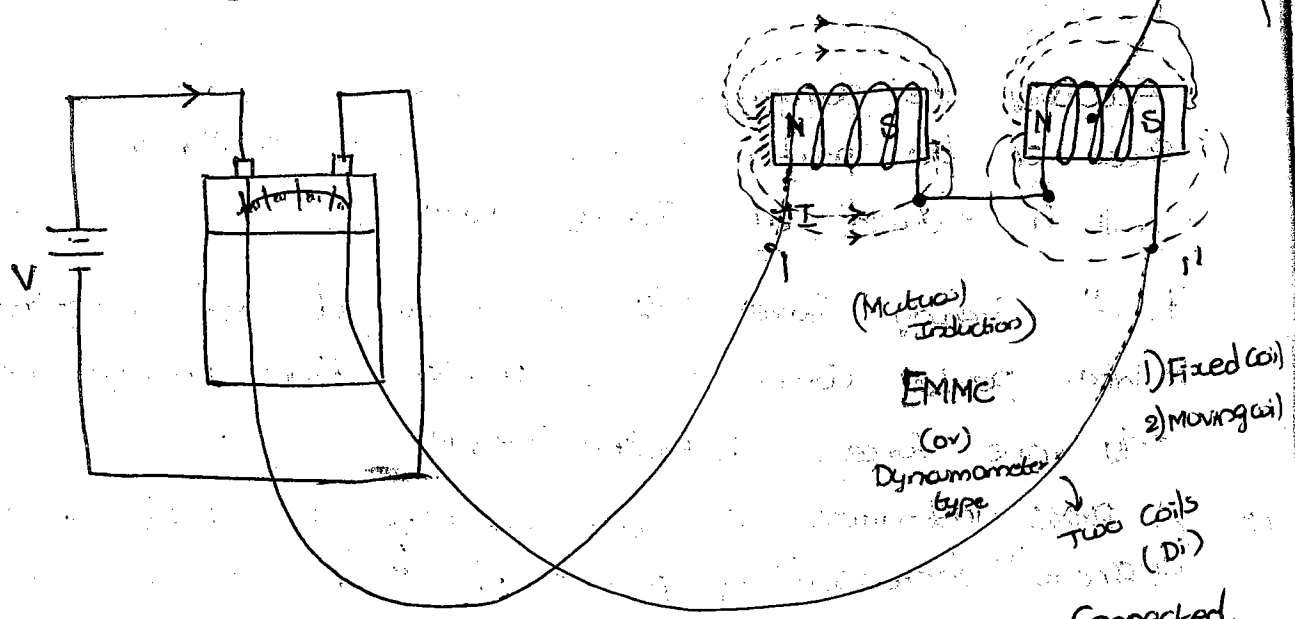2. Force between two current carrying coils



When battery of unknown voltage is connected, it drives a current to enter the coil, apply Fleming's Right hand rule, to find the direction of force. Magnetic lines of force (Flux lines) then it become magnetised. Ifly other also get magnetised. Force of attraction exists btw magnets and  $T_d$  acts on pointer.

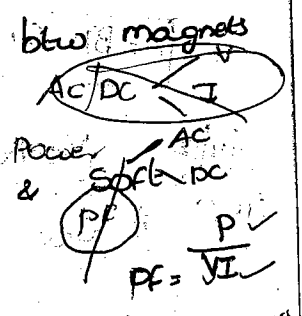3. Force between current carrying coil & Iron Disc (SID)




Power =  $\frac{P}{V}$   
 $P = VI$

(three errors in P, V, I)

Prec  
 mo  
 I  
 \* f  
 \* ↑  
 b  
 te  
 \* |  
 only  
 Co  
 on  
 \* ↑  
 Co  
 G  
 \* I  
 C  
 @  
 \* M  
 I  
 \*



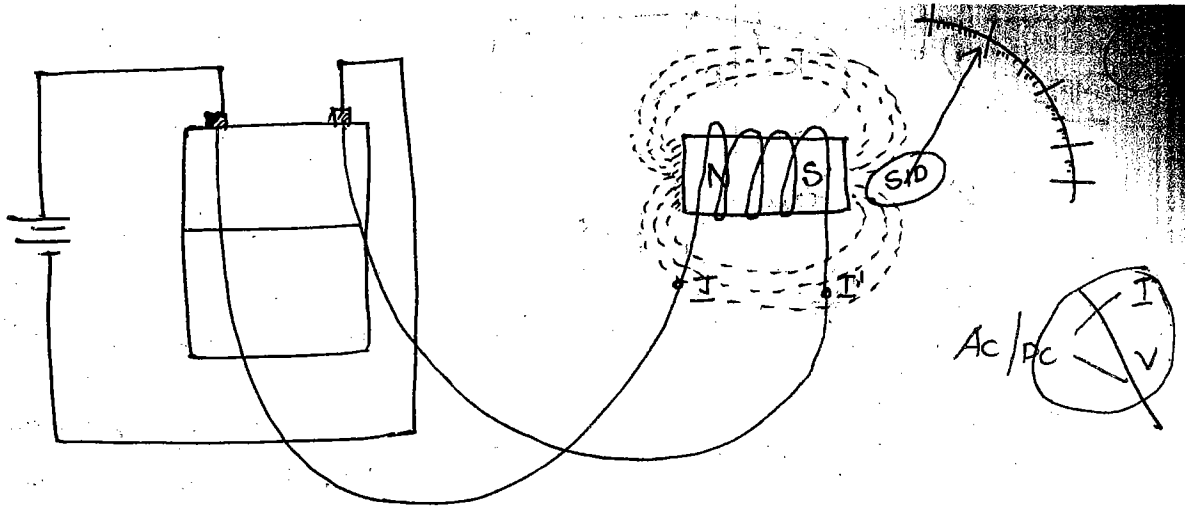

DC  $\begin{cases} I \\ V \end{cases}$

= BIL Sines

### Moving Iron Instruments


SID attracted towards the Magnetised Iron Piece. In this, an <sup>Magnet</sup> [Iron piece] makes the pointer to move (in turn a deflection force) so, it is called Moving

### Iron Instruments

Fixed type

- \* Purpose of fixed coil is to provide magnetic field
- \* MC in Wattmeters have to be short circuited because in Dynamometers the four terminals, two terminals gets short circuited
- \* PMMC are very accurate among, all but the only disadvantage is <sup>it is</sup> suitable for DC. If AC is connected, the pointer won't show deflection exactly and deflects between Initial and final position
- \* MI Instruments suitable for both AC and DC, but when used for DC it is less accurate, sensitive compared to PMMC
- \* In MI meters, the basic principle is Law of Conservation of energy. A coil on Iron piece is equivalent to Inductor. stores energy first and then
- \* Main Working principle of MI Instruments is Self Inductance of fixed coil
- \* By EMMC, we can measure AC, DC Power, Voltage, Current

MC works  
Ovenst's  
Equation

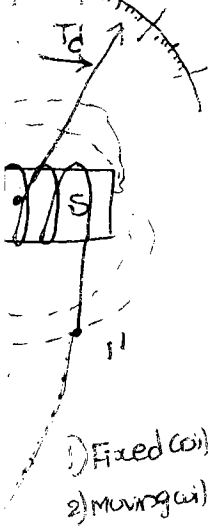


Two coils (Di)

connected,  
piece, then  
ule, to



Then  
let

two magnets

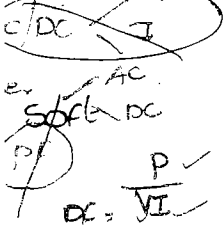

(three errors  
in P, V, I  
... it)

EMMC

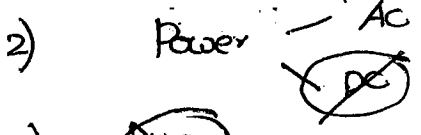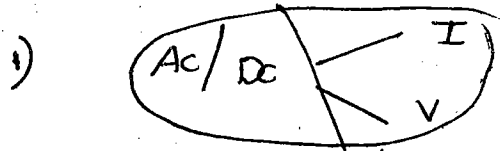


(three types of error)

It is the worst meter still now, to measure AC Power bcz for each & every thing there is an alternative to measure. But for AC power measurement wattmeter is the one & only device used (available)

Mechanism for producing  $T_c$  :-

1) Spring Control :-

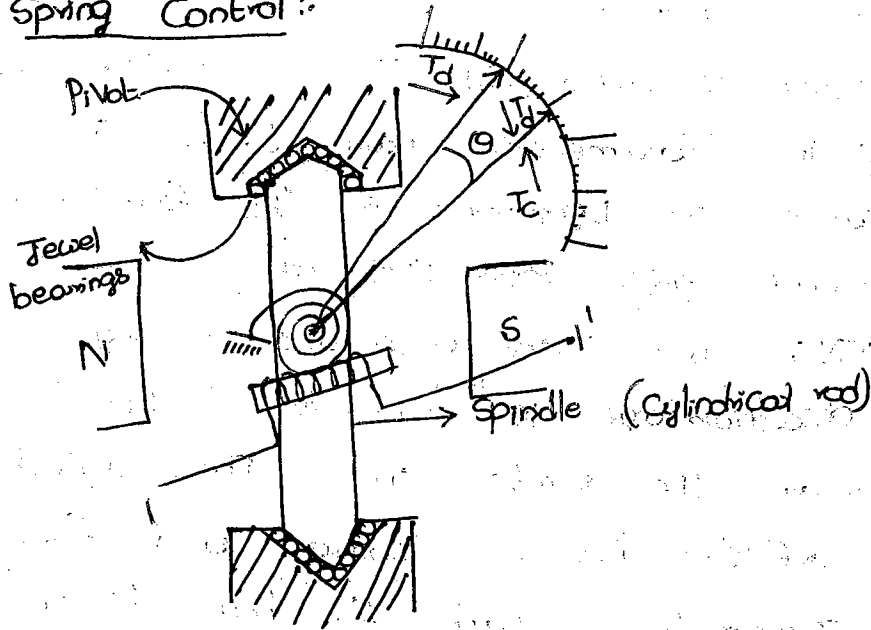

Jewel bearings help to reduce friction between spindle & pivot. Again from one bearing to bearing, friction is reduced by using lubricant like oil, grease

During the action of deflecting torque on the spindle due to rotation of spindle, the spring gets twisted. After the removal of  $I_m$  or  $I_p$  quantity, the spring gets released and controlling torque is generated to restore to its initial position. phosphor-bronze is used for the manufacture of spring.

$$\theta \propto T_d \propto F \propto I$$

$$T_c \propto \text{Spring} \propto \theta$$

$$\theta \propto T_d$$

$$T_c \propto \theta$$

$$\Rightarrow T_c = k_c \theta$$

28/4/12  
(6 to 8:30)

$$K_c = \frac{T_c}{\theta} = \frac{N-m}{deg} \quad \text{or} \quad \frac{N-m}{rad}$$

Advantage:

1\*)  $T_c \propto \theta$  (Linear relation)

Scale is Uniform


2) Both Vertically/horizontally Can be used.

Draw backs:

1) Ageing: As the Age passes, the Springs may lose elasticity property

2) As the temp increases, stiffness decreases, Control Torque decreases,  $T_d$  increases,  $\theta \uparrow$

2) Gravity Control:

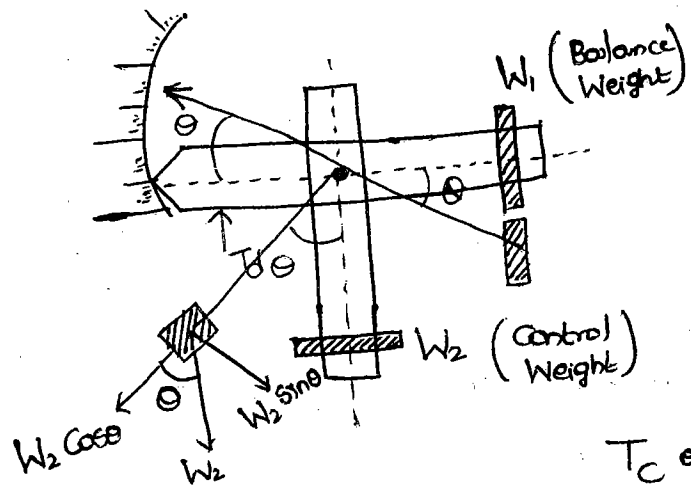

$$T_c \propto W_2 \sin \theta$$

$$T_c \propto \sin \theta$$

$$\theta \propto T_d \propto F \propto I \propto V$$

$W_1$  prevents unnecessary oscillations


- Dis:
- 1) Non-Uniform scale restricted to be
  - 2) Used in Vertical position

- Adv:
- 1) No Ageing
  - 2) Temp. Independent

28/4/12 (6 to 8:30) Mechanism for producing Damping force:


Based on speed Control We have 3 types of damping.

$$\Rightarrow T_c = k_c \theta$$

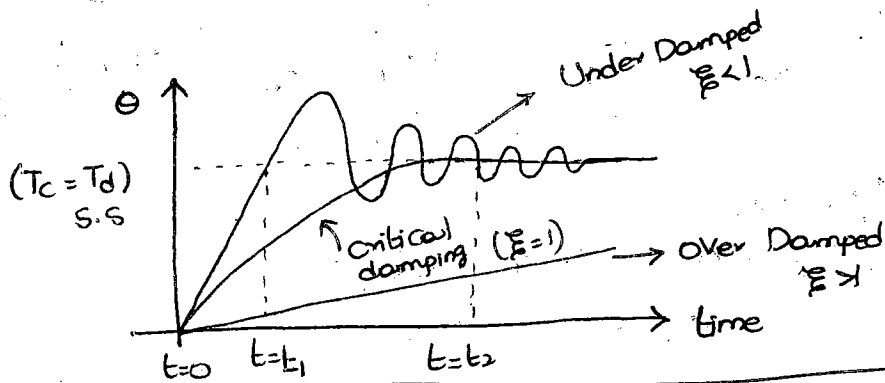

The best design is always "A little bit less than Under Damped System"

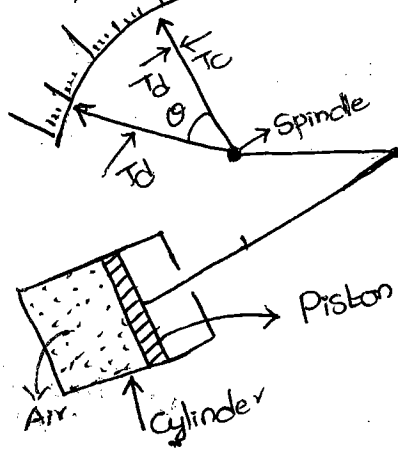1) Air Friction Damping: (90% of Instruments)



The movement of the pointer piston is opposed by the force of the air in cylinder which reduces the speed of pointer

2) Fluid Friction Damping: \* It is better than Air Friction damping because of viscosity

Viscosity of Fluid > Viscosity of Air

\* But we will use it very rarely (less compared to Air Friction Damping)

Drawbacks: ① Maintenance is difficult

3) Eddy Current Damping: (Powerful compared to both)

Order of effectiveness: Eddy > Fluid > Air


order of priority: Eddy > Air > Fluid

It is possible to use eddy current damping where we use permanent magnet

\* Eddy Current Damping is more effective compared to air, fluid friction. But it is not suitable in all electrical instruments as permanent magnet are available

PMMC - Eddy Current ; Dynamometer - Air Friction ; MI - Air

3) Eddy Current Damping:

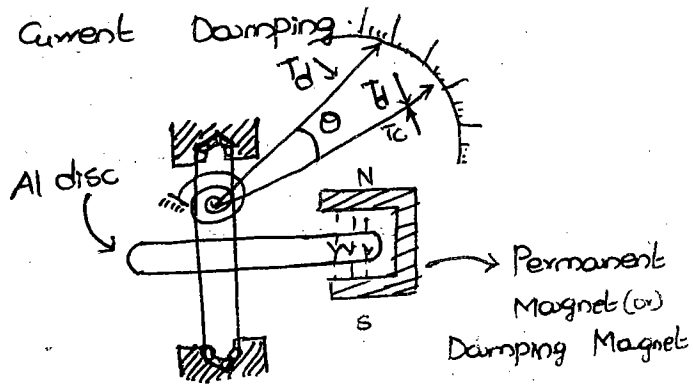


Eddy emf - we can't collect because it is in disc and it is dead emf

\* Faraday's law, Lenz's law are involved in this. As soon as the emf induces, as per Lenz's law effect opposes the <sup>eddy current in disc</sup> causes the current opposes the movement of spindle and comes to rest soon.

\* In case of PM, if we use E.M it gives Variable Magnetic field, then damping varies. But we need constant damping, so we prefer PM.

PMMC Instruments:

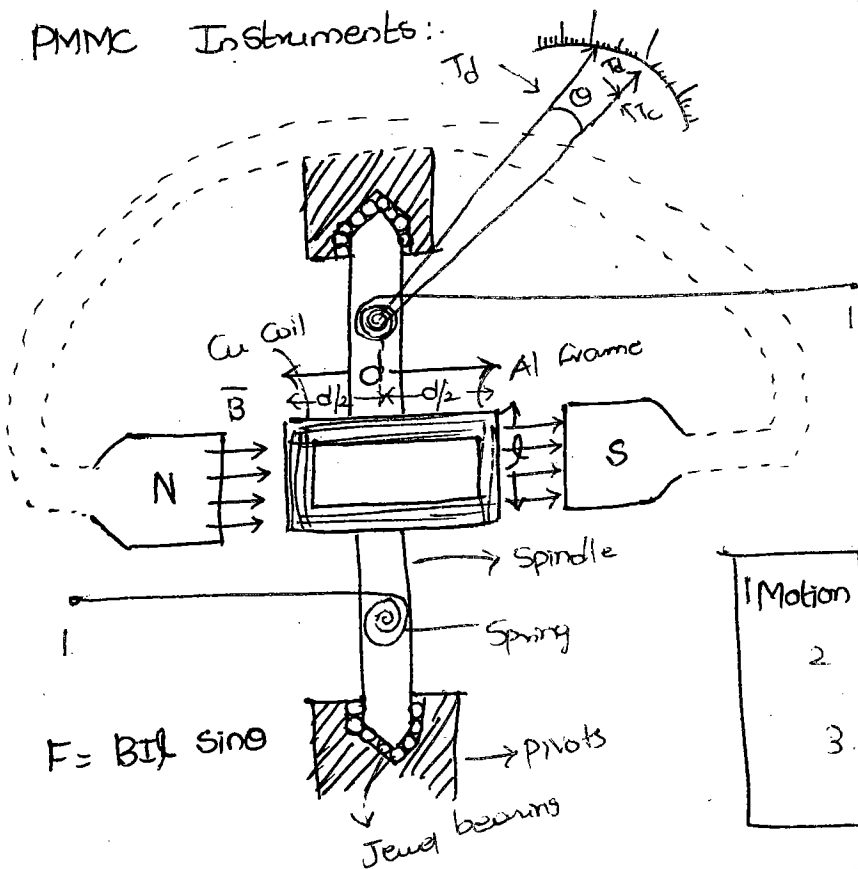

No load current is small in T/F bcz there will be induced emf due to coil on primary which reduces primary voltage there by No load current reduced, otherwise it will be very high

- |           |                      |
|-----------|----------------------|
| btw       |                      |
| 1. Motion | PM & MC              |
| 2.        | Spring Control       |
| 3.        | Eddy Current damping |

\* Current first entering the Spring, next Coil  
 \* There is continuity of conductor inside the spindle (not visible). Current carrying coil in PM, the coil will experience a force. Springs provides Controlling torque. Eddy currents on Al frame produces

\* When a Meter in Working Condition, we send Current  
 after that if spring fails then eff. Spring Const. ( $= k/2$ ),  
 reading will double (i.e., deflection torque doubles) and comes to rest position

\* Inside the meter two mechanical stops are there to prevent the pointer go beyond '0' & Full scale Value

\* While working if two springs are damaged, the pointer goes to full scale value and go back

\* Before measuring, if one spring fails, the pointer will not deflect (For PMMC only)

\* Relation btw Input Current & Output deflection Torque ( $T_d$ )  
 the angle btw Magnetic field & Current carrying coil is  $90^\circ$ .

$$F = BIL$$

{ Two Cond - one turn  
 No. of turns - Coil

$$F/\text{Cond} = BIL$$

$$\begin{aligned} \text{Torque} &= \text{Force} * \text{Per distance} \\ &= (BIL \times d/2) + (BIL \times d/2) \end{aligned}$$

$$T_d = BIL [d] N$$

Deflection Torque,  $T_d = BINA$   $\rightarrow$  (A)

Constant

$$T_d \propto I$$

i.e., Relates Deflection Torque is Linear

$$\begin{aligned} T_d &\propto I \\ &\propto V \end{aligned}$$

$$T_d \propto V$$

change the scale it will be Voltmeter

$$T_c = K_c \theta \rightarrow \text{(B)}$$

At steady state,  $T_c = T_d$

\*

Osc

A

1)

2)

cc

Die

1)

cu

2)

50

Thx

ent

if

\* For

le

3)


W

(cc

sr

30/4/12  
 18:30 - 1:00

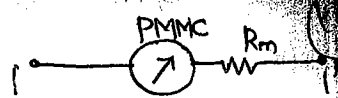\* Eddy Current Damping is used to reduce no. of oscillations at steady state condition



$R_m$  - Moving Coil Resistance

Advantages:

- 1) Scale is (uniform) Linear ( $\because \theta \propto I$ )
- 2) High Accurate and high sensitive, since powerful eddy current damping is used

Disadvantages:

- 1) By using Basic PMMC, we cannot measure high current, since springs are carrying current
- 2) No Maximum Allowable current through Basic PMMC is 50 mA

Through spring only 50 mA enters and the remaining enters at the spring core which is at the end. if we are measuring more than 50 mA.

\* Force direction can be identified by using Fleming's left hand rule

Generator - Fleming's Right hand rule (Two R's, Right)  
 Motor - Fleming's left hand rule (one R, one r)


Fleming left hand rule: Thumb - Force  
 Middle - Current  
 Index - Field

3) By using PMMC instrument we can't measure AC. When we allow AC, the pointer will not deflect (we can't observe deflection, bcz that moves in very small fraction which cannot be detected by eye)

30/4/12  
 (8:30 - 1:00)

Extension Ranges OF PMMC:


PMMC Instrument as Ammeter:

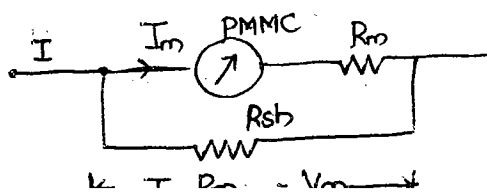


Multiplier

$$R_{sh} = \frac{R_m}{\left(\frac{I}{I_m} - 1\right)}$$

PMMC as Voltmeter:

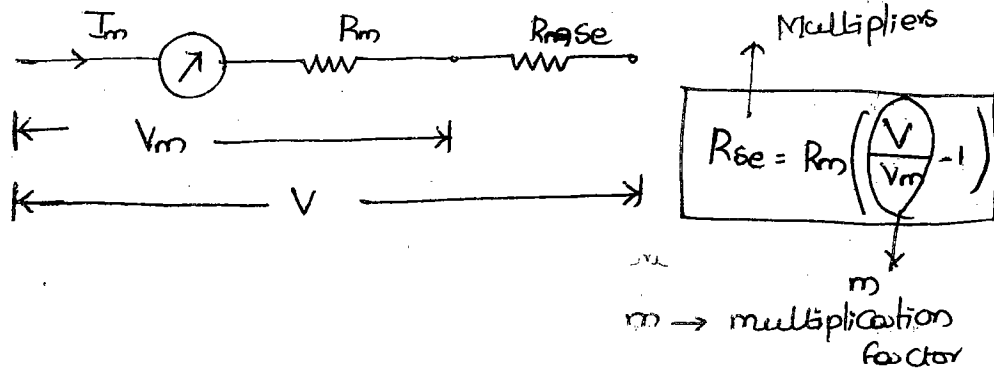

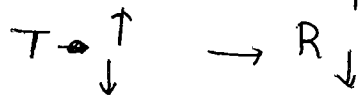\* If  $R_{sh}$  &  $R_{se}$  is made up of Copper (which have a +ve temp coefficient)



So, We don't choose Copper.

We choose a Constant temp. Coefficient Material,  
Manganin & Constantan. (as Multipliers)

1) All Multipliers are made up of


- a) Manganin
- b) Al
- c) Constantan
- d) Any one

Among both Manganin is given 1st priority. Both are brittle materials. Const Manganin is not choosed

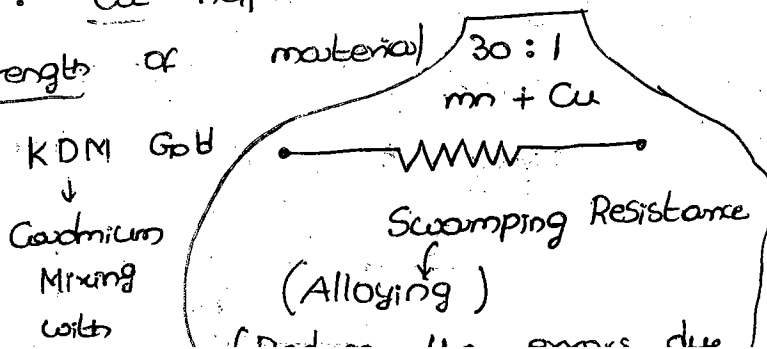- a) More brittle than Manganin
- b) Cost is high
- c) Availability is less compared to Manganin

\* Among Constantan, Manganin  $\rightarrow$  the Constantan gives Accurate results and same time Cost is high

But in practice, We don't use Manganin alone because brittleness come into picture. So, to avoid the brittleness property We use a resistor (made up of mn & Cu). Cu helps in avoiding brittleness and increases strength of material



Errors

- 1) Friction
  - 2) Temperature
  - 3) Friction
  - 4) Hysteresis
  - 5) Stray
- 1) The  
Can't  
dep  
Spin

Fr

\*

\* Friction

To v  
edges

\* In  
more/

\* We

torque  
weng

\* TE  
by


\* Fo  
DC



# Errors in PMMC:

- 1) Frictional errors
- 2) Temp. errors
- 3) Freq. errors
- 4) Hysteresis errors
- 5) Stray Magnetic field errors

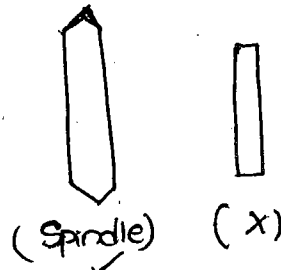1) The errors due to friction can be of low (or) high depending upon the weight of spindle.



Because to reduce the Area of Contact so as to reduce the friction

Torque  $\uparrow \Rightarrow$  Friction  $\downarrow$

Weight on spindle  $\uparrow \Rightarrow$  Friction  $\downarrow$

Friction depends on  $\frac{\text{Torque}}{\text{Weight}}$  Ratio

\*  $\frac{\text{Torque}}{\text{Weight}} \uparrow =$  Moderate

\* Frictional errors are moderate in PMMC Instruments. To reduce the frictional errors by providing a sharp edges to spindle and Jewel bearings in the Grooves

\* In any electrical Instrument, the frictional error is more/less can be decided depending upon  $\frac{\text{Torque}}{\text{Weight}}$  Ratio.

\* We prefer always high  $\frac{\text{Torque}}{\text{Weight}}$  Instruments, as the  $\frac{\text{Torque}}{\text{Weight}}$  is more, frictional errors are less.

\* Temperature errors: The temp. errors can be reduced by introducing Swamping Resistance


\* Frequency Errors is absent in PMMC (meter since DC measurement).

$$T_d = BINA$$

$$\begin{aligned} 1) \oint E \cdot dl &= \frac{1}{\epsilon_0} \int \rho \cdot dl \\ 2) \oint B \cdot dl &= \mu_0 \int I \cdot dl \\ 3) \oint E \cdot dl &= 0 \Rightarrow \text{KVL} \end{aligned}$$

\* The hysteresis error can be reduced by providing Aluminium frame in the moving system. Since Aluminium has less hysteresis loops so that the diff. b/w two Magnetic fields can be neglected.

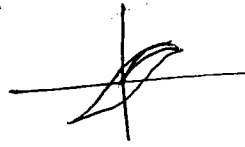\* We cannot eliminate Hysteresis errors, but can reduce them



5) Stray Magnetic field is error:

The stray Magnetic field error is less due in PMMC. Since, a strong Magnetic field is available inside the meter.

\* As all the errors can be minimised in PMMC instruments so that it is high accurate, high sensitive instrument.

Note: 1) By using PMMC instrument, we can measure DC current (or) Voltage but not AC voltage, power

2) PMMC will always Average Value.

1) The deflection Torque of an Ammeter varies as square of the current passing through it. If a current of 5A produces a deflection of 90°. What the deflection occur for a current of 3A, if the instrument is controlled.

Sol.  $T_d \propto I^2$

$\Rightarrow \theta \propto I^2$

i.e.,  $\frac{\theta_2}{\theta_1} = \left(\frac{I_2}{I_1}\right)^2$

$= \left(\frac{3}{5}\right)^2 = \frac{9}{25}$

$\theta_2 = 90 \times \frac{9}{25} = 32.4^\circ$

If the instrument is a Gravity controlled

2. A  
The  
Spiral  
to  
a

3. The  
defl  
1) -  
Shur  
2) :  
Res

$$\frac{\sin \theta_2}{\sin \theta_1} = \left( \frac{I_2}{I_1} \right)^2$$

$$\sin \theta_2 = \left( \frac{9}{25} \right) \Rightarrow \theta_2 = 21.1^\circ$$

2. A PMMC Instrument has dimensions  $15\text{mm} \times 12\text{mm}$ . The flux density in the Air gap is  $1.8 \text{ web/m}^2$ . The Spring Constant is  $0.14 \text{ } \mu\text{N}\cdot\text{m}/\text{rad}$ . Determine the no. of turns reqd to produce angular deflection of  $90^\circ$  when current of  $5\text{A}$  flowing through coil.

$$\theta = \frac{BINA}{k_c}$$

$$\Rightarrow N = \frac{k_c \cdot \theta}{BIA}$$

$$= \frac{(0.14 \times 10^{-6}) \left( 90 \right)^{\frac{\pi}{2}}}{(1.8 \times 10^{-6}) (5) \times (15 \times 12) \times 10^{-6}}$$

$$= 135.74 \approx 136$$

3. The pointer of MC Instrument gives a full scale deflection of  $20\text{mA}$  when the potential diff. is  $400\text{mV}$

1) The instrument is extended to  $200\text{A}$ . Then the shunt resistance reqd. is

2) If the <sup>same</sup> instrument extended to  $1000\text{V}$ . Series Resistance reqd. is

$$1) R_{sh} = \frac{R_m}{\left( \frac{I}{I_m} - 1 \right)} = \frac{\frac{400 \times 10^{-3}}{20 \times 10^{-3}}}{\left( \frac{200}{20 \times 10^{-3}} - 1 \right)}$$

$$= \frac{20}{10^4 - 1} = \frac{20}{9999} = 2\text{m}\Omega$$

$$2) R_{se} = R_m \left( \frac{V}{V_m} - 1 \right) = 20 \left( \frac{1000}{400 \times 10^{-3}} - 1 \right)$$

$$= 49.98\text{ k}\Omega$$

4. What is the Value of  $R_{se}$  reqd. to extend (0-200V) Voltmeter having Sensitivity of  $2000 \Omega/V$  is to be extended to (0-2000)V

$$\Rightarrow R_{se} = R_m \left( \frac{V}{V_m} - 1 \right)$$

$$= \frac{200}{5 \times 10^{-4}} \left( \frac{2000}{200} - 1 \right)$$

$$= 3600 \Omega$$

$$R_m = 200 \times 2000$$

$$= 400 \text{ k}\Omega$$

$$(or) 400 \text{ k} \left( \frac{2000}{200} - 1 \right) = 3.6 \text{ k}\Omega$$

5. A Moving Coil Voltmeter with a resistance of  $20 \Omega$  gives full scale deflection of  $120^\circ$  when a potential difference of  $100 \text{ mV}$  is applied across it.

$$(R_m = 20 \Omega, \theta = 120^\circ, V_m = 100 \text{ mV})$$

Moving Coil has dimensions of  $30 \text{ mm} \times 25 \text{ mm}$  and is wound with 100 turns. The spring constant is  $0.375 \times 10^{-6} \text{ N}\cdot\text{m}/\text{degree}$ . Find the flux density in the air gap and find diameter of Cu. Coil.

$$P = 1.7 \times 10^{-8} \text{ N}\cdot\text{m}, N = 100, \omega = 750 \times 10^{-6} \text{ mm}^2$$

$$R = \frac{Pl}{A} \quad \left\{ \begin{array}{l} k_c = 0.375 \times 10^{-6} \text{ N}\cdot\text{m}/\text{degree} \\ \theta = \frac{BINA}{k_c} \Rightarrow B = \frac{\theta \cdot k_c}{INA} \end{array} \right.$$



$$\star l = 2(l+d) \times 100$$

$$120 \times \frac{\pi}{6}$$

$$20 = \frac{(1.7 \times 10^{-8}) (2) \left( \frac{100 \times 10^{-3}}{20} \right) \times 100 \times 750 \times 10^{-6}}{A}$$

$$= \frac{(1.7 \times 10^{-8}) \times 11}{A}$$

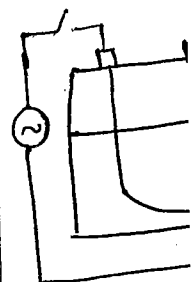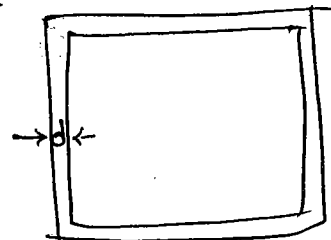
$$\Rightarrow A = \frac{1.7 \times 10^{-8} \times 11}{20}$$



For  
is  
Max  
reqd  
Cor  
Cor  
Jr

# MI Instruments (Moving Iron)

- a) Attraction Type
- b) Repulsion Type

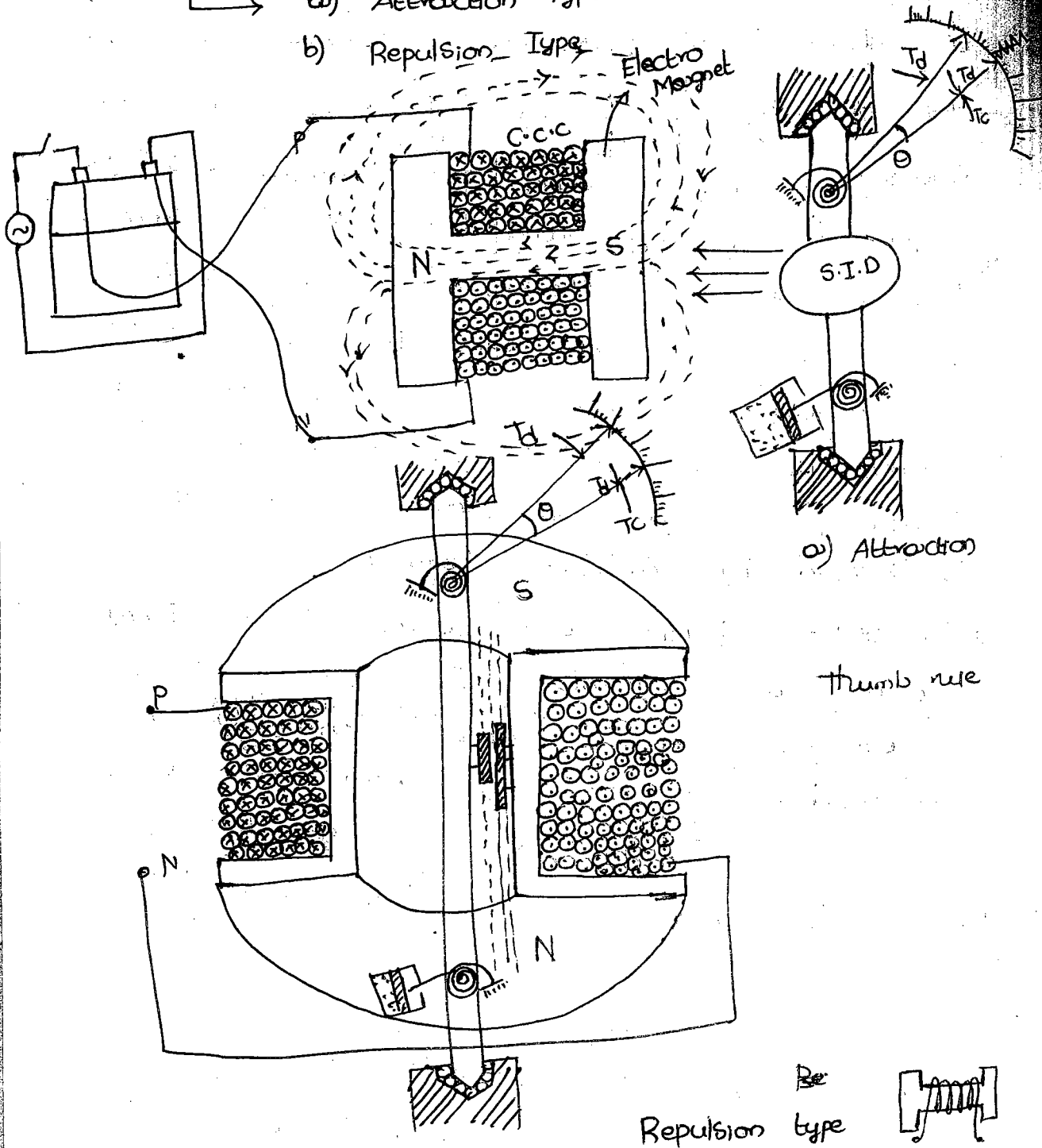

Thumb rule

Re  Repulsion type

Iron piece gets magnetised due to the winding which is carrying current. So, it becomes like an electro Magnet. It attracts the S.I.D which produces read deflection torque then the pointer moves. Here, Control torque is produced by the Spring Control. Damping torque is produced by the Air friction Damping.

In measuring AC, if pos -ve half occurs, the polarities change to (S to N). Thus, it

0 2000

2000

2

200

200

and


is

in

0.6




Repulsion type:

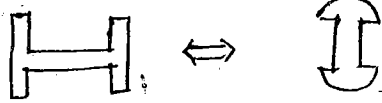It's core is similar to that type of Attraction type (Just rotate by 90° i.e., ). When unknown quantity is passed through P, N terminals, it will get magnetised. By using Thumb rule, N, S are identified. Lines of Force of Attraction 'passes' from South to North. In the path of them, two Iron rods (one fixed, other movable is present) as force of repulsion exists between them and deflects the pointer. Controlling Torque is provided with Spring Control. Damping torque is provided by Air friction Damping

\* In PMMC, Springs carry currents. In MI, Springs does not carry currents. If one of the Springs is damaged, deflection (Control torque reduces to half, pointer goes from final reading to zero). If both springs damaged, pointer reads Full scale, and don't goes back to zero


\* Self Inductance of <sup>Fixed</sup> Coil is the working principle

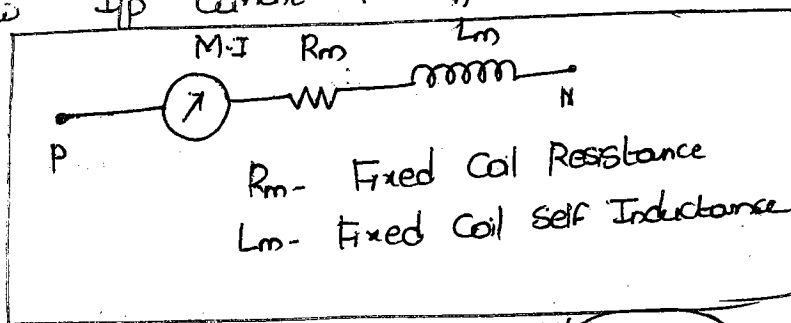\* Relation btw I/p Current & o/p deflection torque



\*  $\phi$  links with its own no. of turns then 'e' is induced. By the time another current is waiting.

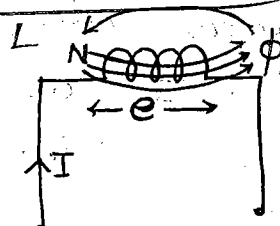Inductor will not allow sudden change of current until flux linking is changed



\* Time Varying Current produces time Varying flux

$$L = N\phi$$

\* St  
 \* N  
 (la  
 \* [J  
 For  
 ope  
 t

\*  
 \*

(dt -

Where c  
 Fro  
 this  
 so

En

So,  $V_L \propto \frac{dI}{dt} \Rightarrow \boxed{V_L = L \cdot \frac{dI}{dt}} \rightarrow \text{Transition}$

At steady state,  $V_L = 0$

So, it acts as short ckt (bcz current will not vary w.r.t time)  $\frac{dI}{dt} = 0$

- \* Never open the Inductor when it is storing Energy, (leads to  $\infty$  Voltage)
- \* Never short the Capacitor when it is storing Energy (leads to  $\infty$  current)
- \* [Inductor <sup>choke</sup> in tube light helps to raise the Voltage from 230v to 2500v (approx). The starter helps to open the Inductor, in turn leading to  $\infty$  Voltage, then it will glow]

\* Inverter like a Capacitor

\* Chopper  $\rightarrow$  Inductor

$$L = \frac{N\phi}{I} \Rightarrow d(LI) = d(N\phi)$$

$$\Rightarrow I \times \left( L \frac{dI}{dt} + I \frac{dL}{dt} \right) = N \frac{d\phi}{dt}$$

(dt - time taken for switch closing, multiply both sides by I)

$$\Rightarrow I \times dt \left( L \frac{dI}{dt} + I \frac{dL}{dt} \right) = e \times I \times dt$$

$$\Rightarrow \boxed{LI dI + I^2 dL = dW} \rightarrow \text{As small time, } dW = e I dt$$

Where  $dW = \text{Total electrical energy consumed by fixed coil / Inductor from the source in } dt \text{ sec}$

this much electrical energy is converted into Mech. energy so that it will do some useful work done

$$\therefore \text{Mech. Work done in } dt \text{ (sec)} = T_d \cdot d\theta \rightarrow \textcircled{2}$$

Energy stored in Inductor in 'dt' seconds:

$$= \text{Energy stored in } (t+dt) - \text{Energy stored in } t \text{ sec}$$

$$= \frac{1}{2} (L+dL) (I+dI)^2 - \frac{1}{2} LI^2$$

$$\begin{aligned}
 &= \frac{1}{2} (L + dL) (I^2 + dI^2 + 2I dI) - \frac{1}{2} L I^2 \\
 &= \frac{1}{2} (L I^2 + 2IL dI + dL I^2 + 2I dI) - \frac{1}{2} L I^2 \\
 &= IL dI + \frac{I^2 dL}{2} \rightarrow (3)
 \end{aligned}$$

Electrical energy = Mech. Energy + change in stored energy

(Law of Conservation of energy)

$$\Rightarrow LI dI + I^2 dL = T_d \cdot d\theta + LI dI + \frac{I^2}{2} dL$$

$$\Rightarrow \frac{1}{2} I^2 dL = T_d \cdot d\theta$$

$$\Rightarrow T_d = \frac{1}{2} I^2 \left( \frac{dL}{d\theta} \right)$$

$$T_d \propto I^2$$

So, MI got scale as Non-Linear

Spring Control:  $T_c = k_c \theta$

$$\frac{1}{2} I^2 \left( \frac{dL}{d\theta} \right) = k_c \theta \quad (\text{At equilibrium, } T_d = T_c)$$

$$\theta = \frac{1}{2} \frac{I^2}{k_c} \left( \frac{dL}{d\theta} \right)$$

\* Air Friction Damping is used to reduce no. of oscillations.

### Advantages:

1. We can measure both AC & DC
2. We can avoid current through the  Springs

### Disadvantages:

1. Non-Linear scale

It is Less Accurate less sensitive since Air friction Damping Instrument is used.

\* We cannot measure high currents using PMMC because  Springs are damaged. In MI also we

Magn  
leads  
(M/c)

01/5/12  
(8:30-1:00) f.  
as

Ra

of

2. A

240

Find

Full

3. the


De

Find

of



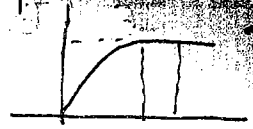Magnetic Saturation Causes a Serious problem. It leads to permanent magnet (M/c will not be under our control)



1. The Inductance of M.I Ammeter is assumed as  $L = (10 + 10\theta - 3\theta^2) \mu\text{H}$ . Where  $\theta$  is the deflection in Radians. Determine the deflection in degree for a current of 8A.  $k_c = 10 \times 10^{-6} \text{ N}\cdot\text{m}/\text{degree}$

$$L = (10 + 10\theta - 3\theta^2) \mu\text{H}$$

$$\frac{dL}{d\theta} = (10 - 6\theta) \times 10^{-6}$$

$$T_c = T_d$$

$$k_c \theta = \frac{1}{2} I^2 \left( \frac{dL}{d\theta} \right)$$

$$\Rightarrow 10 \times 10^{-6} \times \theta = \frac{1}{2} (8)^2 \times (10 - 6\theta) \times 10^{-6} \Rightarrow \theta = 95.7^\circ$$

2. A Moving Iron Ammeter produces a full scale of 240  $\mu\text{N}\cdot\text{m}$  with deflection of  $120^\circ$  at a current of 10A. Find the Rate of Change of Self Inductance at Full scale is \_\_\_\_\_

$$T_d = \frac{1}{2} I^2 \frac{dL}{d\theta}$$

$$\frac{dL}{d\theta} = \frac{2 T_d}{I^2} = \frac{2 \times 240 \mu\text{N}\cdot\text{m}}{(10)^2}$$

$$= 4.8 \mu\text{H}/^\circ \text{ degree}$$

3. The following figures gives the relation btw deflection, Inductance

Deflection	20°	30°	40°	50°	60°	70°	80°	90°
L ( $\mu\text{H}$ )	335	345	355.5	366.5	376.5	385	391.3	396


Find the Current & Torque reqd to give a deflection of  $45^\circ$ .  $k_c = 0.4 \times 10^{-6} \text{ N}\cdot\text{m}/\text{degree}$

$$k_c \theta = \frac{1}{2} I^2 \frac{dL}{d\theta}$$

$$(0.4 \times 10^{-6}) \times 45^\circ = \frac{1}{2} (I^2) \left( \frac{110}{10} \right)$$

$$\Rightarrow I = 1.12 \text{ mA}$$

$$T_d = \frac{1}{2} (I^2) (1) =$$

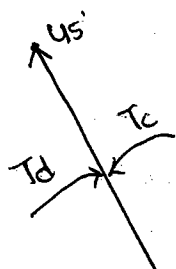

If  $T_c$  is found,  $T_d$  is also same

$$T_c = k_c \times \theta$$


$$= (0.4 \times 10^{-6}) \times 45 = 18 \times 10^{-6} \text{ N}\cdot\text{m}$$

$$T_d = \frac{1}{2} (I^2) \frac{dL}{d\theta}$$

$$(18 \times 10^{-6}) = \frac{1}{2} (I^2) (1.1 \times 10^{-6})$$

$$I = 5.7 \text{ A}$$

Extension of M.I. Instruments:

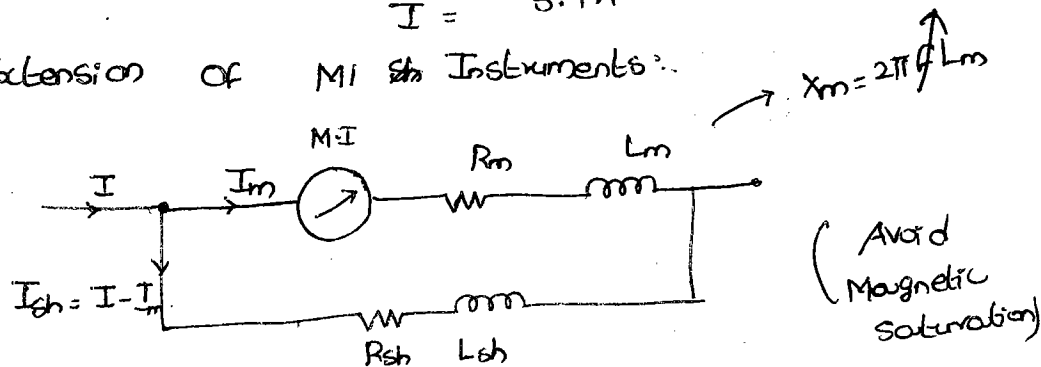

(M.I. Instrument as Ammeter)

In order to bypass higher currents we keep a resistor in shunt 'R<sub>sh</sub>' so as to bypass high currents. But due to L<sub>m</sub>, frequency component exists. Thereby whenever there is a change in frequency, R<sub>m</sub> changes and there by I<sub>m</sub> also changes. So, in order to nullify this problem, we keep 'L<sub>sh</sub>' in series with 'R<sub>sh</sub>'

$$I = \frac{V}{Z} \text{ Const.} \Rightarrow I \propto \frac{1}{Z}$$

$$\Rightarrow \frac{I_1}{I_2} = \frac{Z_2}{Z_1} \Rightarrow \frac{I_m}{I_{sh}} = \frac{\sqrt{R_{sh}^2 + (\omega L_{sh})^2}}{\sqrt{R_m^2 + (\omega L_m)^2}}$$

$$\frac{I_m}{I_{sh}} = \frac{R_{sh}}{R_m} \frac{\sqrt{1 + \left(\frac{\omega L_{sh}}{R_{sh}}\right)^2}}{\sqrt{1 + \left(\frac{\omega L_m}{R_m}\right)^2}}$$

$$\frac{\omega L_{sh}}{R_{sh}} = \frac{\omega L_m}{R_m} \Rightarrow \frac{L_{sh}}{R_{sh}} = \frac{L_m}{R_m}$$

$$\Rightarrow Z_{shunt} = Z_{meter}$$

In case of basic M.I. Ammeter we have to connect a shunt will across basic meter in such a way that the

Constant of the shunt is,  $\boxed{\frac{L_m}{R_m} = \frac{L_{sh}}{R_{sh}}}$ . Then the meter

is independent of frequency

$\odot$   $T = \frac{L}{R} = \frac{H}{\Omega}$   
 $= RC = \Omega \cdot F$


But we write units as seconds, how?

$$V_L = L \frac{dI}{dt} \Rightarrow L = \frac{V \times dt}{dI}$$

$$= \frac{\cancel{V} \times \text{Sec}}{\cancel{I}}$$

$$T = \frac{L}{R} = \frac{R \text{ sec}}{R} = \text{Sec}$$

M-I instrument as voltmeter:

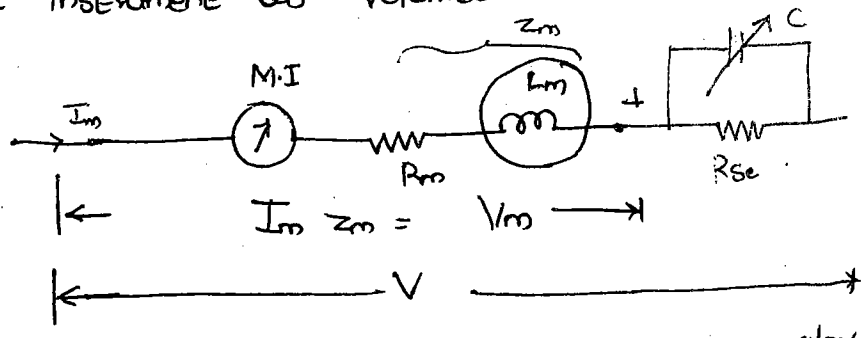

1) We have to choose a value of capacitor so as to nullify the frequency of  $L_m$

$$2) \quad Z = (R_m + j \times X_m) + \left( R_{se} \parallel \frac{1}{j\omega C} \right)$$

$$= (R_m + j \times X_m) + \left( \frac{R_{se}}{R_{se} + \frac{1}{j\omega C}} \right)$$

$$= (R_m + j \times X_m) + \left( \frac{R_{se}}{R_{se} j\omega C + 1} \right) \left( \frac{1 - j R_{se} \omega C}{1 - j R_{se} \omega C} \right)$$

$$= (R_m + j \times X_m) + \left( \frac{R_{se} - j R_{se}^2 \omega C}{1 + \omega^2 C^2 R_{se}^2} \right)$$

$$Z = (R_m + j \times X_m) + \frac{R_{se} - j R_{se}^2 \omega C}{1 + \omega^2 C^2 R_{se}^2}$$

$$= (R_m + R_{se}) + j \times (X_m - R_{se}^2 \omega C)$$

$$= (R_m + R_{se}) + j \times (L_m - R_{se}^2 C)$$

$$L_m - R_{se}^2 C = 0$$

$$\Rightarrow C = \frac{L_m}{R_{se}^2}$$

N-m

Lm

ratio)

due

or

d

fy

b)<sup>2</sup>  
=

next as  
the  
time

In case of MI Voltmeter, we have to connect a capacitor across  $R_{se}$  in such a way that the capacitive reactance is cancelled out by inductive reactance of the meter. Then the meter is independent of frequency.

$$C = \frac{0.41 L_m}{R_{se}^2}$$

Errors in MI instruments:

1. Frictional error
2. Temp error
3. Freq Error
4. Hysteresis error
5. Stray Magnetic field error

1. Frictional error: The frictional error is more in MI compared to PMMC. Since the torque/weight ratio is small/less.

MC	PMMC	MI
↑ Torque	↓	
↑ Weight	↓	

2. Temp error: The temp. error is more in MI instrument compared to PMMC by using Swamping Resistance in basic meter.

3. Freq. error: The frequency error is more in MI compared to PMMC since Ac measurement.

We cannot eliminate PMMC freq. errors in M.I. but we can reduce by using above Arrangements.

4. Hysteresis error: The hysteresis error is more in MI instrument compared to PMMC. Since directly Iron disc by used in the Moving System.

\* We cannot eliminate Hysteresis error in MI Instru-  
-ments

5. Stray Magnetic field error: The Stray Magnetic field is more compared to PMMC since, weak Magnet is available in meters.

All the errors are more compared to PMMC so that it is less Accurate, less sensitive can measure Ac/dc.

Cur  
2.  
Co  
1. A  
Ind  
Wh  
indep  
x Fr  
2. A  
F  
ie  
Or

Current / Voltage but not power

2. In case of AC, the meter will read RMS Value. In case of DC, the meter will read Avg. Value

1. A 250V, MI Voltmeter has a coil resistance of 500Ω and the Inductor of 1 Henry with a series resistance of 2kΩ. What is the value of Capacitance reqd to make independent of frequency.

$$C = 0.41 \frac{L_m}{R_{se}^2} = 0.41 \times \frac{1H}{(2 \times 1000)^2} = \frac{0.41}{4 \times 10^6} = 0.1 \mu F$$

2. A Moving Iron Voltmeter reads correctly on 250V DC if 250 V AC, 50 Hz supply is applied. Then what is the scale reading. The instrument coil has 500Ω and Inductance of 1 H with Series Resistance of 2kΩ

$$C = 0.41 \times \frac{1H}{(2 \times 10^3)^2} = 0.1 \mu F$$



$$I = \frac{250}{500} = 0.5A$$

$$\frac{250}{2} = \sqrt{\frac{50}{2500 + (j(50))}}$$

$$\frac{250}{2} =$$

$$I_{dc} = \frac{250}{2500} = 0.1A$$
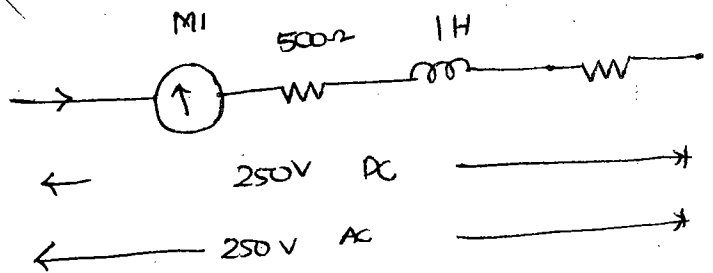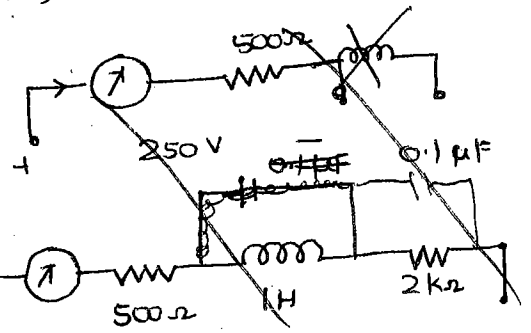
$$I_{ac} = \frac{250}{\sqrt{(2500)^2 + (2\pi \times 50 \times 1)^2}} = 0.0992A$$




$$(0.1)^2 \rightarrow 250V$$

$$(0.992)^2 \rightarrow ?$$

$$250 \times 246.11V$$

To avoid this error, we go for Capacitor

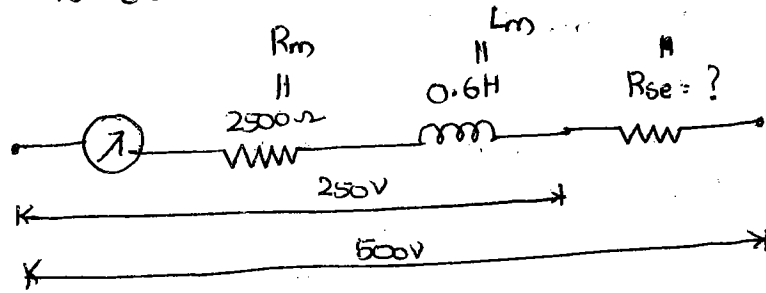3. A MI Voltmeter has an Inductance of  $0.6 \text{ H}$  with a Resistance of  $2,500 \Omega$  with a Full scale deflection corresponding to  $250 \text{ V}$ . It is meant to operate at  $50 \text{ Hz}$ . What is the  $R_{se}$  to read increase the range to  $500 \text{ V}$



$$I = \frac{250}{\sqrt{(2500)^2 + (0.6 \times 2 \times \pi \times 50)^2}}$$

$$= 0.0997 \text{ A}$$

$$0.0997 = \frac{500}{\sqrt{(2500 + R_{se})^2 + (0.6 \times 2 \times \pi \times 50)^2}}$$

$$0.0997 = \frac{500}{\sqrt{(2500 + R_{se})^2 + (35530.5)^2}}$$

$$\Rightarrow \frac{500}{0.0997} = \sqrt{(2500 + R_{se})^2 + (35530.5)^2}$$

$$R_{se} = 2511.50 \Omega$$


EMMC (Electro Magnet M.C)

\* It is a combination of PMMC & MI  
 \* In this, the moving coil will be there and electromagnets are there.

\* It consists of two coils i.e., four terminals (M, L, C, V)

\* The working principle is "Mutual Induction"

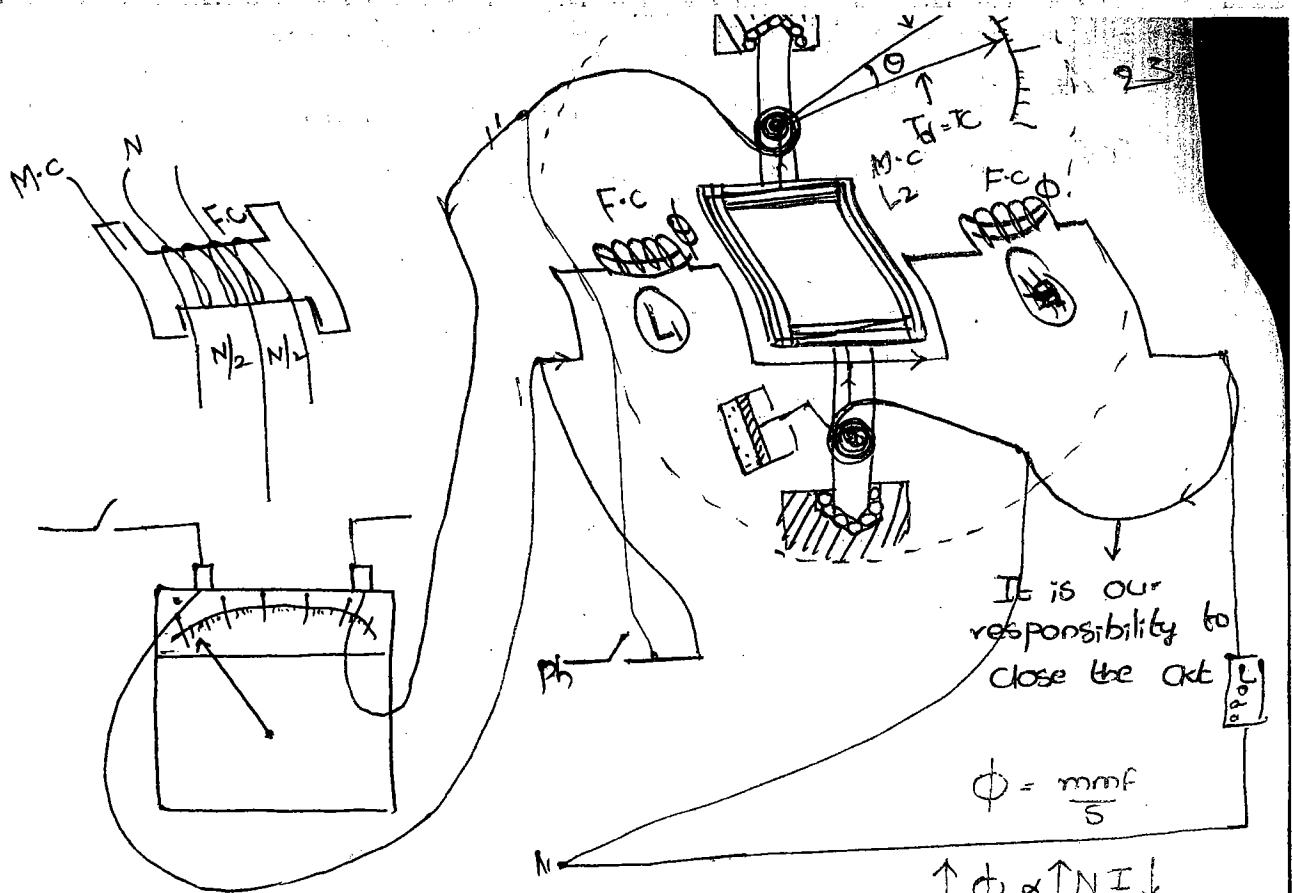\* Among four terminals, two are to be short circuited



\* Scale is Non-Linear.

\* Springs Carry Current

\* In PMMC, eddy Current Damping is used as there are strong permanent Mag. field. But here as electro magnets are there, we use Air Friction damping

\* Two Coils are Connected in series.

\* If 'I' increases, as Spring Carry Currents, they get damage. In order to increase 'I' and to keep springs safe we just go by increasing No. of turns.

\* Current only responsible to produce deflecting

Torque

Relation btw I/p Current & o/p deflecting Torque

Self Inductance of Fixed Coil =  $L_1$

Self Inductance of Moving Coil =  $L_2$

Mutual Inductance =  $M$

$$L_{eq} = L_1 + L_2 + 2M$$

$$\Rightarrow T = \frac{1}{2} I^2 \frac{dL_{eq}}{d\theta}$$

By increasing No. of turns

$$T_d = \frac{1}{2} I^2 \frac{d}{d\theta} (L_1 + L_2 + 2M)$$

As it works on principle of Mutual Induction, the self inductances are negligible

$$T_d = \frac{1}{2} I^2 \cdot \frac{dM}{d\theta}$$

$$\boxed{T_d = I^2 \frac{dM}{d\theta}} \rightarrow (A) \quad T_d \propto I^2$$

So, its scale is Non-Linear

Spring Control:  $\boxed{T_c = k_c \theta} \rightarrow (B)$

At steady state,

$$T_c = T_d \Rightarrow k_c \theta = I^2 \frac{dM}{d\theta}$$

$$\Rightarrow \boxed{\theta = \frac{I^2}{k_c} \frac{dM}{d\theta}}$$

$$\Rightarrow \theta \propto I^2$$

$$P = VI \cos\phi$$

EMMC  $\rightarrow T_d = I^2 \frac{dM}{d\theta}$  (there is a provision to separate)  $\theta \propto I^2$   $\propto V^2$

MI  $\rightarrow T_d = \frac{1}{2} I^2 \frac{dL}{d\theta}$

Hence can EMMC used for the Power measurement

(No provision to split as there is only one coil)

$$* T_d = I_1 I_2 \frac{dM}{d\theta}$$

Let  $I_1 = I_{m1} \sin \omega t$ ,  $I_2 = I_{m2} \sin(\omega t - \phi)$

$$T_d = \frac{1}{2\pi} \int_0^{2\pi} I_1 I_2 \frac{dM}{d\theta} d(\omega t)$$

$$T_d = \frac{1}{2\pi} \int_0^{2\pi} I_{m1} \sin \omega t \cdot I_{m2} \sin(\omega t - \phi) \frac{dM}{d\theta} d(\omega t)$$

$$T_d = \frac{1}{2\pi} \left\{ \frac{I_{m1} I_{m2}}{2} \right\} \frac{dM}{d\theta} \int_0^{2\pi} \sin \omega t \sin(\omega t - \phi) d\omega t$$

$$\boxed{T_d = \frac{1}{2} I_1 \cdot I_2 \cos\phi \frac{dM}{d\theta}}$$

$$I_1 = \frac{I_{m1}}{\sqrt{2}}, \quad I_2 = \frac{I_{m2}}{\sqrt{2}}$$

II  
II  
I  
II  
V

$$\left( \frac{V_p}{R} \right)$$

(b  
\* Mo  
Koc  
\* F  
Co



$$T_d = I_1 I_2 \cos \phi \frac{dM}{d\theta}$$

$$P = VI \cos \phi$$

If two diff currents with some phase,  $T_d = I_1 I_2 \cos \phi \frac{dM}{d\theta}$


If two diff currents with no phase,  $T_d = I_1 I_2 \frac{dM}{d\theta}$

If two currents are same with no phase,  $T_d = I^2 \frac{dM}{d\theta}$

If we know can make  $I_1$  as  $I$  and  $I_2$  as

$V$  we obtained **Wattmeter**

For this

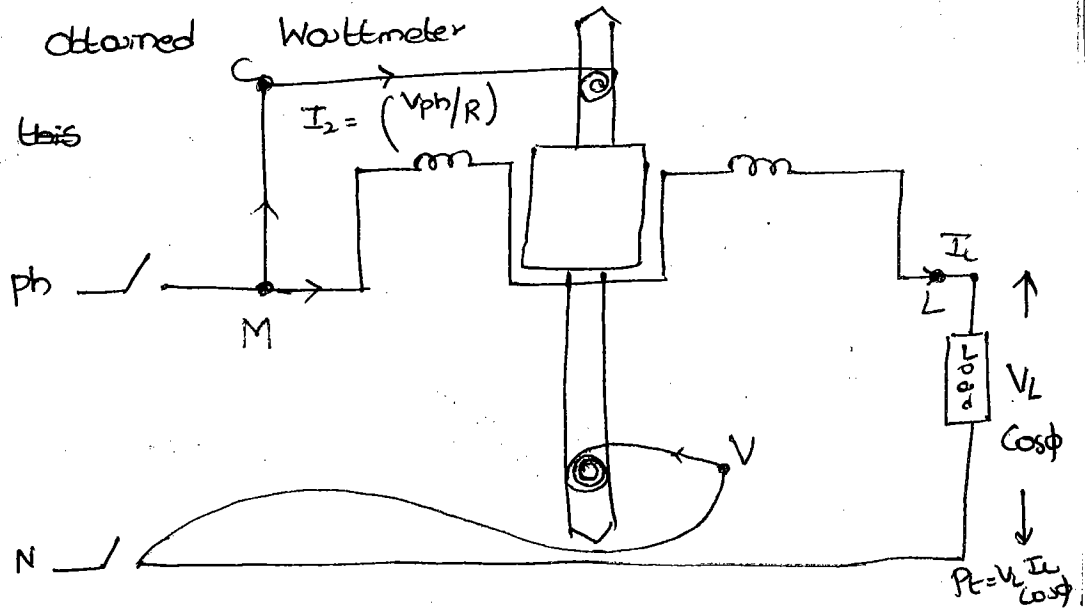

$I_L$  will be equal to  $I_1$  and  $I_2 =$

$$\left( \frac{V_{ph}}{R} \right)$$

$$T_d = I_2 \cdot \frac{V_{ph}}{R} \cos \phi \frac{dM}{d\theta}$$


$$= I_2 \cdot V_{ph} \cos \phi$$

M - Mains, L - Load, C - Common, V - Voltage



Make MC short always

(because we have to split the current always.)

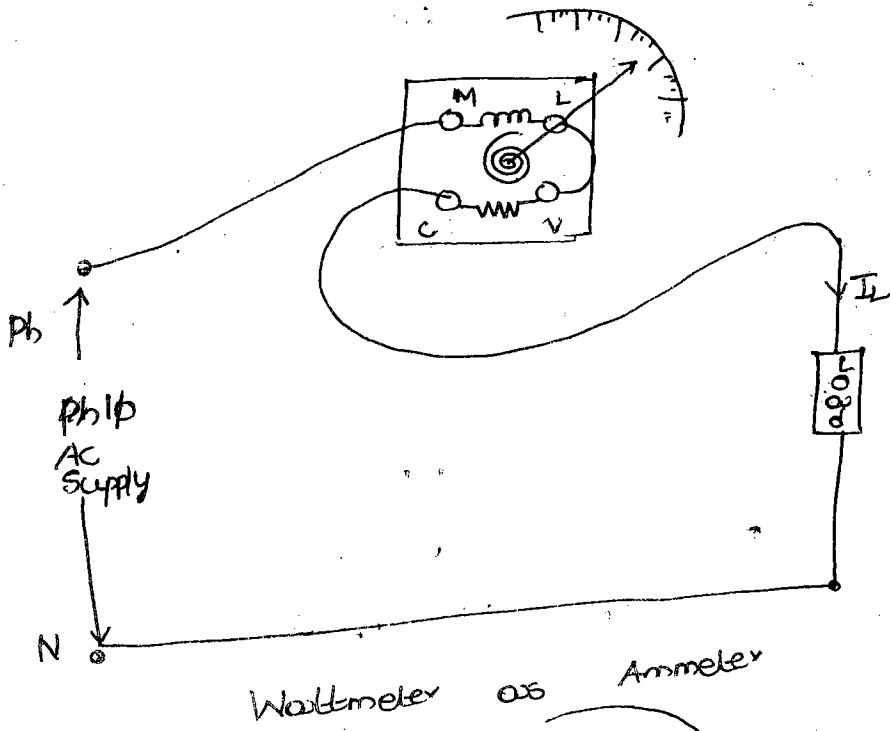- \* Moving coil is connected across voltage. So, it is known as Voltage / pressure coil
- \* Fixed coils are connected in series to load, they carry load current. So, they are called Current coil



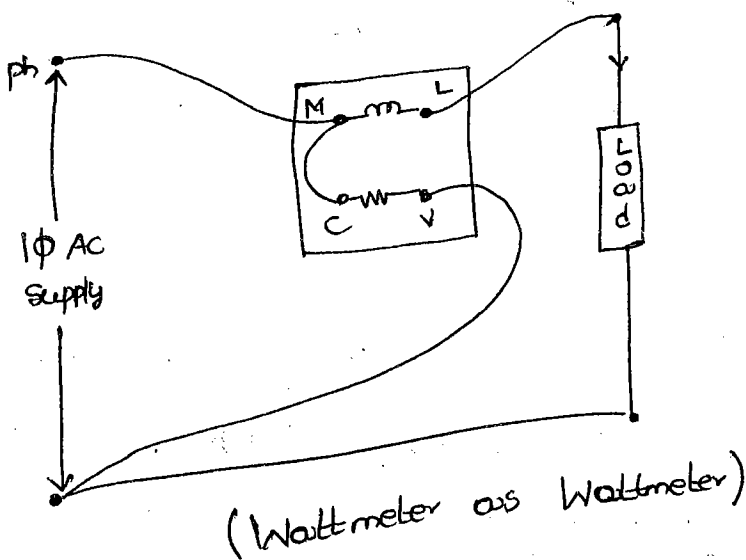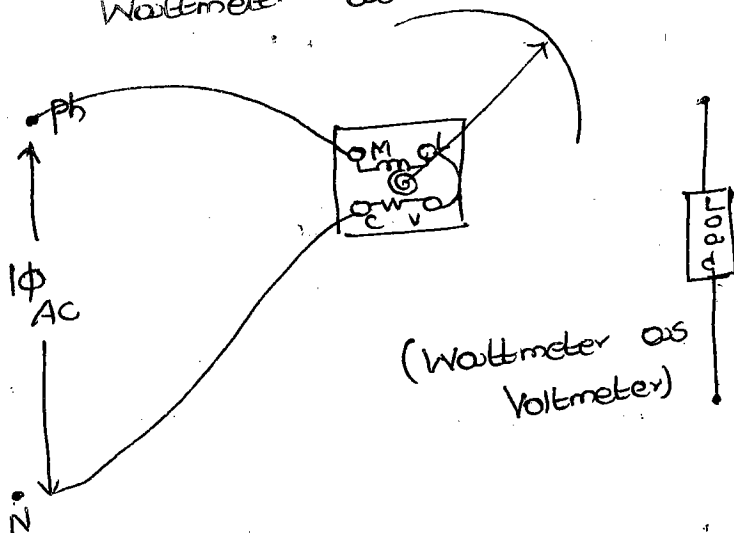\* We can measure current, but we are not supposed to do that because it does not give accurate results.



Thus, Wattmeter can be used exclusively for A.c power.

$$P = VI \cos\phi$$

$$\cos\phi = \frac{P}{VI}$$

Then, Wattmeter is also used in

Note

both

In

Can

Enc

1.

4.

1.

The

M

4

2.

3.

4.

5

Note: In case of Current and Voltage Measurement

both the Coils should be in Series

In case of Power and power factor Measurement both the Coils should be connected in parallel

Errors in EMMC: Order of Accuracy/Sensitivity:  $PMMC > MI > EMMC$

- 1. Frictional error
- 2. Temp error
- 3. Frequency error
- 4. Hysteresis error
- 5. Stray Magnetic field error

1. Frictional error:

$$EMMC > MI > PMMC$$

The frictional error is more in EMMC compared to MI & PMMC. Since, a very very weak magnetic field is inside the meters

Torque to Weight Ratio:

$$PMMC > MI > EMMC$$

2. Temp. Error: The temperature error is more compared to PMMC & MI. But it can be reduced by employing Swamping Resistance

$$EMMC > MI > PMMC$$

3. Frequency Error: Bcz No. of Coils more

$$EMMC > MI > PMMC$$

Bcoz No. of Coils are more, frequency change  $\rightarrow$  Impedance changes more

4. Hysteresis error:

$$MI > PMMC > EMMC$$

In this instrument, hysteresis error is almost absent. Since there is no iron related materials in the moving system

5. Stray Magnetic field error: Stray magnetic field error is more compared to PMMC, MI. A very very weak

$$EMMC > MI > PMMC$$

We can measure current, we are supposed to do that cause it does give accurate results.

ster

r

inside the meters

2/5/12 (9 to 1:00)

1. The Mutual Inductance of a 25A (EMMC) Dynamometer type Ammeter changes at  $0.2 \mu\text{H}/^\circ\text{degree}$ . Spring Constant is  $10^{-6} \text{ N-m/degree}$ . Find Angle of deflection

$$T_c = T_d$$

$$\Rightarrow k_c \theta = I^2 \frac{dM}{d\theta}$$

$$\Rightarrow 10^{-6} \times \theta = (25)^2 \times 0.2 \times 10^{-6}$$

$$\theta = 125^\circ$$


2. A Current of  $i(t) = 80 - 60\sqrt{2} \sin(\omega t + 30^\circ)$  A is passed through three instruments PMMC, MI, Dynamometer type. Then the respective readings will be

PMMC = 80 (only DC Value)

MI =  $\sqrt{80^2 + \frac{(60\sqrt{2})^2}{2}}$  (RMS Value) = 100

EMMC = 100  
↓ DC                      ↓ RMS

Electro Static Effect:

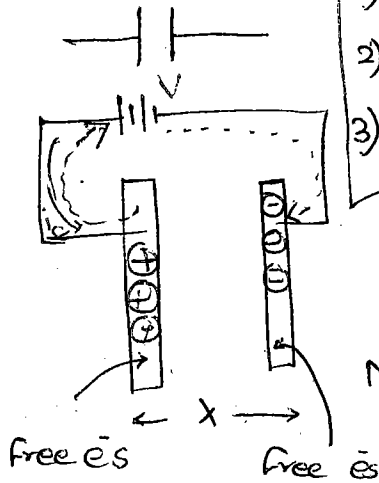

- 1) open ckt, how current flows
- 2) In  $i = C \frac{dv}{dt}$  Where from  $\frac{dv}{dt}$
- 3) How current leads Voltage?

(Free of electrons)  
 1) Two Metal plates separated by  $\epsilon_0$  and dielectric Material placed b/w the plates

After the removal of charge, Potential difference occurs and soon after the time progress, p.d increases. Slowly, it increases upto 'V'. Between these two plates, suddenly Voltage will not appear and takes certain time to develop 'V'

$$i_c \propto \left(\frac{dv}{dt}\right)$$

$$R \rightarrow i \propto \frac{V}{R}$$

$$I \rightarrow V \propto \frac{dV}{dt}$$

$$C \rightarrow i = C \frac{dv}{dt}$$

Inductance will not show sudden

elect  
 →  
 →  
 →

o  
 s  
 E

is

\* Once  
 Curve  
 the  
 +ve  
 force

exist  
 plate


\* 1

C

\* 2

is

Relat

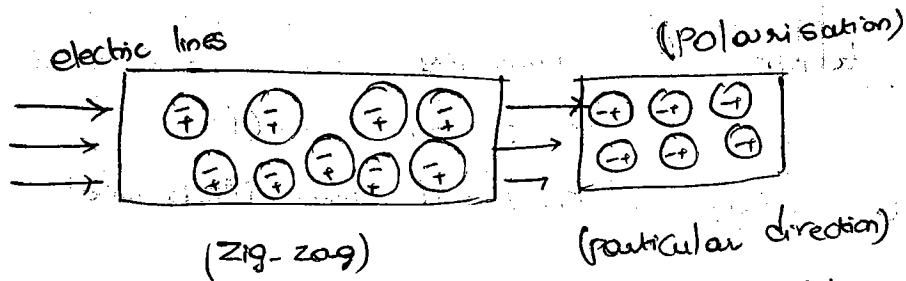

In the middle of the plates, dielectric material is placed which is placed which into particular direction

aligns the dipoles in zig-zag into particular direction so that the net is closed.


Electrostatic Voltmeters:

The responsible quantity is Voltage

~~$Q \propto I \Rightarrow Q \propto IT$~~  Not applicable to Capacitor

$Q \propto V \Rightarrow Q = CV$   
(Capacitor)

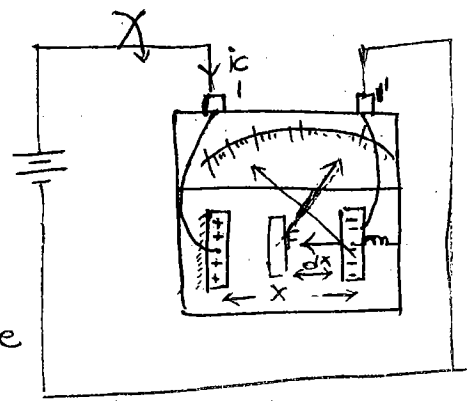\* Once charging current enters the plate becomes +ve charged and force of attraction exists between these plates.



\* Main Working principle of Electrostatic Voltmeter is Capacitance

\* In electrostatic Voltmeter, the responsible quantity is Voltage.

Relation b/w Ip Voltage & E/p Force :-

$$i_c = \frac{dQ}{dt} = \frac{d}{dt}(CV)$$

$\phi = \frac{EA}{d}$  (Variable x, C, V, F, Q)  
(Variable)

$$i_c = \left( C \frac{dv}{dt} + V \frac{dc}{dt} \right)$$

Power  $\Rightarrow V \times i_c = \left( C \frac{dv}{dt} + V \frac{dc}{dt} \right) \times V$

Energy  $\Rightarrow V \times i_c \times dt = dt \left( C \frac{dv}{dt} + V \frac{dc}{dt} \right) \times V$   
 $= CV dv + V^2 dC$

$dt$  - time taken for switching

$$CV dv + V^2 dc = dW \rightarrow \textcircled{1}$$

This electrical energy is converted into Mechanical Work done

$$\therefore \text{Mechanical Work done in 'dt' sec} = F \times dx \rightarrow \textcircled{2}$$

According to law of Conservation of energy

Energy stored in Capacitor in 'dt' sec

$$\begin{aligned} &= (\text{Energy stored in } t+dt) - (\text{Energy stored in } t) \\ &= \frac{1}{2} (C+dc)(V+dv)^2 - \frac{1}{2} CV^2 \\ &= \frac{1}{2} (C+dc)(V^2 + \cancel{dV^2} + 2Vdv) - \frac{1}{2} CV^2 \\ &= \frac{1}{2} (CV^2 + 2VdVc + V^2dc + 2V\cancel{dV}dc) - \frac{1}{2} CV^2 \\ &= \frac{2V dVc + V^2 dc}{2} \\ &= VC dv + \frac{V^2}{2} dc \rightarrow \textcircled{3} \end{aligned}$$

Electrical energy = Mech. Energy + Energy stored

$$CV/dv + V^2 dc = F \cdot dx + VC/dv + \frac{V^2}{2} dc$$

$$\Rightarrow \boxed{F \cdot dx = \frac{1}{2} (V^2) dc}$$

$$F = \left(\frac{1}{2}\right) V^2 \left(\frac{dc}{dx}\right)$$

$$\boxed{F \propto V^2}$$

So, the Scale is Non-Linear

\* Both are storing  
 If use Inductor as storing element, slowly Inductor charges. Inductor can reverse the polarity. It acts as source then; it gives back the energy whatever stored. Capacitor won't reverse after fully charged also.

	Steady state	Transient
Capacitor	open	shorted
Inductor	short cktd	open

\* S  
 \* in  
 Ele  
 F  
 \* a  
 F  
 in  
 To  
 (P) A  
 G  
 P  
 d


\* In place of Capacitors, if we use Inductors the size of device is high

\* In Capacitor, Noise will be less (almost zero) <sup>Eg: Inverter</sup> whereas in Inductor, Noise (will be high) (Generator)

Electrostatic Voltmeters are ~~not~~ <sup>best</sup> suitable for measurement for very high voltages [(Min. 1KV) - Max 500KV]

\* These Instruments are suitable for the measurement of both AC & DC. AC is not measured directly, first converted to DC and then it measures.

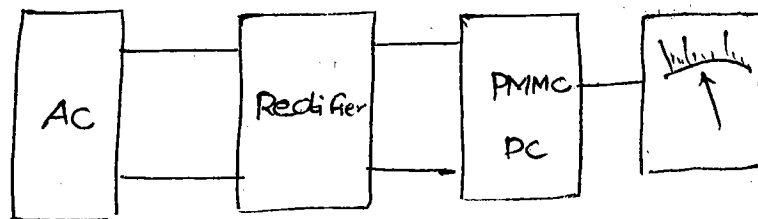To Measure the AC With PMMC, Use a Rectifier in the middle



$$FF = \frac{RMS}{AVG}$$

For change of Scale,

multiply the Value by 1.1  $\Rightarrow RMS = 1.1 \times AVG$   
to get RMS Value.

(P) An Absolute Electrostatic Voltmeter has a Movable Circular plate of 8cm in diameter. If the dist. btw two plates during Measurement 4mm. Find the potential diff. for a force of Attraction is 0.002 N

$$X = 4 \text{ mm}$$

$$F = 0.002 \text{ N}$$

$$F = \frac{V^2}{2} \times \frac{dC}{dX}$$

$$0.002 = \left(\frac{V^2}{2}\right) \times \left(\frac{1.77 \times 10^{-11}}{4 \times 10^{-3}}\right)$$

$$C = \frac{\epsilon_0 A}{d}$$

$$= \frac{8.854 \times \pi (8 \times 10^{-2})^2}{4 \times 10^{-3}}$$

$$= 1.77 \times 10^{-11}$$

$$V = 12 \text{ KV}$$

4/16/12  
(8:30-1:00)

$$C = \frac{EA}{x}$$

$$\left| \frac{dc}{dx} \right| = \frac{EA}{x^2}$$

$$= \frac{(8.85 \times 10^{-12}) \times \left( \frac{\pi}{4} \times 8^2 \times 10^{-6} \right)}{(4 \times 10^{-3})^2}$$

$$= 2.8 \times 10^{-9}$$

$$F = \frac{1}{2} V^2 \left( \frac{dc}{dx} \right)$$

$$0.02 = \frac{1}{2} V^2 \left( \frac{dc}{dx} \right)$$

$$\frac{0.04 \times 1}{2.8 \times 10^{-9}} = V^2$$

Ⓟ The Spring constant of 3000 V E.S.V.M is  $7.206 \times 10^{-6}$  N-m/rad. The FSD of instrument is  $80^\circ$ . Assume the rate of change of capacitance is constant over an operating range. Find the total change in deflection capacitance from zero to F.S.D

$$K_c = 7.206 \times 10^{-6} \text{ N-m/rad}$$

$$F = \frac{1}{2} (V^2) \left( \frac{dc}{dx} \right)$$

[As  $\theta$  are given]

$$T = \frac{1}{2} (V^2) \left( \frac{dc}{d\theta} \right)$$

$$K_c \cdot \theta = \frac{1}{2} (V^2) \frac{dc}{d\theta}$$

$$\Rightarrow (7.206 \times 10^{-6}) \times 80 \times \frac{\pi}{180} = \left( \frac{1}{2} \right) (3000)^2 \left( \frac{dc}{d\theta} \right)$$

$$2 \times \frac{1.006 \times 10^{-5}}{(3000)^2} = \left( \frac{dc}{d\theta} \right)$$

$$\Rightarrow \frac{dc}{d\theta} = (2.23 \times 10^{-12})$$

$$\Delta c = (2.23 \times 10^{-12}) (80) \times \frac{\pi}{180}$$




4/5/12  
(8:30-1:00)

## Potentiometer :-

By using Potentiometers, We can measure a Very Accurately Voltages With an Accuracy

Basic Potentiometers :-

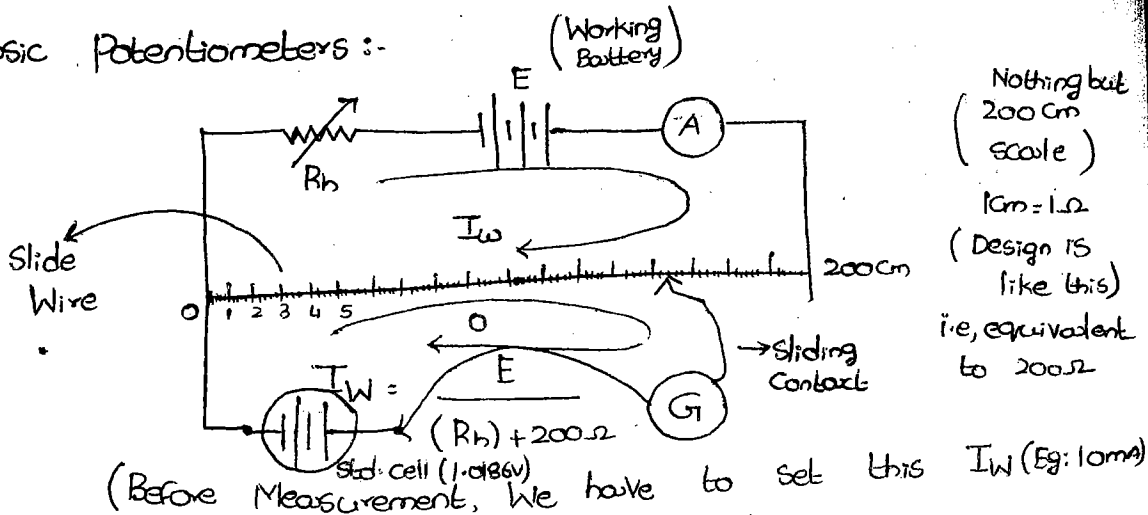

this can be done by Varying Rheostat

\* Really it is circulating 10 mA / not we don't depend on Ammeter, to Cross Check this take a Standard Cell (available in labs as 1.0186 V) & Galvanometer. once, checking is over, we can remove the standard cell. We have to make the contact of sliding contact, whenever it is in contact, the Galvanometer reads zero deflection. It reads zero, whenever the drop across the slide wire equals the standard cell, current in that loop is 0 A.

Now record the value of 'R'

$$10 \text{ mA} \times R = 1.0186$$

$$R = \frac{1.0186}{10 \text{ mA}} = 101.86 \Omega$$

$$= 101.86 \text{ cm at this distance}$$

If Galvanometer is not showing zero, the

Ammeter shows is not correct).

This can be known as standardization. (For 10 mA)

\* To measure the unknown battery voltage, remove the standard cell, connect unknown battery in its place

\* Galvanometer reading will not be zero, then vary the slide wire contact until reading is zero (suppose occurs at 140 cm)

$$\text{Unknown} = 140 \Omega \times 10 \text{ mA} = 1.4 \text{ V}$$

.206  
assume  
it  
ge

$$R = \frac{V}{C_m} \quad [\text{Resolution}]$$

$$= \frac{IR}{C_m} = \frac{10 \text{ mA} \times 200 \Omega}{200 \text{ cm}}$$

$$R = 0.01 \text{ V/cm}$$

Why it is Accurate?

In PMMC, When we working with low Voltages, due to drop in Connecting Wires, resistance in meters, the meter Won't deflect.

But in Potentiometers, the Current is zero (⊗ Current zero method) even though due to the presence of resistance of Connecting Wires, Slide Wire & Contact (due to Current absent) No drop will be there and it is more Accurate.

\* The suitable material for Slide Wire is Platinum - Gold - Silver.

Drawbacks:

- 1) Lengthy Meter (bcz of 2m)
- 2) Resolution is not so high ( $R = 0.01 \text{ V/cm}$ )

Crompton's Potentiometer:


(To overcome the drawbacks of <sup>basic</sup> Potentiometer i.e., to reduce the length and to improve the Resolution of the instrument)

We go for Crompton's Potentiometer

\* Slide Wire is made to reduce by moulding it as circular in shape, there by it is compact in size.

\* In Basic P.M, at 10 mA, the Resistance 101.86 $\Omega$  is completely contributed by slide wire. Now here it is divided into two parts (one by slide wire,

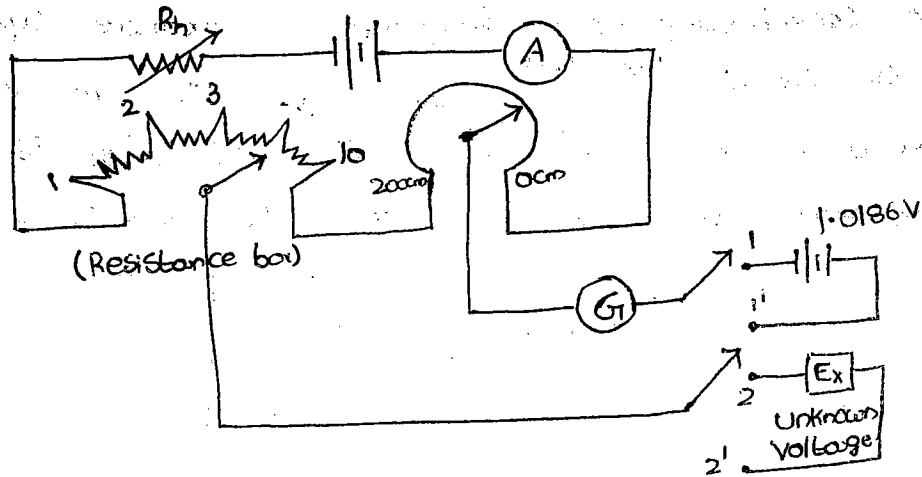\* desi  
1.86  
200  
base  
  
\*  
ch  
2  
Sor  
by  
Res



Resistance box has 10 steps, each step is designed for 10 Ω (Total  $10 \times 10 = 100 \Omega$ ). Remaining  $1.86 \Omega$  is contributed by slight wire. Another thing is  $200 \text{ cm}$  slide wire is designed for  $10 \Omega$  (unlike  $200 \Omega$  in basic potentiometer).

[For Eg.: To obtain  $88 \Omega$   
Take  $80 \Omega$  on resistance box i.e, on 8th step and remaining  $8 \Omega$  on slide wire]

\* After standardisation is over,  $200 \text{ cm} = 10 \Omega$   
Change the switch from 1-1' to ? =  $1.86 \Omega$   
2-2'. Then the Galvanometer reads  $\Rightarrow 1.86 \times \frac{200}{10}$   
Some value. Now, we have to adjust =  $37.2 \text{ cm}$   
by using Resistance box & slide wire  
(For Major deflection) (For Minor deflection)  
Resistance.

Now, if we obtain  $0.5$  on box &  $2$  on wire

$$\Rightarrow (22 \text{ } \leftrightarrow \text{ } 30 + 0.01) \Omega \times 10 \text{ mA} = \text{Unknown Voltage}$$

$$\text{Resolution} = \frac{V}{\text{cm}} = \frac{IR}{\text{cm}} = \frac{(10 \text{ mA})(10 \Omega)}{200} = 0.0005 \text{ V/cm}$$

ment  
of  
contact  
there

eter  
the

it as  
ct n

ce  $101.86 \Omega$   
here it  
re,

① A potentiometer is designed to measure upto 2V, slide of 800 mm. (1mm = 1Ω). A standard cell emf of 1.18 V is balance at 600 mm. At test cell is seen to obtain balance at 680 mm. Then the emf of test cell

Sol:  $I_w \times 600 \text{ mm} = 1.18$


$I_w = 1.96 \text{ mA}$

Unknown =  $I_w \times 680 \text{ mm}$

$= 1.96 \times 680 = 1.337 \text{ V}$

$600 \Omega$	$= 1.18 \text{ V}$
$680 \Omega$	$= ?$
$\Rightarrow 680 \times \frac{1.18}{600}$	
	$= 1.337 \text{ V}$

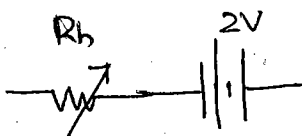② A wire potentiometer of length 11m and resistance 1Ω/m balances a std cell voltage of 1.018 V at a length of 10.18 m. If the voltage of the battery supplying current through potentiometer is 2V. Then the series resistance correspond to connect through P.M. ?



$I_w \times 10.18 = 1.018$

$I_w = \frac{2}{R_h + 11 \Omega}$


$I_w = 0.1 \text{ A}$

$\Rightarrow (R_h + 11) (0.1) = 2$

$\Rightarrow R_h = 20 - 11 = 9 \Omega$

③ The potentiometer is balanced then find the value of  $E_x$ .

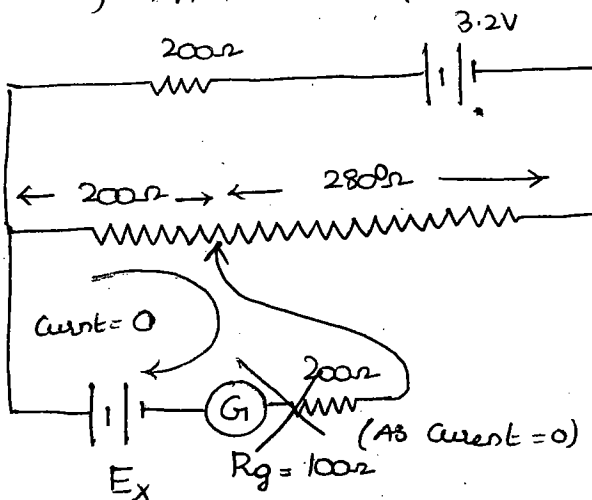$I_w = \frac{3.2}{200 + 200 + 4800}$   
 $= 1 \text{ mA}$




$I_w \times 200 = E_x$

# Measurement of Resistance.

1. Low Resistance ( $R < 1 \Omega$ ) → Armature Winding Resistance, Diode F-B resistance, Series Field Winding
2. Medium Resistance ( $1 \Omega - 100 k\Omega$ ) → Shunt Field Resistance, Potentiometer Slide Wire
3. High Resistance ( $R > 100 k\Omega$ ) → Diode P-B Resistance, OP-Amp I/p Impedance, Insulation Resistance

\* By seeing the terminals, we can identify the Resistances


Low Resistance - 4 terminals

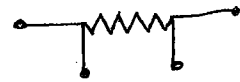

Medium Resistance - 2 terminals



High Resistance - 3 terminals

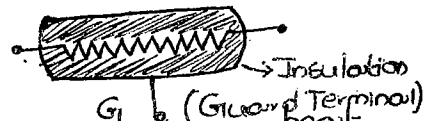

Purpose of Guard terminal: (More heat developed, so heat inside High resistance dissipation is must. So Insulation is there, outside High Insulation Required)

Resistance. When we connect the Multimeter, Req will be the combination of both and we won't get exact value. So, Guard terminal is grounded to avoid leakage current (Makes Insulation Resistance is zero)

Low Resistance	Medium Resistance	High Resistance
1) Kelvin's Double Bridge	Accurate 1) Wheat stone Bridge 2) V-A } method A-V } 3) Substitution Method Worst 4) Ohm-meter Method	1) Megger Accurate 2) Loss of Charge method 3) Direct Deflection Worst 4) Mega ohm Bridge Method


## Measurement of Low Resistance:

Kelvin's Double Bridge:

P, Q, p, q

Bridge Resistances A

'x' - Contact leads Resistance.

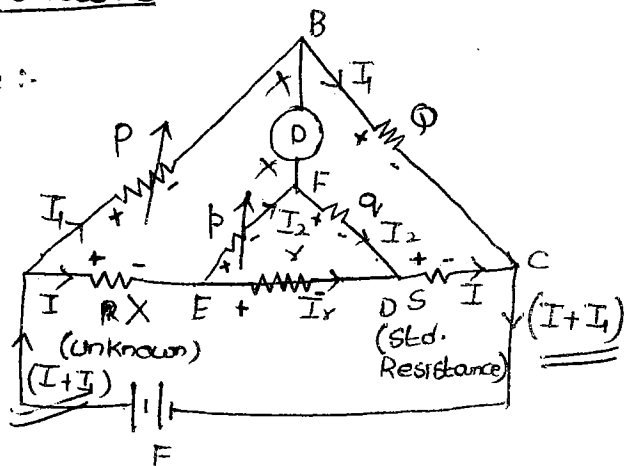

D - Detector

Under balanced condition, 'D' is short circuited

Three KVL Equations,

$$X = \frac{P}{Q} S + \frac{q_1 r}{p + q_1 + r} \left[ \frac{P}{Q} - \frac{p}{q} \right]$$

Kelvin's Double Bridge is useful to measure the low & Medium Resistances


If we want to measure Medium Resistance,

make  $\frac{P}{Q} = \frac{p}{q}$

then  $X = \frac{P}{Q} S$

Measurement of Medium Resistance:

1) Wheatstone Bridge

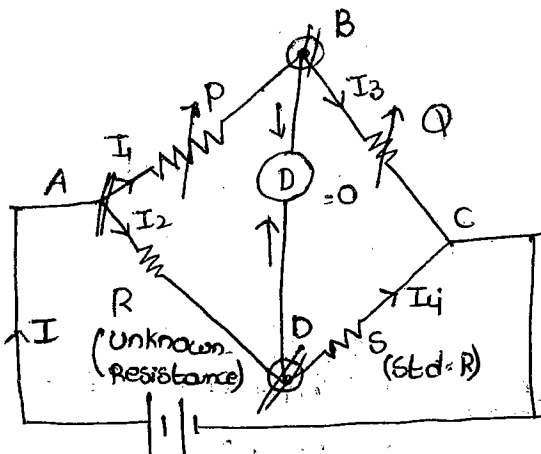

Voltage Drop across AB = Voltage Drop across AD

$$I_1 P = I_2 R$$

$$\frac{I_1}{I_2} = \frac{R}{P} \rightarrow (1)$$

Voltage Drop across BC = Voltage drop across DC

$$I_3 Q = I_4 S$$

$$\Rightarrow \frac{I_3}{I_4} = \frac{S}{Q} \rightarrow (2)$$

$$\frac{R}{P} = \frac{S}{Q} \Rightarrow R = \frac{P}{Q} S$$

Sensitivity: (change in o/p to change in i/p)

1. Detector Sensitivity ( $S_D$ )

2. Bridge Sensitivity ( $S_B$ )

In Between B, D. Detector reads zero bcz of B, D at same. To know the Detector Sensitivity, make the Bridge potential

intentionally unbalance. To achieve this change the Resistance ' $R$ ' to  $(R + \Delta R)$ . ' $e$ ' is change in P.D;

' $\Delta\theta$ ' is the deflection occurs

$$\therefore \text{Detector Sensitivity} = \frac{\text{change in Deflection}}{\text{change in P.D}}$$

$$= \frac{\Delta\theta}{e}$$

$$S_D = \frac{\Delta\theta}{e} \Rightarrow \Delta\theta = S_D \cdot e$$

$$\text{Bridge Sensitivity} = \frac{\text{change in Deflection}}{\text{Unit change in Resistance}}$$

$$S_B = \frac{\Delta\theta}{(\Delta R/R)}$$

$$\therefore S_B = \frac{S_D \cdot e}{\Delta R/R}$$

We always prefer  $\otimes$  high sensitivity; Which in turn depends on detector sensitivity

$$e = V_B - V_D$$

$$= (E - V_{AB}) - (E - V_{AD})$$

$$\Rightarrow e = V_{AD} - V_{AB}$$

$$= E \left[ \frac{R + \Delta R}{(R + \Delta R) + S} \right] - E \left[ \frac{P}{P + Q} \right]$$

$$e = E \left( \frac{R + \Delta R}{R + \Delta R + S} - \frac{P}{P + Q} \right) \rightarrow \textcircled{1}$$

$$\text{We know } \frac{P}{Q} = \frac{R}{S}$$

$$\Rightarrow \frac{Q}{S} = \frac{P}{R}$$

Add '1' on both sides

$$\Rightarrow \frac{Q}{P} + 1 = \frac{S}{R} + 1 \Rightarrow \frac{Q+P}{P} = \frac{S+R}{R}$$

$$\Rightarrow \frac{P}{Q+P} = \frac{R}{S+R}$$

Now substitute the above in ①

$$\Rightarrow e = E \left( \frac{R+\Delta R}{R+\Delta R+S} - \frac{R}{R+S} \right)$$

$$= E \left( \frac{(R+\Delta R)(R+S) + (R(\Delta+R))s}{(R+\Delta R+S)(R+S)} \right)$$

$$= E \left( \frac{\begin{matrix} -R(R) - R\Delta R - SR \\ R^2 + R\Delta R + RS + \Delta RS - R^2 - R\Delta R \\ -SR \end{matrix}}{(R+\Delta R+S)(R+S)} \right)$$

$$= E \left( \frac{S\Delta R}{(R+S)^2 + \Delta R(R+S)} \right)$$

(Neglect) as Very Small

$$e = \frac{ES\Delta R}{(R+S)^2}$$

$$\therefore \text{Bridge sensitivity} = \frac{S_D e}{(\Delta R/R)}$$

$$= \frac{S_D \cdot ES \cancel{\Delta R}}{(R+S)^2} \cdot \frac{R}{\cancel{\Delta R}}$$

$$\therefore S_B = \frac{S_D \cdot ES R}{(R+S)^2}$$

$$= \frac{S_D \cdot ERS}{R^2 + S^2 + 2RS}$$

Divide by  $R^2$

$$\Rightarrow S_B = \frac{S_D \cdot ERS}{RS}$$

2)

\*



$$\Rightarrow S_B = \frac{S_D \cdot E}{\left(\frac{R}{S} + \frac{S}{R} + 2\right)}$$


To get Bridge Sensitivity as Maximum;

$$\frac{R}{S} = \frac{S}{R} = 1$$

$$\therefore S_B = \frac{S_D \cdot E}{1+1+2} = \frac{S_D \cdot E}{4}$$

$$\therefore S_{B \text{ max}} = \frac{S_D \cdot E}{4}$$

2) V-A Method:

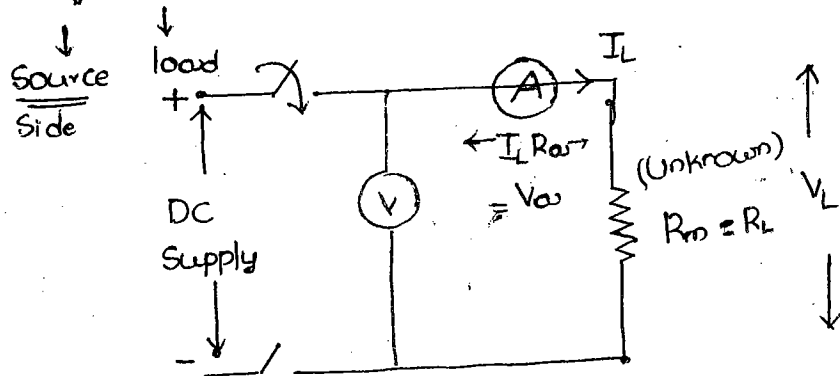

$$\text{True Value} = (R_m)_t = \frac{V_L}{I_L}$$

$$\text{But } (R_m)_m = \frac{\text{Voltmeter Reading}}{\text{Ammeter Reading}} \quad (\text{Apply KVL})$$

(Measured Value)

$$= \frac{V_L + V_a}{I_L} = \frac{V_L}{I_L} + \frac{I_L R_a}{I_L}$$

$$= \frac{V_L}{I_L} + R_a$$

$$\therefore (R_m)_m = (R_m)_t + R_a$$

$$i) (R_m)_m > (R_m)_t$$

\* In V-A method, for the measurement of Medium Resistance, error is because of only Ammeter

$$\therefore \text{Error} = \left( \frac{A_m - A_t}{A_t} \right) \times 100$$


$$\therefore \text{Error} = \frac{R_a}{R_m} \times 100$$

\* Error is always to be less. It occurs when  $R_{av}$  is low (which is not in our hand). /  $R_m$  is high (So, Better to measure high Value in Medium Range) to reduce errors.

Conclusions:

1. In Voltmeter-Ammeter method,  $R_m > R_L$
2. In V-A method, error because of always due to Ammeter
3. This method is useful for measurement of high Resistance in Medium Range so that % error is minimum

A-V Method:

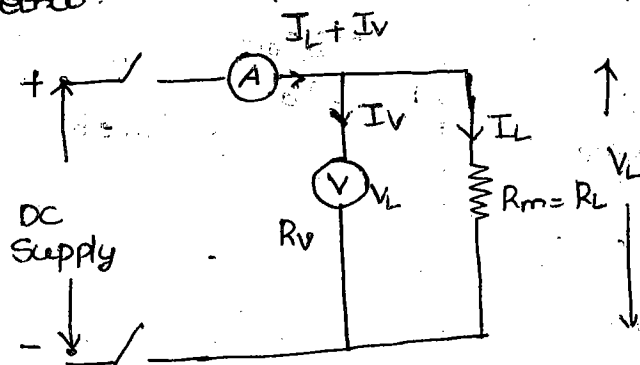

$$(R_m)_E = \frac{V_L}{I_L}$$

$$(R_m)_m = \frac{\text{Voltmeter Reading}}{\text{Ammeter Reading}}$$

$$= \frac{V_L}{I_L + I_V}$$

$$\text{So, } (R_m)_m < (R_m)_E$$

$$(R_m)_m = \frac{V_L}{\left(\frac{V_L}{R_L}\right) + \left(\frac{V_L}{R_V}\right)}$$

$$\Rightarrow (R_m)_m = \frac{1}{\frac{1}{R_L} \left(1 + \frac{R_L}{R_V}\right)}$$

$$(R_m)_m = \frac{R_L}{1 + \frac{R_L}{R_V}}$$

Co  
1.  
2.  
3.  
R  
Not  
1. In  
is  
2. In  
is  
W  
3.

curr  
and) /  
ue in

$$\Rightarrow (R_m)_m \left( 1 + \frac{R_L}{R_V} \right) = R_L$$

33

$$\Rightarrow (R_m)_m - R_L = \frac{-(R_m)_m R_L}{R_V}$$

$$\Rightarrow \left( \frac{(R_m)_m - R_L}{R_L} \right) = \frac{-(R_m)_m}{R_V}$$

$$\% \text{ Error} = \left( \frac{(R_m)_m - R_L}{R_L} \right) \times 100 = \frac{-(R_m)_m}{R_V} \times 100$$

ue to  
gh  
minimum

Conclusions:

1.  $R_m < R_L$
2. Error due to Voltmeter
3. Useful for Measurement of low Resistance in Medium Range

Note:  
1. In any Method, error is due to the instrument (thing) which is connected nearer to load side


2. In order to get the same error while measuring in both the methods, it occurs only when the Unknown Medium Resistance is  $R_L = \sqrt{R_{AV} R_V}$

[error in V-A = error in A-V]

$$\Rightarrow \frac{R_{AV}}{R_L} = \frac{R_L}{R_V} \Rightarrow R_L = \sqrt{R_{AV} R_V}$$

Where 'R<sub>AV</sub>' is Ammeter Internal Resistance  
'R<sub>V</sub>' is Voltmeter Internal Resistance

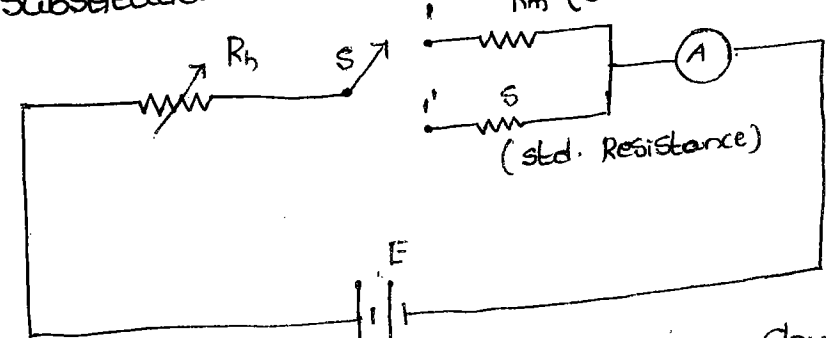3) Substitution Method: R<sub>m</sub> (Unknown Medium Resistance)




1. Connect Switch S to '1', Current flows in Ammeter. Note down it as  $I_1 = \frac{E}{R_m + R_h}$

\* Error is always to be less. It occurs when  $R_m$  is low (Which is not in our hand). /  $R_m$  is high (So, Better to measure high Value in Medium Range) to reduce errors.

Conclusions:

1. In Voltmeter- Ammeter method,  $R_m > R_L$
2. In V-A method, error because of always due to Ammeter
3. This method is useful for measurement of high Resistance in Medium Range so that error is minimum

A-V Method:

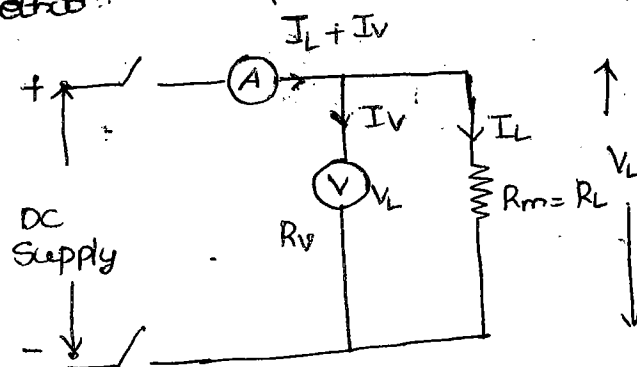

$$(R_m)_E = \frac{V_L}{I_L}$$

$$(R_m)_m = \frac{\text{Voltmeter Reading}}{\text{Ammeter Reading}}$$

$$= \frac{V_L}{I_L + I_V}$$

$$\text{So, } (R_m)_m < (R_m)_E$$

$$(R_m)_m = \frac{V_L}{\left(\frac{V_L}{R_L}\right) + \left(\frac{V_L}{R_V}\right)}$$

$$\Rightarrow (R_m)_m = \frac{1}{\frac{1}{R_L} \left(1 + \frac{R_L}{R_V}\right)}$$

$$(R_m)_m = \frac{R_L}{1 + \frac{R_L}{R_V}}$$

occurs  
hand) /  
value in

$$\Rightarrow (R_m)_m \left( 1 + \frac{R_L}{R_V} \right) = R_L$$

$$\Rightarrow (R_m)_m - R_L = \frac{-(R_m)_m R_L}{R_V}$$

$$\Rightarrow \left( \frac{(R_m)_m - R_L}{R_L} \right) = \frac{-(R_m)_m}{R_V}$$

$$\% \text{ Error} = \left( \frac{(R_m)_m - R_L}{R_L} \right) \times 100 = \frac{-(R_m)_m}{R_V} \times 100$$

due to  
igh  
minimum

Conclusions:

1.  $R_m < R_L$
2. Error due to Voltmeter
3. Useful for Measurement of low Resistance in Medium Range

$$\% \text{ Error} = \frac{V_L}{I_L}$$

Note:  
1. In any Method, error is due to the <sup>instrument</sup> (thing) which is connected nearer to load side


2. In order to get the same error while measuring in both the methods, it occurs only when the Unknown Medium Resistance is  $R_L = \sqrt{R_{av} R_V}$

[error in V-A = error in A-V]

$$\Rightarrow \frac{R_{av}}{R_L} = \frac{R_L}{R_V} \Rightarrow R_L = \sqrt{R_{av} R_V}$$

Where 'R<sub>av</sub>' is Ammeter Internal Resistance  
'R<sub>v</sub>' is Voltmeter Internal Resistance

3) Substitution Method:

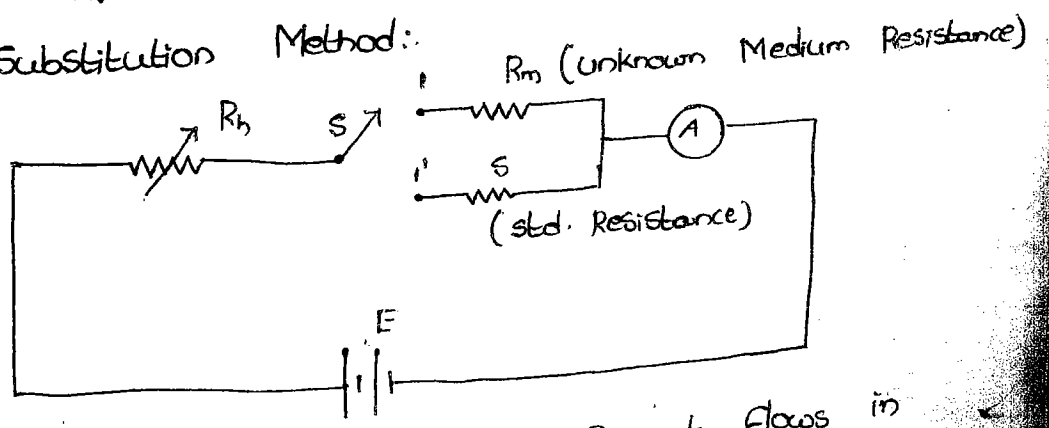

1. Connect Switch S to '1', Current flows in Ammeter. Note down it as  $I_1 = \frac{E}{R_m + R_h}$

Now connect to '1', Note it as  $I_2$


$$I_2 = \frac{E}{R_h + S}$$

Make " $I_2$ " as equal to  $I_1$

To achieve this vary resistance in standard decade box, until it is equal to  $I_1$

Then the std. Resistance is the required Medium (Unknown) Resistance

#### 4) Ohm - Meter Method:-

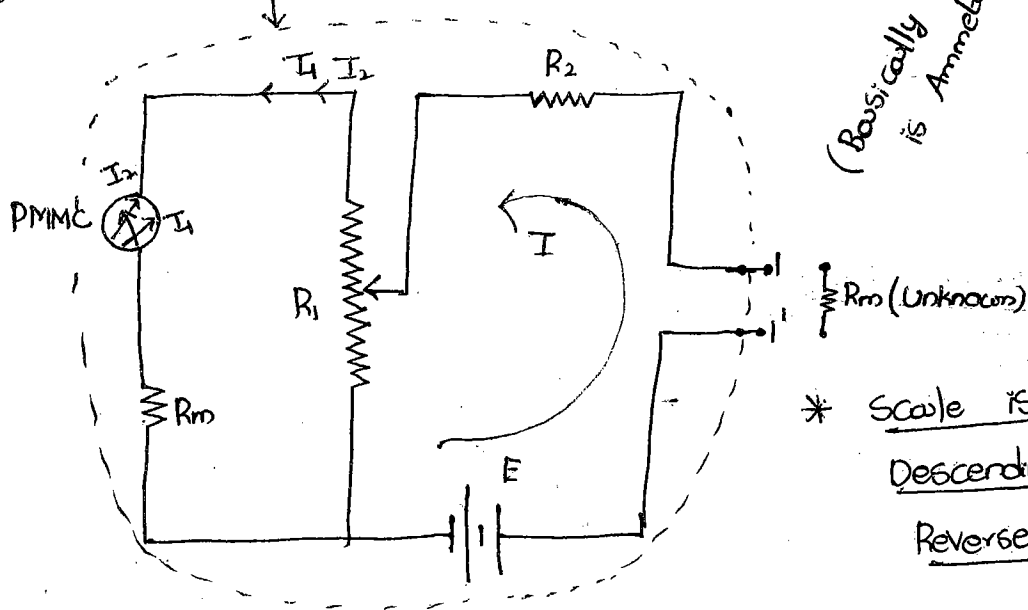

$R_m$  - Internal Resistance of PMMC

\* Before connecting  $R_m$ , short ckt 1 & 1'. Then

'I' flows,  $I_1$  flows through PMMC. Note

$I_1$ .

\* Connect Now  $R_m$ , 'I' decreases because of more Resistance compared to previous.

\* Now  $I_2$  flows through PMMC,  $I_2$  will be less compared to  $I_1$


\* Decrease in this current is equal to the increased Resistance

\* Change the scale of PMMC Ammeter to Resistance scale




\* Ohm-meter measurement of Resistance beyond  $100\text{ k}\Omega$  bcz 'E' is not sufficient. But to increase the measurement of (high) Resistance range, replace "E" with Hand driven generator (Bcz it produces more Voltage compared to Battery) Which is known as Megger.

Megger ::

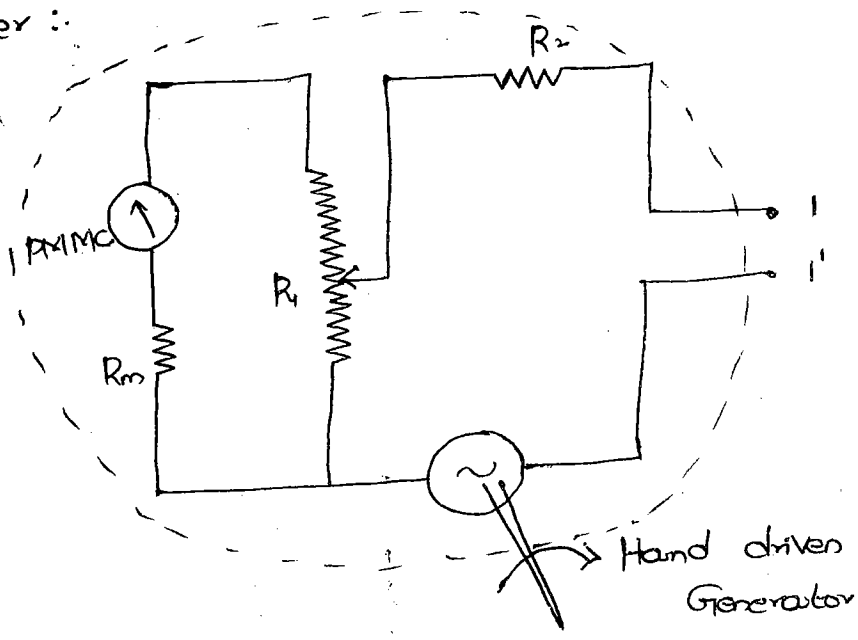


\* By Replacing the Battery with Hand driven generator, we can measure high Resistance. Since, it produces more Voltage compared to battery so that it is sufficient to drive current in the Circuit.

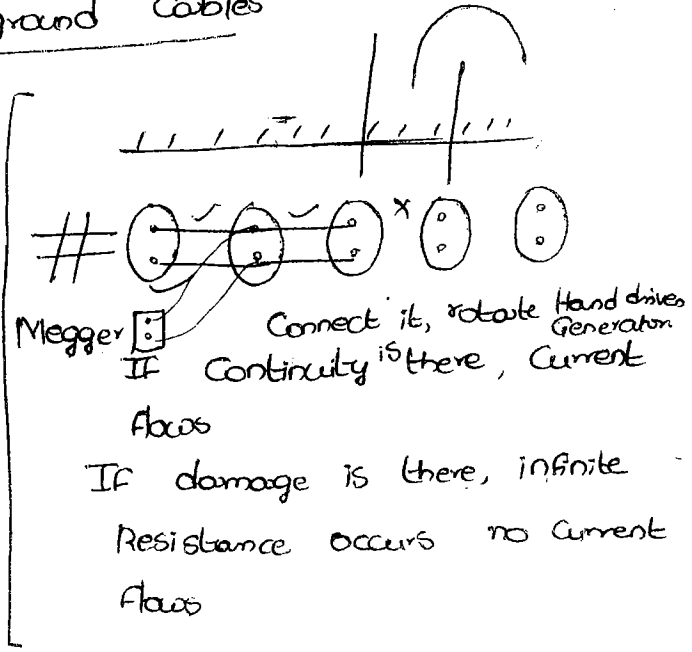\* The Megger is best suitable to check the Continuity in Underground cables.




3/5/12  
11/6/1)

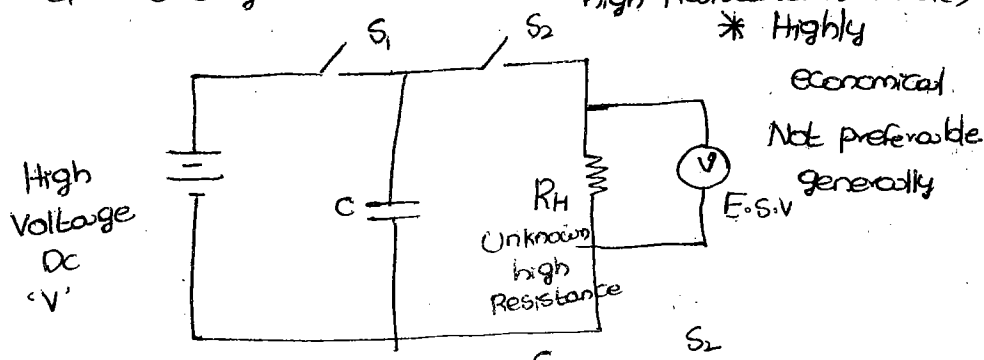Loss of Charge Method: (By using charge, high Resistance is measured)



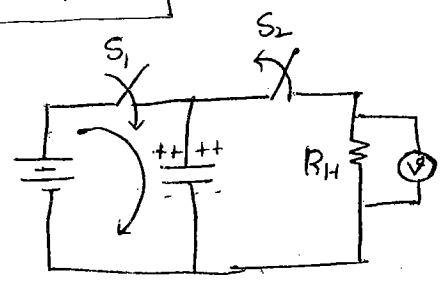Close S<sub>1</sub> and open S<sub>2</sub> then Capacitor will charge.




After t = t(sec)

Open S<sub>1</sub> and close S<sub>2</sub> then the Capacitor starts discharging in exponential manner (decaying)

\* High Voltage ≈ 66 kV  
So, it is of high cost.

$$V(t) = V e^{-t/RC}$$

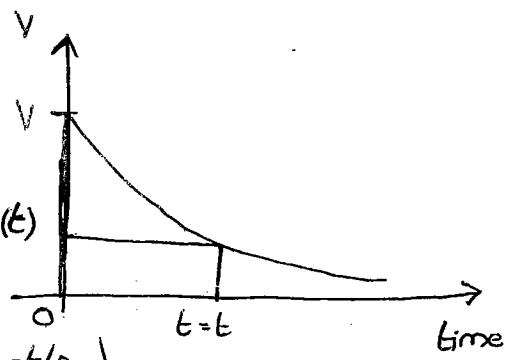

$$\Rightarrow \ln\left(\frac{V(t)}{V}\right) = \ln\left(e^{-t/RC}\right)$$

$$\ln\left(\frac{V(t)}{V}\right) = -t/RC$$

$$\ln\left(\frac{V}{V(t)}\right) = \frac{t}{RC}$$

$$\Rightarrow R = \frac{t}{C \ln\left(\frac{V}{V(t)}\right)}$$


---


$$R = \frac{0.434 t}{C \log\left(\frac{V}{V(t)}\right)}$$

\* Capacitor of high rating reqd bcz of 66 kV which is economical.


\* Loss of charge method is best suitable for measurement of Insulation Resistance in case of cables

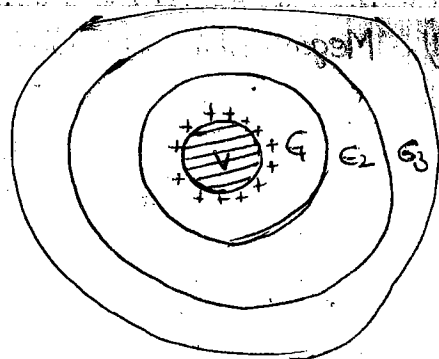3)  
\* T  
the




Charge deposited on outside of Core because of Voltage

\* Electric field lines inside the conductor is 0



Locomotives  $R_1 > R_2 > R_3$  ---  
AC  $E_1 > E_2 > E_3$  ---

$1\phi$  Gauss law  
25KV

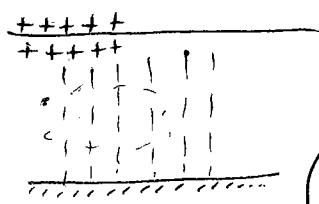


$$\oint \vec{E} \cdot d\vec{A} = \frac{1}{\epsilon_0} Q$$

$$E \cdot 2\pi r = \frac{1}{\epsilon_0} Q$$


$$\Rightarrow E = \frac{Q}{2\pi r \epsilon_0}$$

$$E \propto \frac{1}{r}$$

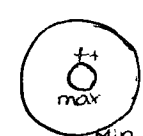

(Equivalent to Parallel Plate Cap)

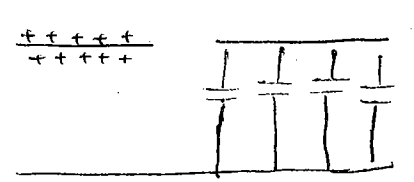In the middle of the line, if it is open. Even though if it is open we can't touch the wire because




$C_{eq}$  increases & current bypasses through our body
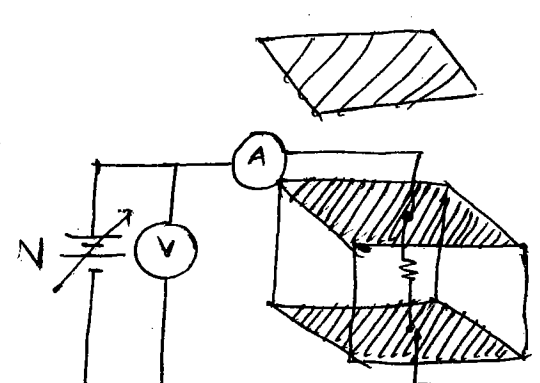
### 3) Direct Deflection Method

\* The direct deflection method is best suitable for the measurement of Resistivity

$$\rho_{Cu} = 1.7 \times 10^{-8} \Omega\text{-m}$$



$$R = \frac{\rho L}{A}$$


Take Unit cube of material from the thing for which resistivity to be found

Measure any two  $l$  as resistance btw any surfaces

$$R = \frac{V}{A}$$

sub in adjacent method

#### 4) Mega-ohm Bridge:

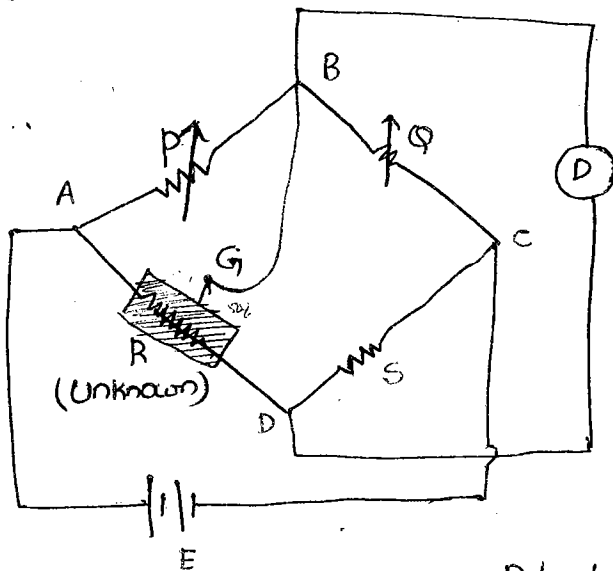

\* III<sub>v</sub> to Wheatstone Bridge, • Detector Connected btw B, D  
Outside

\* Connect high Resistance in place of 'R'

\* Vary P, Q such that deflection is zero

$$R = \left(\frac{P}{Q}\right) S$$

We get Unknown Resistance (Including Insulation Resistance)

\* Connect the Guard terminal of resistance to B:

So, we connected the detector outside

\* P, Half of the <sup>Insulation</sup> Resistance in parallel  
so that Insulation Resistance don't Affect Actual Resistance

M/M Of Inductance: (L) (Maxwell)  
(AC Bridges)

1) Maxwell's Inductance Bridge


2) Maxwell's Inductance - Capacitance Bridge

3) Hay's Bridge

4) Owen's Bridge

5) Anderson's Bridge (Accurate)

# Maxwell's Inductance Bridge:

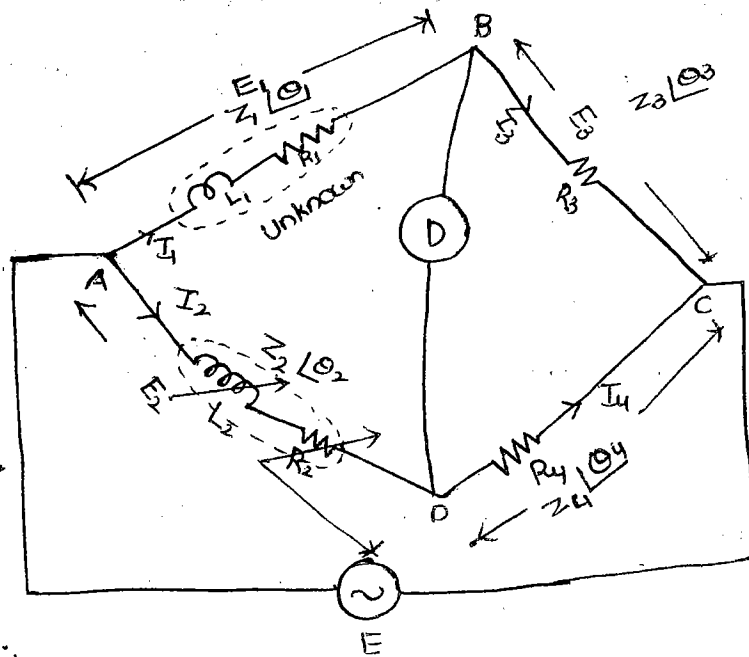


\*\*\*  
 $Z_1 Z_4 = Z_2 Z_3$   
 $\angle \theta_1 + \angle \theta_4 = \angle \theta_2 + \angle \theta_3$

B, D

Step 1:

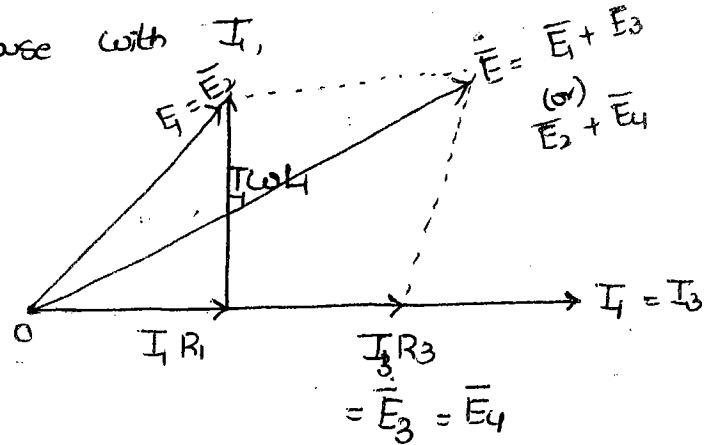- 1)  $I_1 = I_3$ , as no current in Detector
- 2) Draw  $I_1 R_1$  in phase with  $I_1$ ,  
and next draw  $I_1 X_L$  (Current lags Voltage by  $90^\circ$ )



- 3)  $\bar{E}_1 = \bar{E}_2$
- 4) Draw  $I_3 R_3$  in phase with ' $I_3$ '
- 5)  $\bar{E}_3 = \bar{E}_4$
- 6) Draw Resultant of  $\bar{E}_1$  and  $\bar{E}_3$  (or)  $\bar{E}_2$  and  $\bar{E}_4$  to get  $\bar{E}$

$$\therefore Z_1 Z_4 = Z_2 Z_3 \Rightarrow (R_1 + j\omega L_1)(R_4) = (R_2 + j\omega L_2)(R_3)$$

$$\Rightarrow R_1 R_4 + j\omega L_1 R_4 = R_2 R_3 + j\omega L_2 R_3$$

Real:-  $R_1 R_4 = R_2 R_3$  ;  $L_1 R_4 = L_2 R_3$

$$R_1 = \frac{R_2 R_3}{R_4} ; L_1 = \frac{R_3 L_2}{R_4}$$

Quality factor of Inductor,  $L_1$

$$Q = \frac{\omega L_1}{R_1}$$



$\Rightarrow$   ~~$Q = \frac{\omega L_2}{R_2}$~~

\* As no capacitor, we can't get  $\phi$  Resonance condition  
 And the Quality factor formula valid for RLC

→ By using Maxwell's Inductance Bridge, we cannot  
 quality factor ~~we~~ since the bridge cannot  
 be brought to Resonance condition

\* Identification of variable quantities can be  
 obtained by cancellation of common terms from  
 the obtained results

Maxwell's Inductance-Capacitance Bridge:

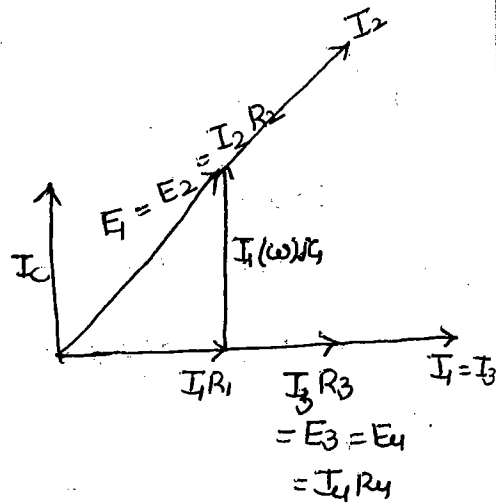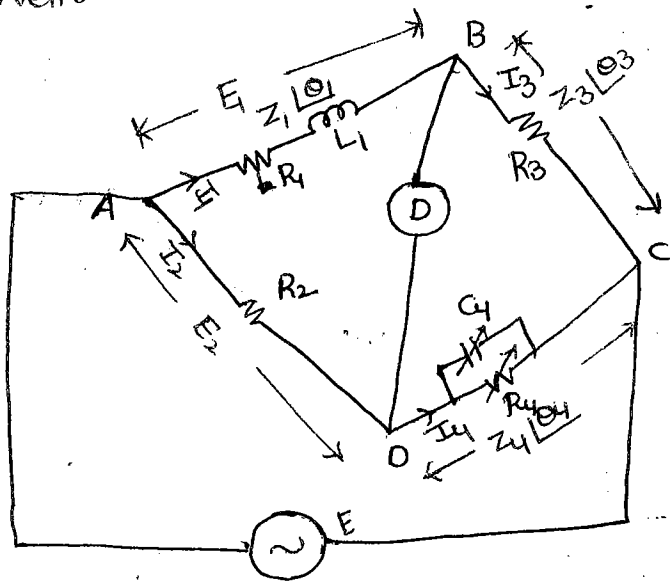

$$Z_1 Z_4 = Z_2 Z_3$$

$$\Rightarrow (R_1 + j\omega L_1) \left( \frac{R_4 \left( \frac{1}{j\omega C_4} \right)}{R_4 + \frac{1}{j\omega C_4}} \right) = R_2 R_3$$

$$\Rightarrow (R_1 + j\omega L_1) \left( \frac{R_4}{R_4 j\omega C_4 + 1} \right) = R_2 R_3$$

$$R_1 R_4 + j\omega L_1 R_4 = R_2 R_3 R_4 j\omega C_4 + R_2 R_3$$

Real:  $R_1 R_4 = R_2 R_3$

$$L_1 R_4 = R_2 R_3 R_4 C_4$$

$$\Rightarrow L_1 = R_2 R_3 C_4$$

$$R_1 = \left( \frac{R_2 R_3}{R_4} \right)$$

$$\phi = \frac{\omega L_1}{R_1} = \frac{\omega (R_2 R_3 C_4)}{R_2 R_3} = \omega C_4 R_4$$


\* It  
 Capac  
 When  
 Indu  
 (Sin  
 Other  
 L:  
 L:  
 \* So,  
 Capac  
 Can  
 Have

Condition

\* It is not easy to manufacture variable capacitor ( $C = \frac{\epsilon_0 A}{d}$ ) we have to vary either A or d. Where as manufacturing fixed Resistor is difficult. Inductor (both cases) are difficult to Manufacture (Since Inductance Values changes even from one person to other person because no. of turns easily changes due to force  $L = \frac{N^2}{S}$ ; (reluctance changes) & Inductor changes  $L = \frac{N\phi}{I}$ , even if it is moved in air,  $\phi$  changes)

\* So, High Quality factor ( $Q \propto C_1$ ). High Capacitor not possible. So, only Low Values can be measured ( $Q < 10$ )

Hay's Bridge:

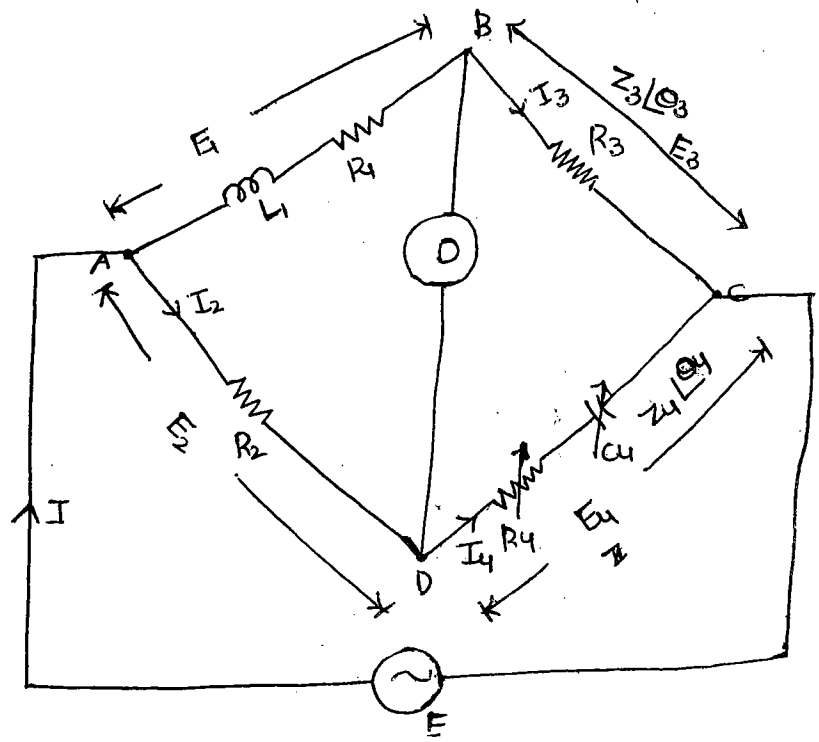

$$\Rightarrow (j\omega L + R_1) \left( R_4 + \frac{1}{j\omega C_4} \right) = R_2 R_3$$

$$j\omega L R_4 + \frac{L}{C_4} + R_1 R_4 + \frac{R_1}{j\omega C_4} = R_2 R_3$$

Real:  $\frac{L}{C_4} + R_1 R_4 = R_2 R_3 \rightarrow (1)$

Im:  $\omega L R_4 - \frac{R_1}{\omega C_4} = 0 \Rightarrow L = \frac{R_1 R_2}{\omega^2 C_4 R_4}$

$\Rightarrow \omega L R_4 = \frac{R_1 R_2}{\omega C_4} \Rightarrow R_4 = \omega^2 L C_4 R_2 \rightarrow (2)$

$I_3 R_3$   
 $E_3 = E_4$   
 $= I_4 R_4$

$\omega C_4 R_4$   
 $\omega C_4 R_4$

② in ①  $\Rightarrow$

$$\frac{L_1}{C_4} = R_2 R_3 - R_4 R_1$$

$$\Rightarrow \frac{R_1}{\frac{R_4}{C_4}} = R_2 R_3 - R_4 R_1$$

$$\begin{aligned} L_1 &= R_2 R_3 C_4 - R_4 R_1 C_4 \\ \Rightarrow &= R_2 R_3 C_4 - \omega^2 L_1 C_4 R_4 R_1 C_4 \end{aligned}$$

$$L_1 (1 + \omega^2 R_4^2 C_4^2) = R_2 R_3 C_4$$

$$\Rightarrow L_1 = \frac{R_2 R_3 C_4}{1 + \omega^2 R_4^2 C_4^2}$$

Again substitute  $L_1$  in ②

$$R_1 = \omega^2 L_1 C_4 R_4$$

$$R_1 = R_4 \frac{\omega^2 R_2 R_3 C_4^2}{1 + \omega^2 R_4^2 C_4^2}$$

Quality factor,  $Q = \frac{\omega L_1}{R_1}$

$$= \frac{\omega (R_2 R_3 C_4)}{1 + \omega^2 R_4^2 C_4^2}$$


$$\frac{\omega^2 R_2 R_3 C_4^2 R_4}{1 + \omega^2 R_4^2 C_4^2}$$

$$= \frac{1}{\omega C_4 R_4}$$

$$Q \propto \frac{1}{C_4}$$

$\therefore Q > 10$  can easily obtained as low capacitances are available.

# Owen's Bridge:-

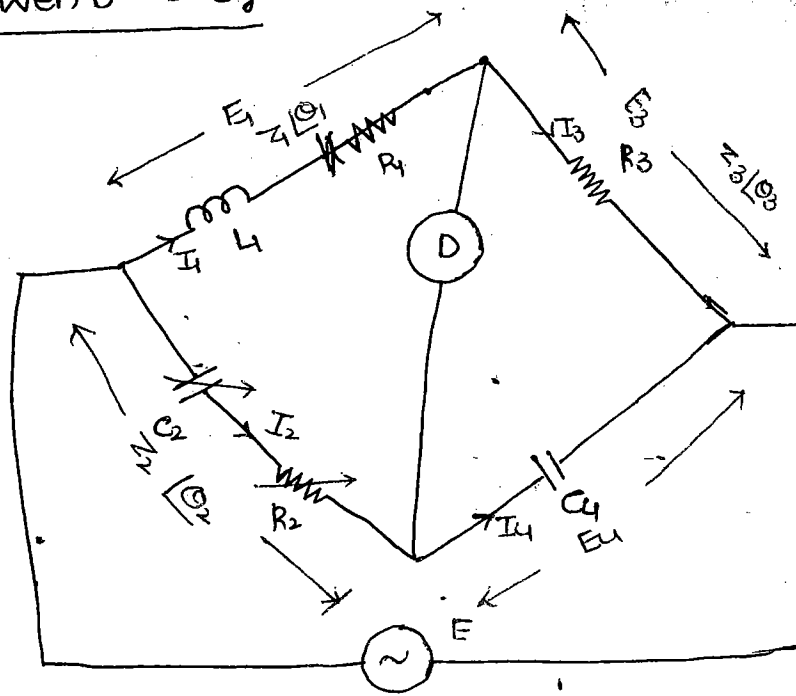

$$\Rightarrow (j\omega L_1 + R_1) \left( \frac{1}{j\omega C_4} \right) = R_3 \left( R_2 + \frac{1}{j\omega C_2} \right)$$

$$\Rightarrow \frac{L_1}{C_4} + \frac{R_1}{j\omega C_4} = R_3 R_2 + \frac{R_3}{j\omega C_2}$$

Real:-  $\frac{L_1}{C_4} = R_3 R_2 \Rightarrow \boxed{L_1 = R_3 R_2 C_4}$

Im:-  $\frac{R_1}{C_4} = \frac{R_3}{C_2}$   
 $\Rightarrow \boxed{R_1 = \frac{R_3 C_4}{C_2}}$


$$Q = \frac{\omega \left( \frac{R_3 R_2 C_4}{C_2} \right)}{\frac{R_3 C_4}{C_2}} = \omega C_2 R_2$$

$\boxed{Q \propto C_2}$


only Low Quality factor is achieved ( $Q < 10$ )

High  $Q \cdot F \rightarrow$   
 Inductive React  $\uparrow$   
 Low Resist  $\downarrow$   
 Low  $Q \cdot F \rightarrow$   
 Inductive React  $\downarrow$   
 High Resist  $\uparrow$


5) Anderson's Bridge:

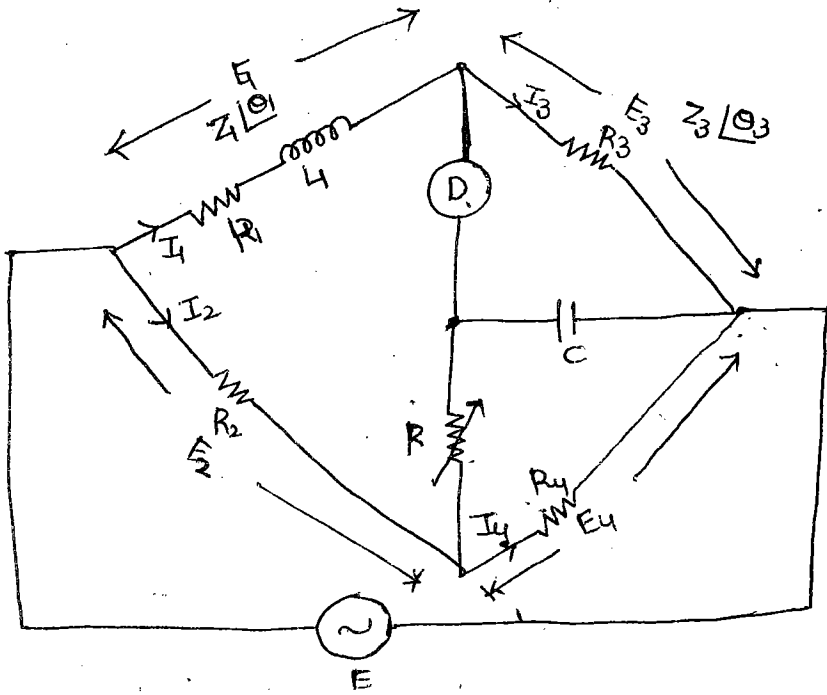

\* Accu  
\* Accu  
Meas

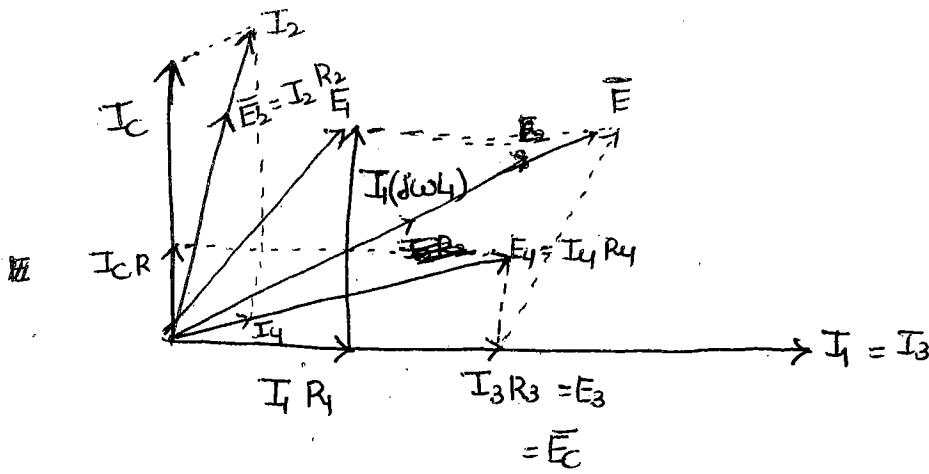

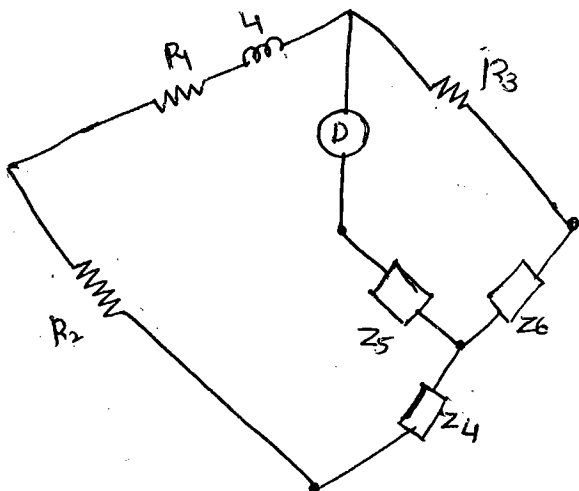First convert '5' point Bridge to 4-point Bridge



$$Z_4 = \frac{R(R_4)}{R(R_4) + R \left( \frac{1}{j\omega C} \right) + \frac{R_4}{j\omega C}}$$

$$Z_5 =$$

$$Z_6 = \frac{R(R_4)}{R + R_4 + \frac{1}{j\omega C}}$$

D-  
G  
\* Pan



$$Z_5 = \frac{\left(\frac{1}{j\omega C}\right)(R)}{R_1 + R_4 + \frac{1}{j\omega C}}$$

on balancing equations,

$$R_1 = \frac{R_2 R_3}{R_4}$$





$$L = \frac{CR_3}{R_4} (R_2 R + R R_4 + R_2 R_4)$$

~~$$\phi = \frac{\omega L}{R_4}$$~~

to be obtained here due to  $\phi$  factor is measured when only at resonance which cannot be obtained here due to invariable capacitor

- \* Accurate Bridge for Inductance - Anderson's Bridge
- \* Accurate Bridge for Quality factor - Hay's Bridge

### Measurement Of Capacitance (C):-

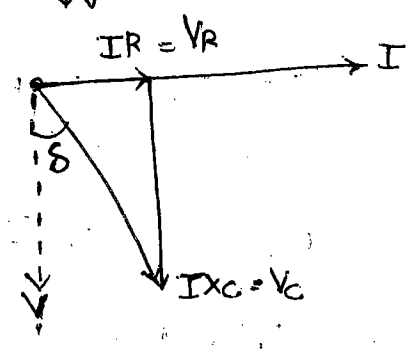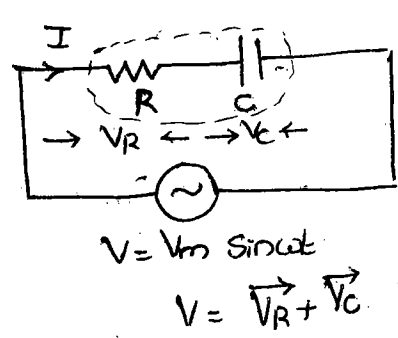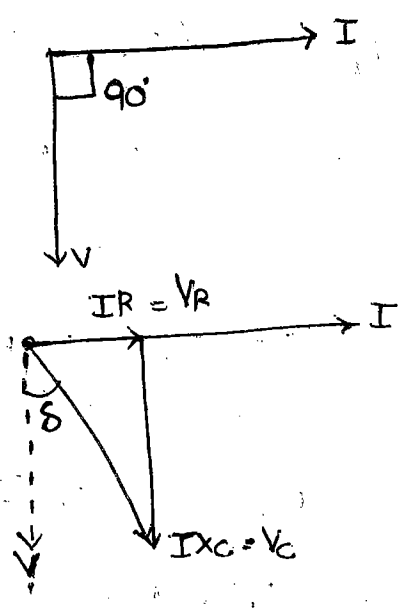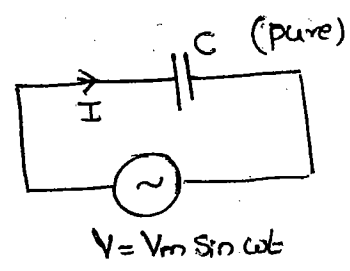

$\delta \rightarrow$  Loss Angle

\* In pure capacitor, the loss angle is '0'

\* In

$$\tan \delta = \frac{V_R}{V_C} = \frac{IR}{IX_C}$$


D-Factor (Quantity of  $\downarrow$  determines capacitance) =  $\frac{R}{X_C} = \frac{R}{1/\omega C}$

Quality of capacitor =  $\omega CR$

\* Pure capacitor, D-factor is '0'  $\Rightarrow \tan \delta = \omega CR$

$$\frac{R(R_4)}{R + \frac{1}{j\omega C} + R_4 \left(\frac{1}{j\omega C}\right)}$$

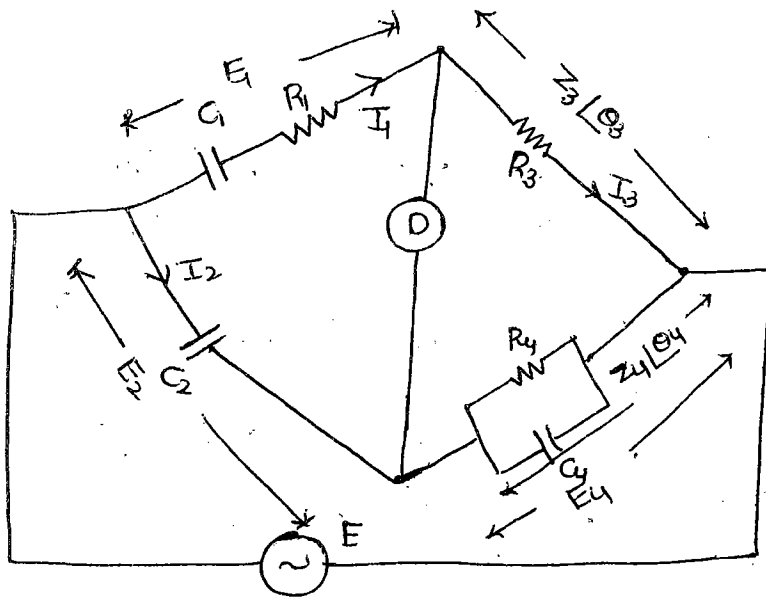- (1) ~~Desauty's Bridge~~ } Not Required  
 (2) ~~Modified Desauty's Bridge~~ }  
 ✓ (3) Schering Bridge (Accurate)



At Balance,

$$Z_1 Z_4 = Z_2 Z_3$$

$$\left( R_1 + \frac{1}{j\omega C_1} \right) \left( R_4 \parallel \frac{1}{j\omega C_4} \right) = \left( \frac{1}{j\omega C_2} \right) R_3$$

$$\Rightarrow \left( R_1 + \frac{1}{j\omega C_1} \right) \left( \frac{R_4}{R_4 + \frac{1}{j\omega C_4}} \right) = \frac{R_3}{j\omega C_2}$$

$$\Rightarrow \left( \frac{R_1 j\omega C_1 + 1}{j\omega C_1} \right) \left( \frac{j\omega R_4}{R_4 j\omega C_4 + 1} \right) = \left( \frac{R_3}{j\omega C_2} \right)$$

$$(R_1 j\omega C_1 + 1) (R_4) (j\omega C_2) = (R_3 j\omega C_1) (R_4 j\omega C_4 + 1)$$

$$\Rightarrow R_1 R_4 (-1) \omega^2 C_1 C_2 + R_4 (j\omega C_2) = R_3 R_4 (-1) \omega^2 C_1 C_4 + R_3 j\omega C_1$$

Im:-  $R_4 C_2 = R_3 C_1$

$$\Rightarrow C_2 = \frac{R_3 C_1}{R_4}$$

Real:-  $R_1 R_4 C_1 C_2 = R_3 R_4 C_1 C_4$


$$\Rightarrow R_1 C_2 = R_3 C_4$$

- D.C.

$$D\text{-factor} = \omega G R_1 = \omega \left( \frac{C_2 R_4}{R_3} \right) \left( \frac{R_3 \omega C_1}{C_2} \right)$$

$$= \omega R_4 C_1 \quad 41$$

Measurement of frequency (Wien's Bridge)

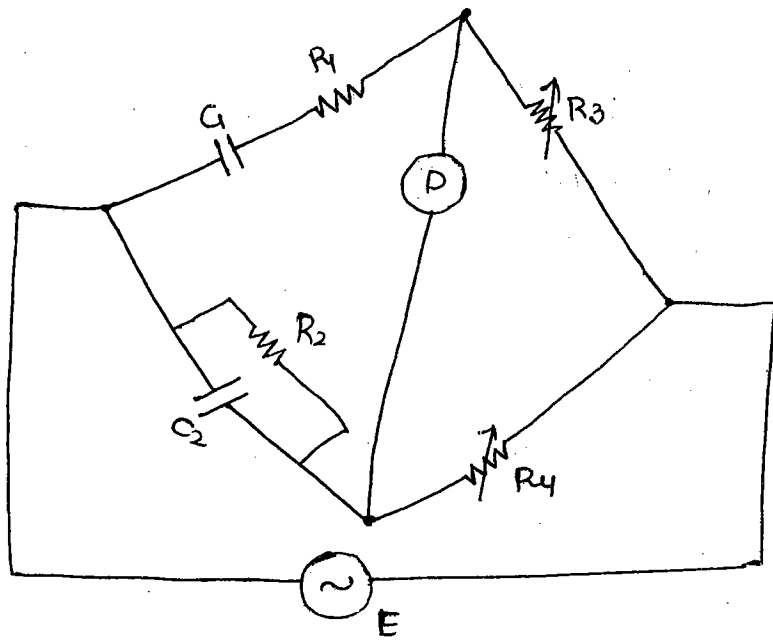

$$\Rightarrow \left( R_1 + \frac{1}{j\omega C_1} \right) (R_4) = R_3 \left( R_2 \parallel \frac{1}{j\omega C_2} \right)$$

$$R_1 R_4 + \frac{R_4}{j\omega C_1} = R_3 \left( \frac{\frac{R_2}{j\omega C_2}}{R_2 + \frac{1}{j\omega C_2}} \right)$$

$$R_1 R_4 + \frac{R_4}{j\omega C_1} = \frac{R_3 R_2}{R_2 j\omega C_2 + 1}$$

$$\Rightarrow \left( \frac{R_1 R_4 j\omega C_1 + R_4}{j\omega C_1} \right) = \left( \frac{R_3 R_2}{R_2 j\omega C_2 + 1} \right)$$

$$\Rightarrow R_2 R_1 R_4 (-1) \omega^2 C_1 C_2 + R_4 R_2 (j)\omega C_2 + R_1 R_4 j\omega C_1 + R_4 = R_3 R_2 j\omega C_2$$

Equate Real parts

$$R_4 = R_3 R_1 R_4 (-\omega^2) C_1 C_2$$

$$\Rightarrow \omega^2 C_1 C_2 R_1 R_4 = 1$$

$$\omega^2 = \frac{1}{R_1 R_2 C_1 C_2} \Rightarrow f = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$

(P)  
1)

Identify the Bridge  
Sol: Owen's Bridge

Venugopal Sir  
86 86 211 233  
86 86 211 200

$$R_3 = 10 \Omega, R_2 = 842 \Omega, C_2 = 0.135 \mu F, C_4 = 1 \mu F$$

$$R_4 = \frac{R_3 C_4}{C_2} = \frac{(10)(1 \times 10^{-6})}{0.135 \times 10^{-6}} = 74.07 \Omega$$

$$L_1 = R_3 R_2 C_4 = (10)(842)(1 \times 10^{-6}) = 8.42 \text{ mH}$$

2)

$$C_2 = 500 \mu F = 500 \text{ pF}$$

$$R_3 = 300 \Omega, R_4 = 72.6 \Omega$$

$$C_4 = 0.148 \mu F$$

$$Q = ?, \delta = ?$$

$$Q = \frac{C_2 R_4}{R_3} = \frac{(500)(72.6) \times 10^{-12}}{300} = 121 \text{ pF}$$

$$\tan \delta = \omega R_4 C_4 = 2\pi(50)(72.6)(0.148 \times 10^{-6})$$

$$\delta = 0.193$$

3)

$$R_4 = 5.1 \text{ k}, C_4 = 2 \mu F, R_3 = 7.9 \text{ k}, R_2 = 790 \Omega$$

$$L_1 = \frac{R_2 R_3 C_4}{1 + \omega^2 R_4^2 C_4^2} = \frac{(790)(7.9 \times 10^3)(2 \times 10^{-6})}{1 + (1000)^2 (5.1 \times 10^3)^2 (2 \times 10^{-6})^2} = 0.118 \text{ H}$$

$$R_1 = \frac{R_4 \omega^2 R_2 R_3 C_4^2}{1 + \omega^2 R_4^2 C_4^2} = \frac{(5.1 \times 10^3)(1000)^2 (790)(7.9 \times 10^3) \times (2)^2 \times 10^{-12}}{1 + (1000)^2 (5.1 \times 10^3)^2 (2 \times 10^{-6})^2} = 1.2 \text{ k}\Omega$$

$$\omega = 1000 \text{ rad/sec}$$

4)

$$R_3 = 1000 \Omega$$

$$C_2 = 50 \text{ pF}$$

$$C_1 = \frac{\epsilon A}{d} = \frac{\epsilon_0 \epsilon_r A}{d}$$

$$= \frac{8.85 \times 10^{-12} \times 2.3 \times (314 \times 10^{-4})}{0.3 \times 10^{-2}}$$

$$\tan \delta = \omega G R_1$$

$$\tan 9^\circ = (2\pi \times 50) (213.14 \times 10^{-12}) R_1$$

$$\Rightarrow R_1 = 2.36 \text{ M}\Omega$$

$$R_4 = \frac{G R_3}{C_2}$$

$$= 4.26 \text{ k}\Omega$$

$$C_4 = \frac{C_2 R_4}{R_3}$$

$$= \frac{(50 \times 10^{-12})(2.36) \times 10^6}{1000}$$

$$= 0.118 \text{ }\mu\text{F}$$

$$= 0.118 \text{ H}$$

$$= 118 \text{ mH}$$

$$790(7.9 \times 10^3) \times (2) \times 10^{-12}$$

$$3^2 (2 \times 10^6)^2$$

$$2 \text{ k}\Omega$$


$$\times 10^{-4}$$

# Measurement OF POWER

- 1) Dc Power  $\Rightarrow P = VI$  ↗ R-Load
  - 2) Ac Power  $\Rightarrow P = VI \cos \phi$
- $\downarrow$  DC (PMMC)  $\downarrow$  DC  
 $\downarrow$  MIX MIX PF  
 Not Accurate Value

Measurement of Dc power:

V-A method

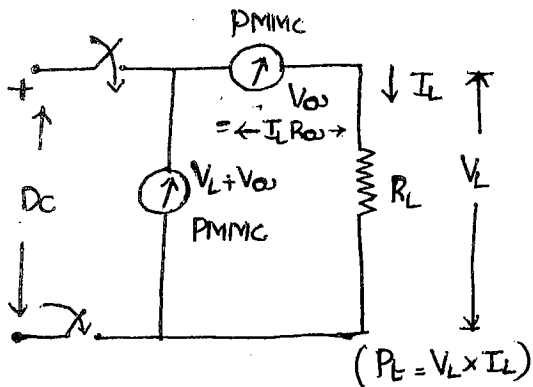


$$\begin{aligned}
 P_m &= \text{Volt} \times \text{Amp} \\
 &= (V_L + V_{0v}) * I_L \\
 &= V_L I_L + V_{0v} I_L \\
 &\quad \downarrow I_L R_{0v}
 \end{aligned}$$

$$P_m = P_L + I_L^2 R_{0v}$$

$\Rightarrow$  1)  $P_m > P_L$

- 2) Error is due to Ammeter (Instrument nearer to load)
- 3) Error is min. when  $I_L$  is less which happens for high Resistive load

A-V method

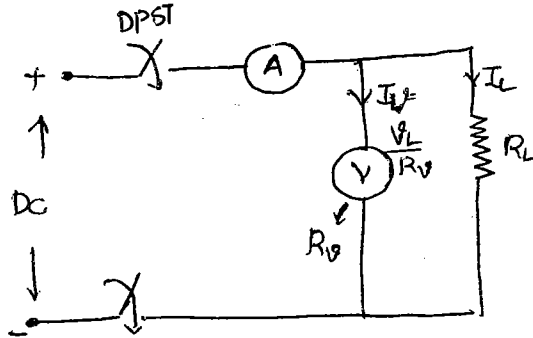

$$\begin{aligned}
 P_m &= V_L \times (I_L + I_v) \\
 &= V_L I_L + V_L I_v \\
 &= V_L I_L + V_L \left( \frac{V_L}{R_v} \right) \\
 &= P_L + \frac{V_L^2}{R_v}
 \end{aligned}$$

$$P_m = P_L + \frac{V_L^2}{R_v}$$

1)  $P_m > P_L$

- 2) Error is due to voltmeter (Instrument nearer to load)
- 3) Error is min when  $I_L$  is less, it occurs when  $I_L$  is more which happens for Light Resistive loads.



Measurement of Ac power :-

Ph  
Ac  
↓  
N



\* the  
are  
carry  
\* the  
Press  
will  
show

\* Both  
diff.

\* Let  
i.e,

\* Ino

meter  
Assu  
Volto:  
Ass  
Pure

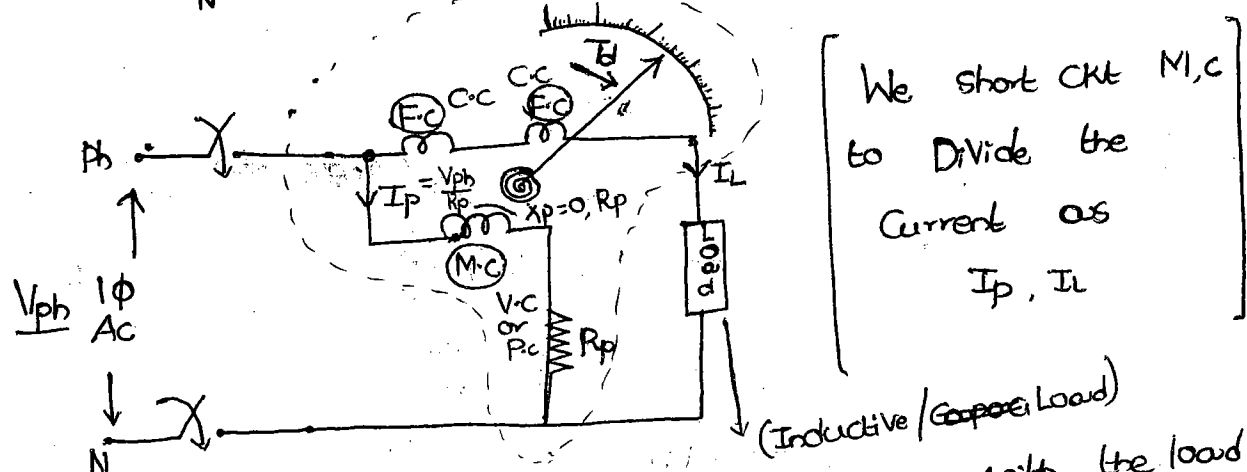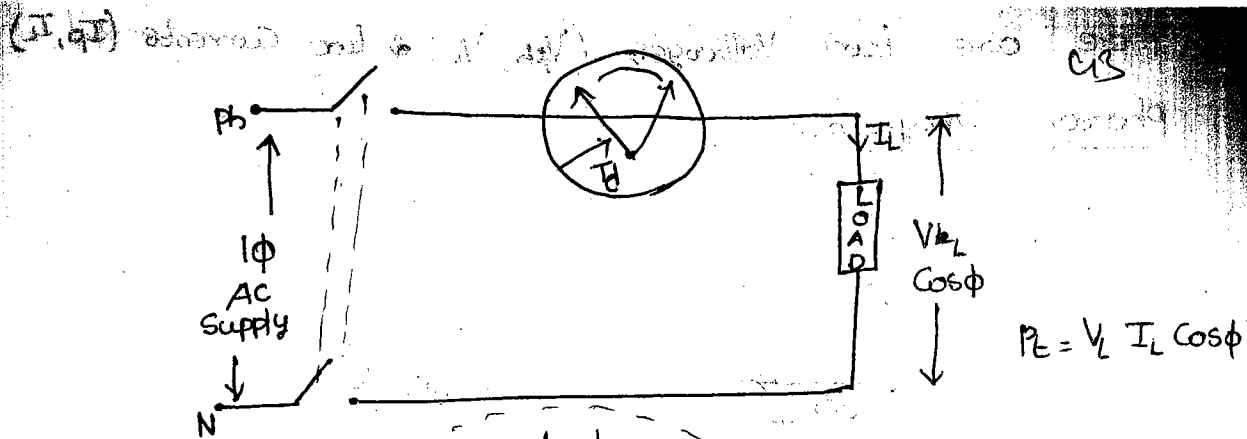

We short ckt M.C to Divide the current as  $I_p, I_L$

- \* The coils which are connected in series with the load are called Current Coils (Same as fixed coil) which will carry a full load current ( $I_L$ ) as shown in the fig.
- \* The coil which is connected across the supply is called Pressure Coil (Voltage Coil) [same as moving coil] which will proportional current of Supply Voltage ( $I_p$ ) as shown in fig.

- \* Both the coils are connected in || so that two diff. currents flow through the coils ( $I_L, I_p$  respectively)
- \* Let us consider the load is lagging load (Inductive load) i.e,  $I_L$  lags  $V_L$  by angle ' $\phi$ '

★ In order to measure the AC power by using this meter we have to consider two Assumptions inside the meter


- ★ Assumption 1: The Supply Voltage is equal to load Voltage i.e, drops in Current Coil Neglected.
- ★ Assumption 2: The pressure Coil is assumed to be purely and highly Resistive in nature

$$X_D = 0$$

\* There are two Voltages ( $V_{ph}$ ,  $V_L$ ) & two Currents ( $I_p$ ,  $I_L$ )

W1

Phasor Diagram:

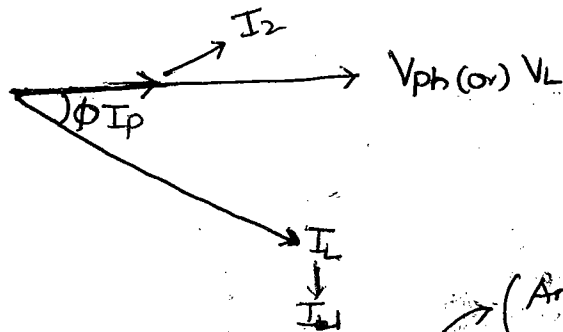

$$T_d = I_1 I_2 \cos(\phi) \frac{dM}{d\theta} \rightarrow P_e$$

$$= I_L I_p \cos \phi \frac{dM}{d\theta}$$

$$= I_L \left( \frac{V_{ph}}{R_p} \right) \cos \phi \frac{dM}{d\theta}$$

$$\Rightarrow T_d = \boxed{I_L \left( \frac{V_L}{R_p} \right) \cos \phi \frac{dM}{d\theta}} \Rightarrow P_e$$

(True power error)

$$T_d \propto V_L I_L \cos \phi$$


(AC Power)

13/5/12  
(6 to 8:30)

Error due to Pressure Coil Inductance:

\* Earlier we assumed pressure coil is purely resistive in nature. But in practice, it cannot be purely resistive.

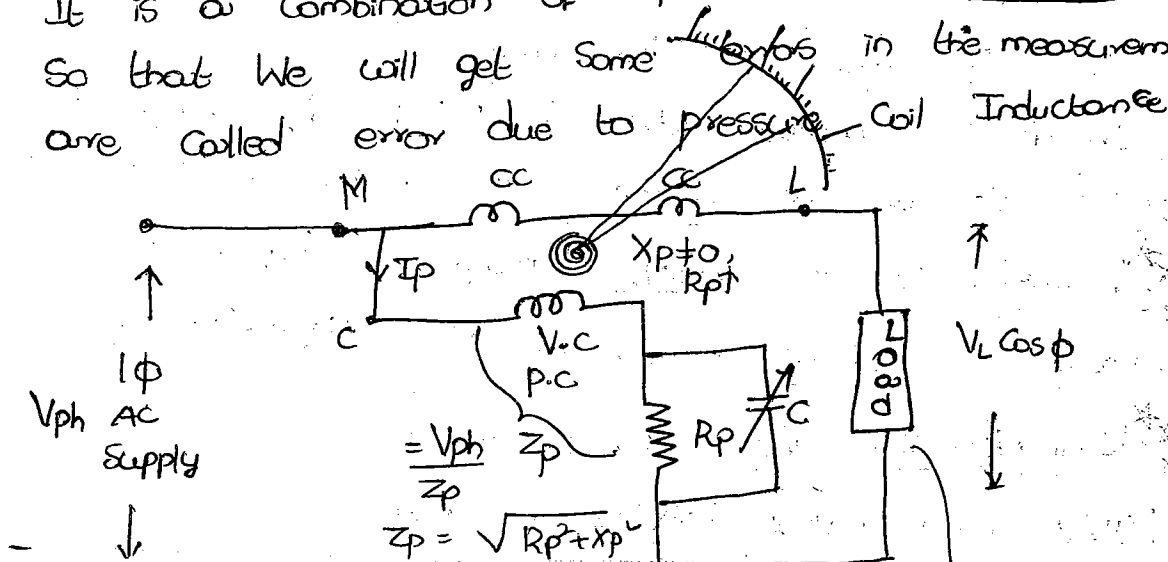It is a combination of  $X_p$  &  $R_p$ , i.e.,  $X_p \neq 0$ . So that we will get some errors in the measurement are called error due to pressure coil inductance.






$(I_p, I_L)$

Where  $Z_p = \sqrt{R_p^2 + X_p^2}$

Where  $Z_p$  is pressure Coil Impedance,  
 $\beta$  is pressure Coil Impedance Angle.

Phasor Diagram :

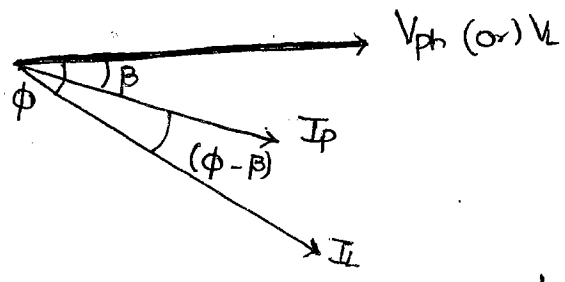

$$T_d = I_1 I_2 \cos(\phi - \beta) \frac{dM}{d\theta} \Rightarrow P_M$$

$$= I_L \left( \frac{V_L}{Z_p} \right) \cos(\phi - \beta) \frac{dM}{d\theta}$$

\*  $P_M > P_L$

$$T_d = I_L \left( \frac{V_L}{R_p} \cos \beta \right) \cos(\phi - \beta) \frac{dM}{d\theta} \Rightarrow P_M - (2)$$

$$P_m \times CF = P_L$$

\*  $CF = \frac{P_L}{P_m} = \frac{\cos \phi}{\cos \beta \cos(\phi - \beta)}$

\*  $P_m \times \frac{\cos \phi}{\cos \beta \cos(\phi - \beta)} = P_L$

\*  $C.F < 1$

\*  $\% \text{ error} = \left( \frac{P_m - P_L}{P_L} \right) \times 100$

$$= \left( \frac{P_m}{P_L} - 1 \right) \times 100$$

\*  $\% \text{ error} = + \left( \frac{1}{C.F} - 1 \right) \times 100$

\*  $\% \text{ error} = + (\tan \phi \tan \beta) \times 100$


Resistive  
 resistive.  
 ≠ 0  
 measurement  
 change

p

These formulae will be valid only when it is  
 lagging loads.

air

In case of leading loads:-

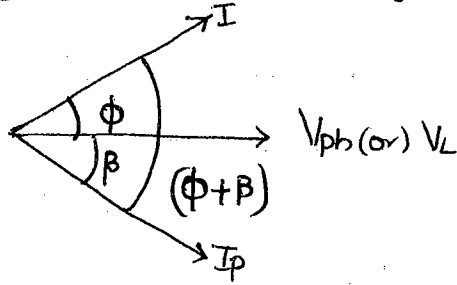

$$T_d = I_L \left( \frac{V_L}{R_p} \right) \cos \phi \frac{dM}{d\theta} \rightarrow P_e$$

$$T_d = I_L \left( \frac{V_L}{Z_p} \right) \cos(\phi + \beta) \frac{dM}{d\theta} \rightarrow P_m$$

$$P_m < P_e$$

$$T_d = I_L \left( \frac{V_L}{R_p} \right) \cos \beta \cos(\phi - \beta) \frac{dM}{d\theta} = P_m \rightarrow (2)$$

$$P_m \times C.F = P_e$$

$$C.F = \frac{P_e}{P_m} = \frac{\cos \phi}{\cos \beta \cos(\phi + \beta)}$$

$$P_m \times \frac{\cos \phi}{\cos \beta \cos(\phi + \beta)} = P_e$$

$$C.F > 1$$

$$\therefore \text{Error} = \left( \frac{P_m - P_e}{P_e} \right) \times 100$$

$$\therefore \text{error} = - \left( \frac{1}{C.F} - 1 \right) \times 100$$


$$\therefore \text{error} = - \left( \tan \phi \tan \beta \right) \times 100$$

(To Minimise all these errors, it is ample to make the  $X_p = 0$ , to do that)

\* The error due to pressure Coil Inductance can be reduced by connecting a capacitor across  $R_p$  in such a way that the capacitive reactance is cancelled out by inductive reactance of pressure coil. then the pressure coil is purely resistive. The

value of  $C = 0.4 \frac{L_p}{R_p^2}$

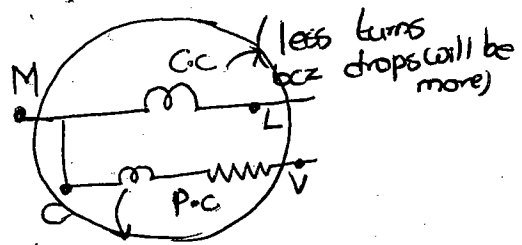\* If the manufacturer shorts M, c it cannot be used as Ammeter, Voltmeter



\* Base

a)

(III)

(

Error

→ Base

a)

1)

1) AC  
See ↓

2)

ε

3)

4)

ε


\* Mc

\* Based on Connections, We have two types of machines

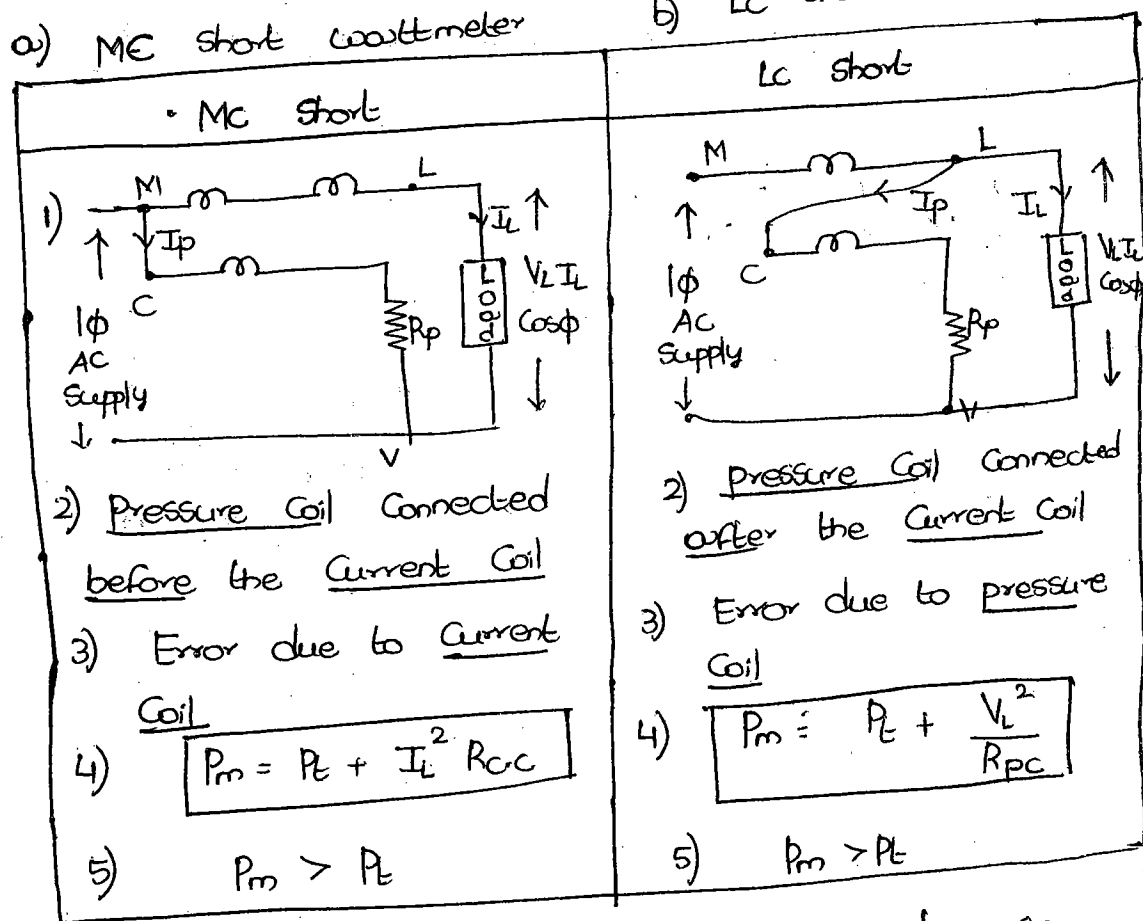- a) M-C short Wattmeter
  - b) LC short Wattmeter
- (III<sup>r</sup> to Voltmeter - Ammeter method) (III<sup>r</sup> to Ammeter - Voltmeter method)  
 (Error due to Current Coil) (Error due to pressure Coil)

Error due to Coil Connections :-

→ Based on Coil Connections, we have two types of Wattmeter




\* MC short is used more frequently because

$$P = I_{cc} \cdot I_{pc} \cos(\theta) \frac{dM}{d\theta}$$

$$MC, P = I_L \cdot I_p \cos(\theta) \frac{dM}{d\theta}$$

$$LC, P = (I_L + I_p) I_p \cos(\theta) \frac{dM}{d\theta}$$

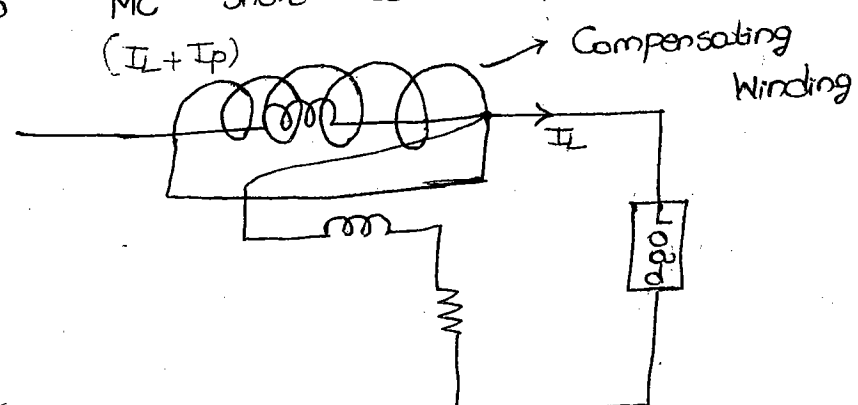Here Current Coil carries extra current compared to MC short connection; which increases the error  $(I_L + I_p)$



be  
 p in  
 e is  
 ssure coil.  
 be  
 rms  
 ops will be  
 more)


Current through <sup>Current</sup> Coil =  $I_L + I_p$

Flux =  $\phi_L + \phi_p$

⇒ To reduce  $\phi_p$ , flow a reverse current  $I_p$  in current coil by using a Compensating Winding

→ Compensating Winding is wound on current coil from 'L' and brought again to 'L'

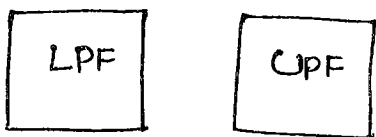→ In general, we use Mc short and don't need compensating Wdg (Necessary in case of Lc short wattmeter)



↳ For Low PF,  $\cos\phi \downarrow$   
 $T_d \propto \cos\phi$   
 $T_d \downarrow$

↳ Unity power factor

Resistance ( $\downarrow$ )  
 Compared to LPF

Deflection is not obtained

For that purpose

$$T_d = I_L \left( \frac{V_L}{R_{pp}} \right) \cos\phi \left( \frac{dM}{d\theta} \right)$$

$R_p$  is increased for that


\* Here, pressure coil resistance is increased for that

Measurement of poly phase power :-  
 ↓  
 N-phase  
 Blondel's

\* According to Blondel's theorem, the no. of wattmeters reqd to measure the total power in N-phase system is N (or) N-1 depends upon coil connections.

\* When separate neutral point is available in system, No. of wattmeters = N


\* When the neutral point not available.

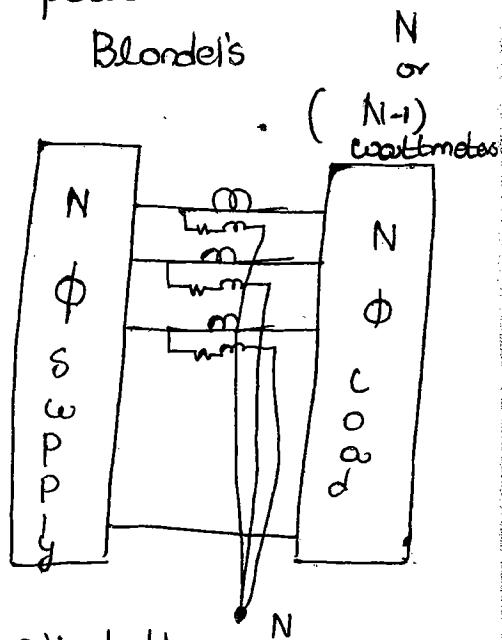

Measurement of 3- $\phi$  power  
 $N=3$   $\left\{ \begin{array}{l} \text{② Wattmeters} \\ \text{③ wattmeters} \end{array} \right.$

46

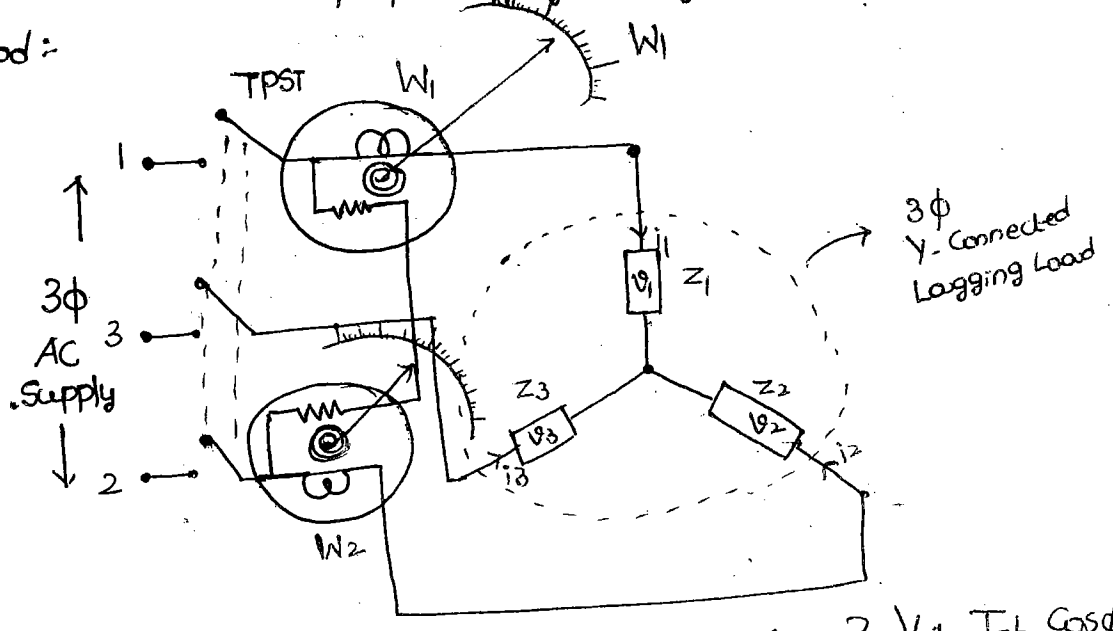Measurement of 3 $\phi$  power by using two wattmeter method:



$P_m = W_1 + W_2$ ;  $P_L = \sqrt{3} V_L I_L \cos \phi$  (or)  $3 V_{ph} I_{ph} \cos \phi$

$W_1 = i_1 V_{13} \cos (i_1, V_{13})$

$= I_{ph} \sqrt{3} V_{ph} \cos (30 - \phi)$

$I_{ph} = I_L$   
 $V_{ph} = \frac{V_L}{\sqrt{3}}$

$W_1 = \sqrt{3} V_{ph} I_{ph} \cos (30 - \phi)$

$= V_L I_L \cos (30 - \phi)$

$W_2 = i_2 V_{23} \cos (i_2, V_{23})$

$= I_{ph} (\sqrt{3} V_{ph}) \cos (30 + \phi)$

$W_2 = \sqrt{3} V_{ph} I_{ph} \cos (30 + \phi)$

$= V_L I_L \cos (30 + \phi)$

$P_m = W_1 + W_2 = V_L I_L \cos (30 - \phi) + V_L I_L \cos (30 + \phi)$

$= \sqrt{3} V_{ph} I_{ph} [\cos (30 - \phi) + \cos (30 + \phi)]$

$= \sqrt{3} V_{ph} I_{ph} (2 \cos 30 \cos \phi)$   
 $\hookrightarrow \sqrt{3/2}$

$\Rightarrow P_m = 3 V_{ph} I_{ph} \cos \phi$

$= W_1 + W_2$

$I_p$  is winding coil from


don't of  $L_c$

ctor

PF


or load

$N$  or  $(N-1)$  wattmeters

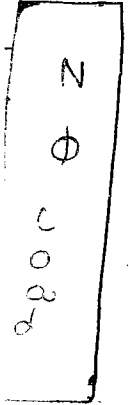

17/5/12  
(6 to 8:30P)

Measurement of Reactive Power

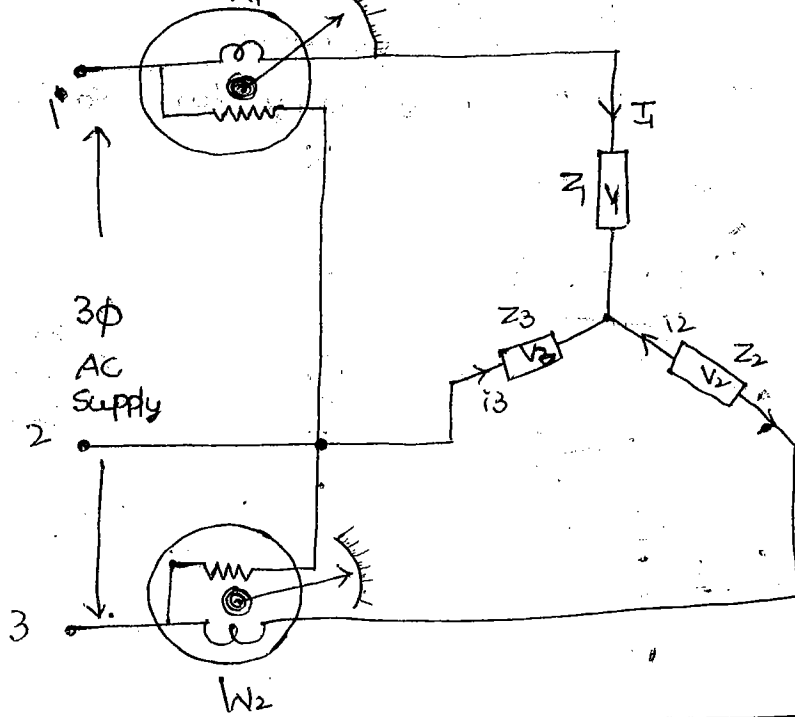

$$W_1 = \sqrt{3} V_{ph} I_{ph} \cos(30 - \phi) = V_L I_L \cos(30 - \phi) \rightarrow \text{Lag}$$

$$W_2 = \sqrt{3} V_{ph} I_{ph} \cos(30 + \phi) = V_L I_L \cos(30 + \phi) \rightarrow \text{Lag}$$

$$P = W_1 + W_2 = \sqrt{3} V_L I_L \cos \phi = 3 V_{ph} I_{ph} \cos \phi \rightarrow (1)$$

$$W_1 - W_2 = \sqrt{3} V_{ph} I_{ph} (\cos(30 - \phi) - \cos(30 + \phi))$$

$$= \sqrt{3} V_{ph} I_{ph} (2 \sin \frac{30}{2} \sin \phi)$$

$$W_1 - W_2 = (\sqrt{3} V_{ph} I_{ph} \sin \phi)$$

$$\Rightarrow \sqrt{3} (W_1 - W_2) = \sqrt{3} (\sqrt{3} V_{ph} I_{ph} \sin \phi)$$

$$= 3 V_{ph} I_{ph} \sin \phi$$

$$\phi \leftrightarrow (2)$$

Measurement of phase Angle

$$\frac{\phi}{\phi} = \frac{(2)}{(1)} =$$


$$\tan \phi = \frac{\sqrt{3} (W_1 - W_2)}{W_1 + W_2}$$

$$\phi = \tan^{-1} \left( \frac{\sqrt{3} (W_1 - W_2)}{W_1 + W_2} \right)$$

M/m of power factor



# Measurement of $\cos \phi$ power of 3 phase driving machines

40

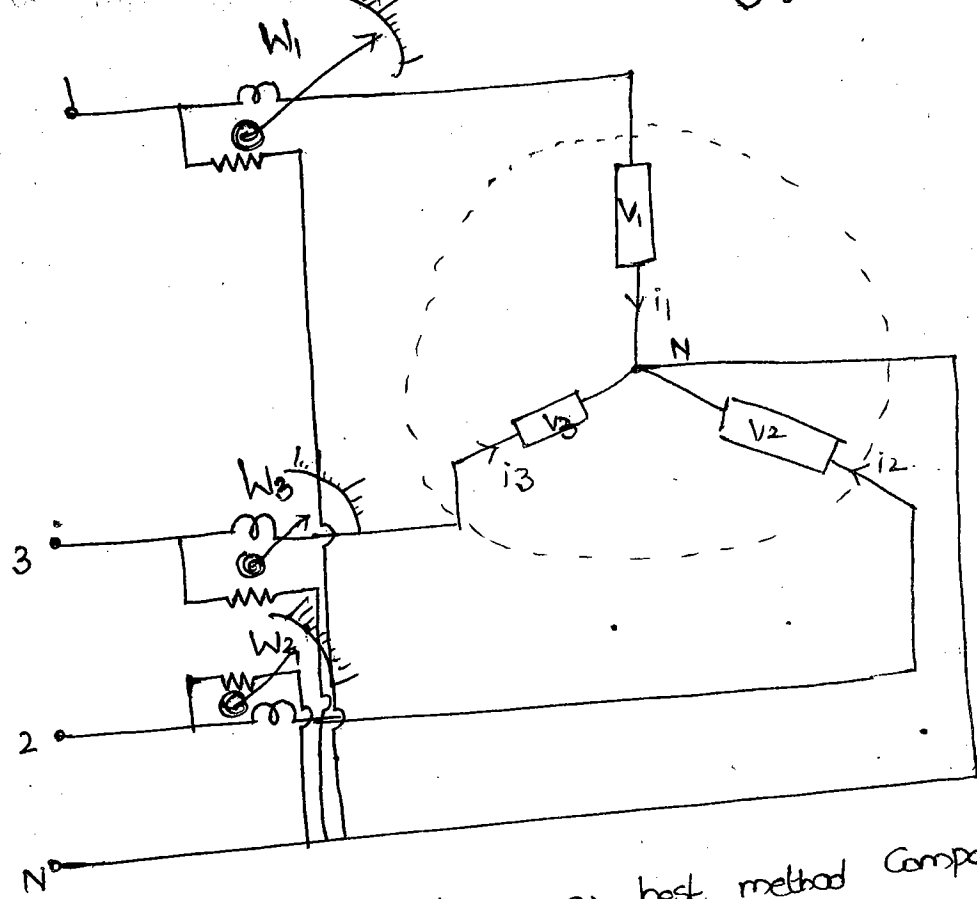

\* Two wattmeter method is a best method compared with three wattmeter method since error can be minimised.
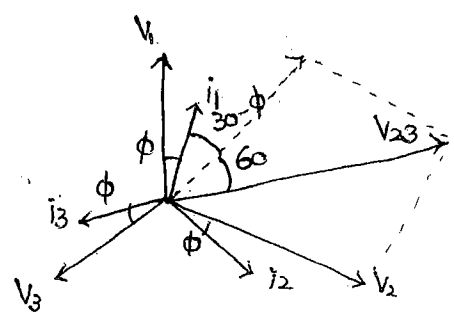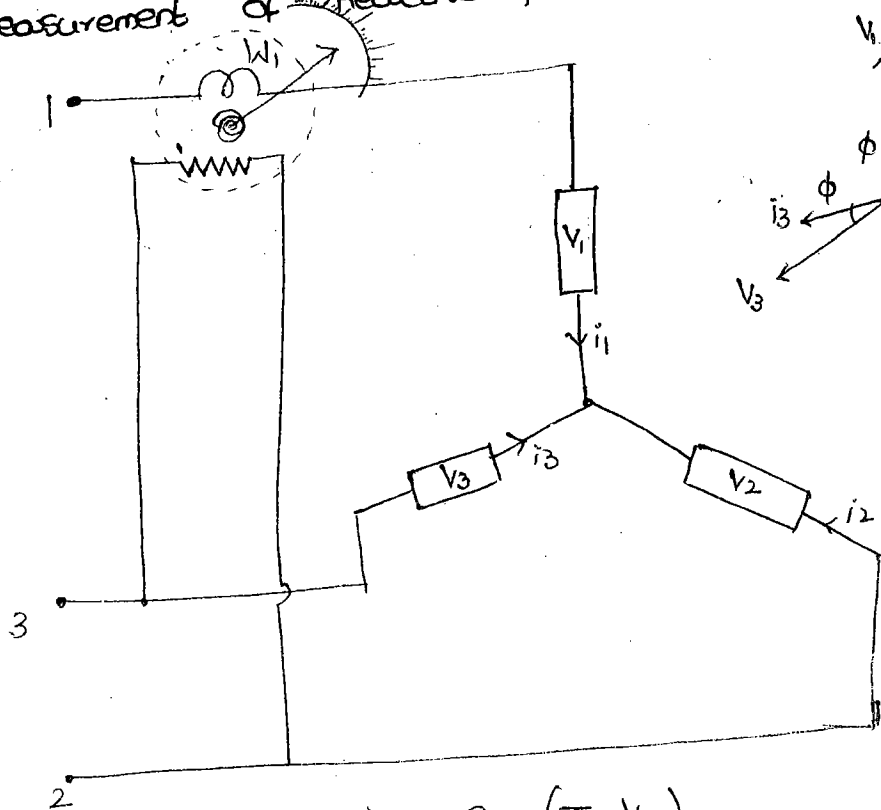
## Measurement of Reactive Power by 1 $\phi$ Wattmeter:



$$\begin{aligned}
 W1 &= i_1 V_{23} \cos(\angle i_1, V_{23}) \\
 &= I_{ph} (\sqrt{3} V_{ph}) \cos(\angle i_1 \& V_{23}) \\
 &= \sqrt{3} V_{ph} I_{ph} \cos(90 - \phi) \\
 &= \sqrt{3} V_{ph} I_{ph} \sin \phi
 \end{aligned}$$

$\curvearrowright$  Lag  
 $\curvearrowleft$  Lead  
 $\curvearrowright$  Lag  
 $\curvearrowleft$  Lead  
 $\cos \phi \rightarrow (1)$

$(+\phi)$   
 $(-\phi)$   
 $I_{ph} \sin \phi$   
 $n \phi$   
 $(2)$

$W2$   
 $i_2$   
 $\sqrt{2}$

$$\Rightarrow \sqrt{3} \times (W) = (\sqrt{3} V_{ph} I_{ph} \sin \phi) \sqrt{3}$$

$$= 3 V_{ph} I_{ph} \sin \phi = Q$$

1.  $\phi$   
 $\uparrow$   
 $\phi$   
 AC  
 $\downarrow$   
 N

\* Single wattmeter method is best method suitable for the measurement of 3 $\phi$  reactive power compared to 2-wattmeter method because errors are reduced

\* Manufacturer does not make M-C short because

- a) It cannot be used as Voltmeter, Ammeter
- b) It cannot be used as L-C short
- c) We cannot use it for reactive power measurement

$\phi$	P.F	Relation b/w $W_1$ & $W_2$
0°	unity	$W_1 = W_2$
30°	0.866 lag	$W_1 = 2W_2$
60°	0.5 lag	$W_2 = 0, W_1 = \text{Total power}$
90°	zero	$W_1 = -W_2$

$$W_1 = V_L I_L \cos(30 - \phi)$$

$$W_2 = V_L I_L \cos(30 + \phi)$$

2



\* When wattmeter reads -ve value, we interchange M, L terminals.

3- $\phi$ 4-Wire	Balanced load	Unbalanced load
3- $\phi$ 4-Wire	1	3
3- $\phi$ 3-Wire	2	2

3.



4. Measurement of power (Pbms)

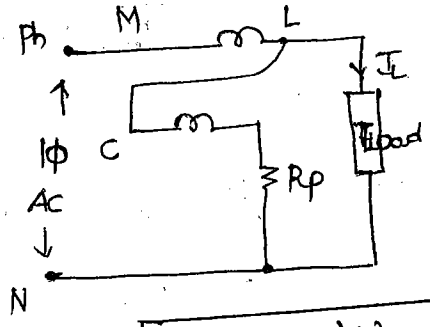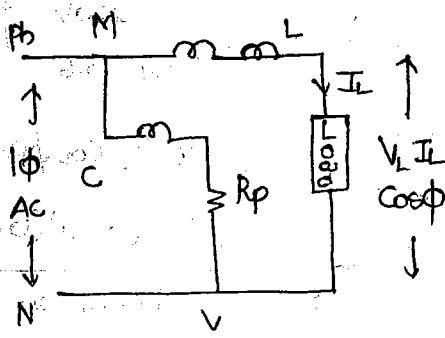

$$P_L = V_L I_L \cos \phi$$

$$= 250 \times 4 \times 1 = 1000 \text{ W}$$

$$P_m = P + \frac{V_L^2}{R_{pc}}$$

$$= 1000 + \frac{(250)^2}{12.5k}$$

$$= 1005$$

$$\% \text{ error} = \left( \frac{1005 - 1000}{1000} \right) \times 100$$

$$= 5 \%$$

$$P_m = P + I_L^2 R_{c.c}$$

$$= 1000 + (4)^2 \times (0.5)$$

$$= 1008$$

$$\Rightarrow \% \text{ Error} = \frac{1008 - 1000}{1000} \times 100$$

$$= \frac{8}{10} = 0.8 \%$$

2

$$X_p = \frac{1}{\%} R_p$$

$$\cos \phi = 0.5$$


lagging

Load lag  $\rightarrow$  +ve % error  
Load lead  $\rightarrow$  -ve % error

$$\% \text{ error} = \pm (\tan \phi \tan \beta) \times 100$$

$$= \pm (\sqrt{3} \times 0.01) \times 100$$

$$= \sqrt{3} \%$$

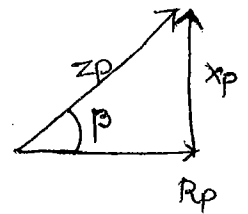

$$\tan \beta = \frac{X_p}{R_p}$$

$$= 0.01 \frac{R_p}{R_p}$$

3.

$$\cos \phi = \cos \left( \tan^{-1} \left( \sqrt{3} \left( \frac{W_1 - W_2}{W_1 + W_2} \right) \right) \right)$$

$$W_1 = 2000 \text{ W}; \quad W_2 = 500 \text{ W}$$

$$= \cos \left( \tan^{-1} \left( \sqrt{3} \left( \frac{1500}{2500} \right) \right) \right)$$

$$= 0.69 \text{ lagging}$$

stable for  
to 2  
because  
low

Measurement

$I_L \cos(30-\phi)$   
 $I_L \cos(30+\phi)$

exchange

balanced
and
3

4.

$R_{c.c} = 0.03 \Omega, R_{pc} = 6000 \Omega, I_L = 20A$

$V_L = 220V$

$\cos \phi = 0.6$

$P_m = P_L + I_L^2 R_{c.c}$

$= 2640 + (20)^2 (0.03)$

$= 2640 + (400) \left( \frac{3}{100} \right)$

$= 2652$

$P_L = V_L I_L \cos \phi$

$= (220)(20)(0.6) = 2640 W$

Current Coil is on Load Side - MC short

$\therefore \text{error} = \left( \frac{2652 - 2640}{2640} \right) \times 100 = 0.4545$

$X_p$   
 $\frac{X_p}{R_p}$   
 $\Rightarrow \frac{X_p}{R_p}$

5.

After modifying the connections, it will measure reactive power

Before modification

$W \phi = \sqrt{3} V_{ph} I_{ph} \sin \phi$

$= (500) (\sqrt{3}) (0.6)$

$= 519.6 VAR$

$V_{ph} I_{ph} \cos \phi = 400$

$V_{ph} I_{ph} (0.8) = 400$

$V_{ph} I_{ph} = 500$

6.

At Angle  $60^\circ$ , one of Wattmeter

Reads '0'

(All are  $5/60^\circ$ )

$W_1 = V_L I_L \cos(30 - \phi) = 100 \times 11.54 \cos 30 = 1000W$

$W_2 = V_L I_L \cos(30 + \phi)$

$= 100 \times 11.54 \cos(30 + 60)$

$I_L = I_{ph} = \frac{V_{ph}}{Z}$

$= \frac{100\sqrt{3}}{5}$

$= 11.54$

$V_{ph}$

\* Let

\* (

\* (

$I_a$   
 $I_{ph}$   
 $V_{ph}$   
of

7.

$P_L = (20)(200) = 4000$

$P_m = 4000 + (20)^2 (0.02)$

$= 4008$

$\therefore \text{error} = \left( \frac{4008 - 4000}{4000} \right) \times 100$

$= 0.2 \%$

$\cos \phi = \frac{\cos \beta}{\cos \beta \cos(\phi - \beta)}$   
 lagging

$CF = \frac{\cos \phi}{\cos \beta \cos(\phi + \beta)}$   
 leading


b. = 2410  
 (0.6) W  
 in Load  
 at

$X_p = 0.5 \cdot R = \frac{0.8}{\cos 26.56 \cos(36.56 - \cos 36.56)}$   
 $\frac{X_p}{R_p} = 0.5$   
 $\Rightarrow \tan \beta = 0.5$   
 $\tan \beta = 0.5$   
 $\beta = 26.56$

Measurement of Power factor

- $P = VI \cos \phi$   
 $\Rightarrow \cos \phi = \frac{P}{VI}$  (3 meters)
- $\cos \phi = \cos \left( \frac{\sqrt{3} (W_1 - W_2)}{W_1 + W_2} \right)$  (2 meters)
- Power factor meter


Dynamometer type P-f meter

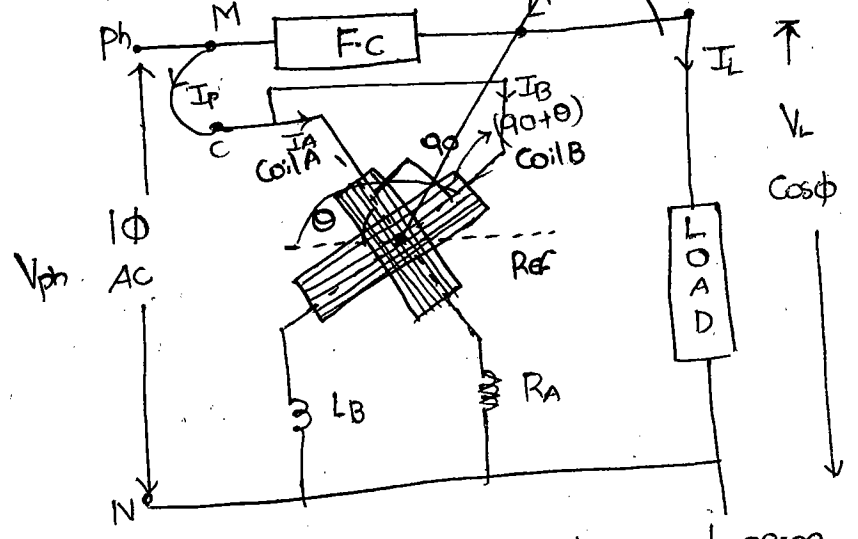

One fixed Coil  
 Two Movable Coils  
 (i.e., two pressure coils)  
 $P_L = V_L I_L \cos \phi$   
 3 - Currents  
 Two Voltages

- \* Let us consider the load is lagging load.
- \* Coil - A is assumed to be purely resistive
- \* Coil - B is assumed to be purely Inductive

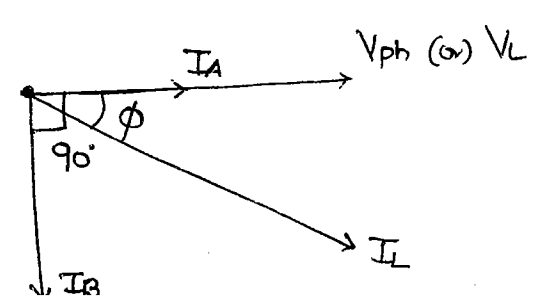$I_{A0}$  is in phase with  $V_{ph}$  because of 'RA'



$$T_d = I_1 I_2 \cos(\theta) \frac{dM}{d\theta}$$

$$T_{dA} = I_L I_A \cos \phi \frac{dM}{d\theta}$$

$$T_{dB} = I_L I_B \cos(90-\phi) \frac{dM}{d\theta}$$

$$M = M_{max} \cos \theta$$



$$\frac{dM}{d\theta} = -M_{max} \sin \theta$$

$$T_{dA} = I_L I_A \cos \phi \times -M_{max} \sin \theta$$

$$\Rightarrow T_{dB} = I_L I_B \cos(90-\phi) \times -M_{max} \sin(90+\theta)$$

Max. flux when  $\theta = 0$

Min flux when  $\theta = 90^\circ$

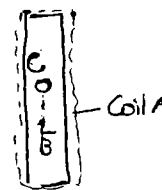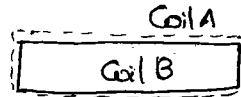

Two torques developed due to two moving coils

$\frac{dM}{d\theta}$  = Change of Mutual Inductance

18/5/12  
(6 to 8:30  
10)

In order to measure the p.f. by using this meter, we have to design both the moving coils in such a way that the resistance of the moving coil A is equal to the inductive reactance of the moving coil B

$$R_A = \omega L_B$$

$$R_A = X_B$$

$$I_A = I_B$$


$$\Rightarrow T_{dA} = T_{dB}$$

$$I_L I_A \cos \phi (-M_{max}) \sin \theta = I_L I_B \cos(90-\phi) (-M_{max}) \sin(90+\theta)$$

$$\Rightarrow \cos \phi \sin \theta = \sin \phi \cos \theta$$

$$\Rightarrow \tan \phi = \tan \theta$$

$$\Rightarrow \phi = \theta$$

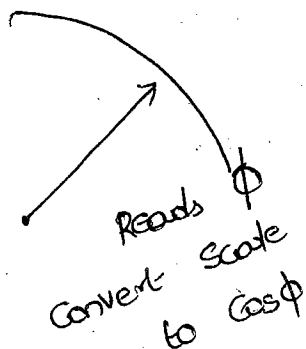

M/

Inc

Due

Two

(Ea

deve

disc


cu

7

16

torques  
 due to  
 moving  
 change of  
 mutual Inductance

18/5/12  
 (6 to 8:30P)  
 10)

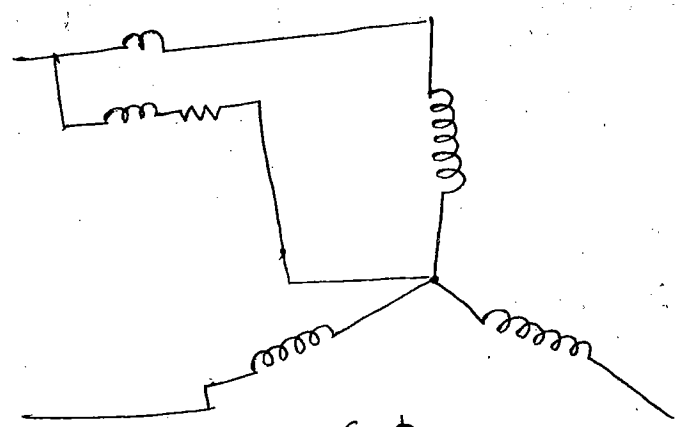

$$P = \sqrt{3} V_{ph} I_{ph} \cos \phi$$

$$5.54 \times 10^3 = \frac{400}{\sqrt{3}} \times 30 \times \cos \phi$$

$$\Rightarrow \cos \phi = 0.8$$

$$\sin \phi = 0.6$$

a)  $W = \sqrt{3} V_{ph} I_{ph} \sin \phi$   
 $= (\sqrt{3}) \left( \frac{400}{\sqrt{3}} \right) (30) (0.6)$   
 $= 7.2 \text{ KVAR}$


b) Total Reactive Power =  $\sqrt{3} \times 7.2 \text{ KVAR}$   
 $= 12.47 \text{ KVAR}$

M/M of Energy:

Energy = Power x time


$$\Rightarrow E = \int (\text{Power}) dt$$

Integrated type Instrument

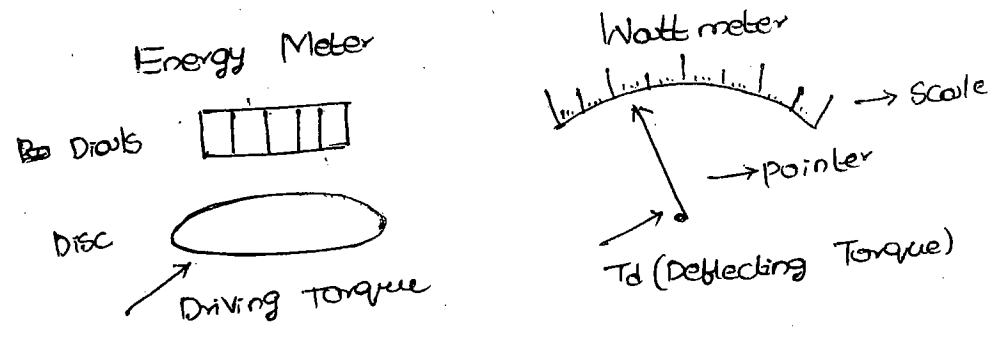

Induction effect

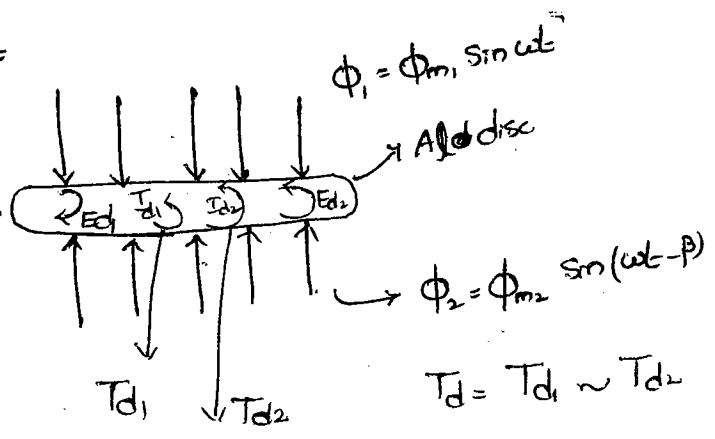Due to fluxes,  
 Two eddy currents  
 $(E_{d1} \& E_{d2})$   
 developed in the  
 disc in turn two  
 currents  $I_{d1}, I_{d2}$   
 these produce  $T_{d1}$   
 &  $T_{d2}$ . the net driving torque  
 is  $T_d = (T_{d1} \sim T_{d2})$




$$\phi_1 = \phi_{m1} \sin \omega t$$

$$\phi_2 = \phi_{m2} \sin(\omega t - \phi)$$

$$T_d = T_{d1} \sim T_{d2}$$

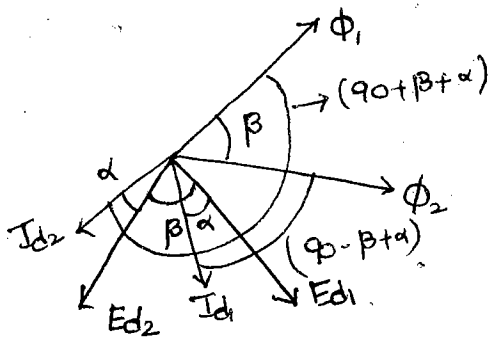$\cos(90 - \phi)$   
 $\sin(90 + \theta)$



AL  $\rightarrow$  98%

resistive

(remaining Inductor)

We   
 #

$\phi_1$  does not interlink with  $I_{d1}$  because angle almost  $90^\circ$

$$\cos 90^\circ = 0$$

$\phi_2$  does not interlink with  $I_{d2}$

$\phi_1$  interlink with  $I_{d2}$  to produce  $T_{d1}$  &  $\phi_2$  interlink with  $I_{d1}$  to produce  $T_{d2}$ .

$$\Rightarrow T_d = T_{d1} \sim T_{d2}$$

$$T_{d1} = \phi_1 I_{d2} \cos(\phi_1, I_{d2})$$

$$T_{d2} = \phi_2 I_{d1} \cos(\phi_2, I_{d1})$$

$$I_{d1} = \frac{E_{d1}}{Z}$$

$$I_{d2} = \frac{E_{d2}}{Z}$$

\* The which flux

Magne

\* The Shunt

Current

in fig

\* Both

\* Let

We have Assum 1)

the

Ass

2)

in

$$\left[ \begin{aligned} E_{d1} &= -N \frac{d\phi_1}{dt} \quad (\text{Acc. Faraday's law}) \\ (E_{d1}) &= N \frac{d\phi_1}{dt} \\ &= \frac{d}{dt} (\phi_{m1} \sin \omega t) \\ I_{d1} &= \frac{\phi_{m1} \cos \omega t (\omega)}{Z} \\ I_{d1} &= \frac{\bar{\phi}_1 \cdot \omega}{Z} \end{aligned} \quad \left[ \begin{aligned} (E_{d2}) &= N \frac{d\phi_2}{dt} \\ &= \frac{d}{dt} (\phi_{m2} \sin(\omega t - \beta)) \\ I_{d2} &= \frac{\phi_{m2} \cos(\omega t - \beta) \omega}{Z} \\ I_{d2} &= \frac{\bar{\phi}_2 \cdot \omega}{Z} \end{aligned} \right.$$

$$T_{d1} = \phi_1 \cdot \frac{\bar{\phi}_2 \omega}{Z} \left[ \cos(90 + (\beta + \alpha)) \right]$$

$$T_{d2} = \phi_2 \cdot \frac{\bar{\phi}_1 \omega}{Z} \left[ \cos(90 - (\beta - \alpha)) \right]$$

$$T_d = T_{d1} - T_{d2}$$


$$= k \phi_1 \phi_2 \left[ \sin(\beta - \alpha) - \sin(\beta + \alpha) \right]$$

$$T_d = k \phi_1 \phi_2 \sin \beta \cos \alpha$$

$$\boxed{T_d \propto \phi_1 \phi_2 \sin \beta \cos \alpha} \quad \alpha = 0$$

3% resistive winding of Inductor) interlink because t 90° 0 interlink

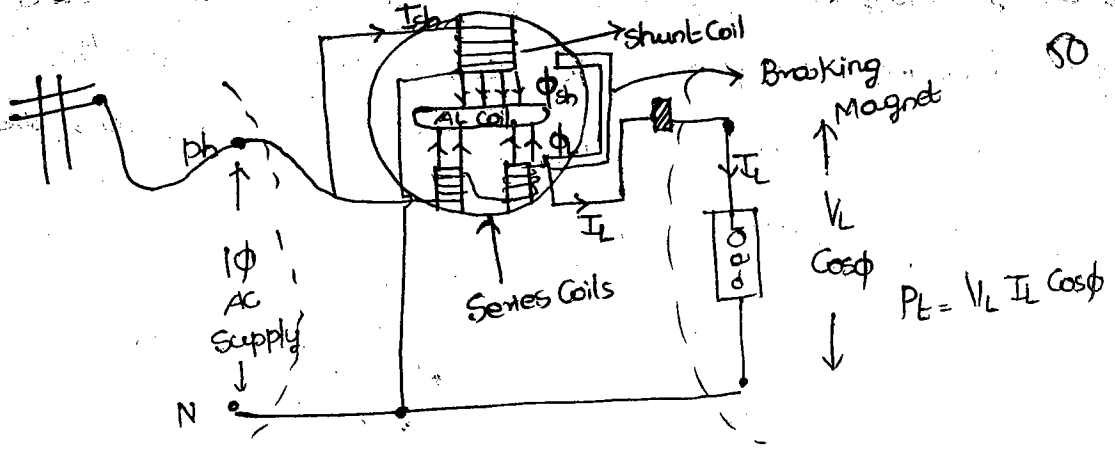We have to make  $T_d \propto V_L I_L \cos \phi$



\* The coil which are connected in series with a load which will carry a full load  $I_L$ , so that it will produce a flux as shown in fig. these magnets are called Series

Magnets

\* The coil which is connected across the supply is called Shunt Coil (same as pressure coil) which will carry a current  $I_{sh}$  so that it produces a flux  $\phi_{sh}$  as shown in fig. These magnets are called as shunt magnets.

\* Both coils are connected in parallel

\* Let us consider the load to be lagging load


In order to measure the energy by this meter we have to consider two Assumptions inside the meter

Assumption: 1

1)  $V_{ph} = V_L$  i.e, the supply Voltage is equal to the load Voltage i.e, drops in series coil neglected

Assumption: 2

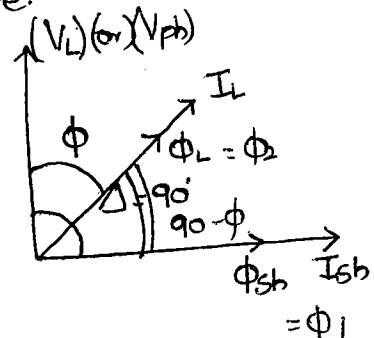2) The shunt coil is assumed to be purely Inductive in Nature.



$$T_d \propto \phi_1 \phi_2 \sin \beta$$

$$T_d \propto \phi_{sh} \phi_{L} \sin(90 - \phi)$$

$$T_d \propto I_{sh} V_L I_L \cos \phi$$

Dr. P. R. Rao

Braking Magnet: The Braking Magnet Will produce some braking torque ( $T_B$ ) which will see the disc to rotate at constant speed as long as the load is constant.

$$T_d \propto \text{Ac power}$$

$$T_B \propto \text{Speed of the disc (N)}$$

At steady state

$$T_d \propto T_B$$

$$\int (\text{Ac power}) dt \propto \int (\text{speed of the disc})$$

$$\text{Energy} \propto \text{No. of revolutions}$$

Meter Constant: The no. of revolutions should be made by the disc in order to indicate the exactly

1 kWhr consumption is called Meter Constant

$$\text{Meter Const} = \frac{\text{No. of Rev}}{\text{kWhr}}$$

5. Measurement of Energy

$$V_L = 230 \text{ V}, \quad I_L = 10 \text{ A}$$

$$\text{M.C} = 1800 \text{ rev/kWh}$$

Half Load

$$A_m = 80 \text{ revolutions}$$

$$\text{Time} = 138 \text{ sec}$$

1/2

⊗

Energy Consumed =

kWh

$$= \text{Power} \times \text{time}$$

$$= \frac{V_L I_L \cos \phi}{1000} \times \text{hr}$$

$$= \frac{(230)(10)}{1000} \times \frac{138}{3600}$$

$$\frac{10}{2} = I_L$$

(As it is out half load)

7.



$$\text{Meter Const} = \frac{\text{No. of revolutions}}{\text{kwh}}$$

51

$$\Rightarrow (kwh)_m = \frac{\text{No. of revolutions}}{M.C} = \frac{80}{1800} = 0.04444 \text{ kw/hr}$$

$$\% \text{ error} = 0.82$$

1.  $V_L = 240V$ ,  $M.C = 600 \text{ rev/kwh}$   
 $I_L = 10A$ ,  $\cos\phi = 0.8 \text{ lag}$   
 $\Delta = 86^\circ$

$$E_c = \text{kwh}$$

$$= \text{Power} \times \text{Time}$$

$$= \frac{V_L I_L \cos\phi}{1000} \times 1 \text{ hr} = \frac{240 \times 10 \times 0.8}{1000} \times 1 = 1.92 \text{ kwh}$$

$$M.C = \frac{\text{No. of rev}}{\text{kwhr}}$$

$$\Rightarrow \text{No. of rev} = M.C \times \text{kwhr} = 600 \times 1.92 = 1152$$

$$\text{Speed rps} = \frac{1152}{3600} = 0.32 \text{ Rps}$$

$$\% \text{ Error} = \frac{A_m - A_t}{A_t} \times 100$$

$$= \frac{V_L I_L \cos\phi - V_L I_L \sin(86 - \phi)}{V_L I_L \cos\phi} \times 100$$

$$= \frac{V_L I_L \sin(86 - \phi) - V_L I_L \cos\phi}{V_L I_L \cos\phi} \times 100$$

$$= \frac{\sin(86 - 0^\circ) - 1}{1} \times 100$$

$$= -0.24$$

$$\Delta = 90^\circ \text{ (Actually)}$$

But  $3^\circ$  departure  $\Delta = 87^\circ$

$$N_{FL} = 40$$

$$N_{FL/4} = ?$$

$$\left[ N \propto \text{AC power} \right]$$

$$\frac{138}{3600}$$

108 kwh

$$N \propto V_L I_L \sin(\Delta - \phi)$$

$$\frac{N_{FL}}{N_{\frac{FL}{4}}} \propto \frac{V_L I_L \sin(\Delta - \phi)}{V_L \left(\frac{I_L}{4}\right) \sin(\Delta - \phi)}$$

$$\Rightarrow \frac{40}{N_{\frac{FL}{4}}} = \frac{\sin(87 - 0^\circ)}{\sin(87 - 60^\circ)} \quad \begin{array}{l} \cos^{-1}(0.5) \\ = 60 \end{array}$$

$$\Rightarrow N_{\frac{FL}{4}} = 40 \times \frac{\sin 27}{\sin 87} = 4.54$$

Electronics measurement

18/07/2011

Review of DC voltmeter

Electronic Voltmeter


- ↳ Amplifier Type
- ↳ Rectifier Type
- ↳ Peak Type
- ↳ TC Type (Thermocouple)

Q-meter

Digital measurement  
voltage, time period of frequency, magnitude  
DVMA ET/C

Cathode ray oscilloscope

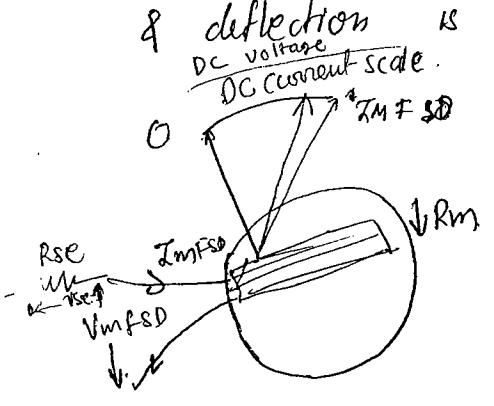Any analog measuring unit is a current measuring unit since current is the only analog quantity that is measurable & deflection is always produce due to current effect only



Ex :-  $0 - I_m, R_m$   
 $0.1V \leftarrow V_m FSD$   
 $\downarrow$   
 $1V \leftarrow V FSD$


DC voltmeter

DC voltmeter (Design) - A DC voltmeter consist of a dc ammeter i.e PMMC instrument with a high value multiplier resistance ( $R_{se}$ ) in series with the ammeter & the scale properly calibrated to read dc volts. multiplier is high value resistance  
DC current can be calibrated in DC scale

$V_m FSD = I_m FSD \times R$

the  $R_m$  = resistance to voltage rating  
 $R_{se}$  = series resistance

## \* Electric Circuit representation

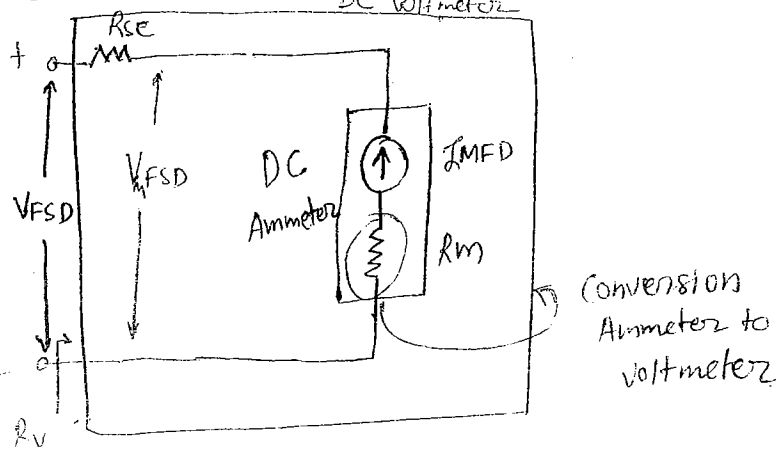

① Voltmeter resistance ( $R_v$ ) :-

\*  $\rightarrow R_v = \frac{V_{FSD}}{I_{mFSD}}$   $\rightarrow$  Full scale DC voltage range  
 Available Full scale current range

\*  $R_v = R_{se} + R_m$

\*  $R_v = R_m [M-1] + R_m$

$R_v = MR_m - R_m + R_m$

$R_v = MR_m$

\*  $R_v = \text{sensitivity} \times \text{voltage range}$

② Series Multiplier resistance ( $R_{se}$ )

\* Series current limiting resistance

\*  $R_{se} = R_v - R_m$

= i/p resistance of voltmeter - internal resistance of meter

=  $\frac{V_{FSD}}{I_{mFSD}} - R_m$

=  $R_m \left[ \frac{V_{FSD}}{I_{mFSD} \times R_m} - 1 \right]$

=  $R_m \left[ \frac{V_{FSD}}{V_{mFSD}} - 1 \right] \Rightarrow R_{se} = R_m [M-1]$

where  $M =$  Multiplying factor

$$M = \frac{V_{FSD}}{V_{MFSD}}$$

or  $M = \frac{R_{se} + 1}{R_m}$

(3) sensitivity of voltmeter ( $S_v$ )

$$S_v = \text{resistance / volt rating}$$

$$= \frac{\text{resistance}}{\text{voltmeter}} = \frac{\Omega}{V} \text{ or } \frac{k\Omega}{kV}$$


\* DC voltmeter have DC sensitivity

$$S_{dc} = \frac{R_v}{V_{FSD}} = \frac{V_{FSD} / I_{mfSD}}{V_{FSD}}$$

$$S_{vdc} = \frac{1}{I_{mfSD}}$$

sensitivity is also known as "Figure of merit"

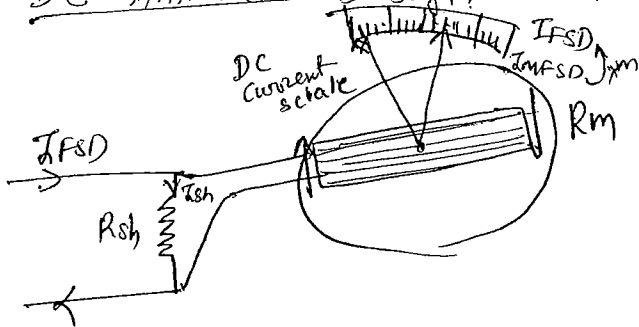~~DC Ammeter~~ Design:- \* A practical DC Ammeter consist of




a PMMC instrument with a low valued shunt resistance. Place across the coil & scale properly calculated

$$R_{sh} = \frac{R_m}{m-1}$$

where  $m =$  multiplying factor  
 $= \frac{I_{FSD}}{I_{mfSD}}$

\* PMMC is scale is linear.

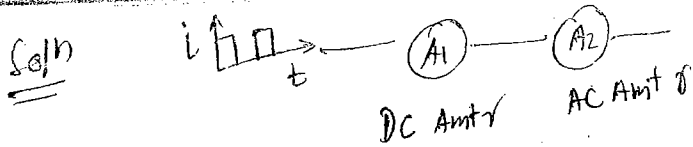\* DC Meter:- A DC meter is an avg measuring (or responding) avg indicating (or reading) meter linear scale & works for only DC i/p. Eg.  $\rightarrow$  PMMC



→ DC ammeter reading =  $I_{dc} = \frac{1}{2} \int_0^T 100 \text{ mA } dt = \frac{100 \text{ mA}}{2}$   
 $= 50 \text{ mA}$  (moving coil ammeter)

Note:- When square wave is given may be symmetrical or unsymmetrical

$I_{dc} = I_m \alpha$   
 where  $\alpha$  is duty cycle =  $\frac{t_{on}}{t_{on} + t_{off}}$

∴  $I_{dc} = 100 \text{ mA} \times \frac{1}{1+1} = \frac{100}{2} = 50 \text{ mA}$

→ AC ammeter reading =  $I_{rms}$   
 $= \sqrt{\frac{1}{2} \int_0^T (100 \text{ mA})^2 dt}$   
 $= \frac{100}{\sqrt{2}} = 70.7 \text{ mA}$


Note -  $I_{rms} = I_m \sqrt{\alpha}$   
 $= 100 \times \sqrt{\frac{1}{1+1}} = \frac{100}{\sqrt{2}} = 70.7 \text{ mA}$

Ques:- Crute An ammeter with internal resistance of  $50 \Omega$  give full scale deflection for  $50 \mu\text{A}$  current. The i/p resistance of a 0-1mA ammeter obtained by connecting a shunt across the  $50 \Omega$  ammeter will be -----

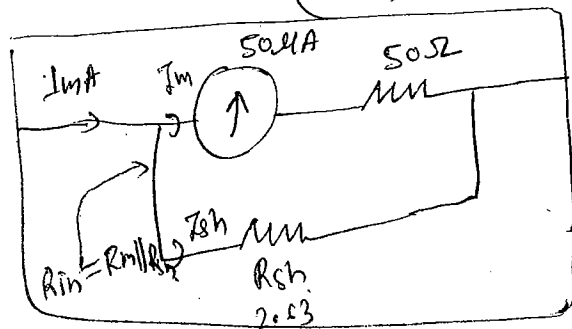
- (a)  $50 \Omega$  (b)  $2.63 \Omega$  (c)  $5 \Omega$  (d)  $2.5 \Omega$

Soln  $R_{in} = 50 \Omega$ ,  $I = 50 \mu\text{A}$ ,  $R_{sh} = ? \rightarrow 1 \text{ mA}$   
 $R_{sh} \approx 0$ ,  $m = \frac{1 \text{ mA}}{50 \Omega} = 20$

$R_{sh} = \frac{50}{(20-1)} = \frac{50}{19} \Omega = 2.63 \Omega$



DC Ammeter (0-1mA)

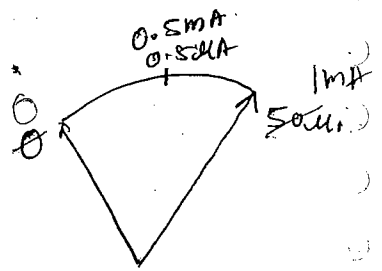


$$R_{in} = R_m \parallel R_{sh} = 50 \Omega \parallel 2.63 \Omega$$

54

$$R_{in} = 2.5 \Omega$$

Note:-  $R_{sh} < 1 \Omega$

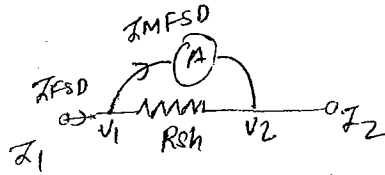

Ques:- A (0-200)  $\mu A$  DC ammeter is to be used in 50 volt dc range. The internal resistance of the ammeter is  $100 \Omega$ . Then the value of  $R_{se}$  is ---

Sol<sup>n</sup>:-

$$200 \mu A = \frac{V}{R_{se} + R_i + 100}$$

Given  $I_{MFSD} = 200 \mu A$

$R_m = 100 \Omega$

$V_{FSD} = 50 V$

$$200 \times 10^{-6} = \frac{50}{100 + R_{se}}$$

$$100 + R_{se} = \frac{50}{200 \times 10^{-6}}$$

$$\Rightarrow R_{se} = 0.25 \times 10^6 - 100 = 249.9 \text{ k}\Omega$$

$$R_{se} = R_v - R_m$$

$$= \frac{50 V}{250 \mu A} - 100 \Omega$$

$$= 250 \text{ k}\Omega - 100 \Omega$$

$$= 249.9 \text{ k}\Omega$$

Ques:- The sensitivity of a 200  $\mu A$  meter movement when it is used as a dc voltmeter is given by ---

(a)  $500 \Omega/mV$

(b)  $5 \Omega/V$

(c)  $0.5 \Omega/mV$

(d)  $5 \Omega/mV$

$$\text{Sol<sup>n</sup>:- } \frac{1}{I_{FSD}} = \frac{1}{200 \mu A} = 0.5 \times 10^4 \frac{A}{V}$$

$$= \frac{5 \text{ k}\Omega}{V} = \frac{5 \Omega}{mV}$$


Ques:- (0-50) V dc voltmeter having sensitivity of  $5 \text{ k}\Omega/V$  is constructed employing a dc ammeter if  $R_{in}$  of ammeter is  $100 \Omega$ . Then the value of  $R_{se}$  = ---

$$S = \frac{R}{V}$$

$$V_{FSD} = 50 V$$

$$S_{dc} = 5 \text{ k}\Omega, R_m = 100 \Omega$$
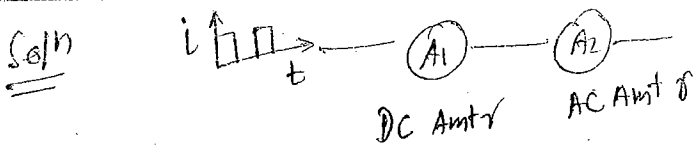
$$\therefore R_{se} = R_v - R_m = S_{dc} \times V_{FSD} - R_m$$



→ DC ammeter reading =  $I_{dc} = \frac{1}{2} \int_0^T 100 \text{ mA } dt = \frac{100 \text{ mA}}{2}$   
 $= 50 \text{ mA}$  (moving coil ammeter)

Note:- When square wave is given may be symmetrical or unsymmetrical

$I_{dc} = I_m \alpha$   
 where  $\alpha$  is duty cycle =  $\frac{t_{on}}{t_{on} + t_{off}}$

$\therefore I_{dc} = 100 \text{ mA} \times \frac{1}{1+1} = \frac{100}{2} = 50 \text{ mA}$

→ AC ammeter reading =  $I_{rms}$   
 $= \sqrt{\frac{1}{2} \int_0^T (100 \text{ mA})^2 dt}$   
 $= \frac{100}{\sqrt{2}} = 70.7 \text{ mA}$



Note -  $I_{rms} = I_m \sqrt{\alpha}$   
 $= 100 \times \sqrt{\frac{1}{1+1}} = \frac{100}{\sqrt{2}} = 70.7 \text{ mA}$

Ques:- An ammeter with internal resistance of  $50 \Omega$  give full scale deflection for  $50 \text{ mA}$  current. The i/p resistance of a  $0-1 \text{ A}$  ammeter obtained by connecting a shunt across the  $50 \Omega$  ammeter will be -----

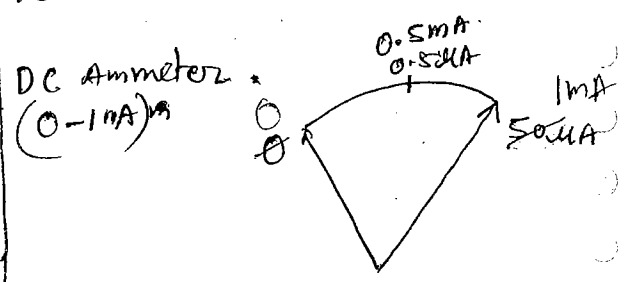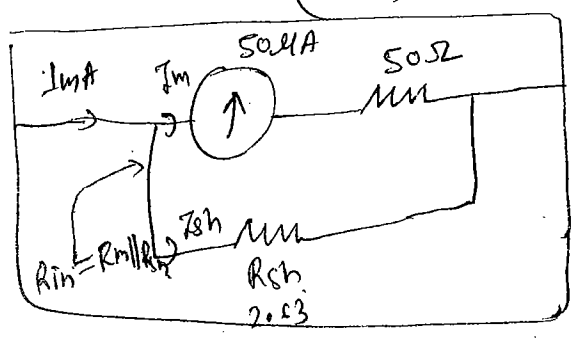- (a)  $50 \Omega$  (b)  $2.63 \Omega$  (c)  $5 \Omega$  (d)  $2.5 \Omega$

Soln  $R_{in} = 50 \Omega$ ,  $I = 50 \text{ mA}$ ,  $R_{sh} = ? \rightarrow 1 \text{ A}$   
 $R_{sh} \approx 0$   $M = \frac{1 \text{ A}}{50 \Omega} = 20$

$R_{sh} = \frac{50}{(20-1)} = \frac{50}{19} \Omega = 2.63 \Omega$







$$R_{in} = 5 \parallel 0.55 \Omega$$

$$= 0.5 \Omega$$

0-10 mA, 0.5  $\Omega$  DC ammeter

Ques - A moving coil ammeter has fixed shunt a 0.02  $\Omega$  with a coil resistance of  $R = 1 \text{ k}\Omega$  & needs potential difference of 0.5 V across it for full scale deflection (1) calculate the current it correspond to (2) Find the value of shunt when total current is 2 Amp.

Soln -

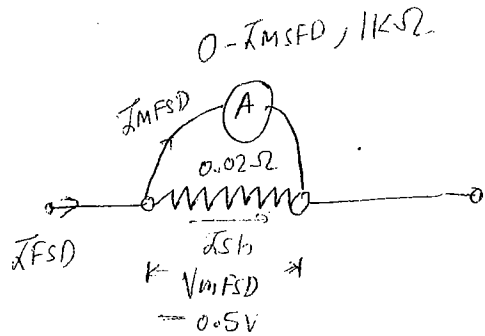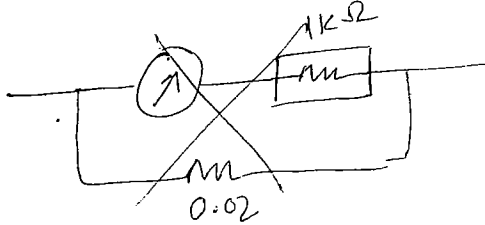

$$(1) I_{mFSD} = \frac{0.5 \text{ V}}{1 \text{ k}\Omega} = 0.5 \text{ mA}$$

$$I_{sh} = \frac{0.5 \text{ V}}{0.02 \Omega} = 25 \text{ A}$$

$$\text{We know } R_{sh} = \frac{R_m}{m-1}, \quad m = \frac{R_m}{R_{sh}} + 1$$

$$= \frac{1 \text{ k}\Omega}{0.02 \Omega} + 1 = 50 \text{ k} \quad I_{FSD} = 0.5$$

$$I_{FSD} = m I_m = 50 \text{ k} \times I_{mFSD}$$

$$I_{FSD} = 0.5 \text{ mA} + 25 \text{ A}$$

$$I_{mFSD} = 0.5 \text{ mA}$$



$$I_{FSD} = 10 \text{ A}$$

$$R_{sh} = \frac{1 \text{ k}\Omega}{\frac{10 \text{ A}}{0.5 \text{ mA}} - 1} = 0.05 \Omega$$

Date  
14/10/21/2

Ques - A voltmeter with internal resistance of  $4750\Omega$  is used to measure the voltage across a resistance of  $600\Omega$  connected in series with a DC source of internal resistance of  $400\Omega$ . What is the error?

Soln

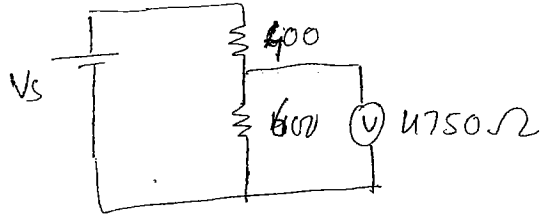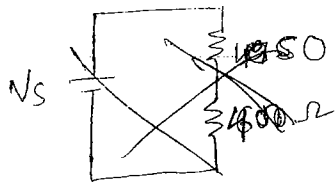

$V_{true} \Rightarrow$  voltage across  $600\Omega$

$$= V_s \times \frac{600}{600+400}$$

$$= 0.6V_s$$

$$R_{eff} = 600 \parallel 4750$$

$$= 532.7\Omega$$

$V_{meas} = V'$  across  $532.7\Omega$

$$= V_s \times \frac{532.7}{400+532.7}$$


$$= 0.57V_s$$

$$\text{Loading error} = \frac{0.57V_s - 0.6V_s}{0.6V_s} \times 100\%$$

$$= -4.8\%$$

$$\approx -5\%$$

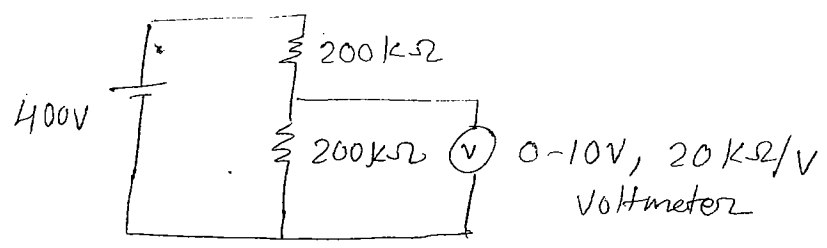Ques ⇒ In a ckt shown in below fig voltage measured by a voltmeter with a sensitivity of  $20,000 \Omega/\text{volt}$  & using the  $10\text{V}$  range find the % error in measurement.



Soln:- It is given that  $V_{fd} = 10\text{V}$  ,  $S_{dc} = 20\text{k}\Omega/\text{V}$

\*  $V_{true} = V_{200\Omega}$   
 $= 400\text{V} \times \frac{200\text{k}\Omega}{400\text{k}\Omega} = 200\text{V}$


\*  $R_V = \frac{20\text{k}\Omega}{10\text{V}} \times 10\text{V} = 200\Omega$

\*  $R_{eff} = R_L \parallel R_V = 200\text{k}\Omega \parallel 200\text{k}\Omega$   
 $R_{eff} = 100\text{k}\Omega$

$V_{meas} = V_{100\text{k}\Omega} = 400\text{V} \times \frac{100\text{k}\Omega}{300\text{k}\Omega}$   
 $= 133.33\text{V}$

% error =  $\frac{133.33\text{V} - 200\text{V}}{200\text{V}} \times 100\%$   
 $= -33.33\%$

Ques:- Explain briefly about sensitivity & loading effect of ammeter the voltage across  $50\text{k}\Omega$  resistor in ckt shown in below fig. Measured with 2 voltmeter separately. Voltmeter ① have sensitivity of  $1000 \Omega/\text{V}$  & voltmeter ② has a sensitivity of  $2000 \Omega/\text{V}$ . Both the meters are used on there  $50\text{V}$  range calculate (1) Reading of each meter (2) The error in each reading expressed as % of the true value

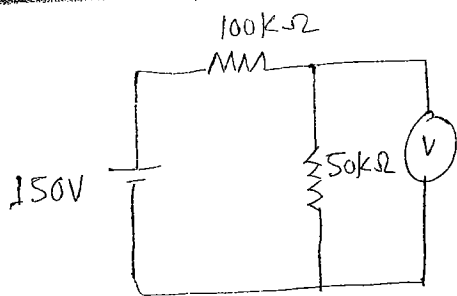

$$S_{dc} = \frac{R_V}{V_{FSD}}$$

$$= \frac{V_{FSD}}{I_{FSD} V_{FSD}}$$

$$S_{dc} = \frac{1}{I_{FSD}}$$

(i) \*  $V_{true} = V_{50k\Omega}$

$$= 150V \times \frac{50k\Omega}{150k\Omega} = 50V$$

\* Voltmeter (1)

$$\rightarrow R_V = 1k\Omega/V \times 50V = 50k\Omega$$

$$R_{eff} = 50k\Omega \parallel 50k\Omega = 25k\Omega$$

$$V_{meas} = 150 \times \frac{25k\Omega}{125k\Omega} = 30V$$

\* Voltmeter (2)

$$R_V = 2k\Omega/V \times 50V = 100k\Omega$$

$$R_{eff} = 50\Omega \parallel 100k\Omega = 33.3k\Omega$$

$$V_{meas} = 150 \times \frac{33.3k\Omega}{133.3k\Omega} = 37.5V$$

reading of  $V_1$  is = 30V

& reading of  $V_2$  is = 37.5V

(ii) % error of Voltmeter (1) =  $\frac{30V - 50V}{50V} \times 100\%$


$$= -40\%$$

% Error in reading of  $V_2$  =  $\frac{37.5 - 50V}{50V} \times 100\%$

$$= -25\%$$

Ques - A Galvanometer with internal resistance of  $100\Omega$  & full scale current setting of  $1mA$  is used to realize a dc voltmeter with a full scale range of  $1V$ . The full scale range of this meter can be extended to  $10V$  by connecting an external resistance of value - - -


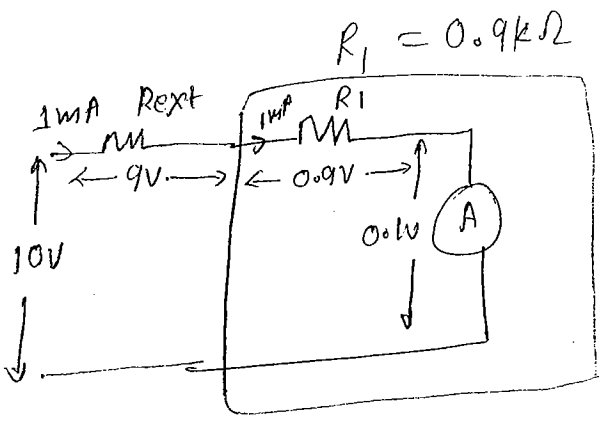
Sol  $\otimes$   $R_1 = \frac{1V - 0.1V}{1mA} = \frac{0.9V}{1mA} = 900\Omega$



$R_{ext} = \frac{10V - 1V}{1mA} = 9k\Omega$

Ques - An analog voltmeter used as external multiplier settings with a multiplier setting of  $20k\Omega$  it read  $440V$  & with  $80k\Omega$  it reads  $352V$ . For multiplier setting  $10k\Omega$  voltmeter read - - -

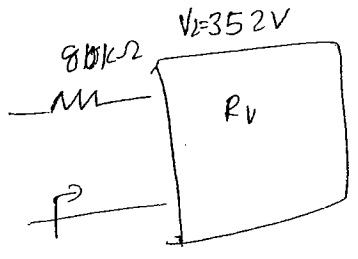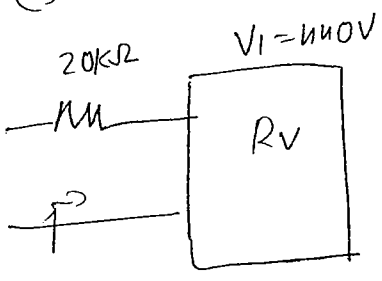- (a) 371      (b) 383      (c) 394      (d) 406



reading of Voltmeter  $\propto \frac{1}{R}$

$$\frac{V_1}{V_2} = \frac{R_2}{R_1}$$

$$\frac{440}{352} = \frac{80k\Omega + R_V}{20k\Omega + R_V}$$

$$8800k\Omega + 440R_V = 28160 + 352R_V$$

$$R_V = 220k\Omega$$


$$\frac{V_1}{V_3} = \frac{R_3}{R_1}$$

$$\frac{440}{V_3} = \frac{40k\Omega + 220k\Omega}{20k\Omega + 220k\Omega}$$

$$\boxed{V_3 = 406 \text{ V}}$$

Ques. Design a multirange ammeter using a 1mA ammeter with internal resistance of  $100\Omega$  required voltage ranges are 0-1V & 0-10V find the value of multiplier resistor for below given voltmeter design (1) Multirange voltmeter with switched multiplier resistor (2) Multirange voltmeter with series connected multiplier resistor i.e. using potential divider arrangement

Soln.

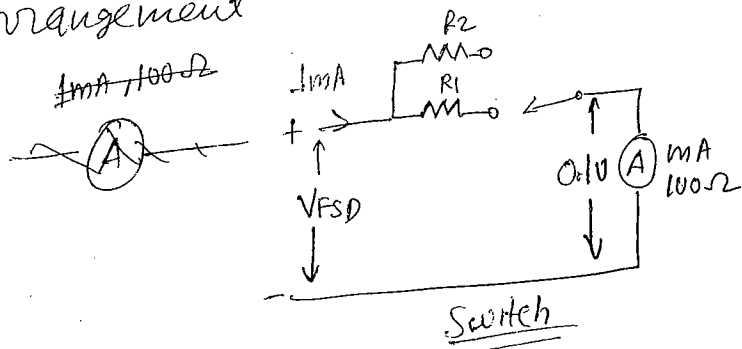

1V range

$$R_1 = \frac{1\text{V} - 0.1\text{V}}{1\text{mA}}$$


$$= 0.9\text{k}\Omega$$

10V range

$$R_2 = \frac{10\text{V} - 0.1\text{V}}{1\text{mA}}$$

$$= 9.9\text{k}\Omega$$

Series

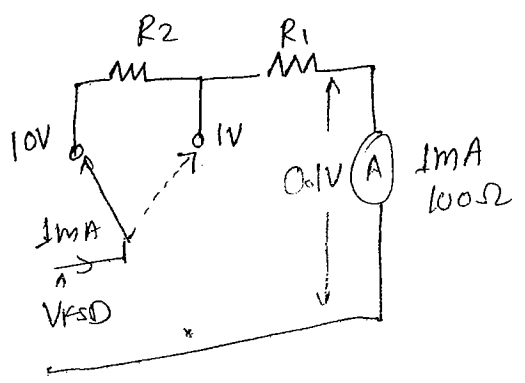

10V range

$$R_1 + R_2 = \frac{10V - 0.1V}{1mA}$$

$$0.9k\Omega + R_2 = 9.9k\Omega$$


$$R_2 = 9k\Omega$$

1V range

$$R_1 = \frac{1V - 0.1V}{1mA} = 0.9k\Omega$$

Que:- 2 mA with full scale currents of 1 mA & 10 mA are connected in parallel & they read 0.5 mA & 2.5 mA respectively. their internal resistances are the ratio of - - - -

Soln:-

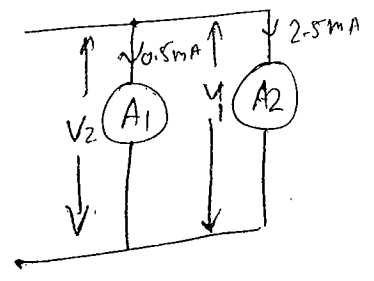

$$V_1 = V_2$$

$$I_1 \times R_1 = I_2 \times R_2$$


$$0.5 \times R_1 = 2.5 \times R_2$$

$$\frac{R_1}{R_2} = \frac{2.5}{0.5}$$

$$\frac{R_1}{R_2} = 5$$

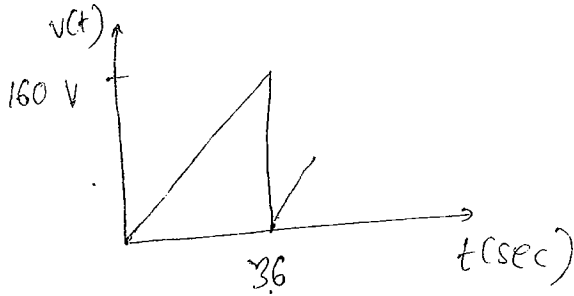- (a) 10:1
- (b) 1:10
- (c) 5:1
- (d) 1:5

Ques:- A sawtooth voltage has peak value of 160V at time periode of ~~3.6~~ 3.6 sec As shown in below fig. Calculate the error at measuring this voltage with an ~~the~~ avg reading voltmeter calibrated in terms of RMS value of sinusoidal wave.



Soln




$$\rightarrow \text{Voltage } V_{\text{RMS (true)}} = \sqrt{\frac{1}{3.6} \int_0^{3.6} \left(\frac{160t}{3.6}\right)^2 dt} \cdot V$$

$$= \sqrt{\frac{160^2}{(3.6)^3} \times \frac{(3.6)^3}{3}}$$

$$= 92.376 \text{ V} \rightarrow \text{Actual or true RMS voltage (to be preferred)}$$

\* The o/p of FWR

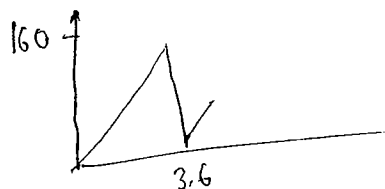

The dc voltmeter reads Avg value of o/p of FWR

$$V_{\text{dc}} = \frac{1}{3.6} \int_0^{3.6} \frac{160}{2.6} t dt$$

$$= 80 \text{ V}^*$$

They indicated rms is 1.11 Vdc since the scale is calibrated in terms of rms of sine wave

$$V_{\text{rms (ind)}} = 1.11 \times 80 = 88.8 \text{ V}$$

= measured rms value



→ error = 88.8 - 92.37V = ~~-3.57V~~  
 = -3.57V

% wave form error =  $\frac{-3.57}{92.37V} \times 100\%$   
 = -3.86%


i.e the reading of FWR voltmeter while measuring above voltage is less than true rms by 3.8% of true rms

[Note: If given as objective Que then.

We know  $FF_{saw} = 1.154$

% error =  $\left[ \frac{1.11}{FFW} - 1 \right] \times 100\%$   
 =  $\left[ \frac{1.11}{1.154} - 1 \right] \times 100\%$   
 = -3.86%

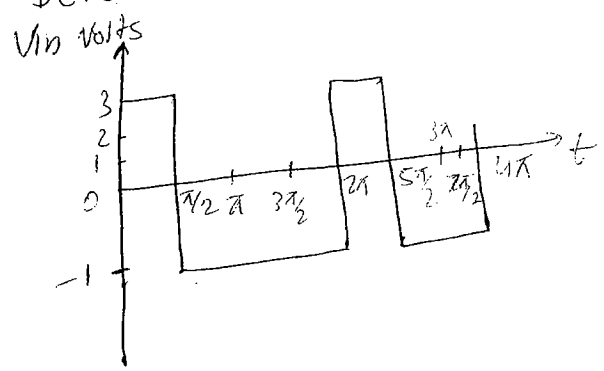
Que - The periodic voltage waveform as shown in below fig is applied to (1) True rms meter (2) An avg measuring, rms indicating meter, (3) Peak measuring rms indicating meter. Determine the reading of each instrument.





Soln

1)  $V_{rms} (True) = \sqrt{3} = 1.73$

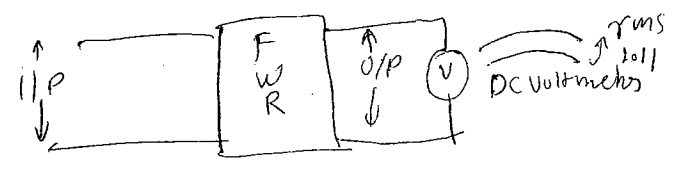2) Given meter is Avg msq - rms ind meter



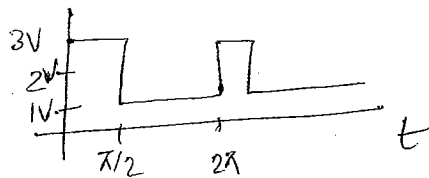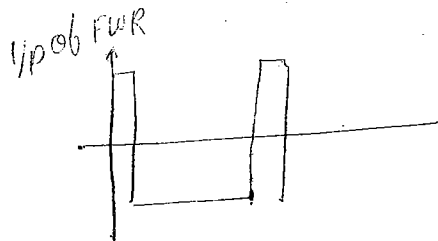

DC voltmeter measures  $V_{dc}$  of o/p of FWR



$$V_{dc} = \frac{1}{2\pi} \left[ \int_0^{\pi/2} 3V dt + \int_{\pi/2}^{2\pi} 1V dt \right]$$

$$= \frac{1}{2\pi} \left[ 3\pi/2 + (2\pi - \pi/2) \right]$$

$$= \frac{1}{2\pi} \left[ 3\pi/2 + 3\pi/2 \right] = \frac{3}{2} = \underline{1.5 V}$$

$$\therefore V_{rms} = 1.11 \times 1.5 = 1.665 V$$

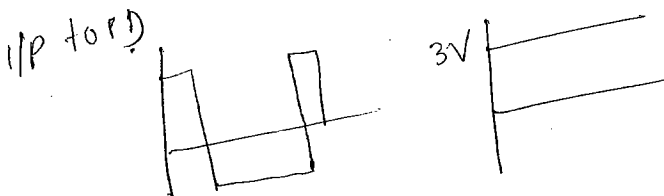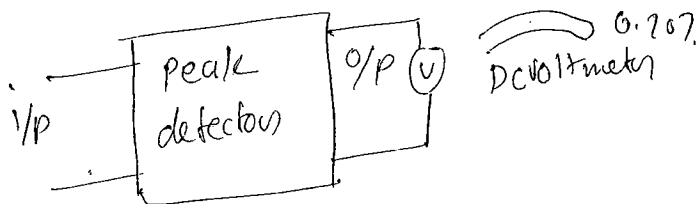(iii) Crompton meter is peak rms indicating meter



DC voltmeter measures  $V_{dc}$  of o/p of peak detector  
(i.e.  $V_p$  of  $i/p$ )

$$V_{dc} = 3V$$


$$V_{rms}(ind) = 0.707 \times 3V = 2.121V$$

from above 2 meter calculate the amount of error introduced into voltage measurement & expressed it as a % of true value.

$$\% \text{ error} = \frac{V_m - V_t}{V_t} = \frac{2.121 - 1.73}{1.73} = 22.54\%$$

Que:- An avg responding electronic voltmeter has its scale calibrated to indicate correctly. The rms value of sinusoidal voltage calculate error in its reading if the instrument is used for measuring value of asymmetrical triangular wave voltage.

Sol<sup>n</sup>:-

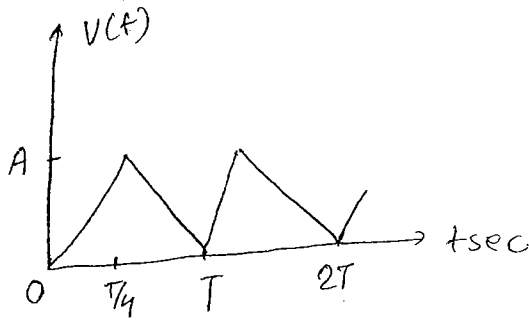

$$(0 < t < T/4)$$

$$(T/4, A)$$

$$(0, 0)$$

$$y = mx$$

$$V(t) = \frac{A}{T/4} \times t$$

$$V(t) = \frac{4A}{T} \times t$$

$$T/4 < t < T$$

$$(T/4, A)$$

$$(T, 0)$$

$$y - y_1 = m(x - x_1)$$

$$V(t) - A = \frac{-A}{T - T/4} (t - T/4)$$

$$= \frac{4}{3} \frac{A}{T} (t - T/4)$$

$$V(t) = \frac{4A}{T} t ; 0 < t < T/4$$

$$= \frac{4A}{3T} (T - t) ; T/4 < t < T$$

$$\rightarrow V_{rms}(\text{true}) = \sqrt{\frac{1}{T} \int_0^T V^2(t) dt}$$

$$= \sqrt{\frac{1}{T} \int_0^{T/4} \left(\frac{4A}{T} t\right)^2 dt + \frac{1}{T} \int_{T/4}^T \left(\frac{4A}{3T} (T - t)\right)^2 dt}$$

$$V_{rms}(\text{true}) = \sqrt{\frac{16A^2}{T^3} \int_0^{T/4} t^2 dt + \frac{(4A)^2}{9T^3} \int_{T/4}^T (T - t)^2 dt}$$

$$V_{rms}(\text{true}) = \sqrt{\frac{1}{7} \left(\frac{4A}{T}\right)^2 \times \left(\frac{t^3}{3}\right)_{0}^{T/4} + \frac{(4A)^2}{9T^3} \times \left(\frac{(T-t)^3}{-3}\right)_{T/4}^T}$$

$$V_{rms}(\text{true}) = \frac{A}{\sqrt{3}}$$


$$= \sqrt{\frac{(4A)^2}{3T^3} \times \frac{T^3}{4^3} + \frac{4A}{27T^3} (T - T/4)^3}$$

$$= \sqrt{\frac{(4A)^2}{3T^3} \times \frac{T^3}{4^3} + \frac{(4A)^2}{27T^3} \times \frac{3^3 T^3}{4^3}}$$


$$V_{rms} \text{ (true)} = \frac{A}{\sqrt{3}} = 0.577A$$

The electronic AC voltmeter consist FWR at primary stage whose o/p is fed to pmmc voltmeters

i/p to FWR

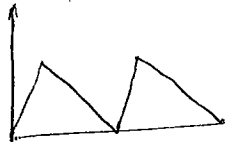

o/p of FWR = i/p to DC voltmeter

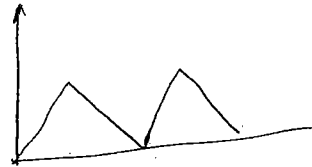

DC voltmeter measures Vdc of o/p of FWR

$$V_{dc} = \frac{1}{T} \int_0^T v(t) dt$$

$$= \frac{1}{T} \int_0^{T/4} \frac{4t}{T} dt + \frac{1}{T} \int_{T/4}^T \frac{4A}{3T} (T-t) dt$$

$$= \frac{4A}{T^2} \int_0^{T/4} t dt + \frac{4A}{3T^2} \int_{T/4}^T (T-t) dt$$

$$= \frac{4A}{T^2} \times \frac{T^2}{4^2 \times 2} + \frac{4A}{3T^2} \times \frac{(3T/4)^2}{2}$$


$$= A/2$$

$$V_{rms} \text{ (ind)} = 1.11 \times A/2 = 0.555A$$


$$e_{err} = \frac{0.555 - 0.577}{0.577} = -0.038$$

Ques - An electronic voltmeter consisting of FWR & avg square wave 100 ckt give correct rms value for a its reading for 2 volt peak to peak sinusoidal i/p will be -

Soln =>

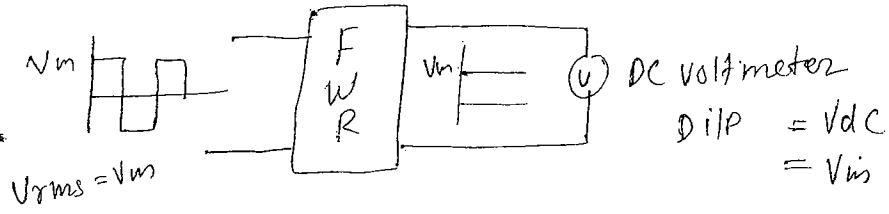

objective = 1 X response

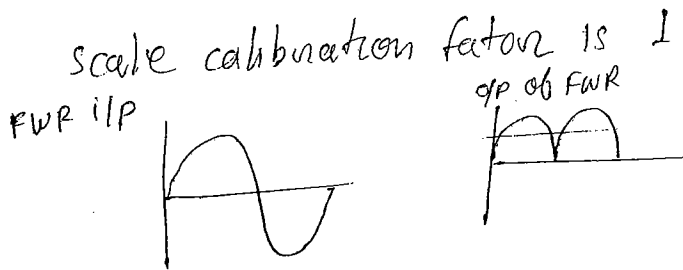

$$V_{dc} = \frac{2V_m}{\pi}$$

$$= \frac{2}{\pi} \quad (\because V_m = 1V)$$

$$V_{rms} = 1 \times V_{dc}$$

$$= 1 \times \frac{2}{\pi} = \frac{2}{\pi} V$$

Essential statement

\* A FWR voltmeter reads the true rms value of i/p waveform

reason - The FWR voltmeter (AC) has a rectifier unit first which feeds its o/p to PMMC indicating instrument

Essential is wrong, reason is true

\* A symmetrical square wave voltage is read by an avg response electronic voltmeter whose scale is calibrated in terms of rms value of a sinusoidal wave. The error in reading is


- (a) -3.9%
- (b) +3.9%
- (c) -11%
- (d) +11%

$$\text{Error} = \frac{1.11 - 1}{1} = 0.11 \text{ or } +11\%$$


Ques:- An avg response rectifier type electronic voltmeter as dc voltage of 10V applied to it what is meter reading

readings

FWR i/p

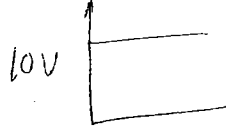

FWR o/p

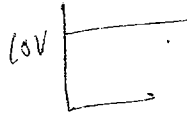

$$\begin{aligned}
 V_{dc} &= 10V \\
 &= 10 \times 1.11 \\
 &= 11.1
 \end{aligned}$$

Ques:- What is the advantage electronic voltmeter over non electronic voltmeter

(a) ~~High~~ <sup>Low power consumption</sup> i/p impedance

(b) low i/p impedance

(c) The ability to measure wide ranges of voltage & resistance

(d) Large portability

Ques:- For measurement of the voltage of the order of mV the voltmeter used is

(1) Rectifier amplifier VPVM

(2) Amplifier rectifier type VPVM

(3) Diode peak VTVM


(4) Slight wire (VTVM)

Ques. PMMC voltmeter has a sensitivity of  $20\text{ k}\Omega/\text{volt}$ . A reading of  $4.5\text{ V}$  is obtained when measuring a voltage source with the internal resistance on it  $5\text{ volts}$  scale. When the scale is change to  $10\text{ volts}$  a reading  $6\text{ volts}$  is obtained. The value of the voltage source & its internal resistance are - - -

- (a)  $10\text{ V}$ ,  $100\text{ k}\Omega$
- (b)  $9\text{ V}$ ,  $100\text{ k}\Omega$
- (c)  $10\text{ V}$ ,  $200\text{ k}\Omega$
- (d)  $9\text{ V}$ ,  $200\text{ k}\Omega$

Soln:  $S = 20\text{ k}\Omega/\text{volt}$

\* 5V scale

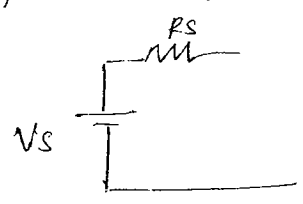

$$\rightarrow R_v = \frac{20\text{ k}\Omega}{\text{V}} \times 5\text{ V}$$

$$R_v = 100\text{ k}\Omega$$

$$\rightarrow \text{Reading} = V_s \times \frac{100\text{ k}\Omega}{R_s + 100\text{ k}\Omega}$$

$$4.5 = V_s \times \frac{100\text{ k}\Omega}{R_s + 100\text{ k}\Omega}$$

$$V_s = \frac{4.5\text{ V}}{100\text{ k}\Omega} [R_s + 100\text{ k}\Omega] \text{--- (1)}$$

\* 10V scale

$$R_v = \frac{20\text{ k}\Omega}{\text{V}} \times 10\text{ V} = 200\text{ k}\Omega$$

$$\text{rdg} = V_s \times \frac{200\text{ k}\Omega}{R_s + 200\text{ k}\Omega}$$

$$6\text{ V} = V_s \times \frac{200\text{ k}\Omega}{R_s + 200\text{ k}\Omega}$$

$$V_s = \frac{6\text{ V}}{200\text{ k}\Omega} [R_s + 200\text{ k}\Omega] \text{--- (2)}$$

equating eqn (1) with eqn (2)

$$\frac{4.5\text{ V}}{100\text{ k}\Omega} [R_s + 100\text{ k}\Omega] = \frac{6\text{ V}}{200\text{ k}\Omega} [R_s + 200\text{ k}\Omega]$$

$$\Rightarrow R_s = 100 \text{ k}\Omega$$

Putting  $R_s$  in eqn ①

$$V_s = \frac{4.5}{100 \text{ k}\Omega} [100 \text{ k}\Omega \parallel 100 \text{ k}\Omega]$$

$$V_s = 9 \text{ volt}$$

## Q meter

### Principle of operation

- \* Direct connection ckt diagram
- \* elements in the connection
- \* working
- \* Mention error, % error & correction factor

Done previously

Que - Explain with the help of ckt diagram the principle of working of a meter.

Que - Describe a method of measuring the dissipative capacitance of coil derive a necessary expression.

Soln - \* Q meter in direct connection can be used for measuring

- of  $C_d$  of coil
- \* Direct connection of ckt diagram
- \* elements in connection
- \* 2 steps of resonant state
- Mention reading of each step
- \* Derivation for  $C_d$
- \* Ex  $f \rightarrow 2f$  }  $C_d = \frac{C_1 - 4C_2}{3}$
- $C_1 \rightarrow C_2$  }

Que - A coil was tested using a Q meter and the following result was obtained

Oscillator frequency	3 MHz	6 MHz
Tuning Capacitance setting	251 PF	50 PF



Find self capacitance of coil

Soln :-  $n = \frac{6\text{MHz}}{3\text{MHz}} = 2$

$C_d = \frac{251\text{PF} - 4 \times 50\text{PF}}{3} = \underline{17\text{PF}}$

Que:- (a) Describe the method of measuring the value of Q factor of an unknown inductance in the range 1μH - 1mH with high accuracy

(b) An unknown inductance resonant at frequency of 1MHz with an external capacitance of 210 PF (tuning capacitor) & has a Q of 100. If the frequency of the source is doubled it is found that the tuning capacitor required for resonant is 45 PF. Determine the value of unknown inductance & other component associated with it in the equivalent ckt

Que:- In a Q meter measurement to determine the self capacitance of a coil the 1st resonant occurred at  $f_1$  with  $C_1 = 300\text{PF}$  the 2nd resonance occurred at  $f_2 = 2f_1$  with  $C_2 = 60\text{PF}$

The self capacitance of  $C_s = \dots$   
 $= \frac{300 - 2 \times 60}{3} = 20\text{PF}$


2003  
 Que - Assertion → The Q meter measures the Q factor of a coil when the ckt is at resonance (True)

Reason → The Q factor of coil depends only on its inductance & not on its resistance (False)

2000  
 Que - Assertion → The basic principle of operation of a Q meter is based on the property of series resonance ckt (True)

Reason → If a fixed voltage is applied to a series resonant ckt the voltage developed across it capacitor is Q time the applied voltage (True)

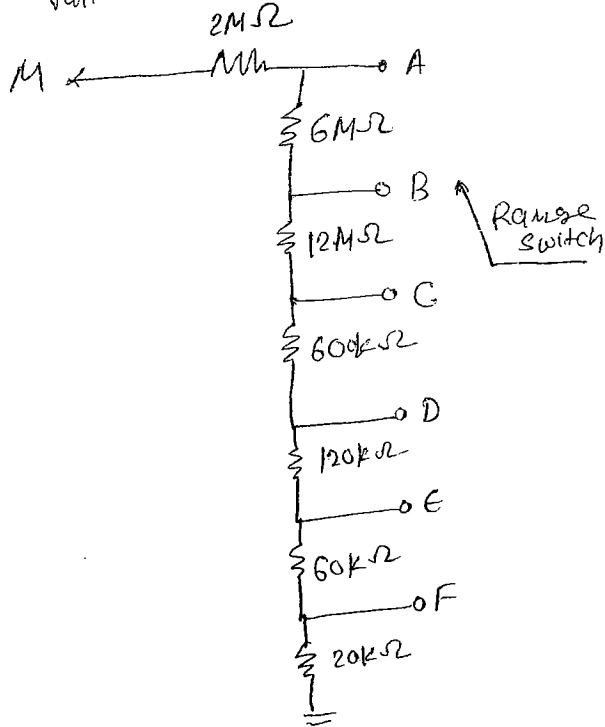Ques:- The figure shows ip attenuation of multimeter, the meter read for scale 10 with 12V at M & range slw at B what is the required voltage at M to obtain full scale deflection with the range for position at D



- (a) 1.2V
- (b) 150V
- (c) 120V
- (d) 147V

Date  
12/04/2012

Que:- An analog single channel CRO is used to measure a time varying signal  $2\sin 100\pi t$  V. Identify the image of signal displayed on screen for the following relation between signal frequency & sweep frequency



(1)  $\frac{f_{\text{signal}}}{f_{\text{sweep}}} = 1$  (2)  $f_{\text{signal}} = \frac{3}{4} f_{\text{sweep}}$

(3)  $f_{\text{signal}} = 1.5 f_{\text{sweep}}$

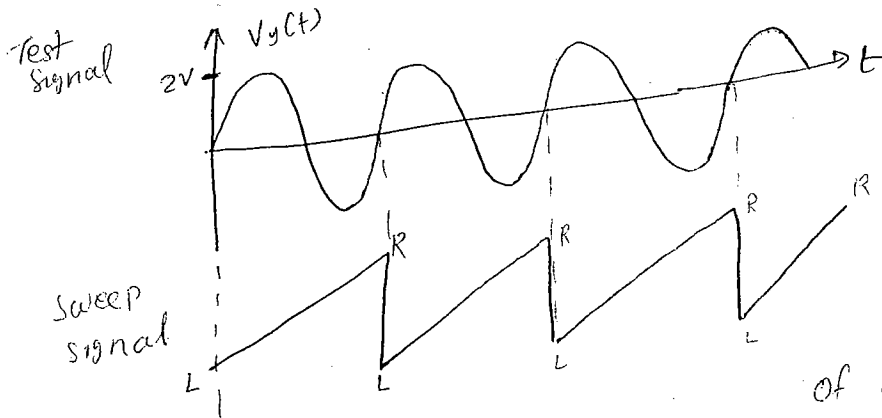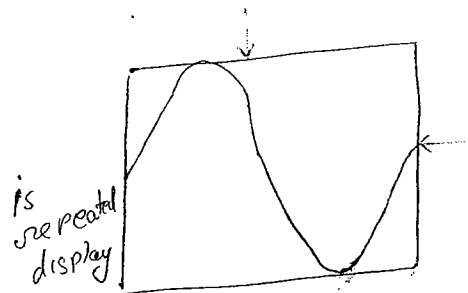(4)  $f_{\text{signal}} = 2 f_{\text{sweep}}$

Assume ~~infinite~~

Soln  $\Rightarrow$  (1)  $\frac{f_{\text{signal}}}{f_{\text{sweep}}} = 1$   
i.e.  $T_{\text{signal}} = T_{\text{sweep}}$





of signal  
 $\rightarrow$  1 cycle displayed

$\left( \because \frac{f_{\text{signal}}}{f_{\text{sweep}}} = 1 \right)$   
 $\rightarrow$  steady display  $\left( \because \text{Same portion of 1 cycle} \right)$

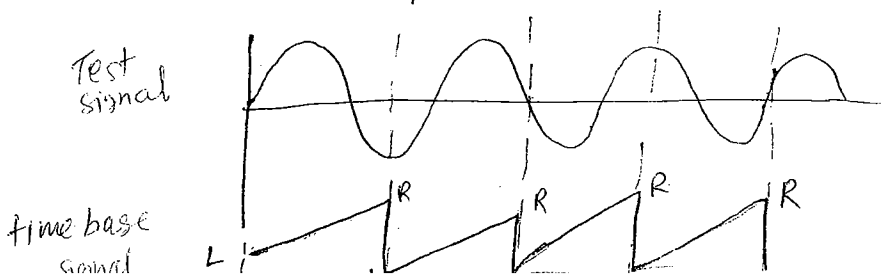(2)  $\frac{f_{\text{signal}}}{f_{\text{sweep}}} = \frac{3}{4}$


$T_{\text{signal}} = \frac{3}{4} T_{\text{sweep}}$  (75% of signal portion)



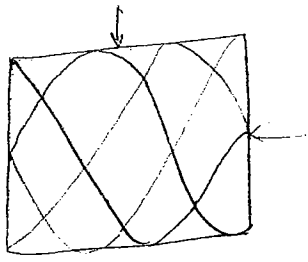



Jumble (∴ different portion of displayed)

Ex :-

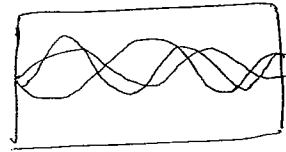


Note ⇒ To avoid such jumble i.e. to get a steady display of image the user has to either synchronised by adjusting Time/div or select proper triggering point
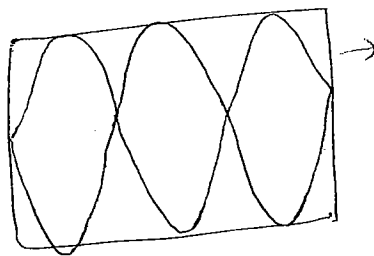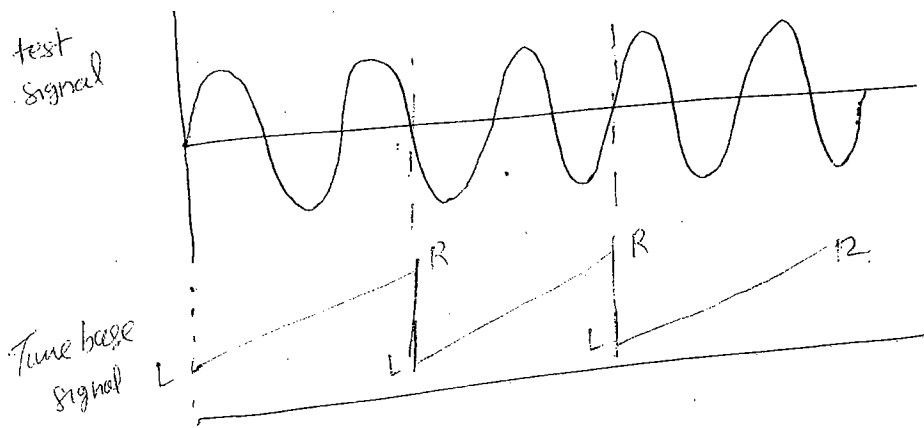
$$\textcircled{3} \quad \begin{aligned} f_{\text{signal}} &= 1.5 f_{\text{sweep}} \\ T_{\text{signal}} &= 1.5 T_{\text{sweep}} \end{aligned}$$




Jumble  
(Different 1.5 cycle of signal displayed)

Ex :-

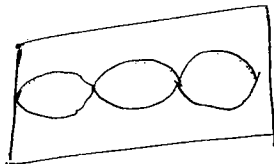

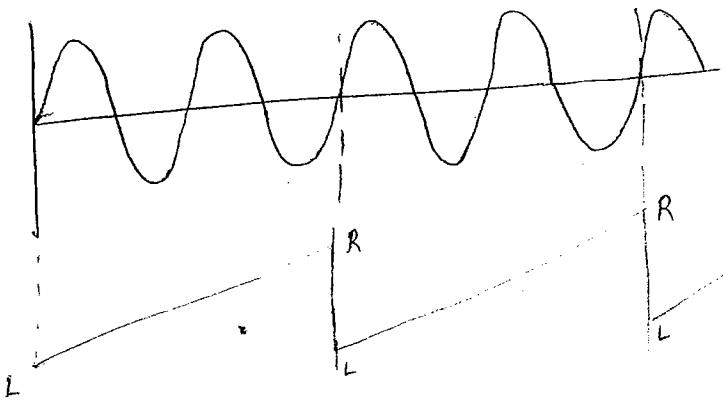
$$\textcircled{4} \quad \begin{aligned} f_{\text{signal}} &= 2 f_{\text{sweep}} \\ T_{\text{signal}} &= 2 T_{\text{sweep}} \end{aligned}$$



⇒ 2 Cycles of signal displayed
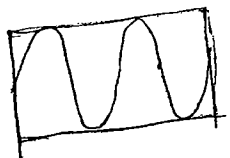
$$\left( \because \frac{f_{\text{signal}}}{f_{\text{sweep}}} = 2 \right)$$



→ steady display  
 (∵ Same 2 cycles are repeatedly displayed)

Que - A single channel analog CRO is used to measure a time varying signal  $2 \sin 100 \pi t$ . Internal trigger source is chosen. Draw the image displayed on the screen for the following case

- 1)  $f_{\text{signal}} = f_{\text{sweep}}$  & trigger point 0V, +ve
- 2)  $f_{\text{signal}} = f_{\text{sweep}}$  & trigger point 0V, -ve
- 3)  $f_{\text{signal}} = 1.5 f_{\text{sweep}}$  & trigger point 0V, +ve
- 4)  $f_{\text{signal}} = \frac{3}{4} f_{\text{sweep}}$  & trigger point 0V, +ve


sol<sup>n</sup>


$f_{\text{signal}} = f_{\text{sweep}}$  & (0V, +ve)

$T_{\text{sweep}} = T_{\text{signal}}$ ,  $t_{\text{V.L}} = 0V$ ,  $t_{\text{S}} = +ve$

Test signal as triggering signal (0V, +ve)

trigger pulse

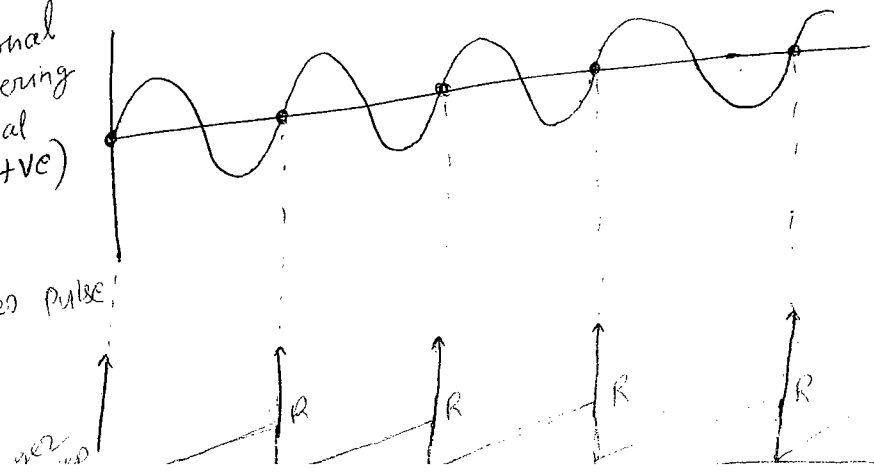


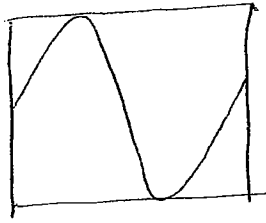


→ 1 cycle of steady image of signal  
 $\left( \because \frac{f_{\text{signal}}}{f_{\text{sweep}}} = 1 \right)$  (Proper triggering)

②  $f_{\text{signal}} = f_{\text{sweep}}$  & (0V, -ve)  
 $T_{\text{signal}} = T_{\text{sweep}}$

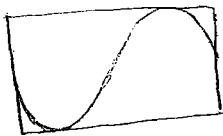→ 1 cycle of signal displayed since  $\frac{f_{\text{signal}}}{f_{\text{sweep}}} = 1$   
 & it will shown from 0V & falling side




Note ⇒ For 1:1 ratio & (2V, -ve) ⇒

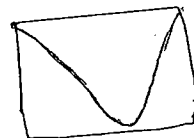


③  $f_{\text{signal}} = 1.5 f_{\text{sweep}}$  & (0V, +ve)


→ For 1:1 ratio & (+1V, +ve) ⇒

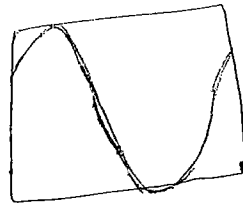

⇒ For 1:1 ratio & (+1V, -ve)


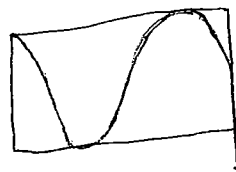


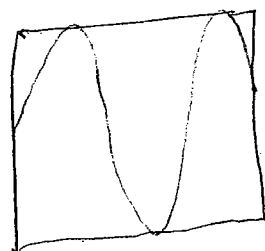③  $f_{\text{signal}} = 1.5 f_{\text{sweep}}$  & (0V, +ve)  
 $T_{\text{sweep}} = 1.5 T_{\text{signal}}$      $V.L = 0V$      $t_s = +ve$





→ 1.5 cycle of signal  
 $\left( \because \frac{f_{\text{signal}}}{f_{\text{sweep}}} = 1.5 \right)$

steady image of  
 (∵ Proper triggering)

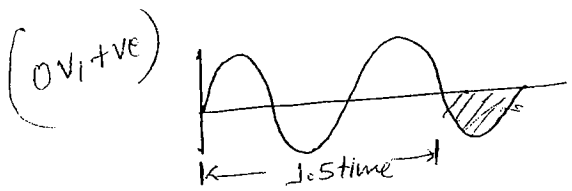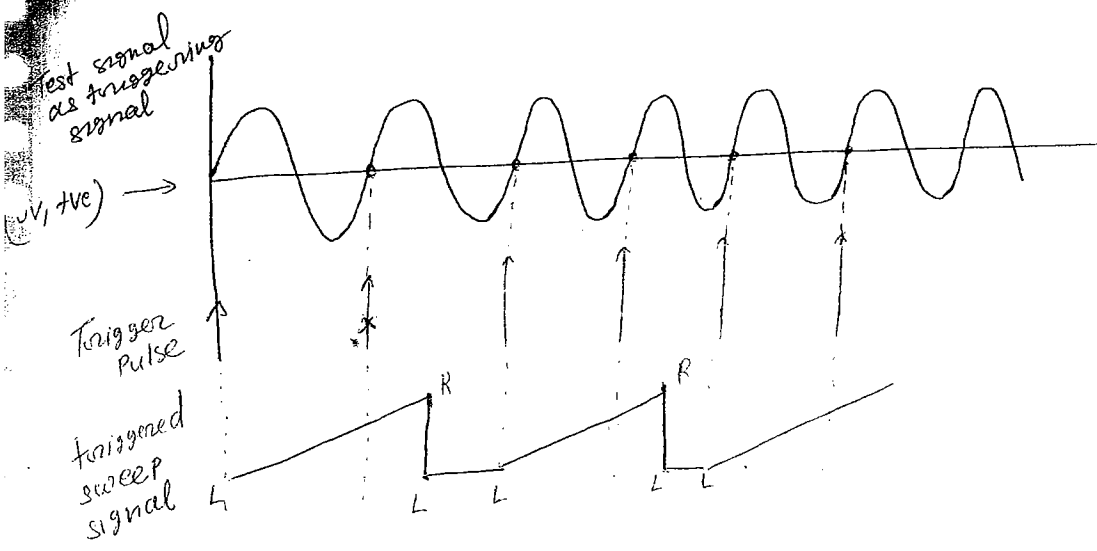


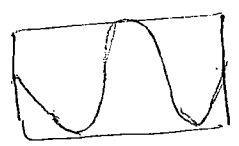
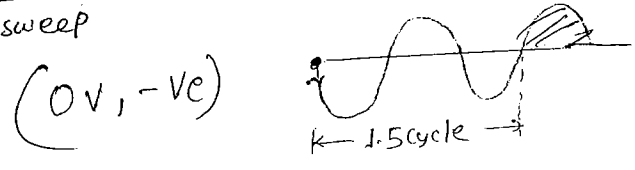
Note:-  $\frac{f_{\text{signal}}}{f_{\text{sweep}}} = 1.5$  &  $0V, -ve$



④  $f_{\text{signal}} = \frac{3}{4} f_{\text{sweep}} (0V, +ve)$

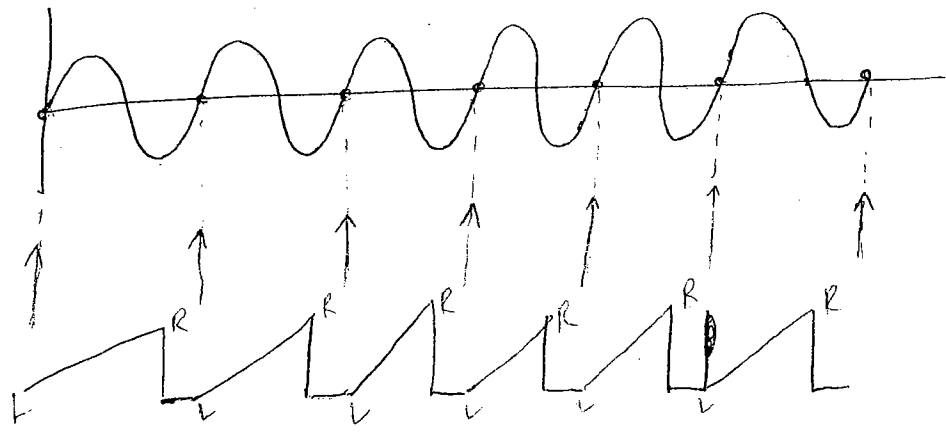$\rightarrow T_{\text{sweep}} = \frac{3}{4} T_{\text{signal}}$   
 $t.v.l = 0V, t.s. = +ve$




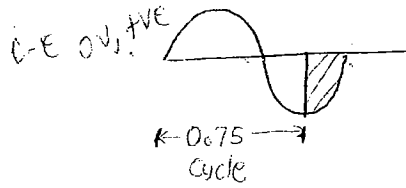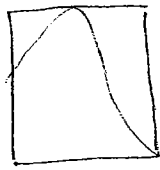


Note:  $\Rightarrow 3/4$  of (0V, -ve)  $\Rightarrow$



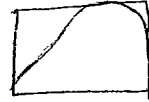$\Rightarrow 3/4$  of (-2V, +ve)  $\Rightarrow$




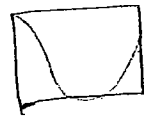$\Rightarrow 3/4$  of (+2V, -ve)  $\Rightarrow$



Not  $\Rightarrow$  Improper triggering always need to rumble whereas proper triggering produces steady image of signal on screen

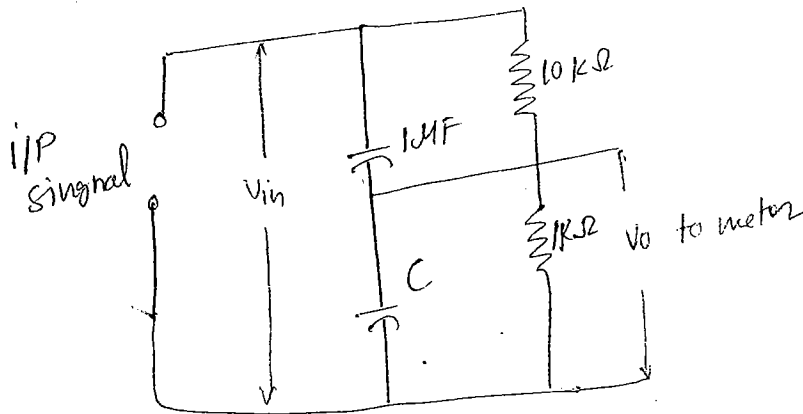Ques  $\Rightarrow$  The arrangement shown in the given figure represents a RC potentiometer for measuring ac voltage what should be the value of C so that  $V_o/V_{in}$  is independent of frequency of the i/p signal



- (a) 10  $\mu$ F
- (b) 11  $\mu$ F
- (c) 0.1  $\mu$ F
- (d) 0.09  $\mu$ F

\*  $R_1 C_1 = R_2 C_2$  to make  $\frac{V_o}{V_{in}}$  independent of frequency


$$10k\Omega \times 1\mu F = 1k\Omega \times C$$

$$\therefore C = \underline{\underline{10\mu F}}$$



Ques:- An oscilloscope has i/p impedance consisting of  $1M\Omega$  &  $67$   $2PF$  in parallel a high impedance + connected to i/p of this oscilloscope ha. of  $10M\Omega$  resistance. Thus  $1M\Omega \parallel 20PF$   $10M\Omega \parallel$  - - -

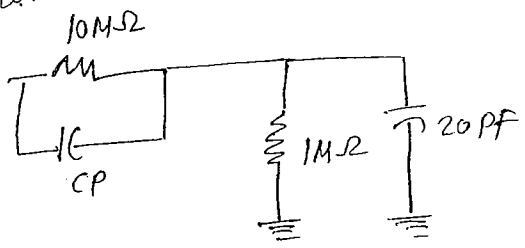- (a) Need not to be shunted
- (b) should be shunted by  $20PF$
- (c) should be shunted by  $200PF$
- (d) should be shunted by  $2PF$



$$R_i C_i = R_p C_p$$

$$1M\Omega \times 20PF = 10M\Omega \times C_p$$

$$\therefore C_p = 2PF$$

or  $\frac{V_i}{V_s} = \frac{R_i}{R_p + R_i} = \frac{1M\Omega}{10M\Omega + 1M\Omega}$

$$= \frac{1}{11}$$

Now  $\frac{V_i}{V_s} = \frac{C_p}{C_p + C_i} \Rightarrow \frac{1}{11} = \frac{C_p}{C_p + 20PF}$

$$C_p + 20PF = 11C_p \Rightarrow C_p = 2PF$$

or  $\frac{V_i}{V_s} = \frac{1}{11}$

i.e 11:1 probe

- $V_s \downarrow$  by 11 times
- $R_p = 10R_i$  &
- $C_p = \frac{C_i}{10} \dots \rightarrow C_p = \frac{20PF}{10} = 2PF$
- $\uparrow R_{eff} = 11R_i$
- $\downarrow C_{eff} = \frac{C_i}{11}$

Que  $\Rightarrow$  The oscilloscope has an i/p capacitance of 50 PF under resistance of  $2M\Omega$  & voltage divider ratio (K) of 10 what are the parameter a high Probe.

$$C_i = 50 \text{ PF} \quad R_i = 2M\Omega$$

$$K = 10 \quad \dots \quad = \frac{V_s}{V_i}$$

$$\text{i.e. } V_i = \frac{1}{10} V_s$$

$\rightarrow$  No time attenuation

$$R_p = (10-1) R_i \Rightarrow R_p = 9R_i$$

$$R_p = 9 \times 2M\Omega \Rightarrow R_p = \underline{\underline{18M\Omega}}$$

$$C_p = \frac{C_i}{(10-1)} = \frac{C_i}{9}$$

$$= \frac{50 \text{ P.F.}}{9} = 5.55 \text{ PF}$$

Que The bandwidth of CRO is from 0 to 20MHz. The fastest rise time which a square wave have in order that it is accurately reproduced by the CRO is -----


$$t_r \times B.W = 0.35$$


$$t_r = \frac{0.35}{20 \text{ MHz}} = \frac{0.035}{2} \mu\text{s}$$

$$= 17.5 \text{ } \mu\text{sec}$$

Que - A CRO with a rise time of 150 nsec measures the rise time of signal as 20 nsec. what is the actual rise time of the signal.


[Pre-requisite

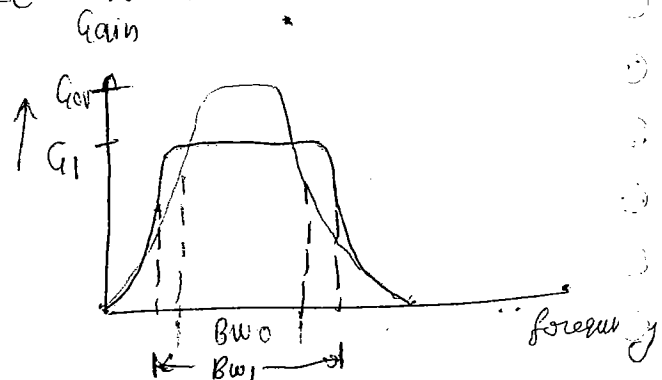

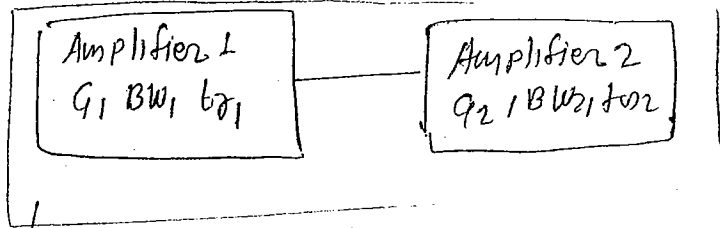

↑G × BW ↓ ~ K  
~~tσ~~ × BW = 0.35

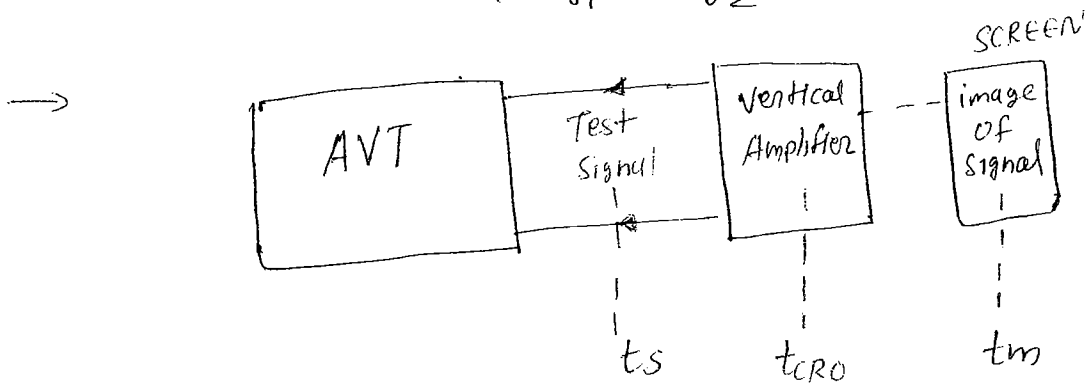↳  $G_{ov} = G_1 \times G_2$   
 $t_{\sigma 2} = \sqrt{t_{\sigma 1}^2 + t_{\sigma 2}^2}$



$t_s$  = Actual osr true rise time of signal  
 $t_{cro}$  = CRO rise time (i.e. Vertical Amp rise time)  
 $t_m$  = measured rise time is overall rise time

$$t_m = \sqrt{t_s^2 + t_{cro}^2}$$

Soln :-

$t_{cro} = 15 \text{ nsec}$

$t_m = 20 \text{ nsec}$

$$20 \text{ ns} = \sqrt{t_s^2 + (15 \text{ ns})^2}$$

$$t_s = \sqrt{(20 \text{ ns})^2 - (15 \text{ ns})^2}$$

$$= \underline{\underline{13.23 \text{ ns}}}$$

Que ⇒ A CRO has a rise time ~~20 ns~~ of 20 ns. The rise time of a signal measured by this CRO is 25 ns. Find the true rise time of signal.

Soln

$$t_m = \sqrt{t_s^2 + t_{CRO}^2}$$

$$25 = \sqrt{t_s^2 + (20)^2}$$

$$t_s = \sqrt{(25\text{ns})^2 - (20\text{ns})^2}$$

$$t_s = \underline{15\text{ ns}}$$

Que  $\Rightarrow$  A CRO is operated with the x & y settings of  $0.5 \frac{\text{msec}}{\text{cm}}$  &  $100 \frac{\text{mV}}{\text{cm}}$ . The screen of CRO is  $10\text{cm} \times 8\text{cm}$ . The cycle of frequency  $200\text{Hz}$  & RMS amplitude of  $300\text{ mV}$  is applied to the  $\therefore$  twice the screen will show - - -

- (a) 1 cycle of undistorted sine wave.
- (b) 2 cycles of undistorted sine wave.
- (c) 1 cycle of the sine wave with clipped amplitude.
- (d) 2 cycle of the sine wave with clipped amplitude.

Given here  $0.5 \frac{\text{ms}}{\text{cm}}$   $100 \frac{\text{mV}}{\text{cm}}$

$10\text{cm} \times 8\text{cm}$  screen

1 cycle or 2 cycle

$$n = \frac{f_{\text{signal}}}{f_{\text{sweep}}} = f_{\text{signal}} \times T_{\text{sweep}}$$

$$= 200\text{Hz} \times \left[ 10\text{cm} \times 0.5 \frac{\text{ms}}{\text{cm}} \right]$$

$$= 200 \times 5 \text{ msec}$$


$$= 1 \text{ cycle}$$

$\therefore$  option (b) & (d) are eliminated

$$R_{in} = R_m \parallel R_{sh} = 50 \Omega \parallel 2.63 \Omega$$

$$R_{in} = 2.5 \Omega$$

Note:-  $R_{sh} < 1 \Omega$

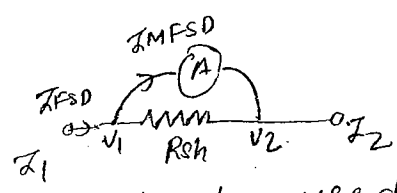

Ques:- A (0-200)  $\mu A$  DC ammeter is to be used in 50 volt dc range. the internal resistance of the ammeter is 100  $\Omega$ . Then the value of  $R_{se}$  is ---

Soln:-

$$200 \mu A = \frac{V}{R_{se} + R_i + 100}$$

Given  $I_{FSD} = 200 \mu A$   
 $R_m = 100 \Omega$   
 $V_{FSD} = 50 V$

$$200 \times 10^{-6} = \frac{50}{100 + R_{se}}$$

$$100 + R_{se} = \frac{50}{200 \times 10^{-6}}$$

$$\Rightarrow R_{se} = 0.25 \times 10^6 - 100 = 249.9 k\Omega$$

$$R_{se} = R_v - R_m$$

$$= \frac{50 V}{250 \mu A} - 100 \Omega$$

$$= 250 k\Omega - 100 \Omega$$

$$= 249.9 k\Omega$$

Ques:- The sensitivity of a 200  $\mu A$  meter movement when it is used as a dc voltmeter is given by ---

- (a) 500  $\Omega/mV$       (b) 5  $\Omega/V$       (c) 0.5  $\Omega/mV$       (d) 5  $\Omega/mV$

Soln:-

$$\frac{1}{I_{FSD}} = \frac{1}{200 \mu A} = 0.5 \times 10^4 \frac{V}{A}$$

$$= 5 \frac{k\Omega}{V} = \frac{5 \Omega}{mV}$$

Ques:- (0-50)V dc voltmeter having sensitivity of 5  $k\Omega/V$  is constructed employing a dc ammeter if  $R_{in}$  of ammeter is 100  $\Omega$  then the value of  $R_{se}$  = ---

$$S = \frac{R}{V}$$

$$V_{FSD} = 50 V, \quad S_{dc} = 5 k\Omega, \quad R_m = 100 \Omega$$

$$\therefore R_{se} = R_v - R_m = S_{dc} \times V_{FSD} - R_m$$

$$= 250\text{K}\Omega - 50\Omega$$


$$= 249.9\text{K}\Omega$$

Ques (ccc)

Que

A dc voltmeter with figure of merite of  $20\text{K}\Omega/\text{volt}$  is used to measured Half full scale voltage in  $10\text{V}$  dc range. then current through meter is ----
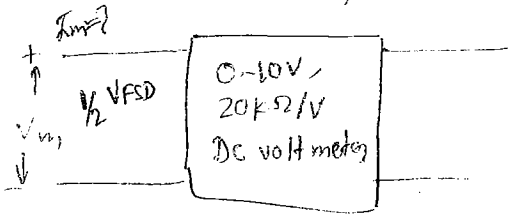
$$S_{dc} = 20\text{K}\Omega/\text{volt}, V_{FSD} = 10\text{V}$$




$$R_V = 20\frac{\text{K}\Omega}{\text{volt}} \times 10\text{V}$$

$$= 200\text{K}\Omega$$

$$V_m = \frac{1}{2} \times 10\text{V} \Rightarrow 5\text{V}$$
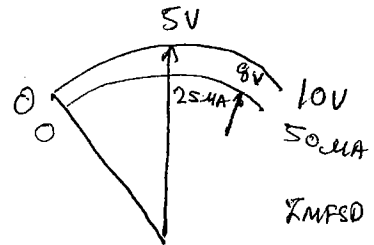
$$\therefore I_m = \frac{5\text{V}}{200\text{K}\Omega} \Rightarrow 25\mu\text{A}$$




$$I_{MFSD} = \frac{1}{200\text{K}\Omega/\text{V}}$$

$$= 50\mu\text{A}$$

Loading effect  $\Rightarrow$

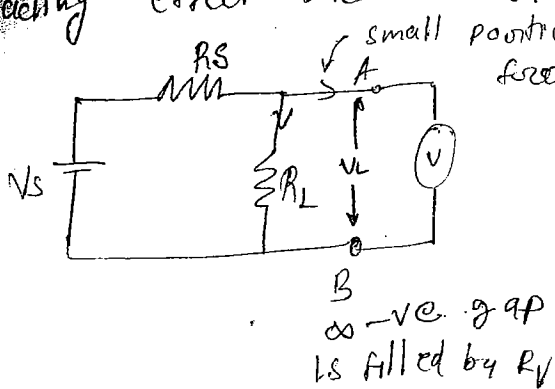loading effect Due to voltmeter resistance :-



small portion of load current is drawn by voltmeter from cut & measured  
if  $R_V \gg R_L$

\* True ckt cond<sup>n</sup> :-

$$R_L (\text{true}) = R_L \parallel \infty = R_L$$

$$V_L (\text{true}) = V_s \times \frac{R_L}{R_s + R_L}$$

= Actual voltage or true voltage

Measured value < True value

\* Measured ckt cond<sup>n</sup>.

$$R_L (\text{eff}) = R_L \parallel R_V = R_{LV}$$

$$V_L (\text{eff}) = V_s \times \frac{R_{LV}}{R_s + R_{LV}}$$

= Measured voltage or indicate voltage or observed voltage  
= reading of voltmeter

\* Introduction of a voltmeter in parallel with load resistance ( $R_L$ ) makes the voltmeter to be a part of load of the circuit under test such as voltmeter indicates value less than the true value.

\* This is known as loading effect which is due to voltmeter resistance ( $R_V$ ) & corresponding difference between measured & true voltages is called as loading error

$$\text{Loading error} = V_{\text{measured}} - V_{\text{true}}$$

$$\% \text{ Loading error} = \frac{V_{\text{measured}} - V_{\text{true}}}{V_{\text{true}}} \times 100 \%$$

\* Loading effect is very much deside effect (since voltmeter measures current drawn from CUT) whereas the amount of error in reading must be minimized.

\* To ↓ L.O.E. , a voltmeter should have High resistance

- \*  $R_v(\text{min}) = 10 R_L$  - - - - for 90% Accuracy
- $= 100 R_L$  - - - - for 99% Accuracy

$$R_v(\text{min}) \geq 10 R_L$$


Selection criteria for a voltmeter

- \* Higher the resistance is better for voltmeter
- \* A voltmeter with High resistor & high sensitivity causes Min<sup>m</sup> (or less) loading


\* The internal resistance of ideal voltmeter is  $\infty$ . but an ideal voltmeter can not be realized or constructed.

<sup>Ques</sup> \* One :- A 35V dc source is connected to series combination of  $600 \Omega$  & unknown resistance  $R_x$ . A voltmeter connected across  $600 \Omega$  read 5 Volts. If the voltmeter resistance is  $1.2 \text{ k}\Omega$ , then value of  $R_x$  is - - - -

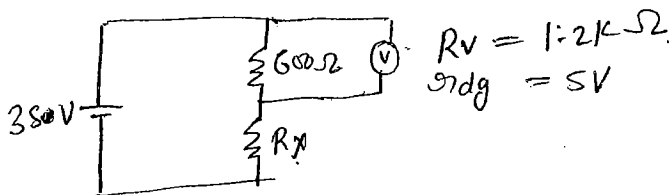- (a)  $1.2 \text{ k}\Omega$       (b)  $2.4 \text{ k}\Omega$       (c)  $3.6 \text{ k}\Omega$       (d)  $4.8 \text{ k}\Omega$


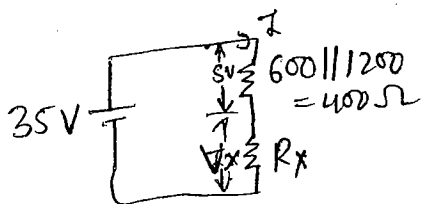
$$5 = 35 \times \frac{\left( \frac{600 \times 1.2 \times 10^3}{600 + 1.2 \times 10^3} \right)}{\left( \frac{600 \times 1.2 \times 10^3}{600 + 1.2 \times 10^3} \right) + R_x}$$



$$I = \frac{5V}{400 \Omega}$$

$$V_x = I R_x$$

$$35 - 5 = \frac{5V}{400 \Omega} \times R_x$$


$$\therefore R_x = 30V \times \frac{400 \Omega}{5}$$

$$= 2400 \Omega$$

$$= 2.4 \text{ k}\Omega$$



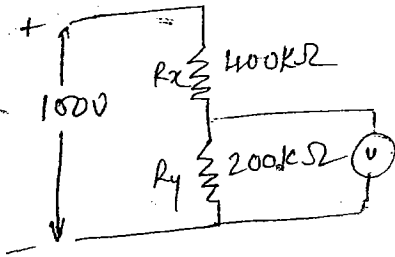Ques:- In a ckt shown in below fig a voltmeter <sup>with</sup> figure of merit of  $2 \text{ k}\Omega/\text{Volt}$  is connected across  $200 \text{ k}\Omega$  the range of voltmeter is  $0-100 \text{ V}$



(a) The reading of voltmeter is ----

(b) % error in reading is ----

$$S = \frac{2 \text{ k}\Omega}{\text{Volt}}$$

$$R_1 \parallel R_V = \frac{200 \times 2(100)}{400} \\ = 100 \Omega$$

$$V = V_s \cdot \frac{R_V \cdot R_1}{R_V + R_1} = 100 \times \frac{100}{400 + 100}$$

$$= 20 \text{ Volt}$$

$$V_L = V_s \frac{R_L}{R_s + R_L} = 100 \times \frac{200}{100 + 200} = 33.33 \text{ V}$$

$$\% \text{ Loading error} = \frac{20 - 33.33}{33.33} \times 100 \\ = -39.93 \%$$

Note:-

\* The Basic indicating device in all electronics device is nothing but PMMC



\* CC is offered high i/p resistance in transistor.

$$\text{M\&: } \theta = \frac{1}{2} I^2 \frac{dL}{d\theta}$$

$$\text{EDM: } \theta = I^2 \frac{dM}{d\theta}$$

$$\theta = k I^2$$

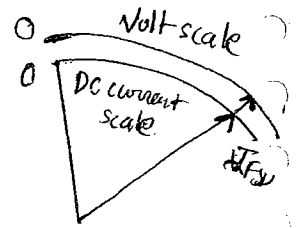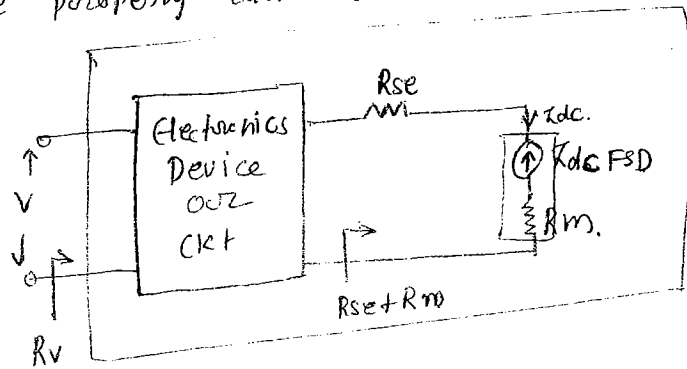Electronics voltmeter :- An electronic voltmeter consist of an electronic device, ~~or~~ ckt whose o/p is feed to a PMMC instrument & scale properly calibrated



$$E_{DC} + R_{se} + PMMC = \text{Electronic voltmeter}$$

Types of electronics device

Type of electronic voltmeter

DC Amplifier

DC amplifier Voltmeter } electron  
or } DC  
Amplifier type voltmeter } voltmeter  
( $I_{dc} = FSD \times \frac{C}{V}$ )

Rectifier

Rectifier type voltmeter } Elec  
Peak responding Voltmeter } n  
RMS detector } AC  
( $V_{0-1} \rightarrow V_m$   
 $\rightarrow 0-V_m$ )

Peak Detector

RMS detector

Note  $\rightarrow$  Indicating device in AC voltmeter is PMMC.

Amplifier type Voltmeter :-


1. DC Amplifier voltmeter :- An amplifier type voltmeter consist of an amplifying device whose o/p is feed to a PMMC.

The design objective is to achieve very high i/p resistance & very high sensitivity.  $A \rightarrow 1 \text{ mA}$

Que:- A  $0-1 \text{ mA}$ ,  $100 \Omega$  DC milliammeter is used to design the following Voltmeter

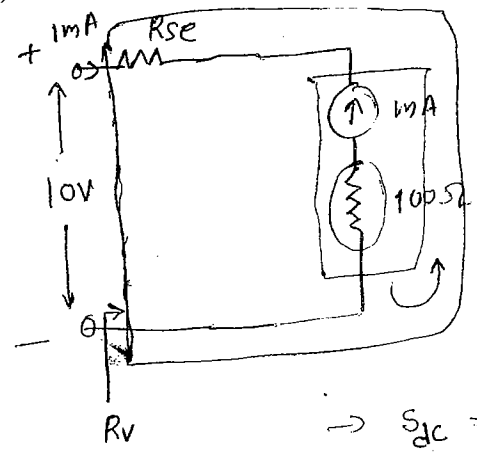- (1)  $0-10 \text{ Volt}$  conventional DC voltmeter
- (2)  $0-10 \text{ Volt}$  electronic DC voltmeter using a BJT with current gain of 100
- (3) Calculate required multiplier resistance, i/p resistance & sensitivity both the voltmeter

Soln:- (1) 0-10V electromechanical DC voltmeter




0-1mA  
100Ω  
 $\Rightarrow R_v = \frac{10V}{1mA} \Rightarrow 10K\Omega$   
 $\Rightarrow R_{se} = 10K\Omega - 100\Omega$   
 $R_{se} = 9.9K\Omega$


$\rightarrow S_{dc} = \frac{10K\Omega}{10V} = \frac{1K\Omega}{V}$   
 $s_{dc} = \frac{0.52}{1mA} = \frac{1K\Omega}{V}$

(2) 0-10V electronics DC voltmeter

\* CE, CB, CC (emitter follower)

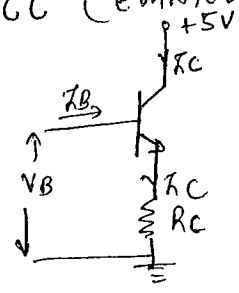

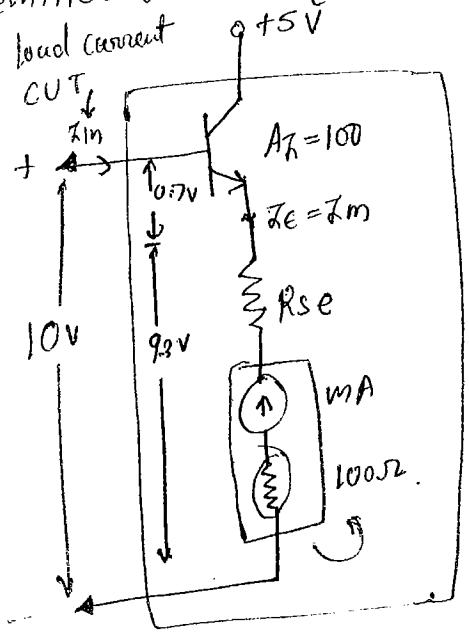\* Common collector is known as emitter follower (CC type)  
 Position of load current drawn by CUT



Transistor Voltmeter or emitter follower voltmeter

$\rightarrow A_v = \frac{R_C}{R_B}$   
 $= \frac{I_m}{I_{in}}$

For FSD

$A_v = \frac{I_{mFSD}}{I_{inmax}}$   
 $100 = \frac{1mA}{I_{inmax}}$

$\therefore I_{inmax} = 10\mu A$   
 $\rightarrow R_v = \frac{10V}{10\mu A} = 1M\Omega$

$V_C = R_C \times I_C$   
 $V_B - V_{BE} = (R_{se} + R_m) I_{mFSD}$

$10V - 0.7V = (R_{se} + 100\Omega) 1mA$   
 $\frac{9.3V}{1mA} = R_{se} + 100\Omega$   
 $\therefore R_{se} = \frac{9.3V}{1mA} - 100\Omega$   
 $= 9.2K\Omega$

$$S_{dc} = \frac{10 \text{ M}\Omega}{10 \text{ V}} = 0.1 \frac{\text{M}\Omega}{\text{V}} = 100 \frac{\text{k}\Omega}{\text{V}}$$

$$S_{dc} = \frac{1}{10 \mu\text{A}} = 0.1 \frac{\text{M}\Omega}{\text{V}} = 100 \frac{\text{k}\Omega}{\text{V}}$$

- \* sensitivity  $\uparrow$  sense small current
- \* It required high i/p resistance.

Conclusion:- A regular conventional DC voltmeter is not suitable for voltage measurement in ~~low~~ high resistive ckt (100k $\Omega$ , 200k $\Omega$ ) since the cause high loading as such a electronics dc voltmeter ~~is~~ design.

### Advantages of electronics amplifier voltmeter :-

1. Electronic <sup>Amplifier</sup> voltmeter offer very high input resistance in the range of M $\Omega$ .
2. ~~Con~~ Electronic amplifier voltmeter offer very high sensitivity & a order of M $\Omega$ /V or  $\Omega$ /mV.
3. Amplifier voltmeter causes min<sup>m</sup> loading even if used across high resistive loads.
4. Electronics amplifier voltmeter can sense ~~of~~ or detect a 'very low level signal. (current in the order of  $\mu\text{A}$  & voltage in the order of mV)
5. Amplifier voltmeter offer faster response, better accuracy & wide frequency range. because of existence of solid state electronics device.
6. This voltmeter can be called as electronic dc voltmeter amplifier type voltmeter or DC amplified voltmeter.

E.g. - (1) Emitter follower voltmeter or transistor voltmeter

(2) OPAMP voltmeter

(3) FET input voltmeter.



All the above electronic dc voltmeter do require external supp for their operation & are sensitive to temperature.

Electronics AC voltmeters:— (Conventional electromechanical & AC meter (moving iron type & electro-dynamometer type) are not true R.M.S meter since they don't follow perfect square law. As such electronics AC voltmeter are designed to achieve the objective of true R.M.S measurement

\* There are three type namely rectifier type, peak type & thermocouple type.

\* Full wave bridge rectifier type AC voltmeter :-

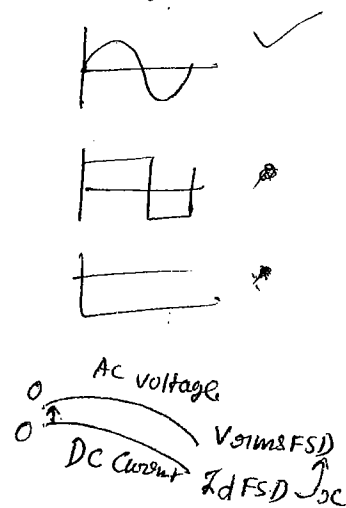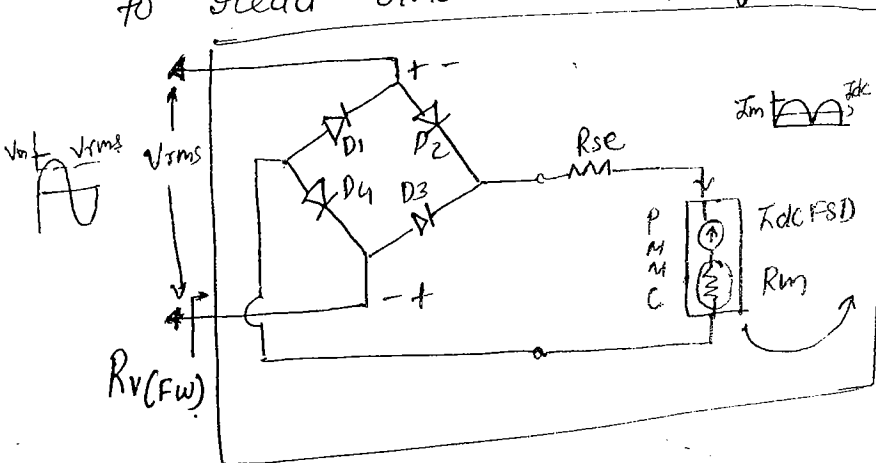A rectifier voltmeter consist a full wave bridge rectifier whose o/p is fed to a PMMC. whose scale is calibrated to read rms voltage of i/p (sinusoidal only)



\* objective of design :  $V_{rms} = \frac{1}{\sqrt{2}} V_m$   
(∵ Sinusoidal i/p is considered)

\* Response of  $I_{dc} = \frac{2 I_m}{\pi}$

\* Relation between  $I_{dc}$  &  $I_{rms}$  for scale calibration:

$$V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{(2R_d + R_{se} + R_m) I_m}{\sqrt{2}}$$

$$V_{rms} = \frac{1}{\sqrt{2}} (2R_d + R_{se} + R_m) \frac{\pi I_{dc}}{2}$$

$$V_{rms} = \frac{\pi}{2\sqrt{2}} (2R_d + R_{se} + R_m) I_{dc}$$

$$V_{rms} = 1.11 (2R_d + R_{se} + R_m) I_{dc} \quad \text{or} \quad V_{rms} = 1.11 V_{dc}$$

\* frequency range  
15 ~~Hz~~ Audio frequency

\* A rectifier voltmeter is an avg measuring, r.m.s indicating meter with a linear rms scale. that works for both ac & dc i/p

\* This rms scale is linear since it is derived from a linear dc scale considering sinusoidal wave as i/p. as such rectifier voltmeter is also called as derived r.m.s meter

\* Rectifier voltmeter give no error for sinusoidal i/p. but introduces error into reading for non sinusoidal i/p (which are known as waveform error)

1. Full wave rectifier voltmeter resistance ( $R_{V(FW)}$ )

$$* R_{V(FW)} = 2R_d + R_{se} + R_m$$

$$* R_{V(FW)} = \frac{1}{1.11} \frac{V_{rms\ FSD}}{I_{dc\ FSD}}$$

$$R_{V(FW)} = 0.9 \frac{V_{rms\ FSD}}{I_{dc\ FSD}} \rightarrow \text{required AC voltage range}$$

Available DC current range

Thus required

$$* R_{V(FW)} = \text{AC sensitivity} \times \text{AC volt range}$$

2. Required  $R_{se}$ :

$$* R_{se} = R_{V(FW)} - 2R_d - R_m$$

3. D.C. sensitivity:

$$* S_{dc} = \frac{1}{I_{dc\ FSD}}$$

4. AC sensitivity

$$* S_{ac(FW)} = \frac{R_{V(FW)}}{V_{rms\ FSD}}$$

$$= \frac{0.9 \frac{V_{rms} FSD}{I_{dc} FSD}}{V_{rms} FSD} = 0.9 \times \frac{1}{I_{dc} FSD}$$

$$\Rightarrow S_{AC} (FW) = 0.9 S_{dc}$$

5. Reading of FWR voltmeter :

For any i/p

$$V_{rms} (ind) = 1.11 V_{dc}$$

where  $V_{dc}$  = avg value of o/p of FWR

\* Error will be present in the reading for non sinusoidal i/p


$$\% \text{ error of non sinusoidal i/p} = \frac{V_{rms} (ind) - V_{rms} (true)}{V_{rms} (true)}$$

→ Amount of waveform error

where  $V_{rms} (ind) = \text{reading} = 1.11 V_{dc}$

&  $V_{rms} (true) = \text{Actual rms value of given non sinusoidal i/p}$

2. Half wave rectifier voltmeter :-

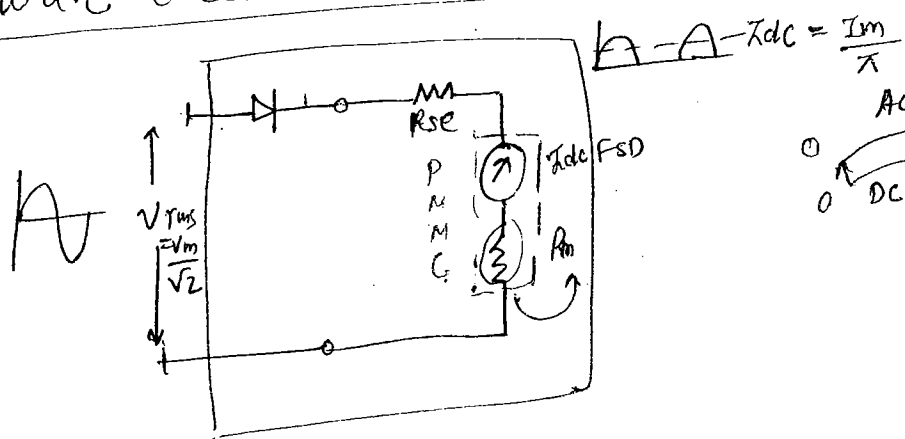

$$\begin{aligned} V_{rms} &= \frac{I_{dc}}{\sqrt{2}} (R_d + R_{se} + R_m) I_{dc} \\ &= 2.22 (R_d + R_{se} + R_m) I_{dc} \\ &= 2.22 I_{dc} \end{aligned}$$

$$* R_v(FW) = R_d + R_{se} + R_m$$

$$R_v(HW) = 0.45 \frac{V_{rms} FSD}{I_{dc} FSD}$$

$$R_v(HW) = AC \text{ sensitivity} \times AC \text{ voltage range}$$

$$* R_{se} = R_v(HW) - R_d - R_m$$

$$* S_{dc} = \frac{1}{I_{dc} FSD}$$


$$* S_{AC} (HW) = \frac{R_v(HW)}{V_{rms} FSD}$$

$$S_{AC} (HW) = 0.45 S_{dc}$$

$$* V_{rms} (ind) = 2.22 V_{dc} \dots \text{rdg}$$

$$* \% \text{ error} = \frac{V_{rms} (ind) - V_{rms} (true)}{V_{rms} (true)} \times 100 \%$$

	<u>FWR</u>	<u>HWR</u>
1mA ↓ 10%	$0.9 \times \frac{10V}{1mA}$	$0.45 \times \frac{10V}{1mA}$
	⇒ 9kΩ	⇒ 4.5kΩ

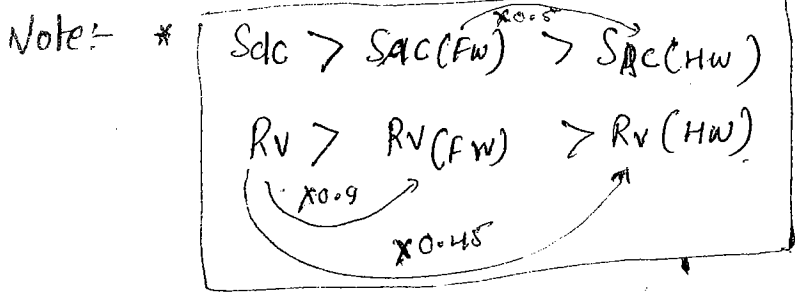


\* Conventional rectifier type AC voltmeter is full wave rectifier type <sup>voltmeter</sup> since it offer more i/p resistance & more sensitivity (2nd) than Half wave rectifier voltmeter.

\* If loading error is more in ac measurement compare to dc measurement High → Low

$$R_v(FET VR) > R_v(EFVR) > R_v > R_v(FWVR) > R_v(HWVR)$$
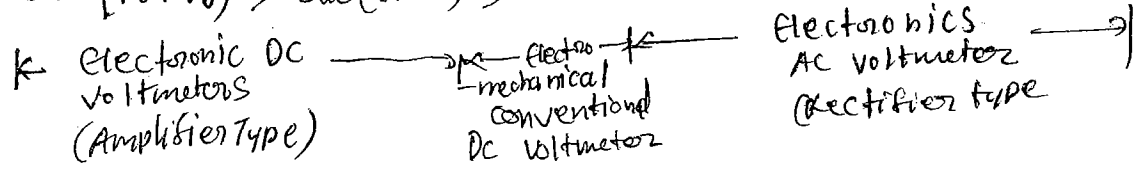
$$S_{dc}(FETVR) > S_{dc}(EFVR) > S_{dc} > S_{AC}(FWVR) > S_{AC}(HWVR)$$






They are designed like amplifier + rectifier type or as rectifier - amplifier type.


### Peak responding Voltmeter :-

A peak volt meter consist of a peak detector circuit whose o/p is fed. to PMMC & scale calibrated to read r.m.s voltage of input (sinusoidal only)


\* Peak detector

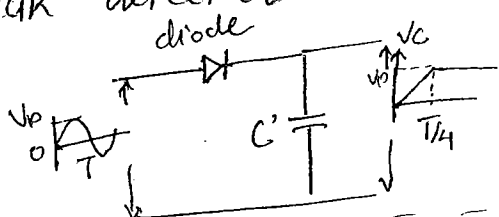

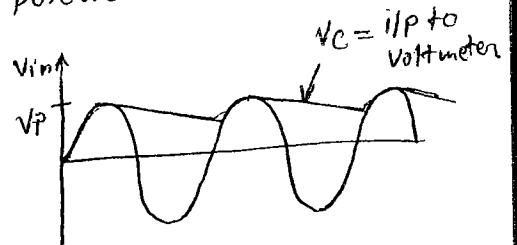
Introduce a PMMC instrument voltmeter across the capacitor (which provide discharge path)



\*

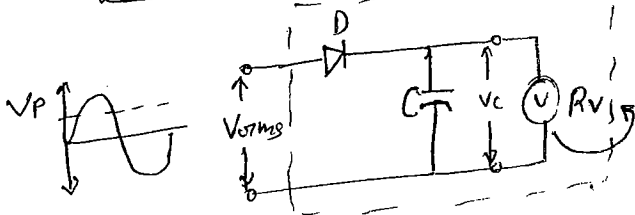

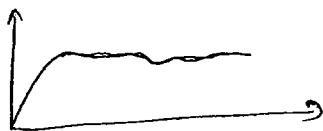\* The moving coil voltmeter connected across capacitor measure average value of its input i.e \$V\_c\$



∴ Measured average value = Peak value

$$\text{i.e. } V_{dc} = V_p$$

between peak to peak capacitor gets discharge & then charge \$R\_v\$ & \$C\$ providing discharging path & \$C\$ & \$R\_v\$ provide discharge path

$$\text{Measured avg value} = \text{Peak value}$$

\* Objective of peak voltmeter design ⇒

$$V_{rms} = \frac{1}{\sqrt{2}} V_p$$

Response of moving coil voltmeter ⇒ \$V\_{dc} = V\_p\$


Average response itself peak response

\* relation

$$V_{rms} = \frac{1}{\sqrt{2}} V_p$$

where \$V\_p = V\_{dc}\$


$$\Rightarrow V_{rms} = 0.707 V_p$$

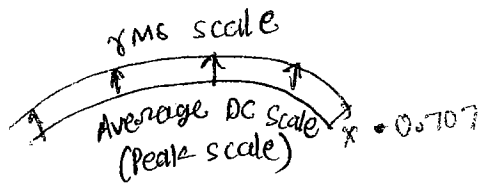

- \* A peak voltmeter is a peak-responding, rms indicating voltmeter having linear rms scale & works for both ac & dc
- \* It is derived rms meter
- \* Gives no error for sinusoidal i/p but introduces error for non sinusoidal i/p i.e. a peak voltmeter is prone to waveform error
- \* Range of frequency is audio frequency
- \* Reading of peak voltmeter for any given input is 0.707 times of  $V_{dc}$  i.e. 0.707 of  $V_p$

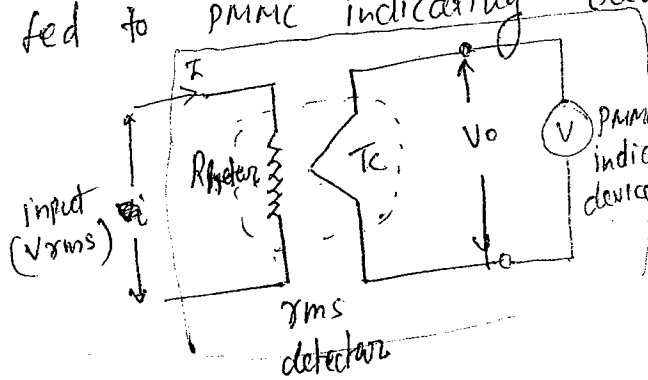5. Thermocouple Type voltmeter :-

DC voltmeter consist of an rms detector whose o/p is fed to PMMC indicating device.



$V_o =$  contact potential is a function of rise in junction temp  
 $V_o \propto$  rise in Junction temp  
 $V_o \propto$  power delivered to Rheater  
 $\propto I_{rms}^2 \cdot R_{heater}$   
 $\propto \frac{V_{rms}^2}{R_{heater}}$

\* PMMC deflection  $\theta \propto V_o$   
 $\Rightarrow \theta \propto V_{rms}^2$

$$\Rightarrow \theta = K V_{rms}^2 \rightarrow \text{Perfect square law}$$

5/11

Since  $K$  is ~~not~~ perfect const that depends on distance between  
 Rheater & TC type of metals used in TC

$$V_{rms} = 1.11 V_{dc}$$

$$V_{rms} = 0.707 V_P$$

A thermocouple instrument is a true R.M.S meter since it follows  
 perfect square law

It measure true RMS value of i/p irrespective of shape & nature.

The scale of thermocouple instrument is a perfect non linear scale.  
 since it is designed from perfect square law

Thermocouple instrument using heating effect of ~~inst~~ current  
 as such it can be used for measurement at very high  
 frequency (radio frequency)

A Thermocouple instrument is a true rms measuring, true  
 rms indicating meter with non linear scale. & work for both  
 dc & ac.

waveform errors are not present by using thermocouple  
 instrument

Q) Loading effects is not due to instrument having - - -

- (a) high <sup>VP</sup> instrument resistance.
- (b) low full scale voltage.

Q) Low sensitivity

- (d) None

Q) The i/p stage of an electronic voltmeter consist of - - -

- (a) UJT
- (b) FET
- (c) SCR
- (d) BJT

Q) Identify the voltmeter that requires an external supply  
 for


- (a) Moving coil
- (b) M-IV
- (c) ~~MTC~~ TC V
- (d) Amplifier Type

Q) Identify the decreasing order of voltmeter in terms of  
 their sensitivity

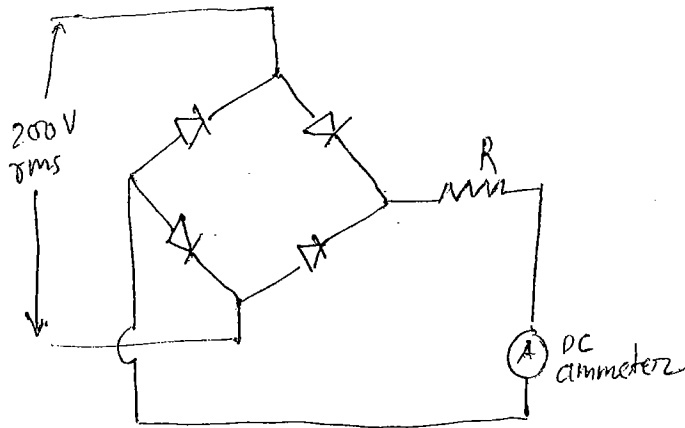- (1) A  $1000 \Omega/V$  dc voltmeter.
- (2) Half wave rectifier type ac voltmeter.
- (3) FET i/p voltmeter.
- (4) Bridge rectifier type ac voltmeter.

Ans  $\Rightarrow$  3, 1, 4, 2.

Ques: - In a rectifier voltmeter shown below, the ammeter used as full scale calibration of  $25 \text{ mA}$ . The internal resistance of the ammeter is  $100 \Omega$  each diode has fwd resistance of  $500 \Omega$  & an infinite o/w resistance then the value of  $R$  is - - - -



- (a)  $7.1 \text{ k}\Omega$
- (b)  $7.9 \text{ k}\Omega$
- (c)  $6.1 \text{ k}\Omega$
- (d)  $6.9 \text{ k}\Omega$

$$I_{\text{MPSD}} = 25 \text{ mA}$$

$$R_{\text{im}} = 100 \Omega$$

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}} = \frac{200}{\sqrt{2}} \text{ V}$$

$$R_d = 500$$

$$R_{\text{se}} = \frac{0.9 V_{\text{rms FSD}}}{I_{\text{dc FSD}}} - 2R_d - R_m$$

$$= 0.9 \times \frac{200}{25 \times 10^{-3}} - 2(500) - 100 \Omega$$

$$= 7.2 \text{ k}\Omega - 1000 - 100 \Omega$$

$$= 7.2 \text{ k}\Omega - 1.1 \text{ k}\Omega$$


$$= 6.1 \text{ k}\Omega$$

sol: -  $0-1 \text{ mA}$  Ammeter having internal resistance of  $100 \Omega$  is to used in  $10 \text{ V}$  AC range, with the help of half wave rectifier assume diodes are ideal the value of  $R_{\text{se}}$  is - - - -

$$R_{se} = 0.45 \times \frac{10}{1 \times 10^{-3}} - 100$$

$$= 4.5 k\Omega - 100$$

$$= 4.4 k\Omega$$

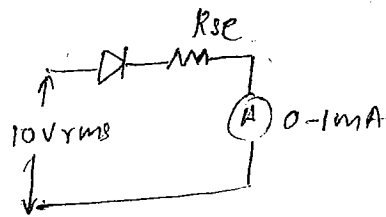

Ques. A rectifier type AC voltmeter has dc sensitivity of  $10 k\Omega/V$ .  
 Then its i/p resistance in 10V ac range is -----  
 (a)  $100 k\Omega$  (b)  $4.5 k\Omega$  (c)  $9 k\Omega$  (d)  $90 k\Omega$ .

$$S_{ac} = \frac{RV}{V_{rms}}, \quad S_{ac} = 0.9 \text{ sdc}$$

$$V_{dc} = 10 \frac{V}{\Omega}, \quad V_{rms} = 10V$$

$$R_{se} = AC \text{ sensitivity} \times AC \text{ volt range}$$

$$RV(FW) = 0.9 \text{ sdc} \times 10$$


$$= 0.90 k \times 10 \frac{kV}{V} \times 10$$

$$= 90 k\Omega$$

Ques Loading error is pre dominant in -----  
 (a) DC measurement (b) AC (c) both AC & DC (d) none

Ques :- A rectifier type ac voltmeter is used to measure a symmetrical square wave voltage with zero mean the peak to peak amplitude of square wave is 2V.

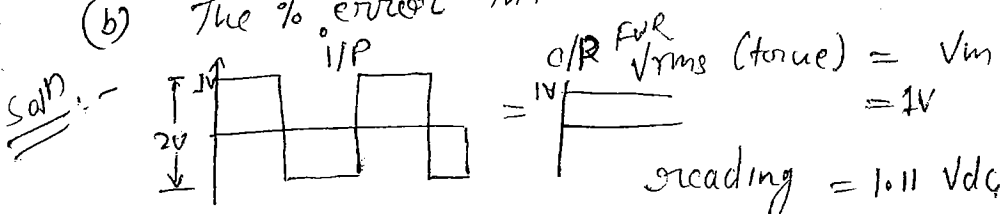- (a) Then the voltmeter indicate -----  
 (b) The % error introduce into the reading is -----



$V_{dc} = \text{avg value of o/p of full wave rectifier}$

reading of FWR  $V_s = \frac{\pi}{2\sqrt{2}} V_{dc}$  or  $1.11 V_{dc}$ .


$$V_{dc} = 1V$$

$$V_s = 1.11 \times 1V$$


$$= 1.11 V = V_{rms} (\text{ind})$$

$$\begin{aligned} \text{Error} &= V_{\text{rms}}(\text{true}) - V_{\text{rms}} \\ &= 1.011 \text{ V} - 1 \text{ V} \\ &= +0.011 \text{ V} \end{aligned}$$
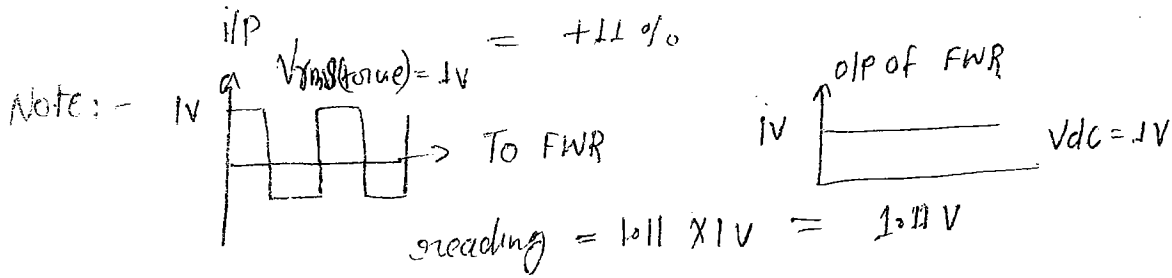
$$\begin{aligned} \% \text{ error in reading} &= \frac{1.011 - 1}{1} \times 100 \% \\ &= \frac{+0.011}{1} \times 100 \% \end{aligned}$$



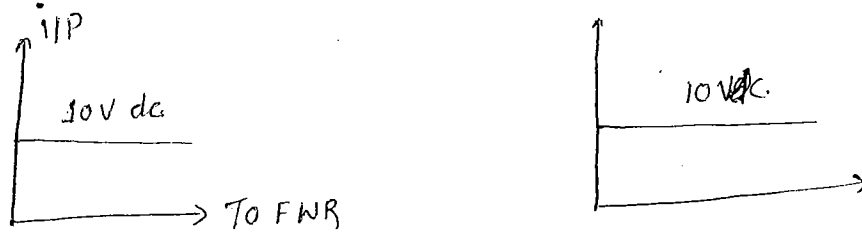Ques: - A 10Vdc is applied <sup>Wave</sup> ~~when~~ electronic voltmeter that uses FWR. Then the reading of the voltmeter is - - -



$$\text{reading} = 1.011 \times 10 = 10.11 \text{ V}$$

$$\text{error} = 10.11 - 10 = 0.11 \text{ V}$$

$$\% \text{ error} = 1.1 \%$$


Ques: - An electronic avg measuring voltmeter whose scale is calculated to read RMS value of sinusoidal waveform uses a half wave rectifier. when used to measured symmetrical square wave with zero mean it indicate 24 volts then the actual RMS of the input is - - -

(a)  $\frac{24\sqrt{2}}{\pi} \text{ V}$  (b)  $\frac{48\pi}{\sqrt{2}} \text{ V}$  (c)  $\frac{24\pi}{\sqrt{2}} \text{ V}$  (d)  $\frac{48\sqrt{2}}{\pi} \text{ V}$

for Half wave rectifier

$$= 2.2 \text{ Vdc} = \frac{24}{2.2} = 10.90 \text{ Volt}$$

$$\cancel{2.2} \times \cancel{10.90} =$$

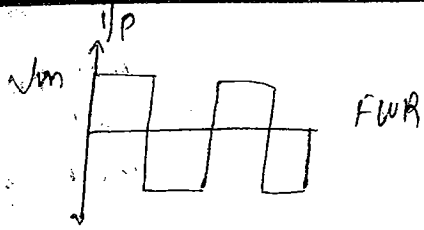


$$V_{rms} (true) = V_m$$

$$V_{avg} = 2.22 \text{ Vdc} \quad \text{27}$$

$$24V = \frac{\pi}{\sqrt{2}} V_{dc}$$
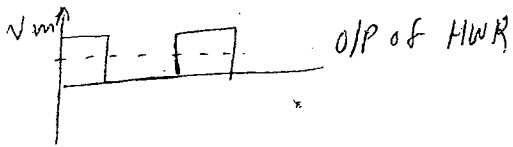
$$V_{dc} = \frac{24\sqrt{2}}{\pi} \text{ V} \quad \text{FWR}$$



$$V_{avg} = 2.22 \text{ Vdc}$$

$$V_{avg} = \frac{\pi}{\sqrt{2}} \times V_{dc}$$

$$24V = \frac{\pi}{\sqrt{2}} \times \frac{V_m}{2}$$

$$\therefore V_m = \frac{48\sqrt{2}}{\pi} \text{ V}$$

= actual rms of i/p square wave

A direct voltage is applied to a peak voltmeter, which reads 45 volts. Then the value of applied voltage is ----

$$V_{dc} = 0.707 V_p$$

$$45 = 0.707 \times V_p$$

$$V_p = \frac{45}{0.707} = 63.65 \text{ Volt}$$

Q. meter

If i/p to rectifier volt is  $|1 + \sin 314t|$

$$\sqrt{1^2 + \left(\frac{1}{\sqrt{2}}\right)^2} = \sqrt{\frac{3}{2}} \text{ Volt}$$

Q-meter :- \* Q-meter stands for quality factor meter which is series RLC ckt. As such the principle of operation behind the working of Q-meter is series resonance.

\* There are 3 types of connection of Q meter.

- (1) direct connection
- (2) Series connection
- (3) Shunt or parallel connection

\* Direct connection is used for measurement of electrical properties of a given test coil like

Tone Q of coil (Q-coil)

self inductance of coil (L)


self capacitance (or) distributed capacitance of coil (Cd)

Because there is calibrated Q scale & it is not quantity but it is property.

\* In series connection element are connected in series & is used for measurement of low impedance.

\* In shunt connection element are connected in parallel & is used for measurement of high impedance.

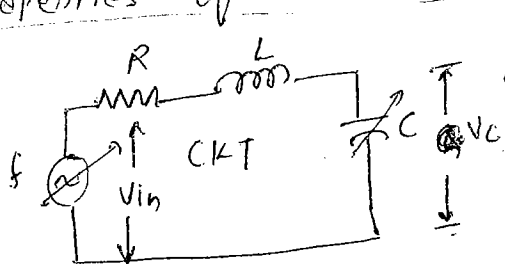Properties of series RLC ckt "at resonance"



\* resonance cond<sup>n</sup>  
 $X_L = X_C$ ,  $\omega L = \frac{1}{\omega C}$   
 $2\pi fL = \frac{1}{2\pi fC}$

To resonant fixed frequency as vary capacitance  
 i.e. fix frequency as  $f_x$

$$2\pi f_x L \neq \frac{1}{2\pi f_x C}$$

↙ vary C ↘

At  $C_x$ :  $2\pi f_x L = \frac{1}{2\pi f_x C_x}$



(1) resonant frequency

$$f_x = \frac{1}{2\pi\sqrt{LC}}$$

(2) Impedance of the ckt

$$Z = R + j(\omega L - \frac{1}{\omega C})$$

If inductive reactance = capacitive reactance

$$Z = R$$

(3) At resonant voltage across capacitor:

$$V_C = I X_C$$

$$V_C = \frac{V_{in}}{Z} \times X_C$$

$$V_C = \left[ \frac{X_C}{R} \right] V_{in}$$

$$V_C = Q V_{in}$$

here  $Q = \frac{X_C}{R}$


$$V_{Cmax} = Q \cdot V_{in}$$

\* At resonance the series RLC ckt behaves as "voltage magnifier" i.e. the oscillatory voltage injected into ckt is magnified by Q-times & appears across the capacitor.

∴ At resonance voltage across capacitor is max<sup>m</sup>

(Note: - ideal behind }  $Q = \frac{V_{Cmax}}{V_{in}}$   
Q-meter design)

Direct connection of Q-meter ⇒

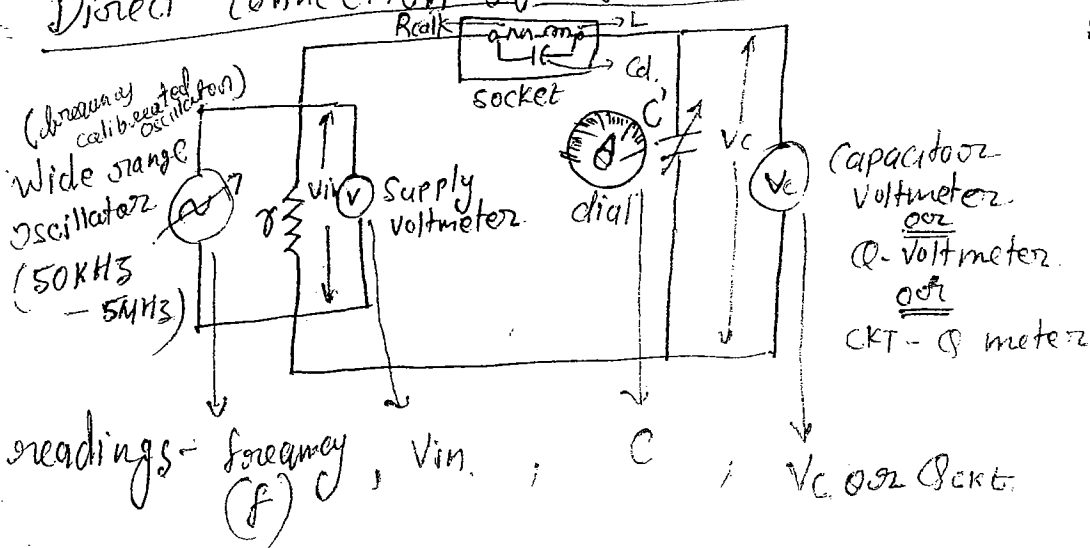

\* Very High frequency we used Thermocoupled Voltmeter.

$$Q = \frac{1}{R} \times V_{Cmax}$$

→ Introduce the test coil into socket & resonant

↳  $F_{fix}$  &  $V_{in}$ , vary capacitance


till capacitor voltmeter show max deflection  
 Note down the reading  $f \Rightarrow$  resonant frequency,  $V_{in}$ ,  
 $C$ ,  $V_{max}$

$$\therefore Q = \frac{V_{max}}{V_{in}}$$

$$= \frac{\text{capacitor voltmeter reading}}{\text{supply voltmeter reading}}$$

\* To avoid such calculation the designer provides a Q-scale calibrated from voltage scale of capacitor voltmeter

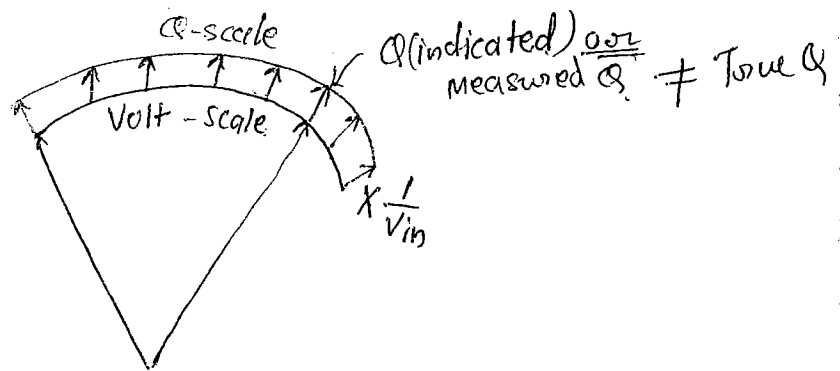\* Source must be accurately high stability



\* Capacitive voltmeter

is also known as Q voltmeter (measured Q)

$$Q_{true} = \frac{\omega L}{R_{coil}} \quad \text{or} \quad \frac{1}{\omega CR} = Q_{coil}$$

But

$$Q_{meas} = \frac{\omega h}{R_{coil} + r} \quad \text{or} \quad \frac{1}{\omega(C+cd)(R_{coil} + r)}$$

\* Measured Q  $\neq$  True Q

\* The indicated Q i.e. measured Q by Q-voltmeter is not the true Q of the coil but it is entire CKT Q.

Error in Q measurement :- \* Measured Q is always less than true Q because of two errors.

occur namely are  $r$  &  $C_d$

$r$  = insertion resistance or shunt resistance ( $R_{sh}$ )  
=  $0.02 \Omega$

$C_d$  = self capacitance or distributed capacitance of coil

$$\% \text{ error} = \frac{Q_{\text{measure}} - Q_{\text{true}}}{Q_{\text{true}}} \times 100\%$$

$$\text{Error} = Q_{\text{measure}} - Q_{\text{true}}$$

Note :- (1) True Q is actual coil Q or coil Q  
(2) Measured Q is indicated Q is observed-Q is circuit-Q

\* Error in Q meter due to 'r'

$$Q_{\text{meas}} = \frac{\omega L}{R_{\text{coil}} + r}$$

$$Q_{\text{true}} = \frac{\omega L}{R_{\text{coil}}}$$

$$* \text{Error} = Q_{\text{meas}} - Q_{\text{true}} = \frac{\omega L}{R_{\text{coil}} + r} - \frac{\omega L}{R_{\text{coil}}}$$

$$\% \text{ error} = \frac{\frac{\omega L}{R_{\text{coil}} + r} - \frac{\omega L}{R_{\text{coil}}}}{\frac{\omega L}{R_{\text{coil}}}} \times 100$$

$$* \text{Error (due to r)} = -\frac{r}{R_{\text{coil}} + r} \times 100\%$$

\* Correction factor :-

$$\frac{Q_{\text{true}}}{Q_{\text{measure}}} = \frac{\frac{\omega L}{R_{\text{coil}}}}{\frac{\omega L}{R_{\text{coil}} + r}} = \frac{R_{\text{coil}} + r}{R_{\text{coil}}}$$

$$Q_{\text{true}} = Q_{\text{meas}} \left[ \frac{R_{\text{coil}} + r}{R_{\text{coil}}} \right]$$

$\downarrow$   
K<sub>r</sub>

\* In general error in  $Q$ -measurement due to  $r$  can be neglected since  $r \ll R_{coil}$

(\*) Error in  $Q$  measurement due to "Cd"

$$Q_{meas} = \frac{1}{\omega(C+cd)(R_{coil} + r)}$$

$$\approx \frac{1}{\omega(C+cd)R_{coil}} \quad (\because r \ll R_{coil})$$

$$Q_{true} = \frac{1}{\omega C R_{coil}}$$

$$\text{error} = Q_{meas} - Q_{true}$$

$$= \frac{1}{\omega(C+cd)(R_{coil} + r)} - \frac{1}{\omega C R_{coil}}$$

$$\% \text{ error} = \frac{\frac{1}{\omega(C+cd)(R_{coil} + r)} - \frac{1}{\omega C R_{coil}}}{\frac{1}{\omega C R_{coil}}} \times 100$$

$$\% \text{ error} = \frac{-cd}{C+cd} \times 100 \%$$

↓  
resonating capacitance

$$* \text{ correction factor} = \frac{Q_{true}}{Q_{meas}}$$

$$\frac{Q_{true}}{Q_{meas}} = \frac{\frac{1}{\omega C R_{coil}}}{\frac{1}{\omega(C+cd)R_{coil}}}$$

$$\frac{Q_{true}}{Q_{meas}} = \frac{C+cd}{C}$$

$$Q_{true} = Q_{meas} \left( 1 + \frac{cd}{C} \right)$$

Where  $Q_{\text{true}} = \text{coil } Q (?)$

$Q_{\text{meas}} = Q - \text{voltmeter reading}$


$C = \text{tuning or resonating capacitance}$

$C_d = \text{self capacitance of coil } (?)$

Note:- To get the value  $Q_{\text{true}}$  of coil,  $C_d$  must be known. Therefore measure  $C_d$  first.

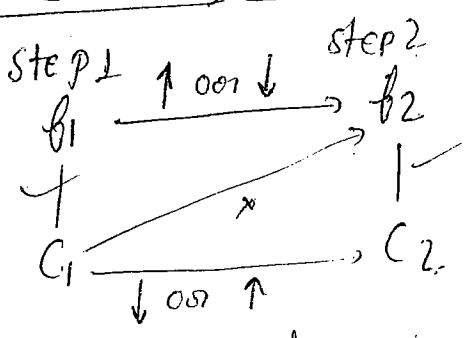(1) Measurement of  $C_d$  of coil (shunt capacitance)

\* Introduce a test coil into socket of Q-meter & resonant twice at  $f_1$  for first coil &  $f_2$  for second coil.



Note down reading in both steps

\* Step (1) readings: frequency  $f_1$ ,  $V_{in}$ ,  $C_1$ ,  $Q_1$ ,  $V_{C1}$

$$f_1 = \frac{1}{2\pi\sqrt{L(C_1 + C_d)}} \quad \text{--- (1)}$$

$$V_{C1} = Q_1 V_{in}$$

Step (2) readings:  $f_2$ ,  $V_{in}$ ,  $C_2$ ,  $Q_2$ ,  $V_{C2}$

$$f_2 = \frac{1}{2\pi\sqrt{L(C_2 + C_d)}} \quad \text{--- (2)}$$

$$V_{C2} = Q_2 V_{in} \quad // \quad 2\pi\sqrt{L(C_1 + C_d)}$$

$$\therefore f_2 = n f_1$$

$$\frac{\text{eqn (1)}}{\text{eqn (2)}} = \frac{f_1}{f_2} = \frac{1/2\pi\sqrt{L(C_1 + C_d)}}{1/2\pi\sqrt{L(C_2 + C_d)}}$$

$$\frac{f_1}{n f_1} = \sqrt{\frac{L(C_2 + C_d)}{L(C_1 + C_d)}}$$

Cancelling both side

$$\frac{1}{n^2} = \frac{C_2 + Cd}{C_1 + Cd}$$

$$n^2 C_2 + n^2 Cd = C_1 + Cd$$

$$n^2 Cd - Cd = C_1 - C_2 n^2$$

$$Cd = \frac{C_1 - C_2 n^2}{n^2 - 1}$$

(2) Measurement of 'L of coil'

\* first measured 'Cd' of coil

Then we know  $f = \frac{1}{2\pi\sqrt{L(C+Cd)}}$

$$f^2 = \frac{1}{4\pi^2 L(C+Cd)}$$

$$L = \frac{1}{4\pi^2 (2\pi f)^2 [C+Cd]}$$

$$L = \frac{1}{\omega^2 [C+Cd]}$$

\* Use either step (1) reading =  $b_1, C_1$   
or step (2) reading =  $b_2, C_2$

To measure 'L of coil'

$$L = \frac{1}{(2\pi f_1)^2 (C_1 + Cd)} \quad \text{or}$$

$$L = \frac{1}{(2\pi f_2)^2 (C_1 + Cd)}$$

Measurement of  $Q$  of coil

\* First measure  $cd$  of coil'

\* Then we know  $Q_{true} = Q_{meas} \left(1 + \frac{cd}{C}\right)$

\* Use either step (1) reading  $Q_1, C_1$   
or step (2) reading  $Q_2, C_2$

along with  $cd$   
to measure 'true  $Q$  of coil'

$$Q_{true} = Q_1 \left(1 + \frac{cd}{C_1}\right)$$

$$Q_{true} = Q_2 \left(1 + \frac{cd}{C_2}\right)$$

10/8/201

Que :-


A reading of 120 is obtained when a stranded conductor is connected to the  $ckt$  of  $Q$  meter & the variable capacitor is adjusted to a value 300 PF a loss less capacitor  $C_x$  is then connected in parallel with variable capacitor & same reading was obtained where the variable capacitor is read just ~~strat~~ to a value of 200 PF the value of  $C_x = \dots$

(1) 200 PF

(2) 120 PF

(3) 100 PF

(4) 50 PF

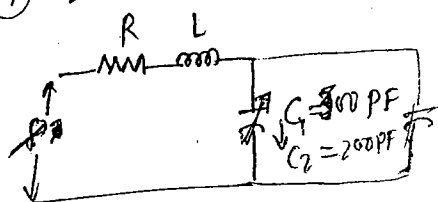

$$Q_1 = \frac{1}{\omega C_1 R} = 120$$

$$Q_2 = \frac{1}{\omega (C_2 + C_x) R} = 120$$

$$\therefore Q_1 = Q_2$$

$$\frac{1}{\omega C_1 R} = \frac{1}{\omega (C_2 + C_x) R}$$

$$C_1 = C_2 + C_x$$

$$300 \text{ PF} = 200 \text{ PF} + C_x$$

$$C_x = 100 \text{ PF}$$

Ques:- A coil is tested with a Q meter under self capacitance of coil is found to be 820 pF. Resonance has occurred at a frequency of  $10^6$  rad/sec with a capacitance of  $9.18 \mu\text{F}$ . Then the self inductance of coil ---

- (a) 100 mH      (b) 100  $\mu\text{H}$       (c) 180  $\mu\text{H}$       (d) 100  $\mu\text{H}$

$$L = \frac{1}{\omega^2 (C + C_d)}$$

$$= \frac{1}{(10^6)^2 (820 \times 10^{-12} + 9.18 \times 10^{-9})}$$


$$= \frac{100 \mu\text{H}}{}$$

Note % error in Q =  $\frac{-C_d}{C + C_d} \times 100\%$

Ques:- A Q meter is supply with an oscillator having 500 mV o/p voltage by testing an unknown coil reading of Q voltmeter is 10 volt then Q factor of coil is ---

Soln:-  $Q = \frac{V_{\text{max}}}{V_{\text{in}}} = \frac{10\text{V}}{500\text{mV}} = 20$

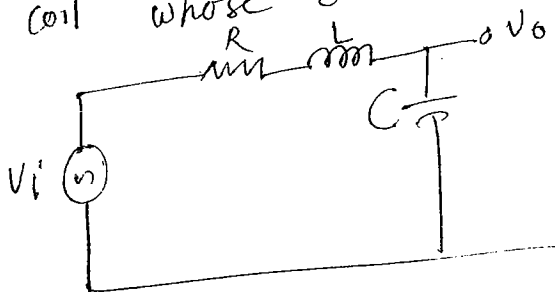
2005 Ques:- The ckt shown in below fig the Q factor of coil whose resistance ~~is~~ R & inductance L is



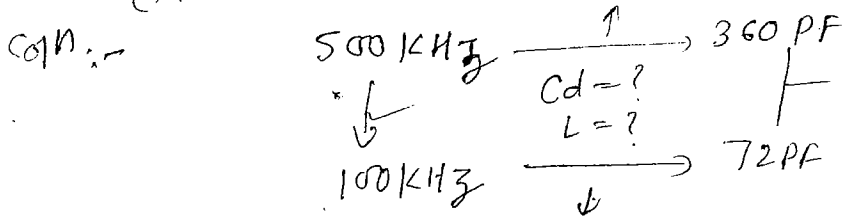- (a)  $\frac{V_1 - V_0}{V_1}$   
 (b)  $\frac{V_0}{V_1}$   
 (c)  $\frac{V_0 - V_1}{V_0}$   
 (d)  $\frac{V_1}{V_0}$



Ques:- A coil is to resonance at 500 KHz with resonant capacitance 360 PF. when the frequency is raised to 1 MHz resonance is obtained at 72 PF. Then the self L of coil is -----  
 (Also self inductance of coil)



$$n = \frac{1 \text{ MHz}}{500 \text{ KHz}} \Rightarrow 2$$

$$C_d = \frac{360 \text{ PF} - (2)^2 72 \text{ PF}}{(2)^2 - 1}$$

$$C_d = \frac{360 \text{ PF} - 288 \text{ PF}}{4 - 1}$$

$$C_d = 24 \text{ PF}$$

Ques:- A coil chords to resonance at 500 KHz with a resonating capacity of 360 PF at 250 KHz the resonance is obtained with a resonating capacity of 160 PF then distributed capacitance of coil is -----

Soln:-

$$n = \frac{250 \text{ KHz}}{500 \text{ KHz}} = \frac{1}{2}$$

$$C_d = \frac{36 \text{ PF} - \left(\frac{1}{2}\right)^2 160}{\left(\frac{1}{2}\right)^2 - 1}$$

$$C_d = \frac{36 \text{ PF} - 40}{\frac{1}{4} - 1}$$

$$C_d = 5.33 \text{ PF}$$

Que:- A coil with a resistance of  $10 \Omega$  is connected in a direct measurement mode of Q meter resonance occur with oscillator frequency  $1 \text{ MHz}$  & resonating capacity set as  $65 \text{ PF}$  Then the magnitude of ~~error~~ % Error introduced in meas of Q by inductance resistance  $0.02 \Omega$  is -


Soln:-

$$\frac{-r}{r + R_{\text{coil}}} \times 100 \%$$

$$\frac{-0.02 \Omega}{10.02 \Omega} \times 100 \%$$

$$= -0.2 \%$$

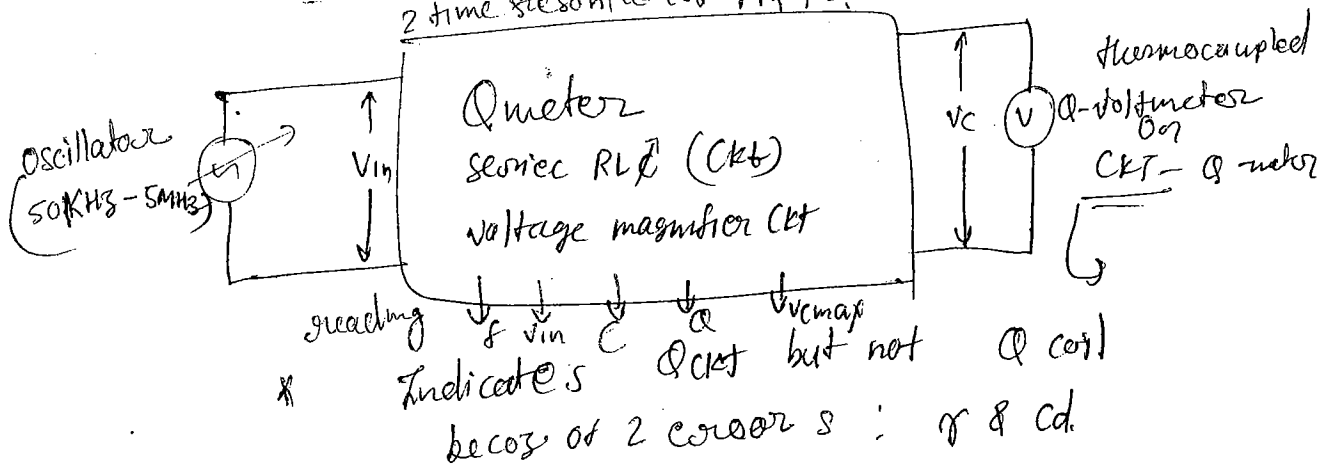Que:- Principle of operation behind the work of Q meter  
 $\rightarrow$  series resonance  
 2 time resonator of  $f_1$  &  $f_2$



\* With respect to  $r$

$$\alpha \frac{Q_{\text{meas}}}{Q_{\text{true}}} = 1 + \frac{r}{R_{\text{coil}}}$$

$$\alpha \% \text{ error} = \frac{-r}{R_{\text{coil}}} \times 100\% \rightarrow$$

negligible  
 ( $\because r \ll R_{\text{coil}}$ )

\* With respect to  $C_d$

$$\alpha \frac{Q_{\text{true}}}{Q_{\text{meas}}} = 1 + \frac{C_d}{C}$$

$$\% \text{ error} = \frac{-Cd}{Cd+C} \times 100\%$$

84

$$f = \frac{1}{2\pi\sqrt{L(C+C_d)}}$$

$$Q = \frac{V_{\max}}{V_{in}}$$

measured  
freq  
react  
resonance

$$\textcircled{1} \quad C_d = \frac{C_1 - n^2 C_2}{n^2 - 1} ; \quad n = \frac{f_2}{f_1}$$

$$\textcircled{2} \quad L = \frac{1}{\omega^2(C+C_d)}$$

$$\textcircled{3} \quad Q_{\text{true}} = Q_{\text{measured}} \left(1 + \frac{C_d}{C}\right)$$

Que:- Explain working of Q meter. To find the self capacitance of coil the Q meter the resonance was obtain with

(1) Tuning capacitor of 1530 PF at 1 MHz

(2) Tuning capacitor of 162 PF at 3 MHz

what is the value of self capacitance

Soln  
Given data, Tuning capacitor  $f_1 = 1 \text{ MHz}$ ,  $C_1 = 1530 \text{ PF}$

$f_2 = 3 \text{ MHz}$ ,  $C_2 = 162 \text{ PF}$

We know  $C_d = \frac{C_1 - n^2 C_2}{n^2 - 1}$ ,  $n = \frac{f_2}{f_1} = \frac{3}{1} = \underline{\underline{3}}$

$$C_d = \frac{1530 \text{ PF} - (3)^2 \times 162 \text{ PF}}{3^2 - 1} = \underline{\underline{9 \text{ PF}}}$$

## Resolution of DVM :-

\* The smallest possible increment change allowable in the i/p is known as resolution of DVM

$$\text{resolution} = \frac{1}{10^N} \quad \rightarrow \text{scale resolution}$$

where  $N$  = total number of FULL digits

$$\left. \begin{array}{l} \text{resolution in a} \\ \text{selected voltage} \end{array} \right\} = \frac{1}{10^N} \times \text{selected volt - range}$$

(Note:- Resolution is nothing but min count)


\* Sensitivity of DVM  $\Rightarrow$  The smallest voltage that can be sensed, measured & displayed in lowest voltage range. is known as sensitivity of DVM.

$$\text{Sensitivity} = \text{resolution} \times \text{lowest volt range}$$

$$= \frac{1}{10^N} \times \text{lowest volt range}$$



(Note:- Sensitivity is ~~is~~ nothing but min of mins)

\* FULL digit

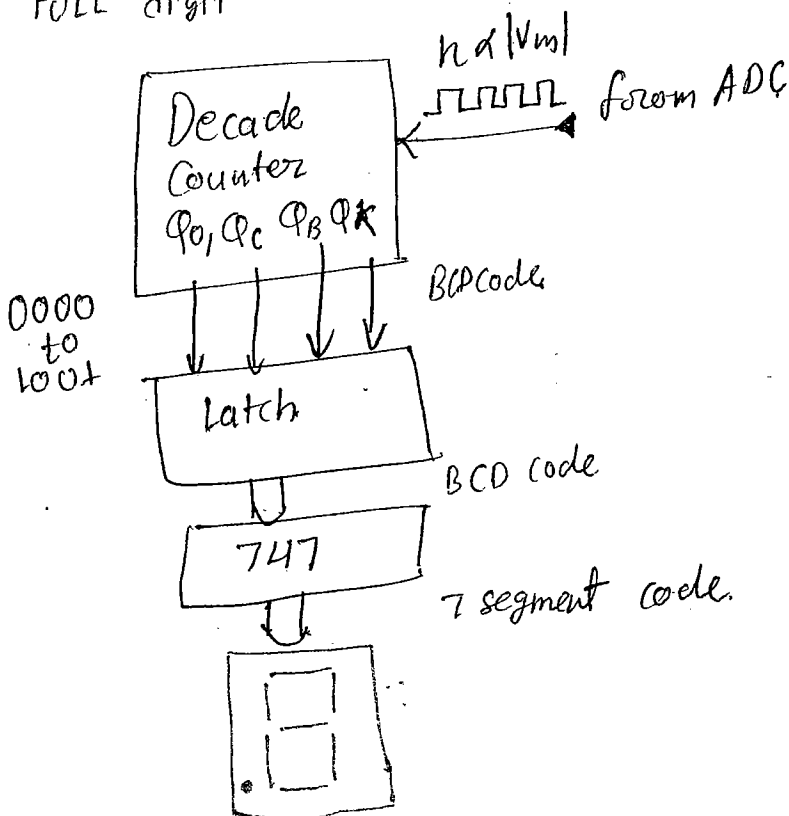


display driver

# \* 3.- digit DVM

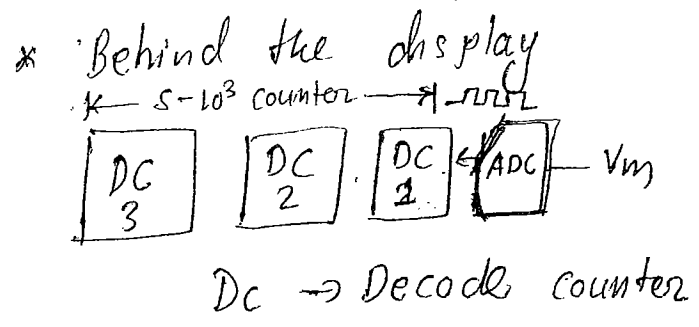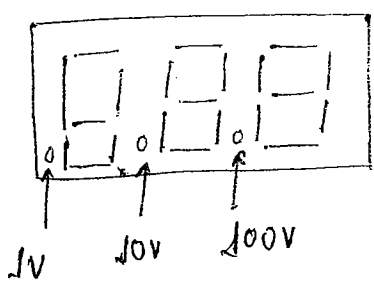

→ Count roll-over

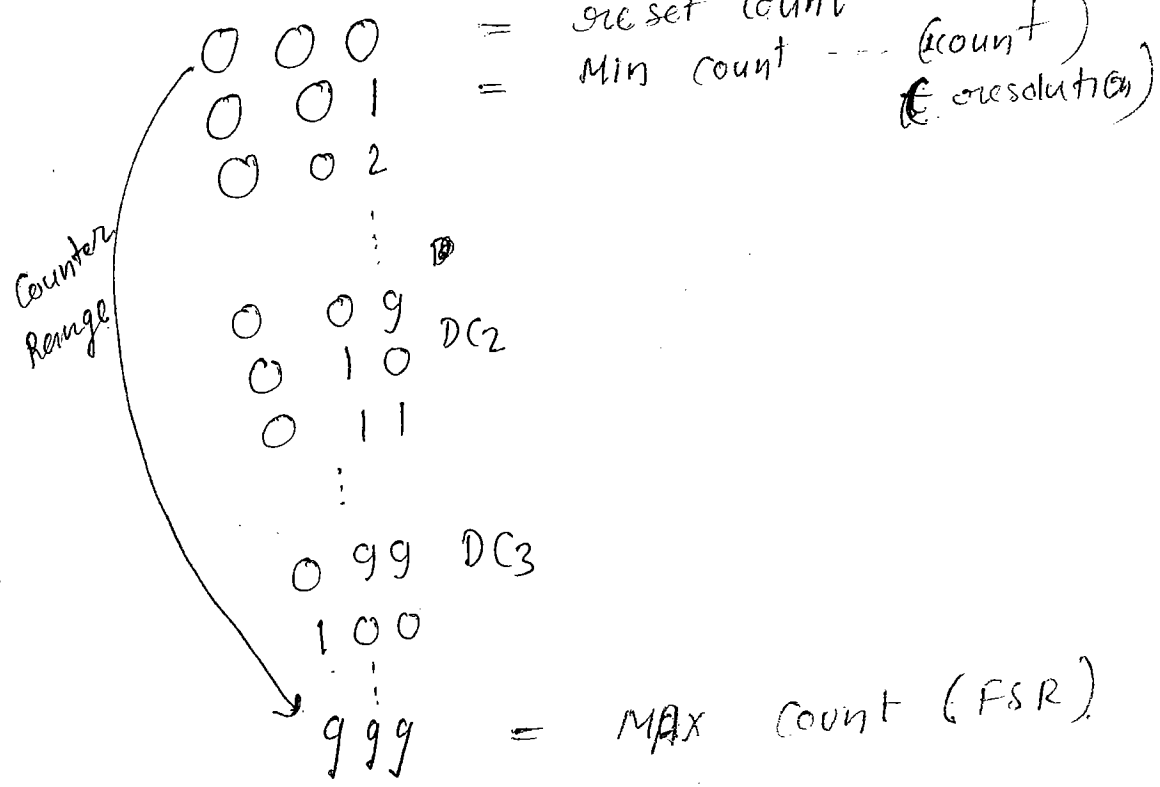


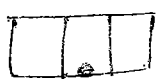
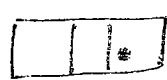
\* Count Range of 3 digit DVM

from 0 to 999

$$\begin{aligned} \text{Scale} &= \text{min} + \text{MAX} \\ &= 001 + 999 \\ &= 1000 \text{ counts} \\ &= 10^3 \text{ counts} \end{aligned}$$

→ resolution of 3 digit ~~count~~ DVM :-

$$\gamma = \frac{1}{10^3} = \frac{1}{1000} = 1:1000 = 0.001 = 0.1\%$$

→ Switch Position	selected volt range	Min voltage	MAX voltage
A (TOP)	0-1V range 	.001V	0.999V
B	0-10V range 	0.01V	9.99V
C (Bottom)	0-100V range 	00.1V	99.9V

1V range      10V range      100V range  
 Sensitivity  $\left\{ \begin{array}{l} .001 \\ .002 \end{array} \right\} 1\text{mV}$        $\left\{ \begin{array}{l} 0.01 \\ 0.02 \end{array} \right\} 10\text{mV}$        $\left\{ \begin{array}{l} 00.1 \\ 00.2 \end{array} \right\} 100\text{mV}$


\* resolution of 3 digit DVM =  $0.001 = 1/10^3$   
 i.e known as scale resolution


\* resolution of 3 digit DVM in 1V range =  $\frac{1}{10^3} \times 1\text{V}$   
 = 1mV

\* resolution of 3 digit DVM in 10V range =  $10 \times \frac{1}{10^3}$   
 = 10 mV

\* resolution of 3 digit DVM in 100V range  
 =  $\frac{1}{10^3} \times 100$   
 = 100 mV

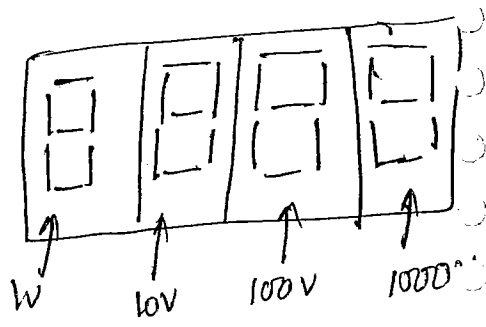\* Sensitivity of 3 digit DVM in lowest voltage range  
 of 1V is  
 $\Rightarrow \frac{1}{10^3} \times 1\text{V} \Rightarrow 1\text{mV}$



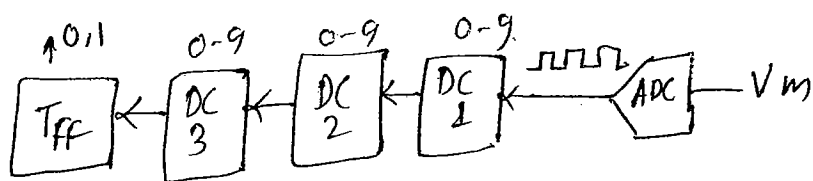

TFF  $\rightarrow$  Toggle flip Flop

$\frac{1}{2}$  digit  
 Max count  
 Total count  
 $\frac{0-3}{4}$ ,  $\frac{0-5}{6}$   
 $\frac{1}{2}$ ,  $\frac{3}{4}$ ,  $\frac{5}{6}$  digit used for stand of count range.  
 \* scale is going to change  
 \* sensitivity is not to change  
 \*

Date  
07/08/2011

## Extension Digit

\* These digits are used for extending a count range of  $n$  digit DVM.

\* Specification:  $\frac{X}{Y}$  digit

where  $X = \text{MAX count}$


$Y = \text{Total count on scale}$   
(multiplication factor)

Available Ext digits	Count range
$\frac{1}{2}$ digit	→ 0, 1
$\frac{3}{4}$ digit	→ 0, 1, 2, 3
$\frac{5}{6}$ digit	→ 0, 1, 2, 3, 4, 5


Note:- No decimal point for extension digit.

### (A) $3\frac{1}{2}$ digit DVM.

\* Counting Unit

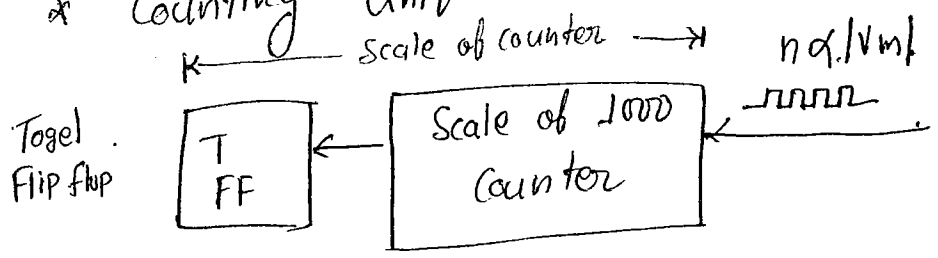


\*

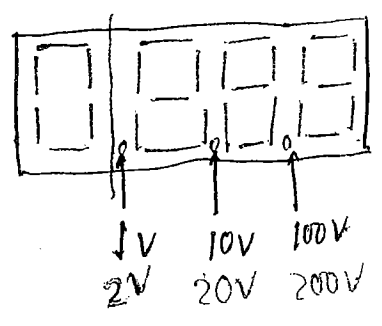



Count roll over

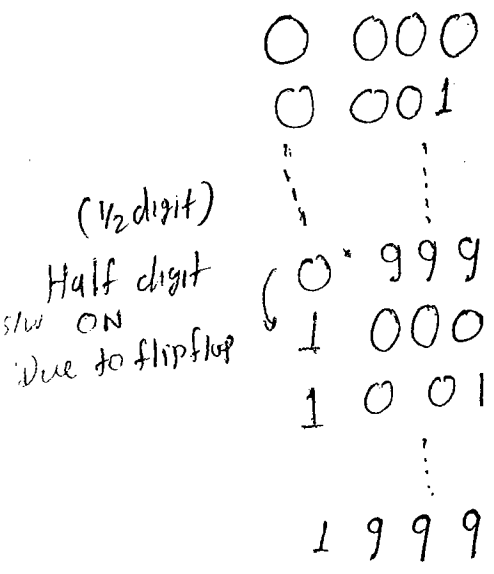

\* reset count = 0

Min count = 0001 → 1 count over resolution

MAX count = 1999

\* scale = 0001 + 1999


= 2,000 counts

=  $2 \times 10^3$  counts

Scale of  $3\frac{1}{2}$  digit DVM is 2 times of scale of 2 digit DVM

\* resolution of  $3\frac{1}{2}$  digit DVM

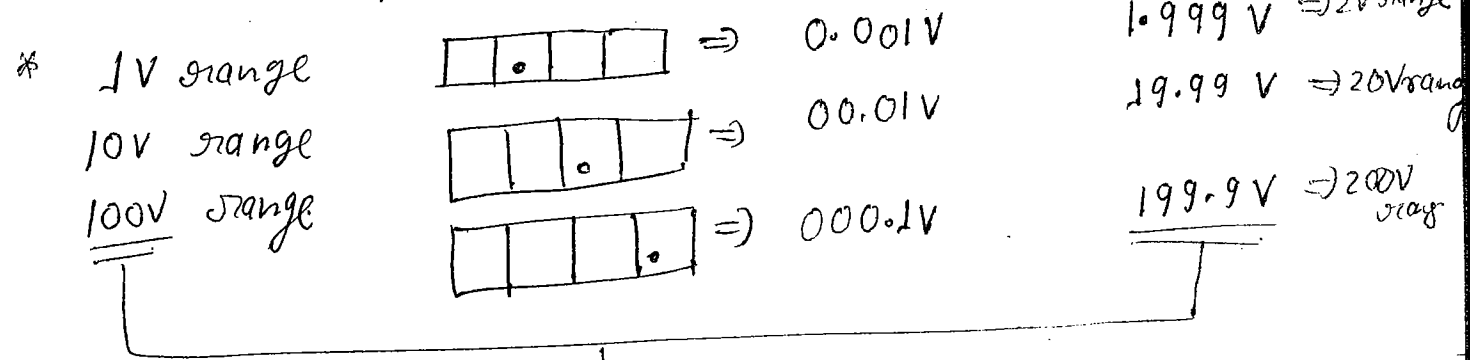$\gamma = \frac{1}{10^3} = \frac{1}{1000} = 0.001$  or 0.1 %  
Min Max



↓  
OVER RANGING  
(Due to 1/2 digit turn on)

\* resolution of  $3\frac{1}{2}$  digit ~~over~~ voltage range  
1mV

\* resolution of  $3\frac{1}{2}$  digit in 10 V range

$$= \frac{1}{2 \times 10^3} \times 200$$

$$= 10 \text{ mV} = 0.01 \text{ V}$$

Resolution of  $3\frac{1}{2}$  digit in 100 V range

$$= \frac{1}{2 \times 10^3} \times 200$$

$$= \frac{1}{10} = 100 \text{ mV}$$

$$= 0.1 \text{ V}$$

\* Note:- \* Because of extension digits resolution & sensitivity are not altered whereas the scale will extend

\* The scale of  $n\frac{1}{2}$  digit DVM is 2 times of scale of  $n$  DVM

\* Similarly the  $n\frac{3}{4}$  digit DVM is 4 times of scale of  $n$  digit DVM

\*  $n\frac{5}{6}$  digit DVM is 6 times of scale of  $n$  digit DVM

### (X) Types of ADCs

\* FLASH type  $\rightarrow$  Fastest ADCs

\* Successive Approx - type, Counter type & Ramp type




\* Dual slope integrating type  $\rightarrow$  slowest (C.S.)

Decrease

$\uparrow$  conversion time  $\propto \frac{d}{\text{time speed}}$   $\downarrow$

\* Flash type or simultaneously or parallel comparators? type same
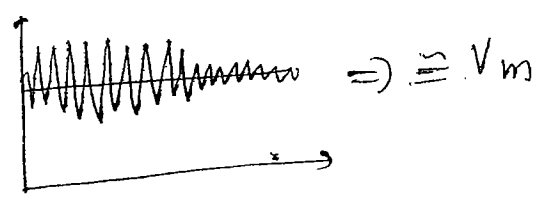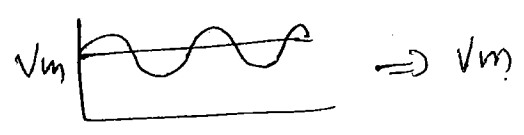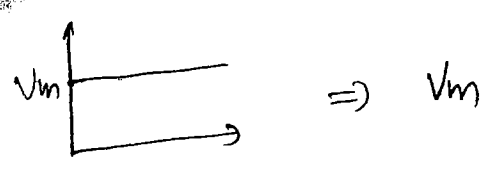
$$\frac{1}{T_0} \int_0^{T_0} v_m dt = \text{Avg value of } v_m$$



There are two types of ADC namely  
 Integrating type (Dual slope type) & non integrating  
 type ADCs (Flash, successive, counter, Ramp type)

In integrating type ADCs an integrator are present in  
 i/p side as such the unknown analog DC to be  
 measured ~~DC value~~ will be integrated for a  
 fixed time period which gives a measurement of true  
 avg value


As such even if there is either AC signal  
 super imposed or noise as present on the dc voltage  
 to be measured, errors will not be introduced into  
 measurement i.e noise effect is suppressed or eliminated,  
 due to existence of indicator. Therefore dual slope integrating  
 type ADCs is the most widely used ADC. since it offer  
 highest noise reduction rejection, highest stability &  
 highest accuracy

\* The basic principle of operation of dual slope design type.  
 design is voltage to time conversion.

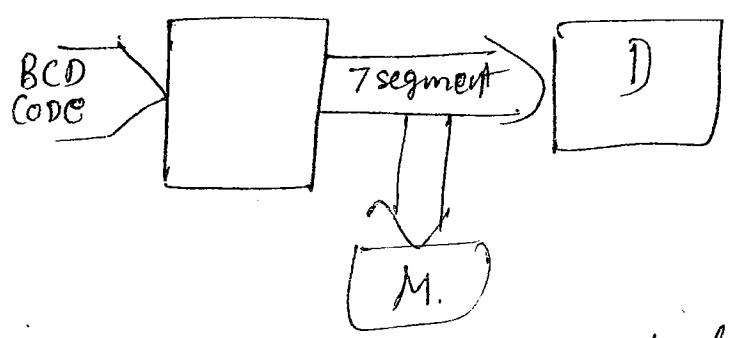x) Advantages: of Digital Voltmeter (over analog meter)

- \* ① The i/p resistance of a digital voltmeter ~~is~~ is in the  
 order of MΩ. As such loading effect on ckt under  
 test minimized.
- \* ② DVM ~~offer~~ offer superior resolution comparative analog  
 meter. superior resolution --- 1 : 10<sup>6</sup> in order of

- ② DVM offer better accuracy. in order of  $\pm 0.005\%$
- ④ The output of DVMs is available in digital form




- \* As such the reading speed of the user increases;
- \* Observational error (Parallax error) are almost eliminated
- \* Further processing (storage) is make possible.

Note: - Any DVM can not present value full context of the selected voltage range.

Que ① A  $4\frac{1}{2}$  DMM has the error specification of  $\pm 0.2\%$  reading  $\pm 10$  counts. If a dc voltage of 100 V is read on its 200 V full scale. The max error that can be expected in the reading.

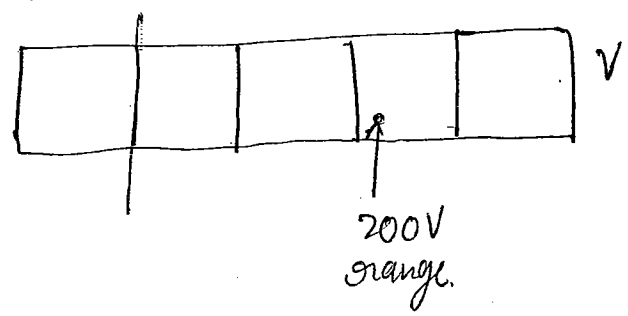- (a)  $\pm 0.1\%$
- (b)  $\pm 0.2\%$
- (c)  $\pm 0.3\%$
- (d)  $\pm 0.4\%$

Soln: -  $4\frac{1}{2}$  digit DMM, 0-200 V range  
 reading  $\Rightarrow 100$   
 Accuracy specification  $\Rightarrow 0.2\%$  of reading  $\pm 10$  count



$\Rightarrow$  reading 100.00  
 $\rightarrow$   $\pm$  count : 000.01 V

$$\Rightarrow 0.01V$$

Q91

$$\begin{aligned} \therefore \text{error} &= \frac{0.2}{100} \times 100V + (10 \times 0.01V) \\ &= 0.2 + 0.1 \\ &= 0.3V \end{aligned}$$

$$\begin{aligned} \% \text{ error} &= \pm \frac{0.3V}{100V} \times 100 \% \\ &= \pm 0.3\% \quad \underline{\text{Ans.}} \end{aligned}$$

Que:- A 4 digit DVM with 100 mV lowest full scale range could have a sensitivity of how much value by resolution of this DVM is 0.0001?

- (a) 0.1 mV    (b) 0.01 mV    (c) 1.0 mV    (d) 10 mV

Soln:- 4 digit dvm or DMM, lowest voltage range 100 mV  
resolution = 0.0001

$$\begin{aligned} S &= \frac{1}{10^4} \times 100mV = 0.001 \times 100mV \\ &= 0.01mV \end{aligned}$$

Que:- A digital voltmeter has a read out range from 0-9999 counts. the resolution of this instrument for full scale reading of 9.999 volts will be.

- (a) 10 ~~uV~~    (b) 1 mV    (c) 100 ~~uV~~    (d) 10 mV

$$\frac{1}{10^4} \times 9.999 = 0.9999V$$

$$\approx 1mV$$

Soln:- Given DVM has 4 digit

$$\begin{aligned} \text{FSR} &= \frac{9.999}{10V \text{ range}} \Rightarrow \text{resolution} = \frac{1}{10^4} \times 10V \\ &= \frac{1}{10^3} = 1mV \end{aligned}$$

Que:- A digit dual slope integrating type DVM reads in its 10 V range of operation is \_\_\_\_\_ ?

Soln:- resolution =  $\frac{1}{10^4} \times 10^V$   
 = 1 mV Ans


Que:- ~~A 4 1/2 digit~~ A DVM has 4 1/2 digit display. In 1 volt range can read upto

1.9999 V

Que A voltage 0.5245 V be displayed as \_\_\_\_\_ on 4 1/2 digit DVM in 10 volt range

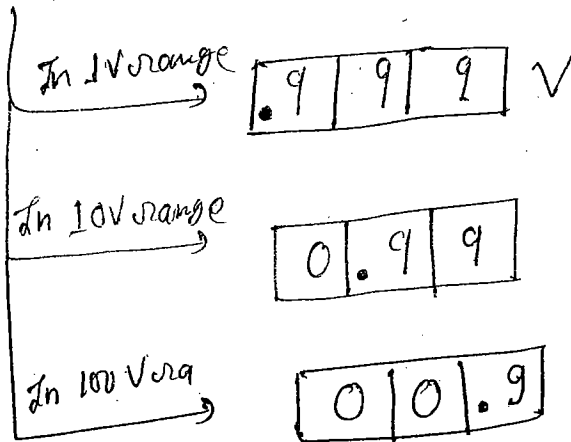0.524 V

Note:-  $V_m = 0.999$  V measured by 3 digit DVM displayed as



Que Over ranging in DVM implies that

- (a) all four digit are switched ON
- (b) 1/2 digit is switched ON
- (c) 1/2 digit is switched OFF
- (d) All full digit are switched OFF





Ques :- what is a range for a 4 1/2 digital meter (count range)

$0 = 1.9999$

Date  
09/08/2011

Multimeter :- A multimeter is used to measure dc voltage, AC voltage, dc current, ac current & resistance

required  
i/p  
interfaces

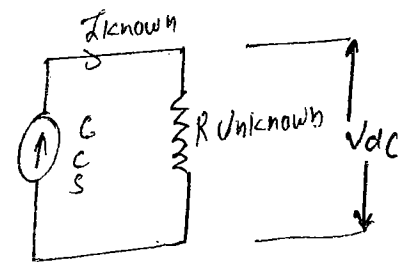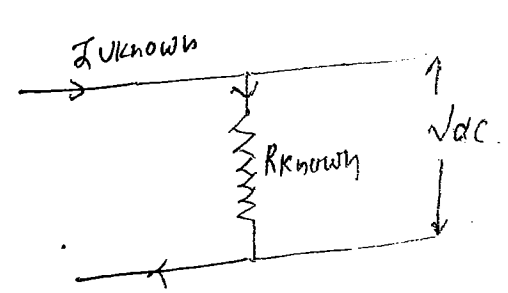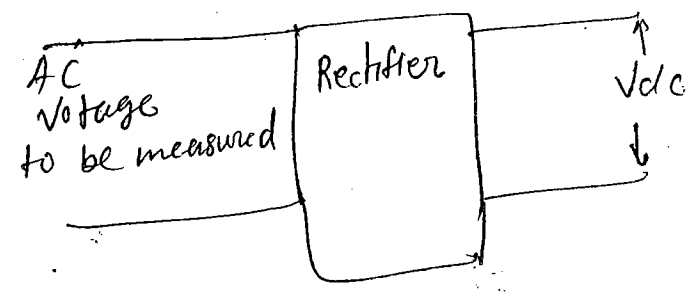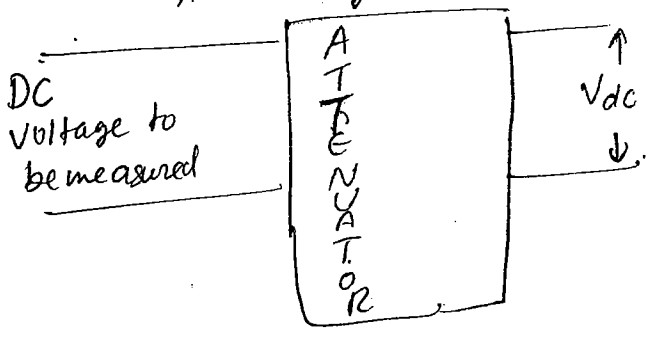

Note :-  
# EMM > VOM  
in terms of Rv  
& ~~SV~~ Sv

Multimeter

Analog Multimeter

Digital multimeter

Ordinary Multi


solid state Electronic Multi

Note: - # EMM > VOM in terms of  $R_v$  &  $S_v$




# Electronic voltmeter > VOM in terms of  $R_v$  &  $S_v$

\* Electronic voltmeter gives accurate or reliable measurement than ordinary multimeter

(X) Electronic Timer/Counter

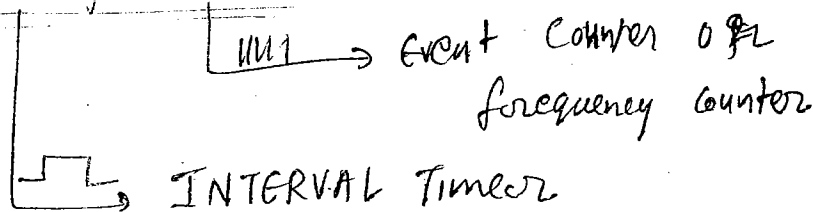

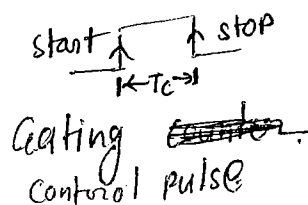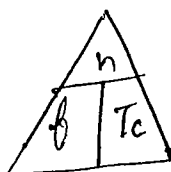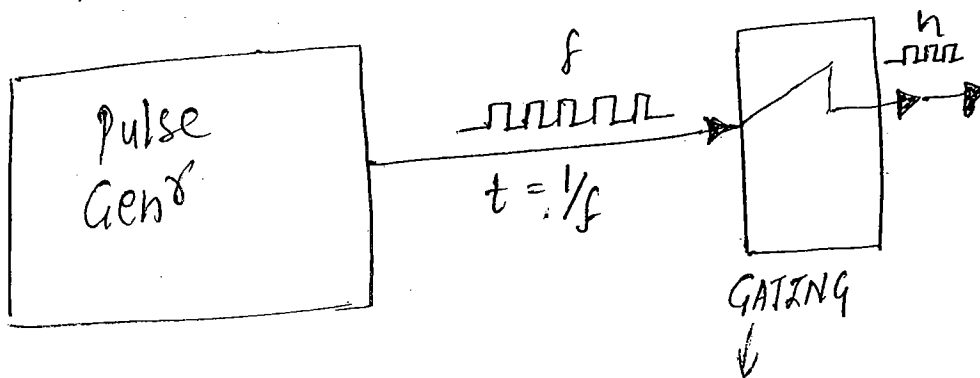\* This electronic measuring unit is used for measurement of unknown time period & unknown frequency



\* Unknown Time period measurement

$$T_c (\text{unknown}) = \frac{n}{f_{\text{known}}}$$

\* Unknown frequency measurement


$$f_{\text{unknown}} = \frac{n}{T_{\text{known}}}$$

Note: - \* For time period measurement it is operated in period mode whereas for frequency measurement it is operated at count mode

\* In digital frequency meter, additional i/p interface will be there like a ~~symmetrical~~ schmitt




Which converts i/p waveform into pulses.

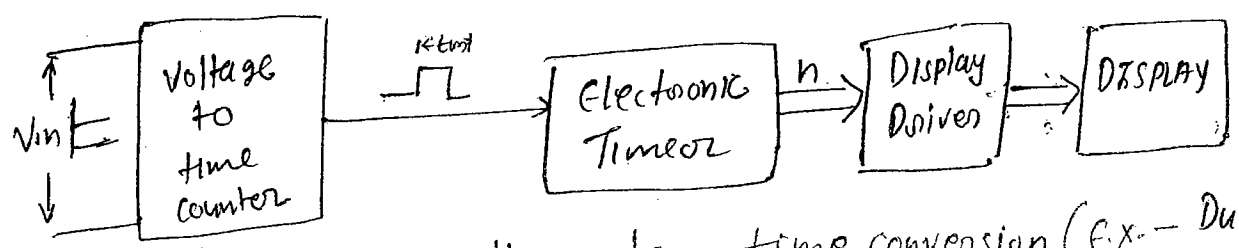

\* DVM based on voltage to time conversion (E.x. - Dual slope integrating type, Ramp type)

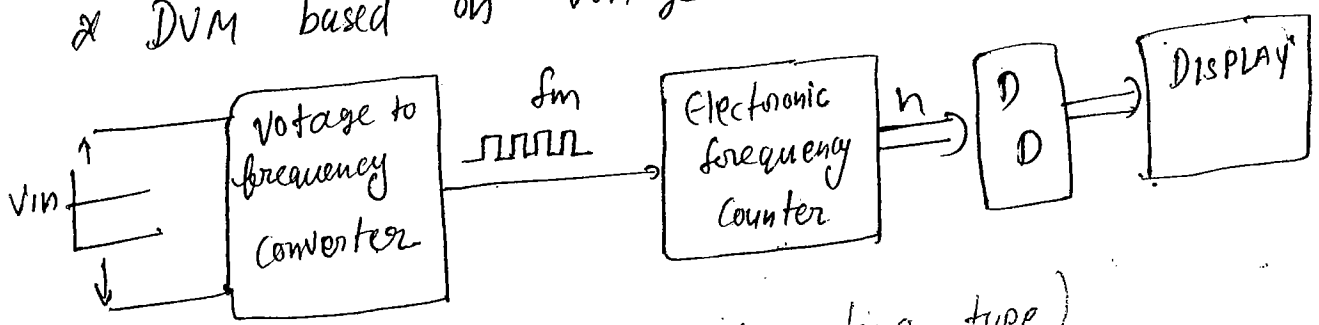\* DVM based on voltage to frequency conversion.



(Exs. :- single slope integrating type)



\* Most widely used ADC's is Dual slope integrating type


# C.R.O (CATHODE RAY OSCILLOSCOPE)

\* CRO is an electronic peak voltmeter which works for both ac & dc. There are two mode of operation for the CRO namely (a) Yt mode & (b) XY mode.

\* In Yt mode the test signal being sensed displayed on the screen known as Yt plot.

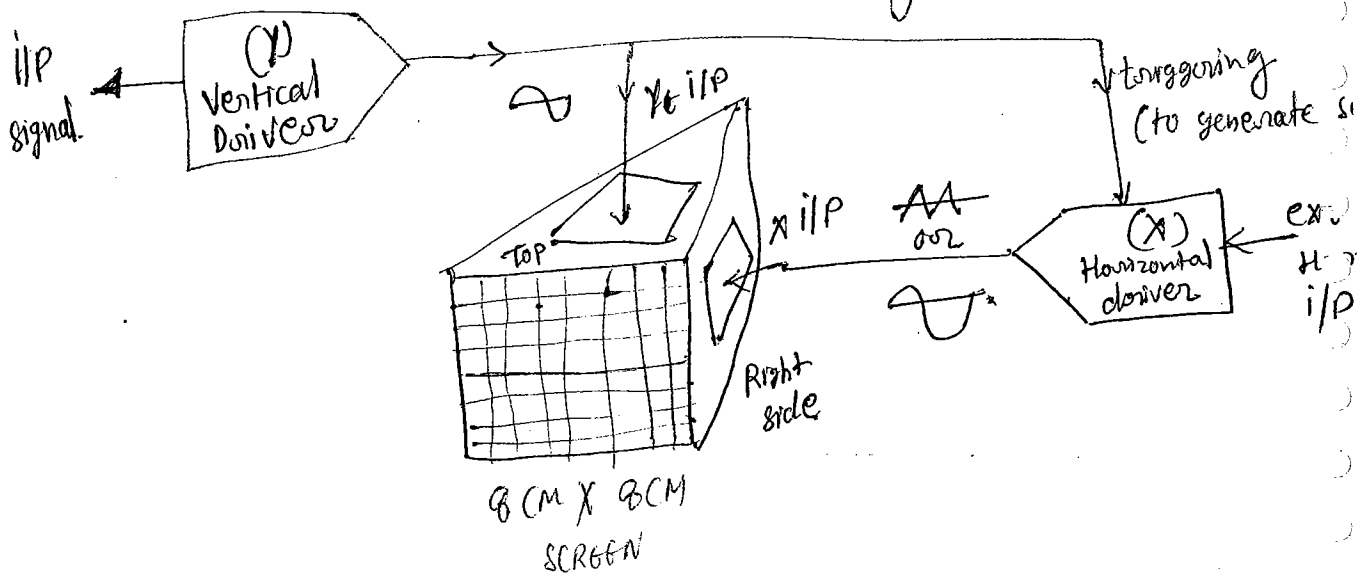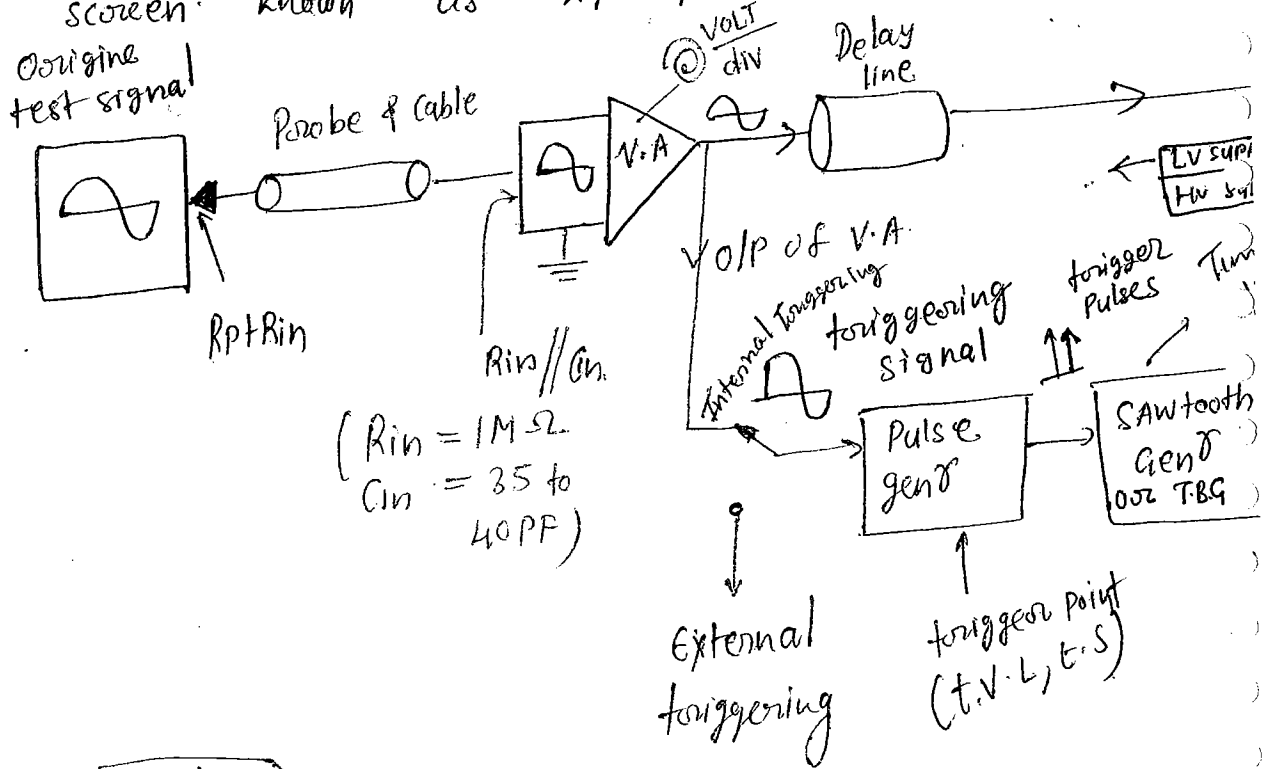\* In XY mode less obvious figure are displayed on screen known as XY plot.



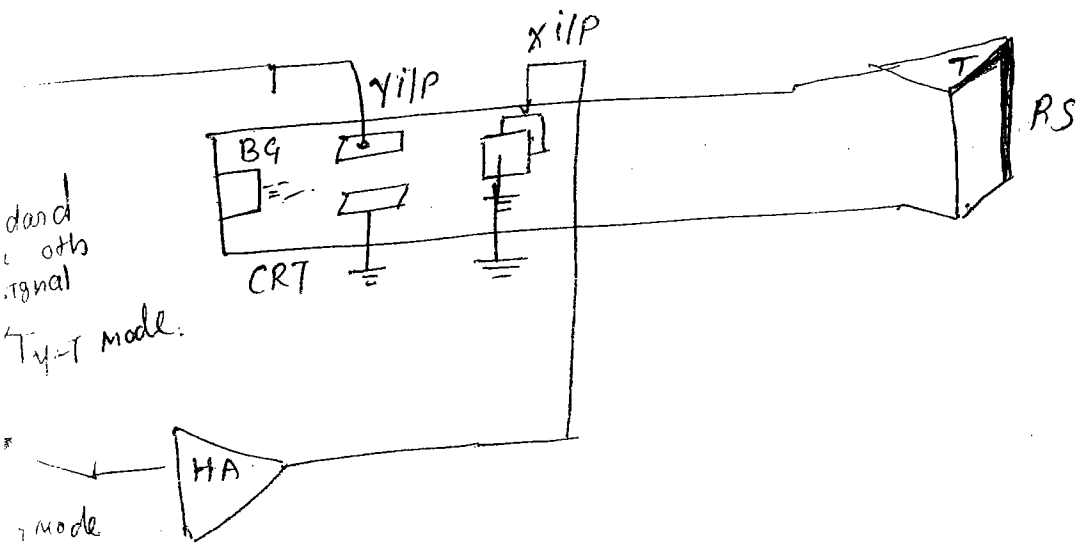

- \* The basic building block of CRO are vertical system, horizontal system, display system
- \* The vertical system provide a path for the test signal to reach Y input of CRT whereas the horizontal system provide a path for either internal generated sweep signal or externally applied ~~signal~~ any signal to reach X input of CRT.

\* CRT provide a path for electron beam generated at one end to reach its target (Fluorescent screen) on the further end. As such during this travel the cathode ray beam gets deflected because of Y input voltage & X input voltage interm a typical image will be displayed on the screen.

CRO = signal path + Horizontal-path +  $e^-$  beam in

\* The test signal is sensed using the probe of scope & then transmitted ~~to~~ to vertical terminal of a cable.

\* The vertical amplifier receives the test signal where it is either attenuated or amplified as the user adjust sensitivity control (VOLT/DIV)

\* Since vertical amplifier is receiving test signal most of the feature of CRO like i/p overstates bandwidth, rise time & gain are decided by vertical amplifier.

\* The i/p resistance of CRO will be range of MS

Note:- Gain  $\times$  Band width = k

risetime  $\times$  Bandwidth = 0.35

\* A delay line is inserted between the o/p of vertical amplifier ~~and~~ & Y input of CRT which delays test signal by a time amount slightly greater than horizontal time delay. As such horizontal signal reaches to X input prior to the test signal reaches to Y input.

3/10/11



In internal triggering the o/p of vertical amplifier is used as triggering signal.

The triggering ckt produces a trigger pulse whenever the triggering signal coincides the preselected triggering point (trigger voltage level, Trigger slope). The trigger pulses emitted by the pulse gen<sup>r</sup> are applied to time base gen<sup>r</sup> which generates sawtooth signal upon receiving each trigger pulse.



In Y-t mode the standard sweep signal is applied to the X<sub>in</sub> where as in X-Y mode any signal externally applied is driven to X<sub>in</sub>.

The sweep frequency can be adjusted by the user with the help of time per div control

Note:-

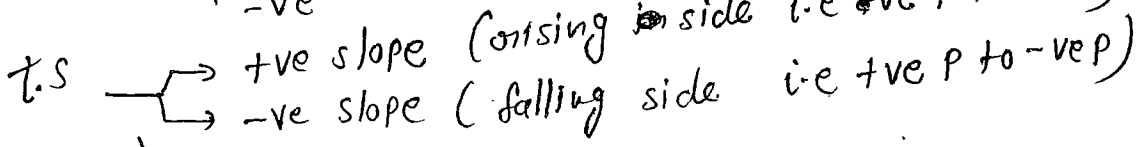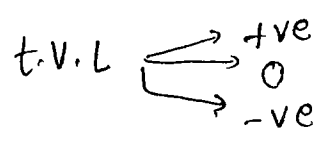

Eg:-

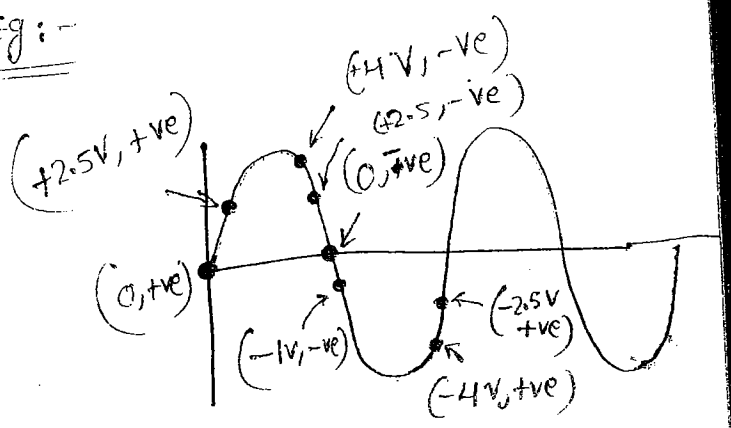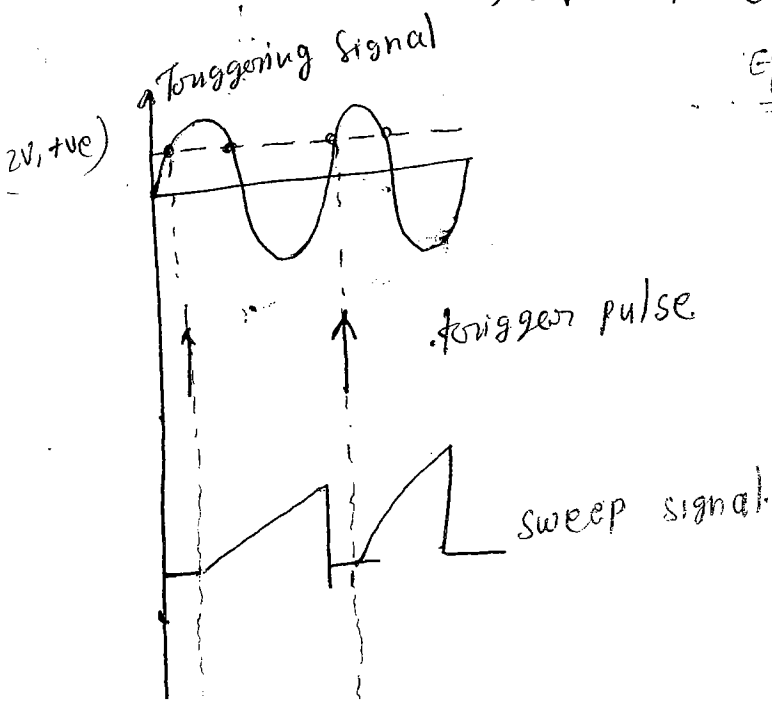


- \* CRT is an evacuated gas tube consisting being generated at one end & beam target at another end
- In the CRT cathode ray beam is generated, accelerated, focused in sharp beam, deflected due to  $y$  input &  $x$  input voltages & finally strikes fluorescent screen.


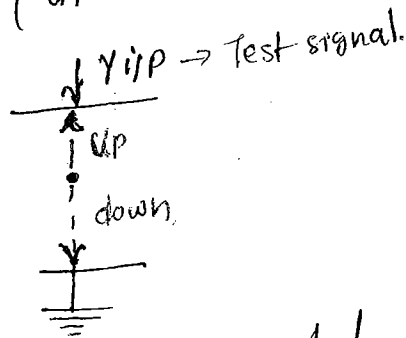
### \* Deflection plate Assembly:-

- \* A total no. of 4 plates are there existing as 2 plates namely V.D.P & H.D.P.

- \* The V.D.P. are horizontally mounted which deflect e<sup>-</sup> beam vertically (up-down direction)



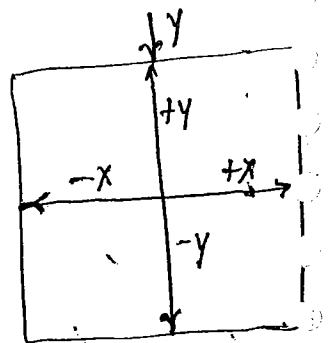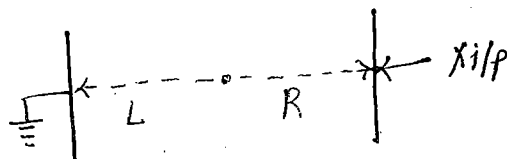- \* The H.D.P are vertically mounted which deflect the e<sup>-</sup> beam horizontally (right-left movement)



### \* Deflection sensitivity :- (S)

- \* The amount of deflection produced per unit voltage applied to corresponding deflection plate is known as deflection sensitivity.

\*  $S = \frac{\text{deflection}}{\text{voltage}}$  in  $\frac{\text{div}}{\text{volt}}$  or  $\frac{\text{cms}}{\text{volt}}$

\*  $S_v = \frac{y}{V_y}$  --- vertical deflection sensitivity

$S_H = \frac{x}{V_x}$  --- Horizontal deflection sensitivity

NOTE :-  $S_v = \frac{d}{V_d}$  → amount of distance travelling in screen  
 Deflection signal voltage (test signal)  
 $= \frac{L \cdot D}{25 V_a}$

- L = Length of each VDP
- D = Distance between VDPS & screen
- s = separation distance between both VDPS
- V<sub>a</sub> = anode voltage (accelerating anode)



⊛ Deflection Factor :-

\* it is reciprocal of sensitivity  
 $D_f = 1/S$  in volts/div. or volts/cm

NOTE :- S → How many div for unit volt.  
 D<sub>f</sub> → How many volts for 1 div deflection.

\* Amount of Deflection = Deflection sensitivity × Applied voltage

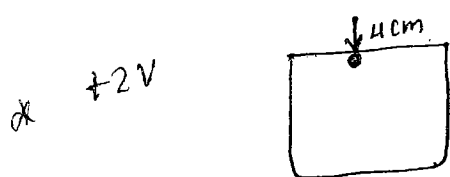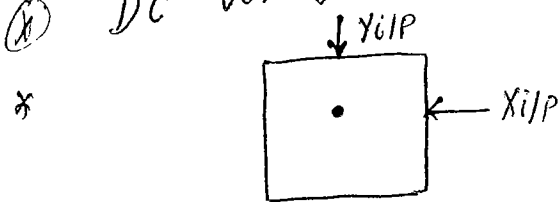
⊛ DC voltages to X<sub>i/p</sub> & Y<sub>i/p</sub>




$V_y = +2V$  ,  $S_v = 2 \text{ cm/V}$

∴  $y = S_v \times V_y$   
 $= 2 \frac{\text{cm}}{\text{V}} \times (+2V)$

$= 4 \text{ cm}$

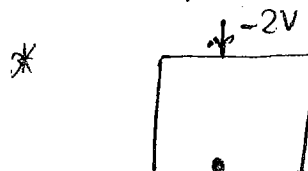

\*

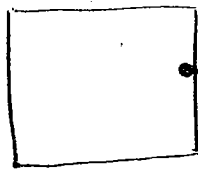


$$V_H = +2V$$


$$S_H = 2cm/V$$

$$x_c = 4cm$$


\*

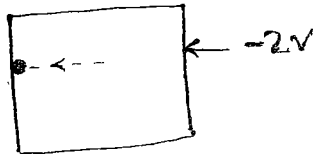


\*

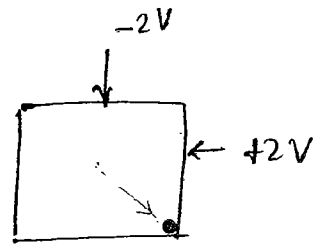


\*

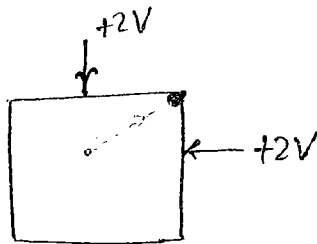


\*

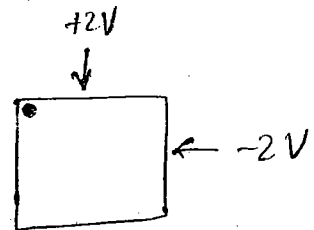


\*

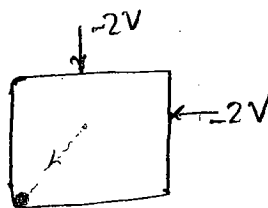


\*

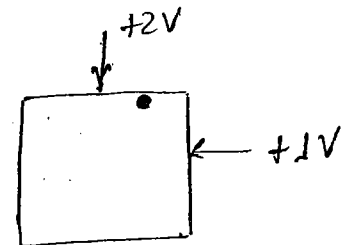

\*

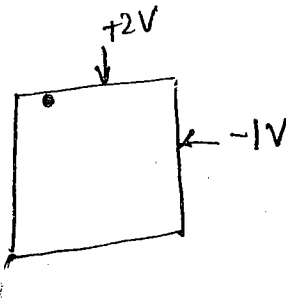

\*

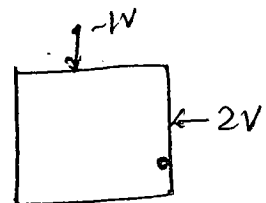




Test signal to the Y-input :- (sense signal) an

Consider a sinusoidal signal is sensed using probe of slope & driven to Y-inputs


$$SV = \frac{2cm}{V}$$

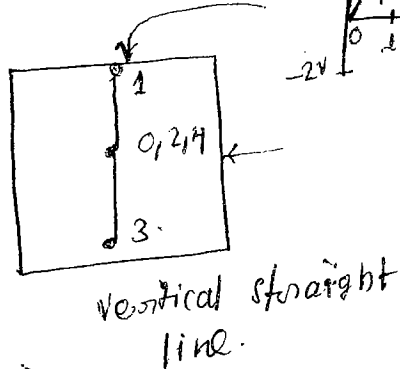- $t_0 \rightarrow$  center
- $t_1 \rightarrow$  Top
- $t_2 \rightarrow$  Center
- $t_3 \rightarrow$  Bottom
- $t_4 \rightarrow$  center




Standard sweep signal to X-inputs :-

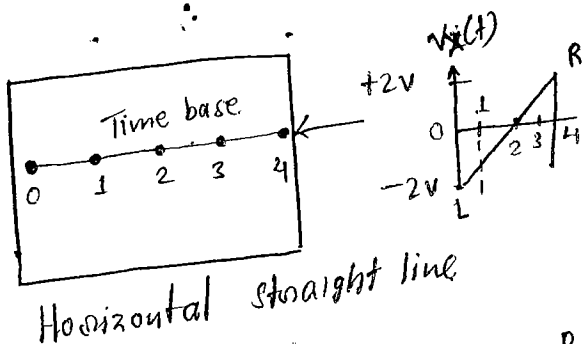- $t_0 \rightarrow -2V$
- $t_1 \rightarrow -1V$
- $t_2 \rightarrow 0V$
- $t_3 \rightarrow +1V$
- $t_4 \rightarrow +2V$



$$SH = \frac{2cm}{V}$$

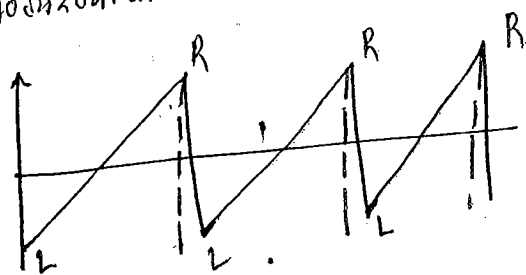

standard sweep

L to R : trace  
R to L : retrace  
or flyback

Due to the sweep voltage applied X-input the  $e^-$  beam (spot on the screen) is swept across the screen of the CRO

Eg. - Total horizontal div = 10

$$\frac{\text{Time}}{\text{div}} = 10 \frac{\mu s}{cm}$$

$$T_{\text{sweep}} = 10 \text{ cm} \times 10 \frac{\mu s}{cm} = 100 \mu \text{sec}$$

$$T_{\text{sweep}} = \text{Total No. of Horizontal} \times \frac{\text{Time}}{\text{div}}$$



$$f_{\text{sweep}} = \frac{1}{T_{\text{sweep}}}$$

⊗ External signal to X i/p ⇒







\* In X-Y mode any signal can be applied to x i/p's via external Horizontal input.


Consider a sinusoidal signal is externally applied

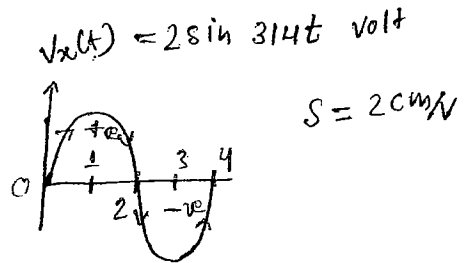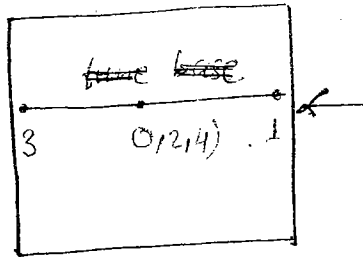- $t_0 \rightarrow 0V$
- $t_1 \rightarrow +2V$
- $t_2 \rightarrow 0V$
- $t_3 \rightarrow -2V$
- $t_4 \rightarrow 0V$



Horizontal straight line

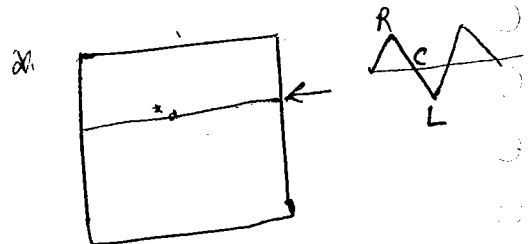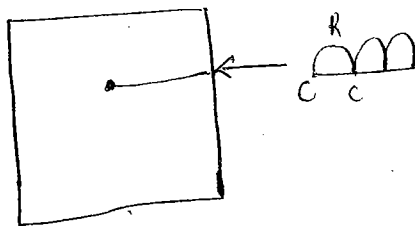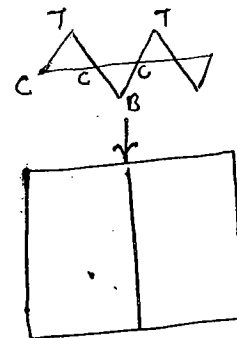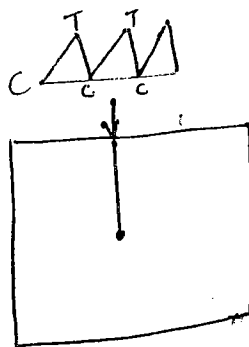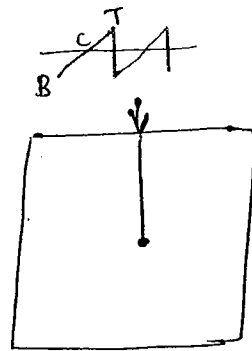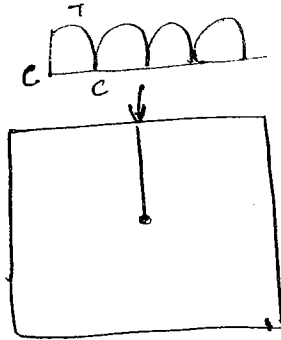

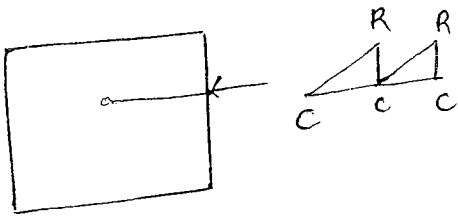


Y-t MODE OF operation ⇒

In y-t mode the sensed test signal is applied to Y i/p & standard sweep signal (internally generated) is applied to X i/p

$$t_{\text{signal}} = t_{\text{sweep}}$$

Time/div.

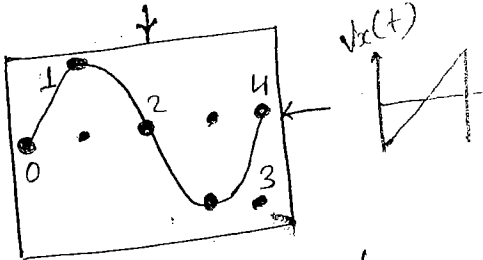- 1 → (-2V, 0V)
- 2 → (-1V, +2V)
- 3 → (0V, 0V)
- 4 → (+1V, -2V)
- 5 → (+2V, 0V)



\* Amplitude variation of Y i/p signal is displayed on screen w.r.t 't'

$$\text{i.e. Y-t plot}$$

(\*) Measurement using Y-t plot

(1) Peak to Peak voltage measurement

$$V_{PP} = N_v \times \frac{\text{VOLT}}{\text{div.}}$$

where  $V_{PP}$  = Peak to peak amplitude of test signal displayed

$N_v$  = No. of vertical divisions between peak to peak points of signal displayed.

$\frac{\text{VOLT}}{\text{div.}}$  = Y-sensitivity setting or Gain setting or Vertical setting

(2) Amplitude measurement (i.e. peak voltage)

$$V_p = \frac{V_{P-P}}{2}$$

- (3) RMS & dc voltage measurement :-  
 (4) Signal Timeperiod measurement

$$T = N_H \times \frac{\text{Time}}{\text{div}}$$

where -  $T$  = test signal timeperiod

$N_H$  = No. of Horizontal division occupied by one cycle. of test signal displayed.

Time/div = X sensitivity setting or Horizontal setting or sweep setting or time base setting or scale setting or line setting


- (5) frequency measurement :-

$$f_{\text{signal}} = \frac{1}{T_{\text{signal}}}$$


- (\*)  $f_{\text{signal}}$  vs  $f_{\text{sweep}}$  :-

what ever with the position of test signal during linear rise of sweep signal will be displayed on the screen.

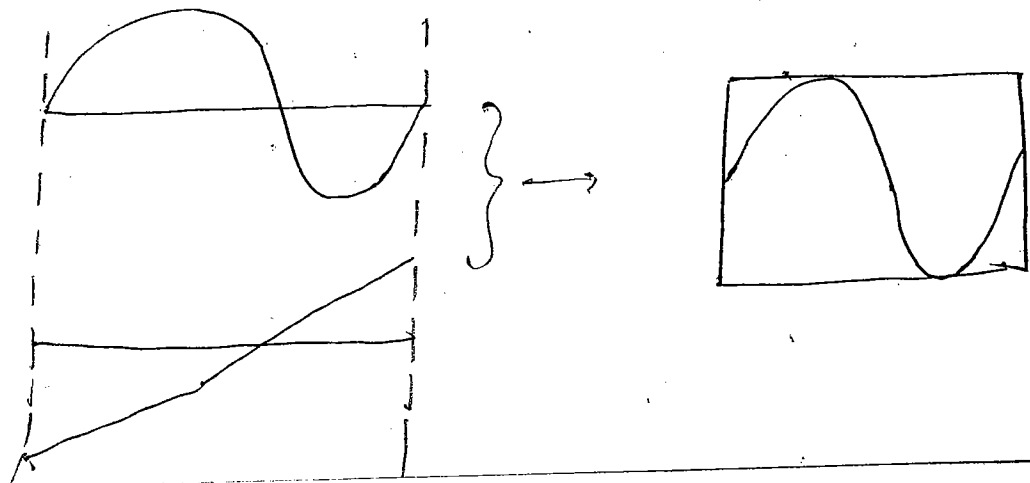
- (1)  $f_{\text{signal}} = F_{\text{sweep}} \rightarrow$  1 cycle of signals is displayed



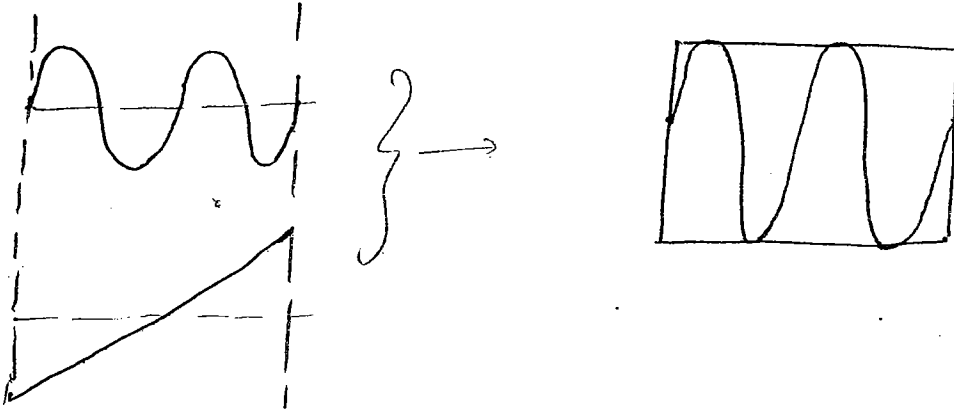$f_{\text{signal}} > f_{\text{sweep}} \rightarrow$  A No. of cycles of signal displayed



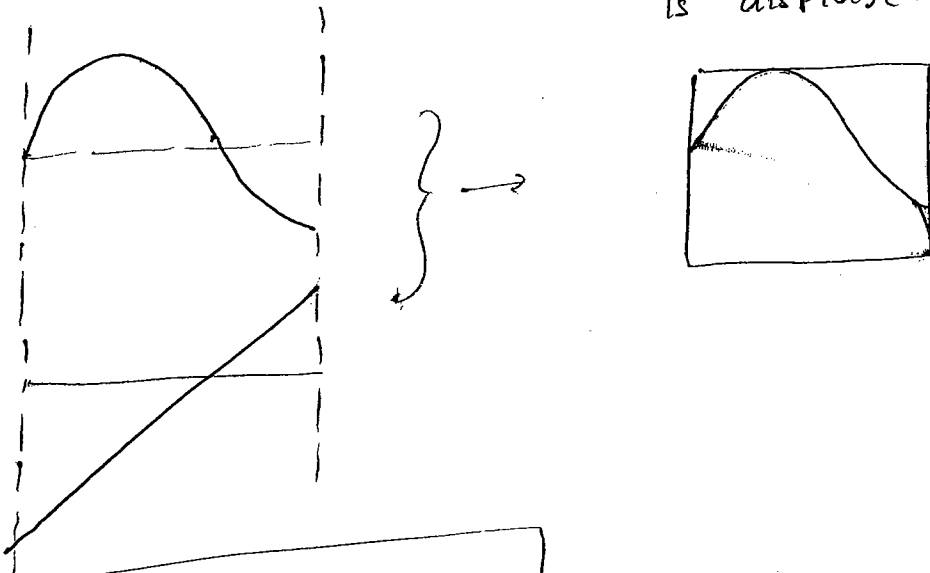$f_{\text{signal}} < f_{\text{sweep}} \rightarrow$  less than 1 cycle of signal is displayed



\*  $f_{\text{signal}} \geq f_{\text{sweep}}$

i.e. min<sup>m</sup> signal frequency = sweep frequency

\*  $f_{\text{signal}} = n f_{\text{sweep}}$

where  $n \geq 1$

$n =$  no. of cycles of signal displayed


\*  $n = \frac{f_{\text{signal}}}{f_{\text{sweep}}}$

\*  $n = \frac{T_{\text{sweep}}}{T_{\text{signal}}}$

Date  
28/10/11
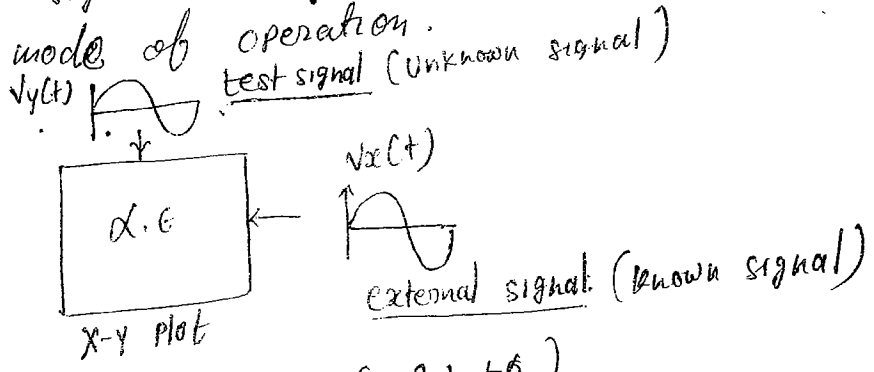
## X-Y mode of operation

\* If sensed tested signal is driven for y-inputs & external horizontal signal is driven for x-inputs then it is known as X-Y mode of operation.




$$V_y(t) = V_y \sin(2\pi f_y t + \phi)$$


$$V_x(t) = V_x \sin(2\pi f_x t)$$

where  $V_y$  &  $V_x$  are amplitudes  
 $f_y$  &  $f_x$  are vertical & horizontal frequencies  
 $\phi$  = phase difference

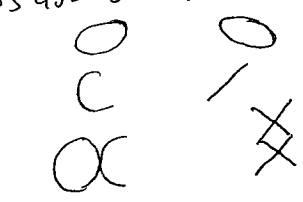3 types of L.F.S. (Lissajous figure signal)  
 Closed loop L.F.S.  
 Open loop L.F.S.  
 Mixed / Hybrid L.F.S.




Note:-

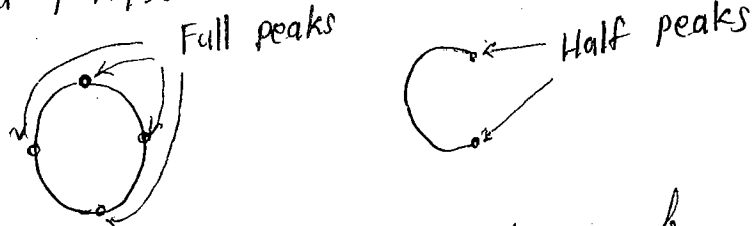

\* Use in Lissajous figure two types of measurement can be carried out namely unknown frequency measurement & phase measurement

### Frequency measurement using Lissajous figure:

Tangent method  
 Eg:

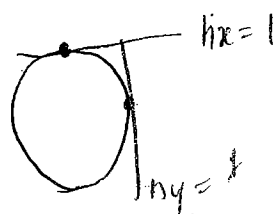

$$f_y/f_x = 1/1$$


$$f_y:f_x = 1:1 \text{ (Vertical \& Horizontal frequency ratio)}$$

## Tangent Method

Draw vertical & Horizontal both tangent line to the L.F. touching Peaks

$$f_y = f_x \times \frac{n_x}{n_y}$$

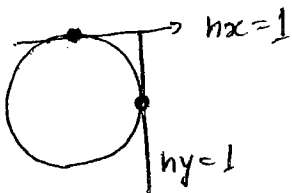where  $n_x$  = no. of peaks as touch by Horizontal tangent line  
 $n_y$  = no. of peaks as touch by vertical tangent line



$$\therefore f_y / f_x = 1/1$$

$$\text{If } f_x = 1 \text{ KHz}$$

$$\text{then } f_y = 1 \text{ KHz} \times 1 = 1 \text{ KHz}$$

## Intersection method


ab

\* Draw both vertical & Horizontal line passing through the L.F.

Rule: Never draw a line via pre-existing intersection.

$$f_y = f_x \times \frac{n_x}{n_y}$$

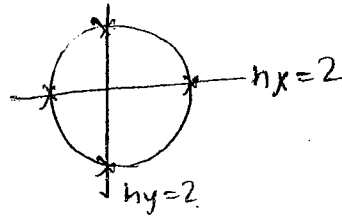where  $n_x$  = no. of cuts as made by horizontal line  
 $n_y$  = no. of cuts as made by vertical line



$$\therefore \frac{f_y}{f_x} = \frac{2}{2} = \frac{1}{1}$$

$$\text{If } f_x = 1 \text{ KHz}$$

$$\text{then } f_y = 1 \text{ KHz} \times 1 = 1 \text{ KHz}$$

## Case 2) Phase measurement using L.F. :-

Condition :- Equal amplitude :-  $V_y = V_x = V$

Equal frequency :-  $\omega_y = \omega_x = \omega$   
 or  $f_y = f_x = f$

Equal sensitivities :-  $S_V = S_H = S$





i.e. 2 sinusoidal signal having same amplitude & frequency are applied to Y & X i/p

$$V_y(t) = V \sin(2\pi ft + \phi)$$

$$V_x(t) = V \sin(2\pi ft)$$

Case 1)  $\phi = 0^\circ$  or  $360^\circ$

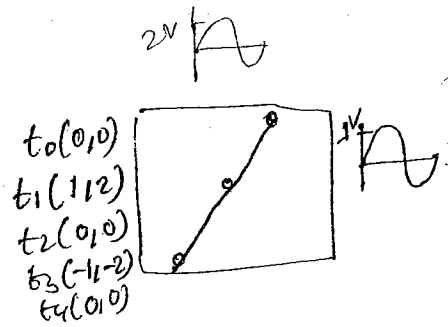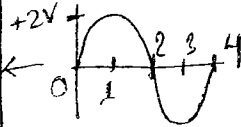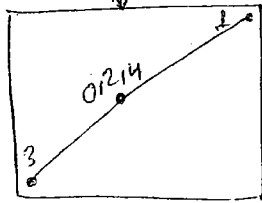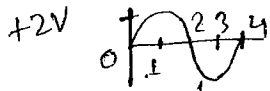- $v_x, v_y$
- $t_0(0,0)$
  - $t_1(+2V, +2V)$
  - $t_2(0,0)$
  - $t_3(-2V, -2V)$
  - $t_4(0,0)$




It is diagonal straight line making  $45^\circ$  from with +ve x axis.

In - PHASE

$$\phi = 0^\circ \text{ or } 360^\circ$$


Note :- ① \*  $f_y = f_x$ ,  $\phi = 0^\circ$  or  $360^\circ$  no change  
Slope exactly  $45^\circ$

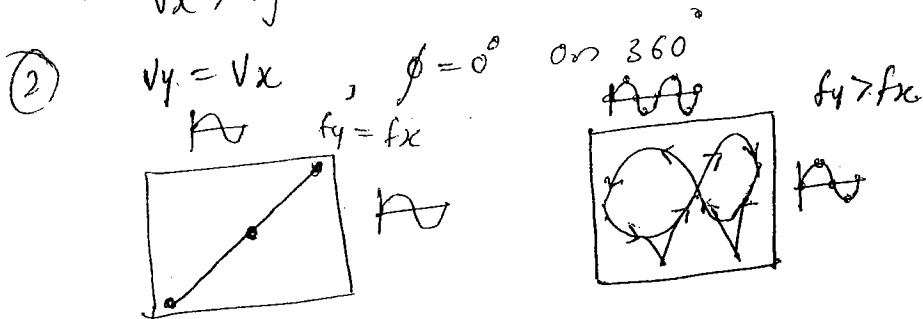- \*  $v_y > v_x$  then slope is greater than  $45^\circ$
- \*  $v_x > v_y$  then slope is less than  $45^\circ$



Case ②  $\phi = 180^\circ$

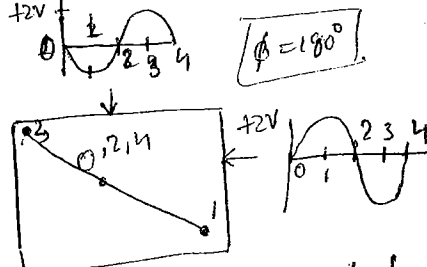
- $v_x, v_y$
- $t_0(0,0)$
  - $t_1(+2, -2)$
  - $t_2(0,0)$
  - $t_3(-2, +2)$
  - $t_4(0,0)$



A diagonal straight line making  $135^\circ$  with +ve x axis

Conclusion w.r.t case ① & case ②



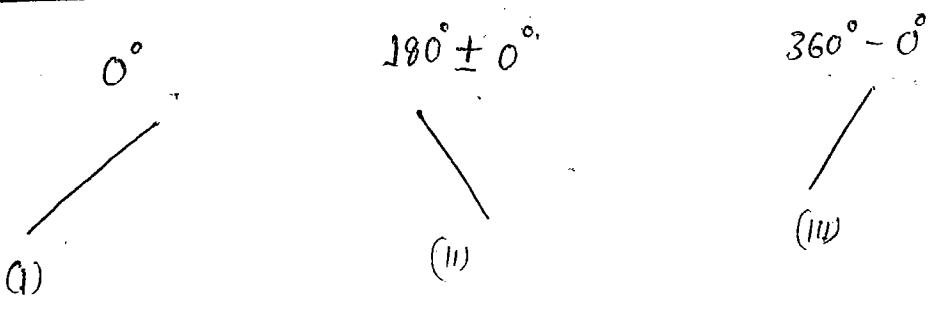


$0^\circ$  minor figure is  $180^\circ \pm 0^\circ$

L.F.  $[\phi]$  & L.F.  $[360^\circ - \phi]$  are same figure

L.F.  $[\phi]$  & L.F.  $[180^\circ \pm \phi]$  are minor

Ex: If L.F. for  $30^\circ$  is known then L.F. for  $360^\circ - 30^\circ$  i.e.  $330^\circ$  will be same

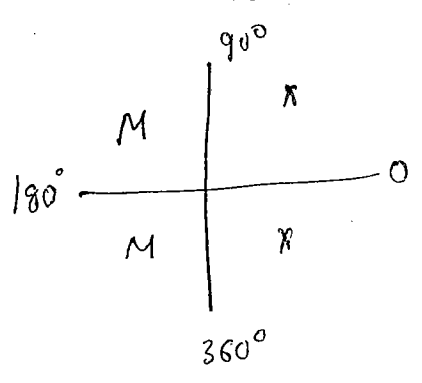& L.F. for  $180^\circ - 30^\circ$  i.e.  $150^\circ$  &  $180^\circ + 30^\circ$  i.e.  $210^\circ$  will be minor





$0^\circ - 180^\circ \rightarrow$  clockwise  
 $180^\circ - 360^\circ \rightarrow$  anticlockwise

Case 3

$\phi = 90^\circ$

$\phi = 270^\circ$  Circle Anticlockwise

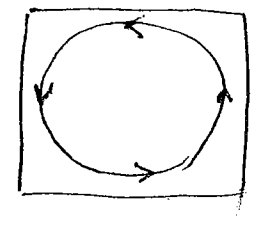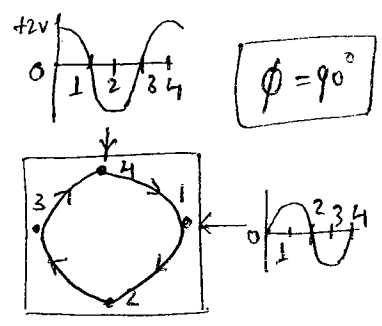- to  $(2, 0)$
- t1  $(0, 2)$
- t2  $(-2, 0)$
- t3  $(0, -2)$
- t4  $(2, 0)$




Circle & it is clockwise rotating

Note:- If  $\phi = 90^\circ$  circle is observed  
 circle is displayed repeated.  
 $f_y = f_x, \phi = 90^\circ$   
 $360^\circ - 90^\circ = 270^\circ$


at  $\phi = 90^\circ$

$$v_y = v_x$$

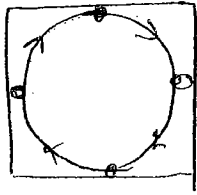


Circle.

$$v_y > v_x$$

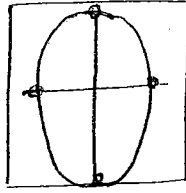


Ellipse with  
y-axis as  
major axis

$$v_x > v_y$$

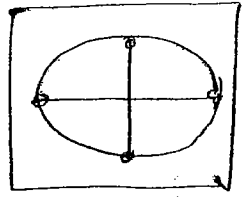

Ellipse with  
x-axis as  
major axis

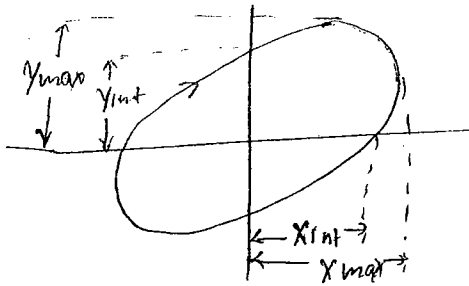
\* Except for  $0^\circ, 90^\circ, 180^\circ, 270^\circ, 360^\circ$  an ellipse will be observed for any other phase difference.



$$\phi = \sin^{-1} \left[ \frac{y_{int}}{y_{max}} \right]$$

or
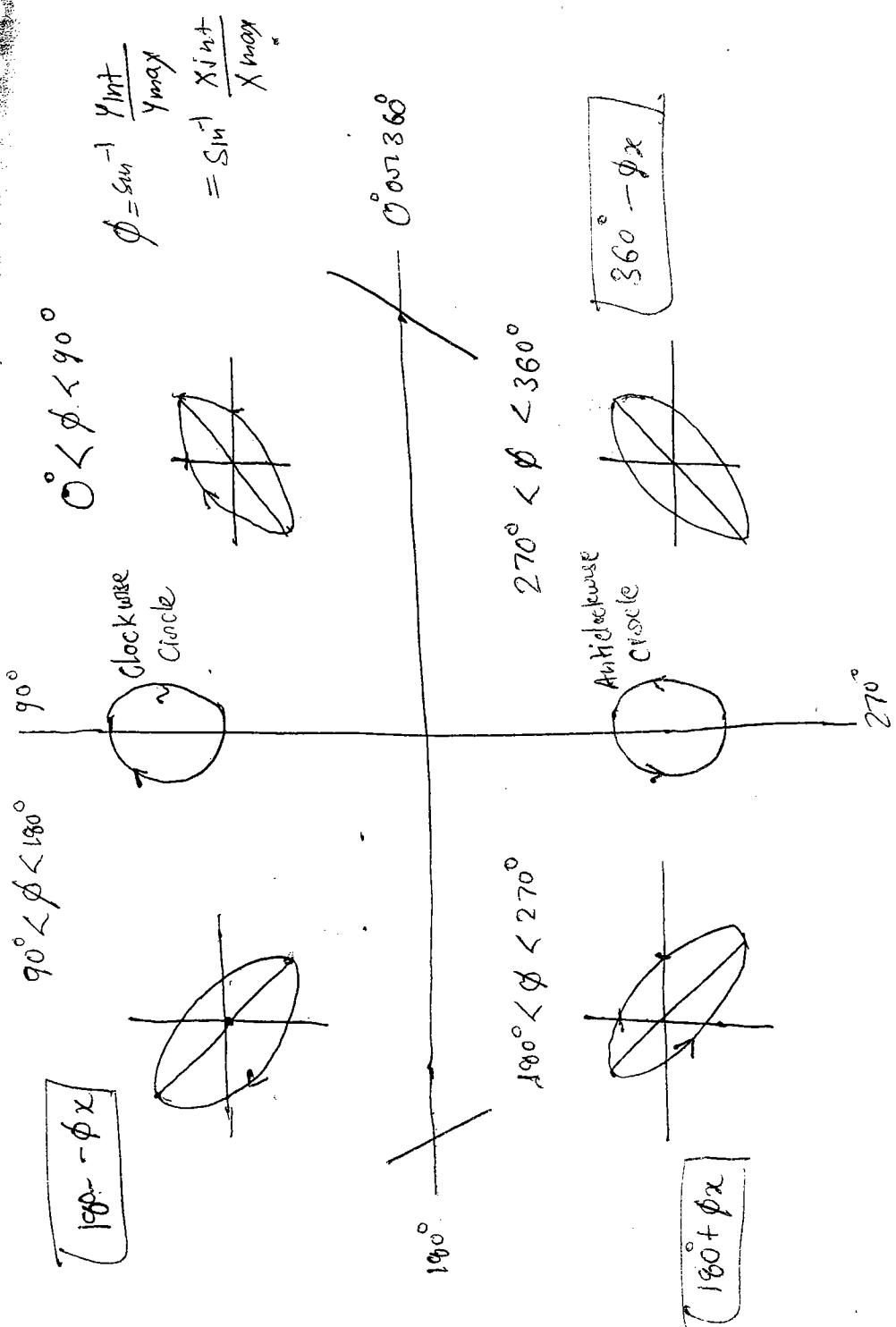
$$\phi = \sin^{-1} \left[ \frac{x_{int}}{x_{max}} \right]$$



Date  
24/08/11

Ques:- If the bandwidth of oscilloscope is given as DC to 10 MHz. What is the fastest rise time time a sine wave can have to be produce accurately by the oscilloscope.

Soln:- for any amplifier for  $k \times B.W. = 0.35$

$$\therefore t_r = 0.35 \\ = 0.035 \mu s \\ = 35 \text{ nsec}$$

Note:- B.W. of CRO = 20 MHz


$$t_r = \frac{0.35}{20 \text{ MHz}} = 17.5 \text{ ns}$$

Ques:- The relationship between  $T_s$  (rise time of signal),  $T_o$  (rise time of oscilloscope) is  $T_o$  (rise time of signal observed) is equal to \_\_\_\_\_



- (a)  $T_s + T_o$     (b)  $\sqrt{T_s^2 + T_o^2}$     (c)  $\sqrt{T_s^2 - T_o^2}$     (d)  $T_s - T_o$

$T_s$  = Actual or true rise time of signal

Amplifier Under Test

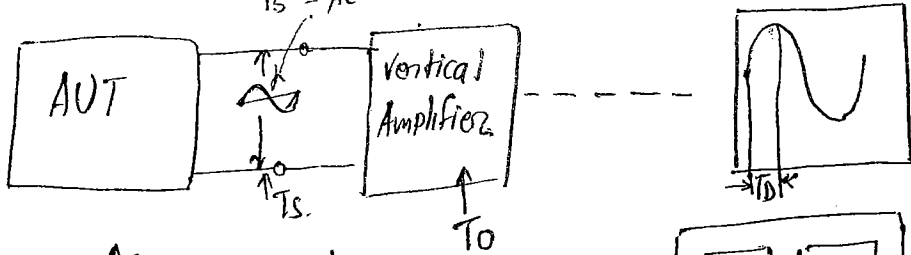

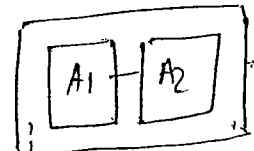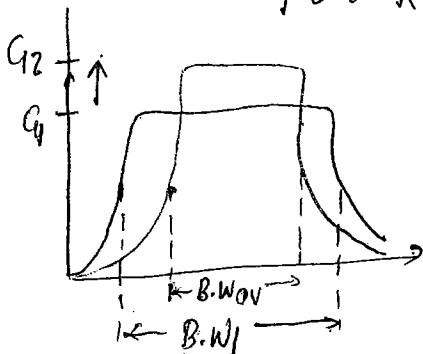Note:-  $\text{Gain} \times \text{B.W.} = k$   
 $\uparrow t_r \times \text{B.W.} = 0.35$



→ overall gain =  $G_1 G_2$

→ overall rise time =  $\sqrt{t_{r1}^2 + t_{r2}^2}$

→ overall bandwidth =  $\frac{0.35}{\sqrt{t_{r1}^2 + t_{r2}^2}}$

$T_s$  = Actual or true rise time of signal  
 $T_o$  = CRO rise time or VA rise time  
 $T_D$  = Detected rise time (Overall rise time)  
 (measure rise time)

Q5

Q:- A CRO with a rise time of 15 ns measure the rise time of a signal ~~is~~ 20 ns. Then actual rise of the signal is

Sol<sup>n</sup>:-  $T_o = 15\text{ns}$  (rise time of vertical Amplifier)  
 $T_D = 20\text{ nsec}$  (rise time by measured)


$$T_D = \sqrt{T_s^2 + T_o^2}$$

$$T_s = \sqrt{T_D^2 - T_o^2}$$

$$T_s = \sqrt{(20)^2 - (15)^2} = \sqrt{400 - 225}$$

$$T_s = 13.23\text{ns}$$

Q:- One cycle of square wave signal is observed on the screen of an oscilloscope is found to occupy 6 cm. at a scale setting of 30  $\mu\text{sec/cm}$ . What is signal frequency.

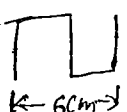Sol<sup>n</sup>:-   $\frac{\text{Time}}{\text{div}} = 30 \frac{\mu\text{s}}{\text{cm}}$

$$\begin{aligned}
 T &= NH \times \frac{\text{Time}}{\text{div}} \\
 &= 6\text{cm} \times 30 \frac{\mu\text{s}}{\text{cm}} = 180\mu\text{s}
 \end{aligned}$$

$$f_{\text{square}} = \frac{1}{180\mu\text{s}} = 5.55\text{kHz}$$

Q:- A symmetrical square wave of frequency 25 kHz & peak to peak amplitude of 10V is fed to YIP of an oscilloscope. The screen appears as shown in below figure



then X, Y sensitivity is

Sol<sup>n</sup>:-

Given data

$$V_{PP} = 10V$$

$$f = 25KHz$$

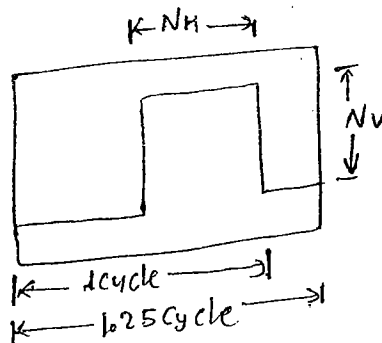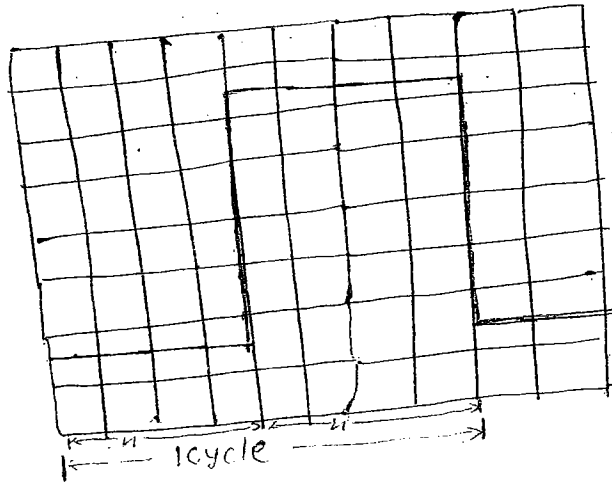

$$N_H = 8$$

$$N_V = 5$$

$$T = N_H \times \frac{\text{Time}}{\text{div}}$$

$$= 8 \times \frac{1}{25}$$

$$\frac{\text{Time}}{\text{div}} = \frac{T}{N_H} = \frac{1}{f \times N_H}$$

$$= \frac{1}{25 \times 8} = \frac{1}{200} = 5 \mu\text{s}/\text{div}$$

$$V_{PP} = N_V \times \frac{\text{VOLT}}{\text{div}}$$


$$\frac{\text{VOLT}}{\text{div}} = \frac{V_{PP}}{N_V} = \frac{10V}{5 \text{ div}}$$

$$= 2V/\text{div}$$

Gate 2006 Ans:- 2V/div & 5 μsec/div


Que - A student connect 1KHz, 5 Vp-p square wave calibration pulse to channel of the scope & observed the screen to be as shown in up trace of the figure & unknown

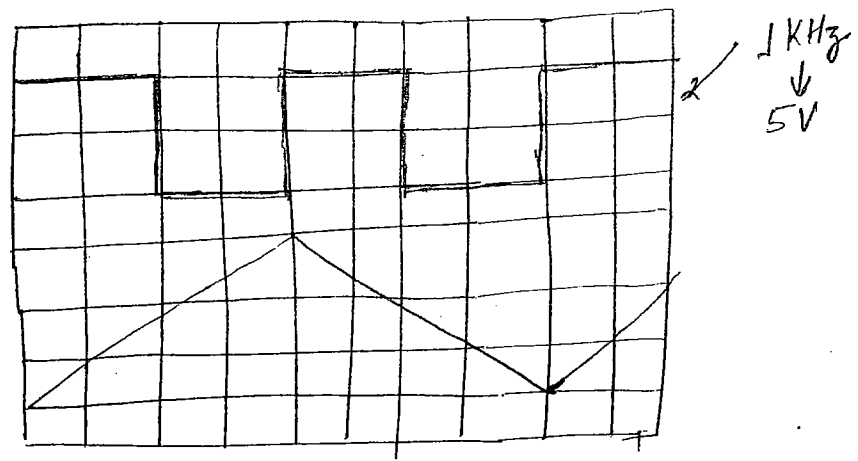Signal is connected to ~~say~~ channel 2 at the scope. produces the lower trace if the time per div. & volt per div of both channel is same then peak to peak amplitude & period of the unknown signal are respectively -----



Note - CRO that consist two vertical channel but only one electron gun is there.

Soln - channel-1 display

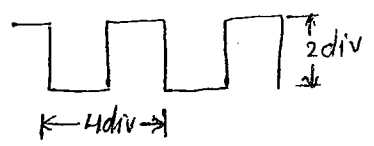

$$f = 1 \text{ KHz}$$

$$V_{pp} = 5 \text{ V}$$


We know :

$$V_{pp} = N_v \times \frac{\text{VOLT}}{\text{div.}}$$

$$5 = 2 \times \frac{\text{VOLT}}{\text{div.}}$$

$$\frac{\text{VOLT}}{\text{div}} = \frac{5}{2} = 2.5$$

Channel-2 display

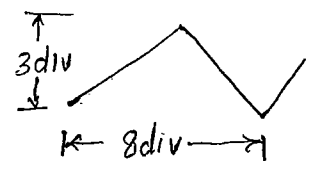

$$V_{pp} = N_p \times \frac{\text{VOLT}}{\text{DIV}}$$

$$V_{pp} = 3 \times 2.5 \frac{\text{V}}{\text{div}}$$

$$= 7.5 \text{ V}$$

$$T = N_H \times \frac{\text{Time}}{\text{div.}}$$

$$\therefore \frac{\text{Time}}{\text{div}} = \frac{T}{N_H}$$

$$= \frac{1}{1 \text{ KHz} \times 4 \text{ divs}}$$

$$= \frac{1 \text{ msec}}{4 \text{ divs}}$$

$$= 0.25 \text{ msec/div}$$

Ans

$$T = 8 \text{ div} \times 0.25 \text{ ms/div.}$$

$$= 2 \text{ ms} \quad \underline{\text{Ans}}$$

Ques. - The CRO screen has 10 div on horizontal squares if a voltage signal  $5 \sin(314t + 45^\circ)$  is examined with a time base setting of 5 msec/div. then the no. of cycle of signal displayed on the screen will be - - -

- (a) 2      (b) 2.5      (c) 4      (d) 4.5

Soln. - ~~Given~~ signal frequency  $\geq f_{\text{sweep}}$ .

$$n = \frac{f_{\text{signal}}}{f_{\text{sweep}}}$$

$$= \frac{T_{\text{sweep}}}{T_{\text{signal}}}$$

$$N_y(t) = 5 \sin(314t + 45^\circ)$$

$$= \frac{\text{Total NH}}{T_{\text{ms/div}}}$$

$$\text{Sweep time periode} = \text{Total NH} \times \text{TIME/div}$$

$$= 10 \text{ divs} \times 5 \text{ ms/div}$$

$$= 50 \text{ ms}$$

Given that  $f_{\text{signal}} = 50 \text{ Hz}$

$$\therefore T_{\text{signal}} = \frac{1}{50 \text{ Hz}}$$

$$= 20 \text{ msecs}$$

$$n_g = \frac{50 \text{ msec}}{20 \text{ msec}} = 2.5 \text{ msec}$$



OA

$$T = N_H \times \frac{\text{Time}}{\text{div}}$$

$$20 = N_H \times \frac{5 \text{ ms}}{\text{div}}$$

$$N_H = \frac{20 \text{ ms}}{5 \text{ ms}} \text{ divs} = 4 \text{ divs} = 1 \text{ cycle}$$


4 div — 1 cycle

$$10 \text{ div} - ? = \frac{10 \text{ div} \times 1 \text{ msec}}{4 \text{ div}}$$

Gate 2004

$$= 2.5 \text{ m sec}$$

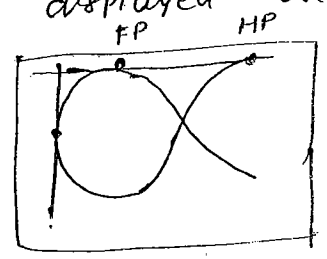Ques:- A CRO is operated in XY mode the below given L.F. sig. displayed on the screen




$$n_x = 1 + \frac{1}{2} = \frac{3}{2}$$

$$n_y = 1$$



Then the Horizontal to vertical frequency ratio is ---  
 (a) 1:3      (b) 2:3      (c) 3:2      (d) 3:1

$$\frac{f_y}{f_x} = \frac{N_x}{N_y}, \quad \frac{f_x}{f_y} = \frac{N_y}{N_x}$$

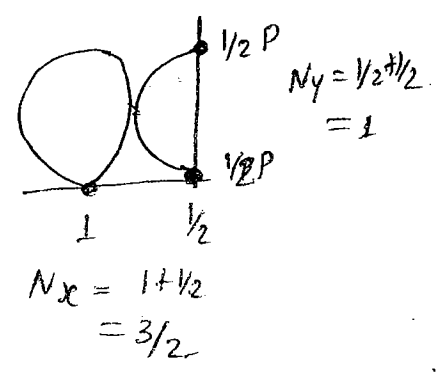
$$\frac{f_x}{f_y} = \frac{1}{3/2} = \frac{2}{3}$$


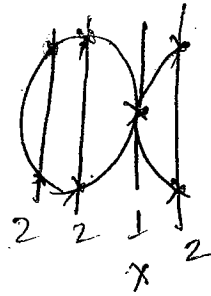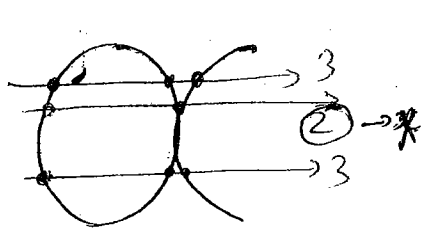
$$\begin{aligned} f_y &= f_x \frac{n_x}{n_y} \\ \frac{f_y}{f_x} &= \frac{n_x}{n_y} \\ \frac{f_x}{f_y} &= \frac{n_y}{n_x} \end{aligned}$$




Rule is not violated

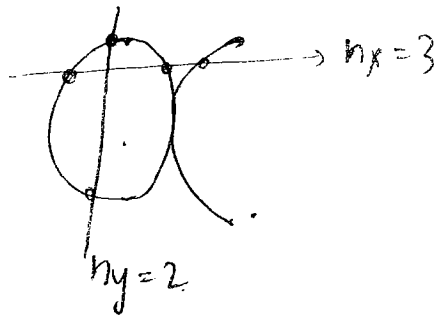

$$\therefore \frac{f_y}{f_x} = \frac{3}{2}$$

$$f_x : f_y = 2/3 \quad \underline{\underline{\text{Ans}}}$$

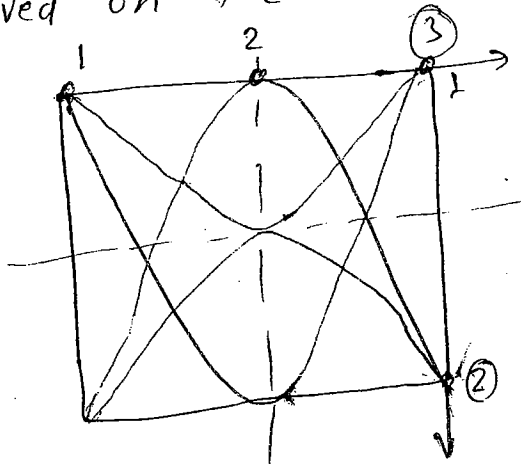Ques: 2 sinusoidal signal are applied having frequency  $f_x$  &  $f_y$  both the i/p of CRO then the below Lissajous pattern is observed on the screen



If the Horizontal frequency is 1 kHz the vertical frequency is -----

(a) 1 kHz

(b) 2 kHz


(c) 1.5 kHz

(d) 2.5 kHz

$$3/2 = 1.5 \text{ kHz}$$


\*\*\*

$f_y n_y = f_x n_x$

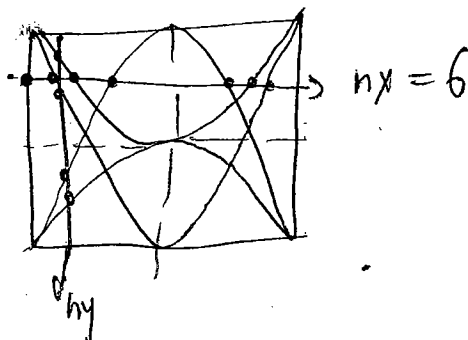


$$f_y = 1 \text{ kHz} \times 3/2 = 1.5 \text{ kHz}$$
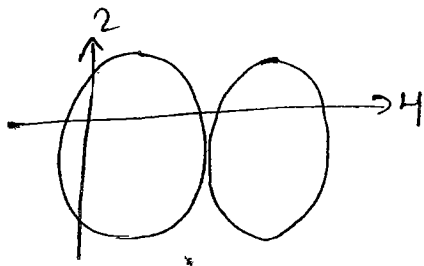
$$f_y = 1 \text{ kHz} \times 6/4 = 1.5 \text{ kHz}$$




$$4/2 = 2/1 = 2:1$$

$$f_y = 2 \text{ KHz}$$

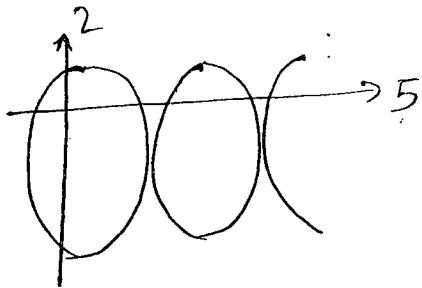


$$5/2 = 5:2$$

$$f_y = 2.5 \text{ KHz}$$

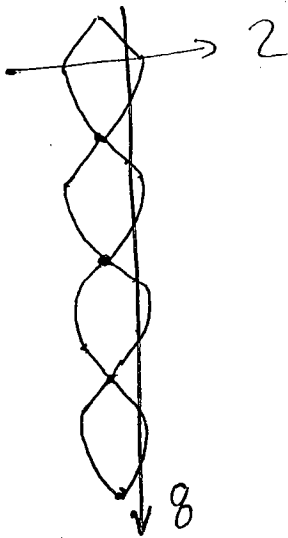


$$\frac{2}{8} \Rightarrow 1:4$$
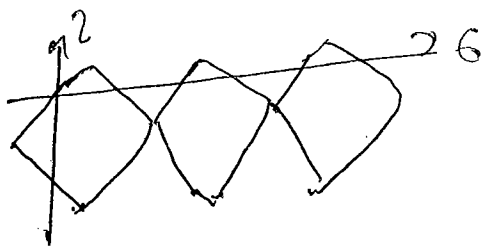
$$f_y = 1 \text{ KHz} \times \frac{1}{4} = 250 \text{ Hz}$$




$$6/2 \Rightarrow 3:1$$

$$f_y = 3 \text{ KHz}$$

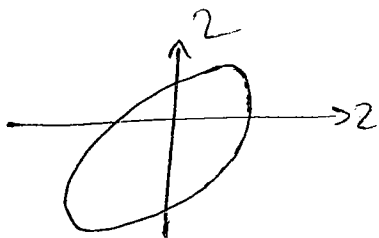


$$\frac{2}{2} = 1:1$$

$$f_y = 1 \text{ KHz}$$

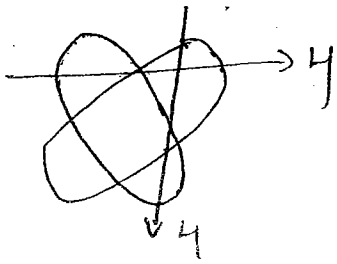


$$\frac{4}{4} = \boxed{1:1}$$

$$f_y = 1 \text{ kHz}$$

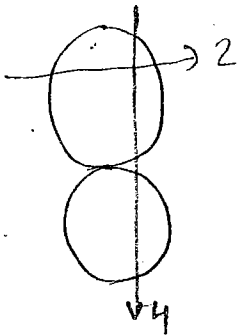


$$\frac{2}{4} = \frac{1}{2} = 1:2$$

$$f_y = 500 \text{ Hz}$$

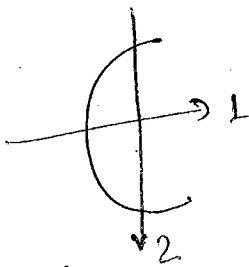


$$= \frac{1}{2} = 1:2$$

$$f_y = 500 \text{ Hz}$$

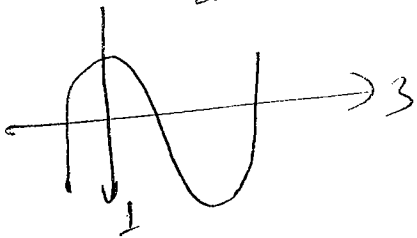


$$\frac{3}{1} = 3:1$$

$$f_y = 3 \text{ kHz}$$

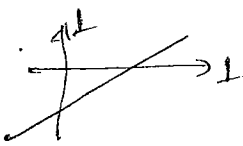


$$\frac{1}{1} = 1:1$$

$$f_y = 1 \text{ kHz}$$

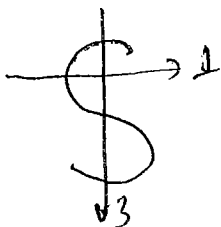

$$\frac{1}{3} = 1:3$$

$$f_y = 333.3 \text{ Hz}$$

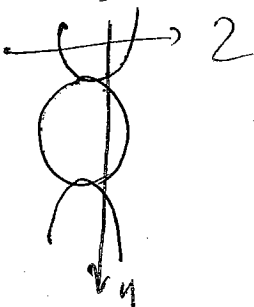


$$\frac{2}{4} = 1:2$$

$$f_y = 1 \text{ kHz} \times \frac{1}{2} = 500 \text{ Hz}$$

An equal amplitude I/P is applied both I/P of CRO an ellipse whose measure axis making a positive slope of  $45^\circ$  if X axis is displayed on the screen the peak Y deflection is 5 div & intersection with Y axis is 3 division.

(a) The phase difference between both the I/P signal is ----.

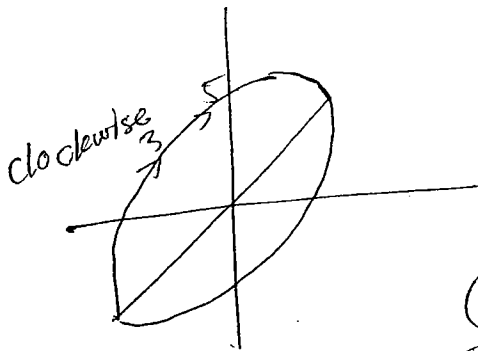(b) The vertical to horizontal frequency ratio is ----.




$$\phi = \sin^{-1}\left(\frac{3}{5}\right)$$

$$= 37^\circ$$

(1) Phase difference =  $37^\circ$

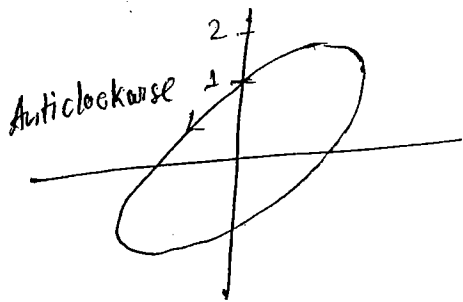(2)  $f_y : f_x = 1 : 1$

Q. An oscilloscope is operated in X-Y mode the below given ellipses is observed on screen.




Then the phase difference between the both I/P signal is ----.

$$\phi = 360^\circ - \sin^{-1}\left(\frac{1}{2}\right)$$

$$= 360^\circ - \sin^{-1}(0.5)$$

$$= 360 - 30^\circ$$

$$= \underline{\underline{330^\circ}}$$

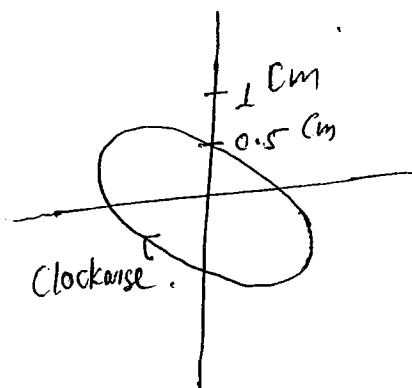


$$\phi = 180 - \sin^{-1}\left(\frac{0.5}{1}\right)$$

$$\phi = 180^\circ - 30^\circ = 150^\circ$$

Ques


(A)

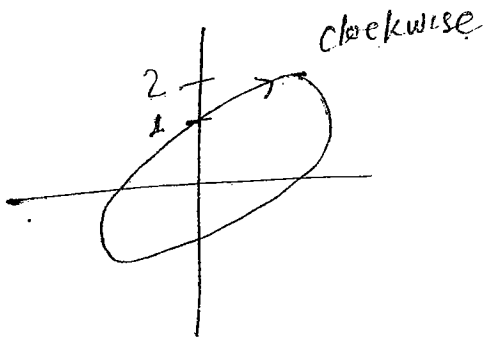

$$\phi = \sin^{-1}(1/2)$$

$$= 30^\circ$$


(B)

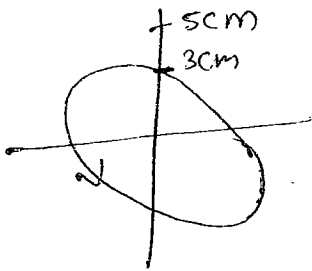


$$\phi = 180^\circ + \sin^{-1}(3/5)$$

$$= 180^\circ + 37^\circ$$

$$= 217^\circ$$

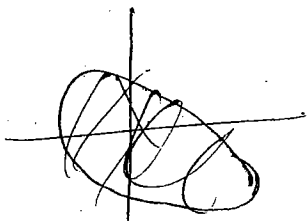

(C)

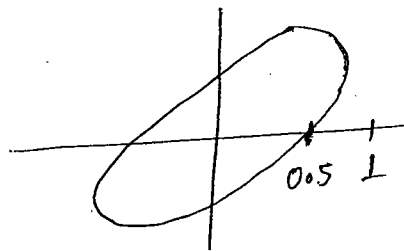


$$\phi = \sin^{-1}\left(\frac{0.5}{1}\right)$$

$$\phi = 30^\circ$$

Ques:- The sinewave o/p of a func<sup>n</sup> gen<sup>r</sup> is fed to both horizontal & vertical i/p of a CRO. Then the pattern displayed on the screen is -----

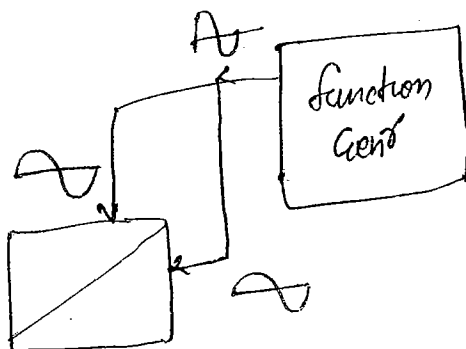- (a) Ellipse (b) Circle (c) Parabola (d) straight line




Ques :- Two voltage across  $10 \sin 314t$  &  $10 \sin 314t$  are both i/p of CRO. The resulting L.F. on the screen is - - -

- (a) Circle
- (b) Parabola
- (c) ~~slant line~~ slant line
- (d) ellipse.

$V_y = V_x$        $f_y = f_x$   
slant line.


Ques Voltage  $100 \sin 1000t$  &  $50 \sin 1000t$  are connected to Y & X terminal of a CRO then the resulting L.F. is - - -

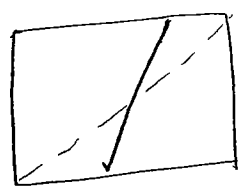$V_y > V_x$        $f_y = f_x$   
 Diagonal line making greater than  $45^\circ$  with +ve axis



(Q)  $50 \sin 1000t \rightarrow Y \text{ i/p}$   
 $100 \sin 1000t \rightarrow X \text{ i/p}$   
 $V_y < V_x$

slant line  $< 45^\circ$  with X-axis

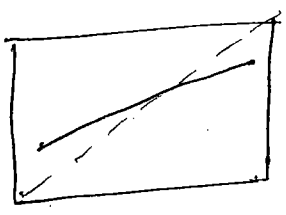

Ques :- The vertical & horizontal i/p's of CRO  $10 \cos(100t + \phi)$ ,  $10 \sin(100t + \phi)$   
 The L.F. in screen is - - -

$V_y = V_x$        $\phi = 90^\circ$        $f_y = f_x$   
 A circle


Ques:- A circle is observed on a screen when 2 sinusoidal signals are applied to having frequency  $f_y$  &  $f_x$  vertical & horizontal i/p of a C.R.O.

- (a) The phase difference is both i/p  $\Rightarrow$   $90^\circ$  or  $270^\circ$   
 (b) The vertical to horizontal frequency  $\Rightarrow$  1:1

Conclusions

Y i/p signal	X i/p signal	Display
$10 \sin 314t$	$-10 \sin 314t$	
$10 \sin 314t$	$10 \cos 314t$	
$10 \cos 314t$	$10 \sin 314t$	
$10 \cos 314t$	$5 \sin 314t$	
$5 \cos 314t$	$10 \sin 314t$	

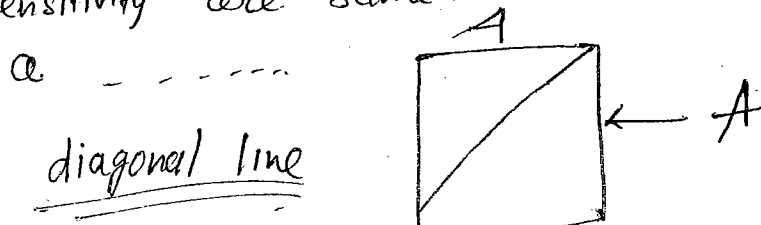Ques:- A circle oscilloscope with  $4\text{cm} \times 4\text{cm}$  screen has its own sweep o/p fed to its i/p if X & Y sensitivity are same the oscilloscope will display



diagonal line

Both XY plot & Y-t plot



An oscilloscope i/p impedance consist of  $1\text{M}\Omega$  in parallel with  $100\text{pF}$ . A compensated  $20:1$  attenuator is obtained by connecting a parallel combination of

- (a)  $19\text{M}\Omega$   $100/19\text{pF}$
- (b)  $19\text{M}\Omega$   $100/20\text{pF}$
- (c)  $19\text{M}\Omega$ ,  $1900\text{pF}$
- (d)  $20\text{M}\Omega$ ,  $2000\text{pF}$

$20:1$

$$V_i = V_s \times 1/20$$

$$\frac{R_i}{R_p + R_i} = \frac{C_p}{C_i + C_p} = \frac{1}{20}$$

$$R_p = 19 \times 1\text{M}\Omega = 19\text{M}\Omega$$

$$C_p = \frac{C_i}{19}$$

$$C_p = \frac{100 \times 10^{-12}}{19}$$

$$C_p = \frac{100\text{pF}}{19}$$

$$R_p = (n-1) R_i$$

$$C_p = \frac{C_i}{n-1}$$

\* A Probe is nothing but basic connecting medium that connects signal under measurement to vertical i/p terminal of CRO. & An ideal probe has to offered feature like almost zero loading & Good signal fidelity based on the type of sense signal. The probe can be classified as


- (1) Current probe
- (2) Voltage Probe
- (3) Logic probe etc

\* Based on the activity in probe had the can be classified as passive & active probe

\* where a passive probe consist of RIG only & An active probe consist of active element like BJT, OPAMP, FET etc.

\* ~~Passive~~ As such active probe are more expensive, bulky, offer more i/p resistance cause less loading than passive probes.

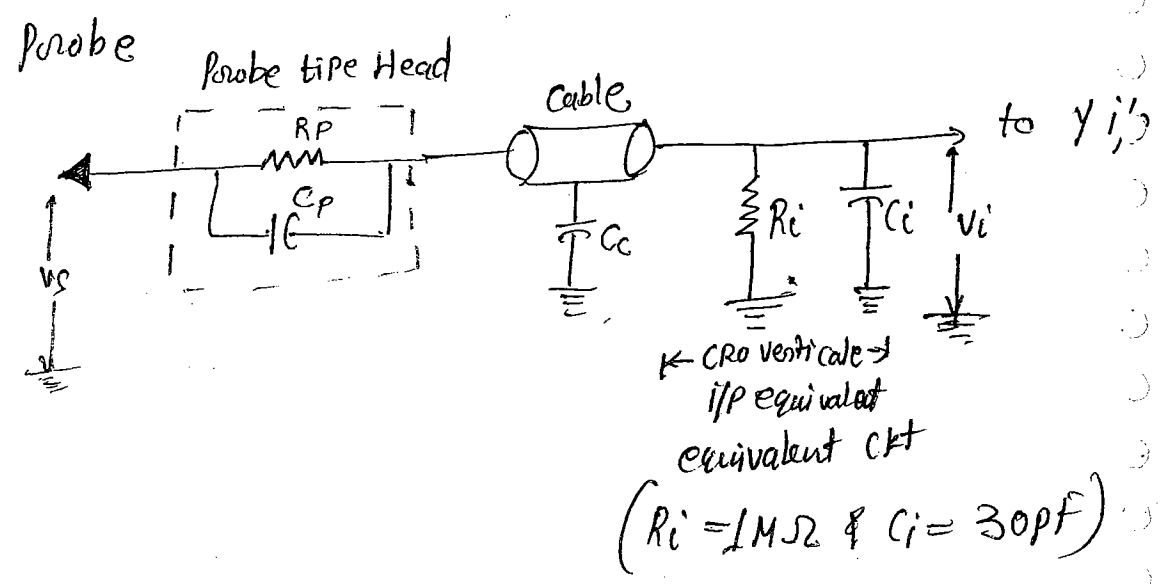
\* A 10 to 1 High impedance Attenuation voltage



## equivalent CKT

At low frequency & medium frequency  
~~medium frequency~~

⇒ Resistive loading.

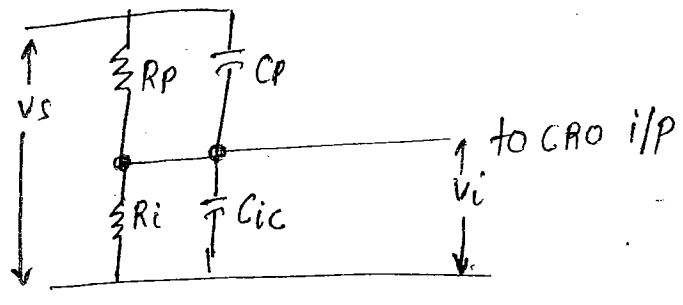

$$V_i = V_s \times \frac{R_i}{R_p + R_i}$$

Amount of Attenuation.

\* At high frequency

⇒ Capacitive loading

$$V_i = V_s \times \frac{X_{CiC}}{X_p + X_{CiC}}$$

$$V_i = V_s \frac{C_p}{C_{iC} + C_p}$$

Amount of attenuation.

⇒ To achieve same (equal) attenuation at all frequencies the condition is

$$\frac{R_i}{R_p + R_i} = \frac{C_p}{C_p + C_{iC}}$$

$$R_i C_p + R_i C_{iC} = R_p C_p + R_i / C_p$$

$$R_i C_{iC} = R_p C_p$$

Compensation of probe  
 (varying Cp to achieve  $R_i C_i = R_p C_p$ )

\* 10:1 Probe means  $V_i = V_s \times \frac{1}{10}$

$$\frac{R_i}{R_p + R_i} = \frac{C_p}{C_p + C_i} = \frac{1}{10}$$

$$\Rightarrow \frac{R_i}{R_p + R_i} = \frac{1}{10}$$

$$10R_i = R_p + R_i$$

$$\therefore R_p = 9R_i$$

$$\Rightarrow \frac{C_p}{C_p + C_i} = \frac{1}{10}$$

$$10C_p = C_p + C_i$$

$$C_p = \frac{C_i}{9}$$

\* 100:1 Probe means  $V_i = V_s \times \frac{1}{100}$

$$\frac{R_i}{R_p + R_i} = \frac{C_p}{C_p + C_i} = \frac{1}{100}$$

$$R_p = 99R_i$$


$$C_p = \frac{C_i}{99}$$

\* 1:1 Probe is known as a direct probe which is simple test lead

\* 10 to 1 Probe  
or  
10% Probe  
or  
10 times Probe  
or  
10X Probe

Ques -

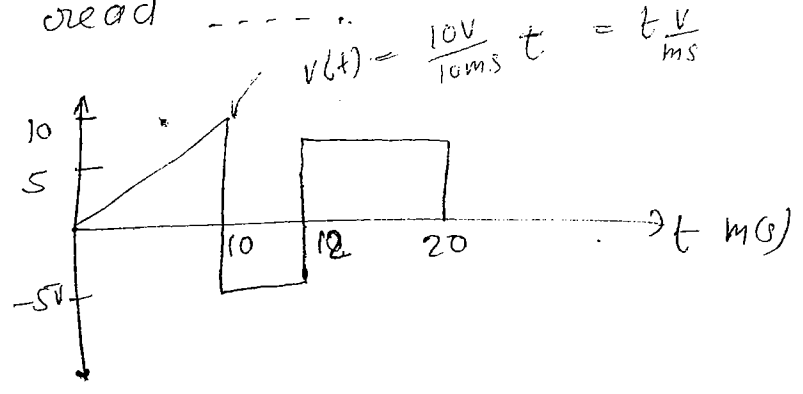A periodic voltage waveform observed on an oscilloscope across the load is shown. A pmmc meter connected across the same wave read



\* The pmmc voltmeter reads -  $V_{dc}$


$$= \frac{1}{20 \text{ ms}} \left[ \frac{1}{2} \times 10 \text{ V} \times 10 \text{ ms} + (-5 \times 2 \text{ ms}) + (5 \text{ V} \times 8 \text{ ms}) \right]$$

$$= \frac{1}{20} \left[ \frac{100}{2} - 10 + 40 \right]$$


$$= \frac{1}{20} [80] = 4 \text{ V}$$

$$\begin{aligned}
 V_{dc} &= \frac{1}{20 \text{ ms}} \int_0^{20 \text{ ms}} v(t) dt \\
 &= \frac{1}{20 \text{ ms}} \left[ \int_0^{10 \text{ ms}} t \frac{\text{V}}{\text{ms}} dt + \int_{10 \text{ ms}}^{12 \text{ ms}} -5 \text{ V} dt + \int_{12 \text{ ms}}^{20 \text{ ms}} 5 \text{ V} dt \right] \\
 &= \frac{1}{20 \text{ ms}} \left[ \frac{\text{V}}{\text{ms}} \times \left( \frac{t^2}{2} \right)_0^{10} - 5 \text{ V} (t)_{10}^{12} + 5 [t]_{12 \text{ ms}}^{20 \text{ ms}} \right] \\
 &= \frac{1}{20 \text{ ms}} \left[ \frac{\text{V}}{\text{ms}} \times \frac{(10 \text{ ms})^2}{2} - 5 \text{ V} \times 2 \text{ ms} + 5 \text{ V} \times 8 \text{ ms} \right] \\
 &= \frac{1}{20} \left[ \frac{100}{2} - 10 + 40 \right] \\
 &= \frac{1}{20} [80] = 4 \text{ V}
 \end{aligned}$$

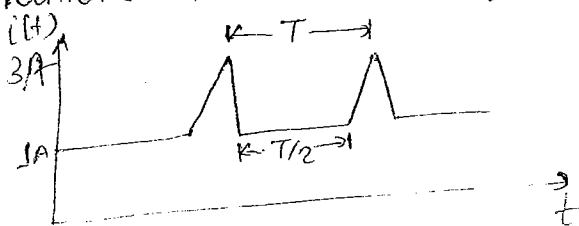Ques - An ac ammeter is used to measure a current which is deper saw tooth superimposed on 1Amp dc calculate the reading of ammeter



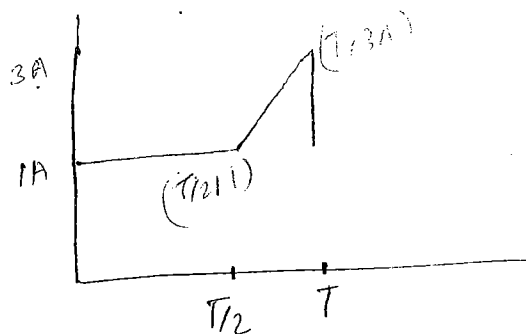Soln - We will suppose to calculate RMS value



$$T/2 < t < T$$

$$y - y_1 = m(x - x_1)$$

$$i(t) - 1 = \frac{3-1}{T-T/2} (t - T/2)$$

$$i(t) - 1 = \frac{2}{T/2} (t - T/2)$$

$$= \frac{4}{T} (t - T/2) = \frac{4t}{T} - 2 + 1$$

$$= \frac{4t}{T} - 1$$

$$i(t) = \frac{1}{T} (4t - T)$$

$$i(t) = 1A, \quad 0 < t < T/2$$

$$= \frac{1}{T} (4t - T), \quad T/2 < t < T$$

AC Ammeter rdg =  $I_{rms}$

$$I_{rms} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

$$= \sqrt{\frac{1}{T} \int_0^{T/2} (1A)^2 dt + \frac{1}{T} \int_{T/2}^T \left(\frac{1}{T} (4t - T)\right)^2 dt}$$


$$= \sqrt{\frac{1}{T} \times (t)_0^{T/2} + \frac{1}{T^3} \left[ \frac{(4t-T)^3}{3 \times 4} \right]_{T/2}^T} \quad A$$

$$= \sqrt{\frac{1}{T} \times \frac{T}{2} + \frac{1}{12T^3} (27T^3 - T^3)} \quad A$$

$$= \sqrt{\frac{1}{2} + \frac{26T^3}{12T^3}} = \sqrt{\frac{32}{12}} \quad A$$

$$= 1.63 \quad A$$

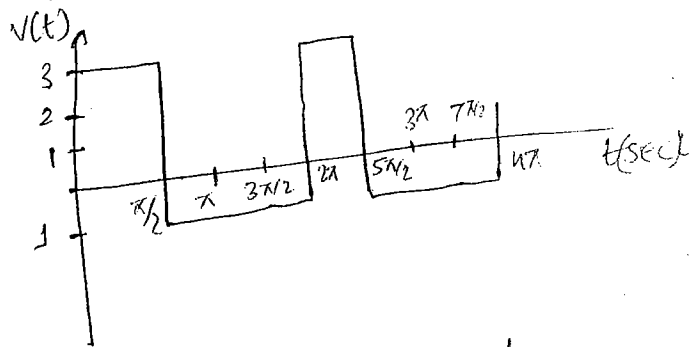Que - The periodic voltage of the form shown in below fig is applied to a true RMS meter determine the reading of the instrument



Soln - True RMS meter measure rms value of i/p

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v^2(t) dt}$$

$$= \sqrt{\frac{1}{2\pi} \int_0^{\pi/2} (3V)^2 dt + \frac{1}{2\pi} \int_{\pi/2}^{2\pi} (1V)^2 dt}$$


$$= \sqrt{\frac{9}{2\pi} \times (t)_0^{\pi/2} + \frac{1}{2\pi} \times (t)_{\pi/2}^{2\pi}} \quad V$$

$$= \sqrt{\frac{9}{2\pi} \times \frac{\pi}{2} + \frac{1}{2\pi} \times \frac{3\pi}{2}} \quad V$$

$$= \sqrt{\frac{9}{4} \times \frac{3}{4}} \quad V = \sqrt{\frac{12}{4}}$$

$$= \sqrt{3} \quad V$$

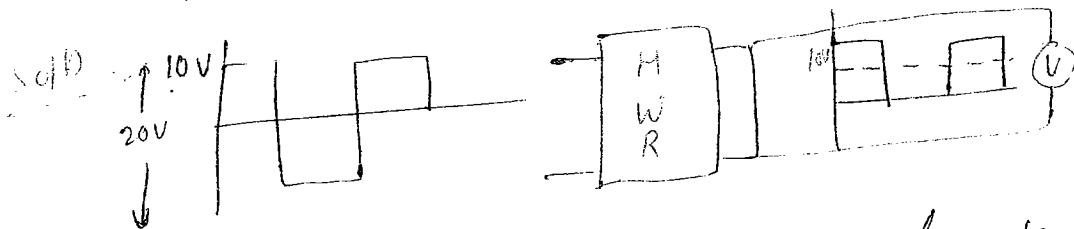Ques:- A symmetrical voltage with zero mean having peak to peak amplitude of 20V. is applied to a half wave rectifier. A dc voltmeter connected the o/p half wave rectifier read - - - -



\* DC voltmeter reading = VDC of o/p of HWR  
 $= 10 \times \frac{1}{2} = 5V$


Ques:- Given 0-1mA meter with there internal resistance of 5Ω how did you exted its range to 10 mA

- Soln
- Available current range = 0-1mA
  - Required current range = 0-10mA
  - The internal range of Ammeter is 5Ω

The current range of an ammeter can be extended by placing a low valued shunt resistance (To bypass excess amount of current) & calculating & calibrating the current scale in terms of extended range.

$$m = \frac{10 \text{ mA}}{1 \text{ mA}} = 10$$
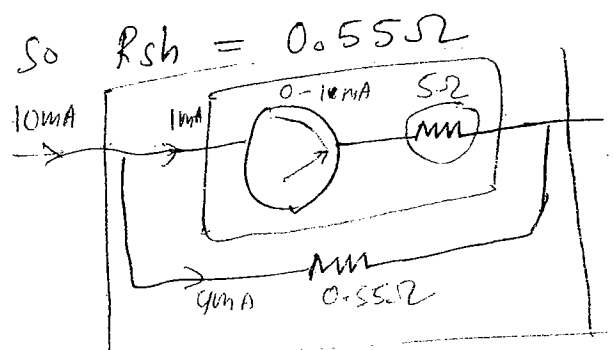
$$R_{sh} = \frac{R_m}{m-1} = \frac{5}{10-1} = \frac{5}{9} = 0.55 \Omega$$





$$R_{in} = 511.055 \Omega$$



$$= 0.5 \Omega$$

0-10 mA, 0.5  $\Omega$  DC ammeter

Ques -

A moving coil ammeter has fixed shunt  $0.02 \Omega$  with a coil resistance of  $R = 1 k\Omega$  & needs potential difference of  $0.5 V$  across it for full scale deflection (1) calculate the current it correspond to (2) Find the value of shunt when total current is 2 Amp.

Soln:-

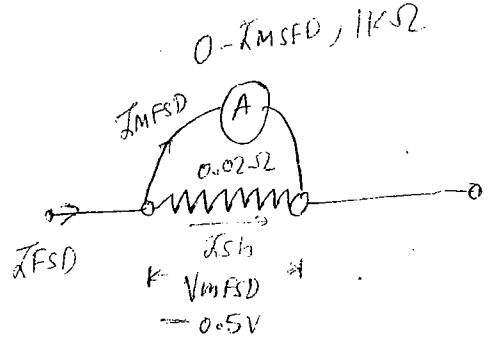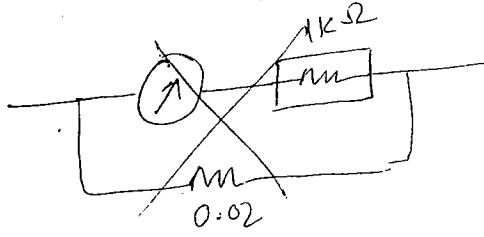

$$(1) I_{MFSD} = \frac{0.5V}{1k\Omega} = 0.5 mA$$

$$I_{sh} = \frac{0.5V}{0.02\Omega} = 25A$$

We know  $R_{sh} = \frac{R_m}{m-1}$ ,  $m = \frac{R_m}{R_{sh}} + 1$

$$= \frac{1k\Omega}{0.02\Omega} + 1 = 50k \quad I_{FSD} = 0.5$$

$$I_{FSD} = m I_m = 50k \times I_{MFSD}$$

$$I_{FSD} = 0.5mA + 25A$$

$$I_{MFSD} = 0.5 mA$$



$$I_{FSD} = 10 A$$

$$R_{sh} = \frac{1k\Omega}{\frac{10A}{0.5mA} - 1} = 0.05\Omega$$

Date  
14/10/21/2

Ques - A voltmeter with internal resistance of  $4750\Omega$  is used to measure the voltage across a resistance of  $600\Omega$  connected in series with a DC source of internal resistance of  $400\Omega$ . What is the error?

Soln

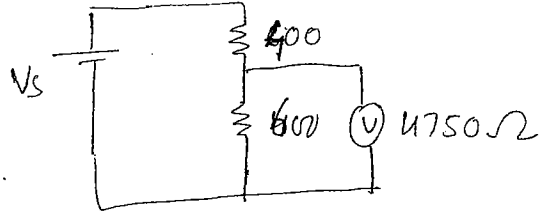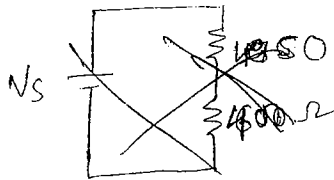

$V_{true} \Rightarrow$  voltage across  $600\Omega$

$$= V_s \times \frac{600}{600 + 400}$$

$$= 0.6V_s$$

$$R_{eff} = 600 \parallel 4750$$

$$= 532.7\Omega$$

$V_{meas} = V'$  across  $532.7\Omega$

$$= V_s \times \frac{532.27}{400 + 532.7}$$


$$= 0.57V_s$$

$$\text{Loading error} = \frac{0.57V_s - 0.6V_s}{0.6V_s} \times 100\%$$

$$= -4.8\%$$

$$\approx -5\%$$

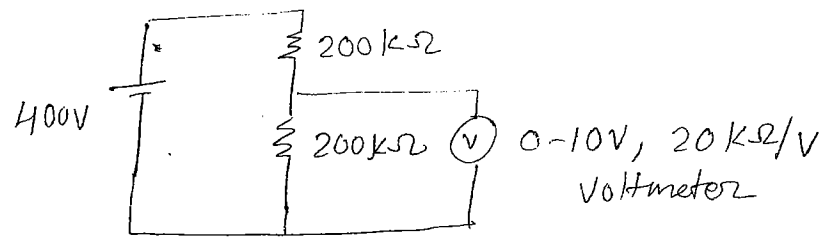Ques  $\Rightarrow$  In a ckt shown in below fig voltage measured by a voltmeter with a sensitivity of  $20,000 \Omega/Volt$  & using the  $10V$  range find the % error in measurement.



Soln:- It is given that  $V_{fd} = 10V$ ,  $S_{dc} = 20k\Omega/V$

\*  $V_{true} = V_{200\Omega}$   
 $= 400V \times \frac{200k\Omega}{400k\Omega} = 200V$


\*  $R_V = \frac{20k\Omega}{V} \times 10V = 200\Omega$

\*  $R_{eff} = R_L \parallel R_V = 200k\Omega \parallel 200k\Omega$   
 $R_{eff} = 100k\Omega$

$V_{meas} = V_{100k\Omega} = 400V \times \frac{100k\Omega}{300k\Omega}$   
 $= 133.33V$

% error  $= \frac{133.33V - 200V}{200V} \times 100\%$   
 $= -33.33\%$

Ques:- Explain briefly about sensitivity & loading effect of ammeter the voltage across  $50k\Omega$  resistor in ckt shown in below fig. Measured with 2 voltmeter separately. Voltmeter ① have sensitivity of  $1000 \Omega/V$  & voltmeter ② has a sensitivity of  $2000 \Omega/V$ . Both the meter are used on there  $50V$  range calculate (1) Reading of each meter (2) The error in each reading expressed as % of the

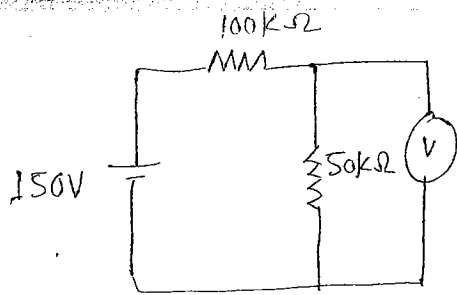

$$S_{dc} = \frac{R_V}{V_{FSD}}$$

$$= \frac{\cancel{V_{FSD}}}{\cancel{R_{FSD}} \cdot V_{FSD}}$$

$$S_{dc} = \frac{1}{I_{FSD}}$$

(i)  $V_{true} = V_{50k\Omega}$

$$= 150V \times \frac{50k\Omega}{150k\Omega} = 50V$$

\* Voltmeter ①

$$\hookrightarrow R_V = 1k\Omega/V \times 50V = 50k\Omega$$

$$R_{eff} = 50k\Omega \parallel 50k\Omega = 25k\Omega$$

$$V_{meas} = 150 \times \frac{25k\Omega}{125k\Omega} = 30V$$

\* Voltmeter ②

$$R_V = 2k\Omega/V \times 50V = 100k\Omega$$

$$R_{eff} = 50\Omega \parallel 100k\Omega = 33.3k\Omega$$

$$V_{meas} = 150 \times \frac{33.3k\Omega}{133.3k\Omega} = 37.5V$$

reading of  $V_1$  is = 30V

& reading of  $V_2$  is = 37.5V

$$(ii) \% \text{ error of Voltmeter ①} = \frac{30V - 50V}{50V} \times 100\%$$


$$= -40\%$$

$$\% \text{ Error in reading of } V_2 = \frac{37.5 - 50V}{50V} \times 100\%$$

$$= -25\%$$


2- A Galvanometer with internal resistance of  $100\Omega$  & full scale current rating of  $1mA$  is used to realize a dc voltmeter with a full scale range of  $1V$ . The full scale range of this meter can be extended to  $10V$  by connecting an external resistance of value . . . .

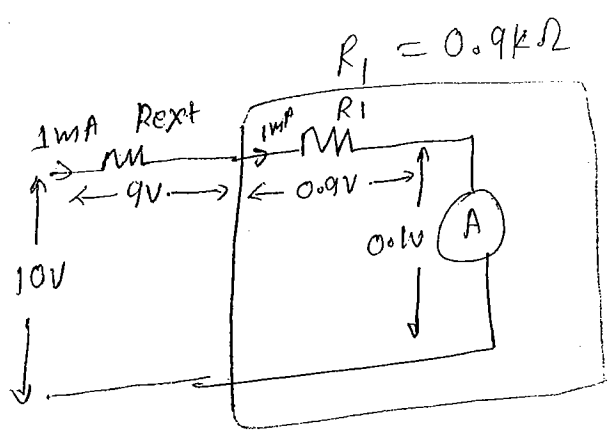Sol  $\otimes$   $R_1 = \frac{1V - 0.1V}{1mA} = \frac{0.9V}{1mA} = 900\Omega$



$R_{ext} = \frac{10V - 1V}{1mA} = 9k\Omega$

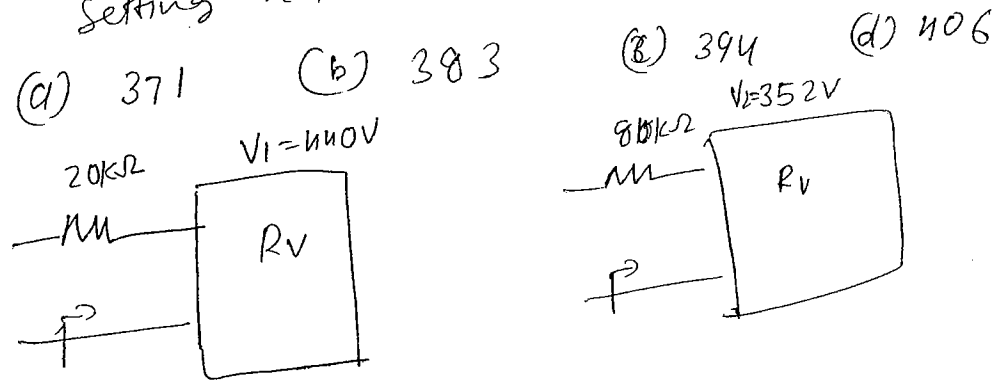Ques - An analog voltmeter used as external multiplier settings with a multiplier setting of  $20k\Omega$  it reads  $440V$  & with  $80k\Omega$  it reads  $352V$ . For multiplier setting  $10k\Omega$  voltmeter read . . . . .



reading of voltmeter  $\propto \frac{1}{R}$

$\frac{V_1}{V_2} = \frac{R_2}{R_1}$   
 $\frac{440}{352} = \frac{80k\Omega + R_v}{20k\Omega + R_v}$

$8800k\Omega + 440R_v = 28160 + 352R_v$   
 $R_v = 220k\Omega$


$$\frac{V_1}{V_3} = \frac{R_3}{R_1}$$

$$\frac{440}{V_3} = \frac{40k\Omega + 220k\Omega}{20k\Omega + 220k\Omega}$$

$$\boxed{V_3 = 406 \text{ V}}$$

Ques. Design a multirange ammeter using a 1mA ammeter with internal resistance of  $100\Omega$ . Required voltage ranges are 0-1V & 0-10V. Find the value of multiplier resistor for below given voltmeter designs (1) Multirange voltmeter with switched multiplier resistor (2) Multirange voltmeter with series connected multiplier resistor i.e. using potential divider arrangement

Soln.

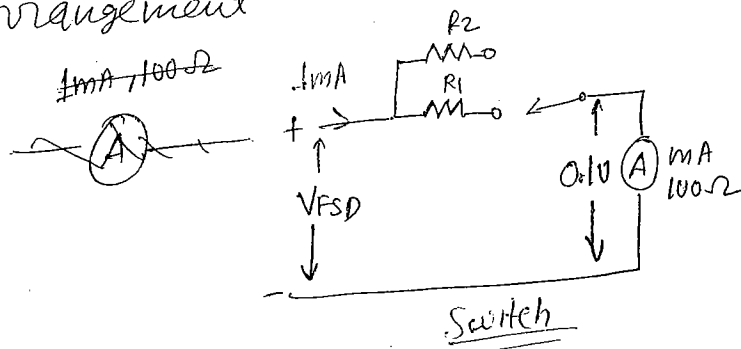

1V range

$$R_1 = \frac{1\text{V} - 0.1\text{V}}{1\text{mA}}$$


$$= 0.9\text{k}\Omega$$

10V range

$$R_2 = \frac{10\text{V} - 0.1\text{V}}{1\text{mA}}$$

$$= 9.9\text{k}\Omega$$

Series

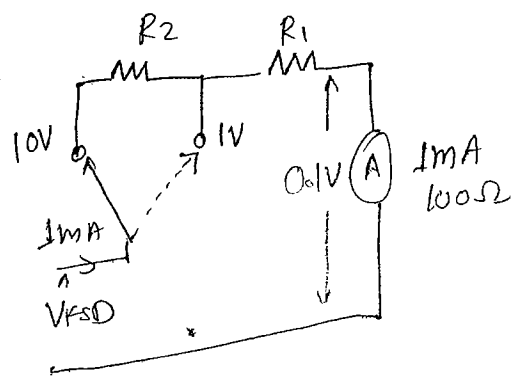

10V range

$$R_1 + R_2 = \frac{10V - 0.1V}{1mA}$$

$$0.9k\Omega + R_2 = 9.9k\Omega$$


$$R_2 = 9k\Omega$$

1V range

$$R_1 = \frac{1V - 0.1V}{1mA} = 0.9k\Omega$$

Que - 2mA with full scale currents of 1mA & 10mA are connected in parallel & they read 0.5mA & 2.5mA respectively there internal resistances the ratio of - - - -

Soln -

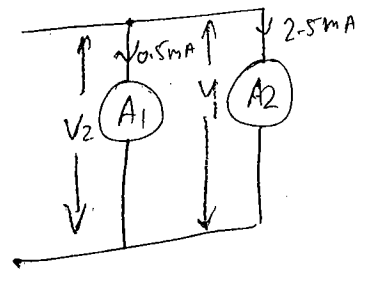

$$V_1 = V_2$$

$$I_1 \times R_1 = I_2 \times R_2$$


$$0.5 \times R_1 = 2.5 \times R_2$$

$$\frac{R_1}{R_2} = \frac{2.5}{0.5}$$


$$\frac{R_1}{R_2} = \frac{5}{1}$$

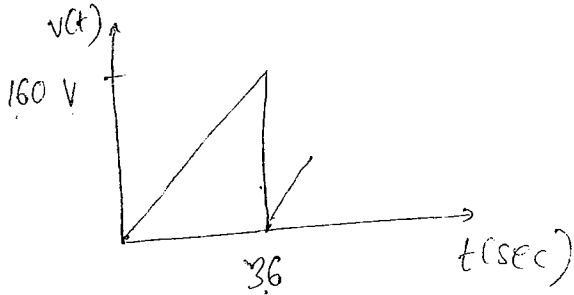- (a) 10:1
- (b) 1:10
- (c) 5:1
- (d) 1:5

Ques:- A sawtooth voltage has peak value of 160V at time period of ~~3.6~~ 3.6 sec As shown in below fig. Calculate the error at measuring this voltage with an ~~the~~ avg reading voltmeter calibrated in terms of RMS value of sinusoidal wave.



Soln

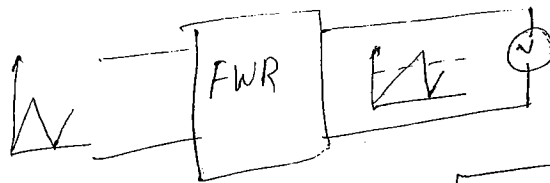


$$\rightarrow \text{Voltage } V_{\text{RMS (true)}} = \sqrt{\frac{1}{3.6} \int_0^{3.6} \left(\frac{160}{3.6}t\right)^2 dt} \cdot V$$

$$= \sqrt{\frac{160^2}{(3.6)^3} \times \frac{(3.6)^3}{3}}$$

$$= 92.376 \text{ V} \rightarrow \text{Actual or true RMS voltage (to be preferred)}$$

\* The o/p of FWR

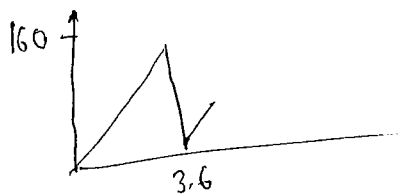

The dc voltmeter reads Avg. value of o/p of FWR

$$V_{\text{dc}} = \frac{1}{3.6} \int_0^{3.6} \frac{160}{2.6} t dt$$

$$= 80 \text{ V}^*$$

They indicated rms is 1.11 Vdc since the scale is calibrated in terms of rms of sine wave

$$V_{\text{rms (ind)}} = 1.11 \times 80 = 88.8 \text{ V}$$

= measured rms value



→ error = 88.6 - 92.37V = ~~-3.57V~~  
 = -3.57V

% wave form error =  $\frac{-3.57}{92.37V} \times 100\%$   
 = -3.86%

i.e the reading of FWR voltmeter while measuring above voltage is less than true rms by 3.8% of true rms

[Note: If given as objective Que than,

We know  $FF_{saw} = 1.154$

% error =  $\left[ \frac{1.11}{FFW} - 1 \right] \times 100\%$


=  $\left[ \frac{1.11}{1.154} - 1 \right] \times 100\%$

= -3.86%

Que - The periodic voltage waveform as shown in below fig is applied to (1) True rms meter (2) An avg measuring, rms indicating meter,

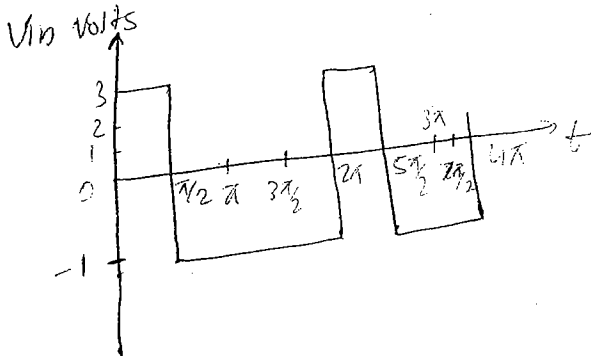(3) Peak measuring rms indicating meter


Determine the reading of each instrument.





Soln

1)  $V_{rms} (True) = \sqrt{3} = 1.73$

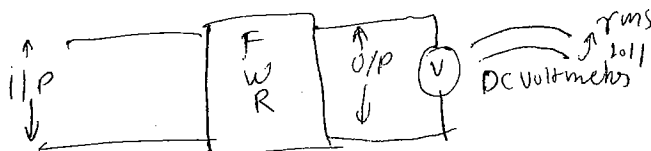2) Given meter is Avg msq - rms ind meter



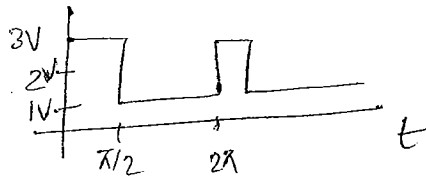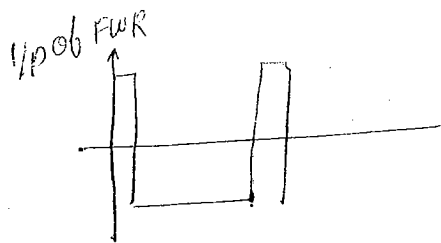

DC voltmeter measures  $V_{dc}$  of o/p of FWR



$$V_{dc} = \frac{1}{2\pi} \left[ \int_0^{\pi/2} 3V dt + \int_{\pi/2}^{2\pi} 1V dt \right]$$

$$= \frac{1}{2\pi} \left( 3\pi/2 + (2\pi - \pi/2) \right)$$

$$= \frac{1}{2\pi} \left( 3\pi/2 + 3\pi/2 \right) = \frac{3}{2} = \underline{1.5 V}$$

$$\therefore V_{rms} = 1.11 \times 1.5 = 1.665 V$$

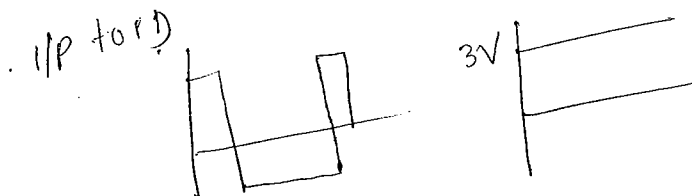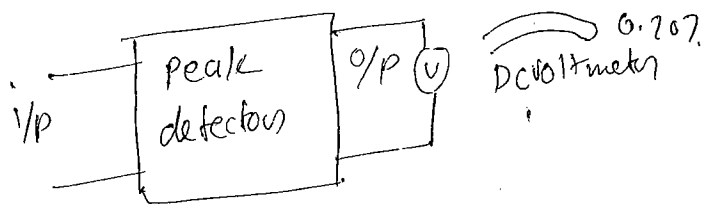(iii) Given meter is peak rms indicating meter



DC voltmeter measures  $V_{dc}$  of o/p of peak detector  
(o/p of i/p)

$$V_{dc} = 3V$$

$$V_{rms}(ind) = 0.707 \times 3V = 2.121V$$


from above 2 meter calculate the amount of error intro into voltage measurement & expressed it as a % of true value.

$$\% \text{ error} = \frac{V_m - V_t}{V_t} = \frac{2.121 - 1.73}{1.73}$$

$$= 22.54\%$$

Ques:- An avg responding electronic voltmeter has its scale calibrated to indicate correctly, the rms value of sinusoidal voltage calculate error in its reading if the instrument is used for measuring value of asymmetrical triangular wave voltage. 116

Sol<sup>n</sup>:-

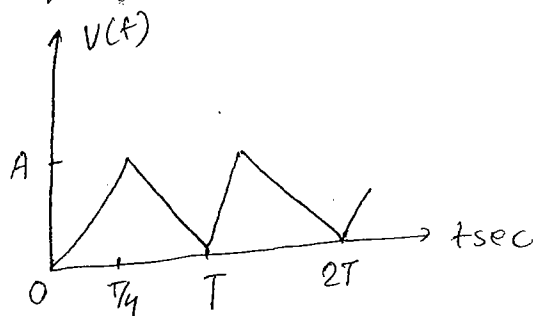

$$(0 < t < T/4)$$

$$(T/4, A)$$

$$(0, 0)$$

$$y = mx$$

$$V(t) = \frac{A}{T/4} \times t$$

$$V(t) = \frac{4A}{T} \times t$$

$$T/4 < t < T$$

$$(T/4, A)$$

$$(T, 0)$$

$$y - y_1 = m(x - x_1)$$

$$V(t) - A = \frac{-A}{T - T/4} (t - T/4)$$

$$= \frac{4}{3} \frac{A}{T} (t - T/4)$$

$$V(t) = \frac{4A}{T} t ; 0 < t < T/4$$

$$= \frac{4A}{3T} (T - t) ; T/4 < t < T$$

$$\rightarrow V_{rms}(\text{true}) = \sqrt{\frac{1}{T} \int_0^T V^2(t) dt}$$

$$= \sqrt{\frac{1}{T} \int_0^{T/4} \left(\frac{4A}{T} t\right)^2 dt + \frac{1}{T} \int_{T/4}^T \left(\frac{4A}{3T} (T - t)\right)^2 dt}$$

$$V_{rms}(\text{true}) = \sqrt{\frac{16A^2}{T^3} \int_0^{T/4} t^2 dt + \frac{(4A)^2}{9T^3} \int_{T/4}^T (T - t)^2 dt}$$

$$V_{rms}(\text{true}) = \sqrt{\frac{1}{7} \left(\frac{4A}{T}\right)^2 \times \left(\frac{t^3}{3}\right)_{T/4}^0 + \frac{(4A)^2}{9T^3} \times \left(\frac{(T-t)^3}{-3}\right)_{T/4}^T}$$

$$V_{rms}(\text{true}) = \frac{4A}{\sqrt{3}}$$


$$= \sqrt{\frac{(4A)^2}{3T^3} \times \frac{T^3}{4^3} + \frac{4A}{27T^3} (T-T/4)^3}$$

$$= \sqrt{\frac{(4A)^2}{3T^3} \times \frac{T^3}{4^3} + \frac{(4A)^2}{27T^3} \times \frac{3^3 T^3}{4^3}}$$

$$V_{rms} \text{ (true)} = \frac{A}{\sqrt{3}} = 0.577A$$

The electronic AC voltmeter consist FWR at primary stage whose o/p is fed to pmmc voltmeters

i/p to FWR

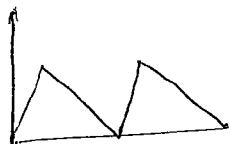

o/p of FWR = i/p to DC voltmeter



DC voltmeter measures Vdc of o/p of FWR

$$V_{dc} = \frac{1}{T} \int_0^T v(t) dt$$

$$= \frac{1}{T} \int_0^{T/4} \frac{4t}{T} dt + \frac{1}{T} \int_{T/4}^T \frac{4A}{3T} (T-t) dt$$

$$= \frac{4A}{T^2} \int_0^{T/4} t dt + \frac{4A}{3T^2} \int_{T/4}^T (T-t) dt$$

$$= \frac{4A}{T^2} \times \frac{T^2}{4^2 \times 2} + \frac{4A}{3T^2} \times \frac{(3T/4)^2}{2}$$


$$= A/2$$

$$V_{rms} \text{ (ind)} = 1.11 \times A/2 = 0.555A$$


$$e_{err} = \frac{0.555 - 0.577}{0.577} = -0.038$$

Ques - An electronic voltmeter consisting of FWR & avg square wave/10 for its reading for 2 volt peak to peak sinusoidal i/p will be -

Soln =>

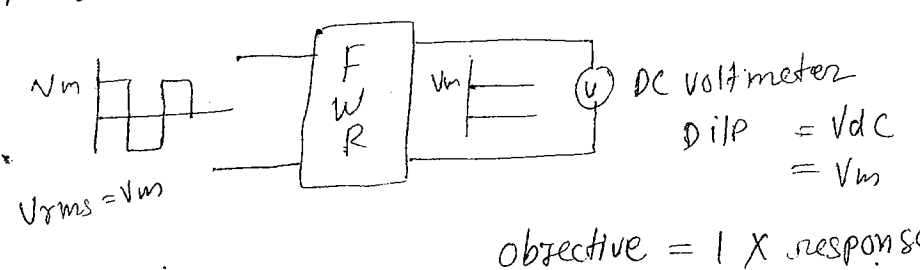

objective = 1 x response

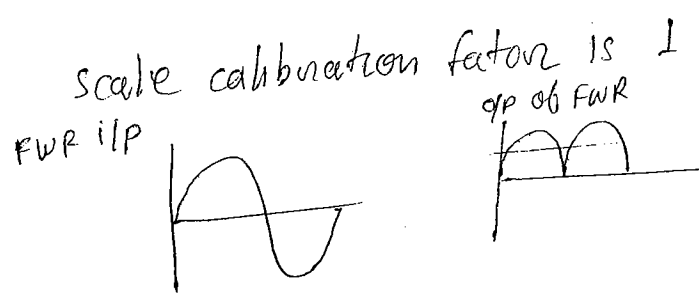

$$V_{dc} = \frac{2V_m}{\pi}$$

$$= \frac{2}{\pi} \quad (\because V_m = 1V)$$

$$V_{rms} = 1 \times V_{dc}$$

$$= 1 \times \frac{2}{\pi} = \frac{2}{\pi} V$$

Essential statement

\* A FWR voltmeter reads the true rms value of i/p waveform.  
reason - The FWR voltmeter (AC) has a rectifier unit first which feeds its o/p to PMMC indicating instrument.

Essential is wrong, reason is true

\* A symmetrical square wave voltage is read by an avg response electronic voltmeter whose scale is calibrated in terms of rms value of a sinusoidal wave. The error in reading is

- (a) -3.9%
- (b) +3.9%
- (c) -11%
- (d) 11%


$$\text{Error} = \frac{1.11 - 1}{1} = 0.11 \text{ or } +11\%$$

Que:- An avg response rectifier type electronic voltmeter as dc voltage of 10V applied to it what is meter reading

FWR i/p



FWR o/p

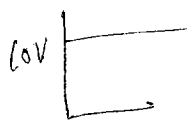

$$V_{dc} = 10V$$

$$= 10 \times 1.11$$

$$= 11.1$$

Que:- What is the advantage of electronic voltmeter over non electronic voltmeter

(a) ~~High~~ <sup>Low Power Consumption</sup> i/p impedance

(b) low i/p impedance

(c) The ability to measure wide ranges of voltage & resistance

(d) Large portability

Que:- For measurement of the voltage of the order of mV the voltmeter used is

(1) Rectifier amplifier VPVM

(2) Amplifier rectifier type VPVM

(3) Diode peak VTVM


(4) Slight wire (VTVM)

Ques... PMMC voltmeter has a sensitivity of  $20\text{ k}\Omega/\text{volt}$ .  
 A reading of  $4.5\text{ V}$  is obtained when measuring a voltage source with the internal resistance on its  $5\text{ V}$  scale. When the scale is changed to  $10\text{ V}$  scale, a reading of  $6\text{ V}$  is obtained. The value of the voltage source & its internal resistance are - - -

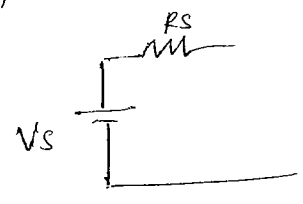- (a)  $10\text{ V}$ ,  $100\text{ k}\Omega$
- (b)  $9\text{ V}$ ,  $100\text{ k}\Omega$
- (c)  $10\text{ V}$ ,  $200\text{ k}\Omega$
- (d)  $9\text{ V}$ ,  $200\text{ k}\Omega$

Soln:-

$S = 20\text{ k}\Omega/\text{volt}$   
 \*  $5\text{ V}$  scale



$\rightarrow R_v = \frac{20\text{ k}\Omega}{\text{V}} \times 5\text{ V}$   
 $R_v = 100\text{ k}\Omega$

$\rightarrow \text{Reading} = V_s \times \frac{100\text{ k}\Omega}{R_s + 100\text{ k}\Omega}$

$4.5 = V_s \times \frac{100\text{ k}\Omega}{R_s + 100\text{ k}\Omega}$

$V_s = \frac{4.5\text{ V}}{100\text{ k}\Omega} [R_s + 100\text{ k}\Omega] \text{ --- (1)}$

\*  $10\text{ V}$  scale

$R_v = \frac{20\text{ k}\Omega}{\text{V}} \times 10\text{ V} = 200\text{ k}\Omega$

$\text{rdg} = V_s \times \frac{200\text{ k}\Omega}{R_s + 200\text{ k}\Omega}$

$6\text{ V} = V_s \times \frac{200\text{ k}\Omega}{R_s + 200\text{ k}\Omega}$

$V_s = \frac{6\text{ V}}{200\text{ k}\Omega} [R_s + 200\text{ k}\Omega] \text{ --- (2)}$

equating eqn (1) with eqn (2)

$\frac{4.5\text{ V}}{100\text{ k}\Omega} [R_s + 100\text{ k}\Omega] = \frac{6\text{ V}}{200\text{ k}\Omega} [R_s + 200\text{ k}\Omega]$

$$\Rightarrow R_s = 100 \text{ k}\Omega$$

Putting  $R_s$  in eqn ①

$$V_s = \frac{4.5}{100 \text{ k}\Omega} [100 \text{ k}\Omega \parallel 100 \text{ k}\Omega]$$

$$V_s = 9 \text{ volt}$$

## Q meter

### Principle of operation

- \* Direction connection ckt diagram
- \* elements in the connection
- \* working
- \* Mention error, % error & correction factor

Done previous

Que- Explain with the help of ckt diagram the principle of work of a meter.

Que- Describe a method of measuring the disruptive capacitance of coil derive a necessary expression.

Soln- \* Q meter in direct connection can be used for measure

- of  $C_d$  of coil
- \* Direction connection of ckt diagram
- \* elements in connection
- \* 2 steps of resonant state
- Mention reading of each step
- \* Derivation for  $C_d$

$$\begin{matrix} * \text{ Ex } & f \rightarrow 2f \\ & C_1 \rightarrow C_2 \end{matrix} \left. \vphantom{\begin{matrix} f \\ C_1 \end{matrix}} \right\} C_d = \frac{C_1 - 4C_2}{3}$$

Que - A coil was tested using a Q meter and the following result was obtained

Oscillator frequency	3 MHz	6 MHz
Tuning Capacitance setting	25 pF	50 pF



Find self capacitance of coil

118

Soln:-  $n = \frac{6\text{MHz}}{3\text{MHz}} = 2$

$$C_d = \frac{251\text{PF} - 4 \times 50\text{PF}}{3} = \underline{17\text{PF}}$$

- Que:- (a) Describe the method of measuring the value of  $Q$  factor of an unknown inductance in the range  $1\mu\text{H} - 1\text{mH}$  with high accuracy
- (b) An unknown inductance resonant at frequency of  $1\text{MHz}$  with an external capacitance of  $210\text{PF}$  (tuning capacitor) & has a  $Q$  of  $100$ . If the frequency of the source is doubled it is found that the tuning capacitor required for resonant is  $45\text{PF}$ . Determine the value of unknown inductance & other component associated with it in the equivalent ckt

Que:- In a  $Q$  meter measurement to determine the self capacitance of a coil the 1st resonance occurred at  $f_1$  with  $C_1 = 300\text{PF}$  the 2nd resonance occurred at  $f_2 = 2f_1$  with  $C_2 = 60\text{PF}$ . The self capacitance of  $C_s = \dots$

$$= \frac{300 - 2^2 \times 60}{3} = 20\text{PF}$$


2003  
Que:- Assertion  $\rightarrow$  The  $Q$  meter measures the  $Q$  factor of a coil when the ckt is at resonance. (True)

Reason  $\rightarrow$  The  $Q$  factor of coil depends only on its inductance & not on its resistance. (False)

2000  
Que:- Assertion  $\Rightarrow$  The basic principle of operation of a  $Q$  meter is based on the property of series resonance ckt. (True)

Reason  $\Rightarrow$  If a fixed voltage is applied to a series resonant ckt the voltage developed across it capacitor is  $Q$  times the applied voltage. (True)

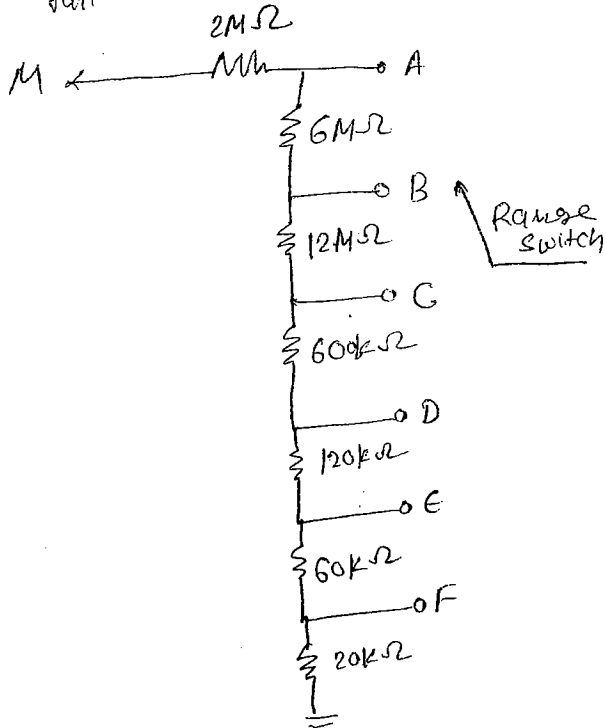Ques:- The figure shows i/p attenuation of multimeter the meter read for the scale 10 with 12V at M & range slw at B what is the required voltage at M to obtain full scale deflection with the range 50 position at D



(a) 1.2V

(b) 150V

(c) 120V

(d) 147V

date  
12/04/2012



Que:- An analog single channel CRO is used to measure a time varying signal  $2 \sin 100\pi t$  & identify the image of signal displayed on screen for the following relation between signal frequency & sweep frequency

(1)  $\frac{f_{\text{signal}}}{f_{\text{sweep}}} = f_{\text{sweep}}$  (2)  $f_{\text{signal}} = \frac{3}{4} f_{\text{sweep}}$

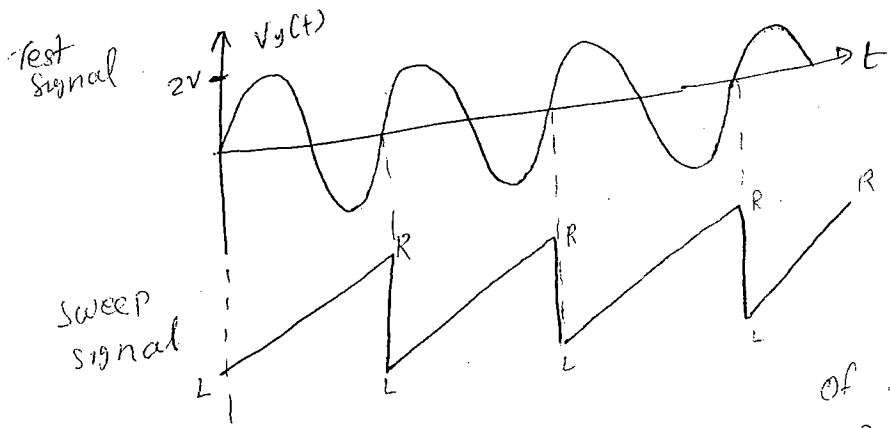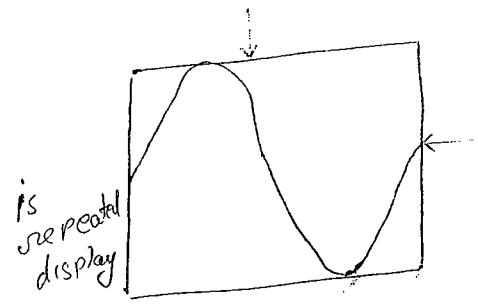- (3)  $f_{\text{signal}} = 1.5 f_{\text{sweep}}$
- (4)  $f_{\text{signal}} = 2 f_{\text{sweep}}$

Assume interval

Soln  $\Rightarrow$  (1)  $\frac{f_{\text{signal}}}{f_{\text{sweep}}} = f_{\text{sweep}}$   
i.e.  $T_{\text{signal}} = T_{\text{sweep}}$





of signal  
 $\rightarrow$  1 cycle Displayed

( $\because \frac{f_{\text{signal}}}{f_{\text{sweep}}} = 1$ )  
 $\rightarrow$  steady display ( $\because$  Same portion of 1 cycle)

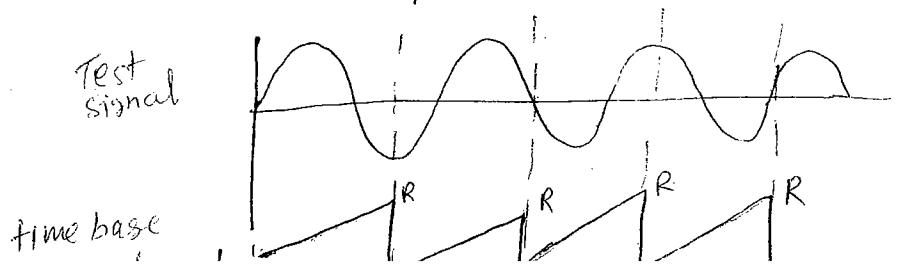(2)  $\frac{f_{\text{signal}}}{f_{\text{sweep}}} = \frac{3}{4} f_{\text{sweep}}$


$T_{\text{signal}} = \frac{3}{4} T_{\text{signal}}$  (75% of signal portion)



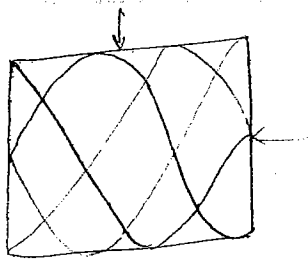



Jumble (∴ different portion of displayed)

Ex :-

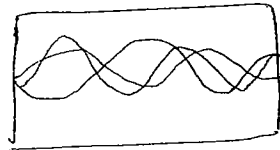


Note → To avoid such jumble i.e. to get a steady display of image the user has to either synchronized by adjusting Time/div. or select proper triggering point

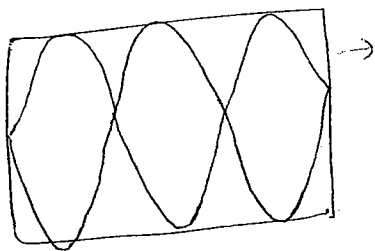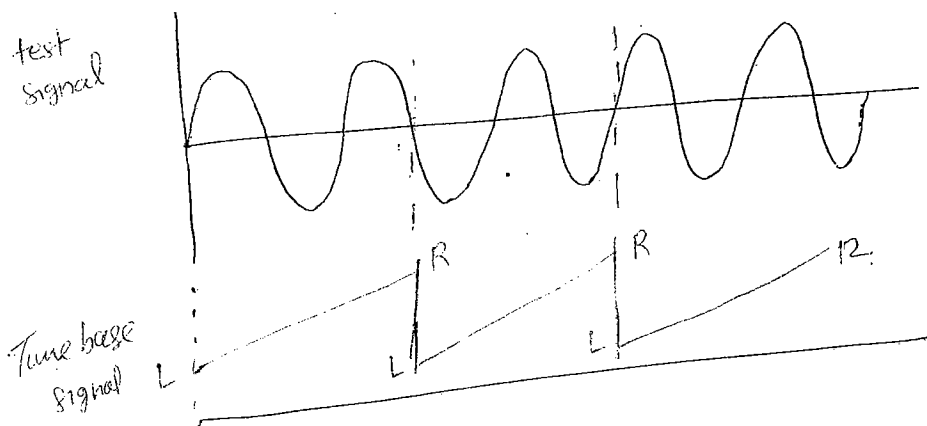③  $f_{\text{signal}} = 1.5 f_{\text{sweep}}$   
 $T_{\text{signal}} = 1.5 T_{\text{sweep}}$




Jumble (Different 1.5 cycle of signal displayed)


Ex :-

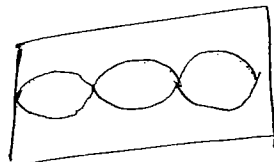

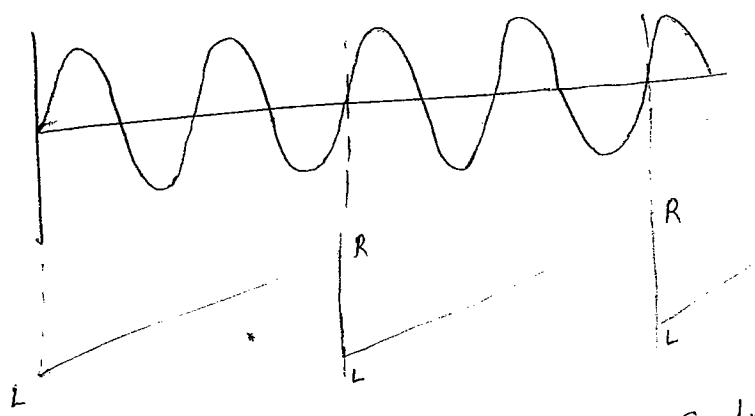④  $f_{\text{signal}} = 2 f_{\text{sweep}}$   
 $T_{\text{signal}} = 2 T_{\text{sweep}}$



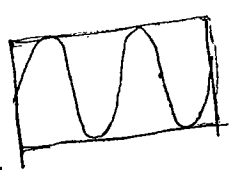⇒ 2 Cycles of signal displayed  
 (∵  $\frac{f_{\text{signal}}}{f_{\text{sweep}}} = 2$ )




> steady display  
 (∵ same 2 cycles are repeatedly displayed)


Que - A single channel analog CRO is used to measure a time varying signal  $2 \sin 100 \pi t$ . Internal trigger source is chosen. Draw the image displayed on the screen for the following case

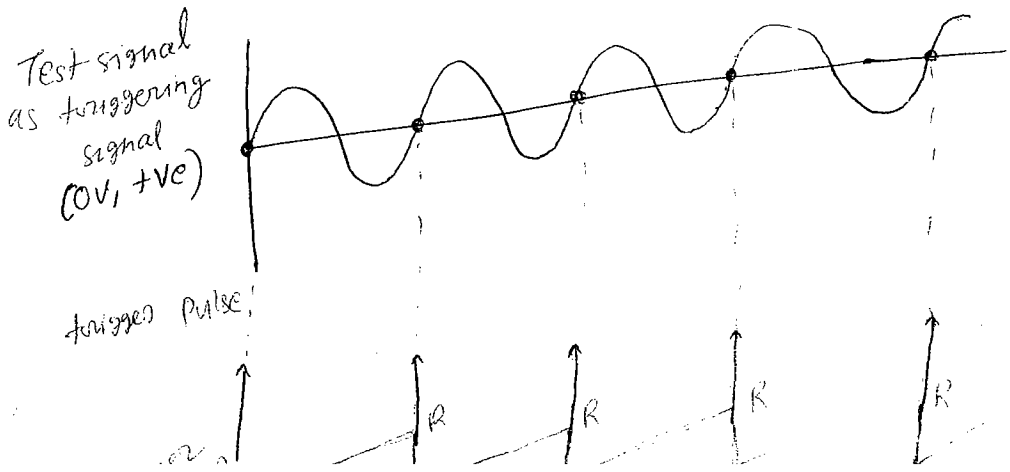- 1)  $f_{\text{signal}} = f_{\text{sweep}}$  & trigger point 0V, +ve
- 2)  $f_{\text{signal}} = f_{\text{sweep}}$  & trigger point 0V, -ve
- 3)  $f_{\text{signal}} = 1.5 f_{\text{sweep}}$  & trigger point 0V, +ve
- 4)  $f_{\text{signal}} = \frac{3}{4} f_{\text{sweep}}$  & trigger point 0V, +ve

soln

$f_{\text{signal}} = f_{\text{sweep}}$  & (0V, +ve)  
 $T_{\text{sweep}} = T_{\text{signal}}$ ,  $t_{\text{V.O.L}} = 0V$ ,  $t-S = +ve$




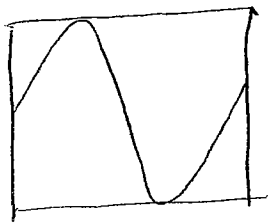


→ 1 cycle of steady image of signal  
 $\left( \because \frac{f_{\text{signal}}}{f_{\text{sweep}}} = 1 \right)$  (Proper triggering)

②  $f_{\text{signal}} = f_{\text{sweep}}$  & (0V, -ve)  
 $T_{\text{signal}} = T_{\text{sweep}}$

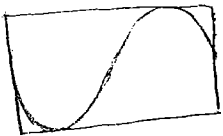→ 1 cycle of signal displayed since  $\frac{f_{\text{signal}}}{f_{\text{sweep}}} = 1$   
 & it will shown from 0V & falling side




Note → For 1:1 ratio & (2V, -ve) ⇒

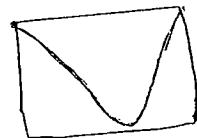


③  $f_{\text{signal}} = 1.5 f_{\text{sweep}}$  & (0V, +ve)


→ For 1:1 ratio & (1V, +ve) ⇒

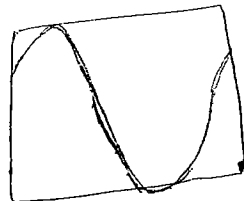

⇒ For 1:1 ratio & (+1V, -ve)

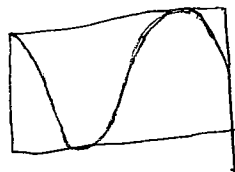


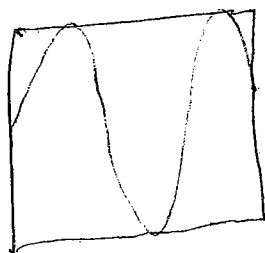
③  $f_{\text{signal}} = 1.5 f_{\text{sweep}}$  & (0V, +ve)  
 $T_{\text{sweep}} = 1.5 T_{\text{signal}}$      $\therefore V.L = 0V$      $t_s = +ve$



→ 1.5 cycle of signal  
 $\left( \because \frac{f_{\text{signal}}}{f_{\text{sweep}}} = 1.5 \right)$



steady image of  
 ↑  
 (∵ Proper triggering)

11/2 19/11

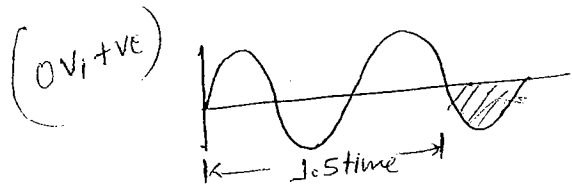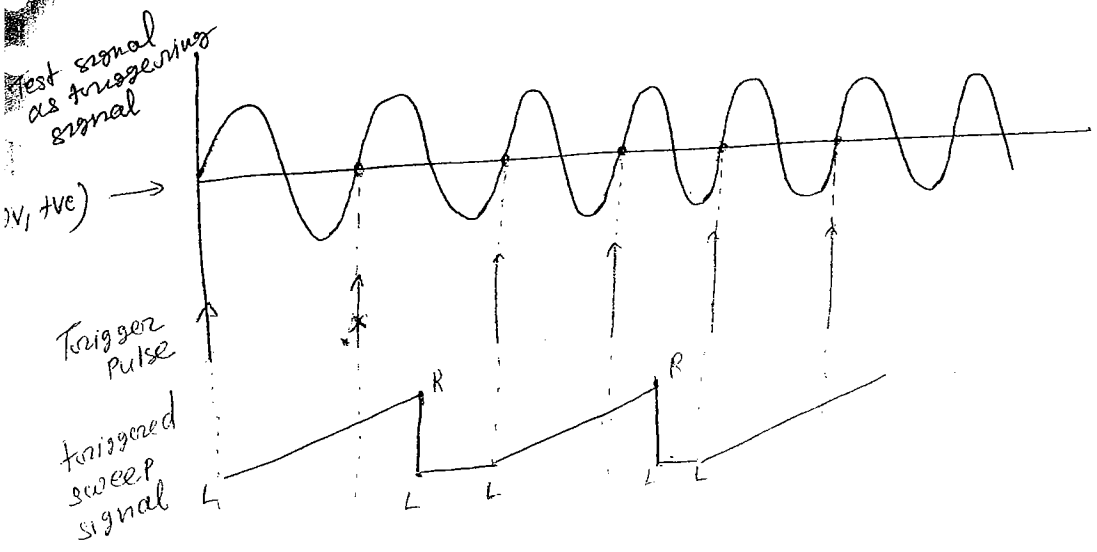

Note:-  $f_{\text{signal}} = 1.5 \times f_{\text{sweep}}$  & (0V, -ve)


(0V, -ve)

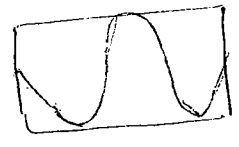
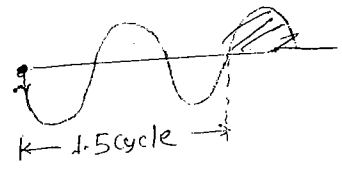


④  $f_{\text{signal}} = \frac{3}{4} f_{\text{sweep}}$  (0V, +ve)


$\rightarrow T_{\text{sweep}} = \frac{3}{4} T_{\text{signal}}$

t.v.l = 0V, t.s. = +ve

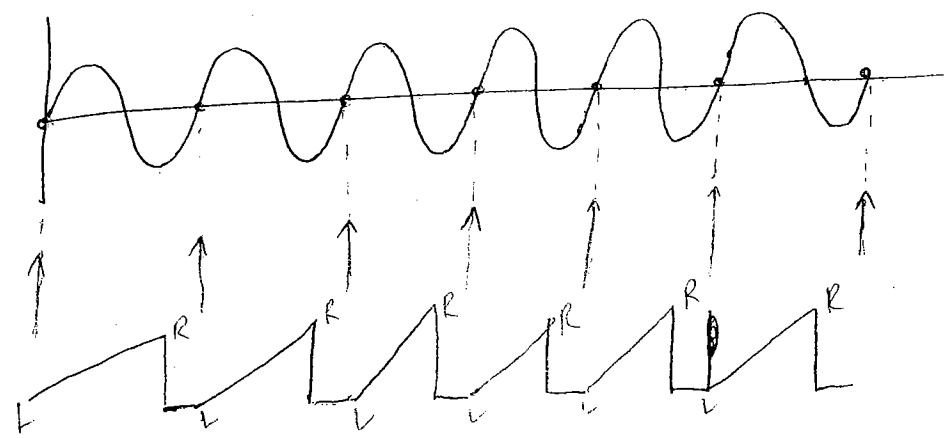

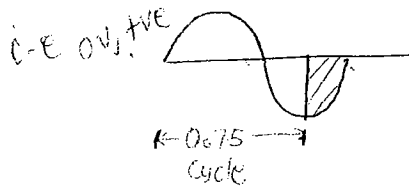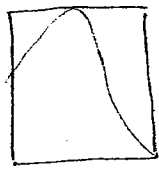

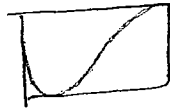
Note -  $\Rightarrow 3/4$  of (0V, -ve)  $\Rightarrow$



$\Rightarrow 3/4$  of (-2V, +ve)  $\Rightarrow$




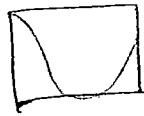$\Rightarrow 3/4$  of (+2V, -ve)  $\Rightarrow$



Not  $\Rightarrow$  Improper triggering always need to rumble where as proper triggering produces steady image of signal on screen.

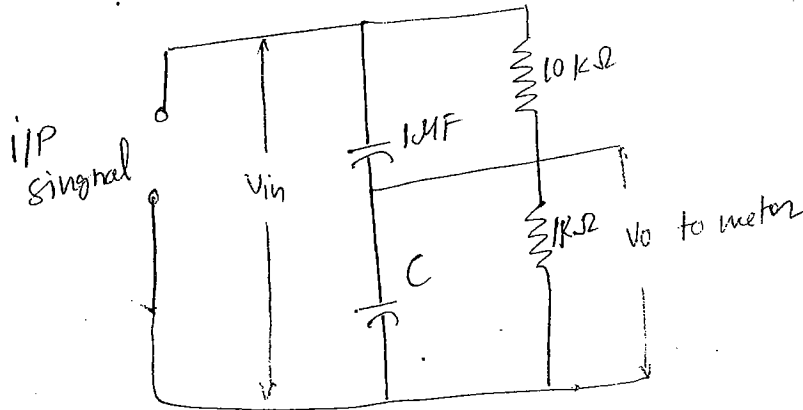Ques  $\Rightarrow$  The arrangement shown in the given figure represents a RC potentiometer for measuring ac voltage what should be the value of C so that  $V_o/V_{in}$  is independent of frequency of the i/p signal



- (a) 10 μF
- (b) 11 μF
- (c) 0.1 μF
- (d) 0.09 μF

\*  $R_1 C_1 = R_2 C_2$  to make  $\frac{V_o}{V_{in}}$  independent of frequency

$10k\Omega \times 1\mu F = 1k\Omega \times C$

$\therefore C = \underline{10\mu F}$




Ques :- An oscilloscope has i/p impedance consisting of  $1M\Omega$  &  $20pF$  in parallel a high impedance + connected to i/p of this oscilloscope has. of  $10M\Omega$  resistance. Thus  $10M\Omega$  resistance

- (a) Need not to be shunted
- (b) should be shunted by  $20pF$
- (c) should be shunted by  $200pF$
- (d) should be shunted by  $2pF$

$$1M\Omega \parallel 20pF$$

$$10M\Omega \parallel \dots$$

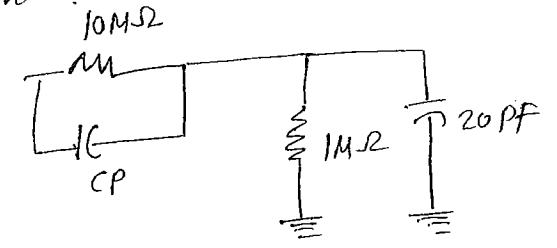

$$R_i C_i = R_p C_p$$

$$1M\Omega \times 20pF = 10M\Omega \times C_p$$

$$\therefore C_p = 2pF$$

Ans  $\frac{V_i}{V_s} = \frac{R_i}{R_p + R_i} = \frac{1M\Omega}{10M\Omega + 1M\Omega}$

$$= \frac{1}{11}$$

Now  $\frac{V_i}{V_s} = \frac{C_p}{C_p + C_i} \Rightarrow \frac{1}{11} = \frac{C_p}{C_p + 20pF}$

$$C_p + 20pF = 11C_p \Rightarrow C_p = 2pF$$

Ans  $\frac{V_i}{V_s} = \frac{1}{11}$

i.e 11:1 probe

- $V_s \downarrow$  by 11 times
- $R_p = 10R_i$  &
- $C_p = \frac{C_i}{10} \dots \rightarrow C_p = \frac{20pF}{10} = 2pF$
- $\uparrow R_{eff} = 11R_i$
- $\downarrow C_{eff} = \frac{C_i}{11}$

Que  $\Rightarrow$  The oscilloscope has an i/p capacitance of 50 pF under resistance of ~~20~~ 2 M $\Omega$  & voltage divider ratio (K) of 10 what are the parameters a high probe.

$$C_i = 50 \text{ pF} \quad R_i = 2 \text{ M}\Omega$$

$$K = 10 \quad \dots \quad = \frac{V_s}{V_i}$$

$$\text{i.e. } V_i = \frac{1}{10} V_s$$

$\rightarrow$  No time attenuation

$$R_p = (10-1) R_i \Rightarrow R_p = 9 R_i$$

$$R_p = 9 \times 2 \text{ M}\Omega \Rightarrow R_p = \underline{18 \text{ M}\Omega}$$

$$C_p = \frac{C_i}{(10-1)} = \frac{C_i}{9}$$

$$= \frac{50 \text{ pF}}{9} = 5.55 \text{ pF}$$

Que The bandwidth of CRO is from 0 to 20 MHz. The fastest rise time which a square wave have in order that it is accurately reproduced by the CRO is -----


$$t_r \times \text{B.W.} = 0.35$$


$$t_r = \frac{0.35}{20 \text{ MHz}} = \frac{0.35}{2} \mu\text{s}$$

$$= 17.5 \mu\text{sec}$$

Que - A CRO with a rise time of 15 nsec measures the rise time of signal as 20 nsec. what is the actual rise time of the signal.

[Pre-requisite]

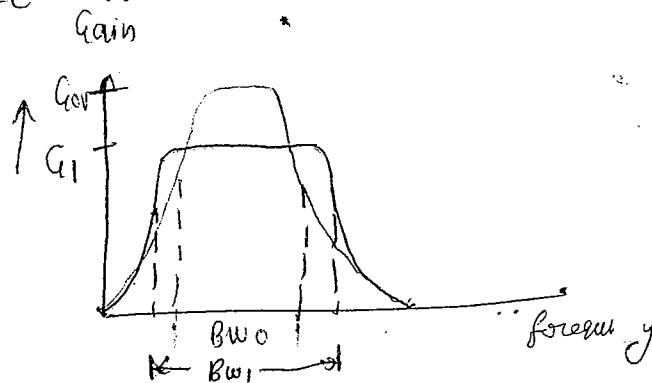

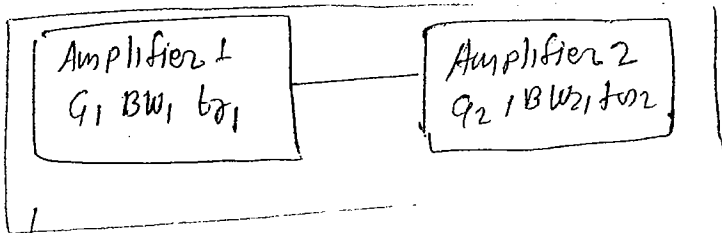


125

$$\uparrow G \times \text{BW} \downarrow \sim k$$

$$\text{tr} \times \text{BW} = 0.35$$

$$G_{ov} = G_1 \times G_2$$

$$t_{or} = \sqrt{t_{r1}^2 + t_{r2}^2}$$

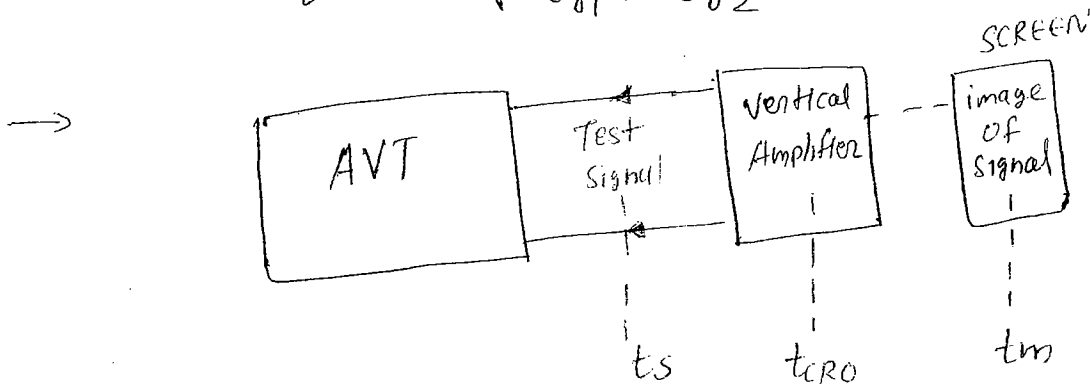

$t_s$  = Actual or true rise time of signal

$t_{cro}$  = CRO rise time (i.e. Vertical Amp rise time)

$t_m$  = measured rise time is overall rise time

$$t_m = \sqrt{t_s^2 + t_{cro}^2}$$

Soln :-

$$t_{cro} = 15 \text{ nsec}$$

$$t_m = 20 \text{ nsec}$$

$$20 \text{ ns} = \sqrt{t_s^2 + (15 \text{ ns})^2}$$

$$t_s = \sqrt{(20 \text{ ns})^2 - (15 \text{ ns})^2}$$

$$= \underline{\underline{13.23 \text{ ns}}}$$

Que  $\Rightarrow$  A CRO has a rise time ~~was~~ of 20 ns. The rise time of a signal measured by this CRO is 25 ns. Find the true rise time of signal.

Soln

$$t_m = \sqrt{t_s^2 + t_{CRO}^2}$$

$$25 = \sqrt{t_s^2 + (20)^2}$$

$$t_s = \sqrt{(25\text{ns})^2 - (20\text{ns})^2}$$

$$t_s = \underline{15\text{ns}}$$

Que  $\Rightarrow$  A CRO is operated with the x & y settings of  $0.5 \frac{\text{msec}}{\text{cm}}$  &  $100 \frac{\text{mV}}{\text{cm}}$ . The screen of CRO is  $10\text{cm} \times 8\text{cm}$ . The cycle of frequency  $200\text{Hz}$  & RMS amplitude of  $300\text{mV}$  is applied to the  $\times$  twice the screen will show

- (a) 1 cycle of undistorted sine wave.
- (b) 2 cycles of undistorted sine wave.
- (c) 1 cycle of the sine wave with clipped amplitude.
- (d) 2 cycle of the sine wave with clipped amplitude.

Given here  $0.5 \frac{\text{ms}}{\text{cm}}$   $100 \frac{\text{mV}}{\text{cm}}$

$10\text{cm} \times 8\text{cm}$  screen

1 cycle or 2 cycle

$$n = \frac{f_{\text{signal}}}{f_{\text{sweep}}} = f_{\text{signal}} \times T_{\text{sweep}}$$

$$= 200\text{Hz} \times \left[ 10\text{cm} \times 0.5 \frac{\text{ms}}{\text{cm}} \right]$$

$$= 200 \times 5 \text{ msec}$$

$$= 1 \text{ cycle}$$

option (b) & (d) are eliminated

Ans either A or C

$$V_{rms} = \frac{V_{p-p}}{2\sqrt{2}} = \frac{NV \times \text{volt/div}}{2\sqrt{2}}$$

$$\therefore NV = 2\sqrt{2} \times \frac{V_{rms}}{\text{volt/div}}$$

$$= 2\sqrt{2} \times \frac{300\text{mV}}{100 \frac{\text{mV}}{\text{cm}}}$$

$$= \underline{\underline{8.48 \text{ cm}}} > \text{Available vertical scale of } 8\text{cm}$$


$\therefore$  Peak points will be applied

So Ans  $\Rightarrow$  C

Que  $\Rightarrow$  A CRO is calibrated for 20V/div & its sweep clt is set for 6msec. 3 complete sine waves with a distance 2.25 divisions between there upper & lower extremities appear on the screen. Find RMS voltage & frequency of signal

$\Rightarrow$  Given data 20 volt/div

$$T_{\text{sweep}} = 6\text{ms}$$

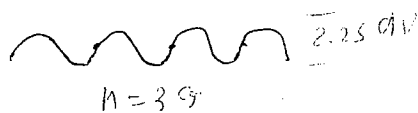

$$V_{rms} = \frac{V_{p-p}}{2\sqrt{2}}$$

$$= \frac{2.25 \times 20 \text{ volt/div}}{2\sqrt{2}}$$

$$= \frac{22.5 \text{ V}}{\sqrt{2}}$$

$$= 15.9 \text{ V}$$

$$\rightarrow f_{\text{signal}} = n f_{\text{sweep}}$$

$$= 3 \times \frac{1}{6\text{ms}}$$

$$= \frac{1}{2\text{ms}}$$

$$= 0.5 \text{ kHz}$$

$$= 500 \text{ kHz}$$

Que - A pulse having rise time of 40 ns is displayed on CRO of 12MHz Bandwidth the rise time of the pulse observed on CRO would be approximately equal to

(a) 40 ns

(b) 83.3 ns

(c) 80 ns

(d) 50 ns

$$\Rightarrow BW = 12 \text{ MHz} \quad t_s = 40 \text{ ns}$$

$$t_m = ?$$


$$t_{cro} = \frac{0.35}{12 \text{ MHz}} = 30 \text{ ns}$$

$$\begin{aligned} t_m &= \sqrt{t_s^2 + t_{cro}^2} \\ &= \sqrt{(40 \text{ ns})^2 + (30 \text{ ns})^2} \\ &= 50 \text{ ns} \end{aligned}$$

Ques 1:


A sine wave voltage is displayed on a CRO its vertical amplifier sensitivity is set at 5 V/cm & time base selector switch is set at a sweep speed of 150  $\mu\text{sec}/\text{cm}$ . The display of sine wave has peak to peak amplitude of 5.4 cm & its two complete cycle or accommodated over 8.0 of horizontal axis. determine the rms value & frequency of o/p voltage.

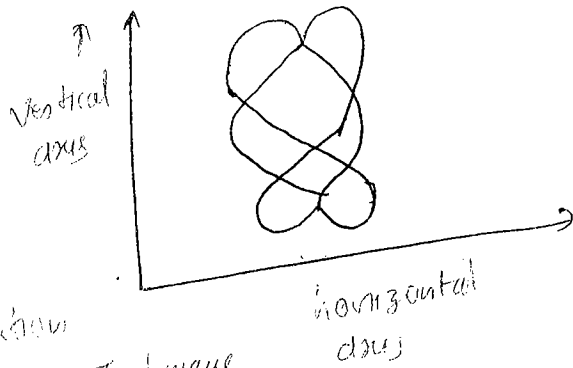Ques. - A screen pattern oscillogram shown in the given figure is obtained when a sine wave of unknown frequency is connected to vertical i/p terminals & same time 600x sine wave voltage is connected to the horizontal i/p terminal of an oscilloscope. What is the value of unknown frequency



- a) 300x
- b) 400x
- c) 600x
- d) 900x

Intersection Technique

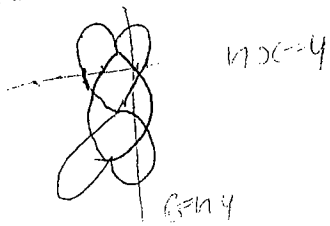


$$\Rightarrow f_y h_y = f_x h_x$$

$$f_y = \frac{f_x h_x}{h_y}$$

$$= \frac{4}{6} \times 600 \text{ Hz}$$

$$f_y = 400 \text{ Hz}$$

Tangent Technique  $f_y = 3$


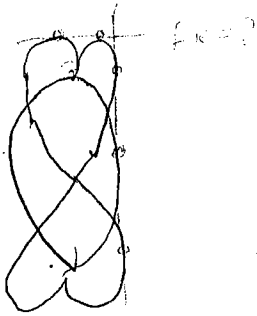


$$f_y = \frac{h_x}{h_y} f_x$$


$$= \frac{2}{3} \times 600$$

$$f_y = 400 \text{ Hz}$$

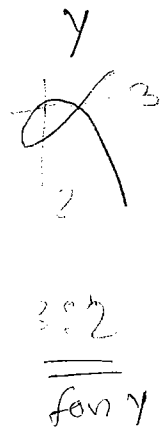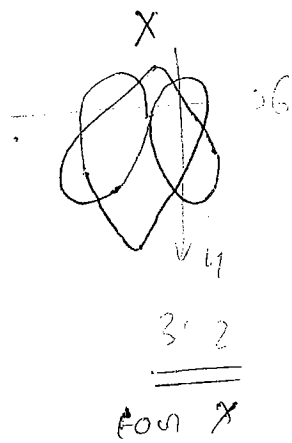Ques. In an oscilloscope 2 Lissajous figure X & Y are observed this indicates the ratio of vertical i/p signal frequency to that of horizontal i/p signal frequency are . . . .



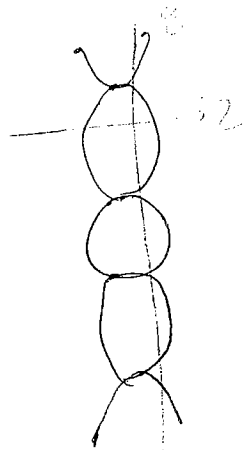Ques. When a CRO is operated in X-Y display in the below given Lissajous figure is displayed the screen what is the horizontal to vertical



$$\frac{f_y}{f_x} = \frac{n_x}{n_y}$$

$$= \frac{2}{8}$$

$$\frac{f_y}{f_x} = 1/4$$

$$f_y : f_x = 1 : 4$$

$$f_x : f_y = 4 : 1$$

Vertical to Horizontal frequency  
Horizontal to vertical frequency

Ques.  $\Rightarrow$  When a sinusoidal signal of 220V, 50Hz Pass on CRO a vertical deflection 2cm at a particular setting of the vertical gain control what would be the value of voltage to be applied to produce a deflection of 3cm  
3 vertical gain



\*  $\frac{\text{Volt}}{\text{div}} \rightarrow$  Deflection factor Df (voltage gain)

$$S = \frac{\text{div}}{\text{Volt}}$$

$$S = \frac{d}{Vd}$$

$$Df = \frac{Vd}{d}$$

$$220V \rightarrow 2cm$$

$$Df = \frac{220}{2}$$

$$= 110V/cm$$

For 3 cm deflection

$$Vd = 3cm \times 110V/cm = 330V$$

Ques: A CRT has deflection factor of 18 V/cm the amount of deflection seen on the screen for deflecting voltage ~~18~~ 54 V

$$Df = 18 V/cm \quad Vd = 54 V$$

$$d = \frac{54}{18 V/cm} = 3 cm$$

Ques: EEE 2005 Which of the following measurement can be made using Lissajose figure






- 1) frequency
- 2) phase difference
- 3) Time ~~ratio~~ <sup>interval</sup> between pulse
- 4) pulse width
- 5) fundamental & higher harmonic component

Ans  $\rightarrow$  1 & 2

Ques: Beam of electrons in CRT eliminates because of

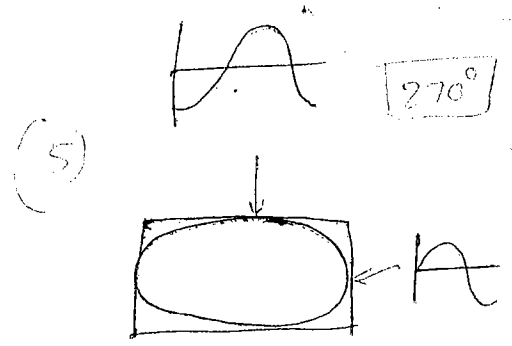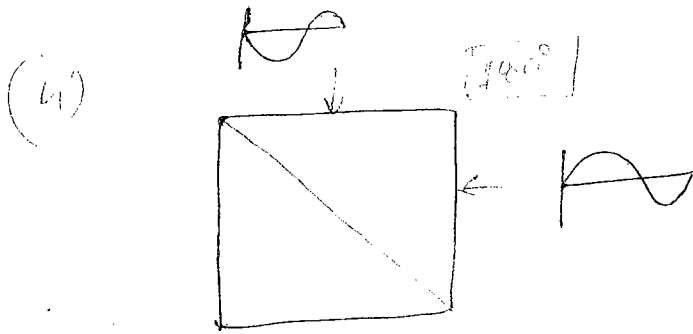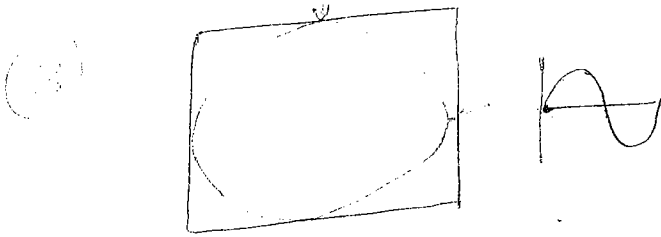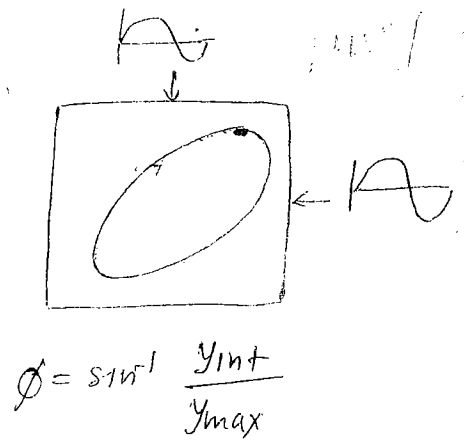
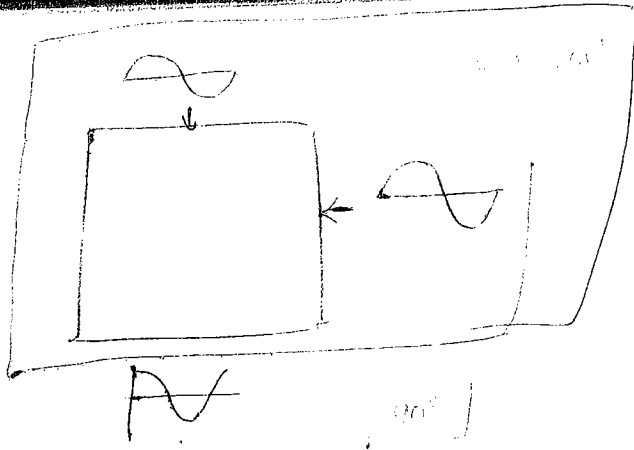
- (a) 2nd emission
- (b) ~~inertia~~ Thermionic emission
- (c) diffusion
- (d) ~~post-acceleration~~ ~~acceleration~~

Ques: 1000 Hz sinusoidal voltage is connected to both X & Y on CRO which of the following waveform is ~~seen~~ seen on screen of CRO





$$90^\circ < \phi < 180^\circ$$


$$0^\circ < \phi < 90^\circ$$

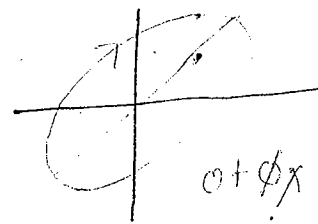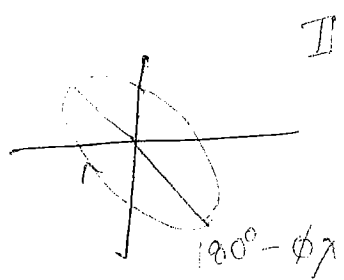

$$180^\circ < \phi < 270^\circ$$

$$270^\circ < \phi < 360^\circ$$

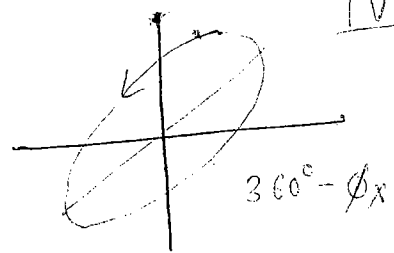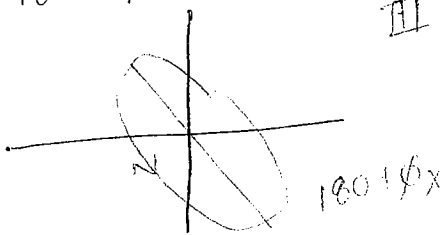

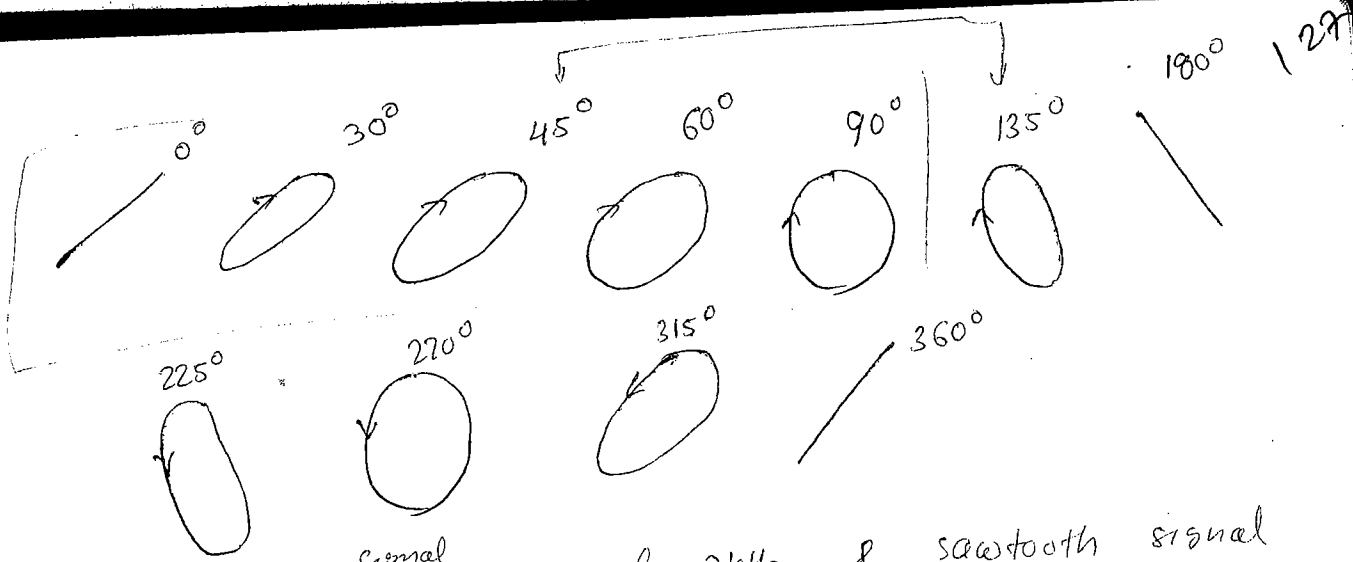

Ques - A sinusoidal signal of frequency  $2\text{kHz}$  & sawtooth signal of frequency  $1\text{kHz}$  applied to Horizontal & Vertical i/p of a CRO the waveform display on the screen will be.

