

POWER ELECTRONICS

~~Diode~~

Thyristor

Diode - uncontrolled device

Thyristor - controlled device

- parameter controlled is voltage, current, power
- (They are dependent parameters)

Diode

- Anode

- Cathode

A @ high potential w.r.t C = conduction

Thyristor

Anode (at high potential w.r.t C) = 2nd anode w.r.t

allow the conduction unless for gate pulse is given

i.e. " instead of ^{conduction} voltage after applying FB can be controlled "

Q17

→ Diode is a uncontrolled device

→ Thyristor is a controlled device, where the conduction of

conduction can be controlled after applying the forward

voltage. due to this output voltage, current, and

power may be controlled.

reference for SCR and thyristor



Thyristor :- Family of devices having PNPN structure.

*** SCR :- First member of Thyristor family

↑
most of our discussion

8/1
"Thyristor is the name given to Family of devices which will be used in power control application having a common structure PNPN".

SCR (SILICON CONTROLLED RECTIFIER)

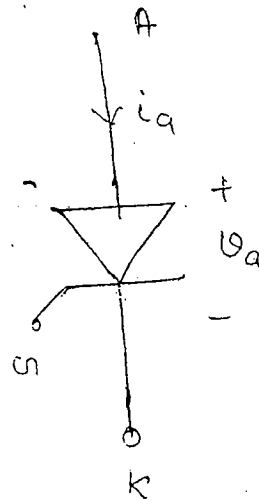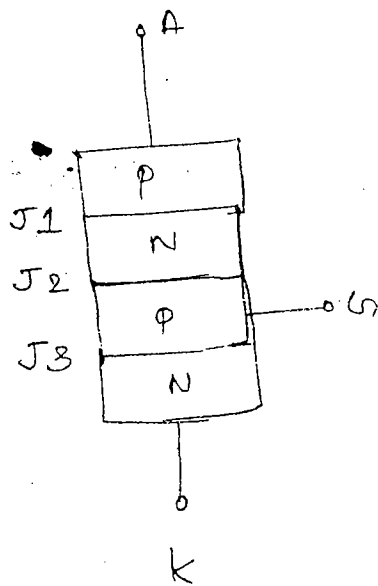

- Four layers, 8 terminals, Anode - External P.

K - External N, Anode P → Cathode

- Three junctions.

V_a = Anode voltage w.r.t cathode

I_a = Anode current (current through anode device)
= device current

Anode circuit = main circuit

Cat circuit = supporting circuit.

4
SCR is a 4 layer, 3 term., 3 Jn, PNPN device!

Characteristics of SCR

3 types

1) static 2) dynamic 3) gate characteristic.

Static characteristics of SCR

V_{BO} = Forward Break over Voltage.


V_{BR} = Reverse Break over Voltage.

REVERSE LEAKAGE CURRENT

Two parts

1) Forward char.

2) Reverse char.

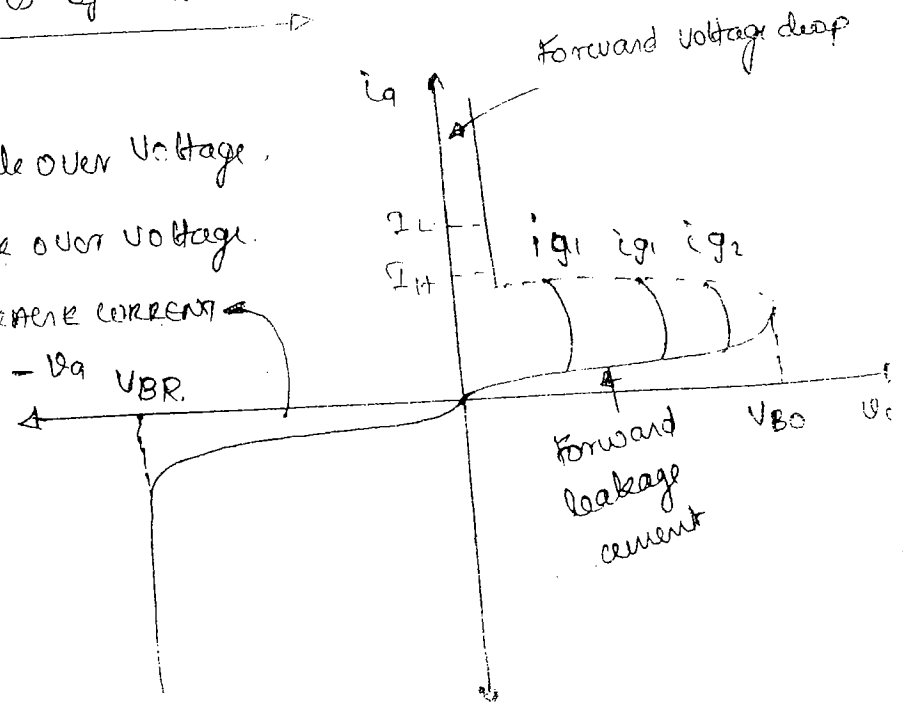

Forward characteristics

- Required operation is happening here
- most focus is here.
- Always we need SCR in Forward, we never operate in Reverse

⇒ Apply Forward V.


- Anode High & Cathode

Consider - Cathode = 0

- Anode = 100V

J_1, J_3 - F.B

J_2 - R.B

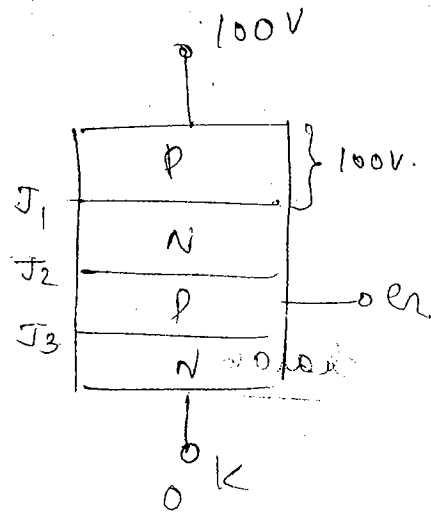

- 100V - distributed across 4 layers.

- I layer - 100V, II layer - definitely less - consider

70V, 3rd layer - 30V, N = 0 (Electrical connection)

$$J_2 \text{ (N 70 - P 30)} = \text{R.B}$$

$$J_1 \text{ (P 100 - N 70)} = \text{F.B}$$

$$J_3 \text{ (P 30 - N 0)} = \text{F.B}$$

→ SCR TURNED 'ON' FORWARD CONDUCTION STATE

⇒ The voltage across supposed to be 'zero',

⇒ Steady state voltage drop
⇒ Conduction voltage drop
⇒ Forward voltage drop } Very less.

⇒ SCR is rated for 100A, if it is conducting, the

~~the~~ SCR current through the SCR will depends up on

LOAD, LOAD CURRENT is passing through the

SCR (Warning is it should not cross 100A, if it crosses

the SCR will damage). Current doesn't depend on Rating.

Q In Forward conduction state SCR is equivalent to

closed switch, the voltage across the device is forward

voltage drop or steady state voltage drop. The current

through SCR is equal to load current.

Supply voltage available = 230, 400V or 440(3φ)
(1φ)

We need to get 1000V to turn ON, again we need a

TRANSFORMER (undiscoverable requirement).


We should be able to turn ON Practically if it

requires voltage other than the supply voltage

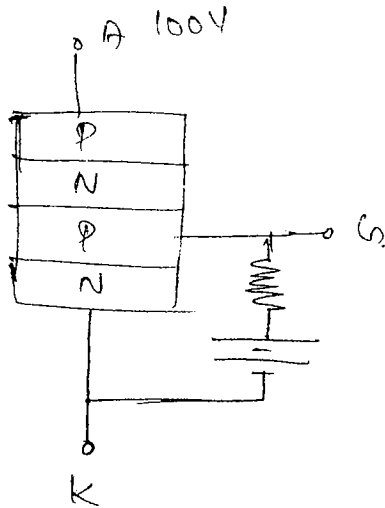2) Gate triggering ***

- Method to turn ON SCR, avoiding transformer as in voltage triggering method.

- Circuit diagram for gate triggering method.



- here also

1) Apply Forward voltage supply voltage (100V)

2) Voltage @ K = 0.

3) $J_1, J_3 - F.B$, $J_2 - R.B$, we need to cross J_2 junction


- Any R.B PN will have depletion layer.

- width of depletion layer more, Applied $V \uparrow$
less, Applied $V \downarrow$

- Depletion layer - (depleted by the charge carrier)

They will have IMMOBILE IONS
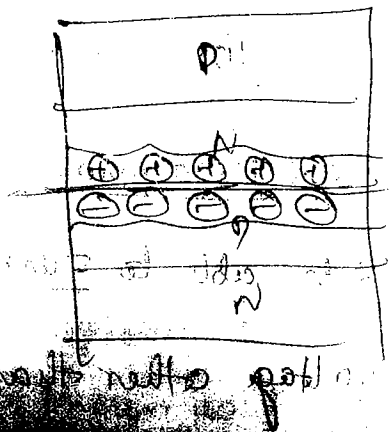
$$\left\{ \begin{array}{l} P = -ve IONS \\ N = +ve IONS \end{array} \right\}$$



a) Potential barrier


Conduction in diode only across potential hill.

It gives the sufficient energy to charge carriers to cross potential hill.

* \Rightarrow 2) As the potential barrier (width of depletion region decreases) with the increasing energy we are able to cross the potential hill.

We are applying a reverse potential at (C).

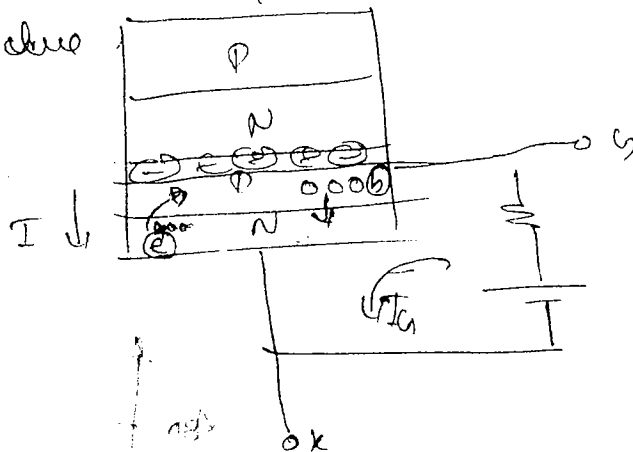Current is happening due to movement of charge carriers in our reverse direction.



Whenever holes are moving, (Random direction)

There is a chance to touch the ions in (N) IONS.

Now Recombination takes place

Again ION \rightarrow Atoms \rightarrow No IONS decrease at the

depletion layer \rightarrow width of depletion layer decrease.

(Q) 4

DA Forward voltage is applied across anode to cathode, terminals due

to which a gate current flows. The current is due to movement of

charge carriers, width of the depletion layer decreases

due to Recombination being taken place on the depletion layer.

energy carriers are able to cross the junction with existing energy hence the device starts conduction."

- After applying, gate bigger, graph changes.

here we took three currents i_{g1}, i_{g2}, i_{g3}

- i_{g1} shown in the graph shows, low voltage required for the SCR to turn ON, if no i_g , $V_{BO} - E_s$ required

$$\Rightarrow i_{g1} > i_{g2} > i_{g3}$$

Conclusion

\Rightarrow For higher values of gate current, the Anode voltage required is LESS.


\Rightarrow Anode w.r.t gate current

Characteristics

$i_g \rightarrow$ increases

$V_a \rightarrow$ Anode voltage
decreases

\rightarrow supplied voltage

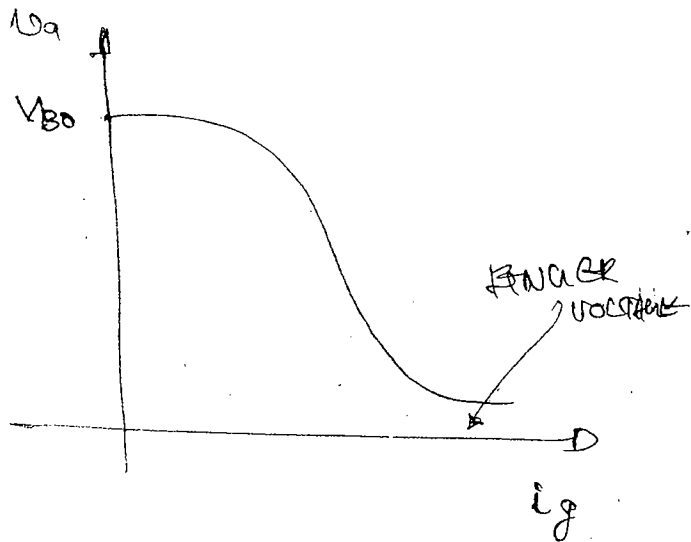

\Rightarrow i_g very high, '0V' Not possible to turn ON SCR

\Rightarrow NO supply, means close the switch, open switch NOT make any difference

FINGER VOLTAGE =

“ If higher values of gate current's employed, then Anode voltage required to turn ON the SCR, decreases, A minimum Forward voltage is required to TURN ON the SCR for any value of gate current and it is known as FINGER VOLTAGE.

Suppose

Supply Voltage = 100V

Find I_g required - Trigger I_g
- I_{g1}

1 ϕ	3 ϕ
= 230V	= 400
= I_{g2}	= I_{g3}
TURN ON	TURN ON

50V dc - supply = $n I_{g1}$ → TURN ON

Advantage of gate triggering

“ We are able to TURN ON SCR for a Range of voltage by applying the appropriate gate current

“ Gate triggering allows the turn ON of SCR for a range of voltage by applying the appropriate gate current”

3) THERMAL TRIGGERING

“ As the name indicates, heat gives the required excitation for the charge carrier to cross J_s , hence conduction starts.

Applied F voltage J_1, J_2 - F.B
 J_3 - R.B

“ In this method SCR is heated up due to which energy levels of charge carrier increases, as a result they are able to cross the

... the carrier will make the conduction"

4) LIGHT TRIGGERING

CONDT - requirement

- Intensity of the light should be high.
- Excitation is provided by light \rightarrow heat




Special app: LASCR [water]

(8) "An intensified light beam is focused on SCR, which makes the charge carriers to be enabled as a result, they are able to cross the junction (J_2) and makes the conduction".

23/12/00

20

5) $\frac{dV}{dt}$ triggering ***

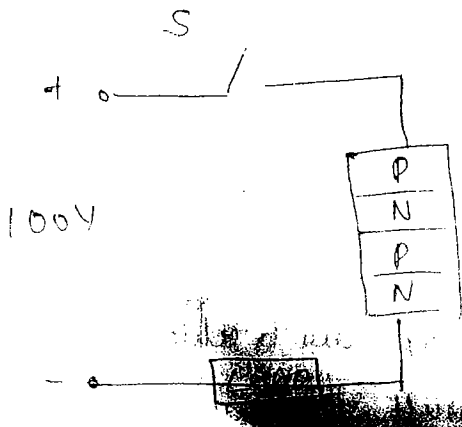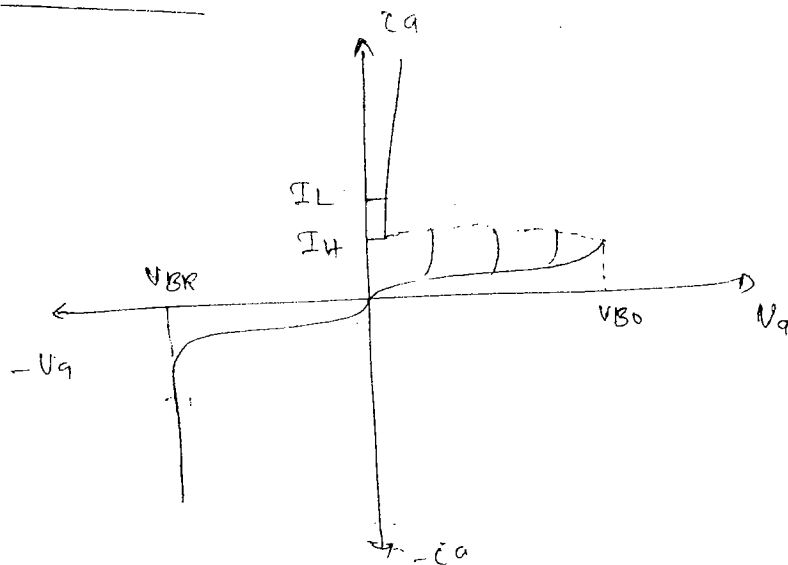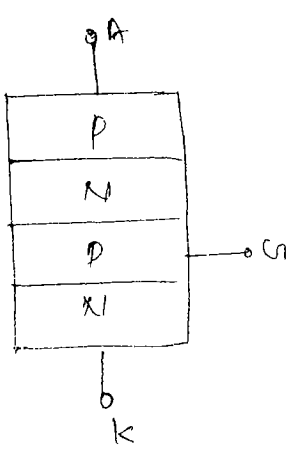

First differentiate this method from others

1) all done 1-4 are externally triggered mechanism

⇒ 2) here INTERNALLY mechanism.

- one coupled F.V here SCR by its own will start the conduction.

- Applying F.V.

Conduction procedure -

→ S = OPEN, voltage across the SCR = 0 = V_1

→ S = CLOSED, voltage across the SCR = ~~0~~ = $V_2 = 100$

→ 0 → 100V ⇒ growth occurs.

here $dt = 1 \text{ ms}$ (Assume time taken from 0-100V).

→ F.V. applied J_1, J_2 - FB, $J_3 - RB$, this R.B

Junction C.F.B junction of capacitance

→ F.B Jn C = diffusion capacitance

R.B Jn C = transition capacitance

- generally Junction capacitance = $1 \mu\text{F} = J_2$

- C → change in stored charge

⇒ $i = C \frac{dV}{dt}$ [capacitance ~~is~~ $\frac{\text{charge}}{\text{voltage}}$]

$$= \frac{1 \times 10^6 \times 100 - 0}{1 \times 10^3}$$

~~***~~ $I = 0.1A$ \Rightarrow If this current is more than ~~value~~

current \Rightarrow Conduction starts (width of depletion layer

decreases, charge carriers cross the barrier)

\Rightarrow Making this way TURN ON SCR is called $\frac{dV}{dt}$ triggering method.

Q8) While applying the Forward voltage sometimes SCR

starts conduction. The junction capacitance subjects to rate of

change of voltage ($\frac{dV}{dt}$) results in to a charging current

($I = C \frac{dV}{dt}$). If the value of the current is more than ~~value~~

gate current of SCR, then it starts conduction."

Not preferable why?

- Control action is not there.

- It is not advised to turn ON this SCR.

$I = 0 \rightarrow$ Not possible

$I = 0.1A \rightarrow$ undesirable \rightarrow

$I = 0.00001A \rightarrow$ desirable

\rightarrow to avoid $\frac{dV}{dt}$ triggering

critical value $\frac{dv}{dt}$ should be of lower value (protection from uncontrolled conduction)

Due to lack of control across $\frac{dv}{dt}$ triggering is to be avoided. It is possible by making lower value of $\frac{dv}{dt}$.

SCR TURN ON - PRECISE METHOD - GATE TRIGGERING

$I_L, I_H \rightarrow$ definition of Anode current

$I_L \rightarrow$ Turn ON process (F.B \rightarrow F.C)

$I_H \rightarrow$ Turn OFF process (F.C \rightarrow F.B)

= How much time gate signal required to apply?

Until Anode current = I_L .

(8)

Latching current (I_L)

= "It is associated with turn ON process"

= "It is the minimum value of current above which Anode current rises for the reliable turn ON of the SCR"

~~It~~ = "gate signal should be applied, along with SCR till Anode current rises above the latching current"

Holding current

= "It is associated with turn OFF process"

= "It is the minimum value of current below which Anode current falls during OFF of the SCR"

- It is useful to apply the reverse voltage for ~~to~~ ^{to} complete the completion of turn OFF process.

Conclusion

$$I_L > I_H \text{ (always) } \underline{\text{***}} \text{ [IESQ]}$$


Empirical Formula

$$\frac{I_L}{I_H} = 2.5 \text{ to } 3$$

Q81 " Always latching current is more than holding current "

Reverse characteristics

- Cathode is more than anode potential

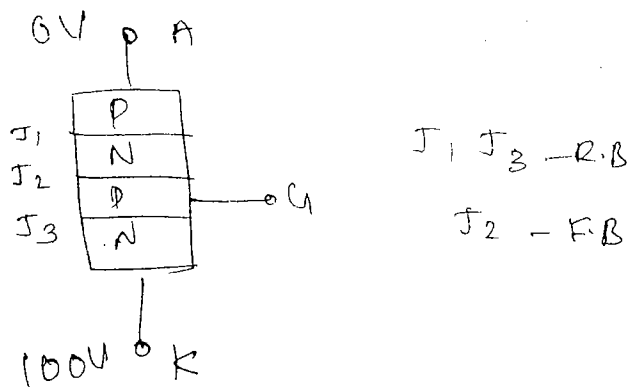

- Reverse leakage current at Reverse blocking state
(current at NC state) (Non conductivity state)

- Reverse conduction occur = Reverse Break over Voltage
= V_{RR}


Q82 " In Reverse Blocking state J1 J3 are R.B but J2 is F.B "

The amount of R.V required to allow the conduction in Reverse direction is known as Reverse break over voltage.

Consider

- No load - only - applied voltage

- If there is load - the SCR chara bends

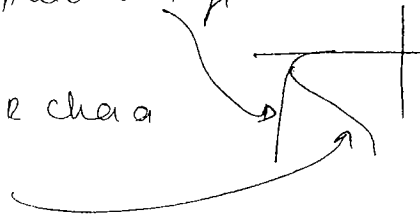

- (50-60V) voltage drop across SCR, for an 100V power loss, we can tolerate, & why we are not using SCR for Reverse conduction mode?

② " The Reverse voltage drop and power loss are more, so hence it is not preferable to utilize, in Reverse conduction state."


DYNAMIC OR SWITCHING CHARACTERISTICS OF SCR

$$t_{ON} = t_d + t_r + t_s$$

$$t_d = \text{delay time} \\ = 0.9 I_g - 0.1 I_a$$

$$t_r = \text{Rise time} \\ = 0.1 I_a - 0.9 I_g$$
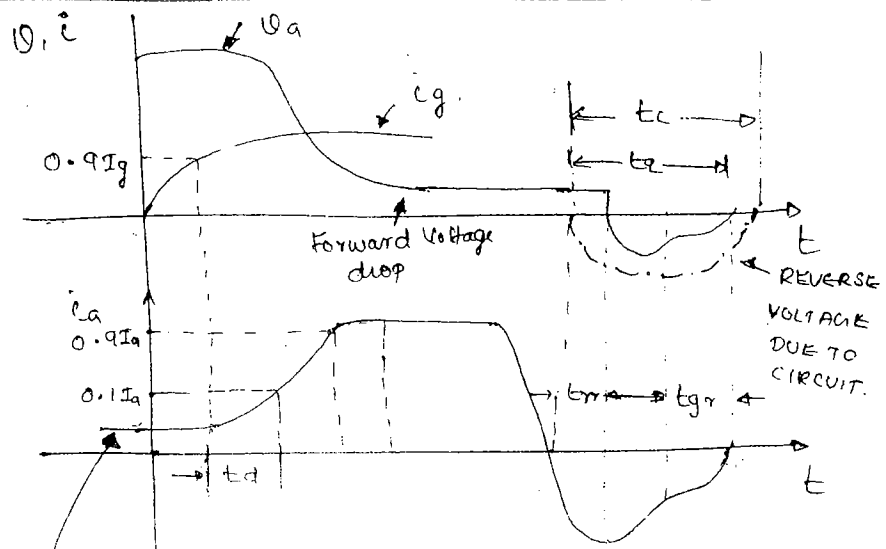
$$t_s = \text{spread time} \\ = 0.9 I_g - I_a$$



Forward leakage current

$$\frac{t_r}{t_f} = \text{Rise time}$$

→ static class - never numbered term

⇒ dynamic → how much term - voltage decreases
- current increases.

→ here everything constant term

⇒ Two parts $\left\{ \begin{array}{l} \text{TURN ON} \\ \text{TURN OFF (Fwd)} \end{array} \right.$

Consider

D Forward Blocking state

SCR

$V = \text{Applied } V.$

$I = \text{back current}$

TURN ON → triggering $\left\{ \begin{array}{l} \text{Voltage? voltage?} \\ \text{current?} \end{array} \right.$

- voltage CAUSE, current = EFFECT

- gate voltage applied, $I_a \uparrow$ (takes term)

- gate response time - current taken to reach I_g

- No validity in turn on process

- SCR, hence avoided on turn on time

- TURN ON → definition, will affect, we cannot start

from the instant, when we applied gate voltage.

divided Turn ON - delay time (10% Ia → 90%)
 - rise time (10% Ia → 90%)

①
TURN ON TIME: It is the time taken by the SCR, from the instant of 90% Ig to steady state value of anode current.
 (load current)

→ SCR as CHARGE CONTROLLED DEVICE

- charge carriers should be allowed to junction as to depletion layer to start the conduction of SCR

- charge required to turn on the SCR

- support $Q = I \times t$

(micro) $1 \mu C = 1 A \times 1 \mu s$ $11 \mu C$ 2A, 0.5 μs
 \uparrow 5A, 0.2 μs
 required

$$Q = I \times t$$

$t =$ turn ON time of SCR.
 (should not be more than rated current of SCR)

⇒ higher value of current, I will give reduces the anode voltage of junction to break down.

②
SCR is considered to be charge controlled device by employing higher values of gate current, turn ON time can be decreased hence the device becomes faster.

LES W > UNIFORMITY ~~A A A~~


- Turn ON - Formation of local hot spots ~~X X X~~

- how? influences on process?

consider

- during turn ON process

- cathode surface

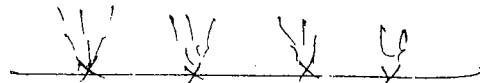

X → areas subjected to high temp?



leads to change of more concentration of charge

causes compared to other area (current density ↑, power

loss ↑, heat generated ↑, temperature ↑ compared to

others) [NON UNIFORM CURRENT DISTRIBUTION

OVER CATHODE]

- NON UNIFORM Distribution -

1) Spread of charge carriers

- requires $t_{\text{rise}} = \underline{\underline{1 \mu s}}$

2) Rate of Rise of Anode current

Rise of Anode current - 100A - rate of } → takes 100 μs
load current - 100A

- Turn ON state -

- 1ns - speedy out of charge carriers

- 100ns - to reach next end current

- See current 1ns - current in device

- 1A \rightarrow linear variation

2-3A \rightarrow Non linear variation

\checkmark $I \downarrow \rightarrow$ No of carriers less \rightarrow CHANCE OF UNIFORM CHARGE CARRIER SPREADING.

1ns < 100ns

\Rightarrow When speedy time > to reach next end time \times
100ns > 1ns \times


\Rightarrow Speedy is NOT COMPLETED.

- FLOODING OF CHARGE CARRIERS

- HOT SPOT FORMATION

Hotspot formation \rightarrow depends on speedy time of charge carriers. (t_1)

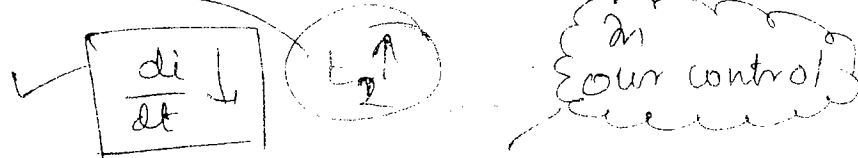Rise of diode current \rightarrow depends on $\frac{di}{dt}$



our requirement $t_1 < t_2$ ($\frac{di}{dt}$)

CONCLUSION

~~$\frac{di}{dt}$ should be less than v~~

(3)

" during the turn ON process LOCAL HOT SPOT will be formed if $\frac{di}{dt}$ is more than the spreading velocity of charge carriers. The local hot spot should be formed due to the ~~NON~~ UNIFORM distribution of charge carriers over the cathode surface. To avoid the formation of local hot spot, the number of carriers at the time of turn ~~on~~ spreading of carriers process should be of lower value, it will facilitate uniform spreading of the charge carriers. ~~to avoid~~

(4)

Note:

*> To avoid the formation of local hot spot rate of rise of anode current ($\frac{di}{dt}$) should be more less than spreading velocity of charge carriers, and practically the value should be lower value.


Q) How to make $\frac{di}{dt}$ lower?

C faster on SCR protection

Practical value of $\frac{dv}{dt}$ should be lower to make controlled conduction.

5a) In which interval of the cycle (Reverse local hot spot MOC-1).

- when the power loss more

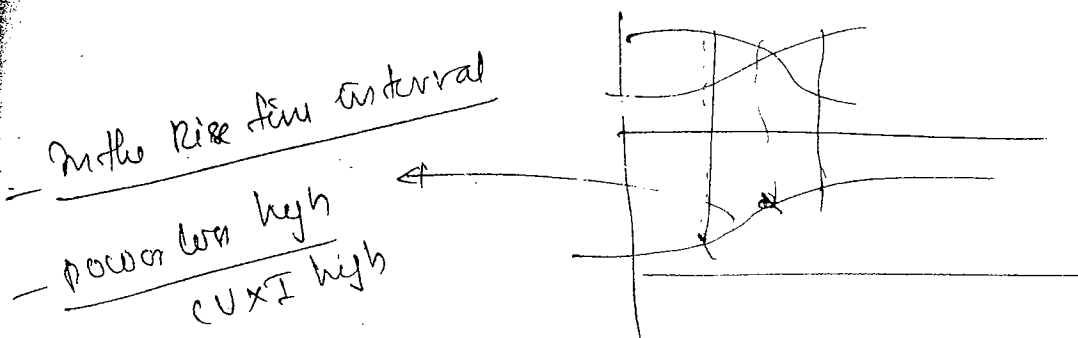

or a local hot spot dominantly occurs during the rise time interval as the power loss is more on that interval.

10) Hot spot problems and effect?

1) - degrade the performance of device

2) - life span will decrease. (useful life span)

H.W local oscillator makes Notes. ***

or

Local hot spot may affect the device, in the following manner

- power loss increases.

- degrade the performance of the device.

- useful life span of the device decreases.

2) TURN-OFF PROCESS

- TURN-OFF \rightarrow current = 0 (SCR)


- how to bring current = 0?

- It is NOT device brings $current = 0$

- It is the responsibility of a circuit to bring the $current = 0$.

- Consider -

- by circuit mechanism $I = 0$

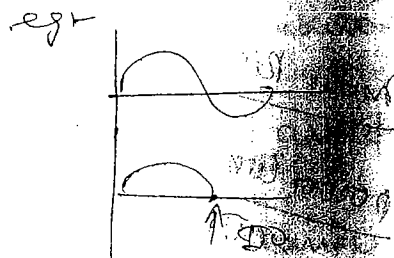

(Value of $A < 1$)

- See the charge graph -

$\triangleright I_a = 0$

= still charge carriers = Energy

\uparrow F.V \rightarrow with this energy conduction can

be again started.

1) Remove the energy ^{had} ~~passed~~ by the charge carrier.


(trap the energy carriers from charge carrier)

Recovery Energy

$\triangleright \Rightarrow$ Removing the carrier

$\triangleright \Rightarrow$ Recombination (Reduce energy of charge carrier)

Obt

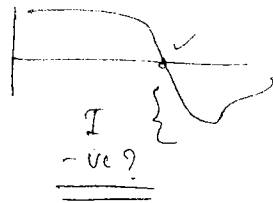


- This cond is not, Reverse conduction cond, it is not possible to maintain or sustain the conduction, it is happening only for a momentary/transient time. after some time I will come to zero.

⇒ Why I goes -ve?

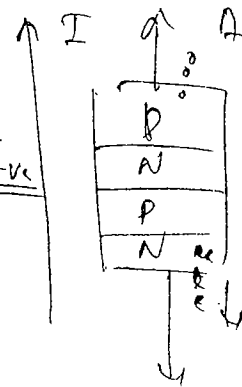a) - Removal causes - External layer

- ~~Recombination~~ - ~~Internal layer~~

- While removal the carrier cond goes to -ve side



b) Inner layer - Recombination

- Reverse voltage applied.

⇒ Recombination in d.

↳ also helpful in remove the carrier by attracting the carrier.

⇒ Why we apply Reverse voltage ✓

↓
SCR Regains Blocking State

↓
No conduction with TRIAC

211
The following conditions are to be satisfied for the turn OFF of the SCR

▷ Reduce the Anode current below the holding current;

▷ Apply the Reverse voltage, for sufficient duration, to remove the energy possessed by the charge carriers.

→ a) The reverse voltage is useful to remove the carrier from external layer

→ b) again Reverse Voltage helps in encouraging Recombination in inner layer

u
- During turn off = Reverse Recovery time, External layer will be recovered

- During gate recovery time = t_g, inner layer will be recovered

- At the end of turn OFF process SCR should Regain Blocking state.

(Q) How to generate Reverse voltage? (Commutator circuit)

- I → Inductor — $L \frac{di}{dt} = V$

- must load = Inductive.

⇒ η load = Not Inductive.

⇒ Mathematically ideal SCR → change to have

SELF INDUCTANCE

NO
guarantee

→ In practical circuit, we have special circuit, to apply

the Reverse voltage, which will quench the Reverse voltage

and turn OFF SCR

(Always SCR will be with this circuit).

Q3) "A special circuit can be employed to apply the reverse voltage during the turn OFF process and it will be called as commutation circuit"

Q4) How much time we should apply Reverse voltage?

- see the char 2 graph.

- $t_c > t_q$

Q5) If $t_c < t_q$ what happens?

- Required - COMS

- Applied - SMS

- At the end 'SMS' again F.V comes across the SCR

again and thus trigger SCR starts to conduction

(commutation failure)

t_q = DEVICE TURN OFF TIME

It is the time required by the device to complete its turn OFF process

t_c CIRCUIT TURN OFF TIME

It is the time ~~required~~ given by the circuit to complete for SCR to complete the turn OFF process

\Rightarrow always $t_c > t_q$

\Rightarrow If $t_c < t_q \rightarrow$ Then the device will be failed its COMMUTATION, Looses the control action.

1) INVERTED GRADE SCRS

- Devices with faster turn OFF time $t_q < 50 \text{ NS}$

known as INVERTED GRADE SCRS

- Applications: 1) Inverters
- 2) Choppers

2) CONVERTED GRADE SCRS

- Devices with slower turn OFF time $t_q > 50 \text{ NS}$

known as converted grade SCRS


- Applications: 1) Phase controlled rectifiers
- 2) AC voltage controller

3-5

6-8

26/12/10

CHARACTERISTICS OF SCR.

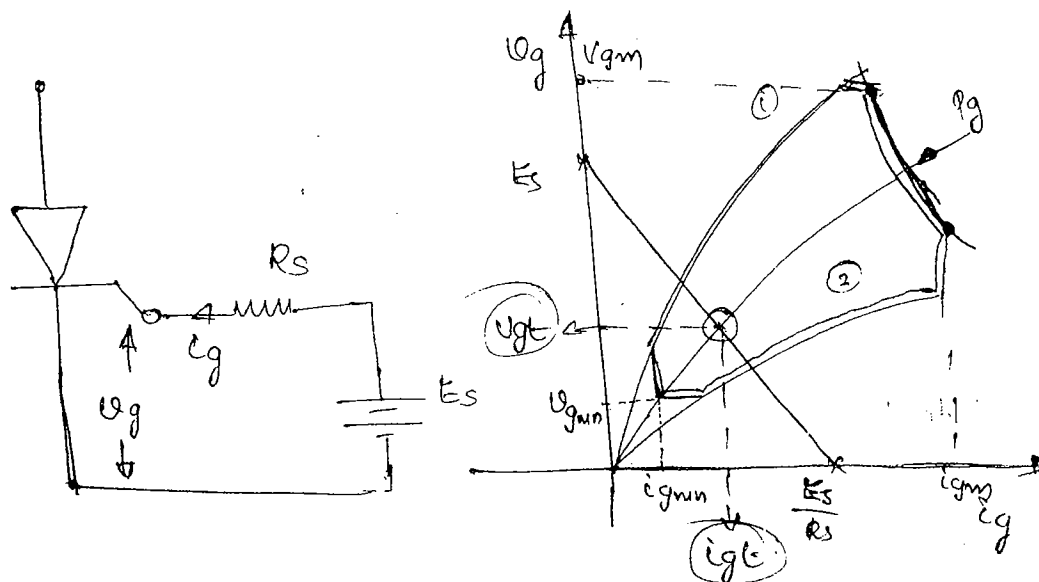

Gate characteristic of an SCR are forward characteristics of p-n junction.

⇒ ② has more doping concentration

Y-axis - current -
X-axis - voltage - here V_g is the case - independent parameter

Check for some exm, changed V_g and I_g and.

⇒ V_{gm} = maximum voltage.

I_{gmn} = minimum current.

⇒ $P_g = V_g I_g$ [Rectangular hyperbola]
 [with fed current]

⇒ V_{gmn} = minimum voltage.
 [with observed]
 I_{gmn} = minimum current.
 [with observed]

- double level - to show the operating point

- why minimum value?

= Electromagnetic Interference

- A voltage is generated \Rightarrow bigger voltage

- Conduction starts

- To avoid noise signal, also start will not

start by mistake (MAL TRIGGERING)

(87) - ~~noise~~

" The minimum value restriction over the positioning of the operating point is to avoid MAL TRIGGERING due to noise signal."

OPERATING POINT (V_{gt} , I_{gt})

- $I_{gt} = 0$, E_s on $V_{ans} = V_{gt}$

- $V_{gt} = 0$, $\frac{E_s}{R} = I_{gt}$

$V_{gt} =$ bigger voltage $= E_s$

$I_{gt} =$ bigger current $= \frac{E_s}{R}$

[load needed]
 " Can be obtained by the intersection of load line


and gate to cathode characteristics.
 post/or min.
 trans. maximum

SCR preferable

SCR - SCR should not get damaged.

- We select ①

- operating current more.

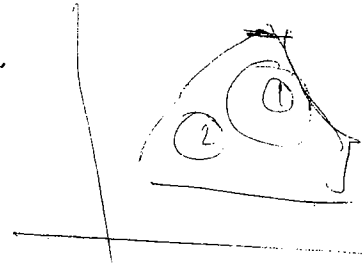

⑤ " The operating point should be so selected in the given region so that the resultant gate current is higher in magnitude, it causes reduction in turn ON time and hence the device becomes faster "

KVL form fig ①

$$E_s = V_g + i_g R_s$$

$$P_g = V_g \dot{C}_g$$

\Rightarrow Slope of the gate-cathode characteristic is equal to

$$V_g / \dot{C}_g$$

\Rightarrow slope of load line = R_s

PROTECTION OF SCR

- We will use soft start circuit

to give protection, i_{TSM} -
12.5A

1. Over voltage protection - VARISTOR, VARIABLE CAPACITOR

2. Over-current protection - CIRCUIT BREAKER, FAST ACTING CURRENT LIMITING FUSE [FACLE]

3. Thermal protection - HEAT SINKS (ALUMINIUM)

4. $\frac{dV}{dt}$ protection - SERIES RC COMBINATION (SNUBBER CIRC) with ω





5. $\frac{di}{dt}$ protection -

> high voltage protection

Ans:

$$- V = L \frac{di}{dt} = \frac{2H}{1A} \times \frac{1ms}{1A} \text{ suddenly } V = 71kV$$

- cause
- character

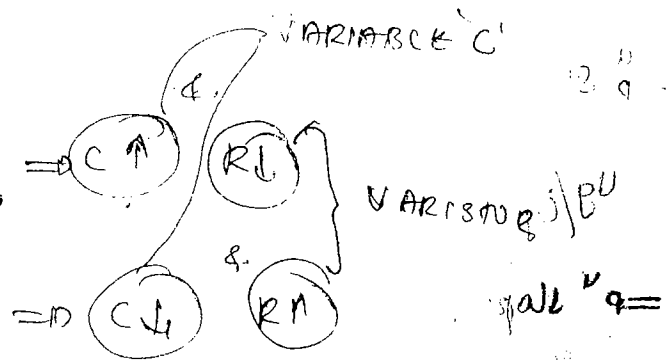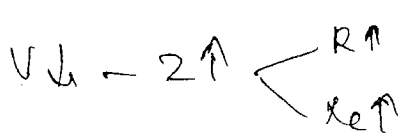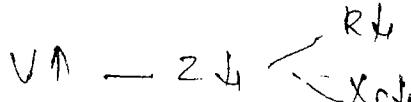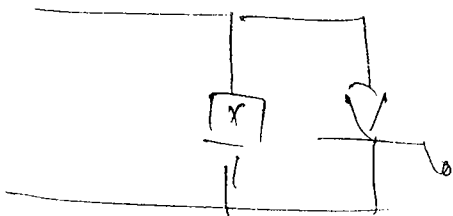

> Over-current protection

ANSWER

- Fuse - Fast acting - Series conductor of the line
- Roddy \uparrow CB. - Normal fuse will not last long

~~***~~ Over load - short circuit

↑ + ON-OFF PROP: ↑
FUSE CB FUSE

- Fuse time (fuse) \propto amount of current passing through it
 $\propto I^2t$ - (Energy loss).

- R - constant

$I \uparrow$, time \downarrow \Rightarrow Energy dissipation of fuse = CONSTANT

Energy $\propto I^2 t$ \rightarrow means
 constant

$P \propto I^2 \uparrow$ $t \downarrow$ $t =$ fusing time

- Fault $I \uparrow$ $t <$ below CB operation

$t < t_{CB}$

FUSE IS GOOD

t_{CB} $\left\{ \begin{array}{l} \text{CB need} \\ \text{Domestic Rely} \\ \text{CB operation} \end{array} \right.$

- CB tripped - Normal fault - takes a chance

- Fuse blows - do not take chance - BIG FAULT

③ Thermal Protection

- Heat sinks.

- material preferable = Aluminium

4) $\frac{dv}{dt}$ problem

$$\frac{dv}{dt} = \text{Rastro } \downarrow - (\text{low})$$

$$\boxed{1) dt \uparrow \quad 2) dV \downarrow} = r \left[\frac{dv}{dt} \downarrow \right] = \text{Transient time in low also see}$$

$dV = \text{change in voltage}$

= 2t. on U and
mal logging.

initially assume $V = 0$ see $V_1 = 0$

supply $V_2 = V_s$

- then $dV = V_s = \text{supply voltage}$

- the $dV \neq$ supply voltage

$$- dV \downarrow = \text{supply voltage } \downarrow \quad \alpha$$

only one way

$$\textcircled{dV \uparrow} = 0 \text{ memory the denominator}$$

How to $dV \uparrow$?


- make for d' more to go from $0 \rightarrow V_s$

- we need a device, opposes the change in voltage

- "capacitor"

mult

- see the diagrams

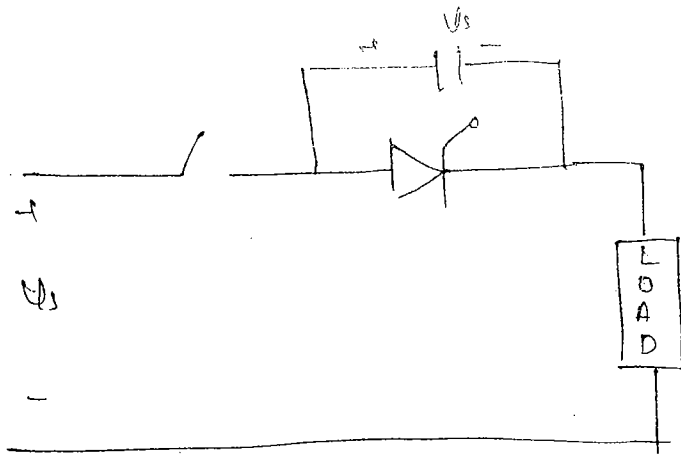

two cases


1) No capacitor

$\Rightarrow V_s = 0, S \text{ OPEN.}$

$V_{SCR} = 0$

$\Rightarrow V_s = V_s, S \text{ ~~CLOSED~~ ^{OPEN}}$

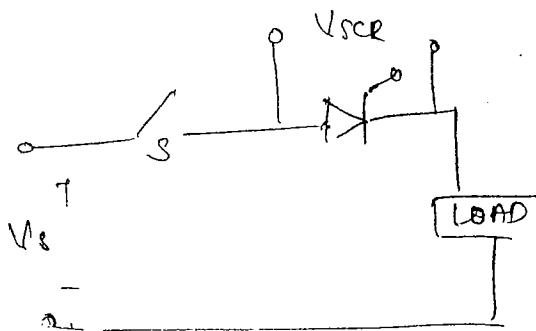$V_{SCR} = V_s (0 - V_i) = \underline{\underline{\text{turn taken is } \frac{t_1}{2}}}$



2) Case with capacitor

$\Rightarrow V_i = 0, S, \text{ OPEN.}$

$V_{SCR} = 0$

$\Rightarrow V_s = 0, \text{ initially } S, \text{ CLOSED}$

$V_{SCR} = 0$

$\Rightarrow \underline{\underline{C \uparrow}}$ Final voltage $\left. \begin{array}{l} \frac{V_c = V_s}{\parallel} \\ \underline{\underline{V_{SCR} = V_s}} \end{array} \right\} \underline{\underline{t_2 \text{ time } (0 - V_i)}}$

$\boxed{t_2 > t_1}$

- time is more with capacitor.

problem!


- during discharging, (SCR already conducting)

⇒ load current + discharge current = Thyristor current

⇒ chance to problem with SCR damage

$\frac{di}{dt} \Rightarrow \frac{di}{dt}$ protection

- local hot spot formation

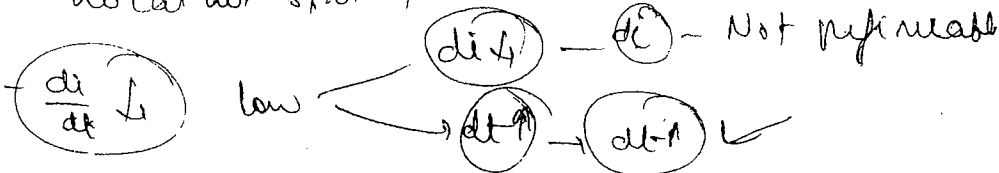

- Blocky state SCR $\rightarrow \bar{i}_1 =$ leakage current \Rightarrow

Conducting state $\rightarrow \bar{i}_2 = \underline{\underline{\dot{i}_2}}$ load


$$d\bar{i} = \bar{i}_2 - \bar{i}_1 = \underline{\underline{\dot{i}_2}}$$

\dot{i}_2 \rightarrow not permitted

~~***~~

- $\frac{di}{dt}$

- current \rightarrow SERIES INDUCTOR

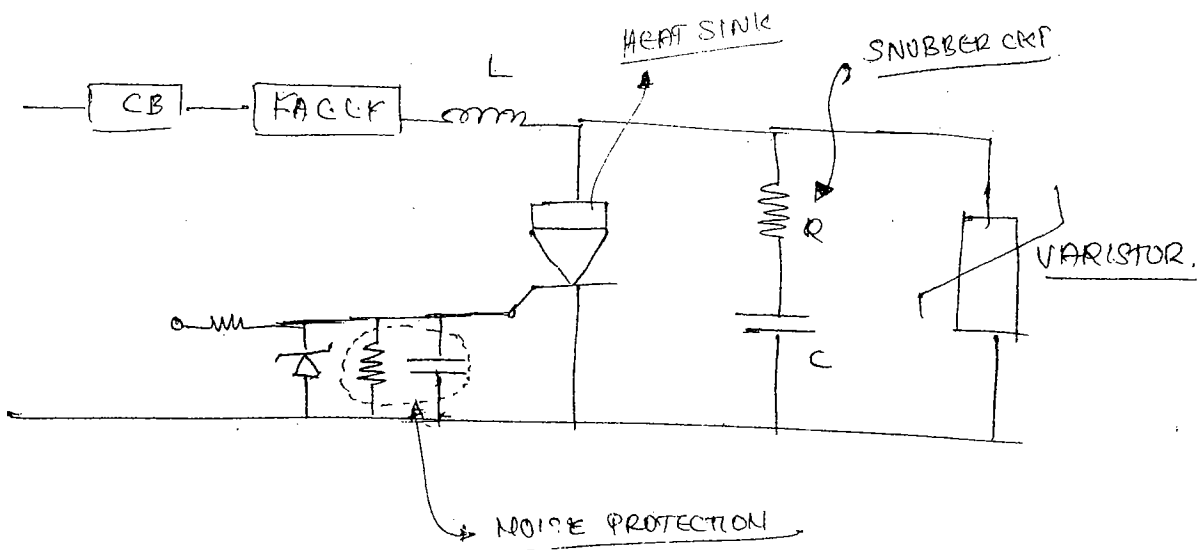

- heat sink - mechanically mounted.

(b) Restarts


with resistance is connected ~~across~~ across the gate to cathode terminal for NOISE PROTECTION, it increases the NOISE IMMUNITY for the SCR.

DESIGN OF SNUBBER CIRCUIT

Q) A thyristor is placed between a constant dc voltage source of 240V and load resistor R_L . The specified limits of $\frac{di}{dt}$ and $\frac{dv}{dt}$ of SCR are, 60A/ μ s and 300V/ μ s respectively determine the snubber circuit parameters along with $\frac{di}{dt}$ inductor. take damping ratio as $\delta = 0.5$.

Solution

Www

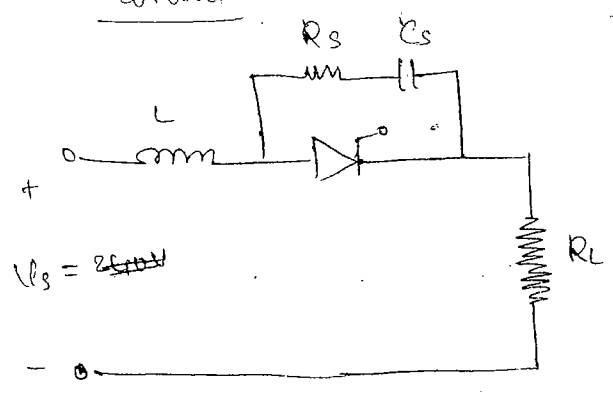


- consider de supply gun


- initial $L = 5 \cdot C$
 $C = 0 \cdot C \quad V_C = 0$
 $\underline{\underline{C = 0}}$ shd

- at $C \neq 0 =$
 $V_C \neq 0 = 0$ ASSUMPTION
 ↑ neglected.

- Approximated Analysis.

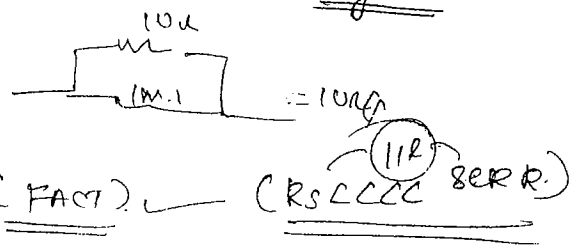

- consider SCR-0.C (FACT)

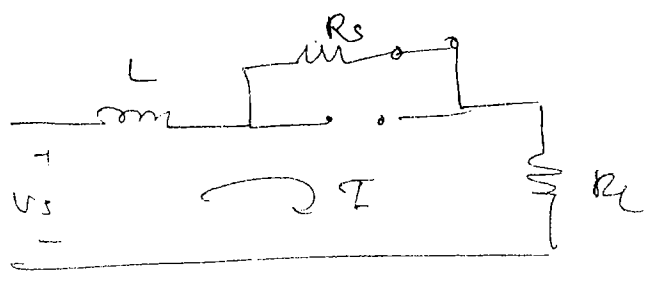

$$KVL = 0 \quad L \frac{di}{dt} + (R_S + R_L) i = V_s$$

$$\Rightarrow \frac{di}{dt} + \left(\frac{R_S + R_L}{L} \right) i = \frac{V_s}{L}$$

xx $i(t) = \text{desired answer}$ (wp)

- Apply C.T

$$\left[s I(s) - 0 \right] + \frac{R_S + R_L}{L} I(s) = 0 \cdot \frac{V_s}{L}$$

$$I(s) \cdot \left[s + \frac{R_S + R_L}{L} \right] = \frac{V_s}{sL}$$

$$I(s) = \frac{V_s}{L} \cdot \frac{1}{s} * \frac{1}{s + \frac{R_s + R_L}{L}}$$

$\frac{1}{s} \rightarrow V/L e^{(1-e^{-t/\tau})}$
 $\frac{1}{s + \frac{R_s + R_L}{L}} \rightarrow \frac{1}{\tau} e^{-t/\tau}$

$$= \frac{V_s}{sL(s + \frac{R_s + R_L}{L})}$$

$$= \left[\frac{1}{s} - \frac{1}{s + \frac{R_s + R_L}{L}} \right] \frac{V_s}{L} * \frac{L}{R_s + R_L}$$

$$i(t) = \frac{V_s}{R_s + R_L} \left[1 - e^{-\frac{(R_s + R_L)t}{L}} \right]$$

$$\tau = \frac{L}{R_s + R_L}$$

$$\frac{di}{dt} = \frac{V_s}{R_s + R_L} \left[0 - e^{-\frac{(R_s + R_L)t}{L}} \cdot \left(-\frac{(R_s + R_L)}{L} \right) \right]$$

$$= \frac{V_s}{R_s + R_L} \cdot \frac{R_s + R_L}{L} \cdot e^{-\frac{(R_s + R_L)t}{L}}$$

$$\frac{di}{dt} = \frac{V_s}{L} \cdot e^{-\frac{(R_s + R_L)t}{L}}$$

$$e^0 = 1$$

substitute $t=0$

$$\frac{di}{dt} = \frac{V_s}{L}$$

$$L = \frac{V_s}{di/dt} \quad \text{--- (1)}$$

$$V(\text{across } R_s) = V(\text{across } R_L)$$

$$V = I R_s$$

$$\frac{dV}{dt} = R_s \frac{di}{dt}$$


$$R_s = \frac{dV/dt}{di/dt} \quad \text{--- (2)}$$

Assumed capacitor back to derivation / circuit

- correlation b/w R-L-C ($R = \sqrt{L/C}$) - char - ω_n form

- imagine series R-L-C circuit energised by DC

supply, solution would be as follows:

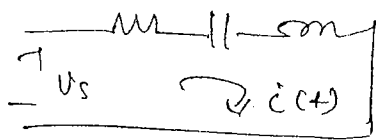

$$Ri + L \frac{di}{dt} + \frac{1}{C} \int i dt = V_s$$

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = 0$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

\uparrow compare

$$s^2 + (2\delta\omega_n)s + \omega_n^2 = 0$$

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

~~$2\delta\omega_n =$~~

$$2\delta\omega_n = R/L$$

$$\omega_n = \frac{1}{\sqrt{LC}}$$

$$\delta = \frac{R}{L \cdot 2\omega_n} = \frac{R}{2L \cdot \frac{1}{\sqrt{LC}}} = \frac{R}{2\sqrt{L/C}}$$

We need R

$$R_s = 2 \cdot \frac{L}{\sqrt{LC}}$$

$$R \quad \boxed{R_s = 28 \sqrt{\frac{L}{C}}}$$

Solution

H, F, Ω
(Scientist Names)

$$\textcircled{A} \quad V = L \frac{di}{dt} \Rightarrow L = \frac{V \cdot s}{A} = H$$

$$\textcircled{A} \quad i = C \frac{dv}{dt} \Rightarrow C = \frac{A \cdot s}{V} = F$$

$$\textcircled{A} \quad R = V/I \Rightarrow R = \frac{V}{A} = \Omega$$

UPSC Intro

$$\Rightarrow R = \sqrt{\frac{L}{C}} \cdot \frac{1}{F}$$

$\Omega \quad \boxed{\sqrt{H/F} = \Omega} \quad ?$

$$\Rightarrow \tau = \frac{L}{R}$$

$$\Rightarrow \tau = RC$$

$$\boxed{S = H/\Omega}$$

$$\boxed{S = \Omega \cdot F}$$

$$\Rightarrow F = \frac{1}{2\pi\sqrt{LC}}; \quad \boxed{\frac{1}{S} = \frac{1}{\sqrt{H \cdot F}}}$$

$$\Rightarrow \sqrt{LC} = \sqrt{H/F}$$

$$L = \sqrt{\frac{V \cdot s / A}{A \cdot s / V}}$$

$$= \sqrt{\frac{V^2}{A^2}} = V/A = \Omega$$

Numerical data given

$$V_s = 240V, \quad \frac{di}{dt} = 10A/ms, \quad \frac{dv}{dt} = 300V/ms$$

$$\underline{S = 0.5}$$

$$L = \frac{240}{60} = \frac{Ls}{di/dt} = \boxed{4H = L}$$

①

$$R_s = \frac{dv/dt}{di/dt} = \frac{300V}{60A} = \boxed{5\Omega = R_s}$$

$$R_s = 28 \sqrt{\frac{L}{C}} \Rightarrow \frac{R_s^2}{48^2 L} = \frac{1}{C} \Rightarrow \boxed{C = 0.16\mu F}$$

⇒ D resigning (good design for better operation)

Q1) $R_s = 5 \Omega$ critical value of $R = i = SCR$ critical. (2x mark)

R_s - greater } For more better operation
- lesser }

① $R_s = 3 \Omega, R_s = 8 \Omega$

⇒ $R_s = 3 \Omega$, i they sep ↑, dangerous op

⇒ $R_s = 8 \Omega$ i (say)

Q2) $C \rightarrow C_f = \text{LESS}$ - $\tau = \text{time constant} = \uparrow$

$C \uparrow - SCR = \underline{\text{SLOW?}}$ ←

- Protection $\left\{ \begin{array}{l} \text{Protection } \uparrow \\ \text{Performance/Response } \uparrow \end{array} \right.$

$C \downarrow$ - Energy loss (during discharge)

Conclusion

time constant = RC = constant = $(R \uparrow C \downarrow)$ ←

Q3) $L = ?$

- First delay time L

$L = 2 \times \sqrt{4C}$ ←

Q.4 For a better operation of SCR, Resistance can be increased and capacitance can be decreased. Substitute these values in the formula and find out L, $R_s = 28\sqrt{L/C}$

It has to seen time constant will NOT change much due to the variation of resistance and capacitance.

$$\therefore R_s = 8\Omega, C = 0.1\mu F, R_s = 28\sqrt{L/C} = 28 \times 0.5 \sqrt{\frac{L}{0.1\mu F}}$$

$$\boxed{L = 6.4\mu H}$$

Design of snubber circuit is over.

Capacitor enabled

— Second order (L) equation

$$R_s = 5\Omega, \omega_{crit} = 4.82$$

↑
we got

— For design $R_s = 8\Omega$ = 'doing the simple analysis'

any way we adjust the value for better performance.

HEATING, COOLING CIRCUIT OF SCR.

— Consider, SCR conducting = Power loss = heat generated.

— This heat should be cooled for better performance of SCR.

- maximum heat = current @ Junctions
= most heat generated.

- creasing of the device :- heat will flow from

Junction to casing → SCR mounted on sink → sink

takes heat → Material - cools.

2) Forced cooling - Fans, A/C, coolant
(water - high heat)

→ depends on ratings of the device.



Surrounding medium (ambient)

(SM)

" whenever SCR carries the current, it produces the heat energy. The charge ~~carries~~ carriers, lose some of

the energy while they are passing through layers


as well as Junctions. Most of the heat energy

will be generated at the junction. Hence

junction will be at high temperature. Heat flows

from junction to surrounding ~~ambient~~ medium

in the following sequence.

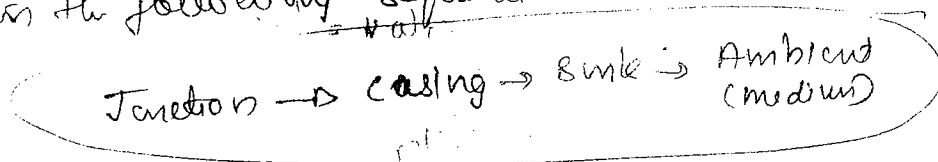

Thermal parameters

- Temperature and diffusion parameters, areas.

- Equivalent electrical circuit for thermal application.

Thermal	Electrical
1. Heat energy (J).	1. charge (C)
2. Temperature difference ($^{\circ}\text{C}$)	2. potential difference (V)
3. Rate of heat transfer (W) Thermal power ($\text{J/s} = \text{W}$)	3. Electric current (Rate of charge transfer) (A)
4. Thermal resistance. $\frac{\text{Wm}^2}{\text{K}} = (\frac{2}{3}) = (^{\circ}\text{C}/\text{W})$	4. Resist Electrical Resistance (V/A) (Opposing). $(\frac{2}{3})$

- Not equal, just equivalent terms, trying to correlate.


Rate of heat transfer = SAME, CONSTANT

= WRITTEN, SAME AND CONST

Thermal circuit = SERIES CIRCUIT ELECTRICAL

② In the given thermal application, Rate of heat transfer is same and constant. It can be represented as series electrical circuit.

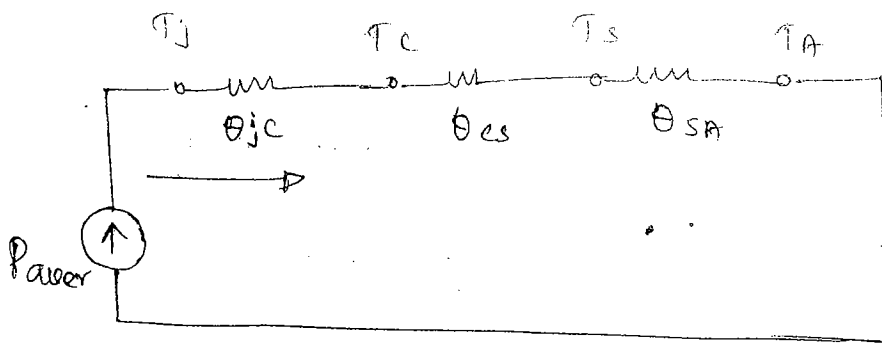- Nodes = 4. (Jm, casey, sink, ambient)
= representing temperatures.



- direction given, is the direction of the thermal flow.

Justification by Electrical analogy

- $T_j > T_c > T_s > T_A$ (Voltage)

$\frac{1}{R} \propto \frac{1}{T_j} = \text{Voltage } \uparrow, \propto \text{temperature } \uparrow$

- current is correct

Thermal power (Rate of heat transfer) (Power)

$$P_{avg} = \frac{T_j - T_c}{\theta_{jc}} = \frac{T_c - T_s}{\theta_{cs}} = \frac{T_s - T_A}{\theta_{sa}}$$

$$P_{avg} = \frac{T_j - T_A}{\theta_{jc} + \theta_{cs} + \theta_{sa}}$$

$$T_s = T_c - P_{avg} \cdot \theta_{cs}$$

$$= T_A + P_{avg} \cdot \theta_{sa}$$

Use for others.

Missed points

09/02/14

- θ_{j-c} value depends on the material and method by which SCR is prepared.
- θ_{cs} value depends on the method of mounting and contact area with the heat sink.
- θ_{sa} value depends on the method of cooling and type of coolant employed in the cooling circuit.

SERIES, PARALLEL OPERATION OF SCR.

- Series operation of SCR is required for higher blocking voltage capacity.
- Parallel operation of SCR is required to increase the current carrying capacity.

STRING EFFICIENCY η_s

$$\eta_s \text{ (SERIES)} = \frac{\text{Actual Voltage rating of the string}}{n_s \times \text{Actual Voltage rating of SCR}}$$

$$\eta_p \text{ (Parallel)} = \frac{\text{Actual current rating of the string}}{m_p \times \text{Actual current rating of SC}}$$

- Always $\eta_s < 1$


2) DERATING FACTOR (DRF)

$$= 1 - \eta_s$$


= 1 - string efficiency

• "It is a measure of rating that is not useful for the operation of the system".

1) SERIES OPERATION OF SCR

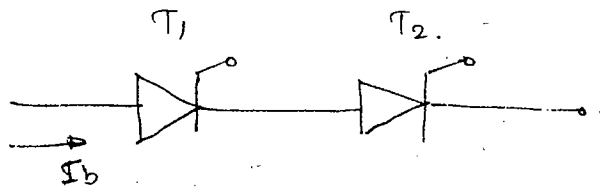

i) STATIC CHARA

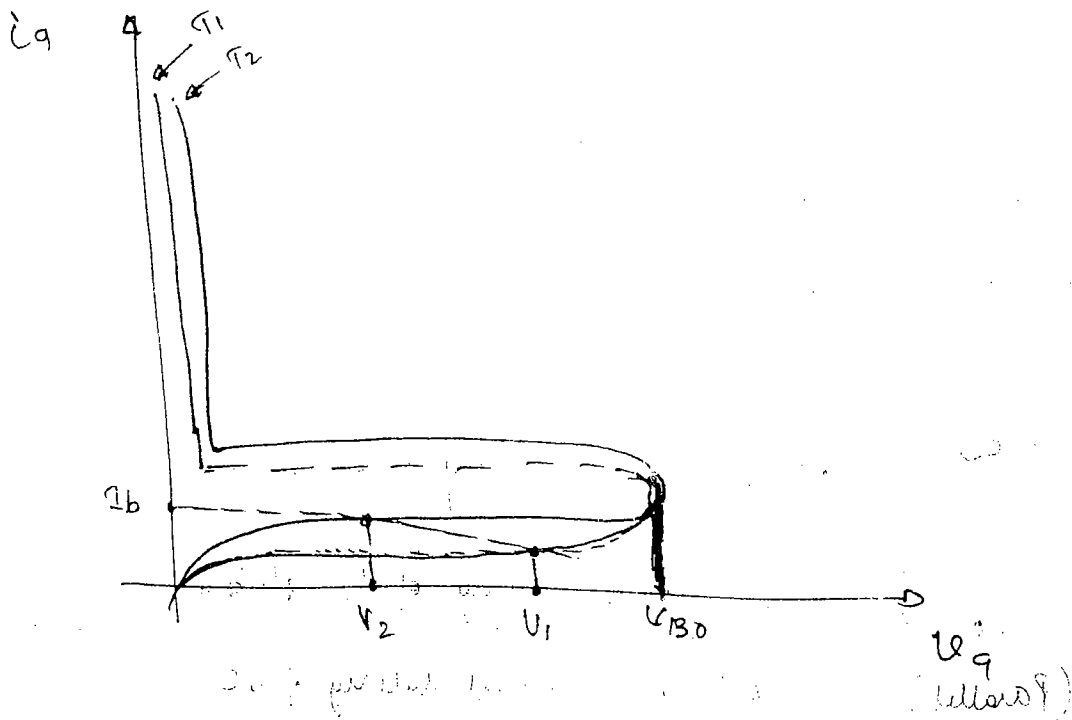


Handwritten notes at the bottom of the page, possibly including the word "forward".

- T_1, T_2 rated for same V_{BO} But $V_1 > V_2$, T_1 Blocking V_1 and T_2 Blocking V_2 at I_b .
- Total Voltage blocked (practical) = $V_1 + V_2$.
- String efficiency = $\frac{V_1 + V_2}{2V_1} < 1$

(*) The difference in static characteristics results in to unequal voltage distribution among series connected SCR.

(*) The unequal voltage distribution among the SCR is because of the unequal leakage resistances offered by the SCR.

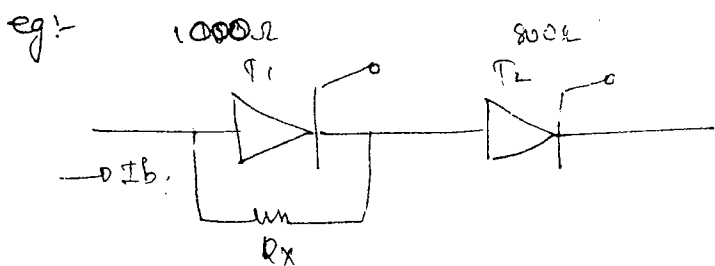(*) If the SCR is having less leakage current rating, then it will block more voltage.



$$R_{eq} = \frac{1}{\frac{1}{R_x} + \frac{1}{100}} = \frac{80}{700}$$


STATIC EQUALISING RESISTOR

• To approximately equalise the static properties

it is required to connect only one value of resistance

across each and every SCR and is known as

STATIC EQUALISING RESISTOR

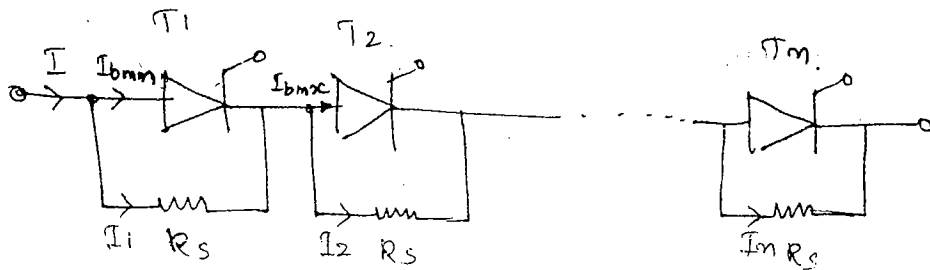

$$V_s = I R_s + I_2 R_s + \dots + I_m R_s$$

$$I = I_1 + I_{bmin}$$

$$I = I_2 + I_{bmax}$$

$$\left. \begin{array}{l} I_{bmin} = I_{bminimum} \\ I_{bmax} = I_{bmaximum} \\ \text{all others} = \underline{I_{bmax}} \end{array} \right\}$$

• Deriving R_s Formula ($R_s = \rho$ static equalising resistor)

⊗ • Assumption

▷ Two groups of SCR

• 1st group = 1 SCR

• 2nd group = $n-1$ SCR.

⊗ ⇒ All SCR is having same current flowing though it except FIRST ONE

→ $V_s = \text{Total supply voltage} = \text{string voltage}$

$$V_s = I R_s + I_2 R_s (n-1)$$

$$= I R_s + (n-1) C \underline{I - I_{bmin}} R_s$$

$$= I R_s + (n-1) \cdot (I - I_{bmin} - I_{bmax}) R_s$$

... ..
... ..
... ..

$$= I_1 R_s + (m-1) (I_1 - (I_{bmax} - I_{bmin})) R_s$$

$$= I_1 R_s + (m-1) (I_1 - \Delta I_b) R_s$$

$$= I_1 R_s + (m-1) I_1 R_s - \Delta I_b \cdot (m-1) R_s$$


$$= m I_1 R_s - \Delta I_b \cdot (m-1) R_s$$

$$V_s = m V_{bm} - \Delta I_b (m-1) R_s$$

$$\Rightarrow R_s = \frac{m V_{bm} - V_s}{(m-1) \Delta I_b} \Rightarrow \text{Approximately equal Resistor value.}$$

R_s is Static Equalizing Resistor.

(i) DYNAMIC CHARACTERISTICS

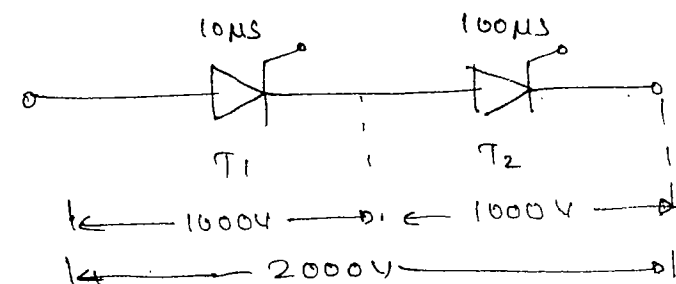

T_1 - Turn ON time - 10 ns


T_2 - " - 100 ns.

T_1 - Blocks - 1000 V


T_2 - " - 1000 V

- The unequal dynamic characteristics of the SCR's results in to damage of the slower devices due to the

applications of unijunction transistors.

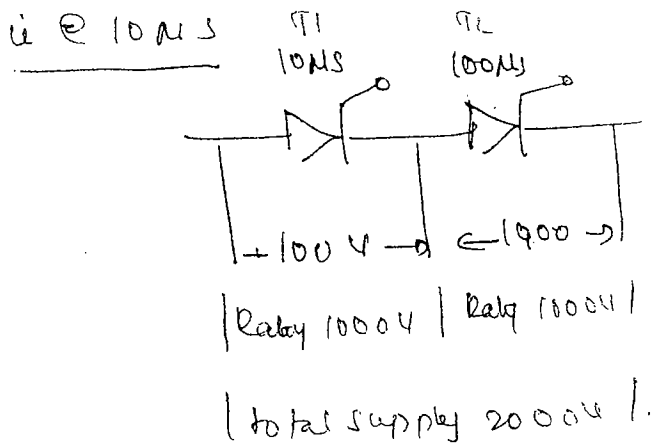

• Difference in turn on time.

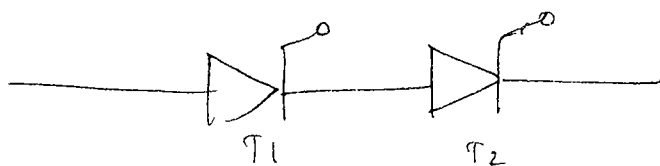

Charge required = 10 μC	= 100 μC
$C_g = 1 \mu F$	= 1 μF
Time required to get req. charge = 10 μs	= 100 μs .
Junction capacitance = C_1	= C_2

• The unequal dynamic properties are because of the unequal junction capacitance offered by the SCE.

• To Equalise the dynamic property one value of capacitor is connected across each and every SCE and it is known as

DYNAMIC EQUALISING CAPACITANCE

DERIVATION :- III^{rd} to R_s

FORMULA :-


$$C = \frac{(m-D) \Delta Q}{mV_{bm} - V_s}$$

$\Delta Q \Rightarrow$ Difference in Reverse Recovery charge.

TIPS

$$R_s = \frac{mV_{bm} - V_s}{(m-D) \Delta I_b} \Rightarrow \frac{V}{I}$$
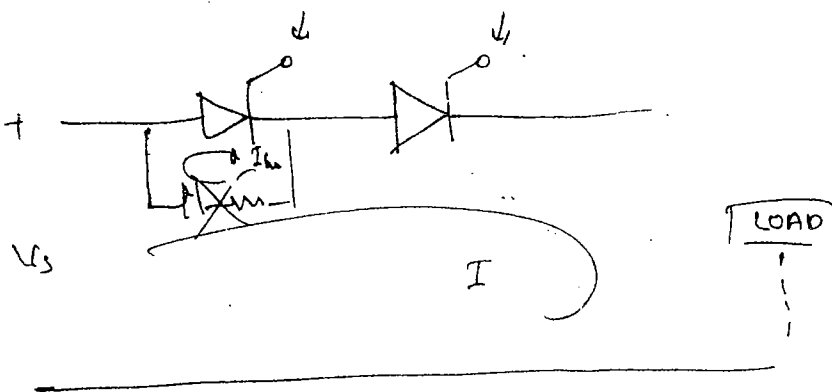
$$C = \frac{(m-D) \Delta Q}{mV_{bm} - V_s} \Rightarrow \frac{Q}{V}$$



IESQ



In the series operation SNUBBER CIRCUIT is useful for

following

1) dV/dt PROTECTION

2) DYNAMIC PROPERTY EQUALISATION

2-30-5-30 = EDC
 G-8-30 = PE-304

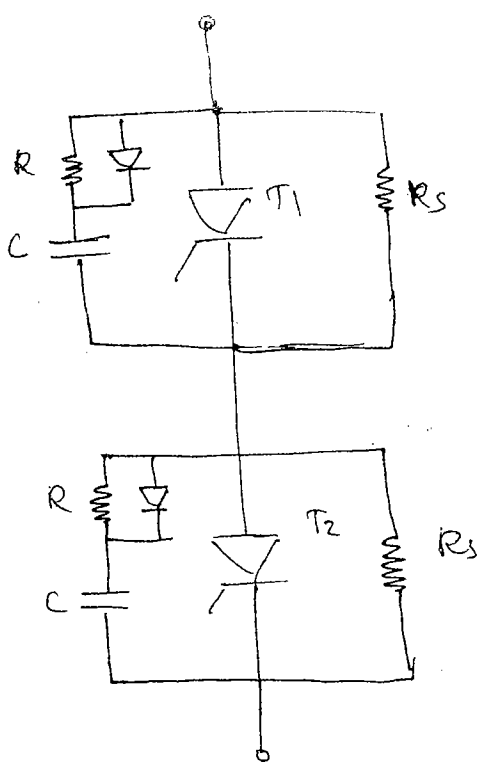
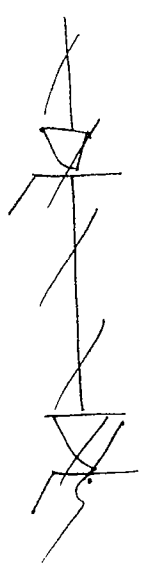


④ Diode connected across the resistance, reduces the ~~time~~ charging time constant so that device become fast.

II) PARALLEL OPERATION OF SCR.

10/02/12

1) STATIC CHARACTERISTICS.

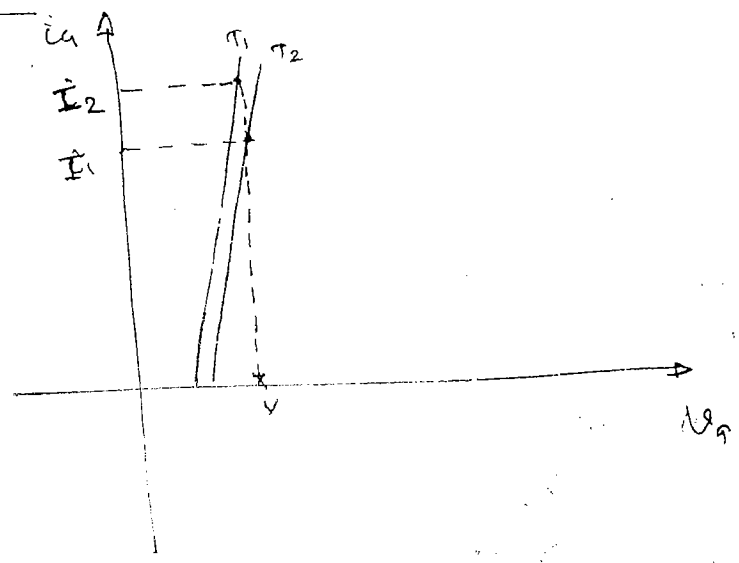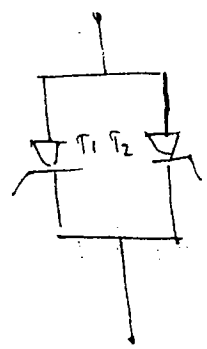


• Blocking char, is not required.

→ • String efficiency = $\frac{I_1 + I_2}{2I_1} = \eta_s$

always $\eta_s < 1$.

- Due to the difference in static characteristics the current distribution will become unequal.
- For equalising the current distribution the devices should have overlapping static characteristics.

eg :-

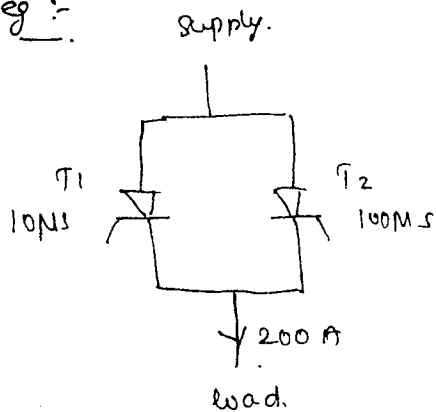

$t = 0$: trigger given


$t_1 = 10\text{ns}$: T_1 ON : 1

- SCR turn ON = Min Voltage.
- $V_{T2} < \text{Min switch ON voltage}$
- only T_1 - conducting.
- 200 A pass through T_1 .

- T_1 damaged • T_2 supply V • T_2 starts conducting • $T_2 \Rightarrow 200\text{A}$.
- Both are damaged. [CASCADE FAILURE OF DEVICE]
CO.O
- REMEDY : manufacturer, manufacturing near by turn ON time.

- The unequal dynamic characteristic leads to cascade damage of SCR's due to the flow, high currents. To get the the satisfactory operation the devices should have VERY near values of dynamic characteristics.

W/ = CONDUCTOR SIZE

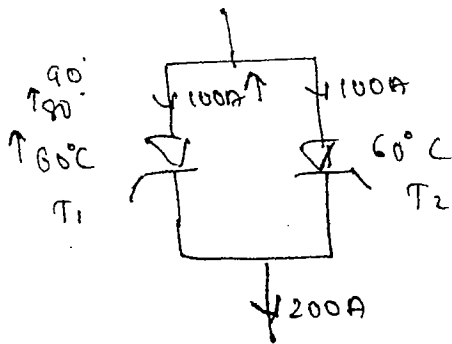

• Consider T_1 Temp $\uparrow = 70^\circ\text{C}$ (due to some reason)


• $T_1 = -ve$ temp coefficient of resistance

• Temp $\uparrow \Rightarrow$ Resistance $\downarrow \Rightarrow$ Current $\uparrow \Rightarrow$ Power loss more $\Rightarrow 85^\circ\text{C}$

\Rightarrow Temp \uparrow THERMAL RUNAWAY occurs.

• T_1 damaged, then same and shifted to T_2 . same can lead failure effect.

SINK POSITION (remedy)

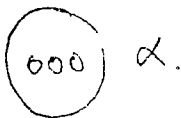


• If the parallelly connected SCR's are at different temperatures

then the devices may be subjected to unequal distribution of currents. some times it may lead to failure of the device.

• It is recommended to mount all the SCR's on the same heat sink in symmetrical positions. to maintain the same temperature.




(ii) MAGNETICALLY COUPLED CONNECTION

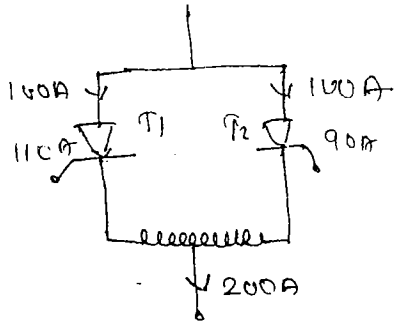

- Current $T_1 \uparrow \Rightarrow \underline{110A} \Rightarrow T_2, I = \underline{90A}$
- Current passing through the coil or inductor, tries to restore the current back to 100A.
- It is preferable to couple the parallelly connected SCR magnetically so as to restore original distribution of currents if any disturbance occurs.

Note:

Inductor Properties (4)

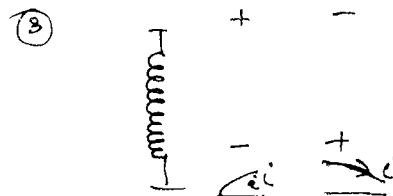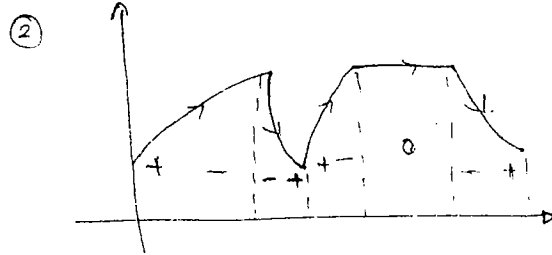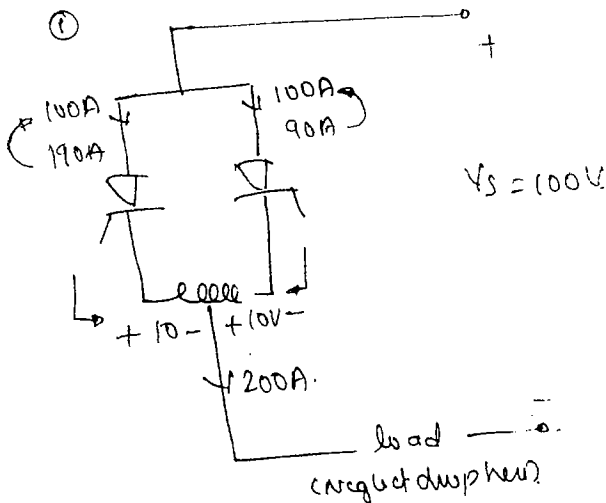

- Property of the inductance is to oppose the change in current by developing an appropriate voltage in magnitude as well as in polarity.


• Polarity of induced voltage depends on slope of variation of current.

• Magnitude of voltage depends on, the value of the
 $L \frac{di}{dt}$.

• In a constant inductive system, instantaneous variation of current is NOT POSSIBLE.

①

$10A$	$\frac{di}{dt}$	V_L
	+ve	+ve
	-ve	-ve
	0	0

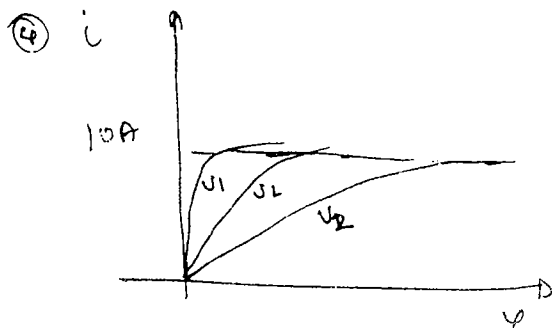

• V_1, V_2, V_3 induced voltage across inductor


• $V_1 > V_2 > V_3$ (slope $>$ slope $>$ slope)

- will no movement of dots, only in terms of first and third value of nodes in cathode voltage.

Applications

▷ Logic, delay, comparing circuits.

3) SCS (Silicon Controlled Switch)

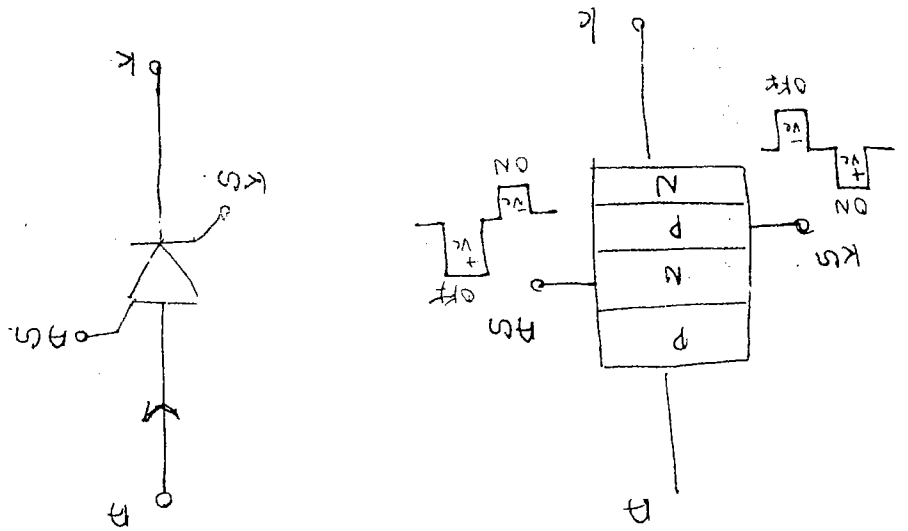

- SCS is a 4 electrode thyristor (4 terminals)

• SCS can be controlled either from anode gate

(or) (ii) cathode gate.

- Opposite nature of gate currents can be employed to make

turn ON and turn OFF of the device.

- It acts like a GTO, but it is limited for low power

applications.

• PVT is similar to SCR. Where the gate terminal is taken from

current N layer



• It is suitable for low voltage switching applications.

→ Logic circuit

→ Turn delay circuit

→ Trigger circuit of SCR.


2) SiC UNILATERAL SWITCH

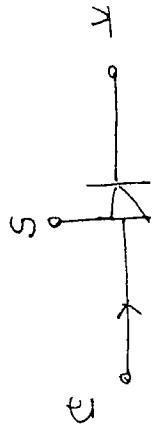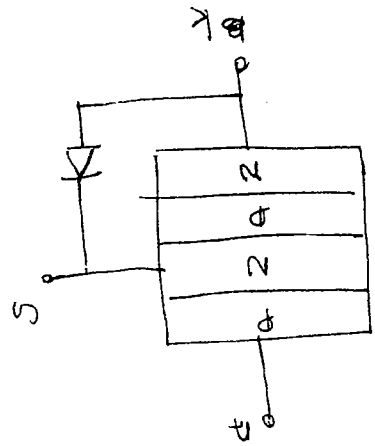

• SiC is same as the PVT, but a low voltage unilaterial diode.

so placed across gate to cathode terminals.

PULSE TRIGGERING OF SCR

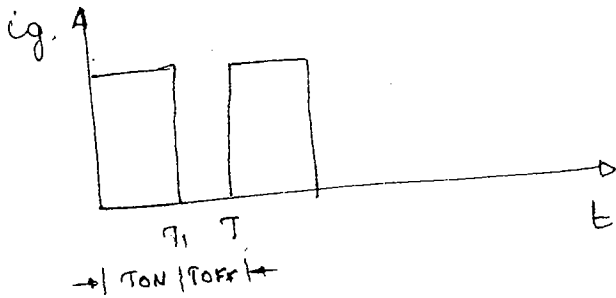

Note:
 • Thermal time constant > Electrical time constant.

- In pulse triggering, the bigger voltage and bigger current will be applied as terms of pulses. Instead of continuous (dc signal) signal.
- It allows to employ higher value of gate current for the same average gate power dissipation. Due to this, TURN ON time of the SCR decreases as a result device becomes faster.

EXPRESSIONS

$$P_{gav} = \delta \cdot P_{gm}$$

$$\delta = \text{Duty cycle} \cdot \left[\frac{\text{ON TIME } (T_1)}{\text{TOTAL TIME } (T)} \right]$$

$$P_{gav} = \frac{T_1}{T} \cdot P_{gm}$$

$$P_{gav} = f \cdot T_1 \cdot P_{gm}$$

f = frequency \Rightarrow PULSE FREQUENCY

Note:

Computer Terminology : $\frac{\text{mark}}{\text{space}} = \frac{1}{4}$

mark = 0 1
 space = 0 0

$$\frac{\text{mark}}{\text{Space}} = \frac{T_{ON}}{T_{OFF}}$$

② 1 cycle \rightarrow 100A

1/2 cycle \rightarrow ? (surge current)

SURGE CURRENT

The surge current rating of the SCR for different durations can be evaluated by using the energy energy dissipation on the device.

$$I^2 R \cdot t = \text{constant}$$



$$I_1^2 \cdot R \cdot t_1 = I_2^2 R t_2$$

$$I_1^2 \cdot t_1 = I_2^2 \cdot t_2$$

OTHER MEMBERS OF THYRISTOR FAMILY.

\rightarrow PUT (Programmable Unijunction Transistor)


• It is a thyristor.

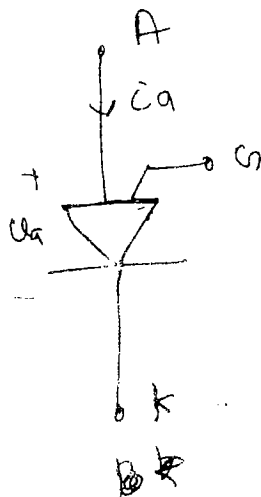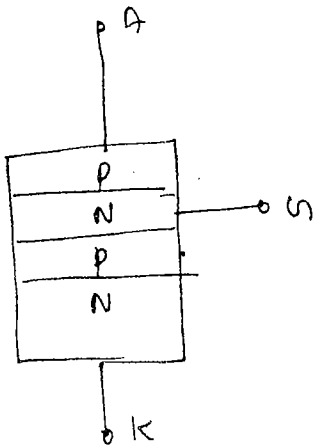

Applications

→ In oscillators, voltage sensors, Function generators, and trigger circuits

4) LA SCR (Light Activated SCR)

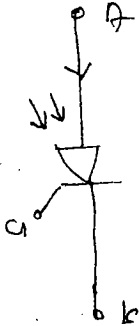

- LA SCR will be turned ON by using the light triggering
- The gate terminal is useful to turn ON the device, under low light intensity conditions. It is possible by applying a small gate pulse.

11-02-11

6:30 - 11:AM = PS



305



Applications

- street lighting, highways lighting
- Home app:

15/02/11

5) DIAC (Bi directional thyristor diode)

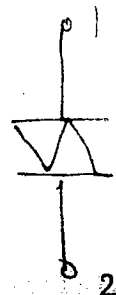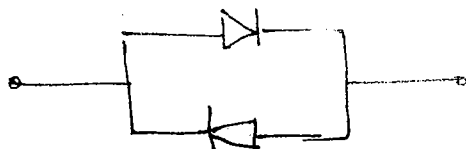

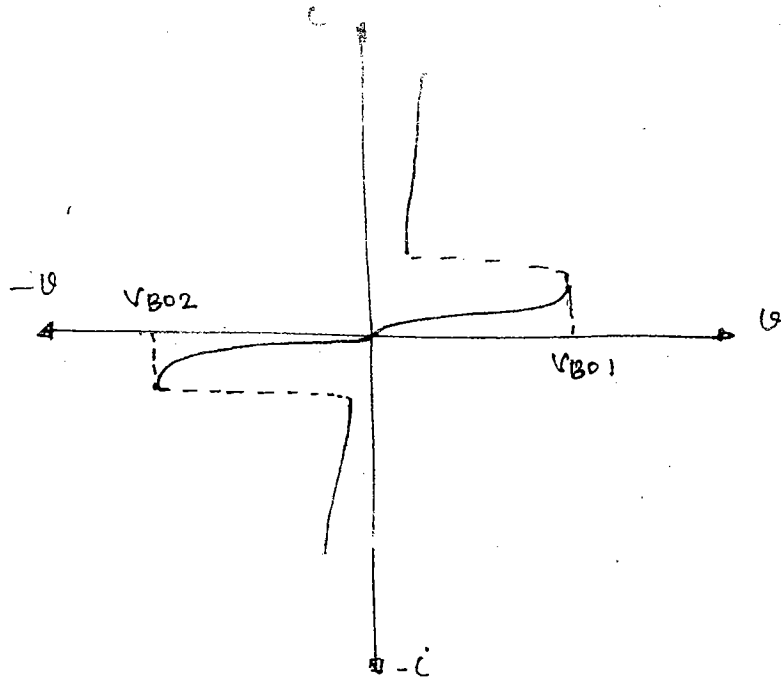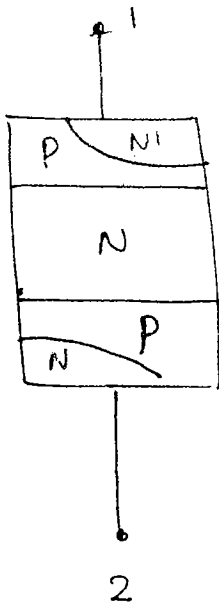

- DIAC is electrical equivalent to antiparallel connection of diode.
- If terminal '1' is at more potential w.r.t '2' and its magnitude exceeds V_{BO1} , and it allows the conduction from terminal 1 to 2.

• Structure PNPNI is activated.




- If terminal '2' is at more potential w.r.t '1' and its magnitude exceeds V_{BO2} , and it allows the conduction from terminal 2 to 1.

→ In this case structure PNPN' conducts

- Due to ~~lack of~~ lack of control action

DIAC finds limited app.

TRIAC (Bidirectional thyristor)

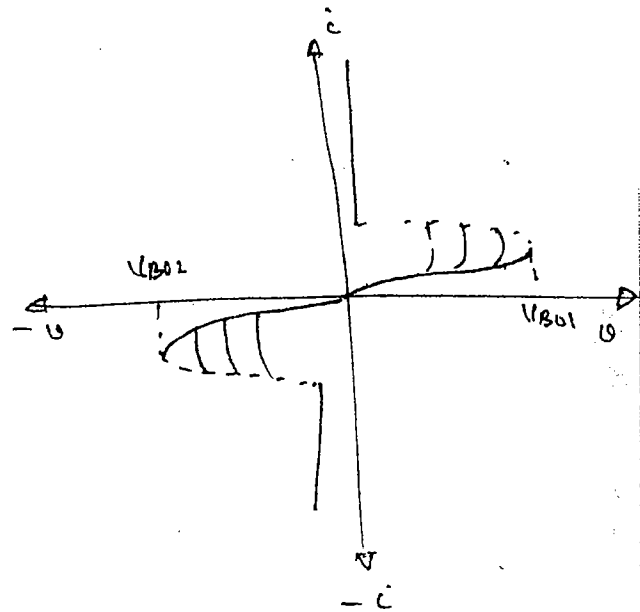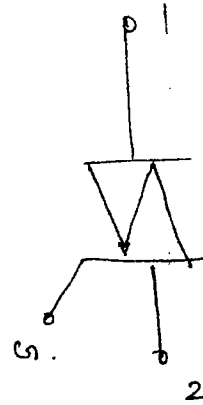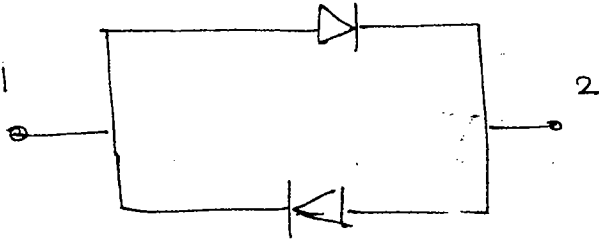


- Triac is electrical equivalent to antiparallel connection of SCR.
- It allows the controlled conduction in both the direction.
- The voltage, current and power ratings of the triac are less compared to SCR. Hence it is limited for medium power applications.

Appl.

- ① Speed control of A/c machines
- ② Fans regulators
- ③ Domestic and Industrial heating circuits.
- ④ Lighting circuits.

77 G.T.O.

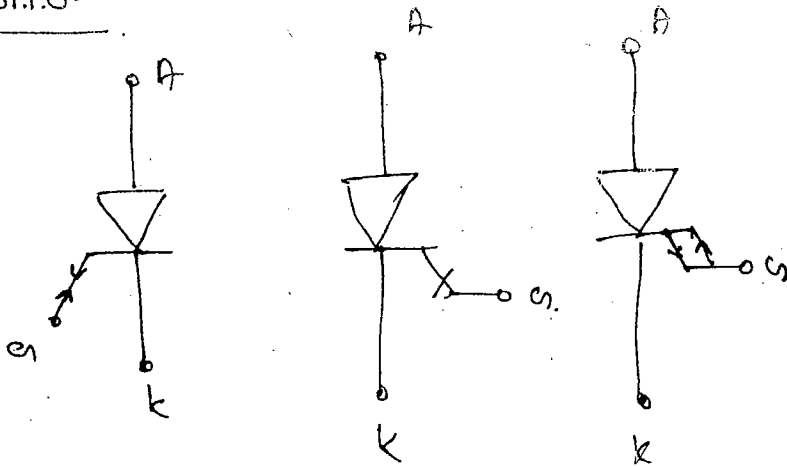

- Gate turn OFF thyristor.
- It can be turned OFF by giving a negative gate current.
- The value of gate current required to turn OFF GTO is quite high (20-30% Anode current).
- The positive gate current required to turn ON GTO is also high compared to SCR.
- The holding and latching current magnitudes are higher in GTO.

App:

- 1) UPS
- 2) Inverter.
- 3) DC-DC Converter

D) A on B?


	A	B
I_g	min	max
1)	SCR	GTO
2)	current gain \uparrow	current gain \downarrow

\Rightarrow $\text{current gain} = \frac{I_A}{I_G}$

Note:

- GTO will have the lower value of current gain since it needs higher gate current for the turn ON of the device.


8) RCT (Reverse Conducting Thyristor)

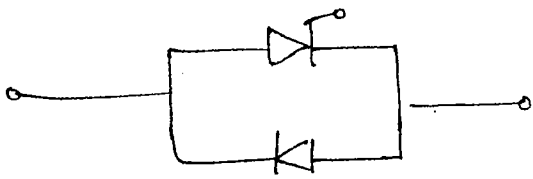

- It is electrical equivalent to antiparallel connection of SCR and diode.
- The commutation of SCR (or) Thyristor will be happened by antiparallel diode

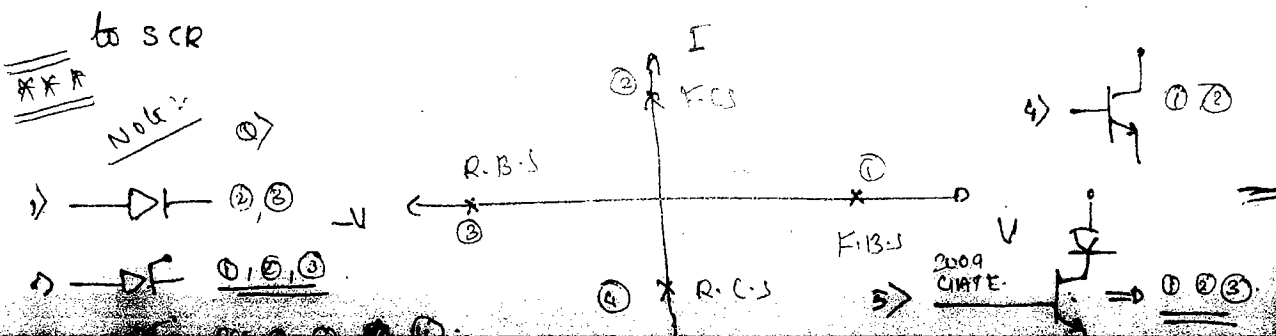9) ASCR (Asymmetrical thyristor)

- Asymmetrical thyristor, of the forward characteristics of the device are optimised compared to SCR. (Reduction in turn ON time, turn OFF time and on state voltage drop).
- The reverse voltage properties of ASCR are inferior compared



08) J_c & width of depletion layer

& knows q volt applied

$$C = \epsilon A / (d) \uparrow \uparrow (C/L)$$

$$I_g = 12 \text{ mA}$$

$$\frac{dV}{dt} = \frac{18}{800} \text{ V/s (critical)}$$

$$= 800 \times 10^6 \text{ V/s (critical)}$$

$$I_c \cdot C = C_j \frac{dV}{dt}$$

$$12 \times 10^{-6} = C_j \times 800 \times 10^6$$

$$C_j = \frac{12}{800} \times 10^{-12}$$

$$= \underline{\underline{0.15 \text{ pF}}}$$

09) $C_j = 20 \text{ pF}$ (under off stability)

$$I = 15 \text{ mA} \quad (15 \text{ mA})$$

$$= C_j + C_i$$

$$= 20 \times 10^{-12} + 0.01 \times 10^{-6}$$

$$= \underline{\underline{10.02 \times 10^{-9} \text{ F}}}$$

$$i = C \frac{dV}{dt}$$


$$15 \times 10^{-3} = 10.02 \times 10^{-9} \times \frac{dV}{dt}$$

$$\frac{dV}{dt} = \frac{15}{10.02} \times 10^6$$

$$= 1.5 \text{ V/}\mu\text{s}$$

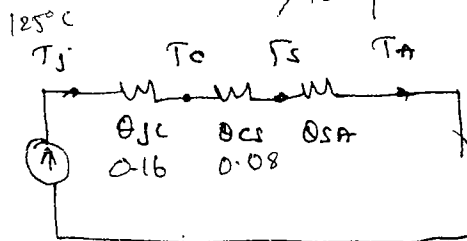10) For a thyristor

$$T_j = 125^\circ\text{C}, 70^\circ\text{C}/60^\circ\text{C}$$



$$P_{avg1} = \frac{T_j - T_s}{\theta_{JC} + \theta_{CS}}$$

$$= \frac{125 - 70}{0.16 + 0.08}$$

$$= \underline{\underline{229.16 \text{ J/s (or) W}}}$$

7. Maximum device

rating

$$P_{avg2} = \frac{125 - 60}{0.16 + 0.08}$$

$$= \underline{\underline{278.8 \text{ J/s (or) W}}}$$

$$\text{Rate of generation} = \text{Rate of dissipation}$$

$$\text{Rate of heat dissipat} \propto I^2 \times R_{avg}$$

$$\Rightarrow I \propto \sqrt{\text{Rate of dissipation}}$$


$$= \underline{\underline{8.717}}$$

$$10) \frac{V_g}{\dot{e}_g} = 20 \text{ V/A}$$

$$\tau_{ON} = 4 \text{ ns}$$

$$\dot{e}_g = 400 \text{ mA} = 0.4 \text{ A}$$

$$V_g \leq 15 \text{ V}$$

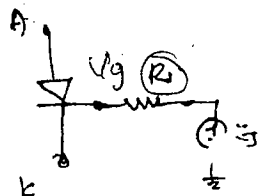

$$\frac{V_g}{\dot{e}_g} \times \dot{e}_g = 20 \times 0.4$$

$$V_g = \underline{\underline{8 \text{ V}}}$$

$$E_s = V_g + \dot{e}_g R_s$$

$$15 = 8 + 0.4 \times R_s$$

$$\underline{\underline{R_s = 17.5 \Omega}} \quad \left| \begin{array}{l} \text{Power loss} \\ P_{avg} = V_g \dot{e}_g \\ = 8 \times 0.4 \\ = \underline{\underline{3.2 \text{ W}}} \end{array} \right.$$

$$\text{Pulse width} = \tau_{ON}$$

$$P_{avg} = 0.2 \text{ W}$$

$$\boxed{P_{avg} = \delta \cdot P_{gm}}$$

$$= \frac{\tau_{ON}}{T} \cdot P_{gm}$$

$$= f \cdot \tau_{ON} \cdot \boxed{P_{gm}} = \underline{\underline{P_{gmax}}}$$

↓
Pulse frequency.

$$0.2 = f \times 4 \times 10^{-6} \times 3.2$$

$$= \underline{\underline{15.625 \text{ kHz}}}$$

$P_{gmax} = 0$ when pulse is available

$$\underline{\underline{P_m = 3.2 \text{ W}}}$$

$$13) f = 4 \text{ kHz}$$

$$\frac{\tau_{ON}}{T} = 0.2$$

Pulse width = ? μ

$$P_{gavg} = 1 \text{ W}$$

maximum allowable gate power

$$\text{duty} = ? = \underline{\underline{\delta}}$$

$$\text{duty cycle} \quad \delta = \frac{T_1}{T} = f \cdot T_1$$

$$0.2 = 4000 \times T_1$$

$$T_1 = \underline{\underline{50 \text{ ns}}}$$

$$P_{gavg} = \delta \cdot P_{gm}$$

$$1 = 0.2 P_{gm}$$

$$P_{gm} = \underline{\underline{5 \text{ W}}}$$

~~XXXX~~


$$14) \text{ For } V_g = 600 \text{ V} - 0 \text{ V}$$

$$I_g = 0 - 100 \text{ A}$$

$$\tau_{ON} = 5 \text{ ns}$$

I_g, V_g - linear transition
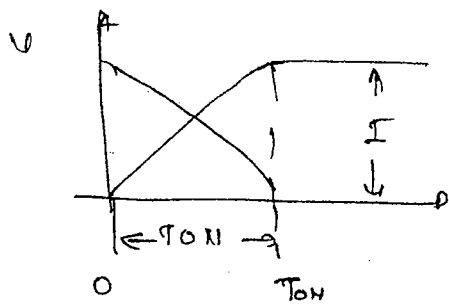
$$f = 100 \text{ kHz} \quad P_{gavg} = ?$$



$P_{g,avg} = \int \delta \cdot Z P_{g,m}$

$P_{avg} = \frac{1}{T} \int_0^{T_{ON}} P_i dt$

- After T_{ON} $V=0$. NO

power loss.

$P_{avg} = \frac{1}{T} \int_0^{T_{ON}} V \cdot I dt$

$V = V + slope$

$= V + \frac{0-V}{T_{ON}} (t)$

$V = V + \left(-\frac{V}{T_{ON}}\right) t$

$i = 0 + slope$

$= 0 + \left(\frac{I-0}{T_{ON}}\right) t$

$i = \frac{I}{T_{ON}} \cdot t$

$P_{avg} = \frac{1}{T} \int_0^{T_{ON}} \left(V - \left(\frac{V}{T_{ON}}\right) t\right) \cdot \left(\frac{I}{T_{ON}}\right) dt$

$= \frac{1}{T} \int_0^{T_{ON}} \left(\frac{VI}{T_{ON}} - \frac{VI}{T_{ON}^2} t\right) dt$

$= \frac{VI}{T} \left[\frac{1}{T_{ON}} \frac{t^2}{2} - \frac{1}{T_{ON}^2} \frac{t^3}{3} \right]_0^{T_{ON}}$

$= \frac{VI}{T} \left[\frac{T_{ON}^2}{2 \cdot T_{ON}} - \frac{1}{T_{ON}^2} \frac{T_{ON}^3}{3} \right]$

$= VI \cdot \frac{T_{ON}}{T} \left[\frac{1}{2} - \frac{1}{3} \right]$

$= VI \cdot \frac{T_{ON}}{T} \cdot \frac{1}{6}$

$P_{avg} = \frac{1}{6} VI \cdot \frac{T_{ON}}{T}$

$P_{avg} = \frac{1}{6} \cdot V I f \cdot T_{ON}$

$= \frac{1}{6} \times 100 \times 100 \times 5 \times 10^{-4}$

$P_{avg} = 0.833 \text{ W} \approx 0.8 \text{ W}$

$T_A = 50^\circ\text{C}$ $T_{J1} = 100^\circ\text{C}$

$P_{avg} = 50 \text{ W}$ ($T_{J2} = 40^\circ\text{C}$)

% Reduction in thermal resistance.

$\frac{100^\circ\text{C} - 50^\circ\text{C}}{100^\circ\text{C} - 40^\circ\text{C}}$

$\frac{50}{60} = 0.833$

$$P_{gaw_1} = \frac{T_j - T_A}{(\theta_{GC} + \theta_{SA} + \theta_U)} = \theta_1$$

$$\theta = \frac{50^\circ 100^\circ - 50^\circ}{50}$$

$$= \frac{50}{50} = \underline{\underline{1 \text{ VAR}}}$$

$$P_{gaw_2} = \frac{70 - 50}{\theta_2}$$

$$= \underline{\underline{0.4 \text{ VAR}}}$$

Y. Reduction θ

$$= \frac{1 - 0.4}{1} \times 100$$

$$= \underline{\underline{60\%}}$$

1) $P_{gaw} = 2W$

$P_m = 2W$

$f = 2 \text{ KHz}$

ratio mark to spaw ratio = ρ

$$P_{gaw} = \rho \cdot P_{gm}$$

$$\rho = \frac{20}{20} = 1/10 = \frac{T_1}{T}$$

$$\left. \begin{array}{l} \text{mark to spaw} = \frac{T_{ON}}{T_{OFF}} \end{array} \right\}$$

$$\rho = \frac{1}{10}$$

$$\frac{T_{ON}}{T_{OFF}} = \frac{1}{9}$$

1) $1/2 \text{ cycle } I_s = 3000A$

$f = 50 \text{ Hz}$
(supply)

one cycle $I_s = ?$

Surge current

$$I_1^2 t_1 = I_2^2 t_2$$

energy dissipation over
element is given by sum

$$\frac{I_1^2}{I_2^2} = \frac{t_2}{t_1}$$

$$\frac{3000^2}{I_2^2} = \frac{t_2}{1/50} \quad \frac{1}{50} = 20 \times 10^{-3}$$

$$t_1 = 1/2 \text{ cycle} = 10 \times 10^{-3}$$


$$t_2 = \text{full cycle} = 20 \times 10^{-3}$$

$$I_2^2 = \frac{I_1^2 t_1}{t_2}$$


$$= \frac{3000^2 \times 10 \times 10^{-3}}{20 \times 10^{-3}} = \underline{\underline{2250000}}$$

18) $I_L = 4 \text{ mA}$

IG9 Ton = width of gate pulse

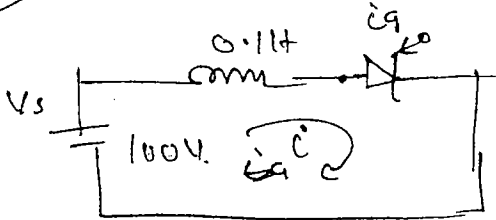

~~$I_a = I_L = I_{ON}$~~

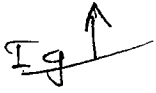

~~$I_g + I_a = I_L = I_{ON}$~~

Note

• The gate pulse should be applied to the SCR till the current reaches to latching current

$T = 0$, gate pulse.

$V_s = L \frac{di}{dt}$

$\int di = \int \frac{V_s}{L} dt$

$i = \frac{V_s}{L} t + k$

Initial condition

$t = 0^+$

Inductor = 0.c (0+)

$i = 0$

$0 = \frac{V_s}{L} t + k$

$k = 0$

then


$i = \frac{V_s}{L} t = i_L$

$4 \text{ mA} = \frac{100}{0.1} t$


$\Rightarrow t = 4 \text{ ms}$

Comment

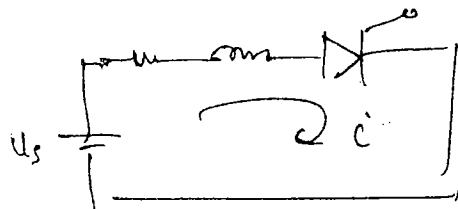
• adequate for 4ms, can be more should not be less




$i = \frac{V}{R} (1 - e^{-Rt/L})$

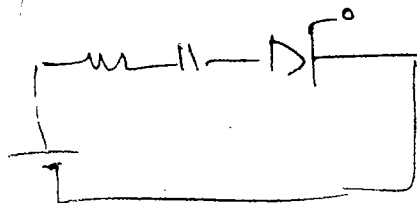

$i = \frac{V}{R} (1 - e^{-Rt/L})$

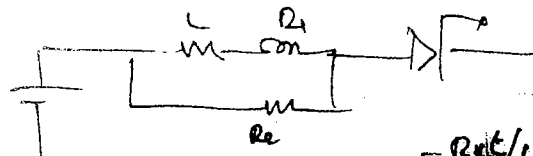

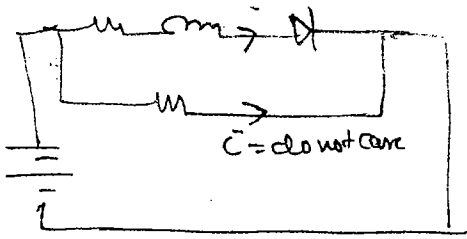$i(t) = \frac{V_s}{R} + \frac{V_s}{R} (1 - e^{-Rt/L})$




$$= \frac{100}{5 \times 10^3} + \frac{100}{20} \left(1 - e^{-\frac{20}{0.1} t}\right)$$

$$50 \text{ mA} = 0.02 + 5 \left(1 - e^{-200t}\right)$$

$$= 150 \mu\text{s}$$

Note:

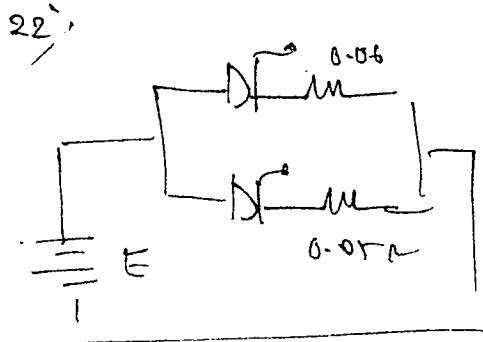• Evaluate the current formula passing through the thyristor and then equate it to the latching current value, to evaluate the minimum width of the gate pulse for reliable turn ON of the SCR.



19) $I_L = 12 \text{ mA}$

$$I_H > I_L$$

$$\frac{I_L}{I_H} = \frac{2.5 \text{ to } 3}{1}$$

$$I_m = 0.06$$


$$I_m \times 0.66 = I_g \times 0.05$$

$$I_m = \frac{120 \times 0.05}{0.066} = 100 \text{ A}$$

$$= 100 \text{ A}$$


20) ✓

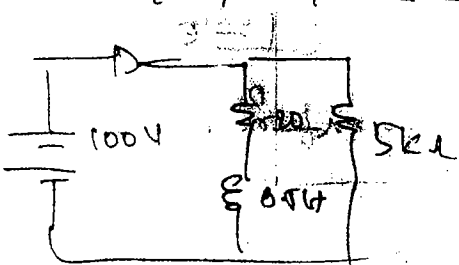21) H.W. $F_{OM} = 50$ $I_C = 50 \text{ A}$ $I_T = 40 \text{ mA}$



22) 23) H.W.

32) $100 \text{ A} = I_g$

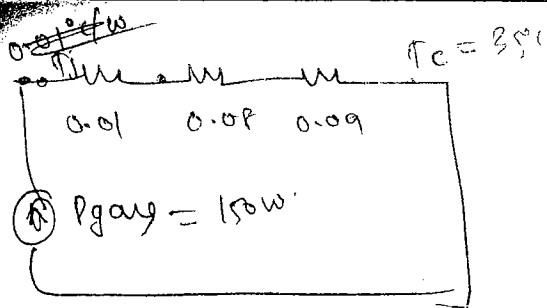


$$P_{gay} = \frac{T_j - T_c}{\theta}$$

$$\theta \cdot P_{gay} + T_c = T_j$$

$$T_j = 0.19 \times 150W + 35^\circ$$

$$= \underline{\underline{62^\circ C}}$$

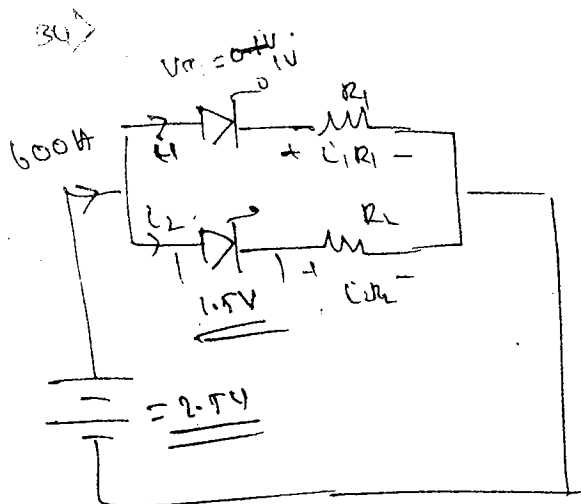

$$I_1 + I_2 = 600mA$$

$$I_1 = \alpha + 10\%$$

$$= 330, 370'$$

\Rightarrow drop in $V_o =$ current change

or more

$$\Rightarrow I_1 = \underline{\underline{330' A}}$$

$$\Rightarrow I_2 = \underline{\underline{270' A}}$$

$$V + I_1 R_1 = 2.5V$$

$$R_1 = \frac{V}{I_1} = \frac{1.5}{330}$$

$$P_{avg} = \frac{150 - 25}{1} = 125 (W)$$

$$P_{gay} = \theta \cdot P_{gmax}$$

$$R_2 = \frac{2.5 - 1.5}{270} = 1.7$$

$$330R + 1 = 270R + 1.7$$

1) CHARACTER


1) PHASE CONTROLLED RECTIFIERS

$i_d = I_m \cdot \omega \cdot R \Rightarrow V_o = \frac{V_m}{\pi} \Rightarrow D \rightarrow T \quad 0 - \frac{V_m}{\pi}$

$i_d = F \cdot \omega \cdot R \Rightarrow V_o = \frac{2V_m}{\pi} \Rightarrow D \rightarrow T \quad 0 - \frac{2V_m}{\pi}$
 ↑
 Diode

→ It is a static power electronics circuit, which converts AC to variable DC. i.e. variation in the magnitude of the voltage.




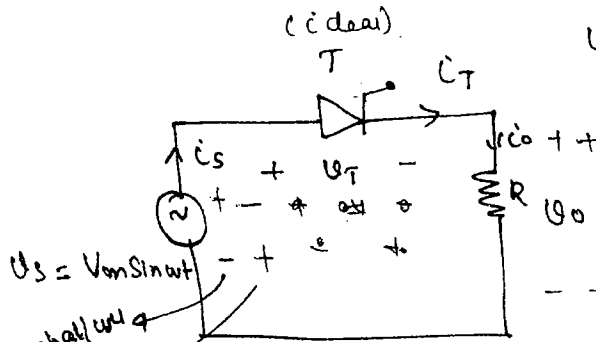
1) Single phase Half wave Rectifier with R-load.



$U_s = V_m \sin \omega t$
 - Vorhalbwelle
 - Nachhalbwelle
 $i_o = \text{output voltage}$

$i_s = \text{output current}$
 $i_T = \text{thyristor current}$
 $i_s = \text{source current}$

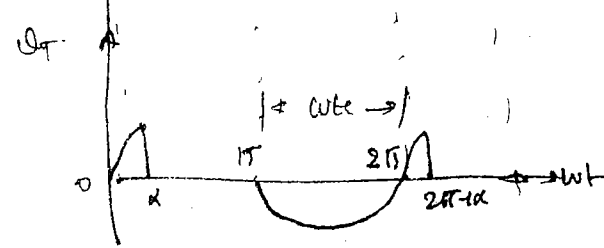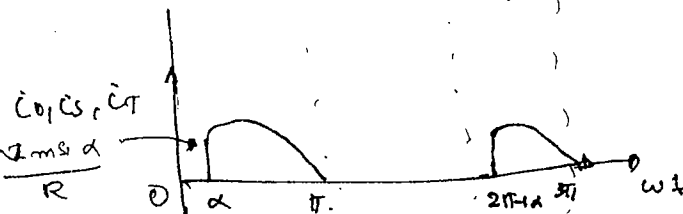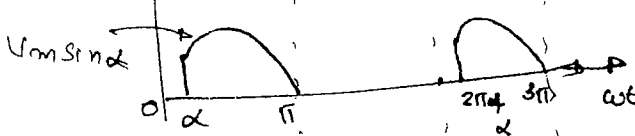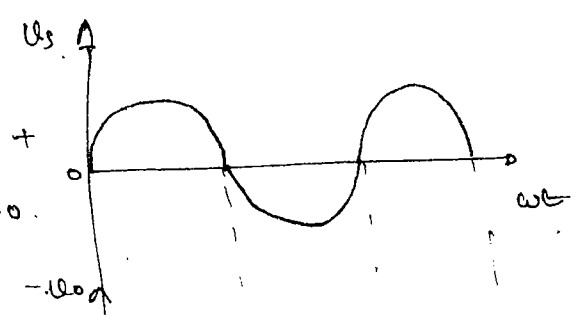$i_s \Rightarrow i_T = i_o \text{ (here)}$



Phase controlled rectifier operations is based on, line (or) Natural commutation. Natural zero of current through the SCR and application of reverse voltage are occurring by the nature of input ac supply. So it is called line (or) Natural commutation.

$t_{tc} =$ circuit turn OFF time

$$= 2\pi - \pi$$

$$t_{tc} = \frac{\pi}{\omega} \text{ sec}$$

\Rightarrow If $f = 50\text{Hz}$, $t_{tc} = 10\text{ms}$ (1/2 cycle). SCR which has to be used here should have more than 10ms

Note:

The SCR is to be selected such that device turn-off time has to be less than the circuit turn OFF time.

$$V_{o \text{ avg}} = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \, d\omega t$$

$$= \frac{V_m}{2\pi} [-\cos \omega t]_{\alpha}^{\pi} = \frac{V_m}{2\pi} [\cos \alpha - (-1)]$$

$$V_{o \text{ avg}} = \frac{V_m}{2\pi} [1 + \cos \alpha]$$

rms Value

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \, d\omega t} =$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\pi} (1 - \cos 2\omega t) \, d\omega t} = \frac{V_m}{\sqrt{2}} \sqrt{\left[\omega t - \frac{1}{2} \sin 2\omega t \right]_{\alpha}^{\pi}}$$

Forward Blocking state

=> After application of F. Voltage, again No conduction

=> we cannot say '0', due to minority carrier

Forward leakage current (minority current, produced

at the forward blocking state) (represented in static chara graph)

Note ***

=> Power Electronics, we have only one application as

SWITCH

- here Blocking state, SCR device acts as OPEN SWITCH

- ideal chara of OPEN SWITCH

$$V = V_s \text{ (applied)}$$

$$I = 0$$

- here ideal case $V = 100 \text{ V}$

$$I = 0$$

- in a static switch, current $I \neq 0$ ~~is~~

85

in FB state $J_1 J_3 \text{ FB}, J_2 \text{ RB}$, in this state SCR is equivalent to OPEN SWITCH

TURNING ON SCR

Forward Blocking state $\xrightarrow{\text{ON}}$ Forward conduction state

OFF

~~TURN ON~~ and OFF

TURN ON of SCR means Forward Blocking state & Forward conduction state. TURN OFF means Forward conduction state to Forward Blocking state.

In Forward Blocking state to Forward conduction state

$J_1 J_3 - F.B$

$J_2 - R.B$ This is for when conduction is

blocked.

- means the applied voltage, a very high voltage

D.B Breakdown occurs, Avalanche Breakdown, J_2 opens hence SCR starts conduction.

The above method is called FORWARD VOLTAGE TRIGGERING

The amount of F. Voltage required to turn ON SCR is

called FORWARD BREAK ~~DOWN~~ ^{OVER} VOLTAGE

Q1
FORWARD VOLTAGE TRIGGERING

When a high FV is applied due to which R.B. J_2 junction gets breakdown (Avalanche), hence the device starts CONDUCTION.

The amount of Forward Voltage required to turn ON the SCR (without CMPE PULSE) is known as F. BREAKOVER VOLTAGE.

$$V_{rms}^2 = \frac{V_m^2}{4\pi} \left[\pi - \alpha + \frac{1}{2} \sin 2\alpha \right] \quad \left\{ \sin \pi = 0 \right\}$$

$$V_{rms} = \frac{V_m}{2\sqrt{\pi}} \left[\pi - \alpha + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

12/02/10

6-9 AM = M-II

9.30-11 = 11 AM

SECRET

6-9.30 - PE

30%

11/11 Current

$I_{avg} = \frac{V_0}{R}$	$I_{or} = \frac{V_{or}}{R}$ (RMS)
---------------------------	--------------------------------------

19/02/11


Phase angle will be supply voltage and current gets controlled with the variation of α and it is also known as phase controlled Rectifier.


Alternatively power factor can be evaluated by equating power on dc side = Power on ac side.

$$P_{ac} = P_{dc} \Rightarrow V_s I_s \cos \phi = V_s \cdot I_{sr} \cdot P_f = P_{dc}$$

$$\Rightarrow P_f = \frac{P_{dc}}{V_s \cdot I_{sr}} = \frac{\text{Power delivered to dc load}}{\text{Source Volt amps}}$$

Note:

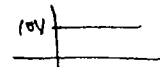rms value \Rightarrow dc component + Ac component  $V_{rms} = 10V$
 $V_{dc} = 10V$

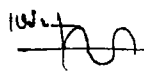avg value \Rightarrow dc component only  $V_{rms} = 10$
 $V_{dc} = 0$

$$\Rightarrow P_f = \frac{V_{or}^2}{V_s \cdot I_{sr}} = \frac{V_{or}^2 / R}{V_s \cdot V_{or} / R} = \frac{V_{or}}{V_s} \quad \boxed{P_f = \frac{V_{or}}{V_s}}$$

\rightarrow In the power electronics circuit power factor may be variable with the variation of the firing angle. The starting of the current w.r.t time depends on the firing angle of the circuit.

as the firing angle changes, power factor also changes.


*** α and o/p voltage

- If $\alpha < 90^\circ$, ~~or $\alpha < 90^\circ$~~ , maximum value of instantaneous output

voltage is V_m .

- If $\alpha > 90^\circ$, the maximum value of instantaneous output voltage

is $V_m \sin \alpha$.

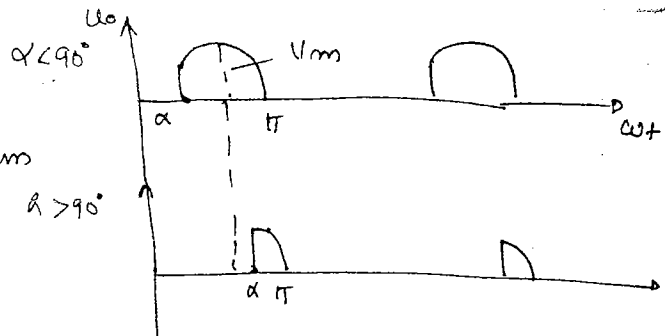

→ $V_o = \frac{V_m}{2\pi} [1 + \cos \alpha]$ • Range of α ~~is~~ $0 < \alpha < \pi$

• $\alpha = 0 \Rightarrow V_o = \frac{V_m}{\pi}$

• $\alpha = \pi \Rightarrow V_o = 0$ { $\cos \pi = -1$ }

- If we are varying α from $0 - \pi$, o/p voltage varies from $(0 - \frac{V_m}{\pi})$

- Range of firing angle ($0 - \pi$), when the firing angle increases, the

o/p voltage decreases. (Area under the curve decreases)

→ circuit turn OFF time = $\frac{\pi}{\omega_c}$

Advantage of F.W.D

- ▷ Average power consumption is increased,
- ▷ Power factor also will be improved.
- ▷ Circuit turn OFF time would be, more (π/ω) . and on the same time it is of FIXED VALUE.

$$V_o = \frac{V_m}{2\pi} [1 + \cos \alpha] \quad \cdot \quad V_{or} = \frac{V_m}{2\sqrt{\pi}} [\pi - \alpha + \frac{1}{2} \sin 2\alpha]^{1/2}$$

$$I_o = V_o/R \quad \cdot \quad I_{or} = V_{or}/R, \quad P_f = \frac{V_{or}}{V_s}$$

$$\frac{20/0.2/12}{7-1 = N/\omega \cdot 305}$$

$$2-5.30 = P.E \cdot 308$$

$$6-8.30 = m \cdot \pi \cdot 308$$


NOB:

F.W.D

- Power diode.
- Diode is wheeling/circulating without taking any energy/power from supply lines directly, the current through the diode is determined by L.

STY

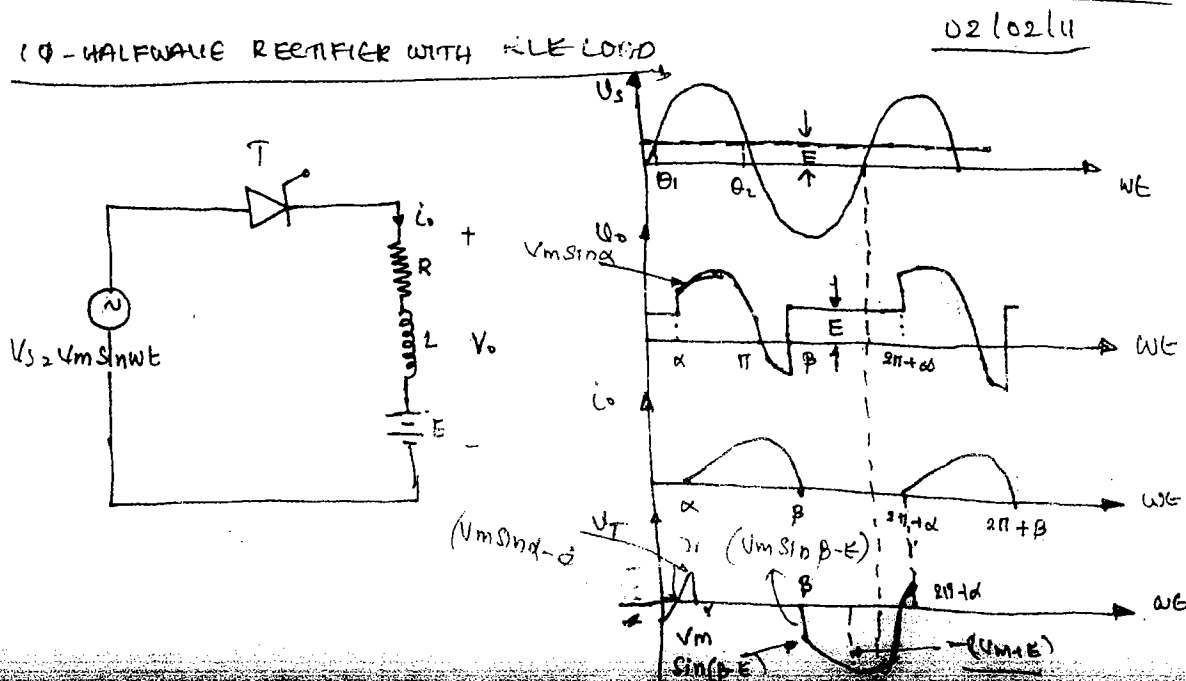- Diode is circulating current on the load, without consuming any energy from supply lines, it may be known as Free wheeling diode.



• Range of Firing angle (θ_1 to θ_2).

• at θ_1 & θ_2

At $\omega t = \theta_1$, $V_s = E$

or $V_m \sin \theta_1 = E$

$$\theta_1 = \sin^{-1} \left(\frac{E}{V_m} \right) \quad \text{OBJ.}$$

$$\Rightarrow \theta_2 = \pi - \theta_1$$

• If the SCR is not in the conduction output voltage is equal to E . If the SCR is in the conduction output voltage is same as the supply voltage.

*** B Values

- In the case of RE load $\beta = \theta_2$.
- In the case of RLE load $\beta > \theta_2$. But β may be less than π or greater than π .

• PIV Rating of the SCR = $(V_m + E)$.

• Voltage across SCR at the time it is starting the conduction = $(V_m \sin \alpha - E)$

• Voltage across SCR at the time it is stopped the conduction = $(V_m \sin \beta - E)$

Here

$$\text{Average of p voltage} = \boxed{V_o = E + I_o R}$$

Derivation for I_o

$I_o =$ Average of p current

$$= \frac{1}{2\pi} \int_{\alpha}^{\beta} \frac{V_m \sin \omega t - E}{R} d\omega t = \frac{V_m}{2\pi R} \left[-\cos \omega t - E(\omega t) \right]_{\alpha}^{\beta}$$

$$\Rightarrow \boxed{I_o = \frac{1}{2\pi R} \left[V_m (\cos \alpha - \cos \beta) - E (\beta - \alpha) \right]}$$



$$V_o = E + I_o R.$$

KVL at arrow 0 to $(\pi - 2\alpha)$

$$\Rightarrow R i + L \frac{di}{dt} + E = V_m \sin \omega t$$

$$\Rightarrow i = \frac{V_m \sin \omega t - E}{2\pi R}$$

II > HALF WAVE RECTIFIER WITH R-L

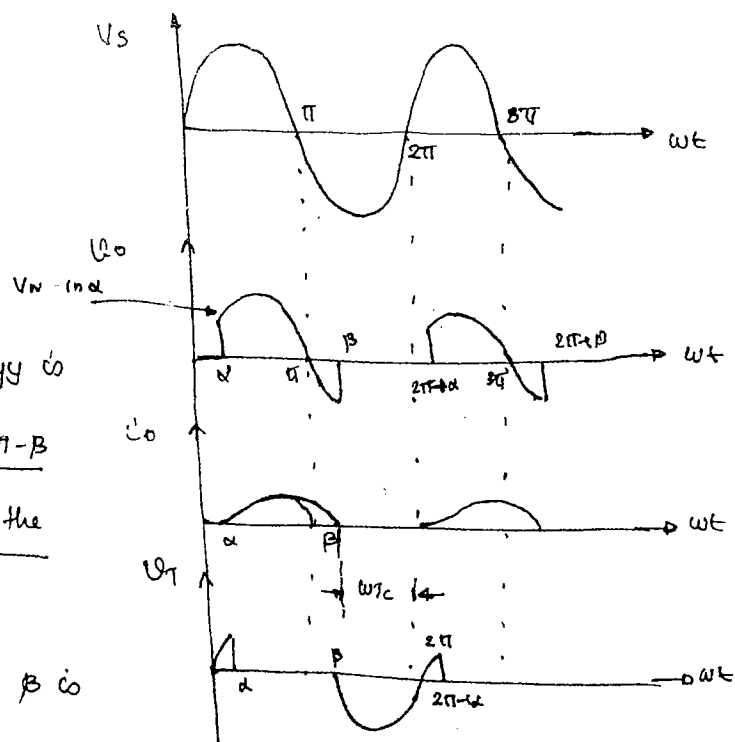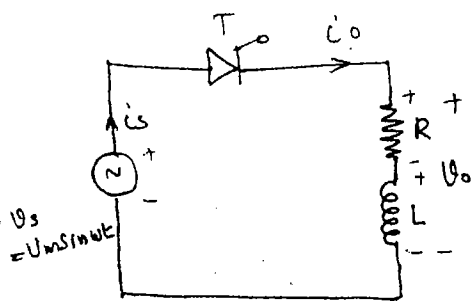

• During $\alpha - \pi$ conduction energy is given by the supply lines. and $\pi - \beta$ it is given by stored energy of the inductor.

• In the case of R-L load, β is greater than π ($\beta > \pi$) and its value depends on the stored energy of the inductor.

• ωT_c = period in which thyristor is subjected to reverse voltage.

$$= 2\pi - \beta = \omega T_c \Rightarrow T_c = \frac{2\pi - \beta}{\omega} \text{ Sec}$$

$$V_o = \frac{1}{2\pi} \int_{\alpha}^{\beta} V_m \sin \omega t \, d(\omega t) = \frac{V_m}{\pi} \left[-\cos \omega t \right]_{\alpha}^{\beta}$$

$$V_o = \frac{V_m}{2\pi} [\cos \alpha - \cos \beta]$$

β = Extinction angle

$$V_{or} = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\beta} V_m^2 \sin^2 \omega t \, d(\omega t)}$$

$$V_{or}^2 = \frac{V_m^2}{4\pi} \left[\omega t - \frac{1}{2} \sin 2\omega t \right]_{\alpha}^{\beta}$$

$$= \frac{V_m^2}{4\pi} \left[\beta - \alpha + \frac{1}{2} (\sin 2\alpha - \sin 2\beta) \right]$$

$$V_{or} = \frac{V_m}{2\sqrt{\pi}} \left[\beta - \alpha + \frac{1}{2} (\sin 2\alpha - \sin 2\beta) \right]^{1/2}$$

• $I_o = \frac{V_o}{R}$; Note $- Z = R + j\omega L$
 $= R + j(2\pi f)L$

• $I_{or} = \frac{V_{or}}{R}$:

$f = 0$ we dont have cyclic frequency.

\Rightarrow current varies across the device in

• Input supply p.f

$= \frac{\text{Power delivered to the load}}{\text{Source VA}}$ unidirectional.

$= \frac{V_{or}^2/R}{V_s I_{sr}} = \frac{I_{or}^2/R}{V_s \cdot V_{or}/R} = \frac{V_{or}}{V_s} = D$ Input supply p.f = $\frac{V_{or}}{V_s}$


• During $(\alpha - \pi)$ power is +ve (V_o is +ve, I_o is +ve) and $(\pi$ to $\beta)$ power is negative (V_o is -ve, I_o is +ve) hence the average power consumption would be decreased.

• Circuit turn off time would be less than $\frac{\pi}{\omega}$ and it is of variable.

Note:


• A Diode will be connected across the load terminal to return the power to the load (or) to stop the power flow to the supply lines. This diode is known as FREE WHEELING DIODE

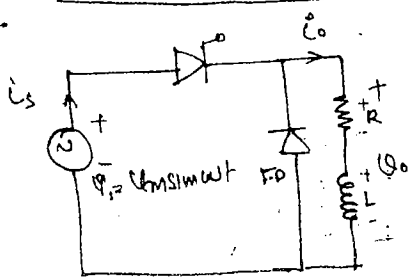III) ϕ HALF WAVE RECTIFIER WITH R-L LOAD and Free wheeling diode



$\omega t_c = \pi$ (TURN OFF)

• $t_c = \frac{\pi}{\omega}$ s

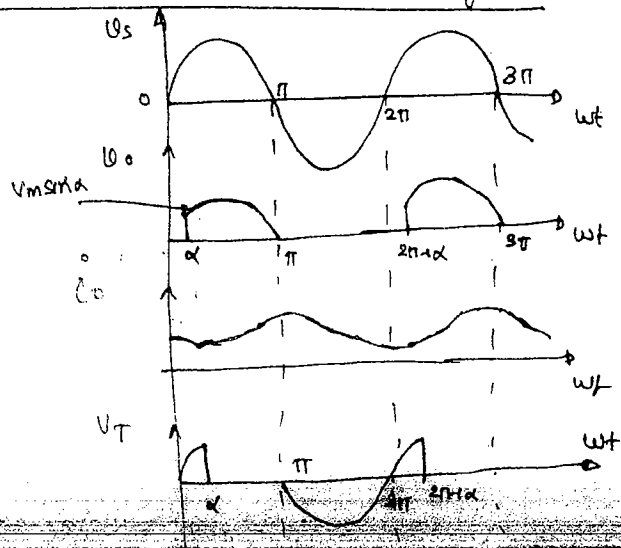

$$I_{O\alpha} = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\beta} \left(\frac{V_m \sin \omega t - E}{R} \right)^2 d\omega t} \quad (\text{H.W.})$$

Power Factor

$$= \frac{\text{Power delivered to load}}{\text{source volt Ampere.}}$$

- E takes average power through average value (DC component) of current.
- R takes power through rms value of current


$$P.f = \frac{E I_0 + I_0^2 R}{V_s I_{s\alpha}}$$

CIRCUIT FOR NOFF TIME.

$$t_c = \frac{2\pi + \theta_1 - \beta}{\omega}$$

- In the RLE load if the SCR is lugged continuously, then it starts conduction from θ_1 onwards ($\alpha = \theta_1$)
- In the R load (or) RL load if the SCR is lugged continuously, then $\alpha = 0$.

1 ϕ HALF WAVE RECTIFIER FOR R-E LOAD.

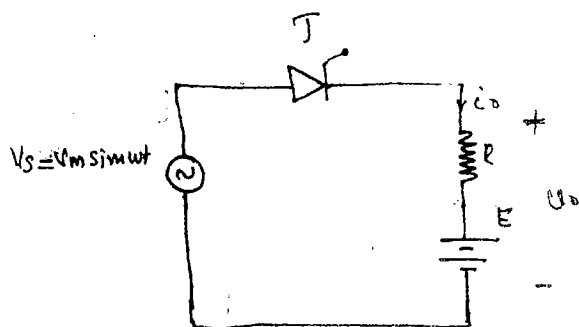

• Range of firing angle
 = $\underline{\underline{\theta_1 \text{ to } \theta_2}}$

• $\theta_1 = \sin^{-1}\left(\frac{E}{V_m}\right)$

$\theta_2 = \pi - \theta_1$


• Average current through R = I_o

$$I_o = \frac{1}{2\pi} \int_{\alpha}^{\beta} \frac{V_m \sin \omega t - E}{R} \cdot d\omega t$$

$$= \frac{1}{2\pi} \left[V_m (-\cos \omega t) - E(\omega t) \right]_{\alpha}^{\theta_2}$$



$$= \frac{1}{2\pi R} \left[V_m (\cos \alpha - \cos \theta_2) - E(\beta - \alpha) \right]$$

$V_o = E + I_o R$

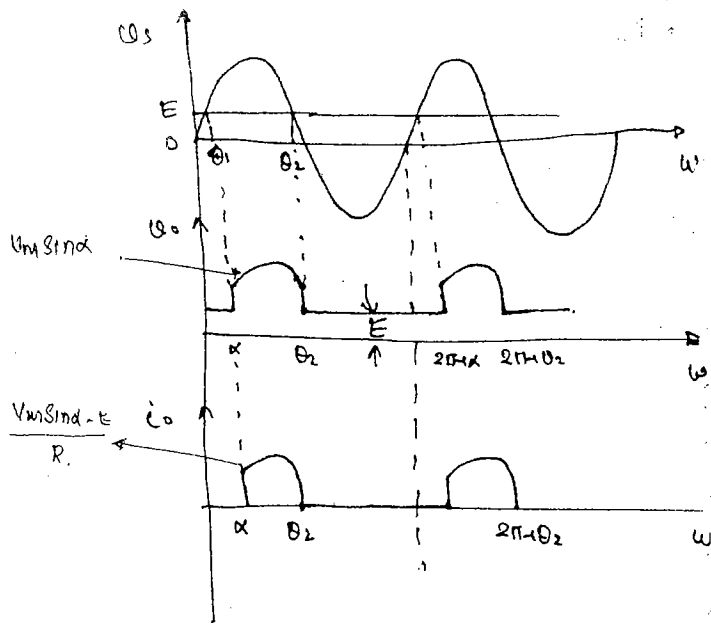

➤ FULL WAVE RECTIFIER

➤ 1ϕ FULL WAVE MID POINT RECTIFIER

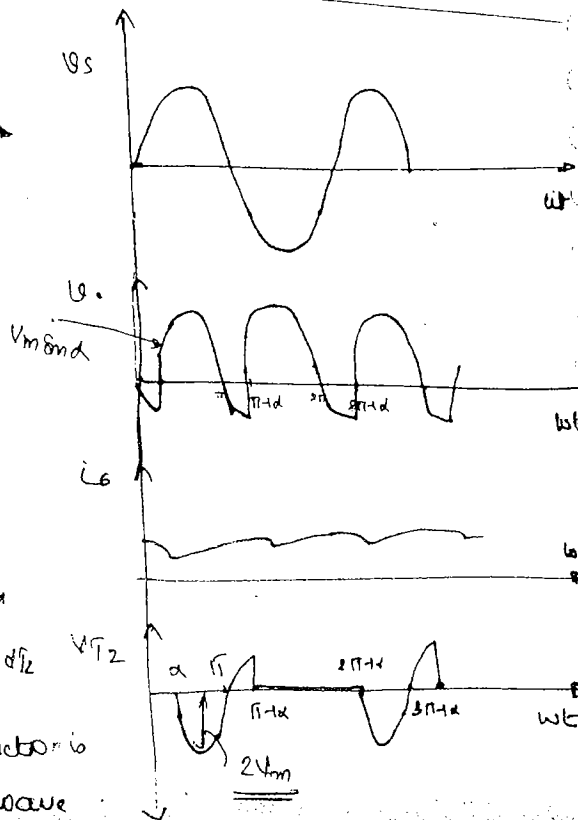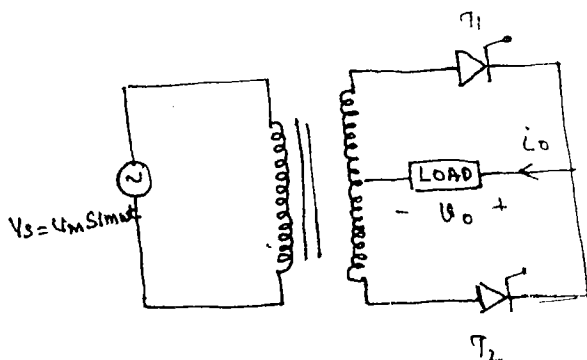

• Number of turns in the secondary is taken to such that it gives same $V_m \sin \omega t$ for T_1 and T_2

• The chance of getting the continuous conduction is more in Full wave rectifier compared to half wave

• W.O.P wave form consists of 2-pulses for one input cycle. so it is known as single phase 2-pulse Rectifier.

• Pulse frequency obtained here is 2 times the supply frequency.

• $2V_m$ is the peak or V_{om} voltage.

V_o = Average o/p voltage.

$$V_o = \frac{1}{\pi} \int_{\alpha}^{\pi-\alpha} V_m \sin \omega t \, d(\omega t)$$

$$= \frac{V_m}{\pi} [-\cos \omega t]_{\alpha}^{\pi-\alpha} = \frac{V_m}{\pi} [\cos \alpha - \cos(\pi - \alpha)]$$

$$V_o = \frac{2V_m}{\pi} \cos \alpha$$

$$I_o = \frac{V_o}{R}$$

$$V_{or} = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi-\alpha} V_m^2 \sin^2 \omega t \, d(\omega t)}$$

$$= \frac{V_m}{\sqrt{2}} \int_{\alpha}^{\pi-\alpha} \frac{1 - \cos 2\omega t}{2} \, d(\omega t)$$

$$= \frac{V_m}{2\sqrt{2}} \left[\omega t - \frac{1}{2} \sin 2\omega t \right]_{\alpha}^{\pi-\alpha} \quad \left\{ \sin 2\pi + 0 = \sin 0 \right\}$$

$$= \frac{V_m}{2\sqrt{2}} \left[\pi - \alpha - \alpha + \frac{1}{2} \left\{ \sin(2\pi - 2\alpha) - \sin 2\alpha \right\} \right]$$

$$V_{OVR}^2 = \frac{V_m^2}{\sqrt{2}} \Rightarrow \boxed{V_{OVR} = \frac{V_m}{\sqrt{2}}}$$

$$V_{OR} = \frac{V_m}{\sqrt{2}} = V_s$$

$$I_{OR} = \frac{V_{OR}}{R} \quad \boxed{PF = \frac{V_{OR}}{V_s}}$$

Voltage Rating of SCR

- $2V_m$, $280V = V_s \Rightarrow$ Rating = $460V$.
- $\cos \phi \uparrow$
- TFR required \uparrow
- SCR size \uparrow


Disadvantages

1) The PIV rating of the SCR is 2 times of the maximum value of supply voltage



2) It needs a COSTLY mid point transformer.

03/03/11

1- FULLWAVE BRIDGE RECTIFIER.

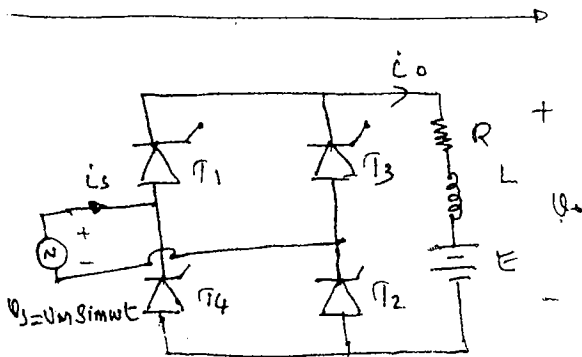

OBJC)

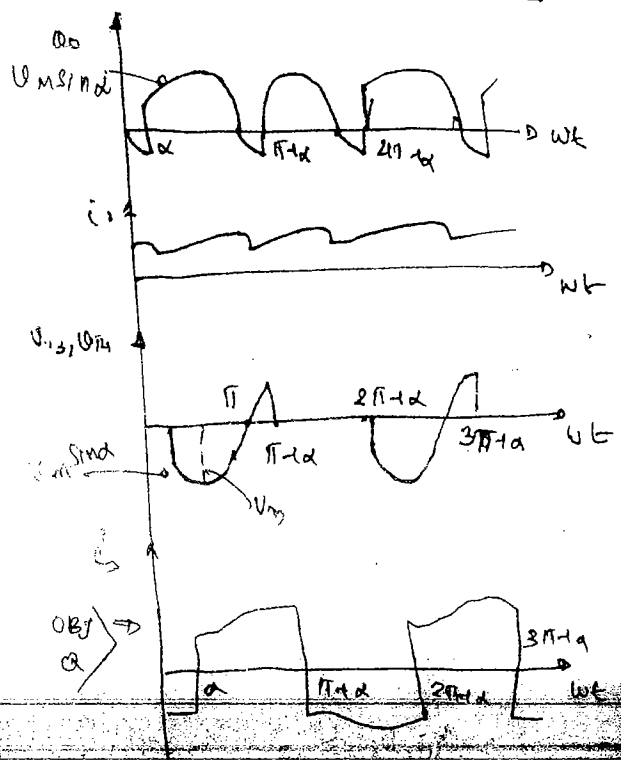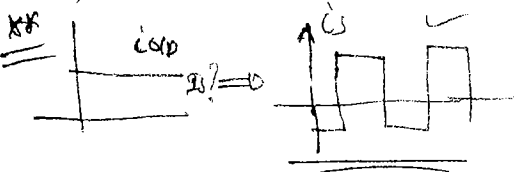

- If the o/p current is assumed to be constant then the shape of supply current would be square wave form.
- PIV rating of the SCR is same as maximum value of supply voltage.

→ Average voltage

$V_o = \frac{2V_m}{\pi} \cdot \cos \alpha$
$V_{or} = V_s$
$I_o = \frac{V_o - E}{R}$
$I_{or} = \frac{V_{or} - E}{R}$

$P_f = \frac{EI_o + I_{or}^2 R}{V_s I_{sr}}$ (REV)

→ motoring Application

$$\alpha < 90^\circ, V_o > E$$

→ generator Application

(REGENERATIVE BRAKING)

$$\alpha > 90^\circ \Rightarrow E \text{ reversed. } \Rightarrow E > V.$$

$$E = \frac{\cancel{Z} \phi \cancel{N}}{\cancel{60}} \times \frac{R}{R} (\phi_{-ve}) \Rightarrow E(-ve)$$

• traction N cannot make -ve.

- If $\alpha > 90^\circ$ then the average output voltage is negative. also the average o/p power would be negative. Hence, the power flows from DC load to AC source. This operation is known as line-commutated inverter.

- Regenerative braking employs the principle of line commutated inverter, the following conditions are to be satisfied for the


Regenerative Braking.

i) $\alpha > 90^\circ$

ii) E should reverse its polarity

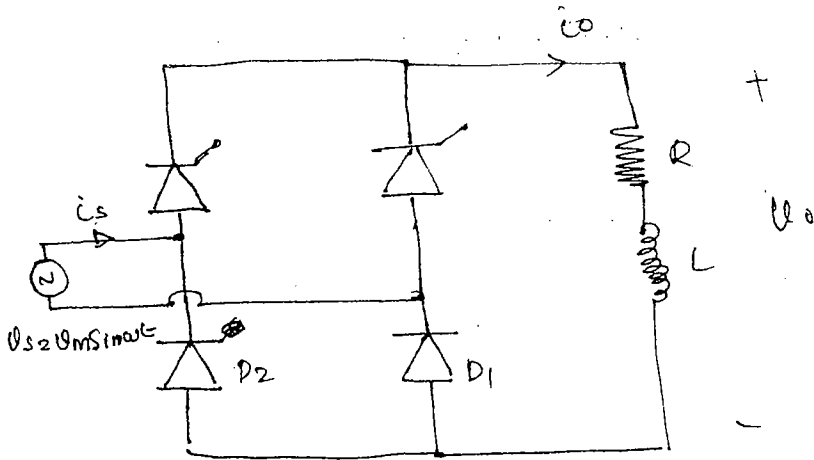iii) $E > V$ (generated > terminal)

1 ϕ - SEMI CONVERTER (OR) 1 ϕ - HALF CONTROLLED RECTIFIER.




Average Voltage

$$V_o = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \, d(\omega t)$$

$$= \frac{V_m}{\pi} [-\cos \omega t]_{\alpha}^{\pi}$$

$$= \frac{V_m}{\pi} [\cos \alpha - \cos \pi]$$
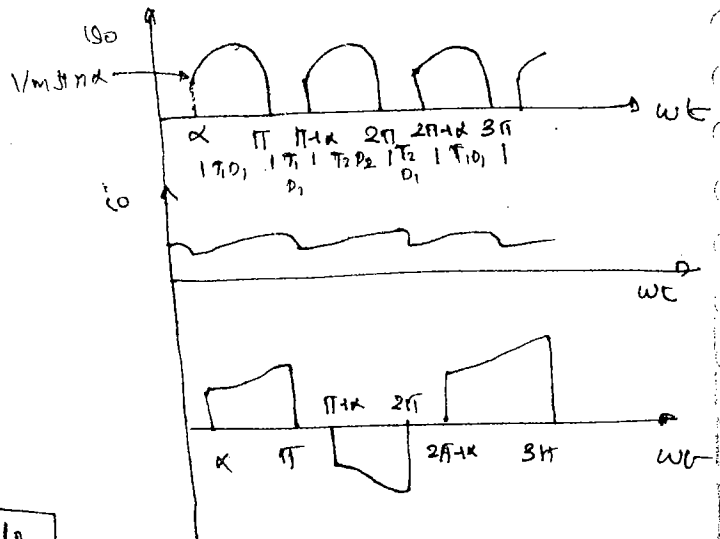
$$V_o = \frac{V_m}{\pi} [1 + \cos \alpha] \quad I_o = \frac{V_o}{R}$$



$$V_{or} = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \, d(\omega t)}$$

$$V_{or}^2 = \frac{1}{\pi} \int_{\alpha}^{\pi} \frac{1 - \cos 2\omega t}{2} \, d\omega t = \frac{V_m^2}{2\pi} [\omega t - \frac{1}{2} \sin 2\omega t]_{\alpha}^{\pi}$$

$$= \frac{V_m^2}{2\pi} [\pi - \alpha + \frac{1}{2} \sin 2\alpha]$$

$$V_{or} = \frac{V_m}{\sqrt{2\pi}} [\pi - \alpha + \frac{1}{2} \sin 2\alpha]^{1/2}$$

$$I_{or} = \frac{V_{or}}{R}$$

Input supply

$$PF = \frac{V_{or}}{V_s}$$


• In the semi-converter, average output voltage is always +ve. The average i/p voltage can be controlled only on positive side, so it is known as 1 ϕ half controlled rectifier.

• A 1 ϕ Full wave rectifier average o/p voltage can be controlled both +ve side and -ve side so it is known as single phase Fully controlled rectifier.


• In a Full wave bridge Rectifier a free wheeling diode is employed then it will be same as the semi-converter. and o/p voltage will always be positive.


Quadrant operation

- No ~~output~~ -ve cur
- V_o always +ve

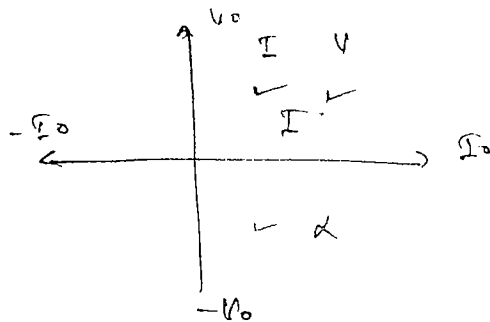

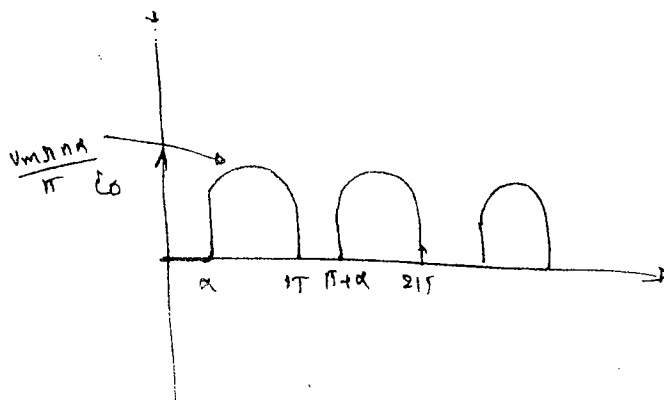*E
• 1 ϕ Full wave Rectifier with R-load.



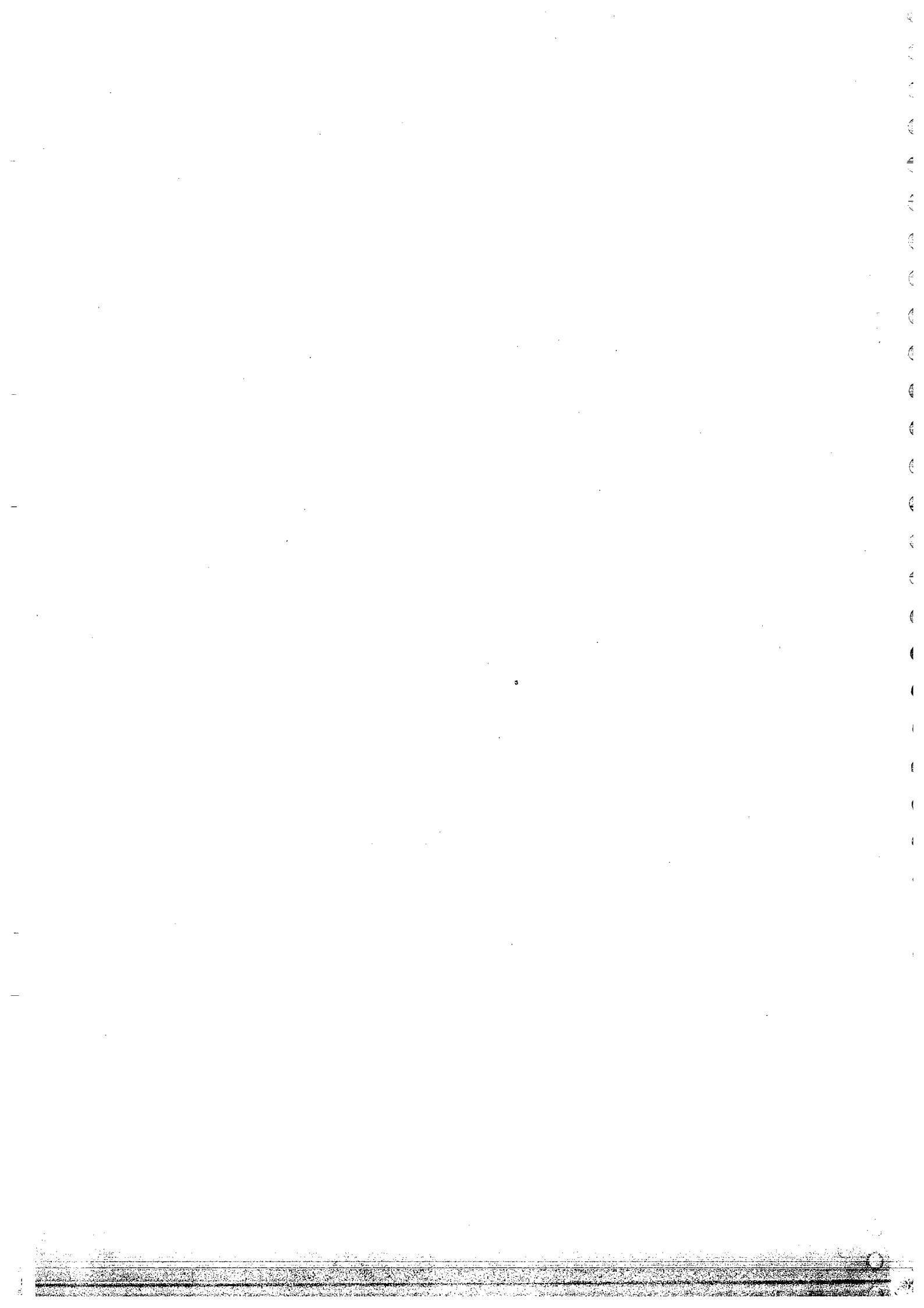

*
 $V_o = \frac{V_m}{\pi} (1 + \cos \alpha)$ $I_o = \frac{V_o}{R}$ $V_{or} = \frac{V_m}{\sqrt{2\pi}} [1 - \alpha + \frac{1}{2} \sin 2\alpha]^{1/2}$

$I_{or} = \frac{V_{or}}{R}$ Input supply pf = $\frac{V_{or}}{V_s}$

1 ϕ Full wave Rectifier with R-E load. (1+10)

3 ϕ HALF WAVE DIODE RECTIFIER:

2/03/11

a) Common cathode configuration b) Common anode configuration.

Common cathode configuration

• In common cathode configuration only one diode which ever is subjected to more +ve charge voltage will be in conduction.

• At any time the load is connected to one phase and neutral wire hence it subjects to phase voltage only.



• The d/c waveform has 3 pulses per every input cycle so it is known as 3 ϕ , 3 pulse rectifier.

• Pulse frequency is 3 times supply frequency

• Pulse duration is 120° , conduction time of each phase is 120° , conduction time of each diode is

$$V_o = \frac{1}{2\pi/3} \int_{150^\circ}^{30^\circ} V_{mp} \sin \omega t \, d\omega t$$
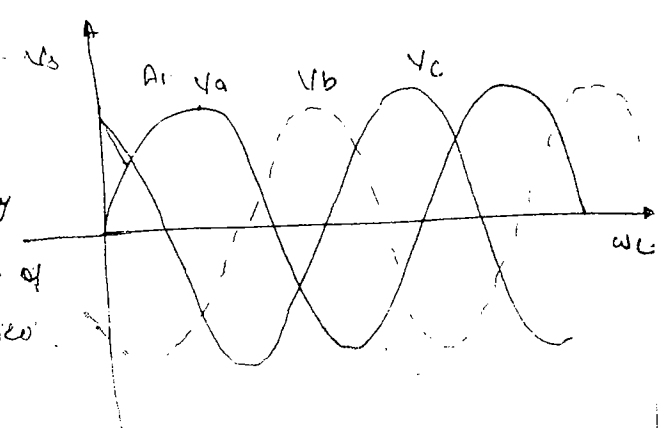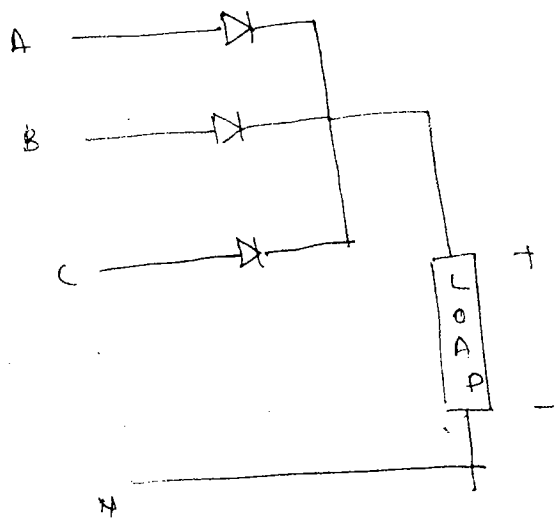
$$= \frac{3V_{mp}}{2\pi} [-\cos \omega t]_{30^\circ}^{150^\circ} = \frac{3V_{mp}}{2\pi} [-\cos 150^\circ + \cos 30^\circ] = \frac{3V_{mp}}{2\pi} [2 \cos 30^\circ]$$




$V_o = \frac{3V_{mp}}{2\pi} [2 \cos 30^\circ]$

$$V_{avr} = \sqrt{\frac{1}{2\pi/3} \int_{30}^{150} V_{mp}^2 \sin^2 \omega t \, d(\omega t)}$$

Common anode configuration:

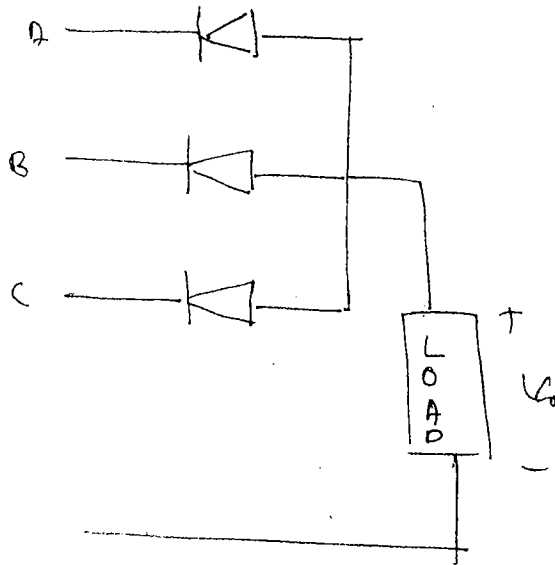
→ In common anode configuration only one diode, which ever is subjected more -ve voltage will be in conduction



→ At any time load will be connected between phase and neutral wires hence, it will be subjected to phase voltages only

→ The polarity of the ~~the~~ voltage is always -ve peak instantaneous

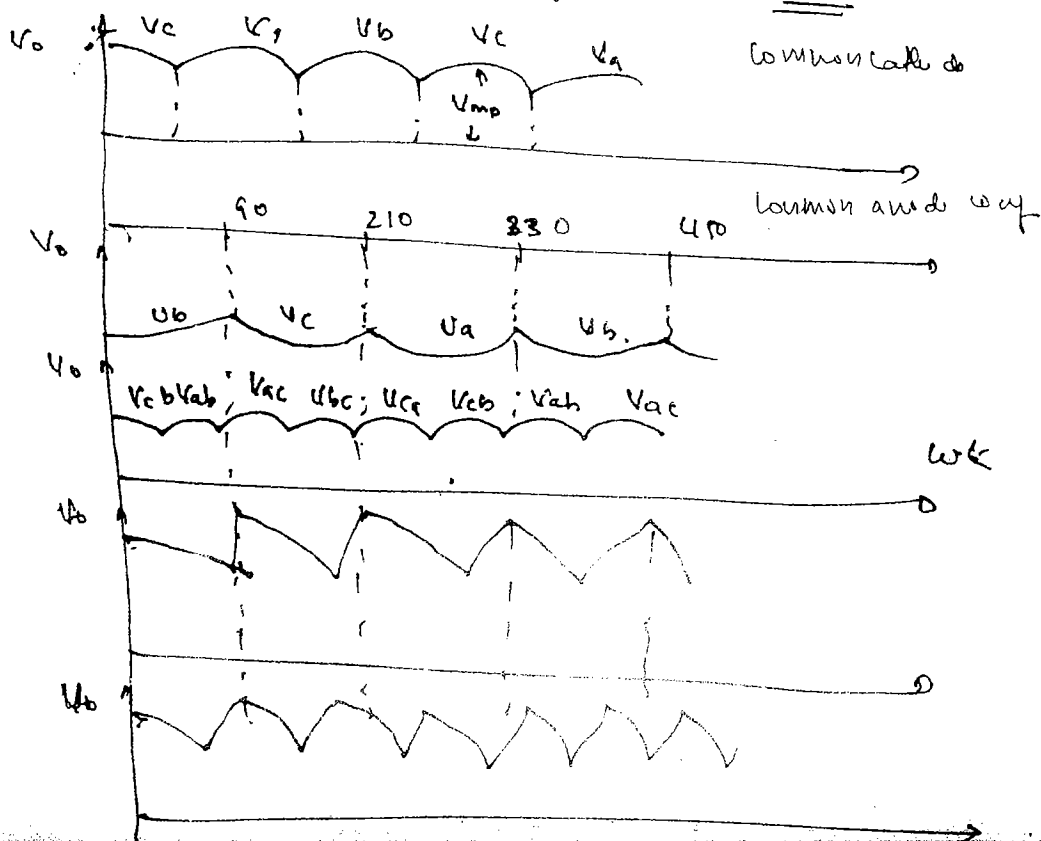
slp voltage is equal $V_{mp} \rightarrow$ PIV rating of diodes is V_{ml} .



3- ϕ Full wave Bridge Rectifier

It can be obtained by merging common cathode and common anode configurations

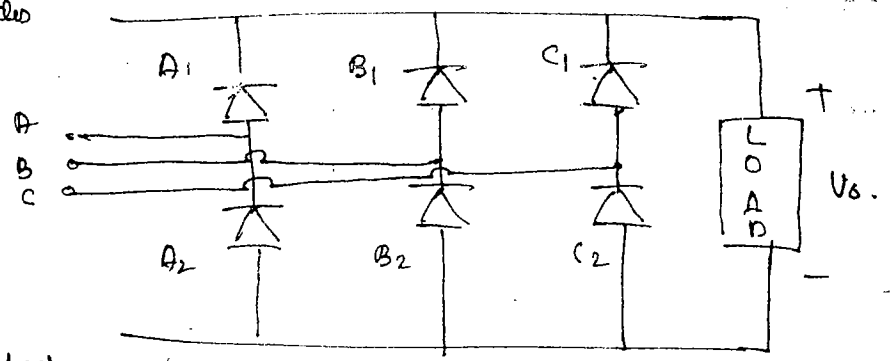
- In full wave rectifier 2 diodes are conducted at a time from top group which is subjected to more positive voltage and another from bottom 2 which is subjected to more -ve voltage



At any time load is connected between 2 ϕ phase wires and hence it is subjected to line voltage.

o/p waveform consists of 6-pulses for every input cycle so it is known as 3- ϕ 6-pulse rectifier.

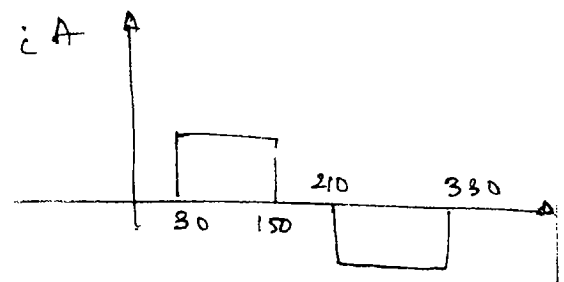- 1) o/p frequency = 6 fs.
- 2) duration of each pulse = 60°
- 3) conduction time of each phase = 240°



$$\begin{aligned}
 V_o &= \frac{1}{\pi/3} \int_{30^\circ}^{90^\circ} V_{m} \sin(\omega t + 30^\circ) d\omega t \\
 &= \frac{3V_{m}}{\pi} \left[-\cos(\omega t + 30^\circ) \right]_{30^\circ}^{90^\circ} \\
 &= \frac{3V_{m}}{\pi} \left[-\cos(90 + 30) - (-\cos(30 + 30)) \right] = \frac{3V_{m}}{\pi} [\cos 60 + \cos 60] \\
 &= \frac{3V_{m}}{\pi} \cdot 2 \cdot \cos 60^\circ = \frac{3V_{m}}{\pi} \times 2 \times \frac{1}{2} \\
 &= \frac{3\sqrt{3}}{\pi} V_{mp} = \frac{3\sqrt{3}}{\pi} \times \sqrt{2} V_{ph} \Rightarrow V_o = \frac{3\sqrt{6}}{\pi} V_{ph}
 \end{aligned}$$

→ The average value of o/p voltage in terms of the half wave rectifier


→ Peak instantaneous o/p voltage is equal V_{m1} .

→ Peak Inverse Voltage (PIV) is equal to V_{m1} .

Note:

$$I_{avg} = i \frac{\pi}{\gamma}$$
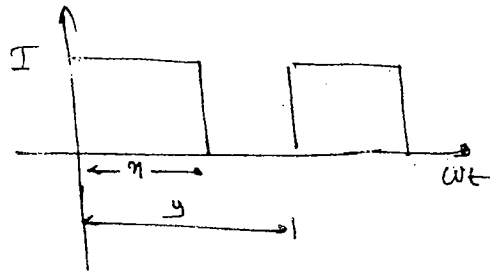
$$I_{rms} = i \sqrt{\frac{\pi}{\gamma}}$$



→ In a half wave rectifier - assume that output current is constant (I) than average value of diode current (I_{DA})

$$I_{DA} = I_{SA} = I \left(\frac{120}{360} \right) = I \quad \boxed{I_{DA} = \frac{I}{3}}$$

• RMS value of diode current $I_{DR} = I_{SR} = I \sqrt{\frac{120}{360}}$

$$\boxed{I_{DR} = \frac{I}{\sqrt{3}}}$$

→ In a full wave rectifier, assuming that o/p current is constant then average value of diode current $I_{DA} = I \left(\frac{120}{360} \right) = \frac{I}{3}$.

→ RMS value of diode current = $\frac{I}{\sqrt{3}}$.

→ Supply

$$I_{avg} = 0$$

$$I_{T.M} = I_{S.T} = I \sqrt{\frac{240}{360}} = I \sqrt{\frac{2}{3}}$$

3 ϕ - Half wave thyristor Rectifier

$$V_o = \frac{1}{2\pi/3} \int_{30+\alpha}^{150+\alpha} U_{mp} \sin(\omega t) d\omega t$$

$$= \frac{3U_{mp}}{2\pi} \left[-\cos \omega t \right]_{30+\alpha}^{150+\alpha}$$

$$= \frac{3U_{mp}}{2\pi} \left[\cos(30+\alpha) - \cos(180 - (30+\alpha)) \right]$$

$$= \frac{3U_{mp}}{2\pi} \left[\cos(30+\alpha) - \cos(150-\alpha) \right]$$

$$= \frac{3U_{mp}}{2\pi} \cdot 2 \cos 60 \cdot \cos \alpha = \frac{3U_{mp}}{\pi} \cdot \frac{\sqrt{3}}{2} \cdot \cos \alpha$$

$$= \frac{3\sqrt{3}}{2\pi} \cdot U_{mp} \cos \alpha$$

$$V_o = \frac{3\sqrt{3}}{2\pi} U_{ph} \cos \alpha$$

3 ϕ - Full wave thyristor circuit

$$V_o = \frac{1}{\pi/3} \int_{30+\alpha}^{90+\alpha} U_{ml} \sin(\omega t + 30) d\omega t$$

$$= \frac{3U_{ml}}{\pi} \left[-\cos(\omega t + 30) \right]_{30+\alpha}^{90+\alpha}$$

$$= \frac{3U_{ml}}{\pi} \left[\cos(60+\alpha) - \cos(120+\alpha) \right]$$

$$= \frac{3U_{ml}}{\pi} \left[\cos 60 \cdot \cos \alpha - 3n/60 \sin \alpha - \cos 120 \cdot \cos \alpha + \sin 120 \sin \alpha \right]$$

$$= \frac{3U_{\text{rms}}}{\pi} 2 \cos 60^\circ \cos \alpha$$

$$= \frac{3U_{\text{rms}}}{\pi} \cos \alpha = \frac{3\sqrt{3} U_{\text{rms}}}{\pi} \cos \alpha$$

$$V_o = \frac{3\sqrt{3}}{\pi} U_{\text{rms}} \cos \alpha$$

→ In a 3φ half wave rectifier feeding R-load, $\alpha < 30^\circ$ conduction

is continuous conduction $V_o = \frac{3\sqrt{3}}{2\pi} U_{\text{rms}} \cos \alpha$ for $\alpha > 30^\circ$ conduction

becomes discontinuous

$$V_o = \frac{1}{2\pi/\pi} \int_{30+\alpha}^{180} U_{\text{rms}} \sin \omega t \, d(\omega t)$$

$$= \frac{3U_{\text{rms}}}{2\pi} \left[-\cos \omega t \right]_{30+\alpha}^{180}$$

$$= \frac{3U_{\text{rms}}}{2\pi} \left[\cos(30+\alpha) + \cos 180 \right]$$

$$V_o = \frac{3U_{\text{rms}}}{2\pi} \left[1 + \cos(30+\alpha) \right]$$

Chapte - 2

14/03/11

01. → a-load $P = \frac{V_{\text{or}}^2}{R}$

$$V_{\text{or}} = \frac{V_{\text{rms}}}{\sqrt{2}} \left[\pi - \alpha + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

$$= \frac{220\sqrt{2}}{2\sqrt{2}} \left[\pi - 60 \left(\frac{\pi}{180} \right) + \frac{1}{2} \sin(2 \times 60) \right]^{1/2}$$

No p.u. bly
with
radian

$$+ \frac{1}{2} \sin(2 \times 60)$$

$$= 139.72 \text{ V}$$

$$P = \frac{139.72^2}{100}$$

$$= 1947 \text{ W}$$

By default


$$\text{PF} = \frac{V_{\text{or}}}{V_s} = \frac{139.72}{220} = 0.634 \text{ lag}$$

02) A SI a) $V_T = V_m \sin \alpha - E$
 $= 230\sqrt{2} \sin 25 - 120$
 $= \underline{\underline{17.46V}}$

b) at $\omega t = \beta, t = 20$

$V_T = V_m \sin \beta - E$
 $= 230\sqrt{2} \sin 220 - 120$
 $= \underline{\underline{-329V}}$

c) $\frac{PIV}{V_m} = \frac{V_m + |E|}{V_m}$
 $= \frac{230\sqrt{2} + 120}{230\sqrt{2}}$
 $= \underline{\underline{1.4534}}$

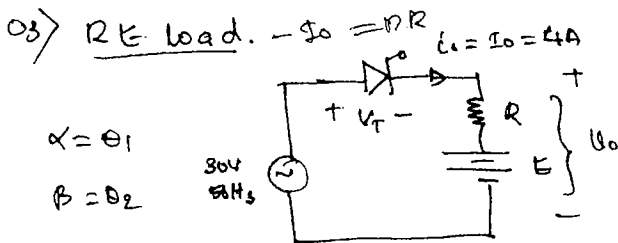

$\theta_1 = \sin^{-1} \left(\frac{E}{V_m} \right) = \sin^{-1} \left(\frac{6}{30\sqrt{2}} \right)$
 $= 8.13^\circ$

$\theta_2 = 180 - 8.13$
 $= 171.87^\circ$

$\int E \sin \omega t$ $\alpha = 0$
 $\omega t = \theta_2$
 $\frac{d}{dt} \sin \omega t = \omega \cos \omega t$

$I_o = \frac{1}{2\pi} \int_{\alpha}^{\beta} \frac{V_m \sin \omega t - E - V_T}{R} dt$

$V = \text{drop across conductors practical}$

$= \frac{1}{2\pi R} \left[V_m (-\cos \omega t) - (E + V_T) \omega t \right]_{\alpha}^{\beta}$

$= \frac{1}{2\pi R} \left[V_m (\cos \alpha - \cos \beta) - (E + V_T) (\beta - \alpha) \right]$

$= \frac{1}{2\pi R} \left[30\sqrt{2} (\cos 8.13 - \cos 171.87) - (6 + 120) \left(\frac{\pi}{180} (171.87 - 8.13) \right) \right]$

$R = \underline{\underline{2.54}} \Rightarrow \text{circuit shown OMS!}$

4) RE load

$\alpha = 30^\circ$

$\theta_1 = \text{calculate}$

$\beta = 180 - \theta_1$

always $\beta = \theta_2$
 $= 180 - \alpha$
 $\theta_2 = 180 - \theta_1$

$\theta_1 = \sin^{-1} \left(\frac{E}{V_m} \right)$

$= \sin^{-1} \left(\frac{110}{230\sqrt{2}} \right) = \underline{\underline{19.76^\circ}}$

$\theta_2 = 180 - 19.76 = \underline{\underline{160.24^\circ}}$

$I_o = \frac{1}{2\pi R} \left[V_m (\cos \alpha - \cos \beta) - E (\beta - \alpha) \right]$

$= \frac{1}{2\pi \times 10} \left[230\sqrt{2} (\cos 30 - \cos 160.24) - 110 (160.24 - 30) \frac{\pi}{180} \right]$


$I_o = \underline{\underline{5.37A}}$

5) An a sing' each secondary

$\frac{N_p}{N_{S1}} = 1.25 = \frac{V_p}{V_{S1}}$

$V_S = V_p = 230V$

$R = 2\Omega$

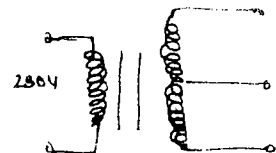

$$a) \frac{V_m}{\pi} V_o = \frac{V_m}{\pi} (1 + \cos \alpha)$$

$$V_o = n V_{omax}$$

$$\alpha = 0$$

$$V_o = V_{omax} = \frac{V_m}{\pi} (1 + \cos 0)$$

$$= \frac{2V_m}{\pi}$$


$$= \frac{2 \times 260.2}{\pi}$$

$$= \underline{\underline{165.63V}}$$

$$I_{omax} = \frac{V_{omax}}{R} = \frac{165.63}{2}$$

$$= \underline{\underline{82.83A}}$$

$$\alpha = 0^\circ$$

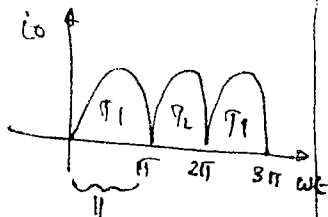

Conduction angle

$$(\gamma) = \underline{\underline{180^\circ}}$$


Physically conduction here

$$b) PIV = 2V_m = 2 \times 260.2 = 2 \times 260.2$$

$$= 520.4V$$

$$= \underline{\underline{520.4V}}$$

Turn Ratio is different

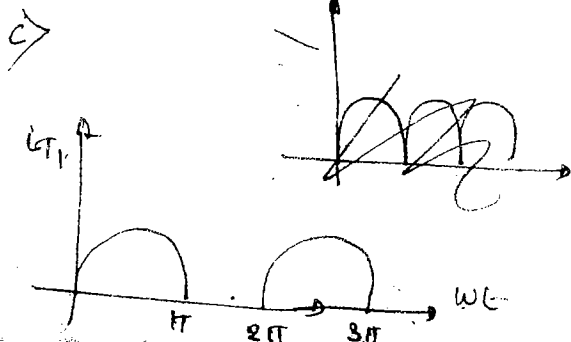

$$I_{T1} = \frac{82.83}{2} = \underline{\underline{41.41A}}$$

$$d) V_o = 100V$$

$$V_o = \frac{V_m}{\pi} [1 + \cos \alpha]$$

$$100 = \frac{260.2}{\pi} [1 + \cos \alpha]$$

$$\alpha = \underline{\underline{78^\circ}}$$

e) RLE load

$$V_o = \frac{V_m}{\pi} (1 + \cos \alpha)$$

$$V_o = \frac{V_m}{\pi} [1 + \cos \alpha]$$

$$= \frac{230\sqrt{2}}{\pi} [1 + \cos 50^\circ]$$

$$= \underline{\underline{180V}}$$


$$V_o = E + I_o R$$


$$I_o = \frac{V_o - E}{R} = \frac{180 - 80}{5} = \underline{\underline{18A}}$$

→ New value of average output current

current

$$\underline{\underline{I_{avg}}}$$

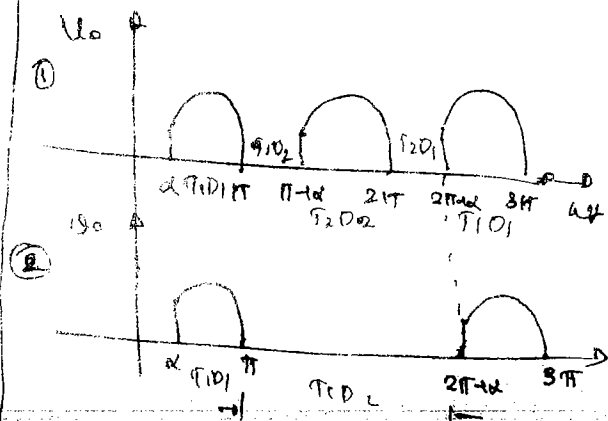

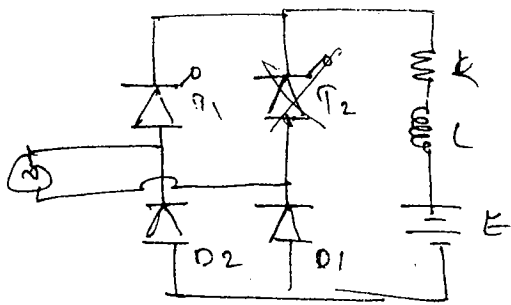

IES description shows wave form + E value of α

- T_2 got damaged, the available path for the currents are, find whichever path is available

available path are T_1, D_1 and T_1, D_2 supply opposite

the current will pass through T_1, D_2 which is equal to free wheeling path inductor is able to give energy for π to $2\pi + \alpha$ (at α supply)

hence the o/p voltage from π to $2\pi + \alpha$ V_o is $\frac{E}{2}$

→ This wave form looks like half wave rectifier.

- do the duration (π) free allow
- average value

→ $V_o = \frac{V_m}{2\pi} [1 + \cos \alpha]$ (170%)

$= \frac{280\sqrt{2}}{2\pi} [1 + \cos 30^\circ] = \underline{\underline{85.4}}$

$I_o = \frac{V_o - E}{R} = \frac{85 - 80}{5} = \underline{\underline{1A}}$

→ It is a continuous conduction mode circuit as the load is a series of constant


$V_o = \frac{2V_m \cos \alpha}{\pi}$ (continuous conduction for $\alpha < 90^\circ$)

$= \frac{2 \times 280\sqrt{2}}{\pi} \cos 30^\circ$

$= E + I_o R$

→ $I_o = \frac{179.8 - 100}{2.5} = \underline{\underline{31.72A}}$

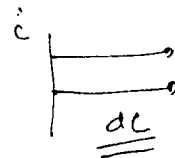P.f. input pf = $\frac{E I_o + I_o^2 \cdot R}{V_s I_{sr}}$



$= \frac{100 \times 31.72 + (31.72)^2 \cdot (2.5)}{280 \times 31.72}$

$= \underline{\underline{0.78 \text{ Lag}}}$ (By default it is lag)

8) a) $\beta = 200^\circ$

→ current extinguishes means the conduction is not continuous. (for $\beta > 90^\circ$)

RLC load, here the L is not capable to support the continuous flow of current

Remember:

$$I_o = \frac{1}{\pi} \int_{\alpha}^{\beta} \frac{V_m \sin \omega t - E}{R} d\omega t$$

$$= \frac{1}{\pi R} [V_m (-\cos \omega t) - E(\omega t)]_{\alpha}^{\beta}$$

$$= \frac{1}{\pi R} [V_m (\cos \alpha) - E(\beta - \alpha)]$$

$$I_0 = \frac{1}{2\pi} \left[230\sqrt{2} (\sin 30 - \cos 20) - 100 (200 - 30) \pi / 180 \right]$$

$$V_0 = E + I_0 R$$

$$= 100 + (46.25 \times 2)$$

$$= \underline{\underline{192.5V}}$$

17.11


$$\beta = 170^\circ, \quad I_0 = 56.82 \text{ A} / V_0 = 293.14$$

$$\frac{N_p}{N_s} = \frac{1}{2}$$

$$I_0 = 5A$$

$$\alpha = 35^\circ$$

$$V_p = 220V$$

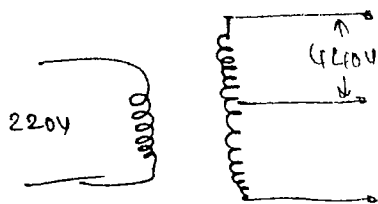

1:2

$$V_s = \underline{\underline{440V}} \quad (2 \times \text{turn Ratio})$$

$$V_{s1m} = 440\sqrt{2} = \underline{\underline{622V}}$$

— without load current correction
conduction

$$V_0 = \frac{2V_m}{\pi} \cos \alpha$$

$$= \frac{2 \times 622}{\pi} \cos 35^\circ$$

$$= \underline{\underline{324.5V}}$$

$$V_0 = \frac{3\sqrt{6}}{2\pi} V_{ph}$$

$$= \frac{3\sqrt{6}}{2\pi} \times \frac{400}{\sqrt{3}}$$

$$= \underline{\underline{270V}}$$

$$I_0 = \frac{V_0}{R} = \frac{270}{5} = \underline{\underline{54A}}$$

$$12) \quad V_0 = \frac{3\sqrt{6}}{2\pi} V_{ph} \cos \alpha$$

$$\alpha = 0$$

$$V_0 = \frac{3\sqrt{6}}{2\pi} \times \frac{400}{\sqrt{3}} \times \cos 0$$

$$= \underline{\underline{270V}}$$

$$P = V_0 I_0$$

$$= 270 \times 30$$

$$= \underline{\underline{8100W}}$$

$$b) \quad \alpha = 80^\circ$$

$$V_0 = \frac{3\sqrt{6}}{2\pi} V_{ph} \cos \alpha$$

$$= \frac{3\sqrt{6}}{2\pi} \cdot \frac{400}{\sqrt{3}} \cdot \cos 80^\circ$$

$$\cos \alpha = 46.911$$

$$P = V_0 I_0$$

$$= 46.911 \times 30 = \underline{\underline{1407W}}$$

13) a) $E = 110V, R = 0.2\Omega, I_0 = 10A$

$V_E = 220V$

$V_0 = E + I_0 R$ } ϕ E load
 $= 110 + (10 \times 0.2)$
 $= 112V$

$V_0 = \frac{3\sqrt{6}}{\pi} \cdot V_{ph} \cdot \cos \alpha$

$112 = \frac{3\sqrt{6}}{\pi} \times \frac{220}{\sqrt{3}} \times \cos \alpha$

$\Rightarrow \alpha = 67.8^\circ$ - Power on ac side

P.f = $\frac{E I_0 + I_0^2 R}{3 \sqrt{6} I_L}$ (ac load)
 Power on ac side 3φ

$= \frac{110 \times 10 + (10)^2 \cdot (0.2)}{\sqrt{3} \times 220 \times (I_L) \frac{10\sqrt{2}}{3}}$

$I_L = I_{sc} = I_0 \sqrt{\frac{2}{3}}$ ~~14/03/22~~

$\phi_f = 0.36 \text{ Lag}$

b) $\alpha = 150^\circ$

$I_0 = 10A, E = -110V$
 (condition)

For power hf $\alpha > 90^\circ, E \cdot$

$V_0 = E + I_0 R$
 $= -110 + 10 \times 0.2$
 $= -108V$

$E_0 = \frac{3\sqrt{6}}{\pi} V_{ph} \cos \alpha$

$-108 = \frac{3\sqrt{6}}{\pi} \times V_{ph} \times \cos 150$

$V_{ph} = 53.34$

$V_L = \sqrt{3} V_{ph}$
 $= \sqrt{3} \times 53.34$
 $= 92.36V$

14) 3φ F.W. TR, $I_0 = 50A, V_0 = 230V$

$V_L = 415V, U_T = 1.1V$

$V_0 = 230 + 2 \times 1.1$
 $= 232.2V$

$V_0 = \frac{3\sqrt{6}}{\pi} \cdot V_{ph} \cdot \cos \alpha$

$232.2 = \frac{3\sqrt{6}}{\pi} \cdot \frac{415}{\sqrt{3}} \cdot \cos \alpha$

a) $\alpha = 65^\circ$

b) rms and SCR.

$I_{Tn} = I_0 \sqrt{\frac{1}{3}}$
 $= 50 \sqrt{\frac{1}{3}} = 28.87A$

$I_{sr} = I_L = I_0 \sqrt{\frac{2}{3}} = 50 \sqrt{\frac{2}{3}}$
 $= 40.82A$

15) half controlled = semi-converter

but full wave rectifier

ϕ S.C, $R = 10 \Omega$, $E = 100V$

$\alpha = 60^\circ$, $V_s = 200V$,

• RLE load $\beta = 180 - \theta_2$
 $\theta_1 = 180 - \theta_2$

• $\theta_1 = \sin^{-1} \left(\frac{E}{V_m} \right) = \sin^{-1} \left(\frac{100}{200\sqrt{2}} \right)$
 $= 20.7^\circ$

$= 180 - 20.7$

$\theta_2 = 159.3^\circ$

$$I_o = \frac{1}{\pi} \int_{\alpha}^{\beta} V_m \sin \omega t \, d\omega t$$

$$= \frac{1}{\pi R} [V_m (-\cos \omega t) - E (\omega t)]_{\alpha}^{\beta}$$

$$= \frac{1}{\pi R} [V_m (\cos \alpha - \cos \beta) - E (\beta - \alpha)]$$

$$= \frac{1}{\pi \times 10} [200\sqrt{2} (\cos 20.7 - \cos 159.3) - 100 (\pi \times 1.5 - 0)] \frac{\pi}{180}$$

$= 7.4A$

16) RLE load


$$V_o = \frac{V_m}{\pi} [1 + \cos \alpha]$$

$$= \frac{200\sqrt{2}}{\pi} [1 + \cos 60]$$


$$I_o = \frac{185 - 100}{10} \left(\frac{V_o - E}{R} \right)$$

$$= 3.5A$$

18)

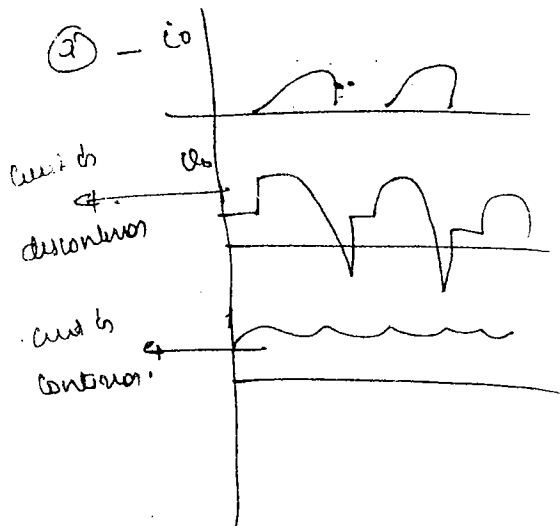


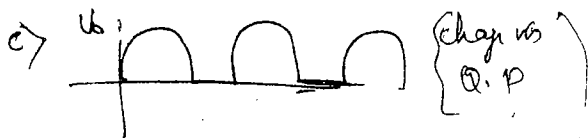• Continuous conduction either with RL load or RLE load



• R load, $\alpha = 0$ (Chap 18)


• $\frac{1}{2}$ wave diode with R

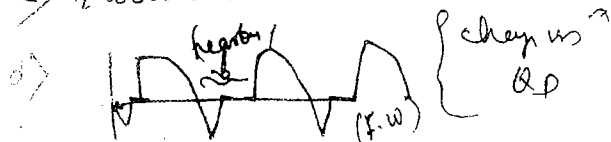

R-L load with discontinuous conduction

giving Hfc & rms

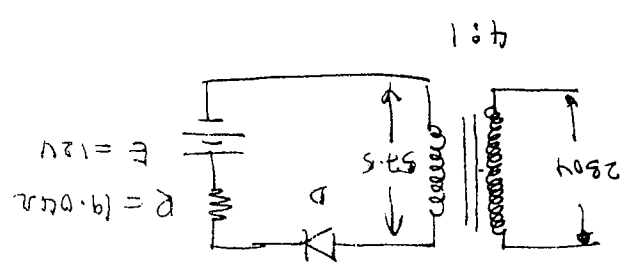→ duty cycle is low, @ number of
 → Angstroms litigand by a constant of
 signal equivalent to diode count



* 25 > uncontrolled - loads resistor
 Load - RE load

25 > average power = $\cos \alpha$
 power factor = $0.92 \cos \alpha$
 single phase converter

$$I_0 = 11.9 \text{ A}$$

$$I_0 = \frac{1}{2\pi R} \left[280 \int_0^{\pi} (\cos \alpha - \cos(\alpha + \theta)) d(\alpha + \theta) - 280 \int_{\pi}^{2\pi} (\cos(\alpha + \theta) - \cos \alpha) d(\alpha + \theta) \right]$$

$$I_0 = \frac{1}{2\pi R} \left[\cos \alpha \int_0^{\pi} (1 - \cos(\alpha + \theta)) d(\alpha + \theta) - \cos \alpha \int_{\pi}^{2\pi} (\cos(\alpha + \theta) - 1) d(\alpha + \theta) \right]$$

$$I_0 = \frac{1}{2\pi R} \left[\cos \alpha \left(\int_0^{\pi} 1 d(\alpha + \theta) - \int_0^{\pi} \cos(\alpha + \theta) d(\alpha + \theta) \right) - \cos \alpha \left(\int_{\pi}^{2\pi} \cos(\alpha + \theta) d(\alpha + \theta) - \int_{\pi}^{2\pi} 1 d(\alpha + \theta) \right) \right]$$

$$I_0 = \frac{1}{2\pi R} \left[\cos \alpha \left(\pi - \sin(\alpha + \theta) \Big|_0^{\pi} \right) - \cos \alpha \left(\sin(\alpha + \theta) \Big|_{\pi}^{2\pi} - (\pi - \pi) \right) \right]$$

$$I_0 = \frac{1}{2\pi R} \left[\cos \alpha \left(\pi - \sin(\alpha + \pi) + \sin(\alpha + 0) \right) - \cos \alpha \left(\sin(2\pi) - \sin(\pi) - \pi + \pi \right) \right]$$

$$I_0 = \frac{1}{2\pi R} \left[\cos \alpha \left(\pi - (-1) + \sin \alpha \right) - \cos \alpha \left(0 - 0 - \pi + \pi \right) \right]$$

$$I_0 = \frac{1}{2\pi R} \left[\cos \alpha \left(\pi + 1 + \sin \alpha \right) - \cos \alpha \left(0 \right) \right]$$

$$I_0 = \frac{1}{2\pi R} \left[\cos \alpha \left(\pi + 1 + \sin \alpha \right) \right]$$


$$I_0 = \frac{1}{2\pi \cdot 19.04} \left[\cos \alpha \left(\pi + 1 + \sin \alpha \right) \right]$$

$$I_0 = \frac{1}{38.08\pi} \left[\cos \alpha \left(\pi + 1 + \sin \alpha \right) \right]$$

$$I_0 = \frac{1}{119.2} \left[\cos \alpha \left(\pi + 1 + \sin \alpha \right) \right]$$

$$I_0 = 11.9 \text{ A}$$

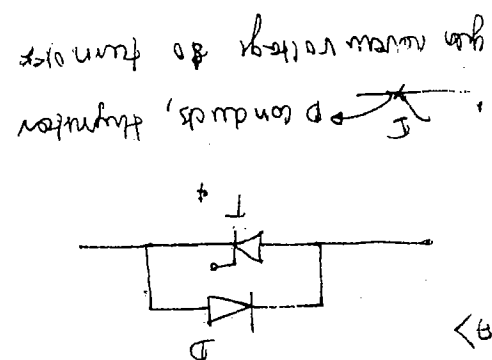→ duty cycle is low, @ number of
 → Angstroms litigand by a constant of
 signal equivalent to diode count



29 > $I_0 = 1.05 \text{ A}$
 $R = 19.04 \Omega$
 $I_0 = \frac{1}{2\pi R} \left[280 \int_0^{\pi} (\cos \alpha - \cos(\alpha + \theta)) d(\alpha + \theta) - 280 \int_{\pi}^{2\pi} (\cos(\alpha + \theta) - \cos \alpha) d(\alpha + \theta) \right]$

$$I_0 = \frac{1}{2\pi R} \left[\cos \alpha \int_0^{\pi} (1 - \cos(\alpha + \theta)) d(\alpha + \theta) - \cos \alpha \int_{\pi}^{2\pi} (\cos(\alpha + \theta) - 1) d(\alpha + \theta) \right]$$

$$I_0 = \frac{1}{2\pi R} \left[\cos \alpha \left(\int_0^{\pi} 1 d(\alpha + \theta) - \int_0^{\pi} \cos(\alpha + \theta) d(\alpha + \theta) \right) - \cos \alpha \left(\int_{\pi}^{2\pi} \cos(\alpha + \theta) d(\alpha + \theta) - \int_{\pi}^{2\pi} 1 d(\alpha + \theta) \right) \right]$$

$$I_0 = \frac{1}{2\pi R} \left[\cos \alpha \left(\pi - \sin(\alpha + \theta) \Big|_0^{\pi} \right) - \cos \alpha \left(\sin(\alpha + \theta) \Big|_{\pi}^{2\pi} - (\pi - \pi) \right) \right]$$

$$I_0 = \frac{1}{2\pi R} \left[\cos \alpha \left(\pi - \sin(\alpha + \pi) + \sin(\alpha + 0) \right) - \cos \alpha \left(\sin(2\pi) - \sin(\pi) - \pi + \pi \right) \right]$$

$$I_0 = \frac{1}{2\pi R} \left[\cos \alpha \left(\pi - (-1) + \sin \alpha \right) - \cos \alpha \left(0 - 0 - \pi + \pi \right) \right]$$

$$I_0 = \frac{1}{2\pi R} \left[\cos \alpha \left(\pi + 1 + \sin \alpha \right) - \cos \alpha \left(0 \right) \right]$$

$$I_0 = \frac{1}{2\pi R} \left[\cos \alpha \left(\pi + 1 + \sin \alpha \right) \right]$$


$$I_0 = \frac{1}{2\pi \cdot 19.04} \left[\cos \alpha \left(\pi + 1 + \sin \alpha \right) \right]$$

$$I_0 = \frac{1}{38.08\pi} \left[\cos \alpha \left(\pi + 1 + \sin \alpha \right) \right]$$


$$I_0 = \frac{1}{119.2} \left[\cos \alpha \left(\pi + 1 + \sin \alpha \right) \right]$$

$$I_0 = 1.05 \text{ A}$$

$280 = V_m \sin \alpha$

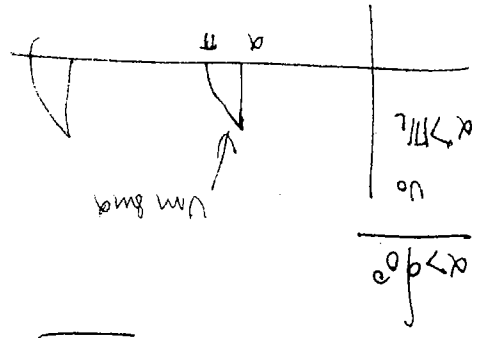


→ given $P_{IV} = 230$ Not 230Ω

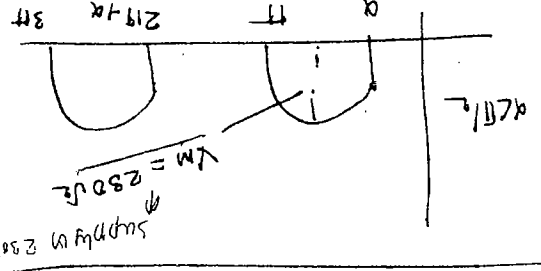


$P_{IV} = 1000 \Omega$

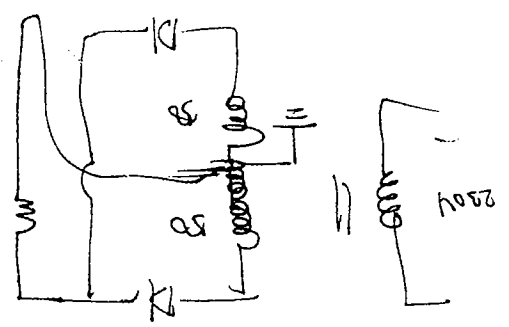50-rms value
 $(50 + 50) = 100$
 Ratio cu
 $230V / 50 - 0 - 50 \Omega$



$V_m = 100 \sqrt{2}$

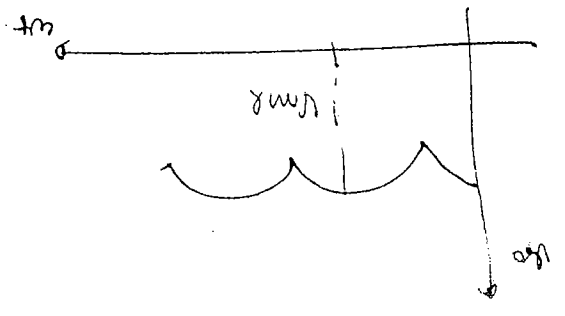

current is half wave
 rectifier feeding
 RL load

conductor starts at θ_1 (current DC)
 $\theta_1 = \sin^{-1} \left(\frac{V_m}{E} \right) = \sin^{-1} \left(\frac{280}{200} \right)$
 $= 39.94^\circ$

$\alpha > \theta_1$ RL load

When $\alpha = 125^\circ$

$-340 = 356 \cdot \frac{\pi}{180} \cdot \cos \alpha$

$V_0 = 856 \cdot \cos \alpha$

$= -340V$

$I_0 = E + I_0 R = -350 + 20 \times 0.5$

current $I = -850V$

$R = 0.5 \Omega$

$I_0 = 20A$

$V_0 = 440V$

$E = 850V$

inverter question

Power factor = 0.9 (load)
 Input displacement factor = load

FORMULA

$\alpha = 45^\circ$ (cos 1.95)
 $\alpha = 8m$ (1/5)
 $V_m = 230 \sqrt{2} \sin \alpha$
 $f_{av} = 1000$
 $f_{av} = 820$
 $f_{EM} = 800$

28) Displacement power factor - check the sin waves it is given in values.
 for $\phi = 0.5$ here they meant it as power factor.

29) For $2 \frac{150}{\sqrt{3}}$ d

30) d | Commonsense

31) to work as inverter = $90^\circ - 180^\circ$


d) Back emf means motor load. may back emf battery solar cell any they be a device low commuted operation

c) 'c' option is not there d is the ans, but here it is the ans, ω is from the load.

note: here converter as inverter can be used in Regenerative braking energy transfer to load to source

32)
$$V_o = \frac{3\sqrt{6}}{\pi} V_{ph} = \frac{3\sqrt{6}}{\pi} \cdot \frac{440}{\sqrt{3}} = 594V$$

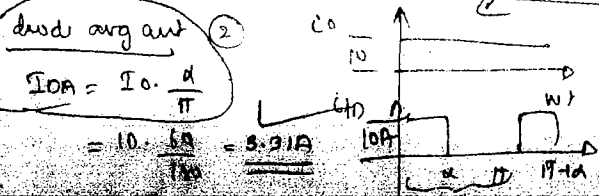33) Half controlled / semi converter Not possible to get negative voltage it is possible only in FWR



34) Semi converter $V_s = 120V, \alpha_1 = 0^\circ$
 $\alpha_2 = 180^\circ$

$$V_o = \frac{V_m}{\pi} (1 + \cos \alpha)$$

For $\alpha = 0$ For $\alpha = 180$

$$V_o = \frac{240m}{\pi}$$

$$V_o = 0$$

$$\left(\frac{2 \times 100\Omega}{\pi}, 0 \right)$$

(c)

35) BLOWER (EXHAUST FANS) - required to operate only in one direction. The average voltage required is only +ve. half controlled at +ve side enough. 'c' is but ans.

36 - H.W

37) Continuous conduction. Full wave converter

$$V_o = \frac{2V_m}{\pi} \cos \alpha = 2 \cdot \frac{230\sqrt{2}}{\pi} \cdot \cos 60^\circ = 103.5V$$


$$I_o = \frac{V_o - E}{R} = \frac{103.5 - 50}{10} = 5.35A$$

38)

No negative portion

same as ~~the~~ semi-con

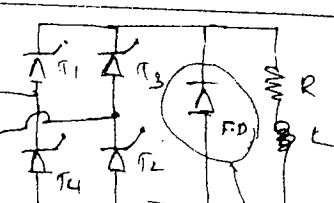
$$V_o = \frac{V_m}{\pi} [1 + \cos \alpha]$$



$$V_o = \frac{230\sqrt{2}}{\pi} [1 + \cos 60^\circ] = 155.3V$$

$$I_o = \frac{V_o}{R-L} = \frac{155.3}{15.4} = 10A$$

Note: Avg they do = 2

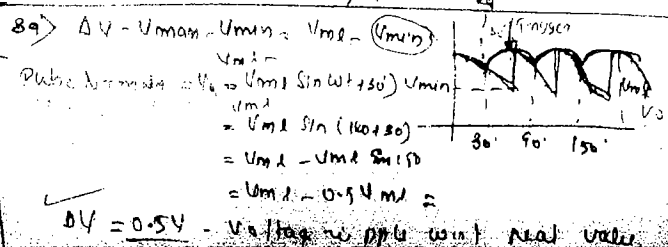

EFFECT OF SOURCE INDUCTANCE ON THE PERFORMANCE OF RECTIFIER.

▷ 1-ϕ Rectifier

• $\mu =$ overlapping angle

• $V_1 = V_m \sin \omega t$

• $V_2 = -V_m \sin \omega t$

• Inductance generally comes from winding

both of alternator source. Assume that V_s

Inductance is L_s .

• Ideally if $\mu = 0$, then i_c will not be

0 but due to overlap for period

α (π to $\pi + \mu$) both of them occur at a time

• V_1 and V_2 - two supplies.

• Consider supply +ve half: T_1, T_2 conductors

• \rightarrow KVL $\Rightarrow L_s \frac{di_1}{dt} + R L_o + L \frac{di_o}{dt} = V_m \sin \omega t$ (1)

Sup - to +

$= V_m \sin \omega t$

• then but T_3 and T_4 conduct at




(π to $\pi + \mu$)

\Rightarrow Sup + to - T_3, T_4

$L_s \frac{di_2}{dt} + R L_o + L \frac{di_o}{dt} = -V_m \sin \omega t$ (2)

• From (1) and (2) Equivalant circuit is drawing

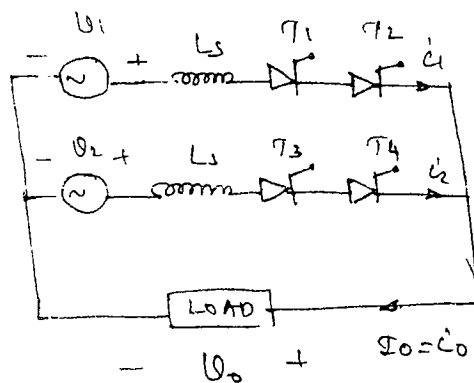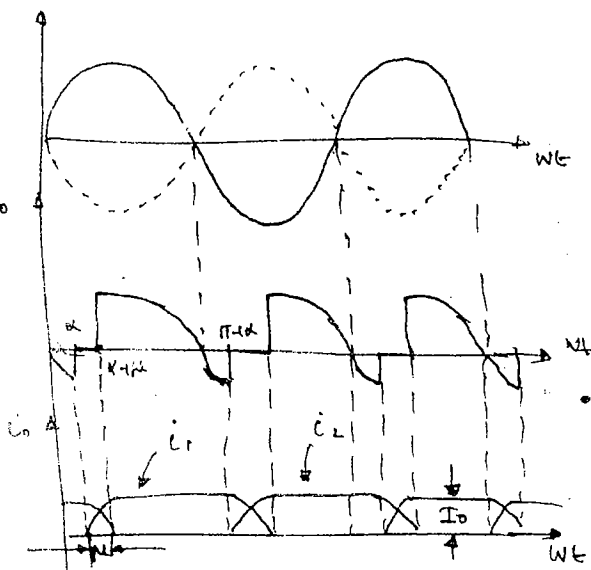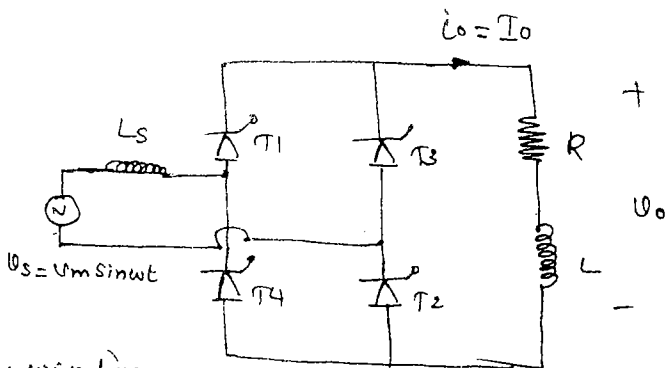\Rightarrow π to $\pi + \mu$: $V_o = 0$? $= \frac{2V_m}{\pi} \cos \mu$ - { ? }



$$1b) V_o = \frac{2V_m}{\pi} \cos \alpha - \frac{\omega L_s I_o}{\pi}$$

$$140 = \frac{2 \times 330}{\pi} \cos 45 - \frac{314 L_s \cdot 5}{\pi}$$

$$L_s = 19.11 \text{ mH}$$

$$\cos(\alpha + \mu) = \cos \alpha - \frac{\omega L_s I_o}{V_m}$$

$$\cos(45 + \mu) = \cos 45 - \frac{314 \times 19.11 \cdot 5}{330}$$

$$\mu = 6.26^\circ$$

$$\frac{V_o}{I_o} = \frac{140}{5} = 28 \Omega$$

$$1a) R = \frac{V_o}{I_o} = \frac{280}{2.8} = 100 \Omega$$

$$V_o = \frac{3\sqrt{6}}{\pi} V_{ph} \cos \alpha - \frac{3\omega L_s I_o}{\pi}$$

$$250V = \frac{3\sqrt{6}}{\pi} \cdot \frac{4V_o}{\sqrt{3}} \cdot \cos 60 - \frac{3 \times 314 \cdot L_s}{\pi}$$

$$L_s = 2.68 \text{ mH}$$

$$1c) \cos(\alpha + \mu) = \cos \alpha - \frac{2\omega L_s I_o}{V_m}$$

$$\mu = 4.8^\circ$$

IES 2007

Q) A 230V, 50Hz, 1 pulse, SCF controlled converter is triggered, at a firing angle of 40° and the load current extinguished at an angle of 120° . Find the current turn OFF time, average o/p voltage, average load current. for $R = 5 \Omega$ and $L = 2 \text{ mH}$

Sol:

• They were Rectifier R-L load.

• They can stop the conduction Rectifier



at 120° using forced commutation. Ecto. ^{stop} _{gate}

angle control.

• average V_o , $I_o \propto \frac{V_m}{2\pi} (\cos \alpha - \cos \beta)$


$$I_o = \frac{V_o}{R}$$

• Turn OFF time t_{off} will later

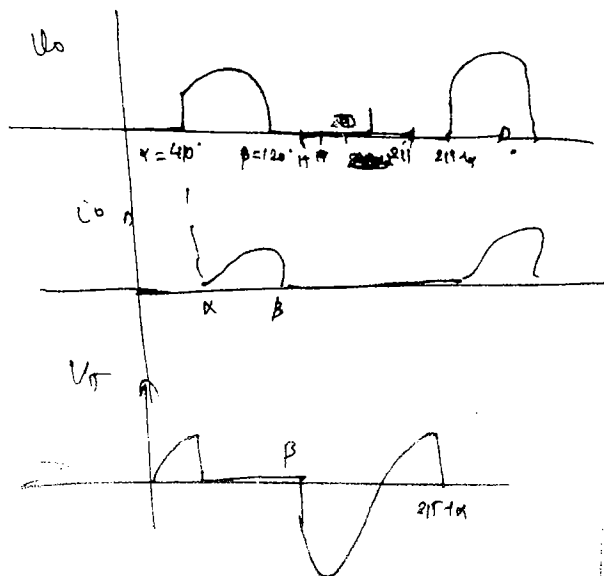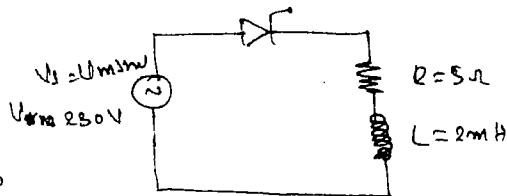

Q) 2005 A single phase Thyristor converter with a resistive load as shown

below

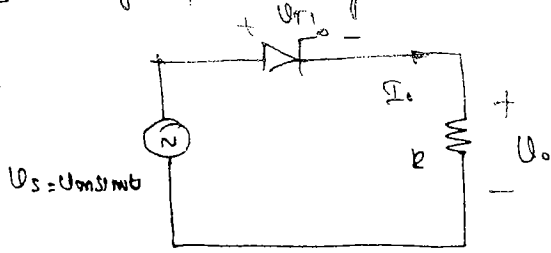

supply voltage \$V_s\$ is sinusoidal at a fixed frequency

i) Draw the wave forms for \$V_s\$, \$V_o\$ and \$V_{T1}\$ and the firing angle \$\alpha = 45^\circ\$. (neglect leakage inductance)

at a frequency

ii) If the supply voltage is 230V (rms) at 50 Hz, when \$\alpha = 45^\circ\$ and

\$R = 100 \Omega\$ calculate, a) Average o/p voltage and current

b) rms value of supply current

c) Ripple factor.

20 - 25 marks

derive the formula used.

Sol:

ii) \$V_s = 230V\$, \$\alpha = 45^\circ\$, \$R = 100 \Omega\$.

$$a) V_o = \frac{V_m}{\pi} [1 + \cos \alpha] = \frac{230\sqrt{2}}{\pi} [1 + \cos 45^\circ] = 88.39V$$

$$I_o = \frac{V_o}{R} = \frac{88.39}{100} = \underline{\underline{0.8839A}}$$

b) rms value of supply current. (\$I_o = I_s\$), \$V_{or} = \frac{V_m}{2\sqrt{\pi}} [\pi - \alpha + \frac{1}{2} \sin 2\alpha]^{1/2}\$

$$= \frac{230\sqrt{2}}{2\sqrt{\pi}} \left[\pi - 45^\circ + \frac{\pi}{180} + \frac{1}{2} \sin (2 \times 45^\circ) \right]^{1/2} = \underline{\underline{155V}}$$

Radian

$$I_{or} = \frac{V_{or}}{R} = \frac{155}{100} = \underline{\underline{1.55A}}$$

c) Ripple factor = $\frac{\text{A/c component}}{\text{dc component (average value)}}$

A/c component = Residual (rms value)

$$V_{ac} = \sqrt{V_{or}^2 - V_{dc}^2}$$

$$V_{dc} = V_o$$

The effect of source inductance is to make the simultaneous conduction of both outgoing and incoming SCs. During this period the output voltage is equal to zero and it is known as overlapping period.

→ The net effect is to reduce the average value of o/p voltage.

Derivation

→ During overlapping period, $\alpha \leq \omega t \leq \alpha + \pi$. $\Rightarrow i_1 + i_2 = i_o$ constant

differentiating both sides $\frac{di_1}{dt} + \frac{di_2}{dt} = 0$ — (1)

→ From equivalent circuit during $\alpha \leq \omega t \leq \alpha + \pi$ then

$$V_o = V_1 - L_s \frac{di_1}{dt} = V_2 - L_s \frac{di_2}{dt} = 0 \quad L_s \left[\frac{di_1}{dt} - \frac{di_2}{dt} \right] = V_1 - V_2$$

$$L_s \left[\frac{di_1}{dt} - \frac{di_2}{dt} \right] = V_m \sin \omega t - - V_m \sin \omega t = 2V_m \sin \omega t$$

$$\Rightarrow \frac{di_1}{dt} - \frac{di_2}{dt} = \frac{2V_m}{L_s} \cdot \sin \omega t \quad \text{--- (2)}$$

$$\text{(1) + (2)} \Rightarrow 2 \frac{di_1}{dt} = \frac{2V_m}{L_s} \cdot \sin \omega t \Rightarrow \underline{\underline{di_1 = \frac{V_m}{L_s} \cdot \sin \omega t dt}}$$

Integrating on both sides with limits from (0 to I_o) and time ($\frac{\alpha}{\omega}$ to $\frac{\alpha + \pi}{\omega}$).

$$\int_0^{I_o} di_1 = \int_{\frac{\alpha}{\omega}}^{\frac{\alpha + \pi}{\omega}} \frac{V_m}{L_s} \sin \omega t \cdot dt$$

divides by ω to get time

$$I_o = \frac{V_m}{L_s} \left[-\frac{\cos \omega t}{\omega} \right]_{\frac{\alpha}{\omega}}^{\frac{\alpha + \pi}{\omega}} = \frac{V_m}{\omega L_s} \left[\cos \alpha - \cos(\alpha + \pi) \right]$$

$$I_o = \frac{V_m}{\omega L_s} \left[\cos \alpha - \cos(\alpha + \pi) \right]$$

Next we : The average value of o/p voltage.

$$V_o = \frac{1}{\pi} \int_{\alpha+\pi}^{\pi+\alpha} V_m \sin \omega t \, d\omega t = \frac{V_m}{\pi} \left[-\cos \omega t \right]_{\alpha+\pi}^{\pi+\alpha}$$

$$= \frac{V_m}{\pi} \left[\cos(\alpha+\pi) - \cos(\pi+\alpha) \right] = \frac{V_m}{\pi} \left[\cos \alpha + \cos(\alpha+\pi) \right]$$

From $I_o = \frac{V_m}{\omega L_s} \left[\cos \alpha - \cos(\alpha+\pi) \right]$

to find of overlapping value

$$\Rightarrow \cos \alpha - \cos(\alpha+\pi) = \frac{\omega L_s}{V_m} \cdot I_o \Rightarrow \cos(\alpha+\pi) = \cos \alpha - \frac{\omega L_s}{V_m} I_o$$


Substituting in V_o .

$$V_o = \frac{V_m}{\pi} \left[\cos \alpha + \cos \alpha - \frac{\omega L_s}{V_m} I_o \right] = \frac{2V_m}{\pi} \cos \alpha - \frac{\omega L_s}{\pi} I_o$$

$$V_o = \frac{2V_m}{\pi} \cos \alpha - \frac{\omega L_s}{\pi} I_o$$


Equivalent circuit of V_o

{ Rectifier } \rightarrow

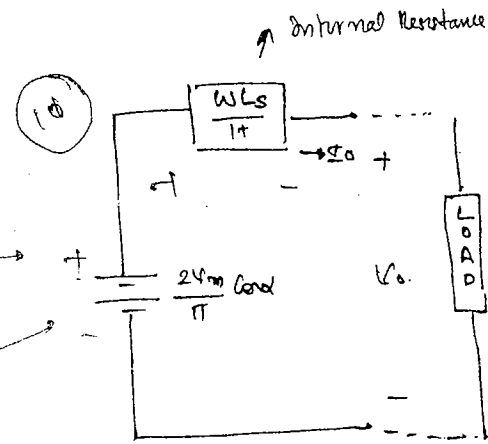

\Rightarrow 3 ϕ - Rectifier
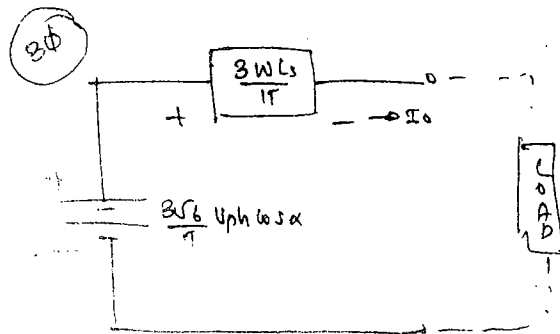
$$V_o = \frac{3\sqrt{3} V_{ph}}{\pi} \cos \alpha - \frac{3\omega L_s}{\pi} I_o$$



$$\frac{V_{dce}}{V_o} = \frac{\sqrt{V_{o1}^2 - V_o^2}}{V_o} = \frac{\sqrt{155^2 - 88.89^2}}{155} \times 100\% = 144\%$$

6-8:15 = PE
 4-5:30 = HISTOR
 6-8:30 = EMT
 8:05


16-05-11

CHOPPERS.


- It converts Fixed DC to variable DC.
- It is a static power electronic circuit which converts DC to variable DC in variation in the magnitude of the voltage.
- Choppers are of two types \rightarrow step down chopper ($V_o < V_s$) \rightarrow step up chopper ($V_o > V_s$).

Realisation of chopper by a mechanical.

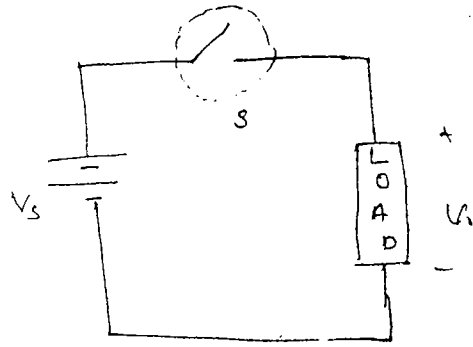
- Switch to closed and opened and closed, so the V_o avg varies at the o/p.
- By varying T_{ON} and T_{OFF} time, we can vary the average o/p voltage from 0 to V_s (step down chopper).



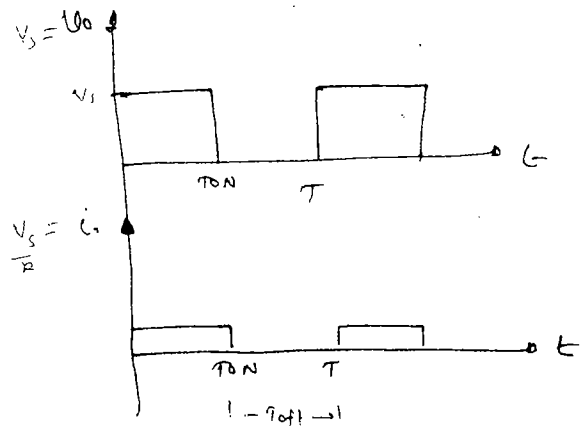
- If the time slot of T_{ON} and T_{OFF} should be $> 1 \mu s$ to get a better performance of the chopper.



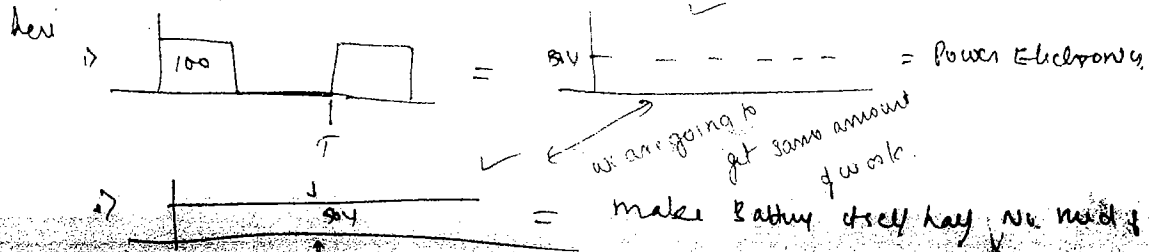- The switch normal, can't able to work at $> 1 \mu s$, here P S D CHOPPER comes in to stage.



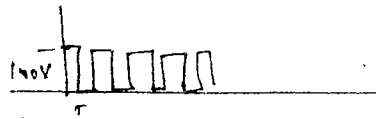3) making small pulse gives rather than large waveforms just similar to 5V constant



• chopper should have higher switching frequency. Time period should be high.

(512) \Rightarrow chopper principle can be realised by using a mechanical switch, output voltage can be controlled by varying on and off times of the switch.

\Rightarrow Due to limitations on the practical switches, mechanical switch should be replaced by power electronic switches that is chopper. If fast switches are available, then the performance of the circuit would be better.

STEP DOWN CHOPPER (BUCK CHOPPER)

Average voltage

$$V_o = \frac{1}{T} \int_0^{T_{ON}} V_s dt$$

$$= V_s \cdot \frac{T_{ON}}{T}$$

$T_{ON} = \alpha T$
 $T_{OFF} = (1-\alpha) T$

$V_o = \alpha V_s$

$\alpha = \text{Duty cycle} = \frac{T_{ON}}{T}$



other $V_o = f \cdot T_{ON} \cdot V_s$

when $f =$ chopping frequency.

or RMS Voltage

$$V_{OR} = \sqrt{\frac{1}{T} \int_0^{T_{ON}} V_s^2 dt}$$
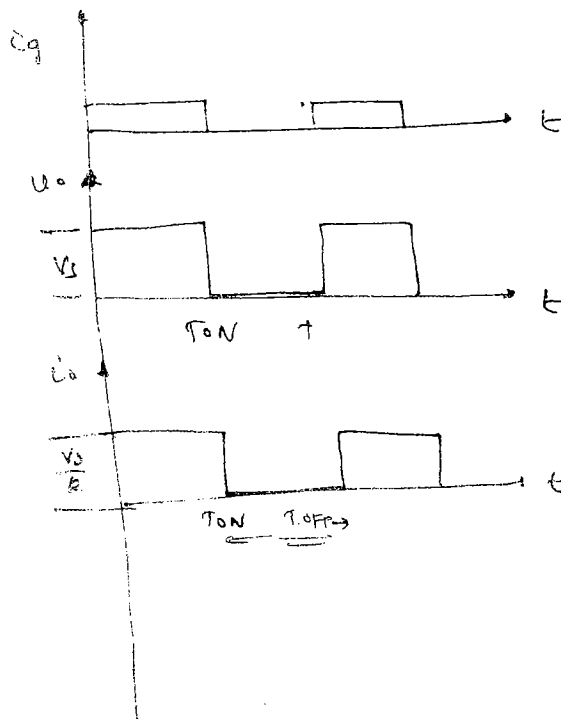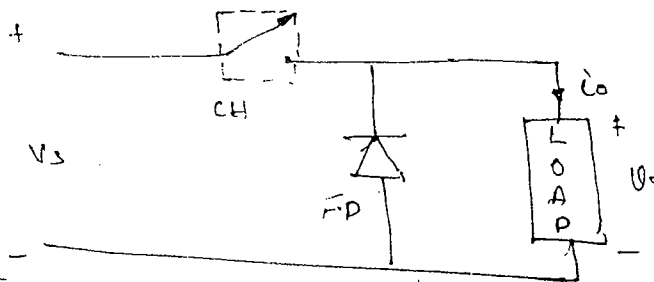
$$= \sqrt{\frac{1}{T} \cdot V_s^2 \cdot T_{ON}}$$



$$V_{or} = \sqrt{\alpha} V_s$$

→ Average voltage is dc component, rms value includes dc and ac, hence α is always $\alpha < 1$ when $\sqrt{\alpha} > 1$

• RMS value of output voltage will be more than average value of a/c voltage. It is equivalent to resultant of a/c component as well as d/c component.

$$\rightarrow I_o = \frac{V_o}{R}, \quad I_{or} = \frac{V_{or}}{R}$$

$$\begin{aligned} \text{Ripple factor} &= \frac{\text{A/c component}}{\text{DC component}} = \frac{V_{orms} - V_{avg}}{V_{avg}} = \frac{\sqrt{V_{or}^2} - V_o}{V_o} \\ &= \sqrt{\frac{1}{\alpha} - 1} = \frac{\sqrt{\alpha^2 V_s^2 - \alpha^2 V_s^2}}{\alpha V_s} = \sqrt{\frac{\alpha - \alpha^2}{\alpha^2}} = \sqrt{\frac{1}{\alpha} - 1} \end{aligned}$$

$$\rightarrow \text{Form Factor} = \frac{V_{or}}{V_o} = \frac{\sqrt{\alpha} V_s}{\alpha V_s} = \boxed{FF = \frac{1}{\sqrt{\alpha}}}$$

S/E → The output voltage can be controlled by any of the following methods,

1) Pulse width Modulation :- In this method the turn ON time of the diodes gets modulated, while maintaining the frequency as constant.

2) Frequency modulation :- In this method chopping frequency gets modulated, while maintaining the turn ON time as constant.

• disadvantages


1) It may interfere with neighbouring communication line

2) Filter design for eliminating the harmonics will be complex because of the wide frequency variations

STEP UP CHOPPER (BOOST CHOPPER)

$$V_s = \frac{L \, di}{dt} \quad \left. \begin{array}{l} s = \text{closed} \\ V_L = V_s \end{array} \right\}$$

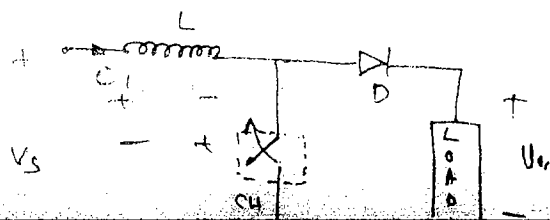
$$dt = \frac{V_s}{\frac{di}{dt}} \, dt = \frac{V_s}{I} \, t + t$$



$$C = \frac{V_S}{L} \cdot t + k \quad \left. \begin{array}{l} \text{Linear variation} \\ y = mx + c \end{array} \right\}$$

at $t = \infty \quad C = \infty \Rightarrow$ S.C

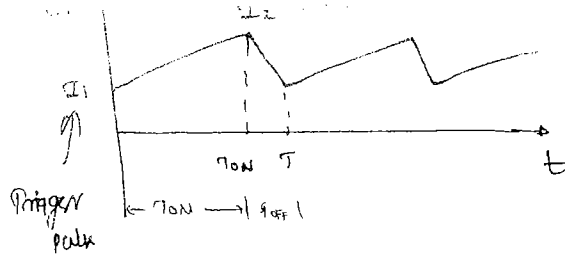at $t = M, N, S \quad C \neq \infty \neq$ S.C



→ current during switch closed, \rightarrow some \rightarrow L stores energy
 \rightarrow switch opens \rightarrow current tends to decrease, \rightarrow some \rightarrow then \rightarrow V_L \rightarrow delivering energy (due to change in slope)

V_S and V_L are supporting. ϵ

$$-V_S - V_L + V_o = 0 \Rightarrow \boxed{V_o = V_S + V_L} \Rightarrow V_o \text{ is more than supply}$$

SIR
 → The extra voltage required to make the output voltage more than supply voltage will be produced by the stored energy of inductor. During 'ON' time inductor stores the energy and during 'OFF' time inductor it deliver the energy.

→ Expression for average o/p voltage can be obtained by equating the energy stored by the inductor and energy delivered by the inductor

During TON PERIOD

$$W_{Lin} = \text{average voltage across inductor} \times I_{avg}(L) \times T_{ON}$$

$$= V_S \cdot \left(\frac{I_1 + I_2}{2} \right) \cdot T_{ON} \quad \text{--- (1)}$$

During TOFF PERIOD

$$W_{Lout} = \text{avg } V_{avg}(L) \times I_{avg}(L) \times T_{OFF}$$

$$= V_o - V_S \cdot V_L \times \frac{I_1 + I_2}{2} \times T_{OFF}$$

Note:

- $I_2 - I_1$ - may not be linear practically because load effect is there
- At time $I_2 - I_1$ is LINEAR
- Area under the curve

$$= (V_o - V_s) \cdot \frac{I_1 + I_2}{2} \cdot T_{OFF}$$

$$\text{①} = \text{②} = 0 \quad w_{in} = w_{out}$$

$$V_s \cdot T_{ON} = (V_o - V_s) T_{OFF} \Rightarrow V_s (T_{ON} - T_{OFF}) = V_o T_{OFF}$$

Notes

$$\alpha = \frac{T_{ON}}{T}$$

$$T_{OFF} = T - T_{ON}$$

$$= T(1 - \alpha)T$$

$$V_s \neq V_o T_{OFF} = V_o (1 - \alpha) T$$

$$= 0 \quad V_o = \frac{V_s}{1 - \alpha}$$

- OBS:
- $\alpha < 1$ always
 - $1 - \alpha = 0$
 - $\frac{V_s}{1 - \alpha} \neq V_o \cdot V_o > V_s$

Mode in the circuit :- inductor load $R(L)$, chopper ON, inductor should store energy, E start making the conduction through chopper.

CLASSIFICATION OF CHOPPERS


• Quadrant operation :- It is best to select a suitable chopper by knowing the quadrant operation.

eg:- we need +ve power chopper only

I quadrant - as the preferred.

-ve power power app (load \rightarrow source)

II or (IV) - voltage neg abve.

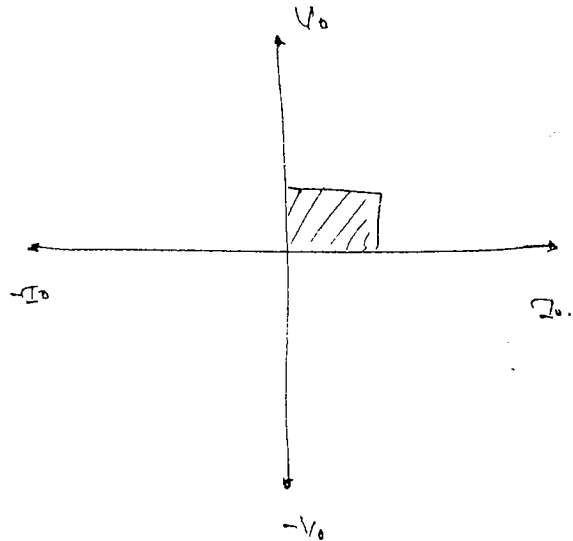


• classification is useful to select a chopper suitable for required application

TYPE A CHOPPER (I Quadrant chopper)

• $v_{in} > 0$, $v_{out} > 0$


\rightarrow out put power is always +ve

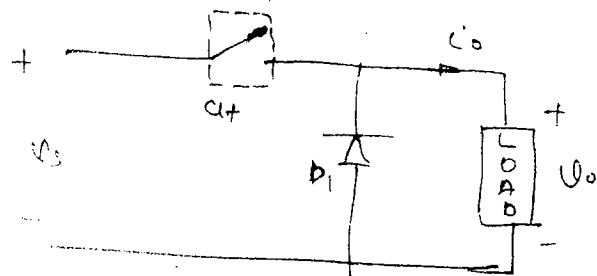i.e. It flows from supply to load terminals,





\rightarrow It is suitable only for motoring applications.

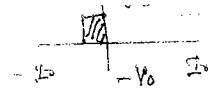2) Type B chopper : It is a two quadrant chopper



• Load must be of RLE in Nature.


• CH₂ closed

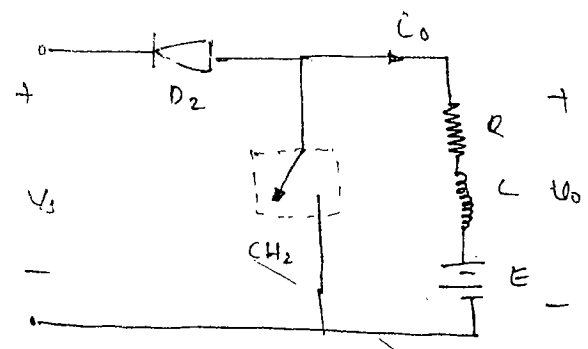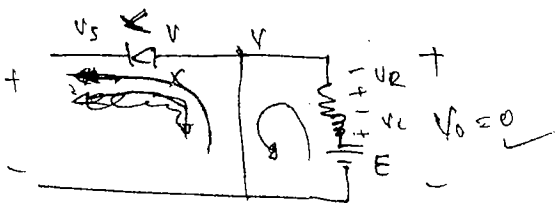

• Current is always -Vc, while voltage +Vr or -Vc

→ Power is -Vc, Flows from load - source, It is suitable only for

Regenerative braking applications.

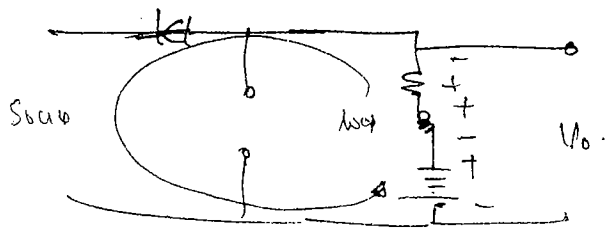


Note:-
Regenerative Application The formula to be employed for the average output voltage is same as the step up chopper.

$$[V_o = \frac{V_s}{1-\alpha}]$$

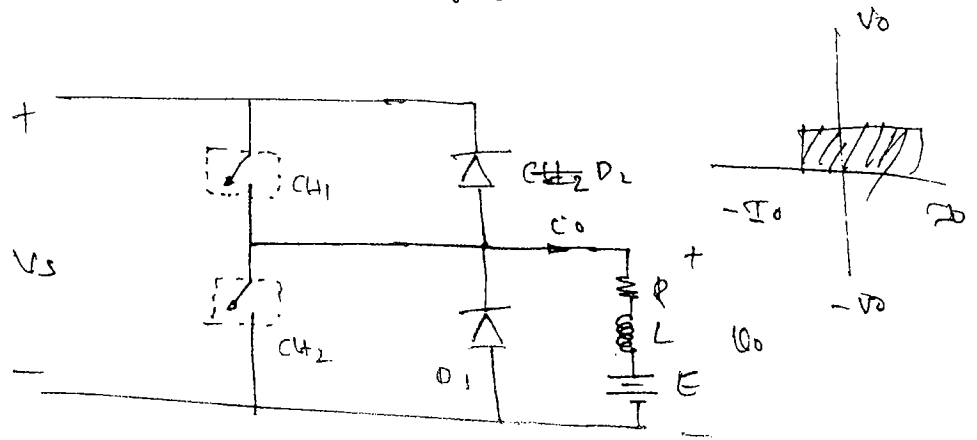3) Type C chopper : Two Quadrant type A chopper

• Type C chopper can be obtained by merging type A and type B choppers.



• Output power can be +ve as well as -ve. i.e. power flows in both the directions. It is suitable for both motoring as well as regenerative braking applications.

4) Type D chopper, two Quadrants type B chopper

$CH_1 + CH_2$ - closed
 $V_o = V_s = +ve$

$DH + CH_2$ - open



D_1, D_2 conductors ~~to~~ L.

→ out put power can be +ve as well as

-ve i.e. it flows in both the direction. It is suitable

for motoring as well as Regenerative braking appl.

V_L depends on ston the cut ②.

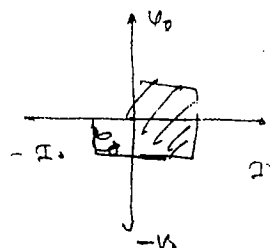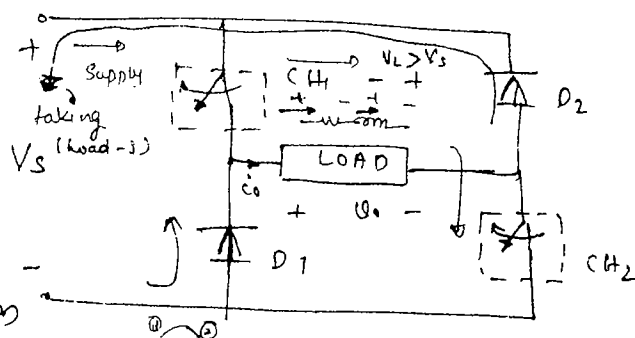

→ ~~com~~ should be there.


5) Type E chopper

20/03/11 2

Type E chopper can be obtained by merging either '2' type C, or '2' type D' choppers

Steady state analysis of type A chopper

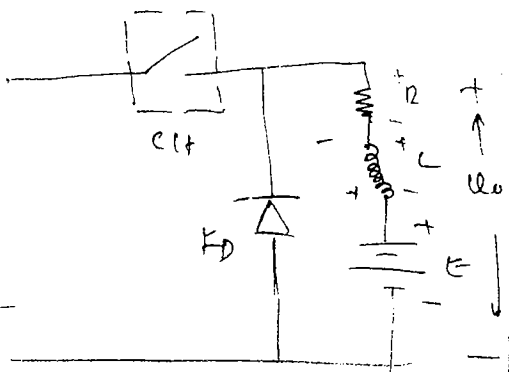The value of inductance is so selected such that it is capable to support the conduction, through out T_{off} time interval. V_s then the conduction of inductor (if conduction does last more $V_o \neq 0$ $V_o = E$)




$V_o = \alpha V_s$

$V_{or} = \sqrt{\alpha} V_s$

$I_{max} = \frac{V_s}{R} \left[\frac{1 - e^{-T_{on}/\tau_a}}{1 - e^{-T/t_a}} \right] - \frac{E}{R}$ (A.W. Derivation)

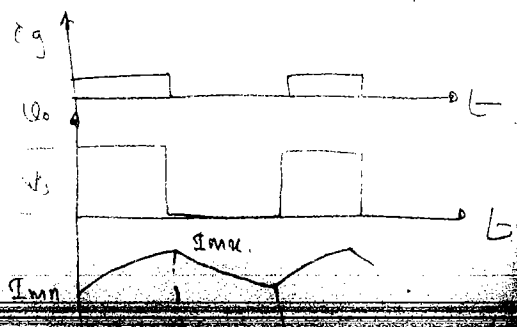$I_{min} = \frac{V_s}{R} \left[\frac{e^{-T_{off}/\tau_a}}{1 - e^{-T/t_a}} \right] - \frac{E}{R}$



$$\Delta I = I_{max} - I_{min}$$

$\tau_a = \text{load time constant} = L/R$

$$= \frac{V_s}{R} \left[\frac{(1 - e^{-T_{ON}/\tau_a})}{1 - e^{-T/\tau_a}} - \frac{e^{-T_{ON}/\tau_a} - 1}{e^{T/\tau_a} - 1} \right]$$

$$= \frac{V_s}{R} \left[\frac{(1 - e^{-T_{ON}/\tau_a})}{(1 - e^{-T/\tau_a})} - \frac{e^{-T_{ON}/\tau_a} (1 - e^{-T/\tau_a})}{e^{T/\tau_a} (1 - e^{-T/\tau_a})} \right]$$

$$= \frac{V_s}{R} \left[\frac{1 - e^{-T_{ON}/\tau_a}}{1 - e^{-T/\tau_a}} \right] \left[\frac{e^{T/\tau_a} - e^{-T_{ON}/\tau_a}}{e^{T/\tau_a} - 1} \right]$$

$$= \frac{V_s}{R} \left[\frac{1 - e^{-T_{ON}/\tau_a}}{1 - e^{-T/\tau_a}} - e^{-T_{ON}/\tau_a} \left(\frac{1 - e^{-T/\tau_a}}{1 - e^{-T/\tau_a}} \right) \right]$$

$$= \frac{V_s}{R} \left[\frac{1 - e^{-T_{ON}/\tau_a}}{1 - e^{-T/\tau_a}} - \frac{e^{-T_{OFF}/\tau_a} (1 - e^{-T/\tau_a})}{1 - e^{-T/\tau_a}} \right]$$

$$\Delta I = \frac{V_s}{R} \left[\frac{(1 - e^{-T_{ON}/\tau_a}) (1 - e^{-T_{OFF}/\tau_a})}{1 - e^{-T/\tau_a}} \right]$$

$$\text{Current Ripple} = (\Delta I) = \frac{V_s}{R} \left[\frac{(1 - e^{-T_{ON}/\tau_a}) (1 - e^{-T_{OFF}/\tau_a})}{(1 - e^{-T/\tau_a})} \right]$$

$$\text{Percent Ripple} = \frac{\Delta I}{V_s/R} = \frac{(1 - e^{-T_{ON}/\tau_a}) (1 - e^{-T_{OFF}/\tau_a})}{1 - e^{-T/\tau_a}}$$


$$T_{ON} = \alpha T; \quad T_{OFF} = (1-\alpha) T$$

$$DI = \frac{V_s}{R} \left[\frac{(1 - e^{-\alpha T/\tau_a}) (1 - e^{-(1-\alpha)T/\tau_a})}{(1 - e^{-T/\tau_a})} \right]$$

ripple is a function of duty cycle.

Graphs current ripple w.r.t duty cycle

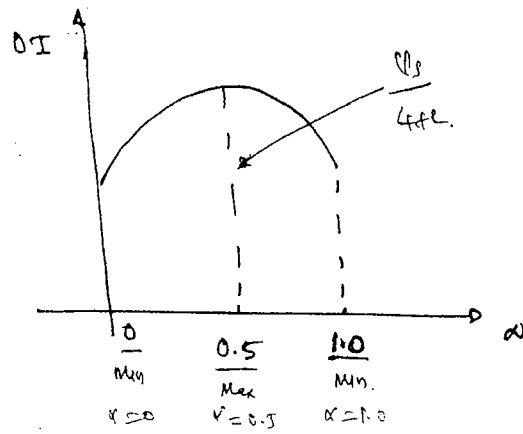- ripple or per ripple varies with the value of α
- ripple is minimum at $\alpha=0$, increases and reaches maximum at $\alpha=0.5$, then decreases minimum at $\alpha=1.0$.
- For $\alpha=0.5$, ripple will be maximum



$$(DI)_{max} = \frac{V_s}{R} \left[\frac{(1 - e^{-0.5T/\tau_a}) (1 - e^{-0.5T/\tau_a})}{1 - e^{-T/\tau_a}} \right]$$

let $\frac{T}{\tau_a} = x$

$$(DI)_{max} = \frac{V_s}{R} \left[\frac{(1 - e^{-0.5x}) (1 - e^{-0.5x})}{(1 - e^{-x}) = (1 + e^{-0.5x}) (1 - e^{-0.5x})} \right]$$

$$= \frac{V_s}{R} \left[\frac{(1 - e^{-0.5x}) (1 - e^{-0.5x})}{(1 + e^{-0.5x}) (1 - e^{-0.5x})} \right]$$

$$= \frac{V_s}{R} \tanh \cdot \frac{1}{4} x$$

$$= \frac{V_s}{R} \tanh \cdot \frac{T}{\tau_a} \cdot \frac{1}{4} =$$

$$(DI)_{max} = \frac{V_s}{R} \tanh \left(\frac{1}{4} \cdot \frac{L}{R} \cdot \frac{1}{L/C} \right) = \frac{V_s}{R} \tanh \frac{R}{4L}$$

$$(DI)_{max} \approx \frac{V_s}{R} \cdot \frac{R}{4fL} = \frac{V_s}{4fL}$$

$$\left. \begin{matrix} 0 \rightarrow 0 \\ \tan \theta = 0 \end{matrix} \right\}$$

$$(DI)_{max} = \frac{V_s}{4fL}$$

Ripple.


(DI) Reduction

$\rightarrow (DI)_{max} \propto \frac{1}{f}$, means the chopping frequency the ripple is less, the time period is less.

Physically in waveform

$\rightarrow I_{avg(1)} \text{ ripple} > I_{avg(2)} \text{ ripple}$

$$I_{avg(1)} = I_{avg(2)}$$

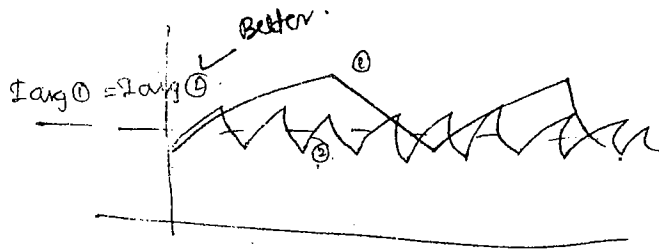


\rightarrow here $I_{avg(2)}$ is better.


SIR

\rightarrow To reduce the current ripple, it is preferable to employ, higher value of chopping frequency. Hence faster devices may be adopted in the chopper.

DISCONTINUOUS CONDUCTION.

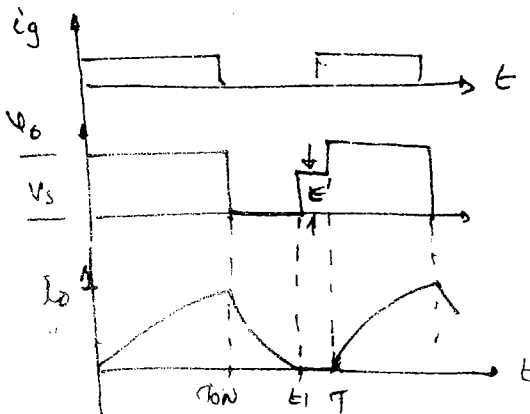
The value of inductance, in load circuit is unable to support the conductor throughout half time interval, then conductor becomes discontinuous - in this period



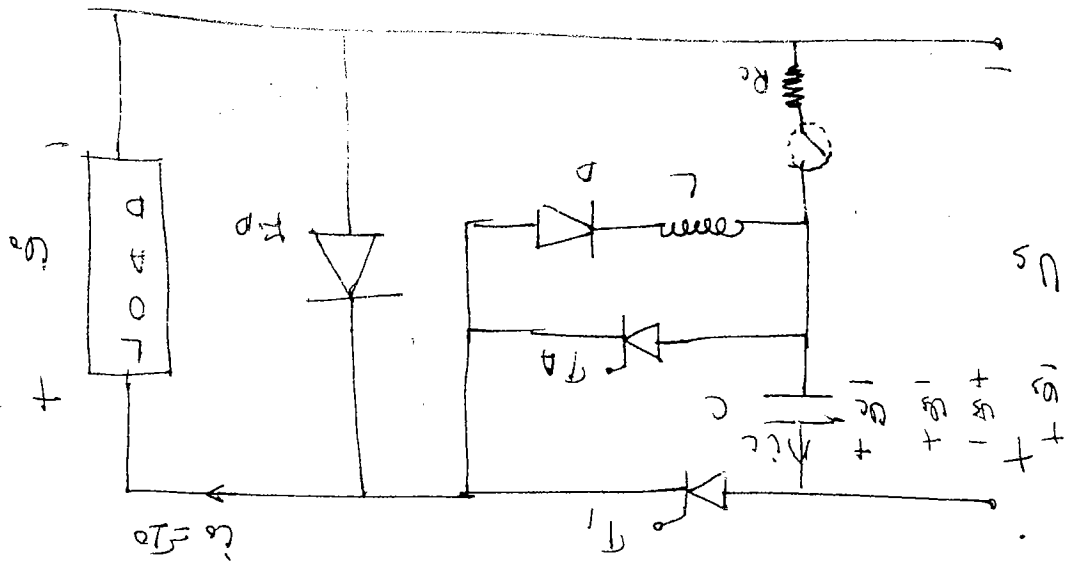

VOCRAHE KOMMUTATED CROPPER

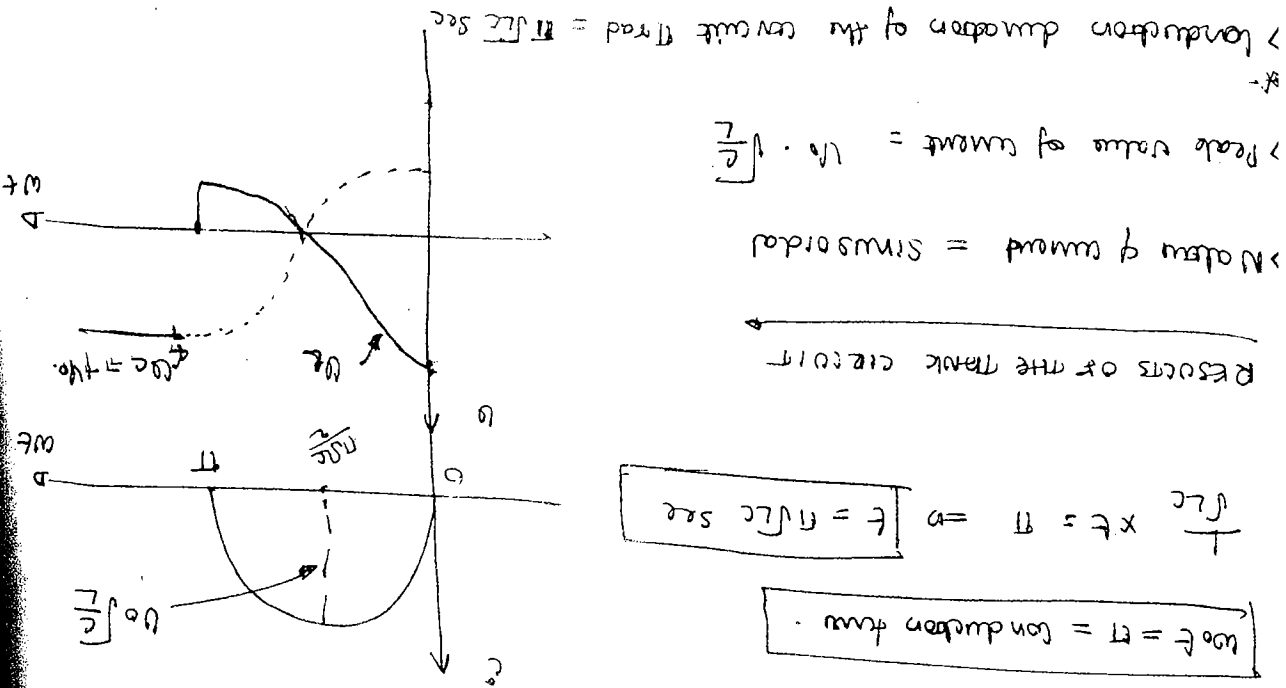* At the end of conduction, the voltage across the capacitor gets reversed.



- in -ve half cycle after π diode is in reverse biasing state hence -ve conduction stops. only the half cycle conduction occurs.

$$V_C = -V_0 \cos \omega t$$

$$V_C = -V_0 \cos \omega t + k$$

$$V_C = -V_0 \cos \omega t + k$$

$$V_C = \frac{1}{L} \int \cos \omega t dt = \frac{1}{L} \left(\frac{\sin \omega t}{\omega} \right) + k$$

$$V_C = \frac{1}{L} \times \frac{1}{\omega} = \frac{1}{\omega L}$$

$$i(t) = V_0 \int \sin \omega t dt = -\frac{V_0}{\omega L} \cos \omega t + k$$

$$= \frac{V_0 \cdot \cos \omega t}{\omega L}$$

$$= \frac{V_0}{L} \cdot \frac{1}{s^2 + \omega^2 L^2}$$

$$I_C = \frac{V_0}{L} \cdot \frac{1}{s^2 + \omega^2 L^2}$$

$$I_C \cdot \frac{1}{s} = \frac{1}{\omega} \left[\frac{1}{s} + \frac{1}{L} \right] = \frac{1}{\omega}$$

$$I_C = \frac{V_0 \cos \omega t}{s}$$

$$+ I_C = V_0 \cos \omega t$$

$$I_C = \frac{V_0 \cos \omega t}{L}$$

The o/p voltage is equal to E .

1000-910

then

→ average voltage V_o

$$V_o = \frac{\text{Area Total}}{\text{Time period Total}} = \frac{1}{T} \left[V_s \times T_{on} + E(T - T_{on}) \right]$$

$$V_o = \alpha V_s + E \left(1 - \frac{E_1}{T} \right)$$

OBS:

→ The average value of o/p voltage is more in discontinuous conduction compared to continuous conduction.

FOURIER ANALYSIS OF OUTPUT VOLTAGE (CONTINUOUS CONDUCTION)

$$V_o = \alpha V_s$$

$$I_{or} = \sqrt{2} V_s$$

$$V_o = V_o + \sum_{n=1,2,\dots}^{\infty} V_m$$

where $V_o = \alpha V_s$

not time varying

Time varying function

$$V_m = \left\{ \frac{2V_s}{n\pi} \sin(n\pi\alpha) \right\} \sin(n\omega t - \theta_n)$$

V_m

$$V_{rms} = \frac{V_m}{\sqrt{2}} \Big|_{n=1} = \frac{2V_s}{\pi\sqrt{2}} \cdot \sin(\pi\alpha) \quad \boxed{V_{o1} = \frac{\sqrt{2}V_s}{\pi} \sin(\pi\alpha)}$$

fundamental

• Choppers operation is based on forced commutation. There are two types

of forced commutation

→ Voltage commutation


→ Current commutation.

TANK CIRCUIT

- It is the main element to realize the forced commutation ckt.
- Tank circuit consists of Inductor, Capacitor and UNIDIRECTIONAL DEVICE (Diode or Thyristor).


THEORY OF TANK CIRCUIT

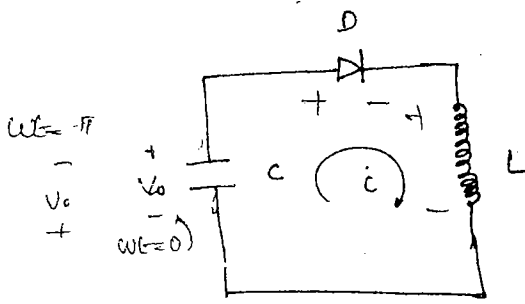- $V_0 = \text{initial voltage of } C$
- due to that 'D' F.B
- current i flows



$$L \frac{di}{dt} - \frac{1}{C} \int i dt \neq 0$$
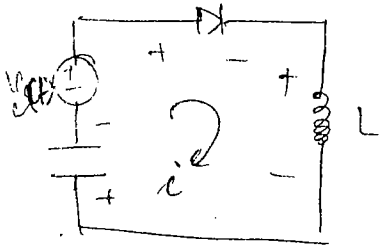
$$L \frac{di}{dt} = \frac{1}{C} \int i dt \quad \text{SIR}$$



~~$L \frac{di}{dt} + \frac{1}{C} \int i dt = V_0$~~ Vels

~~$S \cdot I \cdot \omega + \frac{I \cdot I \cdot \omega}{CS} = \text{Var}$~~

Net:

$$i = \frac{dq}{dt} \quad C = \frac{Q}{V}$$

$$dq = C dt \quad Q = CV$$

Apply L.P


~~$[S I \omega - 0] + \frac{1}{C} [$~~



$$q = \int i dt$$

$$\int i dt = \text{area under curve}$$

$$\int v dt = \psi = Li$$

S-Plan

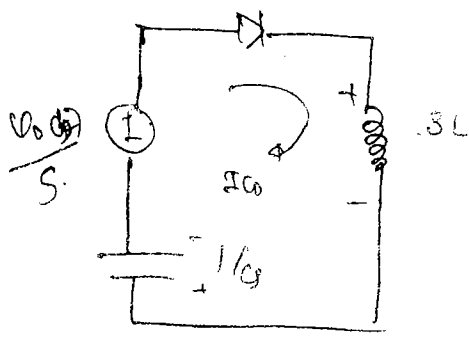

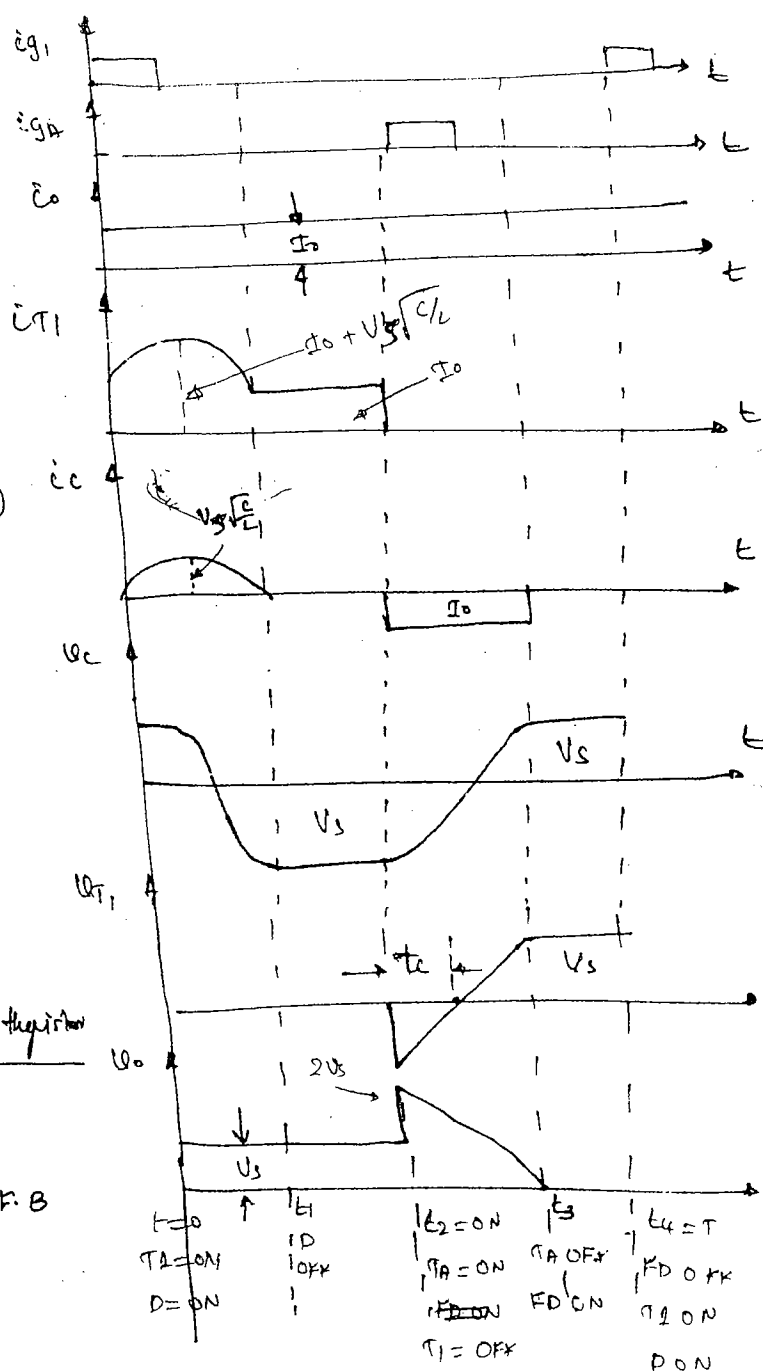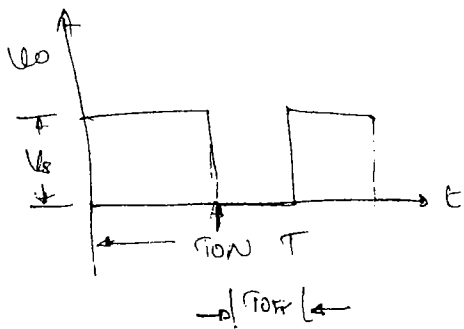

\$t=0\$	\$t_1\$	\$t_2\$	\$t_3\$	\$t_4\$
\$T_A = ON\$	\$T_D = OFF\$	\$T_A = ON\$	\$T_A = OFF\$	\$T_D = OFF\$
\$D = ON\$	\$D = ON\$	\$D = ON\$	\$D = ON\$	\$D = ON\$
		\$T_1 = OFF\$	\$T_1 = OFF\$	\$T_1 = ON\$
				\$D = ON\$

- \$I_o\$ assumed constant.
- \$T_1, T_A\$ - Thyristor (main)
- \$L, C\$ - commutator (Tank circuit)
- \$D\$ - Supporting D.
- \$R_c\$ - charging Resistor.

1) S-closed (initial condition)
 $C \rightarrow V_s$ thru \$R_c - C\$.
 $V_c = V_s$ (after some \$t\$).

2) S-open - \$t=0\$, trigger \$T_1\$ main thyristor

- \$V_o = V_s\$
- Because of \$V_c = V_s\$, diode F.B conduction starts giving \$i_c\$.
- \$T_1\$ holds $I_o + i_c$
- For \$i_c = L, C\$ diode (Tank circuit).

Tank circuit

- \$i_c = \text{sinusoidal}\$
- time of \$i_c = \pi \sqrt{LC}\$ sec.
- end conduction \$e\$ reverse the polarity

$$i_{T1} = I_o + i_c$$

$$i_{T1} = I_o + \frac{V_o \sqrt{C}}{L}$$

from tank circuit (Gal & 2011)

• After \$\pi \sqrt{LC}\$ second or \$\pi\$ radians \$V_c = 0\$.

• diode - RB

3) at $t=0$, T_1 - ON, up to T_{ON} circuit is not disturbed.

So conduction through T_1 continues up to T_{ON} time. at

$T = T_{ON}$, $T_1 =$ Needs to be OFF

Turn OFF T_1

\Rightarrow Turn ON the auxiliary thyristor T_A .

• Trigger is given to $T_A \Rightarrow T_1$ got reverse voltage. $\Rightarrow T_1$ stop the conduction.

• Hence VOLTAERRE COMMUTATION (Applying a reverse voltage)
IMPULSE COMMUTATION.

\hookrightarrow short duration high voltage by T_A . $V \uparrow \uparrow$, I time is less.


• $\dot{C}_{T_1} = 0$

4) $I_c =$ constant?

T_1 - stopped ~~and~~ conduction


T_A - stopped conduction.

F.D = should keep $\Rightarrow 0$.

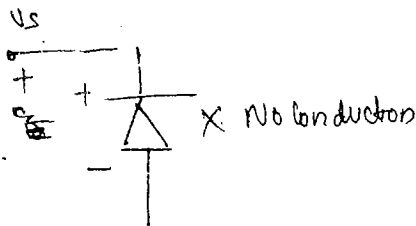

$T_A =$ conducts.

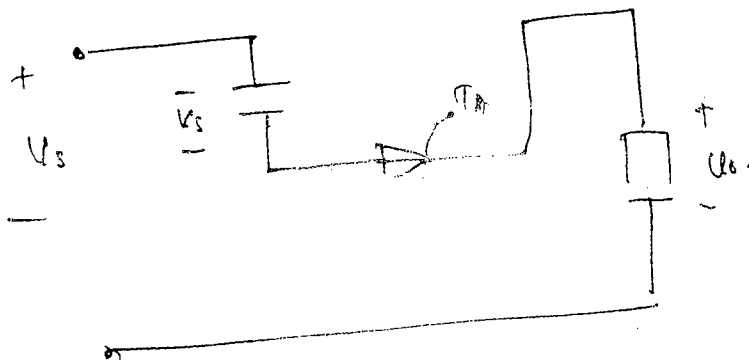$I_c \Rightarrow$ path Supply + C + T_A + load.




By KVL

$$-V_s - V_s + V_o = 0 \Rightarrow \boxed{V_o = 2V_s}$$

If I_o constant
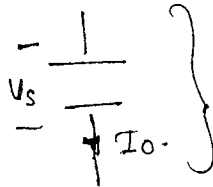
$$\Rightarrow I_c = \text{const} \quad \underline{I_o = -\dot{c}}$$



Discharging V_s decreases gradually
as and after some time τ'
it becomes zero.

$\Rightarrow V_c$

No the voltage is linear, $I_o = \text{constant}$


$$\dot{c} = C \frac{dV}{dt} \Rightarrow \frac{-I_o}{\text{constant}} = \left(\frac{dV}{dt} \right)_{\text{constant}} \Rightarrow \text{constant} = \text{slope} = \text{constant} = \text{linear curve.}$$

again $V_c = \underline{V_s}$

KVL

$$\Rightarrow -V_s + V_s + V_o = 0$$

$$\boxed{V_o = 0}$$

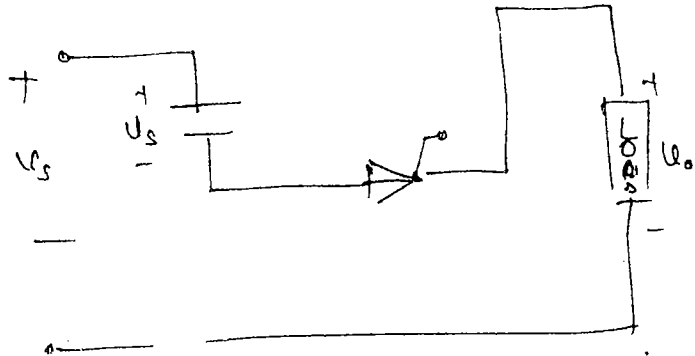

TA

TA stops the conduction when $V_c = V_s$


F.D

Now F.D coming in to conduction

$V_c > V_s$ (Assumption) (like above) it is possible as LC

This extra voltage is given by transfer of energy from L to C.

so FD

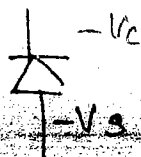

$$-V_c < -V_s$$

conduction starts FD

• at $t = T$, trigger is given to T_1 , cycle repeats.

• BS:

1) No need to close the switches S again to give charging voltage. It is already present on V_c .

2) If $V_c > V_s$ at T_{OFF} , (I_o continues, load is heavy Inductance)
 I_o $\xrightarrow{\text{slow}}$ \Rightarrow load $L \Rightarrow$ produces a voltage.

which makes the $F.D$ conduction occur.

3) $t_c =$ circuit turn OFF time of T_1 . Time taken to $I_{T1} = 0$ after applying the reverse voltage. (Specification of T_1 to be used)

4) Peak value of current through thyristor $I_o = V_s \sqrt{C/L}$

IMPULSE COMMUTATION (SIC)

• In this commutation, a high reverse voltage will be applied across the main thyristor due to which current comes to zero. It is also known as IMPULSE COMMUTATION. Since turn OFF of SCR occurs in a short duration due to a larger voltage.


Equations for C and L values

1) Commutating Capacitor

• Its value will be calculated based on circuit turn OFF time.

$$i = C \frac{dv}{dt}$$

V_c

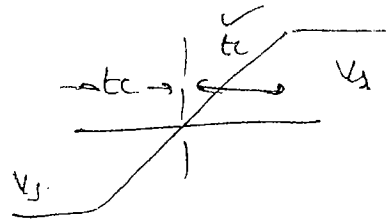

$$\rightarrow I_0 = C \times \frac{2V_s}{2tc}$$

$$C = \frac{I_0 t c}{V_s}$$

2) Commutating Inductor

• Its value is calculated based on peak current through main thyristor

i) peak current through main thyristor $I_{T2P} = I_0 + V_s \sqrt{\frac{C}{L}}$

↑
given 2011, 2012
given by the examiner.

Important points

i) peak current through auxiliary thyristor = I_0 .

ii) peak current through ~~Diode~~ capacitor = i_c
 $= V_s \sqrt{\frac{C}{L}}$ or I_0 .
 (whichever is higher)

Note: if $V_s \sqrt{\frac{C}{L}} > I_0$ } Rating to be taken by this
 • otherwise I_0 .

iii) peak diode current = $V_s \sqrt{\frac{C}{L}}$ only

Note: I_0 will not conduct through D

iii) Peak instantaneous o/p voltage = $2V_s$.

Disadvantage

→ I_{T1} - main thyristor $I_{T1P} = I_0 + V_s \sqrt{\frac{C}{L}}$

main thyristor required to be rated for more than load current. b.c of α is high.

2) $V_o = 0/p$ voltage. ~~V_s~~ is more than calculated.

eg: $\alpha = 0.5$, $V_s = 100V$

$V_o = 50V$ But here $V_o > 50$ (due to peak $2V_s$ during)

Then $\alpha = 0.45$ is chosen in practical circuit.

S12

① Main thyristor will carry more than load current hence the main thyristor is required to be rated for more than load current rating.


② The average value of o/p voltage is more in practical circuit compared to theoretical calculations.

V_o calculation

$$V_o = \frac{1}{T} [V_s \times T_{ON} + \frac{1}{2} \times 2V_s \times 2t_c]$$

$$= \frac{V_s}{T} [T_{ON} + 2t_c]$$
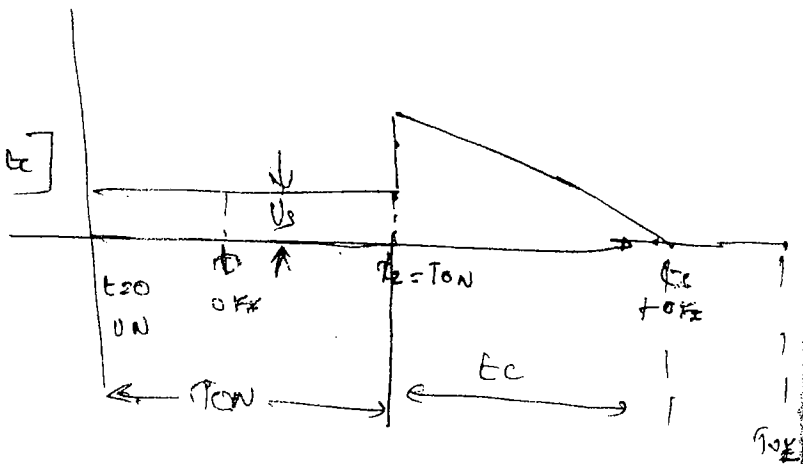
$$= \frac{V_s}{T} \left[T_{ON} + 2 \frac{C V_s}{I_o} \right]$$



$$V_o = \frac{V_s}{T} \left[T_{ON} + 2 \frac{C V_s}{I_o} \right]$$

$$V_o = \frac{V_s}{T} T_{ON}' \quad \text{where } T_{ON}' = T_{ON} + 2 \frac{C V_s}{I_o}$$

$T_{ON}' = \text{effective turn on}$

$$V_o = V_s \times \frac{T_{on}}{T}$$

$$V_o = \alpha' V_s \quad \alpha' = \text{effective duty cycle.}$$

OBS:



i) $\pi C = \pi \sqrt{LC}$ or the minimum time T_1 should be ON condition before that we cannot off the inductor.

→ Minimum turn ON time of the chopper = $\pi \sqrt{LC}$ seconds


gals 2009.

II) CURRENT COMMUTATED CHOPPER (Step down chopper)

Resonant pulse commutation

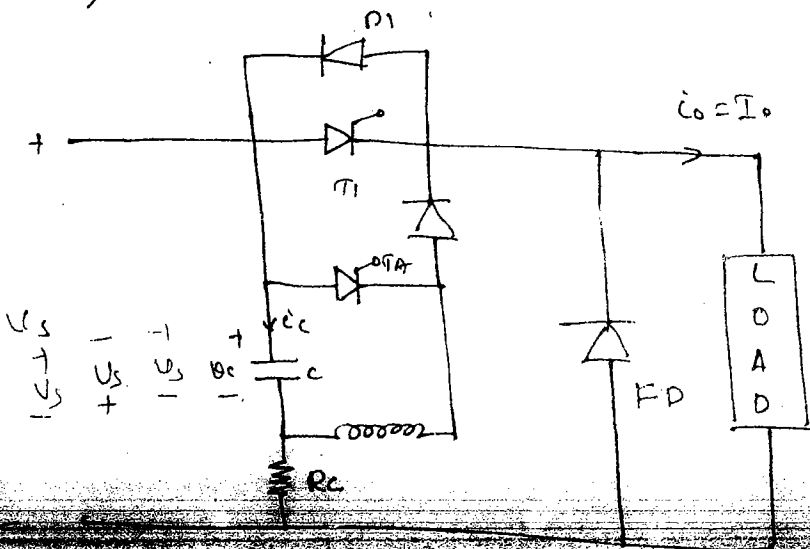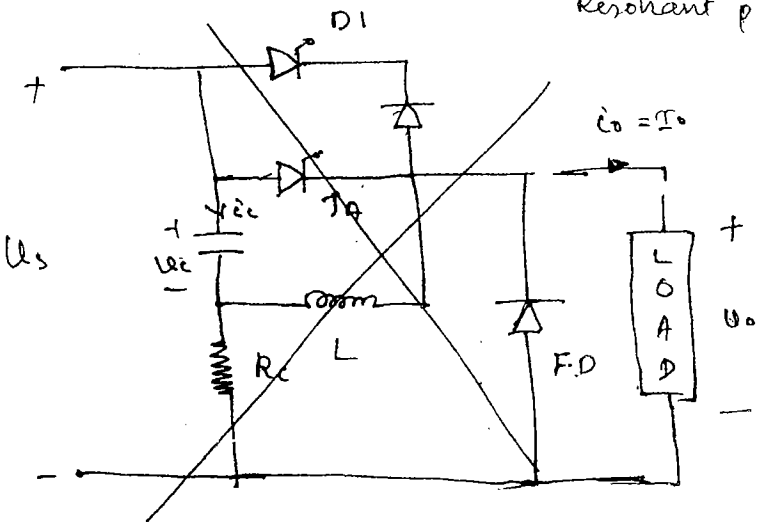


How net amt thry T_1 device?

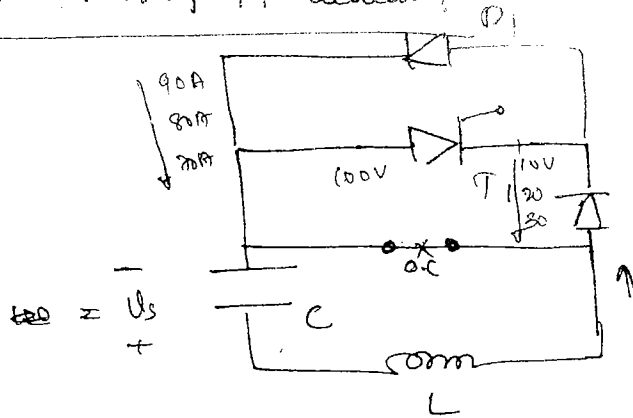

' V_s ' voltage is opposing the supply V_s , hence due to capacitor effect net voltage across T_1 gradually decreases and the net current comes to zero. (Voltage commutation is instantaneous)

How the application of reverse voltage is gradual, TOFF time is more.

D_1 does not conduct?

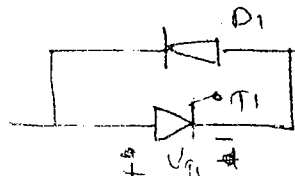


• Antiparallel connection D_1 and T_1 , unidirectional device.

• ' V_{T_1} ' small acts as reverse voltage for D_1 .

Reverse voltage across T_1 after $C_{T_1} = 0$

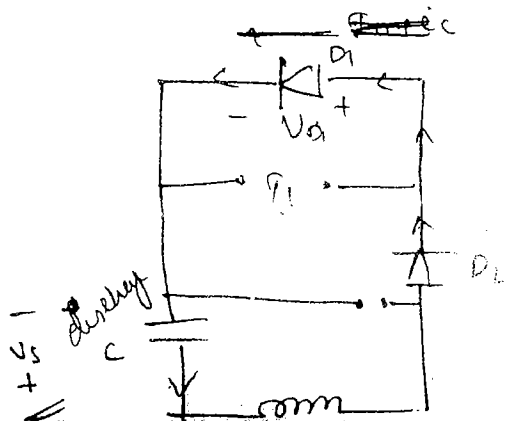• once $C_{T_1} = 0$, D_1 starts conducting.



• V_{D1} gives the reverse voltage to T_1

$$I_{CP} > I_0$$

• $I_{CP} - I_0 = \rho$ area thry D_1

• D_1 conducting

V_{D1} is very less, again's T_1 is turn off slowly.

3) V_c reaches to zero when conduction theory D_1 occurs.

V_c charges towards V_s .


3) at t_{33}

3) at t_4 $V_c < V_s$ beam still and in I_o . To make next cycle V_c needs to be ~~st~~ charged to V_s .


Assumption $I_o = \text{constant}$

FD doesn't conduct

$V_s = 100V$

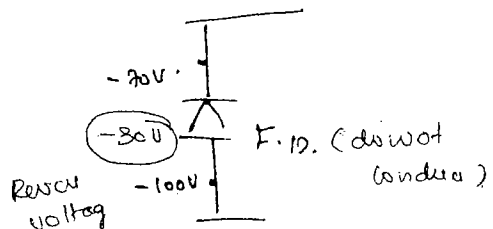

Existing path should support

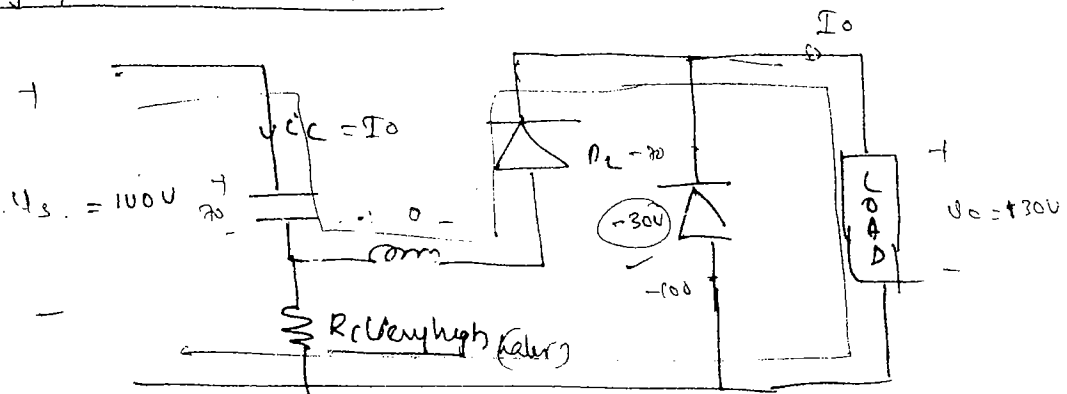

By KVL

$$-100 + 70 + V_o = 0 \Rightarrow V_o = 30V$$

ie V_s drops

$I_o = C \frac{dV}{dt}$ $C = \text{constant}$ $I_o = \text{constant}$ $\frac{dV}{dt} = \text{varies linearly} \rightarrow V_s$

4) at t_5

$V_c > V_s$? (Because of stored energy from C)

105 100

FD starts conduction




→ ~~So~~ C_c gradually reach to zero. Hence capacitor voltage

reaches V_{cp} highest value, due to prolonged conduction.
(130V)

• $V_c > V_s$.

• For next cycle we need to bring back $V_c = V_s$

5) at t_6

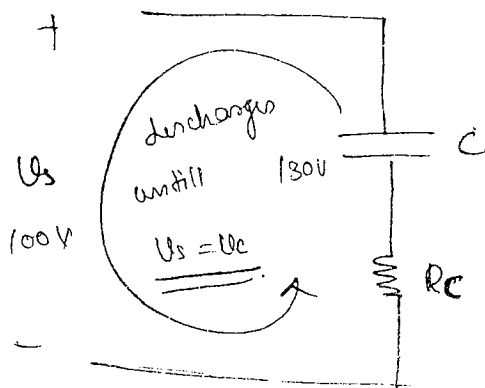

Design of R_c

• It will not hamper operation of cycle.

6) at $t = t_7$

- $F_D \neq F_X$
- T_1 ON
- $V_c = V_s$

SR

• In this commutation, an opposite current pulse is passing through the main thyristor due to which net current through SCR gradually decreases and finally comes to zero.

• It is also known as Resonant pulse commutation since an LC circuit will be connected across the thyristor at the time of commutation.

Anti parallel diode across the thyristor is useful to apply the reverse voltage after the current through thyristor comes to zero. Due to the lower value of reverse voltage it takes more time to turn OFF hence the turn OFF time increases and turn OFF power loss decreases.

- Main thyristor is required to carry only load current
- The main thyristor will stop the conduction, whenever both the currents (I_o, I_c) are equal

Calculations of L & C.

$$V = L \frac{di}{dt}$$

$$i = C \frac{dV}{dt}$$

$$L = \frac{V_s \times t_c}{(\alpha I_o) [\pi - 2 \sin^{-1}(V_s/x)]}$$

$$C = \frac{\alpha I_o \times t_c}{V_s [\pi - 2 \sin^{-1}(V_s/x)]}$$

when $\alpha = \frac{I_{cp}}{I_o} > 1$ ^{always}

occurs due to energy transfer from C to L.

$V_{cp} = V_s + I_o \sqrt{\frac{L}{C}}$ Stored energy of C = stored energy of L


$\frac{1}{2} Li^2 = \frac{1}{2} CV^2$

$V = I \sqrt{\frac{L}{C}}$

$V = I_o \sqrt{\frac{L}{C}}$

material page no: 11 - chapter 3

RE load

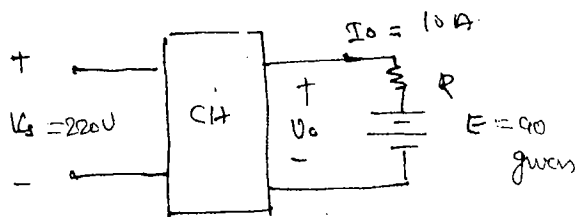

4) $E = 90J$ then $V_o = E + I_o R$.

$V_o = 90 + 10 \times 1 = 100V$

$V_o = 100V$

$\alpha = \frac{V_o}{V_s} = \frac{100}{220} = 0.4545 = 45.45\%$

5) $E = 182J$

$V_o = 121 \times 10 \times 1$

$= 132V$

$\alpha = \frac{V_o}{V_s} = \frac{132}{220} = 0.6$

Range of α (0.45 to 0.6)

$$\alpha = 0.3$$

$$V_o = \alpha V_s$$

$$V_o = 0.3 V_s$$

$$V_{rms} = \sqrt{\alpha} V_s$$

$$= \sqrt{0.3} V_s$$

$$= 0.8 V_s$$

$$P_{\text{power}} = \frac{V_o^2}{R}$$

$$= \frac{(\sqrt{0.3} V_s)^2}{R}$$

$$= \frac{0.3 V_s^2}{R}$$

ii) Ripple factor

$$= \sqrt{\frac{1}{\alpha} - 1}$$

$$= \sqrt{\frac{1}{0.3} - 1}$$

$$= 1.526$$

$$\alpha = 0.5$$

$$V_o = 0.5 V_s$$

$$V_{rms} = \sqrt{0.5} V_s$$

$$= 0.894 V_s$$

$$P_{\text{power}} = \frac{V_o^2}{R}$$

$$= \frac{0.8 V_s^2}{R}$$

$$= \sqrt{\frac{1}{0.5} - 1}$$

$$= 0.5$$

$$3) V_s \text{ dc} = 230V$$

$$R = 10 \Omega$$

$$V_{T1} = 2V \text{ (const)}$$

$$\alpha = 0.4$$

$$V_o = \alpha V_s' = \alpha (V_s - V_{T1})$$

$$= 0.4 (230 - 2)$$

$$= 91.2V$$

$$V_{or} = \sqrt{\alpha} (V_s - V_{T1})$$

$$= \sqrt{0.4} (230 - 2)$$

$$= 144.2V$$

0.6) $f = 500 \text{ Hz}$ a) peak load current

$$R = 30 \Omega$$

$$L = 9 \text{ mH}$$

$$E = V_s = 48V$$

$$\alpha = 0.5$$

$$T = \frac{1}{f} = \frac{1}{500} =$$

$$T = 0.2 \text{ ms}, T_{on} = \alpha T = 1 \text{ ms}, T_a = \frac{L}{R}$$

$$T_a = T_{on} \text{ cont} = 0.9 \text{ ms}$$

$$= \frac{48}{30} \left[\frac{1 - e^{-\frac{1 \times 10^{-3}}{0.0009}}}{1 - e^{-\frac{0.2 \times 10^{-3}}{0.0009}}} \right] - \frac{48}{30}$$

$$= 1.544 \text{ A}$$

$$b) I_{min} = \frac{V_s}{R} \left[\frac{e^{-\frac{T_{on}}{T_a}} - 1}{e^{-\frac{T}{T_a}} - 1} \right] - \frac{E}{R}$$

$$= \frac{48}{30} \left[\frac{e^{-\frac{1 \times 10^{-3}}{0.0009}} - 1}{e^{-\frac{0.2 \times 10^{-3}}{0.0009}} - 1} \right] - \frac{48}{30}$$

$$= 0.048 \text{ A}$$

c) Average load voltage $V_o = \alpha V_s$

$$= 0.5 \times 48$$

$$= 24.0V$$

d) Average load current

$$I_o = \frac{24}{30} = 0.8 \text{ A}$$

(R.L load)

(dc only)

e) CURRENT EXCURSION = cont Rip.

$$\Delta I = I_{max} - I_{min} = 1.544 - 0.048$$

$$= 1.496$$

RLC load. $R = 2 \Omega, L = 10 \text{ mH}$

$E = 26 \text{ V}$

$f = 1 \text{ kHz}$

$\gamma = 0.1$

$V_s = 220 \text{ V}$

$T = \frac{1}{f} = \underline{1 \text{ ms}}$

$T_{ON} = \alpha T = 0.1 \times 1$

$= \underline{0.1 \text{ ms}}$

$\tau_a = \frac{L}{R} = \frac{10}{2} = \underline{5 \text{ s}}$

$I_{max} = \frac{V_s}{R} \left[\frac{1 - e^{-T_{ON}/\tau_a}}{1 - e^{-T/\tau_a}} \right] = \frac{E}{R}$


$= \frac{220}{2} \left[\frac{1 - e^{-0.1/5}}{1 - e^{-1/5}} \right] = \frac{6}{2}$

$= \underline{9.016 \text{ A}}$

$I_{min} = \frac{V_s}{R} \left[\frac{e^{-T_{ON}/\tau_a} - 1}{e^{-T/\tau_a} - 1} \right] = \frac{E}{R}$

$= \frac{220}{2} \left[\frac{e^{-0.1/5} - 1}{e^{-1/5} - 1} \right] = \frac{6}{2}$

$\approx \underline{7.036 \text{ A}}$

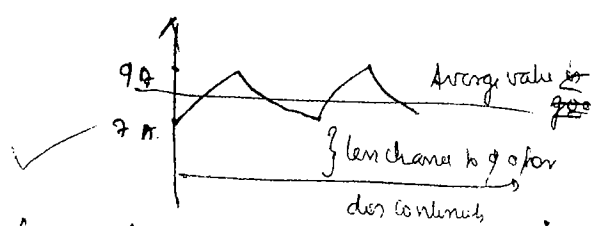

Comment:

• Best wave forms.

66) Step up chopper

$V_0 = \frac{2V_s}{3} = 2V_s$

$= 44 \text{ V}$

$V_0 = \frac{V_s}{1-\alpha} \Rightarrow 2V_s = \frac{V_s}{1-\alpha}$

$1-\alpha = 1/2$

$\alpha = 1/2$

$\frac{T_{ON}}{T_{OFF}} = 1/1$

$T_{ON} = 0.5 T_{OFF}$

$T_{OFF} = 2T_{ON}$

$= 2T$

$\frac{T_{ON}}{T} = \alpha$

$T_{OFF} = \frac{1}{2} \cdot 500 = \underline{250 \mu\text{s}}$
(1-α)T

$T_{OFF} = (1-\alpha)T = \frac{1}{4} \times 500 = 125 \mu\text{s}$

67) $V_s = 200 \text{ Vdc}, R = 40 \Omega$

$I_c = 30 \text{ A}, f = 400 \text{ Hz}$

$V_0 = I_c R = 40 \times 30 = \underline{1200 \text{ V}}$

$V_0 = \frac{V_s}{1-\alpha} \quad \left. \begin{matrix} V_s = 200 \text{ V} \\ V_0 = 1200 \text{ V} \end{matrix} \right\} \text{step up chopper}$

$1-\alpha = \frac{200}{1200} \Rightarrow 1-\alpha = \frac{1}{6}$


$\frac{T_{ON}}{T} = \alpha \Rightarrow T_{ON} = T \times \alpha$

$= \frac{5}{6} \times 2T$

$= \underline{2.093 \text{ ms}}$

$T_{OFF} = (1-\alpha)T = \underline{0.417 \text{ ms}}$

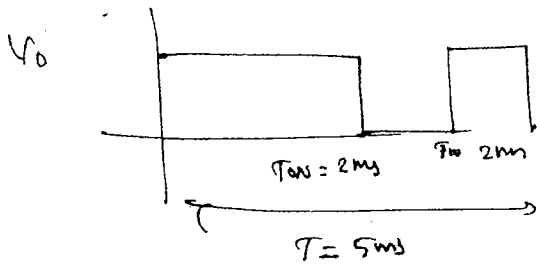08) $V_s = 200V$, $I_{Lmax} = \text{step down}$



$$\alpha = \frac{T_{on}}{T} = \frac{2}{5} = \underline{\underline{0.4}}$$

$$V_a) \gamma = \frac{1}{\sqrt{\alpha}} \cdot \sqrt{\frac{1}{\alpha} - 1}$$

$$= \sqrt{\frac{1}{0.4} - 1}$$

$$= \underline{\underline{1.2247}}$$

$$b) V_o = \alpha V_s = 0.4 \times 200$$

$$= \underline{\underline{80V}}$$

$$V_{or} = \sqrt{\alpha} V_s = \sqrt{0.4} \times 200 = 126.4V$$

$$c) V_{rms \text{ fundam}} = \frac{\sqrt{2} V_s}{\pi} \sin(\pi \alpha)$$

$$= \frac{\sqrt{2} \times 200}{\pi} \sin(180 \times 0.4)$$

$$= \underline{\underline{85.634}}$$

d) AC ripple voltage

AC = Ripple factor \times dc component

$$\text{Ripple factor} = \frac{\text{AC compo}}{\text{DC compo}} \Rightarrow$$

$$\text{AC} = 1.2247 \times 80 = \underline{\underline{97.974}}$$

09) voltage controlled class

$$V_s = 220V$$

load det

$$R = 0.5 \Omega$$

$$L = 20.2 \text{ mH}$$

$$E = 40V$$

control det

$$L = 20 \text{ mH}$$

$$C = 50 \mu F$$

$$T_{on} = 800 \mu s$$

$$T = 2000 \mu s$$

$$I_o = 80 \text{ A (constant) (given)}$$

a) Effective on period

$$T_{ion} = T_{on} + 2 \cdot \frac{C V_s}{F_o}$$

$$= 800 \times 10^{-6} + 2 \times \frac{50 \times 10^{-6} \times 220}{80}$$

$$= \underline{\underline{1075 \mu s}}$$

b) $I_{T1 \text{ peak}}$, $I_{T2 \text{ peak}}$

$$I_{T1 \text{ peak}} = I_o + V_s \sqrt{\frac{C}{L}}$$

$$= 80 + 220 \sqrt{\frac{50}{20}}$$

$$= \underline{\underline{427.85 \text{ A}}}$$


$$I_{T2 \text{ peak}} = I_o = \underline{\underline{80 \text{ A}}}$$

peak 200

Turn OFF time for I_1

$$t_c = \frac{C V_s}{I_0} = \frac{50 \times 10^{-6} \times 220}{20} = \underline{\underline{137.5 \mu s}}$$

V_c

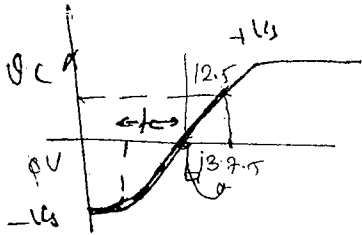

$$t_c = 137.5 \mu s$$

$$t = 150$$

$$t_1 = 12.5 \mu s$$

max capacitor

$$E = V = 0.4 \rightarrow V$$

$$t = 137.5 \rightarrow 150$$

$$V_c = \frac{220}{137.5} \times 12.5$$

$$= \underline{\underline{20V}}$$

$$-6-9 \rightarrow DC M/C - 30T$$

$$9-30-1 \rightarrow MP - 30T$$

$$8-5-30 \rightarrow NP - 30T$$

$$6-9-30 \rightarrow PE - 30T$$

22/03/11

10) $f = 500 Hz$ $\alpha = 0.5$ $I_0 = 20 A$

$$V_s = 100 V$$

a) circuit turn OFF time

$$t_{OFF} = \frac{C V_s}{I_1} = \frac{6 \times 10^{-6} \times 100}{20} = \underline{\underline{30 \mu s}}$$

b) L

$$I_{max} = 1.8 \times I_L$$

$$= 1.8 \times 20$$

$$= \underline{\underline{36 A}}$$

$$I_{max} = \frac{V_s}{R} \left[1 - e^{-\frac{R}{L} t} \right]$$

$$36 A = I_0 + V_s \sqrt{\frac{C}{L}}$$

$$= 20$$

$$\Rightarrow V_s \sqrt{\frac{C}{L}} = 0.8 I_0$$

$$\sqrt{\frac{C}{L}}$$

$$= 100 \sqrt{\frac{6 \times 10^{-6}}{L}} = 0.8 \times 20$$

$$\underline{\underline{L = 234.375 \mu H}}$$

c) $V_{om} = 2V_s = 2 \times 100 = \underline{\underline{200V}}$

11) $I_{cp} = 2 I_0$ max SCR $t_{OFF} = 30 \mu s$

$$V_s = 230V \text{ de.}$$

$$t_c = 30 \mu s$$

$$I_0 = 200 A$$

$$F.S = 2$$

$$t_c = 2 \times 30 = \underline{\underline{60 \mu s}}$$

$$L = V_s \times t_c$$

$$[230] [60 \times 10^{-6}]$$

$$\alpha = \frac{I_{cp}}{I_0} = 2$$

$$L = \frac{230 \times 60 \times 10^{-6}}{2 \times 200 \left[\pi - 2 \sin^{-1} \left(\frac{1}{2} \right) \right] \left(\frac{\pi}{180} \right)}$$

radians

$$= \underline{\underline{16.49 \mu H}}$$

$$C = \frac{(\alpha I_0) (t_c)}{V_s \left[\pi - 2 \sin^{-1} \left(\frac{1}{\alpha} \right) \right]}$$

$$= \frac{2 \times 200 \times 60 \times 10^{-6}}{230 \left[\pi - 2 \sin^{-1} \left(\frac{1}{2} \right) \right] \left(\frac{\pi}{180} \right)}$$

$$= \underline{\underline{49.82 \mu F}}$$

b) V_{cmax} ?

Energy stored in
L & C

$$V_{cp} = V_s + I_0 \sqrt{\frac{L}{C}}$$


$$= 230 + 200 \sqrt{\frac{16.49}{49.82}}$$

$$= \underline{\underline{345 V}}$$

$$\hookrightarrow I_{cp} = 2.200 A$$

$$= \underline{\underline{400 A}}$$

12) load RLK
fall to zero.

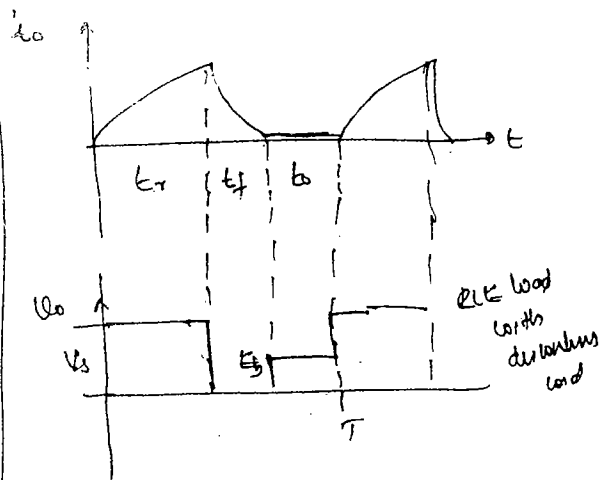

$$V_o = \frac{V_s \times t_r + E_s \times t_b}{t_r + t_b}$$

13) step down diode/buddy
RLK load and conduction to
discontinuous.

$$13) I_0 = 5 A, \alpha = 0.2$$

load = LE load



consider E's with the L load

$$V_c = 6V$$

$$L = 200 \mu H$$

$$t_{off} = 200 \mu s$$

given

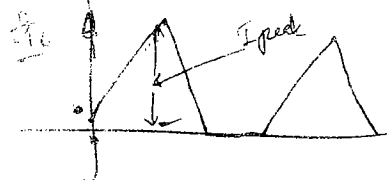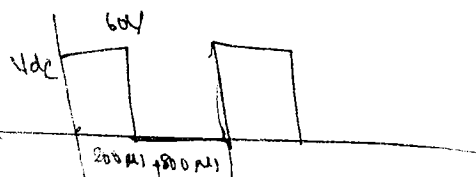

dc gives to pure conductor or a linear reaction.


$$i = \frac{V_s}{L} t$$

boundary E

$$= \Rightarrow i = \frac{V_s - E}{L} \times t_{ON}$$

$$= \frac{15.60 - 12}{20 \times 10^{-3}} \times 0.2 \times 10^{-3}$$

$$= \underline{\underline{0.48 A}}$$



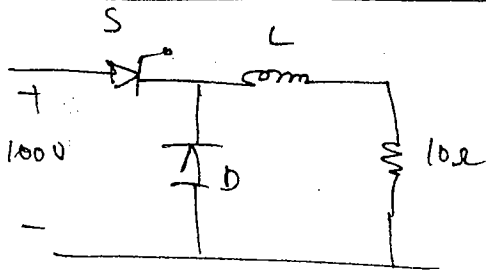


$$V_s = 100V$$

$$\alpha = 0.8$$

$$V_o = \alpha V_s = 0.8 \times 100 = 80V$$
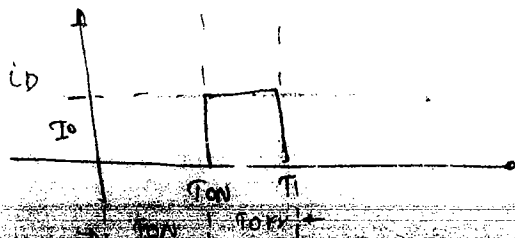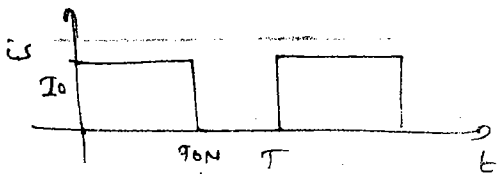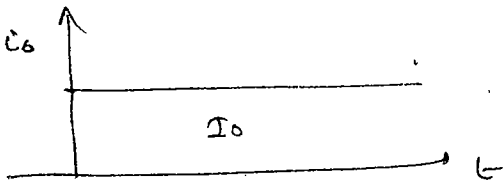
$$I_o = \frac{V_o}{R} = \frac{80}{10} = \underline{\underline{8A}}$$



$$I_{DA} = I_o \times \frac{T_{off}}{T} \quad \text{***}$$

$$= 8 \times \frac{(1-\alpha)T}{T} = 8(1-0.8)$$

$$\underline{\underline{I_{DA} = 1.6A}}$$

emba

$$\text{Switch average current} \quad \text{***}$$

$$= I_o \cdot \frac{V_o T_{ON}}{T}$$

$$\underline{\underline{= 6.4A}}$$

15) whenever S_2 is bigger than S_1 , only capacitor is given.

$$I_{SIP} = I_o + V_s \sqrt{\frac{C}{L}}$$


$$= 20 + 200 \sqrt{\frac{2\mu F}{200\mu H}}$$

$$= \underline{\underline{40A}}$$

16) $I_{ripple} \text{ ripple } \rho = \frac{V_s}{4fL} = \frac{100}{4 \times 1000 \times 200\mu H}$

$$= \frac{1}{8}$$

$$= \underline{\underline{0.125A}}$$

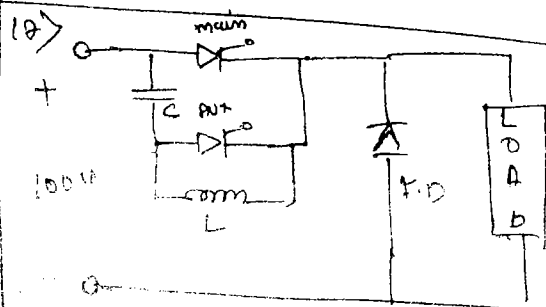

minimum $i_{in} = \frac{V_o}{L} \sqrt{L C} S_{sw}$
 Show t_{ON}

$$= 1.6A$$

$$V_0 = \frac{V_s}{T} [T_{ON}]$$


$$\leftarrow \frac{V_s}{T} \left[T_{ON} + 2 \cdot \frac{C V_s}{I_0} \right]$$

$$f = 1 \text{ kHz}$$

$$T = 1 \text{ ms}$$

$$\rightarrow V_0 = \left[T_{ON} + \frac{2 C V_s}{I_0} \right] = \underline{42.54}$$

19)

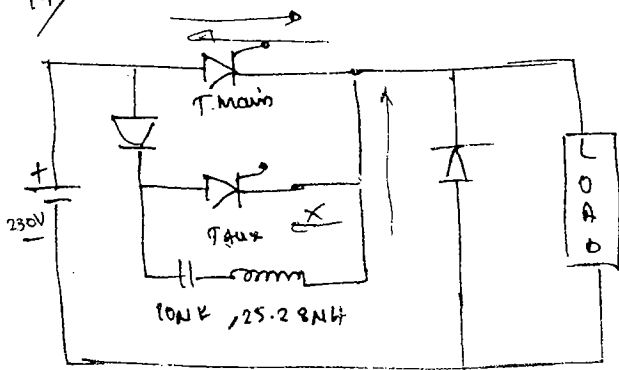


$$t = 0$$


• π SLC ~~at~~ T_{main} switch
 means ON

$$\pi \text{ SLC} = \pi \sqrt{(10 \times 10^{-6}) \times 25.28 \times 10^4}$$

$$= 10 \mu\text{s}$$

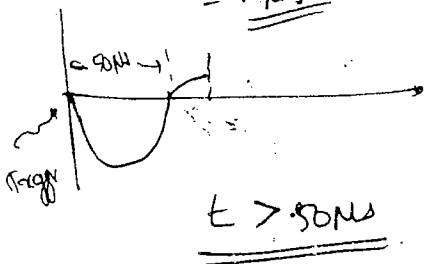

20)

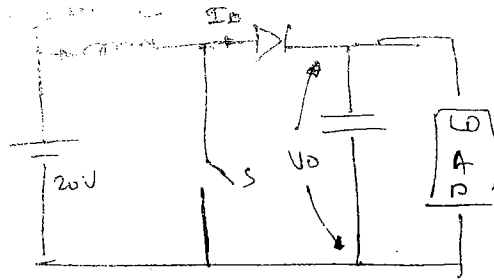

Step up chopper:

S parallel, L series

Note:

Series inductor, parallel capacitor

purpose is to make conduction smooth

• OFF when diode conducts
 (S)

$$I_{D(A)} = I_L \times \frac{T_{OFF}}{T}$$

$$= 4 \times (1 - 0.5)$$

$$I_{D(A)} = \underline{2A}$$

$$\frac{dV}{dt} = \frac{V_0}{1 - \alpha} = \frac{20}{1 - 0.5} = \underline{40V}$$

21) Step down chopper

$$V_1 = \alpha V_s$$

$$= 0.8 \times 100$$

$$= 80V$$

$$I_0 = \frac{V_1}{R} = \frac{80}{2}$$

$$= \underline{40A}$$

$$\frac{dV}{dt} = \dots$$

$$I_0 = \dots = \dots C = \underline{0.2 \mu\text{F}}$$

Step up chopper

$$V_o = 660V$$

$$V_s = 220V$$

$$\text{COFF} = 100\mu s$$

$$V_o = \frac{V_s}{1-\alpha}$$

$$660 = \frac{220}{1-\alpha}$$

$$1-\alpha = \frac{1}{3}$$

$$\alpha = \frac{2}{3} =$$

Period $T = T_{ON}$

$$T_{ON} = \alpha T$$

$$T_{OFF} = (1-\alpha)T$$

$$T = \frac{100}{1-\frac{2}{3}} = 300\mu s$$

$$T_{ON} = 300 \times \frac{2}{3} = 200\mu s$$

23) $R_L = 10\Omega$

$$V_s = 220V$$

$$f = 1kHz$$

$$2V = E_B$$

$$\alpha = 0.5$$

$$V_o = \alpha (V_s - E_B) = 0.5(220 - 2)$$

$$= 109$$

24) Boost Regulator - step up chopper

$$V_s = 5V, V_o = 15V$$

$$15 = \frac{5}{1-\alpha} \quad 1-\alpha = \frac{1}{3}, \alpha = \frac{2}{3}$$

25) Current commutation, diode

~~and~~

antigen, L and R.

$$I_1 = I_o = \frac{V_s}{R} \text{ only}$$

$$T_A = V_s \sqrt{\frac{C}{L}} = (\text{tank time})$$

26) $L = 5mH, C = 20\mu F$

$$V_C = 200V$$

3) t_{20} I_o and

$$I_p = V_o \sqrt{\frac{C}{L}} = V_s \sqrt{\frac{C}{L}}$$

$$= 200 \sqrt{\frac{20}{5}}$$


$$= 400A$$

$$t_{com} = \frac{1}{f} \sqrt{\frac{C}{L}} = 15.8\mu s$$

27) L & C connected across main when

main ON = current commutation

$$I_o = 70.7A$$

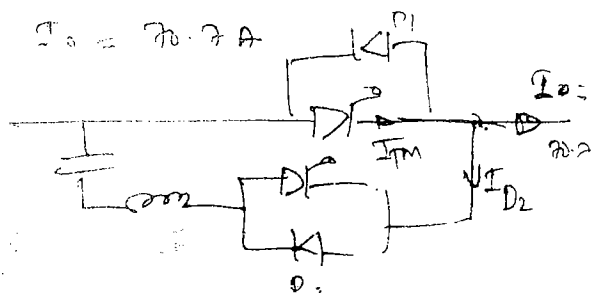

$$I_{max} = 70.7 + 200 \sqrt{\frac{10}{5}} = 170.7A$$

20) $f = 500 \text{ Hz}$, $V_s = 60 \text{ V}$

$R = 3 \Omega$, $L = 9 \text{ mH}$

2000FEES

$\frac{T_{on}}{T_{off}} = 1$

$\alpha = 0.5$

step down to mostly energy
hence use less, if no thing
is given step down.


$V_o = \alpha V_s$

$= 0.5 \times 60$

$= \underline{\underline{30 \text{ V}}}$

$I_o = V_o / R = 30 / 3 = \underline{\underline{10 \text{ A}}}$

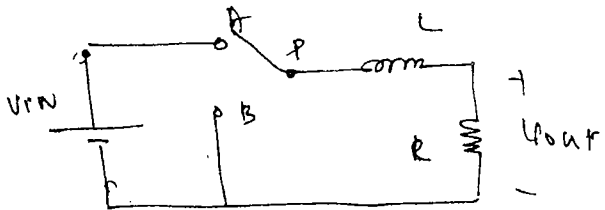
29) Rectifier \times $d_{in} - dc$
 $d_o - dc$





PA = $V_{IN} = L - \text{store}$
 $R - \text{dissipate}$

PB = $V_{IN} = 0$, $L - \text{dissipates}$ $\frac{L}{R}$

V_{out} only across R


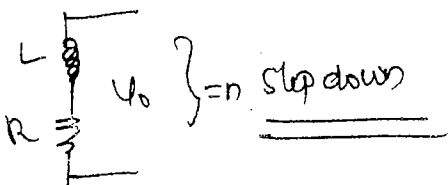


step

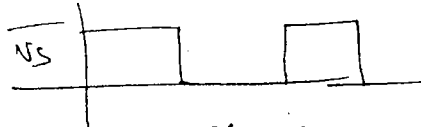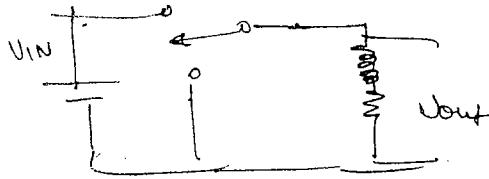

step up

here

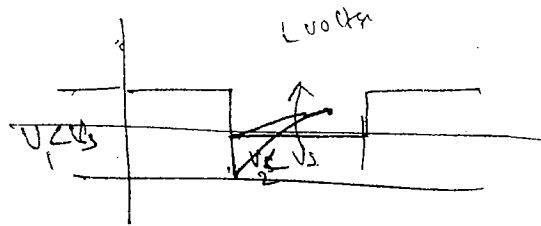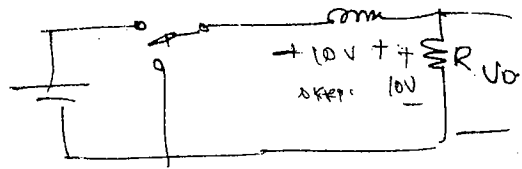

Vary $< V_s$

step down chapter

30) Regenerative braking mode

$\alpha = 0.7$, $V_s = 600 \text{ V}$
 $L - \text{step up to transfer power}$


$V_o = \frac{V_s}{1-\alpha}$

$= \frac{600}{1-0.7} = \underline{\underline{2000 \text{ V}}}$

$V = 2000 \times 9 = \underline{\underline{18 \text{ kW}}}$

2000 gauss

21/03/11

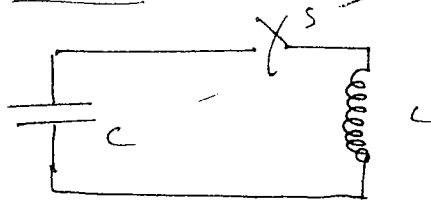


$$i = V_0 \sqrt{\frac{C}{L}} \sin \omega_0 t$$

$$i = V_0 \sqrt{\frac{C}{L}} \sin \frac{1}{\sqrt{LC}} \cdot t$$

22/03/11

$$\left. \begin{aligned} L &= 1 \text{ mH} \\ C &= 10 \text{ nF} \end{aligned} \right\}$$

$$i = 10 \sin 114 \text{ kA}$$

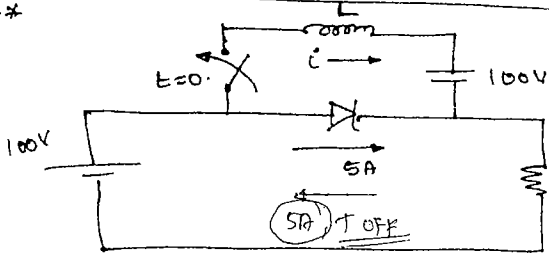

current commutation


$$i = V_0 \sqrt{\frac{C}{L}} \sin \frac{1}{\sqrt{LC}} \cdot t$$

$$C = 10 \text{ ns } 10^4 \text{ L} = 5$$

$$L = ?$$

$$L = 52 \text{ nH}$$

another method

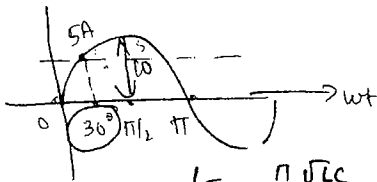

$$L = \frac{\pi \sqrt{LC}}{6} = 52 \text{ nH}$$

IES @ metal chop

$R = 20 \Omega$, $V_s = 200 \text{ V}$, $E_b = 1.5 \text{ V}$

$f = 2 \text{ kHz}$, $\alpha = 0.5$


IES
2009

$$V_{or} = \sqrt{\alpha} (V_s - V_T)$$

$$= \sqrt{0.5} (200 - 1.5)$$

$$= 140.3 \text{ V}$$
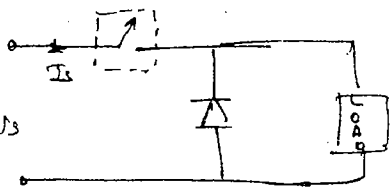
$$\text{Power} = \frac{V_{or}^2}{R} = \frac{(140.3)^2}{20} = 985 \text{ W}$$



$$V_o = \alpha (V_s - V_T)$$

$$= 0.5 (200 - 1.5)$$

$$= 99.25 \text{ V}$$

$$I_o = \frac{99.25}{20} = 4.9625 \text{ A}$$

$$f = 500 -$$


$$T = 0.5 \text{ ms}$$

$$T = 500 \text{ ns}$$

Next class

R-LOAD

23/03/11 classification

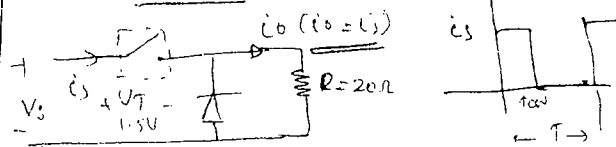

$$i_s = \frac{V_s - V_T}{R} \Rightarrow I_{SA} = \left(\frac{V_s - V_T}{R} \right) \cdot \frac{T_{ON}}{T}$$

$$P_i = 200 \times 4.96$$

$$= 992 \text{ W}$$

$$P_o = 985 \text{ W}$$

$$\eta = \frac{985}{992} = 99.2 \%$$

$$= \alpha \left(\frac{V_s - V_T}{R} \right)$$


$$= 0.5 \left(\frac{200 - 1.5}{20} \right)$$

$$= 4.96 \text{ A}$$

02) $\tau_{OFF} = 100 \mu s$

IES
2007

$\tau_{ON} = 200 \mu s$

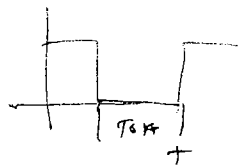

$V_0 = \frac{V_s}{1-\alpha}$

$660 = \frac{220}{1-\alpha} \Rightarrow 1-\alpha = \frac{1}{3}$
 $\alpha = \frac{2}{3}$

$\tau_{OFF} = (1-\alpha)T = \frac{1}{3}T$

$T = 300 \mu s$

$\tau_{ON} = 200 \mu s$

Pulse width halved

$\tau_{ON} = \frac{200 \mu s}{2} = 100 \mu s$

f - sam

$T = 300 \mu s$

$\alpha = \frac{100}{300} = \frac{1}{3}$

$V_0 = \frac{V_s}{1-\alpha} = \frac{3 \cdot 220}{2} = \underline{\underline{330V}}$

03) 2007

Step chopper

$\alpha = 0.5, V_0 =$

2V? can be obtained.

02) $V_0 = 600V$

$V_s = 200V$

$\tau_{OFF} = 50 \mu s$

$\tau_{ON} = ?$

$600 = \frac{200}{1-\alpha}$

$1-\alpha = \frac{1}{3}$

$\alpha = \frac{2}{3}$

$\tau_{OFF} = (1-\alpha) \cdot T$

$50 = \frac{1}{3} \cdot T$

$T = 150 \mu s$

$\tau_{ON} = 100 \mu s$

$\rightarrow \tau_{ON} \text{ km } f - \text{sam}$

$V_0 = 300V$

$T = \text{sam} = 150 \mu s$

$\tau_{ON} =$

$V_0 = \frac{V_s}{1-\alpha} = \frac{200}{1-\alpha} = 300$

$1-\alpha = \frac{2}{3}$

$\alpha = \frac{1}{3}$

$\tau_{ON} = \alpha T$

$= \frac{1}{3} \cdot 150$

$= 50 \mu s$

4) Chopping frequency


ii) increase the chopping frequency

i) frequency ↑

→ slipdown

∴ L replace C, operation not

feasible (Reason).

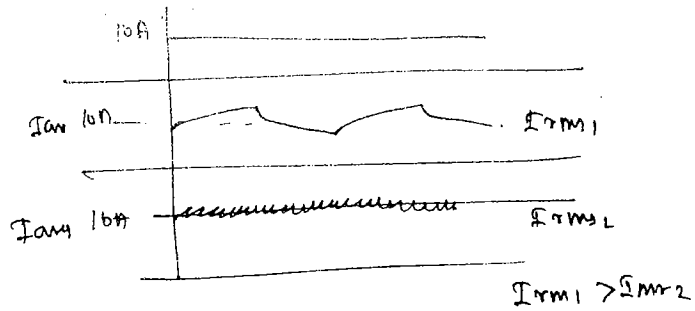

• good performance.

• Form factor = $\frac{I_{rms}}{I_{avg}}$

• Form factor → 1.1

$$\frac{I_{rms}}{I_{avg}} = 1$$

6-9-DCM/C-307
4-850-PE-307

→ Labor at DC drives speed control.

INVERTER

23/03/11

• line commutated inverter

• designed based on Appl.

• make it ON whenever P3

• Not available

• cannot feed the load directly

Force commutated inverter

• It is automatically ON when P3 is not there.

• It is having control over f , V_{out} No. of phases

• Can be feed the load directly.

• Phase controlled Rectifiers when operated with $\alpha > 90^\circ$, they are known as

line commutated inverter.

• It transfers the energy from dc to an existing ac supply network.

• The o/p voltage, frequency and No. of phases cannot be controlled.

→ INVERTER: It is a static power electronic circuit, which convert

dc to variable ac, i.e. variation in magnitude of voltage, frequency,

and No. of phases.


1- ϕ Half Bridge Inverter

- 1 ϕ supply across the load
- frequency

Std :- 50Hz

T :- 20ms


$T/2$:- 10ms

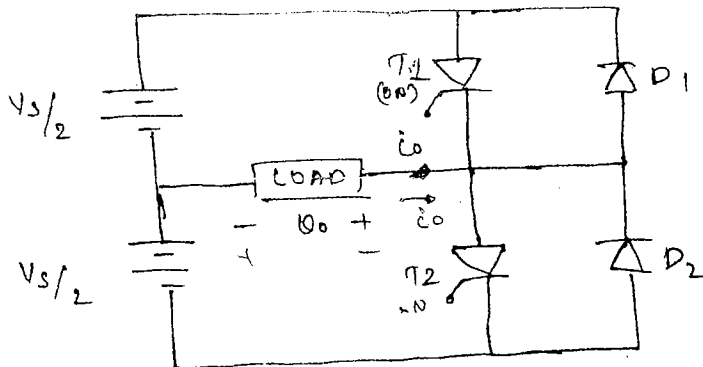

- For every 10ms we need +ve -ve transition.

Centre tapping
 $\approx Vs/2$

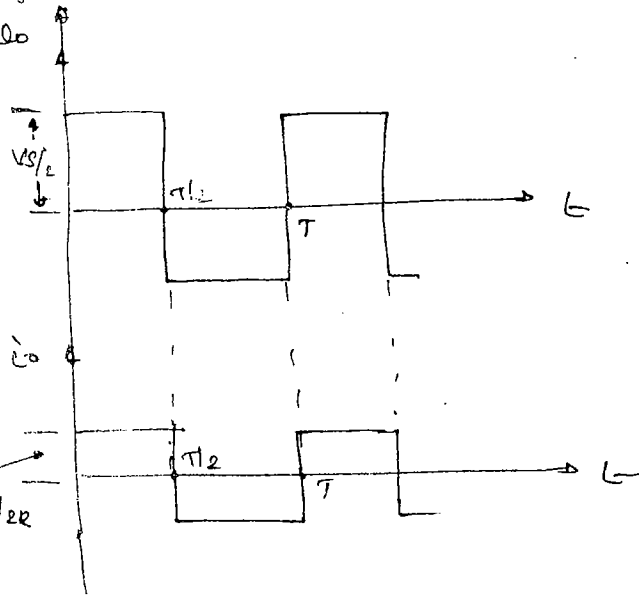T_1, T_2 are FB - (if triggered both dead s.c occur) (careful)



T_1 - triggered ON.

$$\left. \begin{aligned} V_o &= Vs/2 \\ i_o &= Vs/2R \end{aligned} \right\} \begin{array}{l} +ve \text{ (then direction)} \\ \text{convention} \end{array}$$

ON condition $T_{ON} = 10ms$ for T_1

at 10ms T_1 - OFF

T_2 triggered T_2 - ON

Again T_2 - OFF T_1 - triggered ON. } given V_o 's graph

$$\left. \begin{aligned} V_o &= -Vs/2 \\ i_o &= -Vs/2R \end{aligned} \right\} \begin{array}{l} -ve \text{ opposed to} \\ \text{conventional dir.} \end{array}$$

OBS

1) o/p is square wave changing (Alternating) Voltage or Current (this is the possible wave form).

Unwanted.

- Power through Filter to eliminate harmonics

2) Forced commutation.

• o/p dc voltage never comes to zero.

• Voltage/Current commutation applied (do not show here)

Diodes D_1 and D_2


D_1 and D_2 are required for RL load, RLC load

- Inverter operation is based on forced commutation. o/p wave forms are square wave forms. They will be passed thru filters to eliminate unwanted harmonics. The anti parallel diodes are required for all the loads except 'R load'

Average & RMS value.

Average value $V_o = 0$.

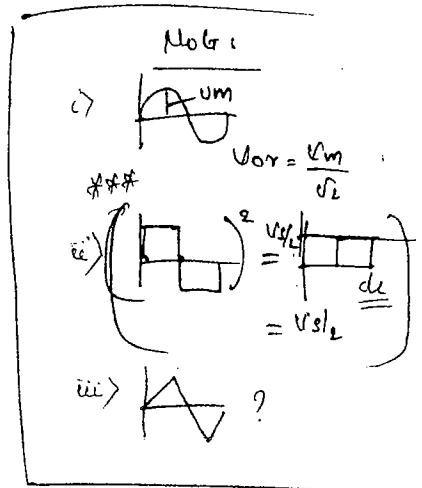
RMS value $V_{or} = \frac{V_s}{2}$ for square waveform



Disadvantage.

- At any time o/p voltage is half of the available supply voltage hence source using efficiency would be 50%.

1 ϕ - Full Bridge Inverter -

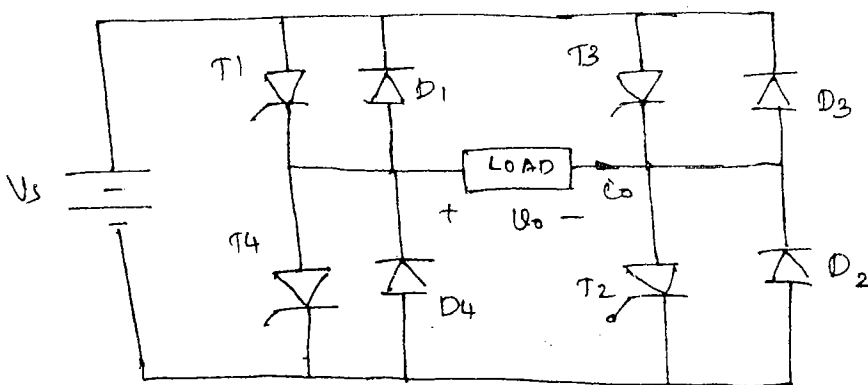



4 SCR, 4 diode.

dc i/p, load = AC with $f = 50\text{Hz}$
 $T = 20\text{ms}$
 $T/2 = 10\text{ms}$

(T_1, T_2, T_3, T_4) = All are Forward Bias

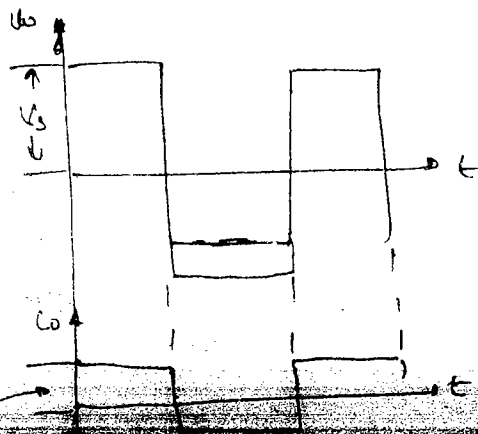CAUTION: when triggering thyristors for other wise S.C



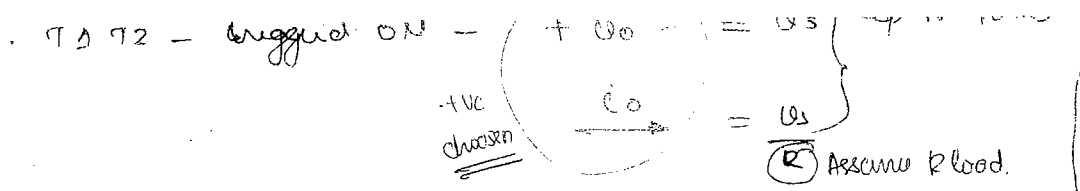

cycle repeats.

2) $T_1 = 10ms$, T3 T4 - triggered ON - $V_o + = -V_s$
 $C_0 = -\frac{V_s}{R}$

OBS

1) o/p waveform square \Rightarrow Filtered \Rightarrow sinusoidal

2) commutation forced.

3) Diode D1, D2, D3, D4 - other than R load.

4) ADVANTAGE - At any time o/p voltage is same as the supply voltage, hence 100% utilization factor is 100%

- 5) $f_1 = 50Hz$, $T = 20ms$, $T/2 = 10ms$
 $f_2 = 100Hz$, $T = 10ms$, $T/2 = 5ms$
 $f_3 = 200Hz$, $T = 5ms$, $T/2 = 2.5ms$

frequency varied \Rightarrow vary the conduction time of thyristor (o/p)

The o/p frequency of the a/c waveform, can be controlled by varying the conduction time of thyristor.

6) given supply, R-load, o/p voltage and o/p power in F Bridge inverts compare to $1/2$ Bridge relation.

$V_{oFB} = 2 \times V_{o 1/2 Bridge}$
 $P_{oFB} = 4 \times P_{o 1/2 Bridge}$

The output voltage is 2 times and output power is 4 times in full bridge inverter compared to half bridge inverter.

Steady state analysis of 2 ϕ - Full bridge inverter.

R load circuit discussed above.

Sign convention (general)

$T1, T2$	$-V_o$	\dot{C}_o
	$+V_c$	$+V_c$
$T3, T4$	$-V_c$	$-V_c$

R-L load current

i) Lagging current.

ii) shape: DC given to R-L load,

exponential variation of current.

(exponential rise and decay).

By sign convention

$$+V_c = 0 \text{ } T1, T2$$

$$-V_c = 0 \text{ } T3, T4$$

Voltage $+V_c$, $\dot{C} = -V_c$ (diode?).

1) $D1, D2$ - conduction $+V_o - = +V_c$
 $\dot{C}_o = -V_c$

2) $D3, D4$ - conduction $-V_o + = -V_c$
 $\dot{C}_o = +V_c$

(Later: diode conduction situation)


8) R-L-C load $X_L > X_C$ (overdamped) (Lagging C)

constant dc supplied to R-L-C, second order equation, which gives

the shape of o/p current as sinusoidal.

$X_L > X_C$ mean lagging.

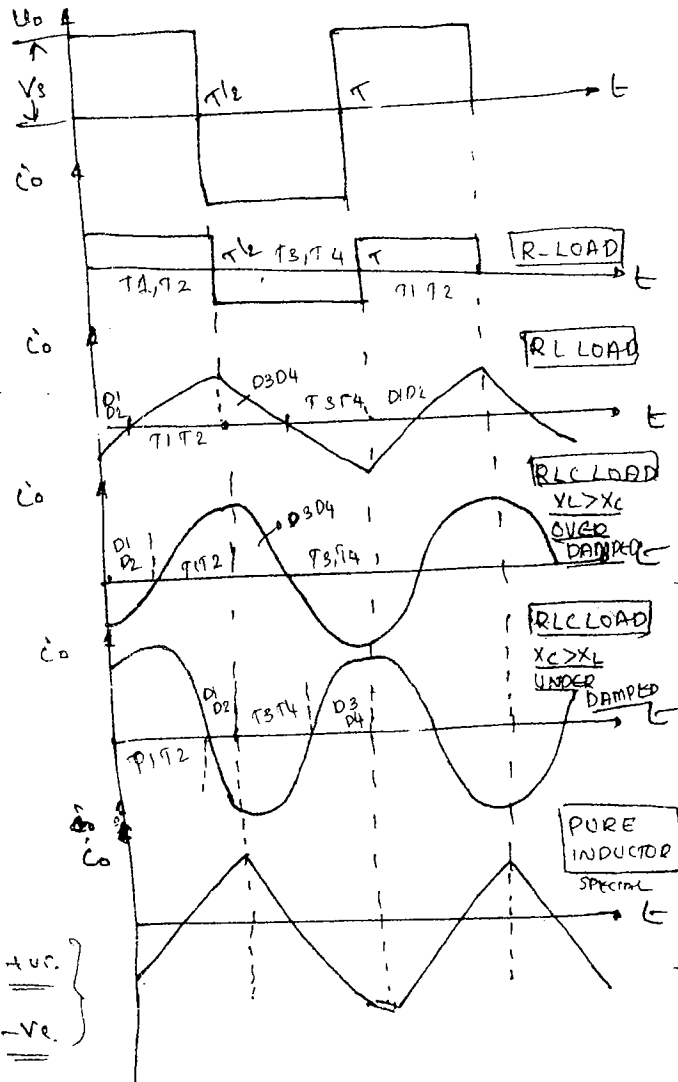R-L-C $X_C > X_L$ (leading C) (underdamped)




view waveform, view for K.W. ad 2

- D1D2 conducting $\Rightarrow n \text{ FB} = U_A > \frac{U_A}{V_s} \Rightarrow \underline{U_A > U_s}$

▷ RL load

• wave forms, before D1D2 ~~was~~ in conduction T3T4 in conduction.

• which means

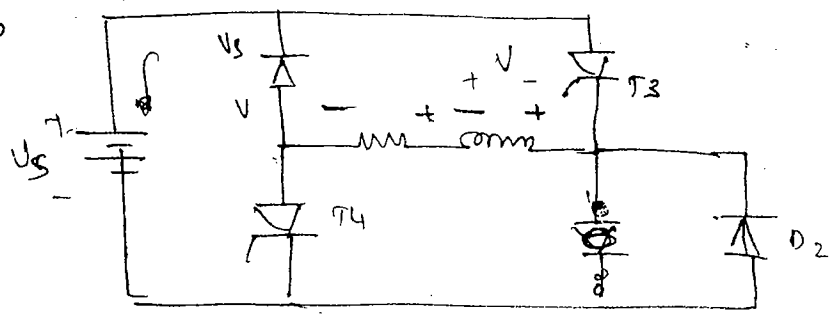

• when T3T4 - turned OFF, current polarity changes and has to become zero

here gives a slope, inductor voltage ~~has~~ reverses and produces a

$U_s > U_s$ by the $\frac{di}{dt}$ which happens while T3T4 gets OFF

• Power = - Negative power
• intermittent

NOTE:
 ▷ No Regenerative braking only happens when
 average power = 0 - U.
 ⇒
 Inductive power delivered.

OBS:

▷ Commutation

• ~~1 to 4 loads required~~ Forced commutation.


▷ LOAD COMMUTATION:

⇒ RLC load $X_L > X_C$ and $X_C > X_L$


• Diodes D1D2 conduction
then T1T2.

RLC / $X_C > X_L$

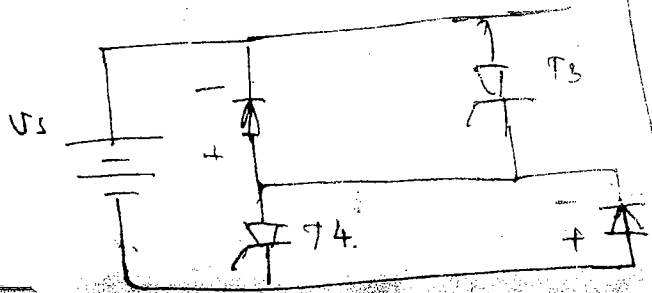• here load commutation :- commutation
 -ve voltages coming because of the nature
 of the load.



• condition

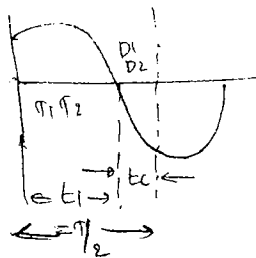

$$X_c > X_L$$

(SIR)

• In underdamped loading condition when $X_c > X_L$ load commutation can be achieved. It is possible only when anti-parallel diodes conduct for a duration $(T/2 - t_1) = t_c$

on the duration zero turnoff time t

• t_c on the turn off

we apply reverse voltage

across T_1, T_2 after this current becomes zero.

$$\frac{T}{2} - t_1 = t_c > t_g$$

• $T/2 - t_1 >$ Total turnoff time of T_1 and T_2 .

2) The current through thyristor is coming to zero and immediate application of reverse voltage are happening due to the nature of the load so it is known as

LOAD COMMUTATION


5) SPECIAL LOAD (PURE INDUCTIVE)

• de quanta pure inductor, current variation is always linear.

• slope $+V_c = 0 \Rightarrow i_0 = +V_c$
 • slope $-V_c = 0 \Rightarrow i_0 = -V_c$ } Δi waveform.

• 90° lag, $\pi/2$ crossover.

• Average power = 0 (symmetrical)

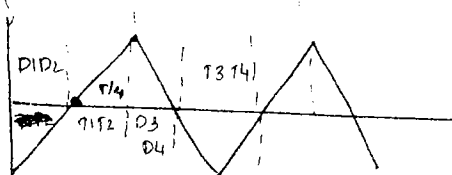

1) $i_{peak} = 3) 0$ to peak time required = $T/4$

4) Peak-Peak time = $T/2$.

OBS \Rightarrow conduction time = $T/4$ (for T_1 and T_2)

• If the inverter is feeding a pure inductive load, following are the points w.r.t

o/p wave forms.

• Nature of o/p current = Δ form 2) Nature of o/p voltage = square wave form

• Slope of current variation = V_s/L 4) Peak value of current $i_{peak} = \frac{V_s}{L} \cdot T/4$

\Rightarrow peak to peak current $= 2 I_{peak} = \frac{V_s}{Z} \cdot T/2$

\hookrightarrow conduction duration of either thyristor or diode per cycle $= T/4$.

FILTERED OUTPUT

1 ϕ 1) $V_{or_1} = \frac{V_s}{2} \implies$ Filtered (Removed unwanted harmonics) $\implies \underline{V_{or_2}}$

11 ϕ 2) $V_{or_1} = V_s \implies$ Filtered (Remove unwanted H) $= n V_{or_2}$

FOURIER ANALYSIS OF 1 ϕ INVERTERS.

1)
$$V_o = \sum_{n=1,3}^{\infty} \left\{ \frac{2 V_s}{n\pi} \right\} \sin n\omega t$$
 Symmetrical wave form } 1 ϕ - Half Bridge Inverter.

$$i_o = \sum_{n=1,3}^{\infty} \left\{ \frac{2 V_s}{n\pi Z_n} \right\} \sin(n\omega t - \phi_n)$$
 Impedance offered by nth harmonic } ϕ_n - phase angle.

11 ϕ
2)

$$V_o = \sum_{n=1,3}^{\infty} \left\{ \frac{4 V_s}{n\pi} \right\} \sin n\omega t$$
 } 1 ϕ - Full Bridge Inverter.

$$i_o = \sum_{n=1,3}^{\infty} \left\{ \frac{4 V_s}{n\pi Z_n} \right\} \sin(n\omega t - \phi_n)$$

generally

$V_o = (V_m) \sin \omega t$

$i_o = (I_m) \sin \omega t$

Fundamental component


Effective Bridge meter $V = \frac{2 U_s}{\pi \sqrt{2}}$ others (11) y

where $Z_n = \sqrt{R^2 + \left(nX_L - \frac{X_C}{n}\right)^2}$


$\phi_n = \tan^{-1} \left(\frac{nX_L - \frac{X_C}{n}}{R} \right)$

Note:
 - at nth harmonic $f = n f$
 = n x fundamental
 - hence $X_L = n X_L$
 $X_C = \frac{X_C}{n}$

Note :- Power waves

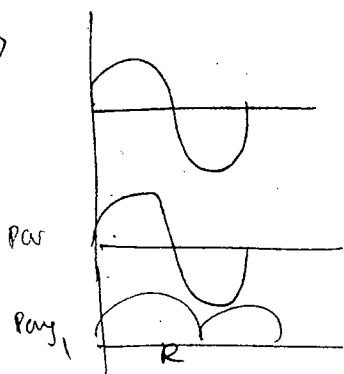

$P_{avg1} > P_{avg2}$


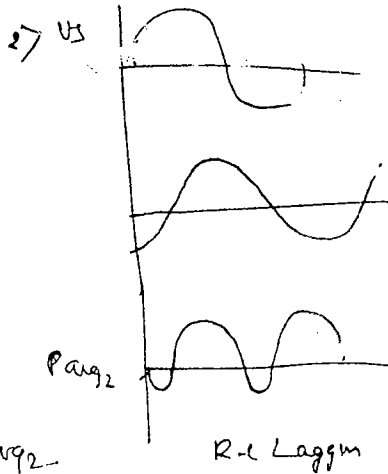


R-L Laggm


$P_f \propto n P_{avg} \downarrow$

$P_{max} = V I \cos \phi$

$\phi = 90^\circ$

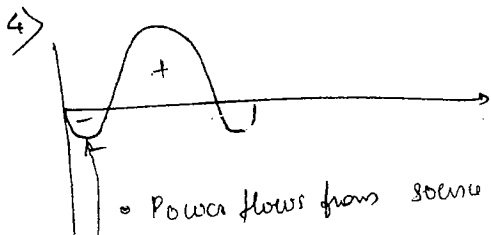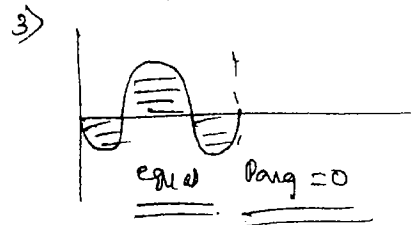

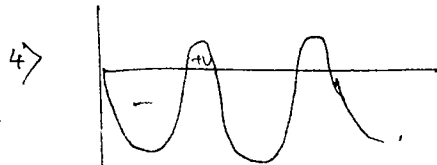- Power flows from source to load (Pavg +ve)
- No Regenerative braking only instantaneous power -ve
- net power supply from source to load.



- Regenerative braking
- Net power load to source
- $P_{avg} = -ve$

3) order of harmonics increases, Z_{in} also increases

• At electronics - $f = MHz$ (MHz) - impedance of the coil is very high hence draw a very less current (RF coil)

SIR - As the order of the harmonics increases, for RLC load, impedance increases

4) Harmonic Factor of nth harmonic (Hfn) :- It is the measure of individual harmonics present in o/p voltage w.r.t fundamental component

$$Hfn = \frac{V_n}{V_1} \quad \left\{ \begin{array}{l} \text{used to find out other harmonics in} \\ \text{fundamental (which we require)} \end{array} \right.$$

5) Total Harmonic distortion (T.H.D) :- It is the measure of resultant of all harmonics w.r.t fundamental harmonics.

$$THD = \frac{\sqrt{\sum_{n=2,3}^{\infty} V_n^2}}{V_1}$$

• How to evaluate infinite individual components after fundamental.

1) Calculate the fundamental.

$$\frac{\text{Total harmonics} = 1000V}{\text{Fundamental} = 80V} = \sqrt{1000^2 - 80^2}$$

Remaining harmonics other than fundamental

$$= \frac{\sqrt{V_0^2 - V_1^2}}{V_1} = \frac{\sqrt{\sum_{n=2,3}^{\infty} V_n^2}}{V_1} = THD$$

Distortion factor of nth harmonics

$$(D.F_n) = \frac{V_n}{n^2 V_1}$$

24/03/19


$$6 - 8 = M/c \text{ II}$$

$$6 \text{ pm} - 5.10 = PE \quad 30A$$


3φ BRIDGE INVERTER

IES Q

24/03/19

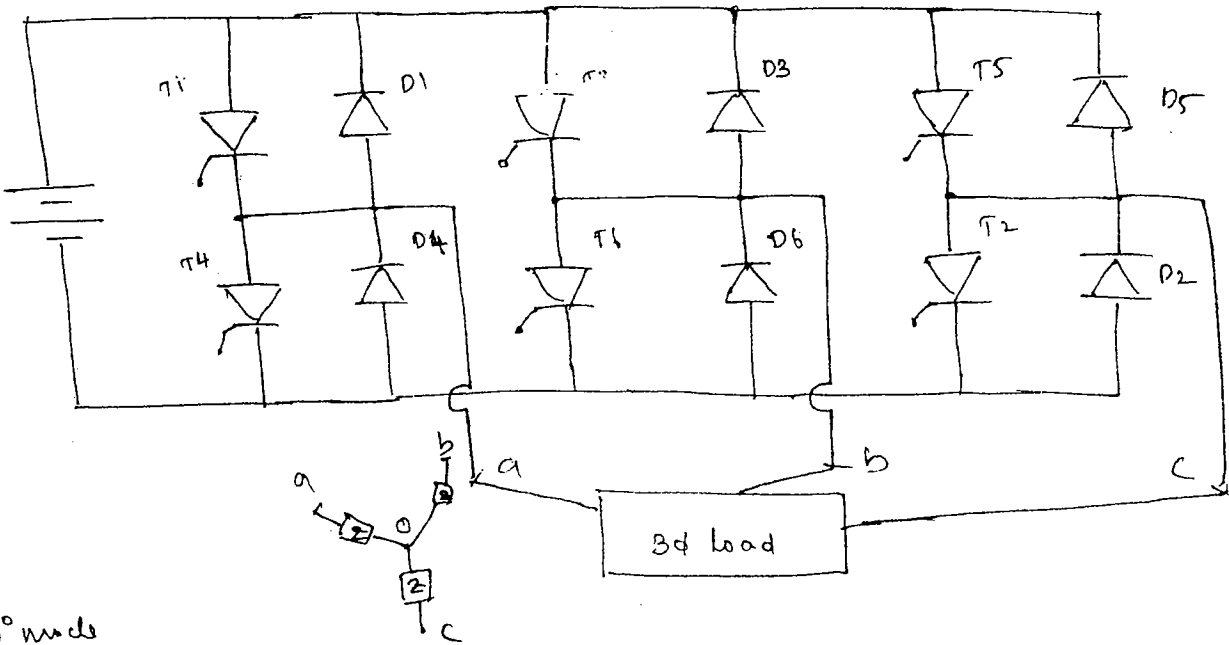

180° mode

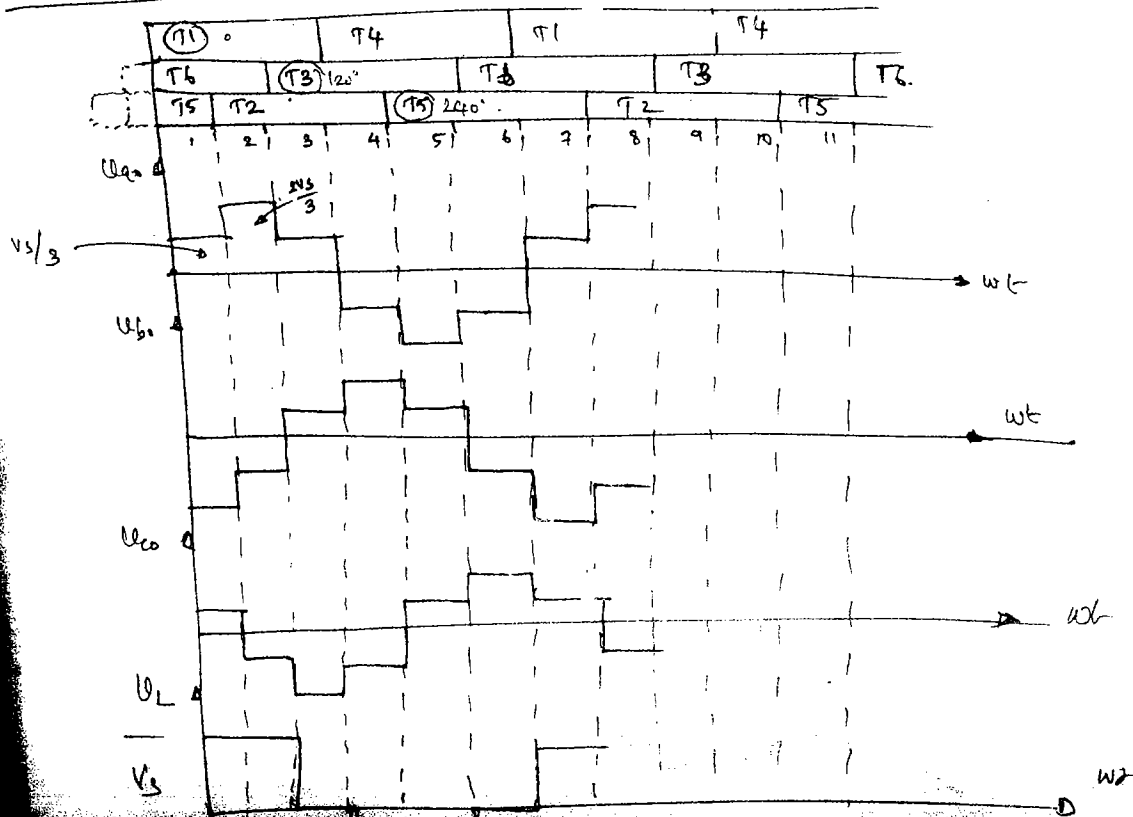

~ ~ ~ ~ ~ 4 3 0

▷ 120° displacement between a b c

⇒ conduction time 180°

• Numbering of the Thyristor and diode take care

▷ Vs supply, Set T1 as FB, Band on requirement bigger or given.

▷ Two modes of operation 180° mode and 120° mode

a) conduction time for each SCR conduct for 180°

each SCR = 180°

b) phase angle ϕ w two sequential thyristors from top group or bottom group is 120° (to obtain 120° phase diff)

sequential thyristors from top group or bottom group is 120°

is 120°

- 120° mode
- Each SCR conducts for 120°
- 180 - 120 = 60° time is given to turn OFF the SCR.

3) graph, each interval of 60°, 3 ϕ are shown as 3 lines.

I) ▷ T1 = triggered at $t=0$ - 180° conduction. ii) T4 - triggered - 180° - conduction

iii) T2 - triggered (180°) iv) T4 - triggered (180°) = 3.1 CYCLE

II) ▷ T3 = triggered at $t=120^\circ$ (180° conduction), T6, T3, T6 ...
0-120° = T3


III) ▷ T5 = triggered at $t=240^\circ$ (180° conduction) T2, T5, T2.
0-240° = T2

⇒ At any time 3 SCRs will be in conduction.

5) Consider a star connected load. (balanced load) with impedance Z.

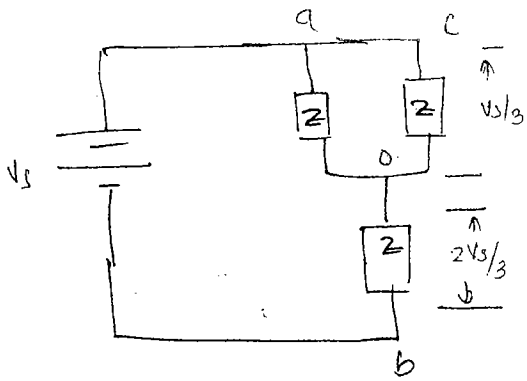a) T1 conducting → a → connected to +ve
 T6 → b → -ve
 T5 → c → +ve

Now draw the equivalent circuit for (0-60°)



(0-60°)


• calculate $V_{ph an}$

• $V_{a ph an} = V_s/3$ $V_{c ph an} = V_s/3$ } Plotted on the graph

• $V_{b ph an} = -2V_s/3$


$= (V_{c ph an} + V_{a ph an} + V_{b ph an})$ at any time
 $= 0$

60-120° (T1 T6 T2)
 a b c
 +ve -ve -ve

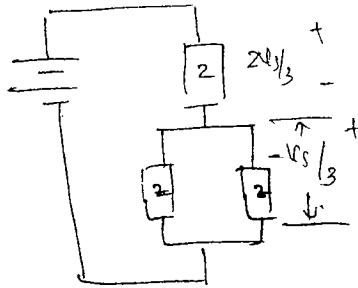

Plot the graph.

120-180° (T1 T3 T2)
 a b c
 +ve +ve -ve

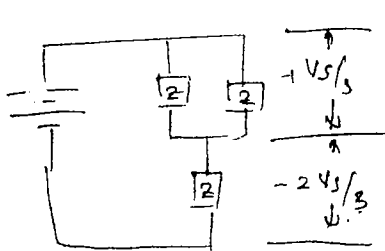

Plot the graph.

6) line voltage V_{ab}

$V_{ab} = V_{ao} - V_{bo}$

$= \left\{ \frac{V_s}{3} - \left(-\frac{2V_s}{3} \right) \right\} \left\{ \frac{2V_s}{3} - \frac{V_s}{3} - \frac{V_s}{3} \right\}$

7) shape of the waveform

i) shape of the phase voltage is 3 stepped waveform.

ii) shape of line voltage Quasi-Square waveform.

8) Disadvantage.

→ at 180°, T1 - turned OFF at zero time, T4 triggered. If T1 is not correctly switched off, T1 may go conduction.

→ 120° mod

→ In this mode of operation, there is 'no turn gap' between commutation of

outgoing SCR and conductors of incoming SCR. It may lead to short circuit of the supply due to simultaneous conduction of both the SCRs. Hence 120° mode is preferable.

9) Numbering Sequence


• $\omega t = 0 \Rightarrow T1$ only (T6, T5 already conducting)

• $\omega t = 60 \Rightarrow T2$, $\omega t = 120 \Rightarrow T3$, $\omega t = 180 \Rightarrow T4$, $\omega t = 240 \Rightarrow T5$

$\omega t = 300 \Rightarrow T6$)

• The thyristors have been numbered in the sequence, they are getting the bigger pulses.

10) 120° mode.

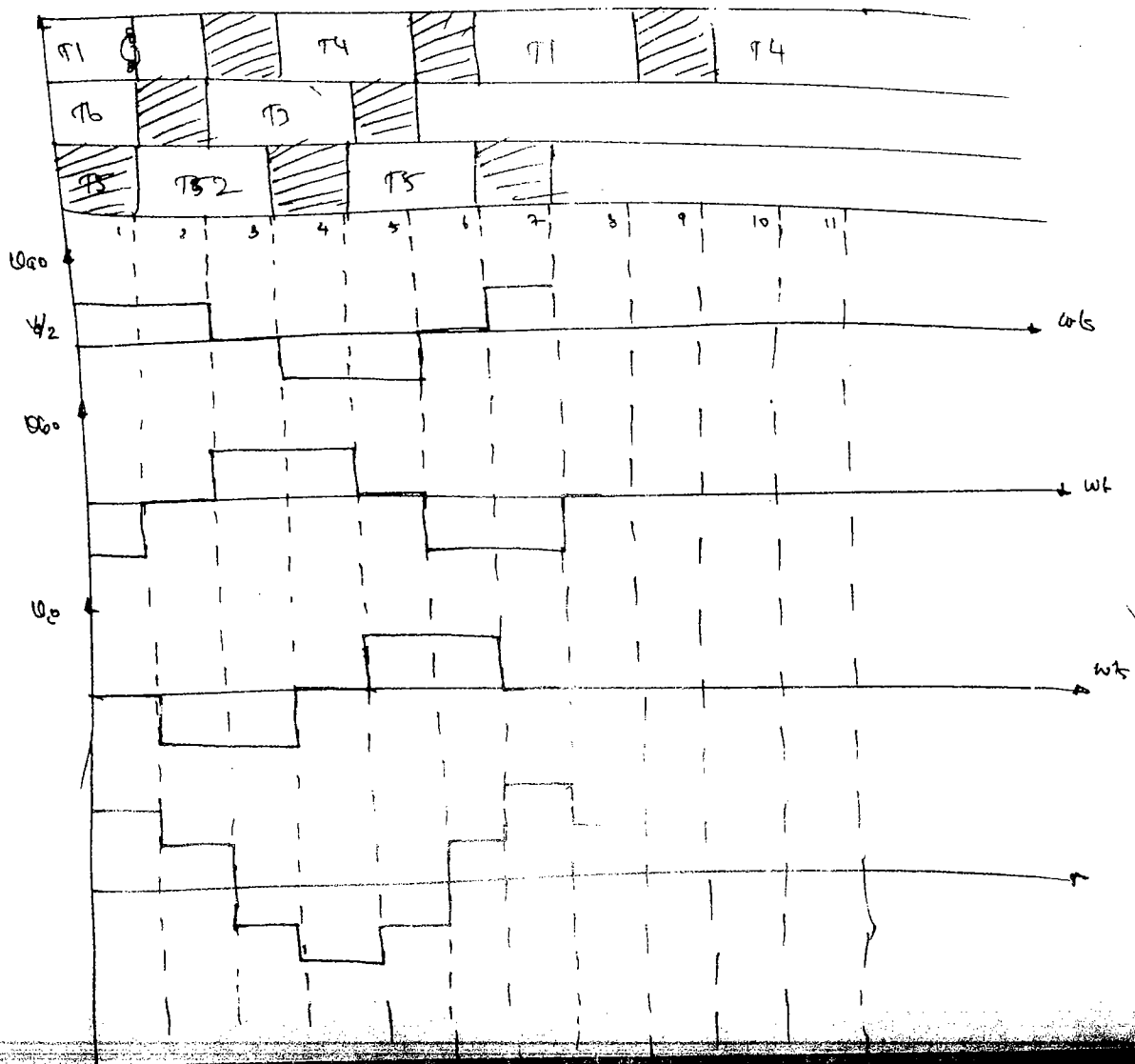

Conduction

1) Conduction time 120°

2) phase angle b/w two sequential SCR = 120°

• After 120° , the next 60° , in one phase there will not be any conductors.

• The time (60°) is given to the SCR to reach the off state clearly.

* conduction time of each SCR is equal to 120°

• Phase angle b/w two sequential SCR is 120° either from top group or from bottom group = 120°

2) we are starting to divide the time slot on upper line =====

RESOBJ


• At any time only 2 SCR's will be in conduction.

3) ~~Draw~~ Equivalent circuit.


• Consider Δ connected load with impedance Z .

phase voltage


i) $0-60^\circ$

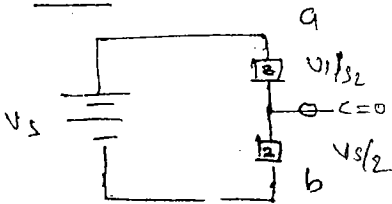

ii) $60-120^\circ$

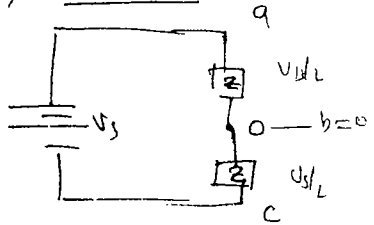

iii) $120-180^\circ$

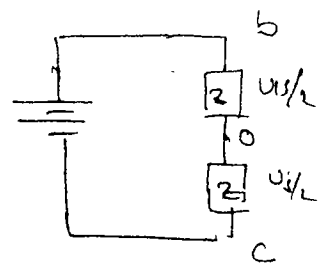

line voltage

$$V_{ab} = V_{ao} - V_{bo}$$

4) shape of ~~line~~ voltage

- shape of the phase voltage is Quasi square wave, ~~shape of line~~
- shape of the line voltage 3-step waveform

5) Disadvantage

• Any time 't' only two phases are supplied. If the load is unbalanced, the voltage occurs (unbalanced voltage) for other phase.

• At any time only 2 phases one of the phase is neither connected to +ve plate

• ~~At any time only 2 phases one of the phase is neither connected to +ve plate~~

II) Mathematical Expressions.

In both mode ~~the~~ phase is calculated means ~~the~~ can be calculated.

• In quasi square wave it is easy to do integration



I) 180° mode

$$V_{ab} = \sum_{n=1,3}^{\infty} \left\{ \frac{4V_s}{n\pi} \cos \frac{n\pi}{6} \right\} \sin n(\omega t + \pi/6)$$

$$V_{bc} = \sum_{n=1,3}^{\infty} \left\{ \frac{4V_s}{n\pi} \cos \frac{n\pi}{6} \right\} \sin n(\omega t - \pi/2)$$

$$V_{ca} = \sum_{n=1,3}^{\infty} \left\{ \frac{4V_s}{n\pi} \cos \frac{n\pi}{6} \right\} \sin n(\omega t - 5\pi/6)$$

Vector diagram

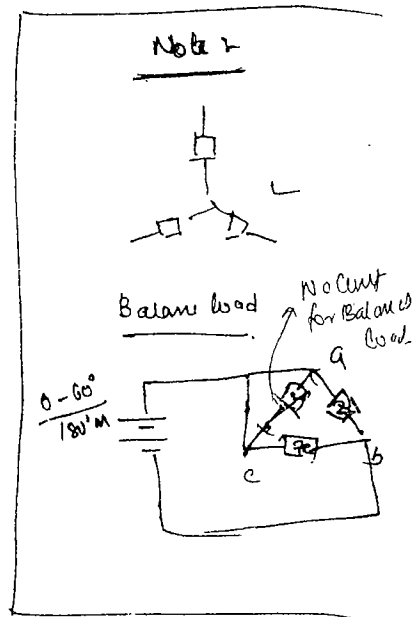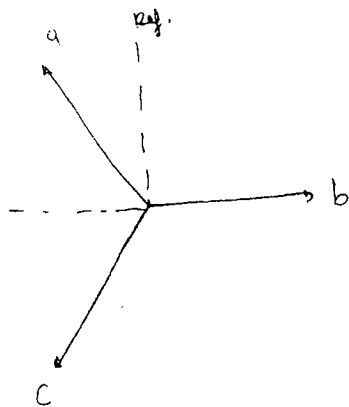

→ OBS → a ~~is multiple~~ for $n=3$, $\cos \frac{n\pi}{6} = 0$, hence all the line voltages are

due from triple n (3n) harmonics.

→ RMS value of line voltage (V_L) = $V_s \sqrt{\frac{120}{180}} = V_s \sqrt{\frac{2}{3}} = 0.8165 V_s$

$$V_{L_{rms}} = 0.8165 V_s$$

→ RMS value of phase voltage $\frac{V_L}{\sqrt{3}} = V_{ph} = \frac{0.8165}{\sqrt{3}} V_s$ $V_{ph} = 0.4714 V_s$

120° mode

$$U_{a0} = \sum_{n=1,3}^{\infty} \left\{ \frac{2U_s}{n\pi} \cos \frac{n\pi}{6} \right\} \sin n(\omega t + \pi/6)$$

$$U_{b0} = \sum_{n=1,3}^{\infty} \left\{ \frac{2U_s}{n\pi} \cos \frac{n\pi}{6} \right\} \sin n(\omega t - \pi/6)$$

$$U_{c0} = \sum_{n=1,3}^{\infty} \left\{ \frac{2U_s}{n\pi} \cos \frac{n\pi}{6} \right\} \sin n(\omega t + 5\pi/6)$$

→ For $n=3$, $\cos \frac{n\pi}{6} = 0$, hence the phase voltages are free from triplen harmonics (3rd harmonics).

→ RMS value of phase voltage (U_{ph}) = $\frac{U_s}{2} \sqrt{\frac{120}{180}}$

$$U_{ph} = 0.4082 U_s$$

→ RMS value of line voltage (U_L) = $U_{ph} \cdot \sqrt{3} = 0.4082 \times \sqrt{3} U_s$

$$U_L = 0.7071 U_s$$

cos: ***

→ For a given dc supply more o/p voltage can be obtained from single phase inverter even compared to 3 ϕ inverter.

CONTROLLING MAGNITUDE OF OUTPUT VOLTAGE (0 to V_{max})

I) VOLTAGE CONTROL IN 1 ϕ INVERTERS. IES @ 20 marks

Introduction: o/p voltage of the inverter can be controlled by any of the following methods.

1) External control of a/c o/p voltage. :- In this method an a/c

voltage controller will be employed at the o/p of the inverter. to make a c/h

variable magnitude a/c voltage.

2) External control of dc i/p voltage. :- A dc chopper will be

connected at the i/p of the inverter to make the dc to variable dc voltage.

3) output voltage of inverter - in this method Pulse width modulation (PWM)

techniques are employed to control the output voltage.

Repeat IGL

• In PWM method, width of the o/p pulse will be controlled to achieve the o/p voltage across it.

i) Single pulse modulation

• For every half cycle of unmodulated


across there is only one pulse is

there. as o/p wave form

• o/p voltage waveform is having

only one pulse per half cycle. hence known

as single pulse modulation.

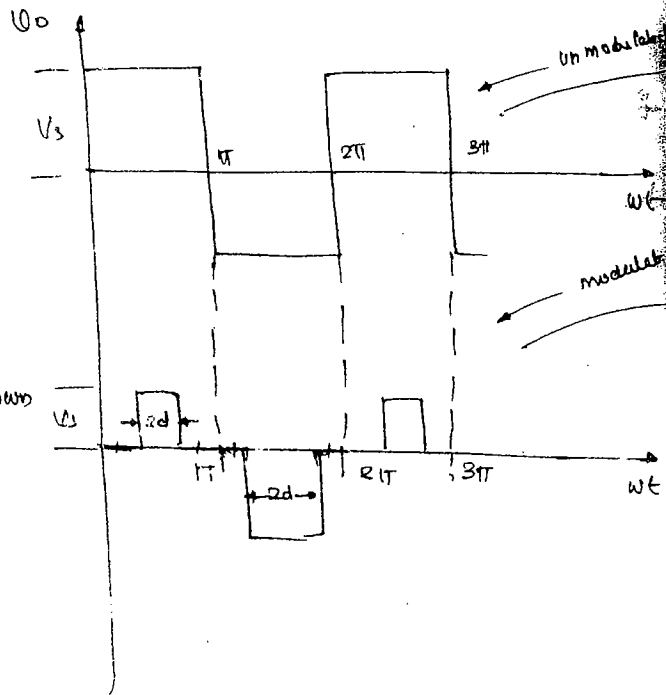

i) Vo rms $V_{or} = V_s \sqrt{\frac{2d}{\pi}}$ # # #

• conventional → derive the equation

$$V_{or} = \sqrt{\frac{1}{\pi} \int_{\pi/2-d}^{\pi/2+d} V_s^2 d(\omega t)}$$

• Symmetrically placed $\frac{2d}{\pi}$ to avoid harmonics.

• limits of integration

$$\begin{aligned} 2d + 2\pi &= \pi \\ 2\pi &= \pi - 2d \\ \pi &= \frac{\pi}{2} - d \\ \pi &= \frac{\pi}{2} + d \end{aligned}$$

$$V_{or} = \sqrt{\frac{V_s^2}{\pi} [\omega t]_{\pi/2-d}^{\pi/2+d}} =$$

$$V_{or} = V_s \sqrt{\frac{2d}{\pi}}$$

OBS

i) $|V_o|$ varied using by varying '2d' (or width)

ii) Minimum width of pulse = 0 a) Maximum width of pulse = 0

$$2d = 0$$

$$V_{or} = 0$$

$$0 \leq V_{or} \leq V_s$$


$$2d = \pi$$

$$V_{or} = V_s$$

2) To control the width of the pulse

i) delay the firing of the thyristor

ii) Advance the commutation

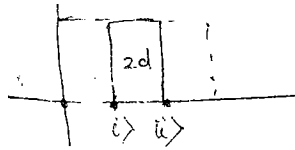

→ The width of the o/p pulse can be controlled by varying firing delay angle and advancement of commutation.

3) Fourier Analysis Expression

$$V_o = \sum_{n=1,3}^{\infty} \left\{ \frac{4V_s}{n\pi} \sin \frac{n\pi}{2} \sin nd \right\} \sin n\omega t$$

6.30 - 10.30 PM - IM-305

2-PM-5.30 - Study 304

6-5.30 - DC MC 304

$$V_{or_1} = \left\{ \frac{4V_s}{\pi} \sin \frac{\pi}{2} \cdot \sin d \right\} \frac{1}{\sqrt{2}}$$

4) Harmonic Elimination. (n^{th} from o/p waveform)

• For $n=3$, $V_{or(3)} \neq 0 = 0 \Rightarrow \sin 3d = 0$ $2d = \frac{2\pi}{3} = 120^\circ$

• generally $\sin nd = 0 \Rightarrow nd = \pi$ (take only π , not 0)
 $d = \pi/n$
 $d = 0$ non-sensory

$$2d = 2\pi/n$$

a) By properly selecting the width of the pulse one of the harmonics on the o/p waveform can be eliminated. It is possible only when amplitude is equal to zero for that value of 'n'.


eg:- 3rd Harmonics can be eliminated by making the width of the pulse $2d = \frac{2\pi}{3} = 120^\circ$

3) Disadvantage

• The o/p waveform will have the large amount of harmonics particularly at low o/p voltage levels. Hence multiple pulse modulation is more preferable.

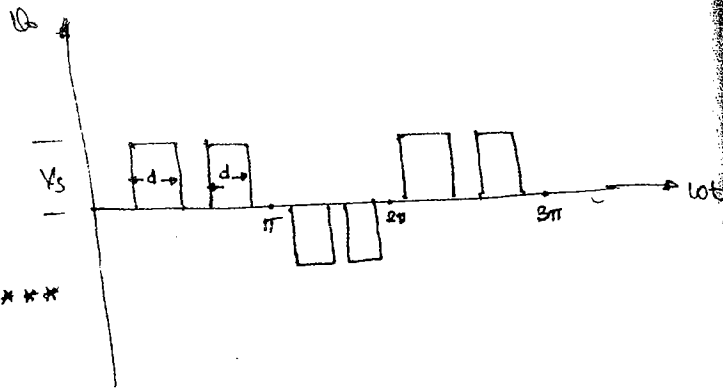ii) Simple multiple pulse modulation

• All the pulses are having equal height = V_s width, hence called simple multiple pulse modulation.



• $V_{or} = \text{rms value of o/p voltage}$

$$V_{or} = V_s \sqrt{\frac{d+d}{\pi}} = V_s \sqrt{\frac{2d}{\pi}}$$

• Realising two pulses by T_1, T_2 ON and OFF, here two times.

n pulses \Rightarrow n times ON and OFF of T_1, T_2 .

\Rightarrow Short on time, switching frequency high.

\Rightarrow Harmonics becomes less, high span decreases. So average and

Economically Number of pulses are selected.

Q. If the number of pulses per half cycle are made more than switching duty on

the thyristor increases, hence optimum number of pulses will be selected to reduce the harmonics - as well as minimizing the switching duty.


OBJ \Rightarrow The amplitudes of lower order harmonics will be decreased, at some of

the higher order harmonics will be increased significantly, These are easy to filter out. (Size of the filter required to eliminate higher order frequency

is less, $f = \frac{1}{2\pi\sqrt{LC}}$, $L \rightarrow$ small, $C \rightarrow$ small)
 f small.


IMPLEMENTATION OF SINGLE MULTIPLE PULSE

CONTROL CIRCUIT

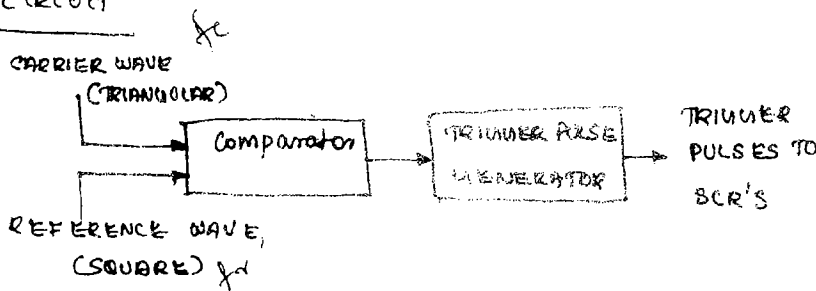

carrier wave f_c \triangleright Reference wave f_r .
 (for sinusoidal V_r)
 (It is square wave)

Comparator

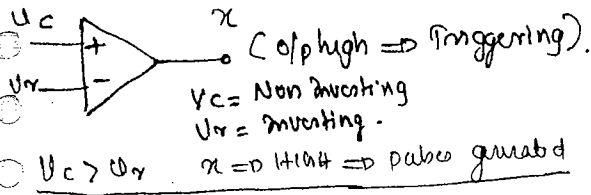

- Width of all pulses, because square is having a constant magnitude and time same - for $V_c > V_r$ is same every when

• Time period of carrier = $\frac{1}{f_c}$

• Time period of reference = $\frac{1}{2f_r}$

- carrier wave is a high frequency triangular wave form, Reference wave is a low frequency square wave form, is


• No. of pulses/half cycle $N = \frac{\text{Width of one half cycle of reference wave.}}{\text{Width of one cycle of carrier wave form.}}$

we $N = \frac{1/2T_r}{1/2T_c} = \frac{f_c}{2f_r}$ $N = \frac{f_c}{2f_r}$ IES 2010 Q



SINUSOIDAL PULSE WIDTH MODULATION. (Elaborate Study)

- \triangleright CARRIER WAVE \triangleright High frequency triangular wave form
- \triangleright REFERENCE WAVE \triangleright Low frequency sinusoidal waveform

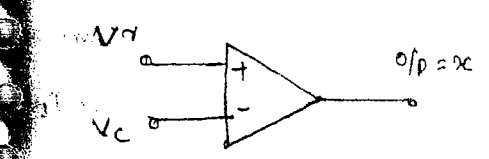Width of the o/p pulses \triangleright It varies as accordance with the magnitude of sinusoidal waveform.



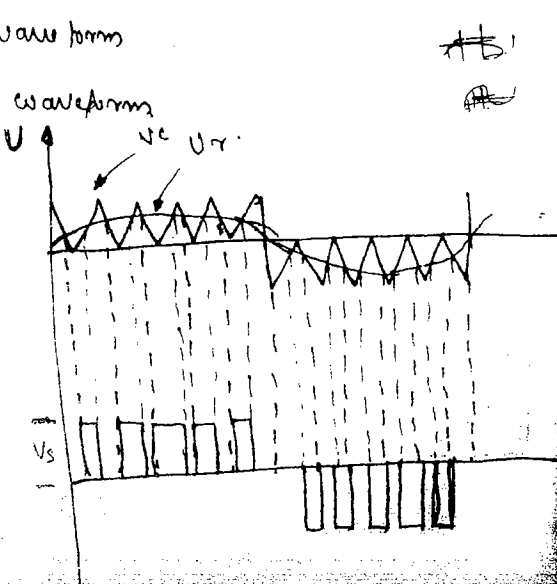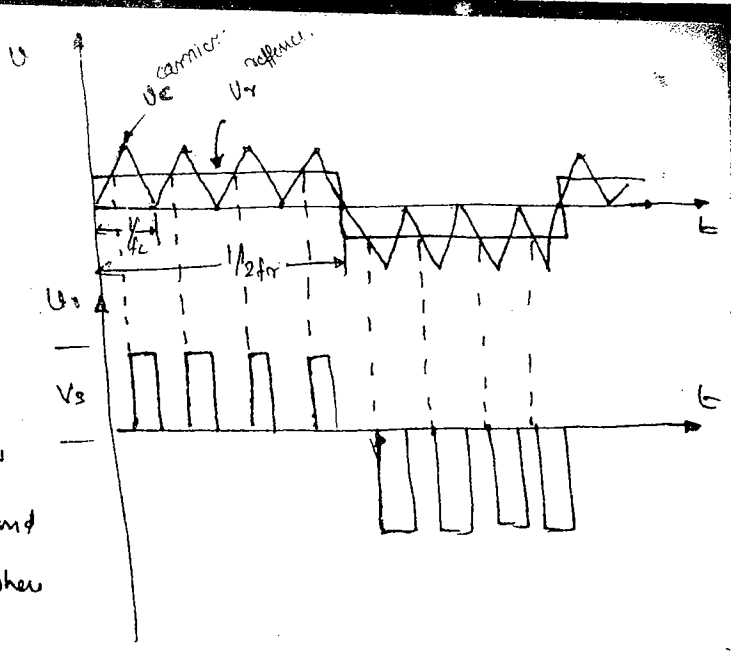- here note that $V_c =$ Inverting, $V_r =$ Non-Inverting
- $V_r > V_c \Rightarrow x$ HIGH \Rightarrow PULSE



• Time ($U_0 > U_c$) \propto width of the pulse

• Amplitude here is U_0 , largest de.

No of pulses / cycle = N (2 cases)

1) Peak of carrier coincident with zero of reference, then the number of pulse / half cycle

$$N = \frac{f_c}{2f_r} \approx \text{simple multiple modulation.}$$

2) If zero of carrier, coincident with zero of reference, then

$$N = \frac{f_c}{2f_r} - 1 \quad \left\{ \begin{array}{l} \text{1 pulse less} \end{array} \right\}$$

• So we choose the reference carrier from maximum and reference from zero.

Modulation Index $MI = \frac{U_0}{U_c}$ • physically how much carrier is available as the reference wave.

$MI < 1 \Rightarrow |U_0| < |U_c|$

→ • Do show here: the comparison of which

• Largest harmonic amplitude

in the o/p waveform are associated of the order

$(2N \pm 1)$ $N \Rightarrow$ No. of pulses / half cycle.

are called power waveforms which orders enables the bigger pulses to produce the biggest to the thyristor T_1 and T_2 .

• By increasing the value of N the order of the harmonic frequency will increase, which is easy to filter.

→ • U_0 , width is giving a zero for T_1 and T_2 which time the thyristor is ON.

→ • Using U_0 , power waveforms, we can generate power waveforms for the T_1 and T_2 by analysing the time period / width of U_0 .

SERIES INDUCTOR

3) For any combination of load, total load acts as RLC.

1) T_1 inductance, conducting.

2) Supply de given the reactance $X_L = \omega L$ (in order equation)

- we have induct by RLC and X_L is blocked by T_1 .

Then after some time T_2 begins conducting

$$X_{L2} > X_{L1} \text{ (decrease than } X_{L1} \text{ time)}$$

- we have cycle in inductor. This continued.

3) commutation: Load commutation (load inducts are impossible formula)

the circuit is given

SE \rightarrow series inductor employs load commutation. The circuit commutation is given

due to the nature of load circuit, so it is a load commutation.

OBS:

$$\omega L > X_C = 0 \quad \omega L - \frac{1}{\omega C} = \frac{2\pi f L}{\omega} - \frac{1}{2\pi f C}$$

$f = 0$ old frequency

$f = 0 \Rightarrow$ RINGING FREQUENCY

$$X_{L2} = \frac{1}{2} \left[\frac{1}{f} - \frac{1}{f_2} \right]$$


$\frac{1}{f_2} = X_C = X_L$ = find on RLC parameter depend (Natural conduction field)

$f = f_2 =$ depends on X_{L2} (By convention)

$\omega < \omega_2$ } old frequency \rightarrow Ringing frequency


OBS:

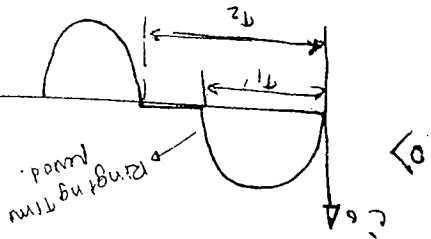RINGING FREQUENCY: Natural frequency of RLC circuit.



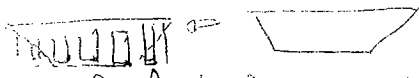11) TRIANGLE PULSE WIDTH MODULATION


- width of the U_0 is required to know, Δ carrier wave
 \rightarrow carrier wave is high frequency triangular
 \rightarrow regular wave is low frequency triangular
 \rightarrow width of the output pulse varies in accordance to the magnitude of triangular wave form



\rightarrow triangular pulse width modulators

\rightarrow carrier wave is high frequency triangular

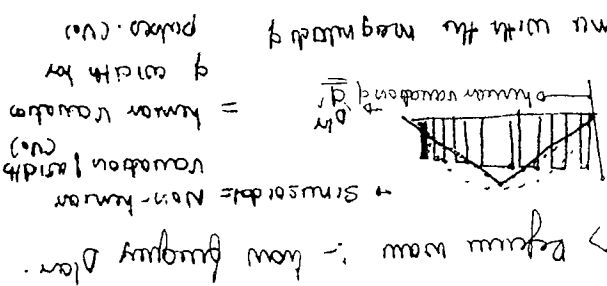\rightarrow width of the U_0 pulse varies in accordance with the magnitude of pulses. (V0)



Regular wave is low frequency triangular

SELECTION OF MODULATION TECHNIQUE

\rightarrow usually depends upon type of load and harmonics effect on load.
 \rightarrow Inductor motor :- Estimate 9th harmonic :- take best method.
 \rightarrow Heater :- simple heater do not worry about harmonics :- take simple method.



\rightarrow In general the best commutation is sinusoidal

\rightarrow The type of modulation technique to be employed depends on the type of load and its capability to accommodate the harmonics.

Steps to follow

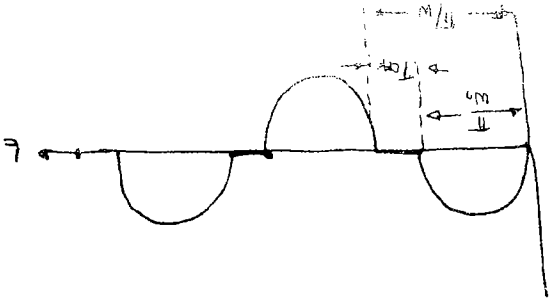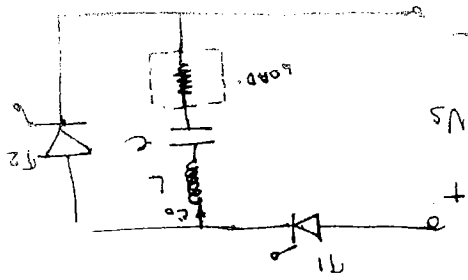- 1) Load
- 2) Load \rightarrow formula given
- 3) Load \rightarrow then
- 4) Load \rightarrow then
- 5) Load \rightarrow then

SERIES INVERTER. (At 892 inverted in scale)



CURRENT SOURCE INVERTER

Current source

Symbol:



Natural = voltage source

Current source we are made. A constant


current flowing through the load with

out any change w.r.t load.

Realising Current source

voltage source and a HIGH VALUE OF


INDUCTOR IN SERIES.

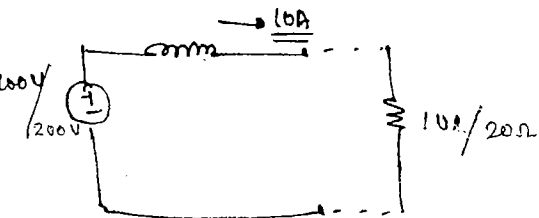

Assum: S.S

Maximizing 10Ω to 20Ω


10A tends to decrease

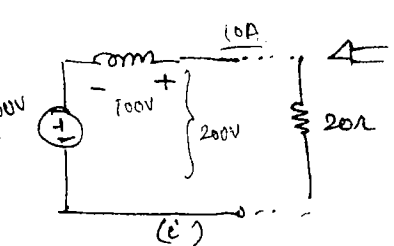



$$\begin{aligned} \text{slope} &= -ve \\ \frac{di}{dt} &= -ve \\ L \frac{di}{dt} &= -ve \text{ voltage} \end{aligned}$$

Reducing 10Ω to 5Ω

10A tends to increase

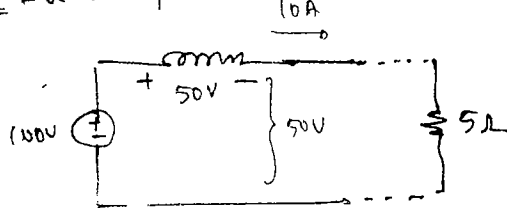

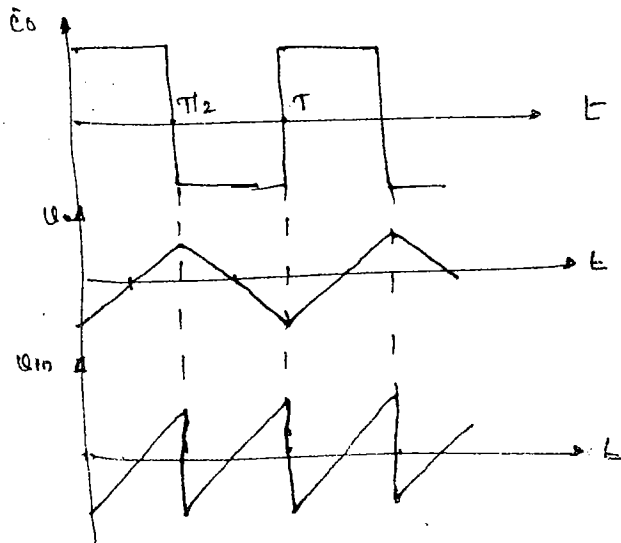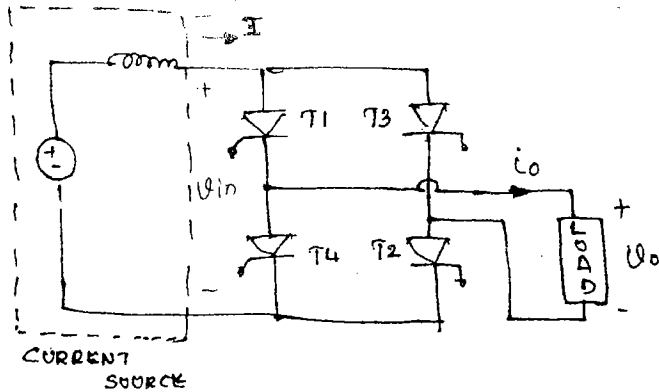
$$\text{slope} = +ve, \frac{di}{dt} = +ve, L \frac{di}{dt} = +ve \text{ voltage}$$



I constant, our reference is current, frequency expected = 50Hz

$$T = 20ms$$

$$T/2 = 10ms$$

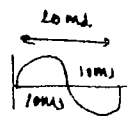

i) T1 T2 ON, io flows, + Uo = +ve

ii) T1 T2 T4 ON, T3 T4 triggered OFF, io opposes, - Uo = -ve


Uo is defined by the load connected.

2 load = same sign


u) was given we. No of inductor it should not be used.

✓ 5) pure capacitor ~~power~~ ~~performance~~ ~~not~~ ~~expected~~.

calculations

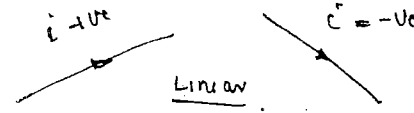→ $i = \overset{\text{constant}}{C} \frac{dV}{dt} \Rightarrow$ linear variation 

→ $V_o = V_c = \frac{1}{C} \int i_c dt = \frac{tC - I}{C}$

→ slope $\cdot \frac{dV_c}{dt} = \frac{I}{C}$  } • Voltage

512 • current source inverter feeds a pure capacitor load, when the following points are relevant

1) shape of o/p current = Square wave.


2) shape of o/p voltage = triangular wave.

3) slope of o/p voltage = $\frac{I}{C}$.


4) peak value of o/p voltage = $V_{peak} = \frac{I}{C} \cdot \frac{T}{4}$

5) peak-peak voltage = $V_{pp} = \frac{I_0}{C} \cdot \frac{T}{2}$.

Variation of input voltage V_i to keep I constant

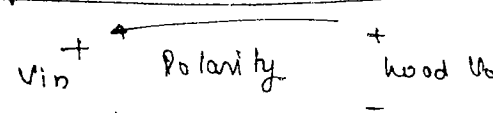1) T_1, T_2 - conducting. 

$\Rightarrow \underline{V_{in} = V_o}$ - reference.

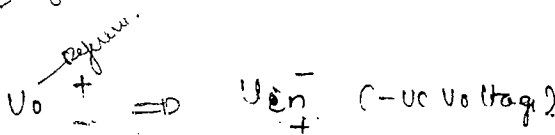
2) T_3, T_4 - conducting, we need V_o  $\Rightarrow \underline{V_{in}^-}$ (-ve voltage)

$\Rightarrow \underline{V_{in} = -V_o}$

$T_{in} = T/2$

$f_{in} = 2f_0$

• V_{in} V_{imp}

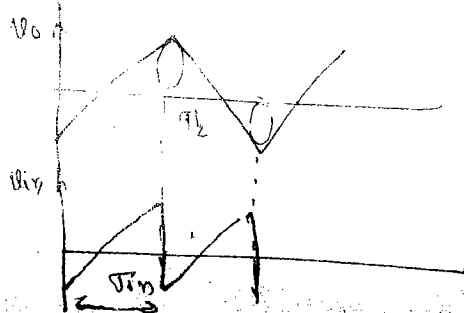

To produce a o/p at 50Hz frequency, the r.p.s voltage to the inverter is required to be varied at 100Hz as because, whenever T₁, T₂ conducting V_{in} = V_o, whenever T₃, T₄ are conducting V_{in} = -V_o.

Q1) Page 06, chapter 4

$$\omega L = X_L = 8 \Omega, \frac{1}{\omega C} = X_C = 9 \Omega$$

$$a) i_o = \sum_{n=1,3} \left\{ \frac{4V_s}{n\pi Z_n} \right\} \sin(n\omega t - \phi_n)$$

$$I_{o1} = \frac{4V_s}{\pi Z_1} \times \frac{1}{\sqrt{2}} \quad \text{Fundamental.}$$

$$Z_1 = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z_1 = \sqrt{(1.2)^2 + (8-9)^2} = 1.56 \Omega$$

$$I_{o1} = \frac{4V_s}{\pi Z_1} \times \frac{1}{\sqrt{2}} = \frac{4 \times 48}{\pi \times 1.56} \times \frac{1}{\sqrt{2}}$$

$$= 132.56 \text{ A}$$

$$b) P_1 = I_{o1}^2 R$$

$$= (132.56)^2 \times 1.2$$

$$= 21.1 \text{ kW}$$

Forced commutation is required since, $X_L > X_C$

Forced commutation is required

$$a) V_{o1} = \frac{2V_s}{\pi} \cdot \frac{1}{\sqrt{2}} \quad \text{Fundamental.}$$

$$= \frac{2 \times 48}{\pi \sqrt{2}} = 21.6 \text{ V}$$

$$b) \text{ o/p power} = P = \frac{V_{o1}^2}{R} = \frac{V_s^2}{R} \quad \text{Fundamental.}$$

$$\text{Fundamental power} = \frac{(48/2)^2}{1.2} = 240 \text{ W}$$

Q3) Half Bridge Inverter.

$$R = 10 \Omega, V_s = 400 \text{ V}, V_{or} = 200 \text{ V}$$

Fundamental frequency.

$$V_{o1} = \frac{2V_s}{\pi \sqrt{2}} = \frac{2 \times 400}{\pi \sqrt{2}} = 180 \text{ V}$$

$$I_{o1} = \frac{V_{o1}}{R} = \frac{180}{10} = 18 \text{ A}$$

Q4) Full Bridge Inverter, load = R=3, L=, C. $X_C > X_L$

periodicity = 1 cycle period = 0.2ms, $t_d = 12 \mu\text{s}$

f.s = 2

load commutation $X_C > X_L$.

$$\text{Circuit TOFF} = 2 \times \text{diode turnoff} = 2 \times 12 \mu\text{s} = 24 \mu\text{s}$$

Factor of safety.

$$\phi = \text{p.f. angle}$$

$$= \theta = \tan^{-1} \frac{X_C - X_L}{R}$$

$$\tan \phi = \frac{X_C - X_L}{R} \quad \text{given}$$

$\phi?$

Antiparallel diodes are in conduction.

$$\phi = \omega t_c$$

For reliable conduction

during the period antiparallel diodes are conducting and applying the reverse voltage (ωt_c) = p.f. angle of the current. $\therefore \phi = \omega t_c$

$$\phi = \omega t_c \Rightarrow d = \frac{2\pi f_c}{T} = \frac{2\pi \times 5000 \times 24 \times 10^{-6}}{0.2 \text{ ms}} = 0.95 \text{ rad}$$


$$= 0.95 \text{ rad}$$

$$= 43.2^\circ$$

$$\tan 43.2^\circ = \frac{X_C - X_L}{R} = 0 \quad X_C = 14.8 \Omega = \frac{1}{\omega C}$$

$$\frac{1}{2\pi \times 5000 \times C} = 14.8 \Rightarrow C = 2.15 \mu\text{F}$$
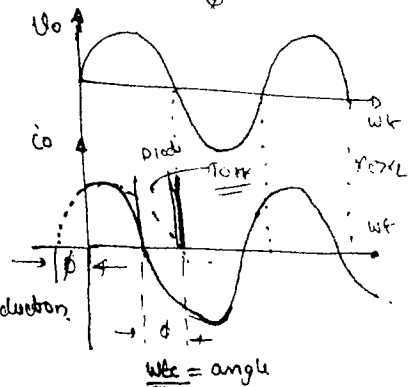
$$C < 2.15 \mu\text{F} \quad \text{Reliable duty 9}$$



to select a capacitance, which is LESS THAN

THE CRITICAL VALUE.

5) $D = 152/\text{pha}, V_s = 420\text{V}, \text{ s.f. BI } \left\langle \begin{matrix} 180^\circ \\ 120^\circ \end{matrix} \right\rangle$

180° mode

c) $V_{ph} = 0.4714 V_s$
 $= 0.4714 \times 420$
 $= 197.9\text{V}$
 $I_{ph} = \frac{V_{ph}}{R} = \frac{197.9\text{V}}{15}$
 $= 13.2\text{A} = I_{Lm}$

e) $I_{T\text{rms}} = I_p \sqrt{\frac{180}{360}}$
 $= 13.2 \sqrt{\frac{180}{360}}$
 $= 9.33\text{A}$

w) R-load

Power = $V_{ph} I_{ph} \times 3$
 $= 3 \times 197.9 \times 13.2$
 $= 7.82\text{kW}$

120° mode

e) $V_{ph} = 0.4082 V_s$
 $= 0.4082 \times 420$
 $= 171.4\text{V}$
 $I_{ph} = \frac{V_{ph}}{R} = \frac{171.4}{15} = 11.43\text{A}$

ii) $I_{T\text{rms}} = 11.43 \sqrt{\frac{120}{360}}$
 $= 7.57\text{A}$

iii) R-load

Power = $V_{ph} I_{ph} \times 3$
 $= 3 \times 171.4 \times 11.43$
 $= 5.8\text{kW}$

6) 1st FB. V_{o1} - single pulse modulation.
 $- 110\text{V}$

$2d?$ $V_{o1}?$ $V_s = 220\text{V}$

$V_{o1} = \sum_{n=1,3,5} \left\{ \frac{4V_s}{\pi} \cdot \sin \frac{n\pi}{2} \cdot \sin nd \right\} \sin n\omega t$

$V_{o1\text{rms}} = \frac{\left\{ \frac{4V_s}{\pi} \sin \frac{\pi}{2} \cdot \sin d \right\} \text{max value}}{\sqrt{2}}$

$110 = \frac{4 \times 220}{\pi \sqrt{2}} \cdot \sin d$

$d = 33.73^\circ$

pulse width $2d = 67.46^\circ$

$V_{o2} = \text{Total o/p } V_{o1\text{rms}} = V_s \sqrt{\frac{2d}{\pi}}$
 $= 220 \sqrt{\frac{67.46}{180}} = 134.8\text{V}$

$\frac{1}{q} = \frac{1}{200} = 5\text{msec}$


08) $\alpha = 120^\circ$

$V_{o1} = \frac{4V_s}{\pi} \sin \frac{\pi}{2} \sin d \times \frac{1}{\sqrt{2}}$
 $= \frac{4 \times (V_s = 220\text{V})}{\pi} \left(1 \times \sin \frac{120}{2} \right) \times \frac{1}{\sqrt{2}}$
 $= 0.78\text{V}$

09) Eliminate 5th harmonic

$2d = \frac{2\pi}{m} \Rightarrow 2d = \frac{2 \times 180}{5} = 72^\circ$

10)

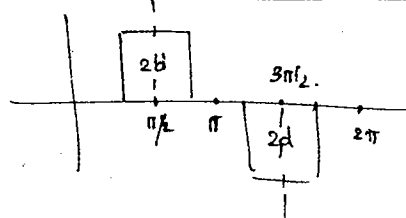

$2d = 144^\circ \Rightarrow 5^{\text{th}} = 0$

$V_{o3} = \frac{4V_s}{3\pi} \times \sin \frac{3\pi}{2} \times \sin \frac{3\pi}{2} \times \sin 3d \times \frac{1}{\sqrt{2}}$
 $V_{o1\text{max}} = \frac{4V_s}{\pi} \times \sin \frac{\pi}{2} \cdot \sin \frac{\pi}{2} \cdot \sin 72^\circ \cdot \frac{1}{\sqrt{2}}$
 $= \frac{1}{3} \times \frac{1}{1} \times \frac{\sin 3 \times 72}{\sin 72} \times 100\%$
 $= 20.6\% \approx 19.6\% \text{ am list}$

Now consider $V_{o1\text{max}}$

$V_{o1\text{max}} = \text{Am same as above } \times$

$V_{o3} = \frac{(V_{o1\text{rms}}) / \sqrt{2}}{\text{max value}} = \frac{20.6}{\sqrt{2}} = 14.4 \times$
 $V_{o1\text{max}}$

$V_{o1\text{max}}$ is at 90° (amplitude of $\sin 72^\circ$, $\sin 90^\circ$)


$V_{o3} = \frac{4V_s}{3\pi} \times \sin \frac{3\pi}{2} \times \sin \frac{3\pi}{2} \cdot \frac{1}{\sqrt{2}}$
 $V_{o1\text{max}} = \frac{4V_s}{\pi} \times \sin \frac{\pi}{2} \cdot \sin \frac{\pi}{2} \cdot \frac{1}{\sqrt{2}}$
 $= 19.6$

$$3) \frac{V_s \times I}{Z} = I_{peak} = \underline{\underline{10A}}$$

4) current sequential inverter.

$$f_{frequency} = \frac{1}{\text{minimum time period}}$$

Time period = 0 +ve half + -ve half.

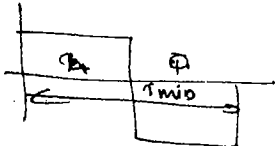

Paths $T_1, 920N$ — $T_1, 0.14\mu s, 100\mu s, 10$
 $0.2\mu s, 0.1\mu s, 92$

$$Z = R_{eq} = 10 \times 0.05 \mu s = \underline{\underline{0.5 \mu s}}$$


Steady state response 5Z, error 0.1x.

4Z error 0.2x.

Consider 5Z

$$\Rightarrow 5 \times 0.5 = 2.5 \mu s = \frac{1}{2} \text{ cycle}$$

$$\text{Time period} = 5 \mu s$$

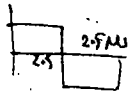

$$f = \frac{1}{5 \mu s} = 200 \text{ kHz}$$

Ans Not in options

Consider 4Z

$$\Rightarrow 4 \times 0.5 = 2.0 \mu s = \frac{1}{2} \text{ cycle}$$

$$\text{Time period} = 4 \mu s$$

$$f = \frac{1}{4 \mu s} = 250 \text{ kHz}$$

Ans or given in the options

$$3) V_{or} = V_s \sqrt{\frac{2d}{\pi}} = 220 \sqrt{\frac{2 \times 0.4}{\pi}} = \underline{\underline{179.65V}}$$

$$4) \frac{V_{os}}{V_{oi}} = \frac{4V_s}{5V} \cdot \frac{1}{\sqrt{2}} \times 100 = \underline{\underline{20\%}}$$

5) c) 16) $V_s = 480V, L = 2.4$


$$V_{oi} = \frac{4V_s}{\pi \sqrt{2}} = \frac{4 \times 480}{\pi \sqrt{2}} = 91$$

Use design load value

main circuit and left to commutating circuit

L & C commutating elements. modification is done in the commutation circuit

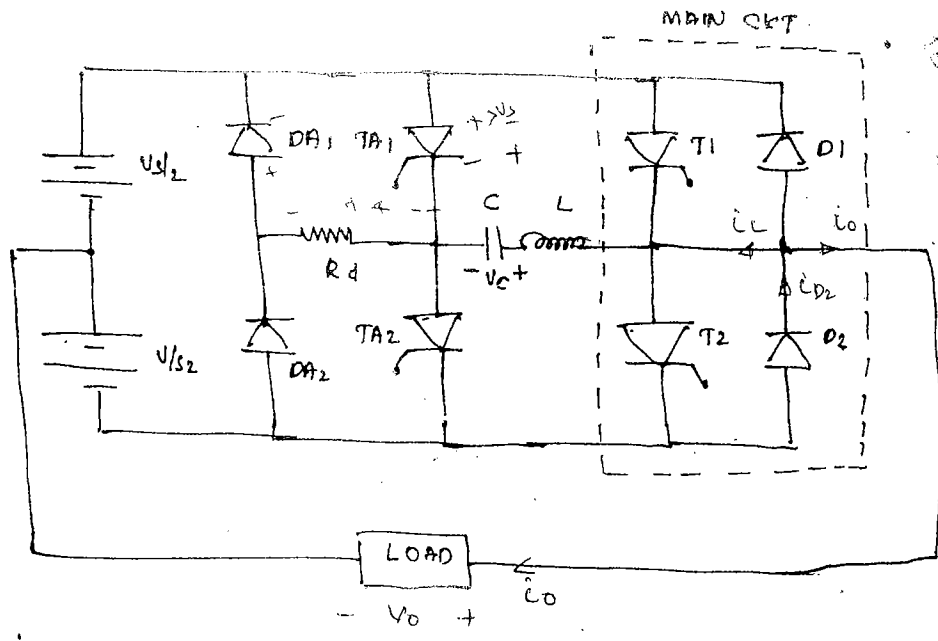We assumed that I_o constant. $+I_o, -I_o$



+ve half cycle = $+I_o$
-ve half cycle = $-I_o$

Voltage across the capacitor = $V_c = V_s$ (initially)

T_1 - Triggering ON $V_c = +V_s$
 T_2 - Triggering ON $V_c = -V_s$
must for continuous conduction. Then gives

Failure for turn OFF.

1) $t=0$, T_1 conducting
 $V_o = +$
 $V_s/2$

$V_c = +V_s$ (we set).


Conduction time = As per our requirement.

half cycle is completed, to go to next half cycle, T_1 should OFF T_2 should ON.


2) T_1 - triggered ON, $V_c = +V_s$, $I_c = +I_o = I_o$ ($T_1 = I_o$ both same and opposite)

Reverse voltage, D_1 conducts. (when T_1 is OFF). This gives reverse voltage for T_2


Turn OFF completed

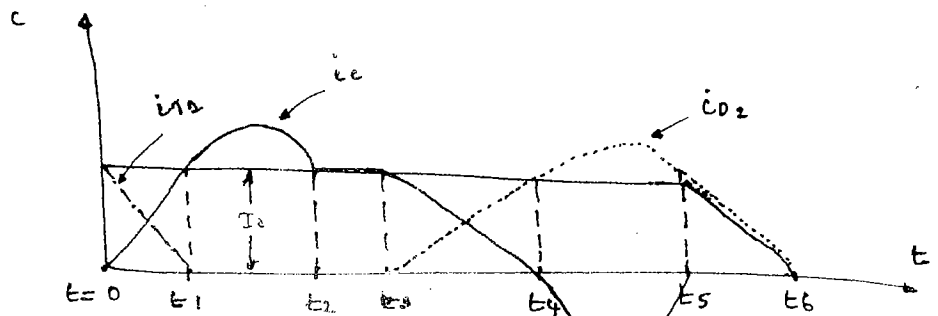


$t=0$	t_1	t_2	t_3	t_4	t_5	t_6
TA1 ON	T1 OFF D1 ON	D1 OFF	D2 ON	TA1 OFF D1 ON	TA1 OFF D1 OFF	D2 OFF T2 ON

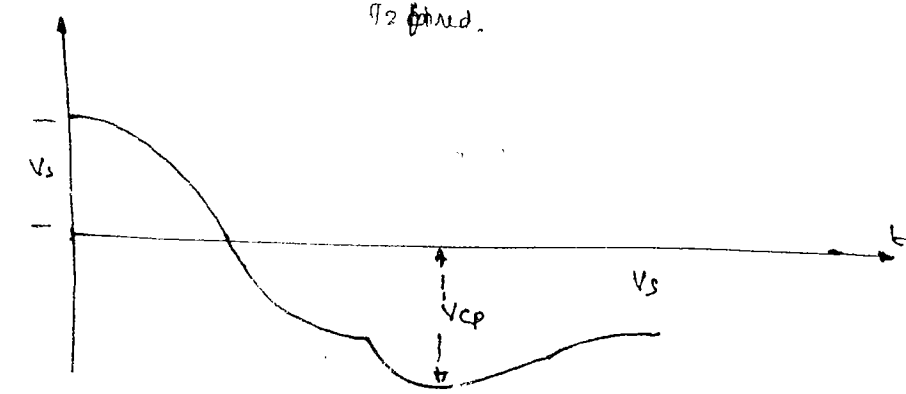


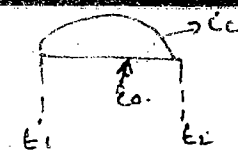• Designed $i_c > i_o$ to pass the extra current through $D1$



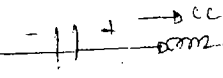• $T1$ OFF, i_c  $V_s \downarrow$ at t_2 $V_c = 0$

3) $t_2 \rightarrow t_3 \Rightarrow V_c < V_s$ (by $T1$ it charged), to maintain i_o constant, whenever

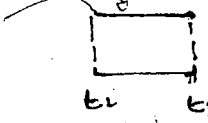$i_c = i_o$ (shown)  $\Rightarrow V_c > V_s$ with.

4) After $\pi \sqrt{L/C}$ second $T2$ is triggered on, i_c passes through inductor and gradually decays $i_c = 0$, $i_{T2} \uparrow \uparrow \approx i_o \rightarrow i_{T2} = i_o$. $t_3 \rightarrow t_4$, prolonged charging

$V_c > V_s$ Extra energy transferred to C & inductor.

5) t_4 := until then i_c tends to go on in direction, path available is R_d and

DA1 $\frac{V_{Rd} + V_{DA1}}{i_c} = 0$ Reverse voltage for $DA1$, $DA1$ ensured for OFF.
 $\frac{i_c + i_o}{i_c} =$ discharging at reactor $-V_s$.

6) t_5 , $V_c = -V_s$, $DA1$ OFF

7) t_6 - $DA2$ OFF, $T2$ ON Not $DA2$ triggered and cycle repeats $T2$ again OFF

Modification of Bridge

1) Ensuring the Turn OFF of $T1$ and $T2$.

Sol:

1) Half Bridge Inverter operation is based on current commutation, modification of the circuit is useful to ensure the turn OFF of auxiliary thyristors by applying the reverse voltage

2) Anti parallel diode $D1$ on output to apply the reverse voltage across $T1$ after its current comes to zero.

CALCULATIONS

1) Capacitance formula

$$C = 0.892 \frac{t_c \times I_{om}}{V_{mm}}$$

2) Inductance

$$L = 0.9164 \frac{t_c \times V_{mm}}{I_{om}}$$

3) Damping Resistance

$$R_d = 2 \sqrt{\frac{L}{C}}$$


where, t_c = circuit turn OFF time.
 V_{mm} = minimum supply voltage.
 I_{om} = maximum output current.

11.2 AC Voltage Controller

Def: It is a static power electronics circuit, which converts AC to variable AC with variation in the magnitude of the voltage.

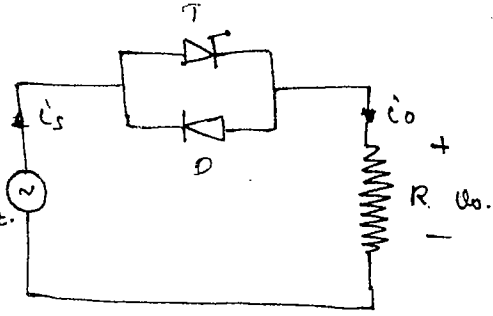1) 1 ϕ Half wave AC Voltage Controller.


- AC supply
- T & D connected in antiparallel
- $i_s = i_o$
- Considering R load



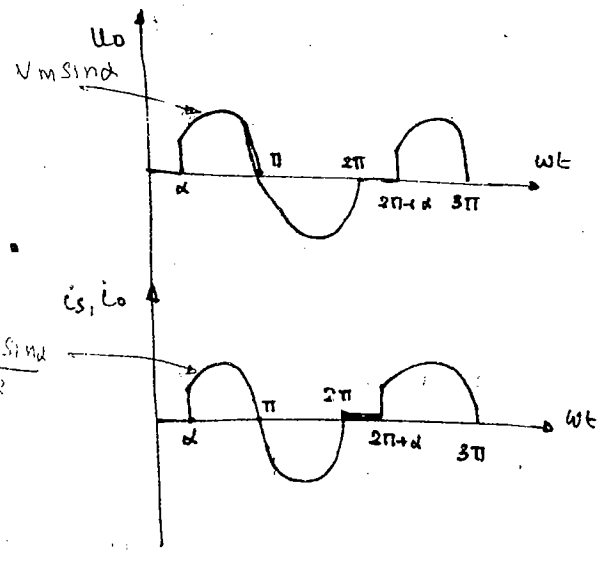1) +ve half cycle T-F. voltage α triggered. as if
D-R. voltage

a closed switch. up to π (α to $\pi = V_m \sin \alpha$)
(0 to $\alpha = 0$ V)

$$i_s, i_o = \frac{V_m \sin \alpha}{R} \begin{cases} 0 \text{ to } \alpha = 0 \text{ A} \\ \alpha \text{ to } \pi = \frac{V_m \sin \alpha}{R} \end{cases}$$



2) $\pi - 2\pi$:- D = F.B. \rightarrow starts conducting at π .

$$\begin{cases} V_o = -V_c \text{ same as } V_s \\ i_o = -i_c \text{ same as } i_s \end{cases} \text{ up to } 2\pi$$

3) To maintain symmetry after a delay ' α ' from 2π T again triggered on.

(SLE) - A/c voltage controller employs two (or) Natural commutation.

• Output of A/C

1) RMS value

V_o period = 2π ,

$$V_{or} = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{2\pi} V_m^2 \sin^2 \omega t \, d(\omega t)}$$

$$V_{or}^2 = \frac{V_m^2}{2\pi} \int_{\alpha}^{2\pi} \frac{1 - \cos 2\omega t}{2} \, d(\omega t)$$

$$V_{or} = \frac{V_m}{2\sqrt{\pi}} \left[2\pi - \alpha + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

$$= \frac{V_m^2}{4\pi} \left[\omega t - \frac{1}{2} \sin 2\omega t \right]_{\alpha}^{2\pi}$$

$$= \frac{V_m^2}{4\pi} \left[2\pi - \alpha + \frac{1}{2} \sin 2\alpha \right]$$

2) Rms current

$$I_{or} = I_{sv} = \frac{V_{or}}{R}$$

3) Input supply pf = $\frac{\text{Power delivered to load}}{\text{Source VA}}$

$$= \frac{V_{or}^2/R}{V_s \cdot I_{sv}} = \frac{V_{or}^2/R}{V_s \cdot V_{or}/R}$$

Disadvantage

$$PF = \frac{V_{or}}{V_s}$$

1) o/p wave forms are Not-symmetrical, so they consist of all types of harmonics

2) o/p voltage can be controlled only during +ve half cycle.

2) 1ϕ Full wave AC voltage controller

• o/p A/c.

• A TRIAC, can be employed on the place of antiparallel connection of ser's to realise full wave ac voltage control.

• Consider R load

1) +ve half cycle, T1 - Forward at α - triggered $\Rightarrow V_o = V_m \sin \omega t$ ($\alpha - \pi$)

($\pi - \alpha$) - T1 conducts.

2) -ve half cycle, T2 - Forward, T1 - Reverse } To maintain symmetry

T2 triggered at $\pi + \alpha$ -ve conduction.

consp. ($\pi + \alpha - 2\pi$) T2 conducts

same cycle repeats.

3) $\frac{V_{T1}}{V_{T2}}$ i) $0 - \alpha$: T1 = +ve voltage } same as V_s
T2 = -ve voltage

2) $\alpha - \pi$: T1 conducting = V_{T1} small (+ve)

T2 Non conducting = $-V_{T1}$ small (-ve)



3) π to $\pi + \alpha$ \rightarrow -ve half cycle } same as V_s

$V_{T1} = -V_c$

$V_{T2} = +V_c$

4) arc time T1 or T2 = $\frac{\pi \text{ to } \pi + \alpha \text{ to } \pi + \alpha + 2\pi}{\text{Supply } -V_c} = \frac{\pi \text{ to } 2\pi}{V_{T2} \text{ small}}$

decip to many arcs
 V_{T1}

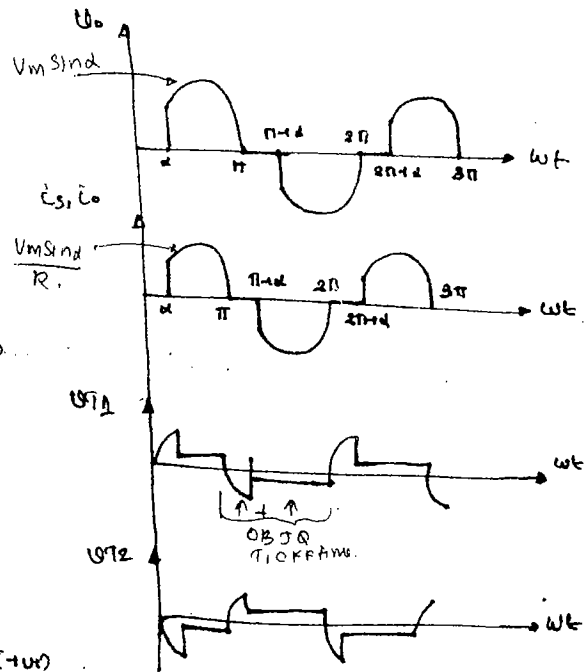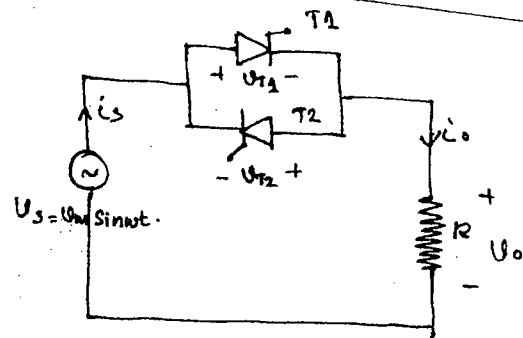

$$L = \frac{V_s}{\omega \cdot I_{f1}}$$

$$Q = \frac{V_s L}{\omega L}$$

$$\frac{V_s}{X_L} = \frac{V_s}{\omega L} = \frac{V_s}{\omega L}$$

2) For $\alpha > 90^\circ$, I_s would be less. But its fundamental component I_{f1} lags the supply voltage by 90° .

The value of I_{f1} would ~~increase~~ ^{decrease} with the increment of firing angle from 90° . The effective inductance will increase and reactive power will decrease.

$$I_{f1} = \frac{V_s}{\pi \omega L} [2\pi - 2\alpha + \sin 2\alpha]$$

at $\alpha = 90^\circ$

$$I_{f1} = \frac{V_s}{X_L} \quad [\text{substit}]$$

$$Q = V_s \cdot I_{f1} = V_s \cdot \frac{V_s}{\pi \omega L} [2\pi - 2\alpha + \sin 2\alpha]$$

$$Q = \frac{V_s^2 L}{\omega L} \frac{1}{\pi} [2\pi - 2\alpha + \sin 2\alpha]$$

→ For $\alpha \leq 90^\circ$ Reactive power will be MAXIMUM ($Q = Q_{max}$)


→ For $\alpha = 180^\circ$ Reactive power will be 0. ($Q = 0$)

	X_L	I_{f1}	Q
$\alpha \leq 90^\circ$	ωL (MINIMUM)	$V_s / \omega L$ (MAXIMUM)	V_s^2 / X_L (MAX)
$\alpha > 90^\circ$	INCREASE	DECREASE	DECREASE
$\alpha = 180^\circ$	∞	0	0

⇒ Ideally

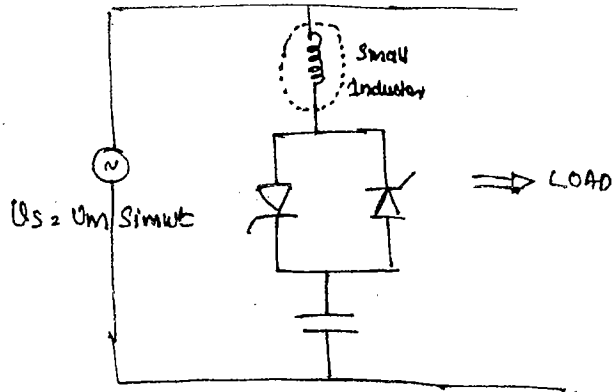2) Thyristor switched capacitors.

TSC means makes the availability or non-availability of the capacitor on the supply system. i.e. it switches the capacitor on to the supply systems.




TSC employs integral cycle control to connect the capacitance.

A small inductor will be connected ~~also~~ in series with the TSC to avoid the short circuit of the supply through capacitor. { (not) drawn }.

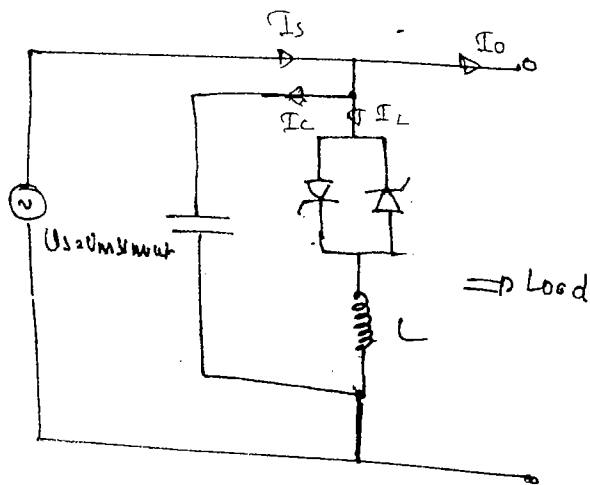3) Static VAR compensator (SVC)

SVC consists of a fixed capacitor connected across TCR. This combination controls the VAR requirement on the supply system. to maintain the power factor at the desired value.



leading VAR compensated = $\frac{V_s^2}{X_c}$ rms
 (Fixed always)
 $= \frac{V_s^2}{1/\omega c} = \underline{\underline{V_s^2 \cdot \omega c}}$


Maximum lagging VAR = $\frac{V_s^2}{X_L} = \frac{V_s^2}{\omega L}$ rms
 (variable).

L & C values of the compensator will be selected in such a fashion that

$\frac{V_L}{\omega L} > V^2 \cdot \omega c$

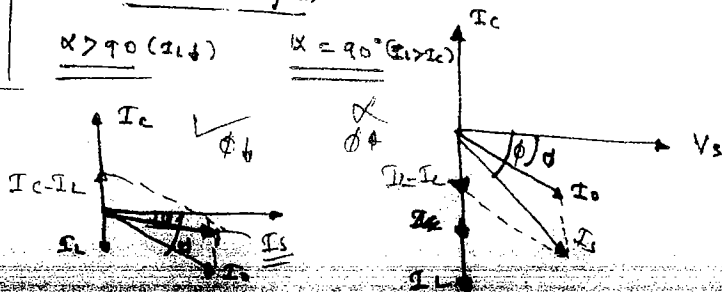4) Phasor diagram

$\alpha > 90^\circ$ (lag) $\alpha = 90^\circ$ (unity)










→ SVC supplies the required VAR on the supply system to adjust the power factor near to unity value.

→ In a 3φ circuit TCR should be connected in Δ fashion so that the (3n) triplen harmonics would be restricted inside the Δ, they will not inject on the supply systems.

POWER DIODE CIRCUITS.

28/05/11

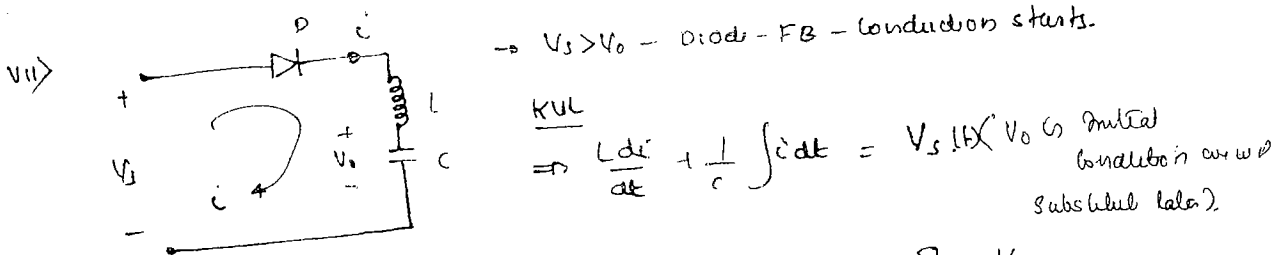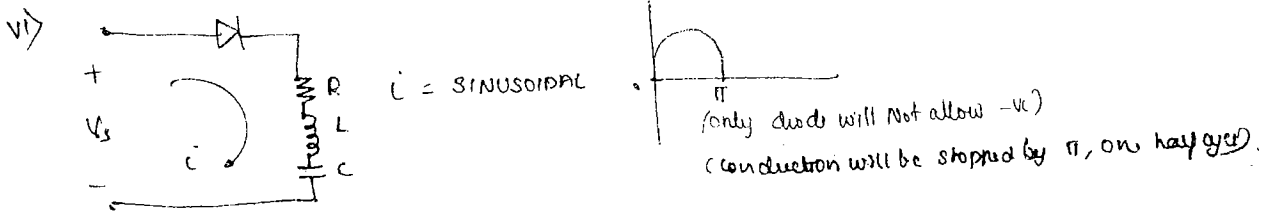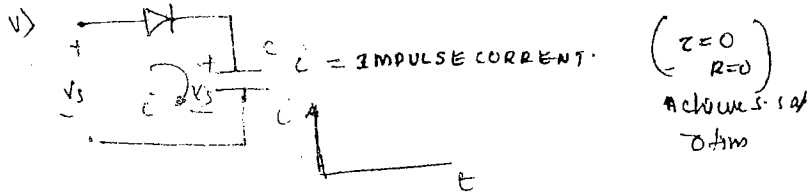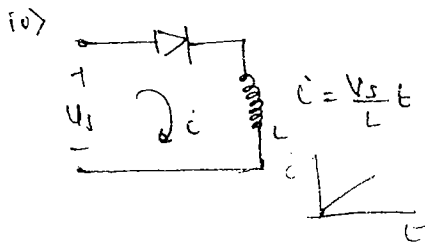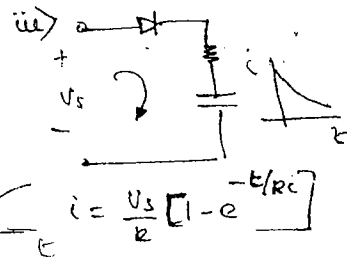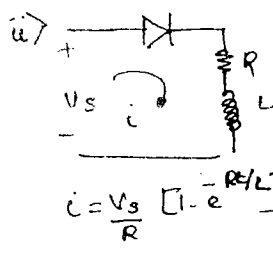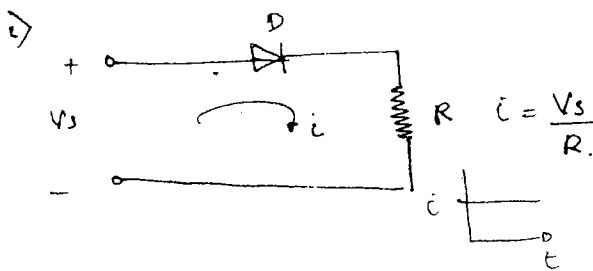

• Applying L.T $L [s^{-1} \omega] - 0 \uparrow$ initial $\frac{1}{C} \left[\frac{1 \omega}{s} + \frac{+eV_0}{s} \right] = \frac{V_s}{s}$

$$I(\omega) \left[sL + \frac{1}{C} \right] = \frac{V_s}{s} - \frac{V_0}{s} = \frac{V_s - V_0}{s}$$

$$I(\omega) = \frac{L}{s} \left[s^2 + \frac{1}{LC} \right] - \frac{V_s - V_0}{s}$$

$$I(s) = \frac{V_s - V_0}{L} \cdot \frac{1}{s^2 + \left(\frac{1}{LC}\right) \omega_0^2} \quad \text{Substitute}$$

$$I(s) = \frac{V_s - V_0}{L} \cdot \frac{1}{s^2 + \omega_0^2} \quad \text{where } \omega_0^2 = \frac{1}{LC} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$= \frac{V_s - V_0}{\omega_0 L} \cdot \frac{\omega_0}{s^2 + \omega_0^2}$$

From LF

$$\left. \begin{aligned} i(t) &= \frac{V_s - V_0}{\omega_0 L} \sin \omega_0 t \\ i_C(t) &= (V_s - V_0) \sqrt{\frac{C}{L}} \sin \omega_0 t \end{aligned} \right\} \omega_0 L = \frac{1}{\sqrt{LC}} \times L = \sqrt{\frac{L}{C}}$$

$$\Rightarrow \text{Inductor voltage} = L \frac{di}{dt} = L \cdot \frac{(V_s - V_0)}{\omega_0 L} \cos \omega_0 t \times \omega_0$$

$$V_L = (V_s - V_0) \cos \omega_0 t$$

$$\Rightarrow \text{Capacitor voltage } (V_C) = \frac{1}{C} \int i dt = \frac{1}{C} \cdot \frac{V_s - V_0}{\omega_0 L} \times \frac{\cos \omega_0 t}{\omega_0} + K$$

$$= - (V_s - V_0) \cos \omega_0 t + K$$

$$\left\{ \omega_0^2 = \frac{1}{LC} \right\}$$

Initial condition $t=0^+$, $V_C = V_0$

$$V_0 = - (V_s - V_0) \times 1 + K$$

$$K = V_0 + V_s - V_0 = V_s \quad \boxed{K = V_s} \text{ substitute}$$

$$V_C = - (V_s - V_0) \cos \omega_0 t + V_s$$


$$\boxed{V_C = V_s - (V_s - V_0) \cos \omega_0 t}$$

to find initially condition $V_0 = 0$ $V_C = V_s - V_s \cos \omega_0 t$ $i_{max} = V_s$

conditions allowed only for 'PI' systems $\omega_0 t = \pi$ $\boxed{t = \pi \sqrt{LC}}$

Initial condition	I_{peak}	Final voltage across capacitor	Conduction duration
1) $V_0 = 0$	$V_s \sqrt{\frac{C}{L}}$	$2V_s$	$\pi \sqrt{LC}$ s
2) $V_0 = +V_s$	$(V_s + V_0) \sqrt{\frac{C}{L}}$	$2V_s - V_0$	$\pi \sqrt{LC}$ s.
3) $V_0 = -V_s$	$(V_s - V_0) \sqrt{\frac{C}{L}}$	$2V_s + V_0$	$\pi \sqrt{LC}$ s.

viii)

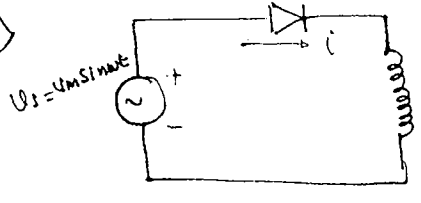

By KVL at +ve half cycle

$$L \Rightarrow L \frac{di}{dt} = V_m \sin wt$$

$$di = \frac{V_m}{L} \sin wt dt$$


Integrating $i = -\frac{V_m}{\omega L} \cos \omega t + k$ initial condition.

at $t=0 \Rightarrow i=0$ ($t=0 \Rightarrow \cos = 1$) $0 = -\frac{V_m}{\omega L} + k \Rightarrow k = \frac{V_m}{\omega L}$

$$i = -\frac{V_m}{\omega L} \cos \omega t + \frac{V_m}{\omega L} = \frac{V_m}{\omega L} [1 - \cos \omega t]$$


$$i = \frac{V_m}{\omega L} [1 - \cos \omega t]$$

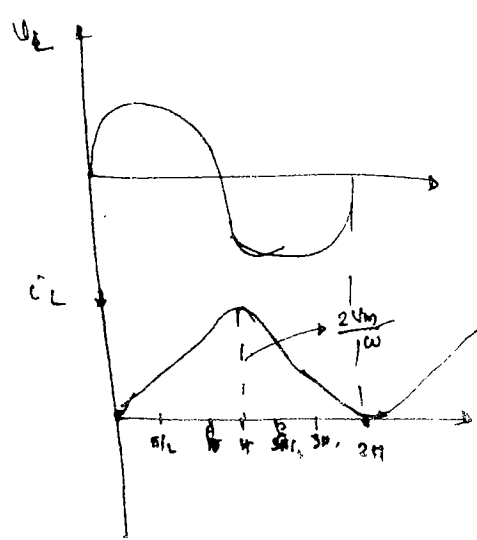$\cos \omega t = -1 +ve$
 $\cos \omega t = 1 +ve$ } $i = +ve$ always



$\omega t = 0$	$\omega t = \pi/2$	$\omega t = \pi$	$\omega t = 3\pi/2$	$\omega t = 2\pi$
$i = 0$	$i = \frac{V_m}{\omega L}$	$i = \frac{2V_m}{\omega L}$	$i = \frac{V_m}{\omega L}$	$i = 0$

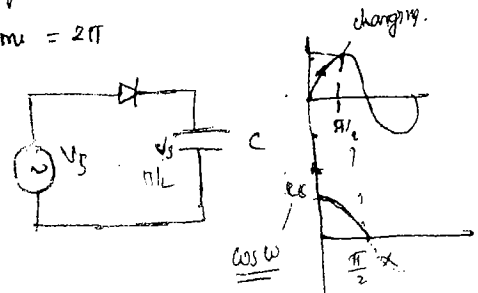
- Current always = +ve
- Conduction time = 2π




• conduction duration of the current is equal to 2π .

Note: If the circuit is feeding a pure resistor, then conduction time is equal to π .

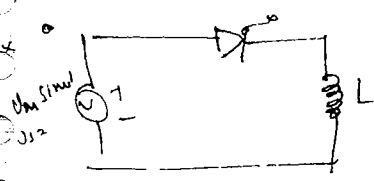If the circuit is feeding pure capacitor, then the conduction time = $\pi/2$.





$$\omega t = \theta \text{ (radians)}$$

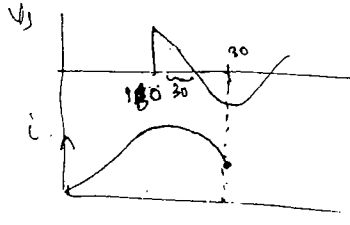

II > POWER BJT current controlled switch.

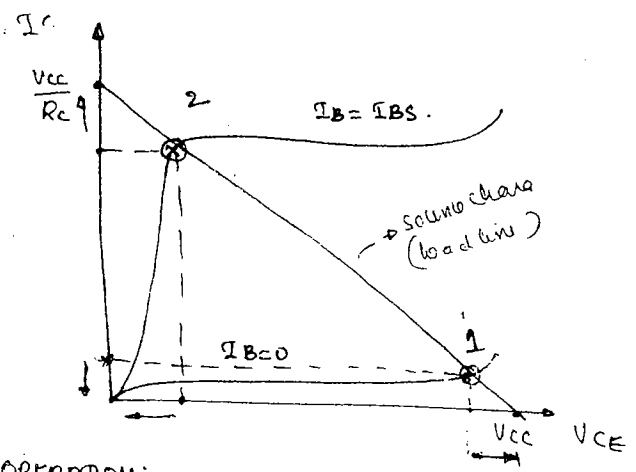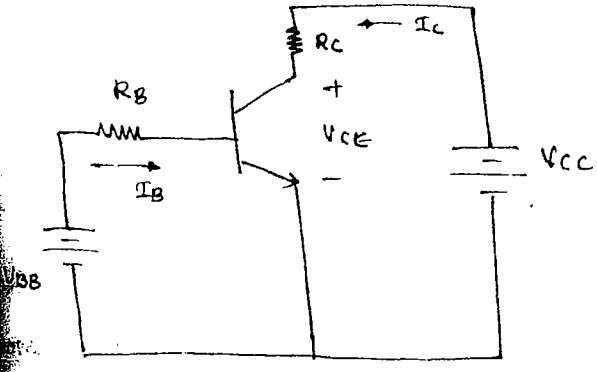Power BJT in n-p-n configuration and common emitter connectivity is suitable for power control applications.



- I_C = load current
- R_C = Load.
- V_{CC} = supply voltage.
- V_{CE} = voltage across the switch.
- I_B = control signal

OPERATION:-

- $\begin{cases} I = 0 \\ V = V_C \end{cases} \rightarrow 1. \text{ OFF STATE / OPEN SW}$
- $\begin{cases} V = 0 \\ I = I_L \end{cases} \rightarrow 2. \text{ ON STATE / OFF SW}$

loadline


- $V_{CE} = 0, I_C = \frac{V_{CC}}{R_C}$
- $I_C = 0, V_{CE} = V_{CC}$

I_{BS} = Base current corresponding to saturation.

Power BJT in cut off region acts as a open switch, in saturation region it acts as closed switch.

Power BJT being controlled by base current, it is known as current controlled device.

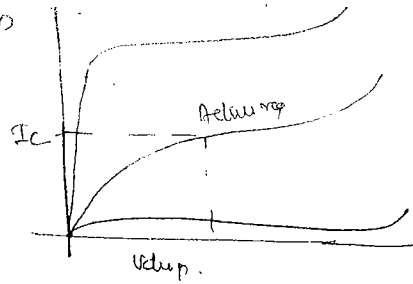power BJT should not operate in the active region as it leads to more voltage drop and power loss across the switch.



$$1) I_C = \frac{V_{CC} - V_{CE(sat)}}{R_C}$$

→ saturation V_{CE}

$$3) \beta = \frac{I_C}{I_B} = \text{current gain}$$

$$2) I_B = \frac{V_{BB} - V_{BE(sat)}}{R_B}$$

→ saturation V_{BE}

Control signal is there as long as switch is ON


$$4) \text{Power loss in switch} = V_{CE(sat)} I_C + V_{BE(sat)} I_B$$

6) OVER DRIVE FACTOR

$$= \frac{I_B}{I_{B(sat)}}$$

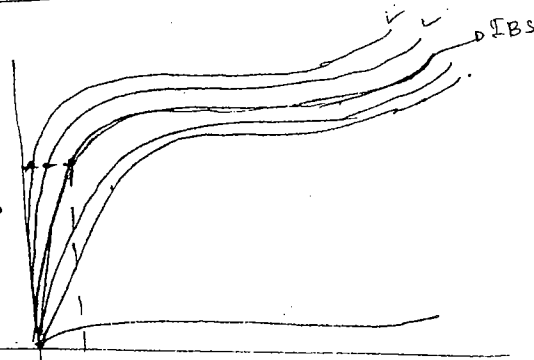5) Applied $I_B > I_{B(sat)}$.



Some times transistor will be driven with higher value of base current, thus switching performance would be improved.



At this condition, Transistor is said to be HARD DRIVEN TRANSISTOR

(or) OVER DRIVEN TRANSISTOR.

III > POWER MOSFET

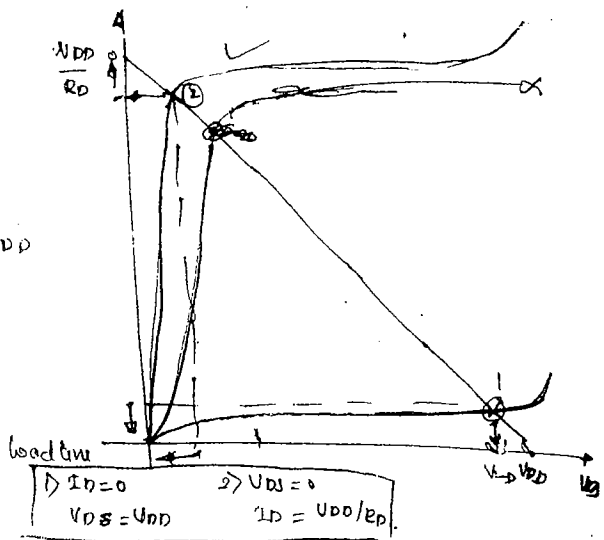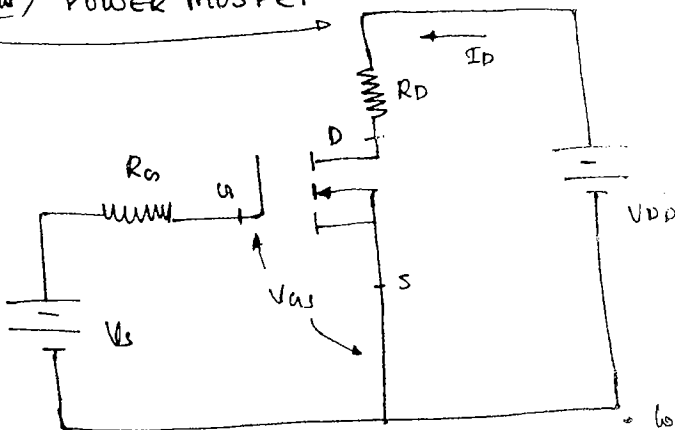

$$\begin{aligned} \triangleright I_D = 0 & \quad \triangleright V_{DS} = 0 \\ V_{DS} = V_{DD} & \quad I_D = V_{DD}/R_D \end{aligned}$$

\triangleright N channel MOSFET in common source configuration is the best suitable for power control applications.

Control applications.

$\triangleright I_D = \text{load current}, R_D = \text{load}, V_{DD} = \text{supply voltage}, V_{GS} = \text{control signal}$

$$I_D = \frac{V_{DD}}{R_D} = \text{Ideal load current}$$

3) Power MOSFET in cut-off region acts as a open switch and in saturation region

it acts as a closed switch.

4) MOSFET being controlled by voltage across gate to source junction (V_{GS})

it is known as voltage controlled switch.

5) It is having the faster switching time and switching losses will be less steady state voltage drop and conduction power loss could be more as MOSFET compared to BJT.

6) Power MOSFET is best suitable for parallel operation since it is possessing +ve temperature coefficient of resistance.

• IGBT has been developed by eliminating the limitations of transistor and MOSFET families. (BJT + MOSFET Family)

• IGBT is free from second breakdown problem that is present in BJT and conduction losses would be less compared to MOSFET.

POWER DEVICES IN THE DESCENDING ORDER IN THEIR SPEEDS OF OPERATION ARE AS FOLLOWS

MOSFET > IGBT > BJT > THYRISTOR

~~ELC~~ → DC DRIVES

29/03/11

- DC drive consists of DC motor, power electronic converter (rectifier or chopper), speed sensing mechanism (Tachometer), intelligent system (µP or µC)

The following dc motors are suitable for speed control applications

→ Separately excited dc motor

→ dc series motor

• During the speed control applications ~~used~~ ~~variable~~ - constant ϕ , armature current is assumed to be constant.

Note: • DC shunt motor is not preferable for speed control applications since, independent

Variation of armature voltage and field flux cannot be possible.

→ Induced Emf.

$$E_a = \frac{Z \phi N}{60} \cdot \frac{P}{A} \Rightarrow Z \phi n \times \frac{P}{A} \frac{E_a}{\text{Volt/s}}$$

$$\omega_m = 2\pi n \quad \text{when } n = \frac{\omega_m}{2\pi} \quad \text{so } E_a = Z \phi \cdot \frac{\omega_m}{2\pi} \times \frac{P}{A}$$

$$E_a = \left(\frac{Z \phi}{2\pi} \frac{P}{A} \right) \cdot \phi \omega_m$$

$$E_a = K_a \phi \omega_m \quad \text{where } K_a = \frac{Z P}{2\pi A}$$

→ Torque. Mechanical power = Electrical power (By energy conservation)

$$T_e \omega_m = E_a I_a$$

$$T_e = \frac{E_a I_a}{\omega_m} = K_a \phi \omega_m \times \frac{I_a}{\omega_m}$$

$$T_e = K_a \phi I_a$$

→ Separately excited DC motor.

a) $E_a = K_a \phi \omega_m$ where

$$K_m = K_a \phi$$

$$K_m = \left(\frac{V \cdot s}{\text{rad}} \right)$$

$$T_e = K_a \phi I_a$$

b) $T_e = K_m I_a$

$$K_m = K_a \phi$$

$$K_m = \left(\frac{Nm}{A} \right)$$

Same ***

ii) DC series motor

$$E_a = K_a \phi \omega_m$$

$$\phi \propto I_a \Rightarrow \phi = C \cdot I_a \quad \text{again}$$


$$E_a = K_a C \phi \omega_m$$

$$E_a = K_1 I_a \omega_m$$

$$K_1 = \frac{V \cdot s}{\text{rad} \cdot \text{A}}$$

$b) T_e = k_a \phi I_a = k_a C \phi_a I_a = k_1 I_a^2$
 $T_e = k_1 I_a^2$
 $k_1 = \frac{Nm}{A^2}$

SINGLE-PHASE HALF WAVE RECTIFIER DRIVE

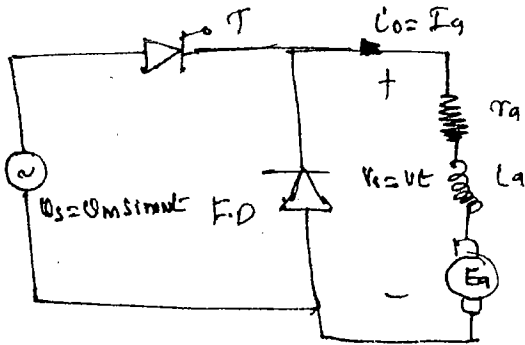

v_t ← (of semi-converter)

Note:

Solving Numerical. Find v_o of terminal side is asked find v_t of the converter is on T or F.D, v_s .

1) $i_T = i_s$ ($\alpha - \pi$ and $2\pi - \alpha$ to 3π)

2) i_{fd} ($0 - \alpha$, π to $2\pi - \alpha$)

3) $v_o = v_t = \frac{V_m}{\pi} [1 + \cos \alpha_1]$ *armature*

4) $v_t = \frac{V_m}{\pi} [1 + \cos \alpha_2]$ *power converter*


5) $I_{sr} = I_{tr} = I_a \sqrt{\frac{\pi - \alpha_1}{2\pi}}$

6) $I_{fd} = I_a \sqrt{\frac{\pi + \alpha}{2\pi}}$

7) *armature* $P_{in}(C_r)$ *input* $P_{in} = \frac{E_b I_a + I_a^2 r_a}{V_s I_{sr}}$

$= \frac{I_a (E_b + I_a r_a)}{V_s I_{sr}}$

$$P_{in} = \frac{V_t I_a}{V_s I_{sr}}$$

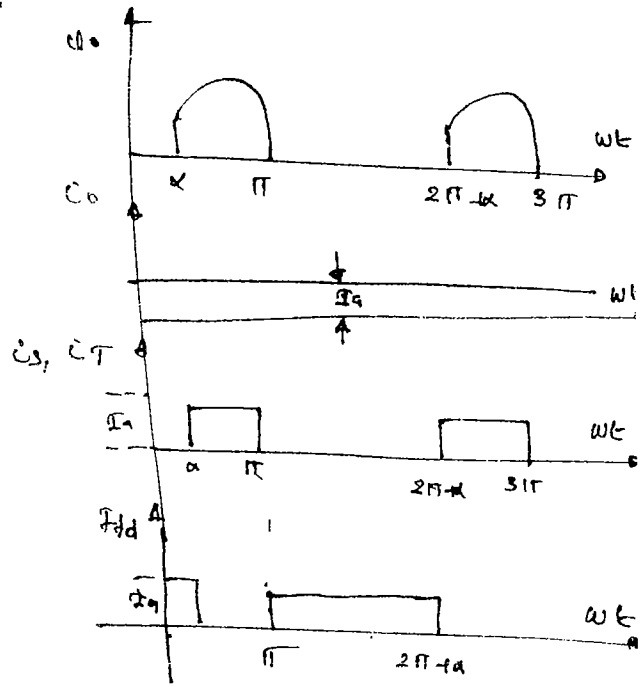

RLE load. \rightarrow *power loss in the resistor.*

$I_{sr} = I_{avg}$

Q1) S.E.M. DC / 1 d HWR

$$V_s = 230V, \gamma_a = 0.5$$

$$\frac{V-s}{r} = k_m = 0.4$$

$$T_L = T_e = 20 \text{ N-m}, N = 1500$$

$$I_a = \text{constant}$$

Sol:

$T_g(\text{arm}) = 0$ I_a we can calculate

$$T_e = k_m I_a$$

$$I_a = \frac{20}{0.4} = \underline{\underline{50A}} - \text{constant}$$

c) firing angle (converter side)

Start numerical from motor side

$$V_E = E_a + I_a r_a$$

↓ separately induced motor

$$= k_m \omega_m + I_a r_a$$

$$= 0.4 \times \frac{2\pi \times 1500}{60} + 50 \times 0.5$$

$$= \underline{\underline{87.8V}}$$

$$\Rightarrow \frac{V_m}{2\pi} [1 + \cos \alpha] = V_E$$

$$\frac{230\sqrt{2}}{2\pi} [1 + \cos \alpha] = 87.8$$

$$\alpha = \underline{\underline{45.8^\circ}}$$

$$c) I_s = I_a$$

$$I_s r = I_a \sqrt{\frac{V-s}{2T}}$$

$$= 50 \sqrt{\frac{230 - 87.8}{2 \times 30}}$$

ratio $\frac{V-s}{2T}$ keep in mind

$$= \underline{\underline{30.52A}}$$

$$iii) P_f = \frac{V_E I_a}{V_s I_s}$$

$$= \frac{87.8 \times 50}{230 \times 30.52}$$

$$P_f = \underline{\underline{0.625 \text{ lag}}}$$

Q2) S.E

$$N = 1400 \text{ rpm}$$

$$V_s = 330 \text{ sin } 314t$$

$$E_b = 80V$$

$$\alpha = 30^\circ$$

$$R_a = 4\Omega$$

$$I_a = ?, T = ?$$

→ This way calculate

$$V_o = \frac{V_m}{\pi} [1 + \cos \alpha]$$

$$= \frac{330}{\pi} [1 + \cos 30^\circ]$$

$$V_o = 196V, V_b = V_E = E_b + I_a r_a$$

$$196 = 80 + I_a \times 4 \quad T_e = k_m \cdot I_a$$

$$I_a = 29A$$

$$E_a = k_m \omega_m$$


$$k_m = \frac{80}{2\pi \times \frac{1400}{60}} = 0.545 \frac{V-s}{\text{rad}}$$

$$T_e = 0.545 \times 29 = \underline{\underline{0.83 \text{ N-m}}}$$

2) 1- ϕ Half controlled / Converter drive.

I) 1 ϕ - SEMI CONVERTER DRIVE / 1- ϕ HALF CONTROLLED CONVERTER

DRIVE :

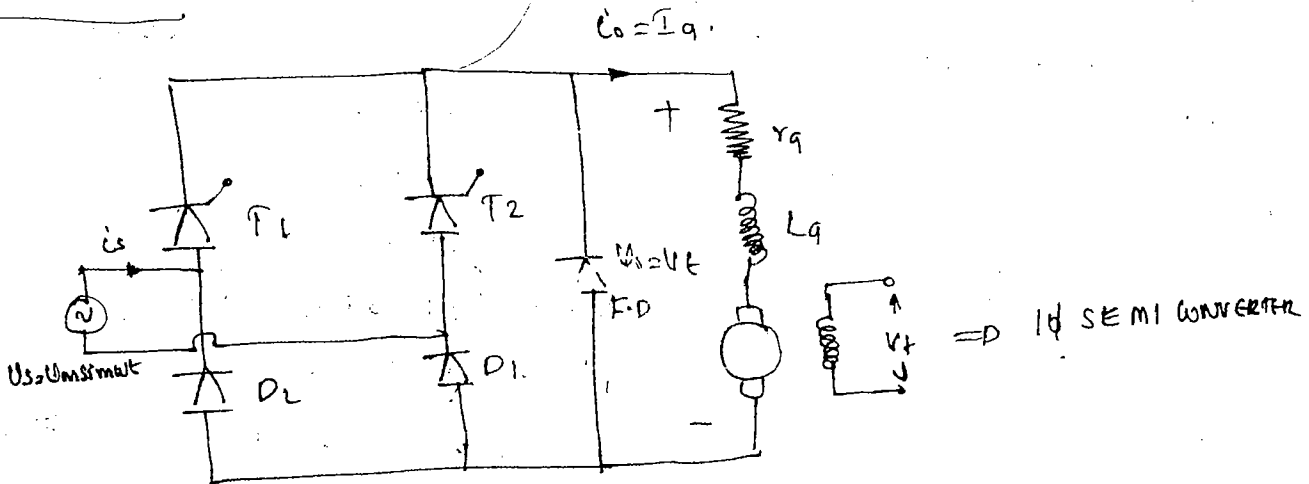


$\cdot U_o = U_E = \frac{V_m}{\pi} [1 + \cos \alpha]$

$\cdot U_f = \frac{V_m}{\pi} [1 + \cos \alpha_2]$

$\cdot I_{Tn} = I_{Dn} = I_a \sqrt{\frac{\pi - \alpha}{2\pi}}$

$\cdot I_{S\gamma} = I_a \sqrt{\frac{\pi - \alpha_1}{\pi}} \quad (\gamma_{\text{M}} = \left(\frac{I_{Tn}^2 + I_{Dn}^2}{I_a^2} \right)^{1/2} = \frac{I_a}{I_a} = 1)$

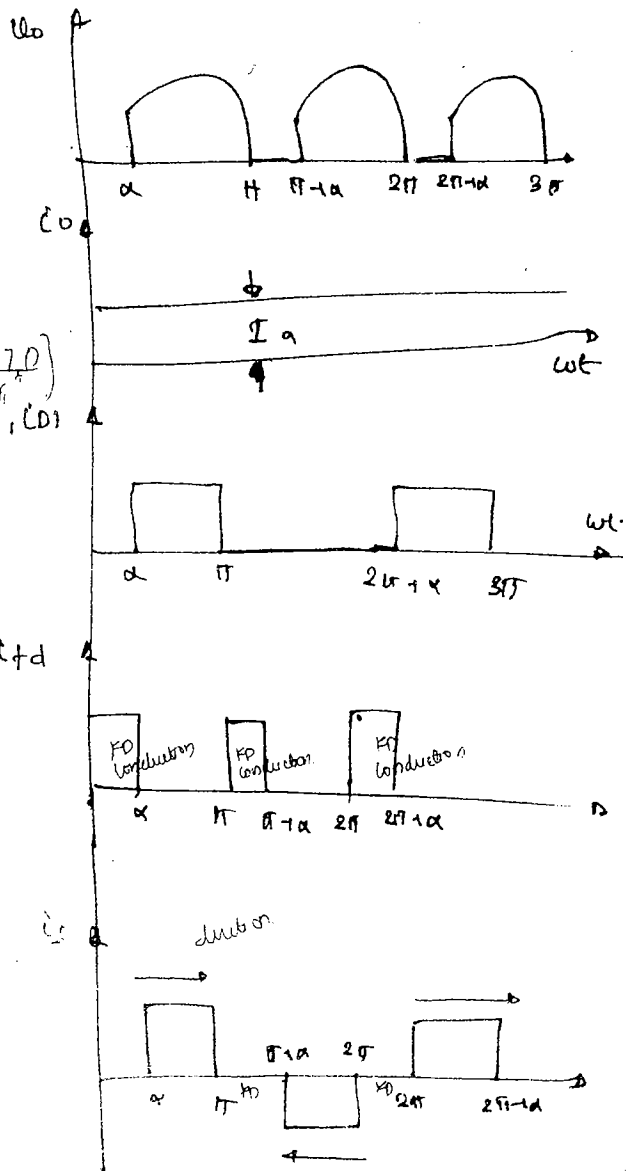$\cdot I_{FD\gamma} = I_a \sqrt{\frac{\alpha_1}{\pi}}$



03) DC series motor $\left\{ \begin{array}{l} 220V \\ 1000rpm \end{array} \right\}$ Motor Rating

$$r_a + r_s = 0.2 \Omega$$

$$\dot{N} = 1000 rpm, \quad k_1 = 0.03 \frac{Nm}{A^2}$$

$$\underline{V_s = 250V}$$

• Rating of the motor is useful to evaluate the motor constant.

• Current and torque are on motor side start from converter side.

$$V_o = \frac{V_m}{\pi} [1 + \cos \alpha]$$

$$= \frac{250\sqrt{2}}{\pi} [1 + \cos 30]$$

$$= 210V$$

$$V_o = V_E = D \cdot 210 = E_a + I_a (R_a + R_s)$$

$$V_o = (k_1 I_a \omega_m) + I_a (r_a + r_s)$$

$$= 0.03 \times I_a \times \frac{2\pi \times 1000}{60} + I_a \times 0.2$$

$$210 = 0.03 \times I_a \times \frac{2\pi \times 1000}{60} + I_a \times 0.2$$

$$\underline{I_a = 62.84}$$

$$T = k_1 I_a^2$$

$$= 0.03 \times (62.84)^2$$

$$\underline{T = 1184.6 Nm}$$

04) 220V, 1500rpm, 10A
(V) N I
• Separately excited dc motor.

$$r_a = 1 \Omega$$

• Fully controlled bridge rectifier

$$V_s = 230V$$

$$f = 50Hz$$

• Continuous load current

a) $\alpha = 30^\circ$, $T = 5 Nm$, $N = ?$

$$V_E = E_a + I_a r_a$$

$$220V = k_m \omega_m + I_a r_a = k_m \cdot \frac{2\pi \cdot 1500}{60} + (10 \times 1)$$

$$k_m = 1.337 \frac{V \cdot s}{\text{rad}} \quad (\text{keep up to 3 digits})$$

$$I_a = \frac{T}{k_m} = \frac{5}{1.337} = \underline{3.74A}$$

$$V_o = V_E = D \cdot 210 = \frac{2V_m}{\pi} \cos \alpha$$

$$= \frac{2 \times 230\sqrt{2}}{\pi} \cos 30 = \underline{179.53V}$$

$$V_o = V_E = D (k_m \omega_m + I_a r_a) = 179.53$$

$$179.53 = 1.337 \times \frac{2\pi \times N}{60} + 3.74 \times 1$$

$$\underline{N = 1254.95}$$

b) $\alpha = 45^\circ$, $N = 1000 rpm$

$$V_o = \frac{2V_m}{\pi} \cos \alpha$$

$$= \frac{2 \times 230\sqrt{2}}{\pi} \cos 45$$

$$= 146$$


$$146 = k_m \omega_m + I_a r_a$$

$$= 1.337 \times \frac{2\pi \times 1000}{60} + I_a$$

$$I_a = \underline{5.959A}$$

$$T = k_m I_a^2 = 1.337 \times 5.959^2 = \underline{8.7 Nm}$$

III > 1- ϕ - Full wave rectifier wave.

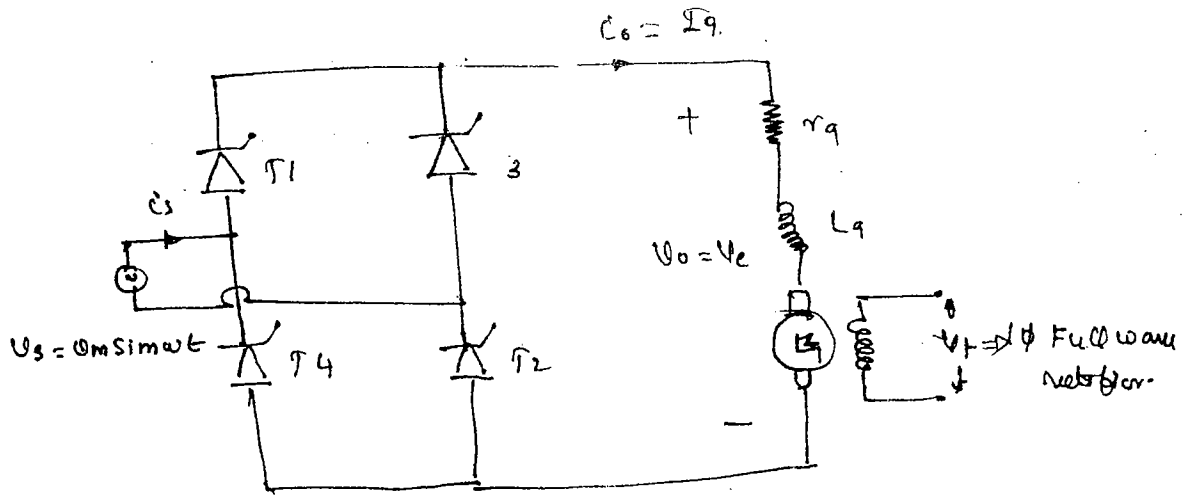

• Full wave Rectifier is specially used when
 motor + REGENERATIVE BRAKING, mode.


1) $U_o = U_e = \frac{2U_m \cos \alpha}{\pi}$

2) $U_f = \frac{2U_m}{\pi} \cos \alpha$

3) $I_{T\alpha} = I_g \sqrt{\frac{\pi}{2\pi}} = \frac{I_g}{\sqrt{2}}$

4) $I_{sr} = I_g$

5) $P_f = \frac{U_e I_g}{U_s I_{sr}}$

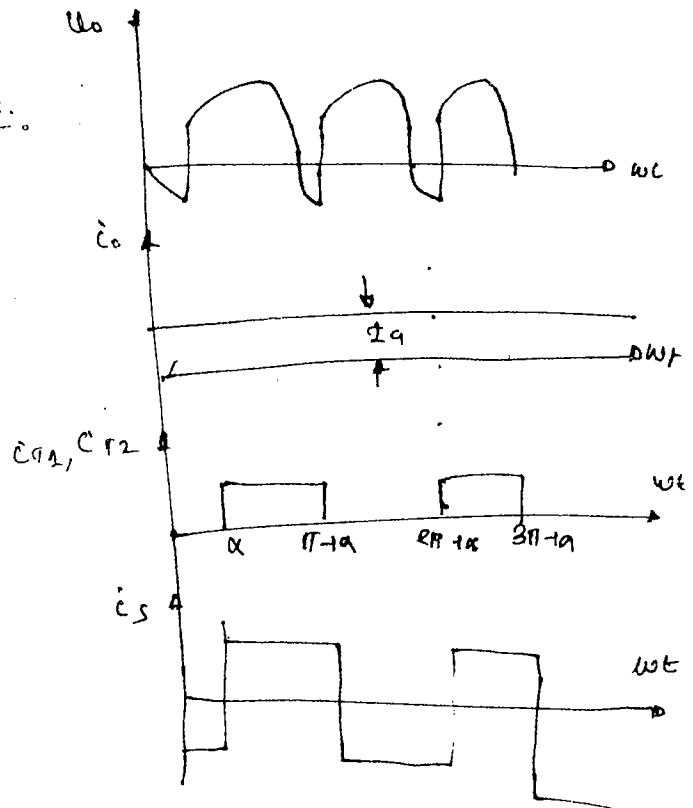

8125 387847

65) 2000
1000
100

inducting
(separable motor)

$$V_s = 230V, f = 50Hz$$

$$r_a = 1\Omega$$

$$I_a = \text{cont. max.}$$

a) $I_a = \text{rated} = 10A$ for Torque

rated

$$V_t = E_g + I_a R_a$$

$$200 = k_m \omega_m + 10 \times 1$$

$$200 = \frac{2\pi \times 100}{60} k_m + 10$$

$$k_m = 1.815 \text{ V}\cdot\text{s}/\text{rad.}$$

7

THE D

The End

$$30 - 450 = 11/10 \cdot 302$$

$$11 - 11.30 = 11/10 \text{ Syn.}$$

$$4 \text{ pm} - 11.30 = 11/10 \text{ Syn.}$$

$$\begin{array}{r} 106 \\ 25 \\ \hline 129 \end{array}$$