

20/9/10


Power Systems
- Seshaiyer

Syllabus:-

- Power generation $\left\{ \begin{array}{l} \text{Steam (or) Thermal} \\ \text{Hydel} \\ \text{Nuclear} \end{array} \right.$
- Power Transmission - ac - overhead
- Basic concepts in Transmission lines
- Transmission line constants - evaluation of L.C.
- Steady state performance of TL lines $\left\{ \begin{array}{l} \text{Short} \\ \text{medium} \\ \text{long} \end{array} \right.$
- Wave propagation phenomena in TL lines
- Voltage control and Power factor correction
- Overhead line insulators
- Concept of corona
- Under ground cables
- Distribution system
- Per unit system
- Symmetrical components
- Fault analysis
- Power system stability analysis
- Relays and C.B's
- Load flow studies (Ybus)
- Economic aspects and economic load dispatch
- HVDC transmission


vali
re

4/10/10

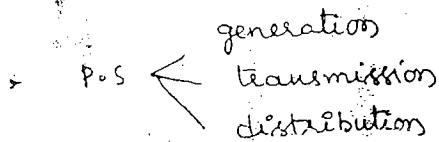



Power System :-

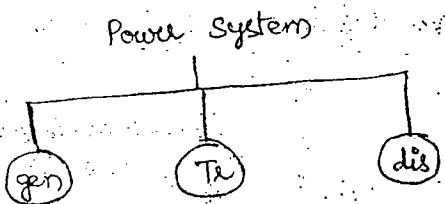It is the system which can deal with power generation, transmission and distribution.



(or)
 It is the system which can able to deliver the electrical energy to the consumer on economical basis. i.e. the cost of energy should be minimum.

Electrical energy = power x time

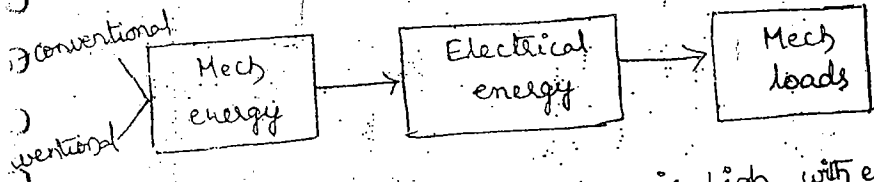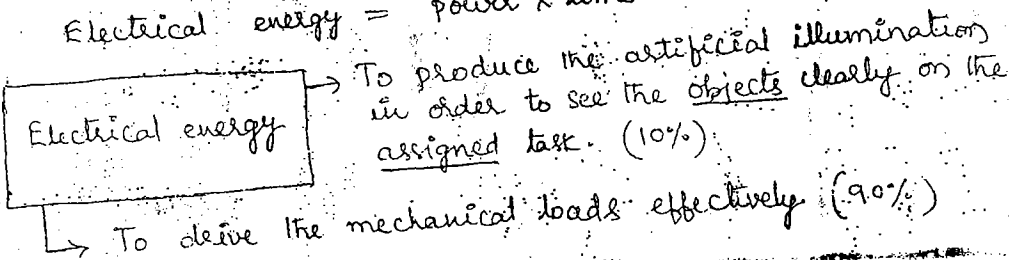

- ⇒ The efficiency of the system is high with elec energy at medium.
- ↳ The mechanical energy used for driving the mech loads will result as ineffective energy transformation.
- ↳ So that the loss in the s/m will be high and the η of the system is less.
- ↳ If the electrical energy used to drive the mech load, there will be effective energy transformation, so that the loss in the system will be less and the efficiency will be high.

Non-conv

Co


- 1) These renewable energy have so capacity short

Ex:-

bic (ma



- 2) Mech energy that are

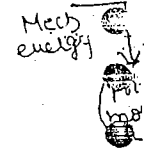

- 3) For used various

POWER SYSTEM

→ It consists of Generation, Transmission and Distribution



→ It consists of almost all electrical equipments which are placed at different locations and working together to supply the Electrical Energy to the consumer on Economic basis


→ What is the need to have Electrical Energy?

Electrical Energy! 1) To have an artificial illumination so that the objects can be seen very clearly (10% used)

2) To drive the mechanical loads (90% utilized)

The above ① & ② can be done by using some Non-Electrical energy. But to go for electrical energy is because of following advantages

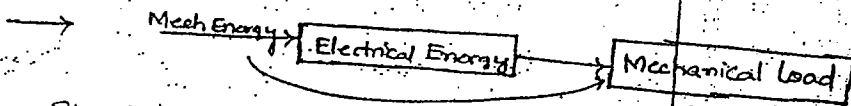
- 1) Efficiency is high (ii) Reliability is high (iii) Cost is Less
- 3) Easy control (v) No pollution



Since both are in same form we call it as ineffective energy transformation. then efficiency is Less.

→ But Mech → Elec → Mech is effective energy transformation then efficiency is more

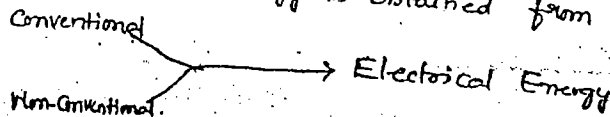→ Mechanical energy is obtained from two forms (or) sources



NON-CONVENTIONAL

1. Small Capacity power generation for short interval of time
2. Range of only kW

CONVENTIONAL

1. Bulk capacity of power generation for a longer time continuously

3. kW can be generated with 220V, 615V and 3.1KV

Ex: Solar, Tidal, Geothermal, Biomass, Diesel and MHD (Magneto Hydro Dynamo Generator)

4. Reliability is less


5. No Geographical constraints to install these plants

6. Running of plant is based on atmospheric conditions

7. Cost Analysis: Fixed + Running
 $R_2/kw + R_{fuel} \times t/kwhr.$


Fixed cost is less
 Running cost is high.

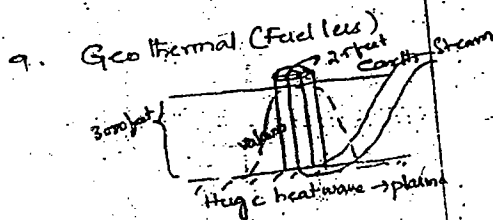8. Application: Except Geothermal remaining are suitable for Peak load



10. Generators used are Asynchronous generators i.e. Variable speed Ex: Induction generator

11. Used for sparsely distributed areas

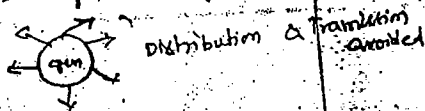

3. Generation levels are of 3.3 KV, 6.6KV, 11KV, 13.2KV, 18.6KV and 22KV

Ex: Steam (a) Thermal, Hydro, Nuclear and Gas.


4. Reliability is high

5. Installation of these plants based on Geographical constraints

6. The running of plant does not depend on atmospheric conditions

7. Fixed cost / Kw is high. Running cost is less

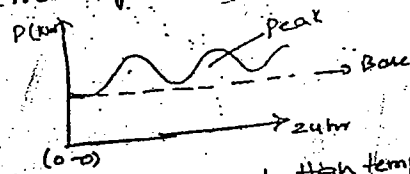8. Appln: Except Gas plants the remaining suitable to base load.



9. High pressure and high temp steam

10. Generators used are of constant speed type Ex: Synchronous generator (a) alternator

11. Bulk capacity power generation

is made at remote place. So it is necessary to carry over a long to the populated areas which is known as power transmission and then followed by power distribution.

→ 1,30,000 MW total power generation in India (from 1950 to 2000)

STEAM (OR) THERMAL STATIONS

The high pressure and high temperature steam (mechanical energy) is converted into an Electrical Energy

→ Thermal plants based on capacity

- 1. Industrial plants — (5 MW - 10 MW) — ^{Pressure} 1.5 kg/cm²
- 2. Commercial plants — (10 MW - 500 MW) — 160 kg/cm²




→ Selection of site :

- (i) Large capacity thermal plants are proposed to locate near the pit head
- (ii) Available of ample water
- (iii) Land requirement at less cost
- (iv) Accessible to road and rail

→ The principle of operation of Thermal plants is based on RANKIN CYCLE


→ Capacities of plants in APGENCO

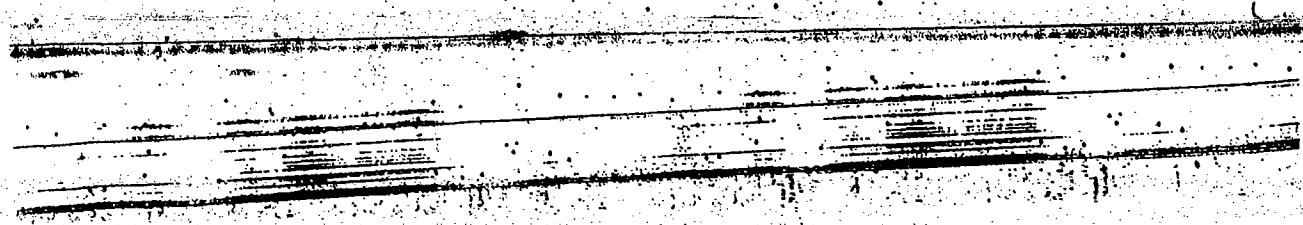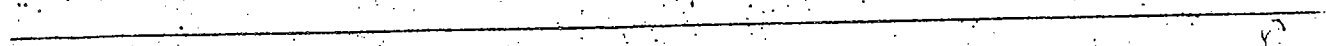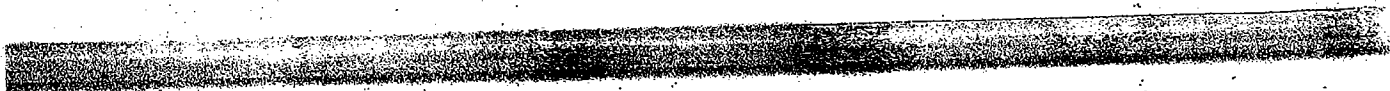- VTPS → 210 X 6 MW
- RTPP → 210 X 4 MW
- KTPS → 60 X 4 → I & II stages
- 110 X 4 → III & IV stages
- 250 X 2 → V stage
- RTPS → 66.5 MW
- NTPC → 1000 MW (Vizag)
- NTPC → 2600 MW (Ramagundam)




→ For effective utilization of the steam at higher pressure and higher temperature, allow the steam for expansion at more than one stage

→ Impulse turbine

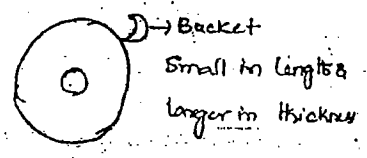

Reaction turbine

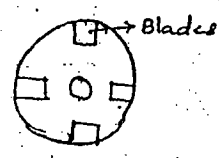

→ The purpose of the turbine is to rotate the alternator by using the mechanical energy (steam)

→ The generator which is placed at the thermal station is synchronous generator (alternator) with cylindrical rotor

→ For 2-pole machine the maximum speed is 3000 rpm for a cylindrical rotor at $f = 50\text{Hz}$.

→ Cylindrical alternator is also called as Turbo alternator

→ Cooling of the Alternator: Rotor

(i) For $\leq 100\text{MW}$ plant → Natural cool

(ii) For $> 100\text{MW}$ plant → Natural cool + Hydrogen gas (lightest gas)

*pressure is 0.035kg/cm^2

→ At present the turbo alternator available are with a capacity of 500MW

→ CONDENSER: The purpose of the condenser is to provide vacuum to the turbine so that the steam will be expanded over a larger area which will result that the output of steam will come out with

0.04 kg/cm^2 and 40°C

→ pH value of the D.M water is slightly greater than 7.

→ The pressure of steam in steam drum is 110-160 kg/cm² with a temperature of 300°C

→ SUPER HEATER: The purpose of the super heater is to increase the temperature of the steam without changing the pressure with the help of the temperature of the FLUE GASES

→ The maximum temperature at which thermal station is working is 540°C and maximum pressure is 160 kg/cm²

→ The super heater consisting of series of tubes in which the amount of steam is allowed and over the surface of the tubes, the flue gases are allowed to flow so that the amount of temperature of the flue gases is extracted by the steam in the tubes of the economizer

→ Range of temperature of flue gases is 240°C

→ The purpose of the steam valve is to control the amount of steam based on the loading conditions on the alternator

→ TURBINE (PRIME MOVER):


→ Based on Principle of operation

1. Impulse turbine Ex: Pelton wheel

2. Reaction turbine Ex: Francis, Kaplan, propeller


→ The turbine used in thermal power plant is

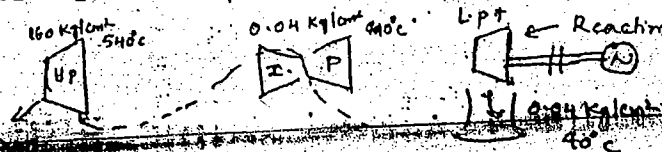a) Impulse (b) Reaction (c) Either Impulse or Reaction (d) Impulse-Reaction



→ Most common way of handling ash is called is

Hydraulic system

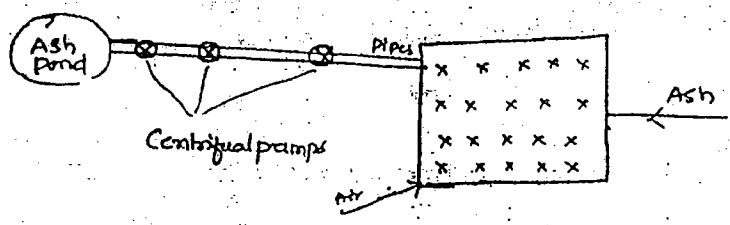

→ BOILER: The purpose of the boiler is to generate the amount of steam required with sufficient pressure as well as temperature [Boiler is a series of tubes]


→ TYPES OF BOILERS:

- 1. Water tube Boilers: Water in tubes and heat is surrounded. *Recommended*
- 2. Fire tube Boilers: Fire in tubes and water is surrounded. *Not recommended*

→ Water is used in the boiler tubes to get an amount of steam is Demineralized water (DM water)

→ Scaling [deposits of sodium & calcium] is formed in the tubes if we use mineral water

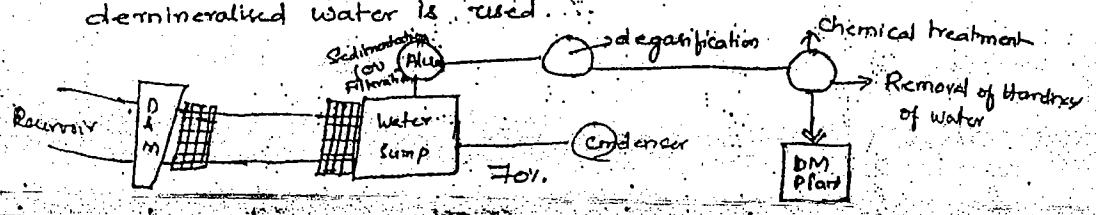→ In order to avoid the scale formation inside the boiler tubes demineralized water is used.



→ FUELS

(i) Liquid fuels → low grade petroleum for normal start up
Sweden

(ii) Coal → Semi bituminous coal is used in all the thermal stations in India

→ The liquid fuels are normally used during the normal start up and also variation of the load

→ The ash content in Indian coal is 20-40%

→ Coal → 1) peat → Lignite → Bituminous → Semi Bituminous → Anthracite

1) Coal is unloaded by wagon Tippler

2) Coal transportation is done from open yard to boiler is by using Belt Conveyers.

3) Coal preparation →
1) Crushers
2) Dryers
3) Separators

→ Coal used in furnace is pulverized coal (fine powder) which is done in "Ball mills"

→ The purpose of the pulverized coal is to increase the heating and burning properties of the coal.

→ The Ash in Thermal power plants is of two types

(i) Heavy ash (or) bottom ash

(ii) Fly ash

→ Ash handling ways

1) Mechanical system

2) Jet of steam → injected water

3) Pneumatic system → Air injected

6

→ The pressure and temperature is very low at condenser.


→ TYPES OF CONDENSERS!

(i) Jet type (ii) Surface type

(i) Jet type: In jet type condenser, a jet of water is mixed with the steam and the combination is discharged into the down stream canal may be utilized for irrigation purpose.

In this method, there is no recollection of water from the expanded steam.

(ii) Surface type:

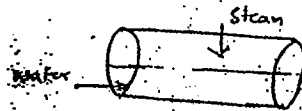

In the surface type condenser, one side the expanded steam is allowed and the other side the water is allowed so that the temperature of the steam is extracted by the water.

→ The purpose of the condensed extraction pump is to collect the water from the expanded steam, which is not sufficient as the feed water to the boiler due to some amount of loss of steam during the expansion.

→ The feed water is a combination of Condensated extraction water as well as make up water from the D.M plant.

→ The purpose of the cooling tower is to send the vapour particles into the atmosphere, so that the normal water


will be collected at the bottom of the cooling tower and can be recirculated for the purpose of the condenser again.

→ There are two types of draughts in the Thermal Station

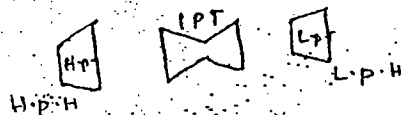- 1) Natural draught → pressure difference [Ex chimney]
- 2) Artificial draught → Fan
 - Induced draught fan (I.D) [-ve pressure]
 - Forced draught fan (F.D) [+ve pressure]

→ The cooling towers are attached with forced draught so that the air is blowing on the vapour particles in order to send them into the atmosphere

→ The purpose of the I.D fan at the chimney is to collect the flue gases and send it in to the atmosphere.



→ The purpose of the low pressure heater and high pressure heater is to increase the pressure and temperature of feed water.

→ The Economizer consisting of series of tubes in which the feed water is allowed and over the surface of the tubes the flue gases are flowing. The amount of temperature of flue gases are extracted by the feed water in the economiser tubes.

→ The purpose of the economiser is to supply the feed water to the boiler tubes with certain temperature and pressure so that the actual amount of coal required in the boiler furnace is less. Hence the boiler efficiency is increased. So the economiser is one of the accessory (Auxiliary equipment) for the boiler.

→ Economizers are normally employed if the pressure of the steam which is required is more than 70 kg/cm²

→ The another auxiliary equipment for the boiler is Airpreheater. The purpose of the airpreheater is to supply the hot air to the boiler furnace for effective conversion of the coal.


→ The air to the boiler surface is supplied through chimney as well as F.D fan which is placed near to the air-preheater (APH).

→ The temperature of the flue gases is extracted by the air in the Airpreheater, so that the air supplied to the boiler furnace will attain certain temperature.

→ ELECTROSTATIC PRECIPITATOR: The flue gas consisting of the ash particles as well as the poisonous gases like CO, CO₂ and SO₂. The purpose of the ESP is to collect the flyash particles as well as the poisonous gases.

→ Efficiency of ESP is from 99.5% to 99.8%.

→ It consists of few plates

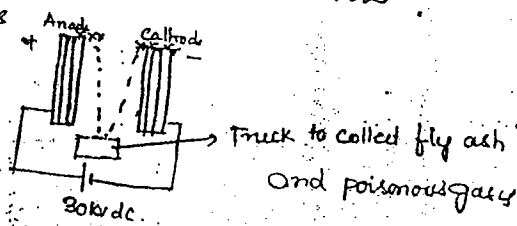

→ Fly ash is used in brick industries & cement industries otherwise it is sent to heavy air and disposed through hydraulic system.

→ EFFICIENCY:

The overall efficiency of a thermal station is

$$\eta_o = (\eta_b \times \eta_t) \times \eta_e$$

$\eta_b \rightarrow$ boiler efficiency
 $\eta_t \rightarrow$ turbine efficiency
 $\eta_e \rightarrow$ Electrical efficiency

$$\eta_o = \frac{\text{Heat equivalent of Electrical output (Kwh)}}{\text{Heat of combustion of coal (Kcal)}}$$

→ $1 \text{ Kwh} = 860 \text{ Kcal}$

$1 \text{ KWh} = 36 \times 10^5 \text{ Joules}$

$\therefore \eta_o = 30\%$

→ Life of Thermal station is 20 years

→ 1 MW of generation in T.S requires 10 tonnes of coal per day
 1 ton → 1000 kg

$$\eta_o = \eta_T \times \eta_e$$

$\eta_T \rightarrow$ Thermal efficiency

→ Without A.P.H and Economiser the boiler efficiency is 70% only

$\eta_{\text{APH}} \rightarrow 8\%$, $\eta_{\text{Economiser}} \rightarrow 12\%$

→ The efficiency of the Thermal plant is less because

(i) There is a huge loss in pressure & temperature of the steam at condenser.

(ii) The Auxiliary consumption of the station is high because of wide auxiliary equipment.

(2) HYDEL PLANTS:

It is also a conventional source of electrical energy

→ Working principle: The potential energy of a stored water is first converted into high velocity and high pressure kinetic energy which is later converted into Electrical Energy

→ Selection of Site:

- (i) Ample quantity of water is available with specific head
- (ii) Storage facility
- (iii) Accessible to road
- (iv) Near to Load centres

→ Capacities of Hydel plants in Andhra Pradesh

1. Nagarjuna Sagar → $110 \times 1 \rightarrow 110 \text{ MW}$ (BHEL)
→ $100 \times 7 \rightarrow 700 \text{ MW}$ (S&W) } 810 MW

2) Srisailem → R → $100 \times 7 = 700 \text{ MW}$
→ L → $150 \times 6 = 900 \text{ MW}$ } 1600 MW

3) Upper Silera → $60 \times 4 = 240 \text{ MW}$
Down Silera → $110 \times 4 = 440 \text{ MW}$ } 680 MW

→ HYDROLOGY:

1. Precipitation (P): It is the amount of water which is available on the earth's surface due to melting of the ice @ direct rains.

2. Run off (R): It is the amount of water which is flowing through valleys in the form of a stream of water from the available precipitation after infiltration by the soil.

3) EVAPORATION (E): It is the amount of water which got evaporated to atmosphere during summer.

$$P = R + E$$

$$R = P - E$$

4) HYDROGRAPH: It is electrically called as load curve.

→ It gives the variation of the discharge in the m^3/sec with respect to time. It is an equivalent of load curve.

(1) The area of the curve upto this specified area will provide the volume of water which got discharged.

(2) The peak point will indicate maximum discharge.

(3) It provides the discharge in m^3/sec at any particular point of time.

(4) It can also provide the average discharge.

(5) FLOW DURATION CURVE: It gives the variation of discharge in m^3/sec w.r.t percentage of time and the discharges are rearranged in descending order.

→ From the given flow duration curve, it can estimate the total available power.

→ $Cu-cc$ → discharge, TMC → volume of water
 ↓ ↓
 Cubic feet Thousand million cu-ccs.

(6) MASS CURVE: It gives the cumulative amount of water which got stored in the reservoir w.r.t percentage of time over a specified period.

→ Mass Curve is expressed as Day - sec - meter.

→ The amount of power that can be generated is

$$P = \frac{9.81 \times W \times Q \times H \times \eta}{1000} \text{ kW}$$

- W → Density of the water = 1000 kg/m³
- Q → Discharge → m³/sec
- H → available Head → m
- η → efficiency = 0.85

Q: The amount of power generated in kW in a mass curve of day - sec - m and η is 100%

Sol: Day - sec - m → $\frac{24 \times 3600 \times 1}{144}$
 $\frac{72}{86400} \text{ m}^3$

∴ Volume → 86400 m³

∴ Discharge/sec → $\frac{86400}{24 \times 3600} = 1 \text{ m}^3/\text{sec}$

∴ $P = \frac{9.81 \times 1000 \times 1 \times 1 \times 1.0}{1000} = 9.81 \text{ kW}$

→ If 10 day - sec - m = 10 × 24 × 3600 × 1 = 8,64,000 m³

Discharge = $\frac{8,64,000}{24 \times 3600} = 9.81 \text{ kW}$

→ If Day - sec - 10m = 24 × 3600 × 10 = 8,64,000 m³

Discharge = $\frac{8,64,000}{24 \times 3600} = 10 \text{ m}^3$

→ If 100m → 100 m³/sec

But if 10 days → 1 m³/sec

∴ For 10³ m³/sec

$P = \frac{9.81 \times 1000 \times 10 \times 10 \times 1}{1000} = \frac{9.81 \times 1000 \times 1 \times 10 \times 10 \times 1}{1000}$

9.81 kW

CLASSIFICATION OF THE HYDEL PLANTS

1) Based on the installed capacity

- (i) Micro $\rightarrow \leq 5$ MW
- (ii) Medium $\rightarrow 5$ to 100 MW
- (iii) Large $\rightarrow 100$ to 1000 MW \rightarrow In general preferred
- (iv) Super \rightarrow above 1000 MW

2) Based on the available head

- (i) Low head plants $\rightarrow < 70$ MW
- (ii) Medium head $\rightarrow 70$ to 300 MW
- (iii) High head $\rightarrow > 300$ MW

3) Based on the availability of water

(i) Base load Run off river without pondage

(ii) Peak load Run off river with pondage \rightarrow temporary storage of water with small capacity

(iii) Reservoir type \rightarrow Most common type in India

(iv) pumped storage plant

(i) RUN OFF RIVER WITHOUT PONDAGE:

If the water is available with natural head then the available water in the river can be directly utilized for power generation, however the reliability of this plant is very less.

(ii) RUN OFF RIVER WITH PONDAGE:

It is expected to run if there are floods in the river. During the dry season the stream of water in the river is very very low and it can be stored continuously over time. The stored water can be utilized to generate the power to meet the peak load demand. So

→ CLASSIFICATION OF DISTRIBUTORS

(1) Based on Construction → S.H.T.
 → U.G. (Highly populated areas)

(2) Based on nature of Current → a.c. (I, z) (vector calculation) Time required ↑
 → d.c. → IR (Arithmetic calculation)

→ The voltage drop calculations will be taking much time in case of a.c. distribution when compared to d.c. distribution. Hence the distributor performance can be carried out for most of examples with d.c. currents

(3) Based on no. of wires → dc → 2 wire ✓
 → 3 wire (rare)
 → ac → 1-φ 2 wire ✓
 → 3-φ 4 wire ✓ → (1-φ, 2 wire calculations)
 → 1-φ, 3 wire (rare)


(4) Based on the source (or) scheme

- (i) Radial distributor fed from one end with concentrated load (or) uniform loading
- (ii) Radial distributor fed from both the ends with concentrated load (or) uniform loading, with equal voltages (or) unequal voltages.
- (iii) Ring main distributor
- (iv) Interconnected ring main distributor.


→ In rural areas, Radial distribution schemes are employed

→ In urban areas, Ring main distribution schemes are employed.

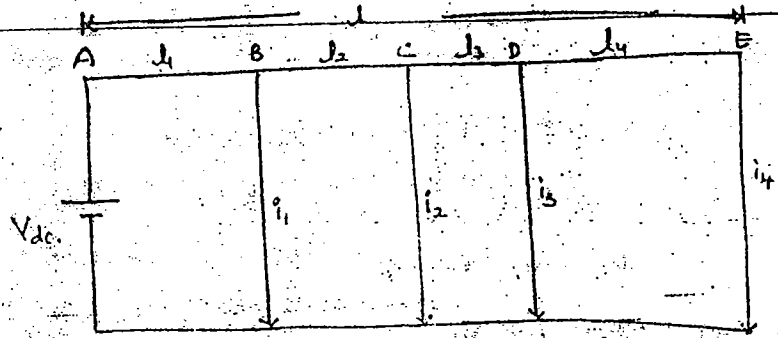
DC WIRE
 → RADIAL DISTRIBUTOR FED FROM ONE END WITH CONCENTRATED LOADS



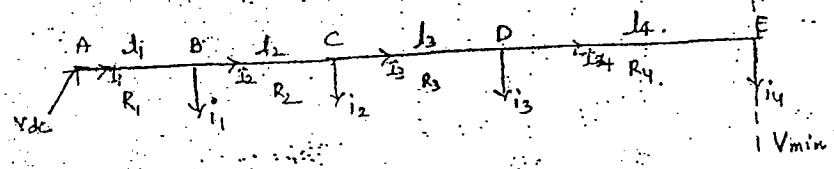$r' \rightarrow$ be the resistance of conductor in Ω/m
 $r = 2r' \rightarrow$ resistance of distributor in Ω/m



$R_1 = r \times l_1$	$I_1 = i_1 + i_2 + i_3 + i_4$
$R_2 = r \times l_2$	$I_2 = i_2 + i_3 + i_4$
$R_3 = r \times l_3$	$I_3 = i_3 + i_4$
$R_4 = r \times l_4$	$I_4 = i_4$

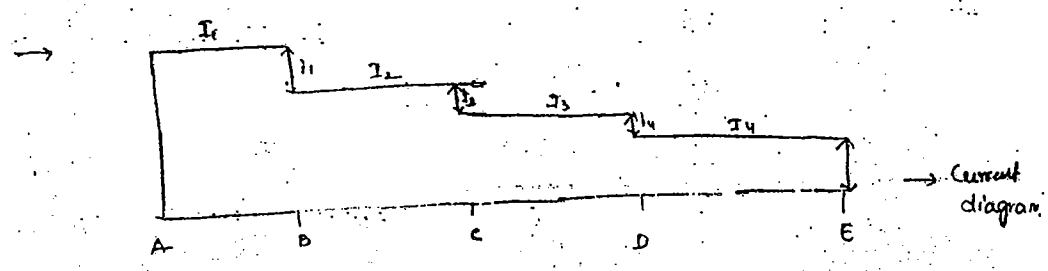

Voltage drop at A = 0


B = $I_1 R_1$

C = $I_1 R_1 + I_2 R_2$

D = $I_1 R_1 + I_2 R_2 + I_3 R_3$

E = $I_1 R_1 + I_2 R_2 + I_3 R_3 + I_4 R_4$ → drop

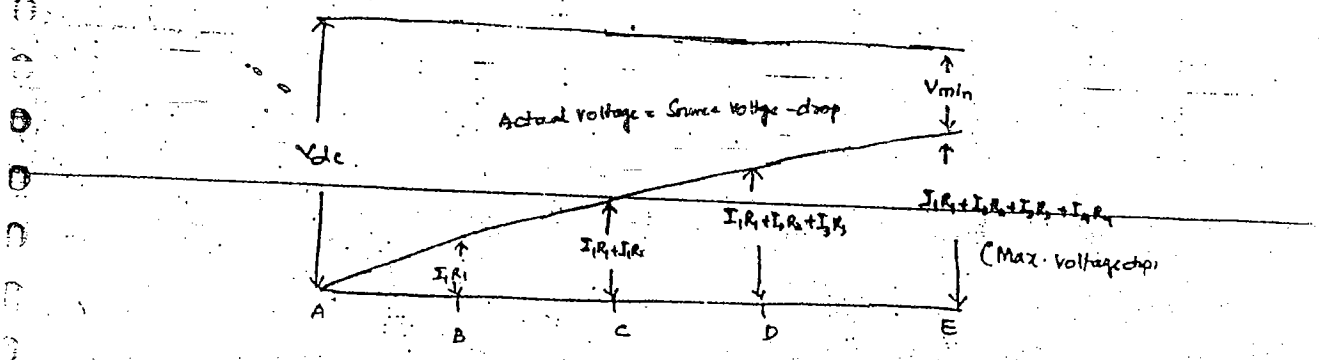Power loss = $I^2 R = I_1^2 R_1 + I_2^2 R_2 + I_3^2 R_3 + I_4^2 R_4$




→ A radial distributor fed from one end is having a maximum voltage drop at the tail end of the consumer so that there will be a minimum voltage for that consumer.

→ In general the voltage at a distance of 'x'

$$V_x = V_{dc} - \sum IR$$

→ UNIFORM LOADING

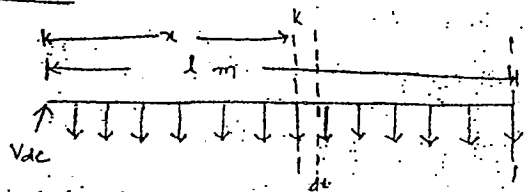

$$\text{Max voltage drop} = \frac{IR}{2}$$

i = uniform current Amp/m.

r = resistance of distributor in Ω/m

→ In practical case, the loads on the distribution are the concentrated loads. The uniform loading is the special case.

→ The leakage current of the U.G.C under no load condition is called as uniform loading.

$$\text{Max voltage drop} = \frac{IR}{2}$$

$$\text{Voltage drop in 'dx'} = i(1-x) \cdot r \cdot dx$$

$$\text{Drop upto 'x'} = \int_0^x i(1-x) r \cdot dx$$

$$\text{Drop at } x' = iR \left[lx - \frac{x^2}{2} \right]_0^x$$

$$= iR \left[lx - \frac{x^2}{2} \right]$$

of $x = l$, Maximum Voltage drop

$$\text{MVD} = iR \left[l^2 - \frac{l^2}{2} \right]$$

$$= \frac{iRl^2}{2}$$

$$= \frac{(i \times l)(R \times l)}{2} = \frac{I \cdot R}{2}$$

$$V_{\text{min}} = V_{\text{dc}} - \frac{IR}{2}$$

$$\rightarrow \text{Power loss} = \frac{I^2 R}{3}$$

$$\downarrow$$

$$\text{loss in } dx = [i(1-x)]^2 R dx$$

$$\text{loss up to } x' = \int_0^x i^2 (1-x)^2 R dx$$

$$= i^2 R \int_0^x (1^2 + x^2 - 2lx) dx$$




$$= i^2 R \left[1^2 x + \frac{x^3}{3} - 2l \cdot \frac{x^2}{2} \right]_0^x$$

$$\text{loss up to } x' = i^2 R \left[1^2 x + \frac{x^3}{3} - lx^2 \right]$$

$$\text{Total loss } (x=l) = i^2 R \left[l^3 + \frac{l^3}{3} - l^3 \right]$$

$$= \frac{(iRl)^2 (R \times l)}{3}$$
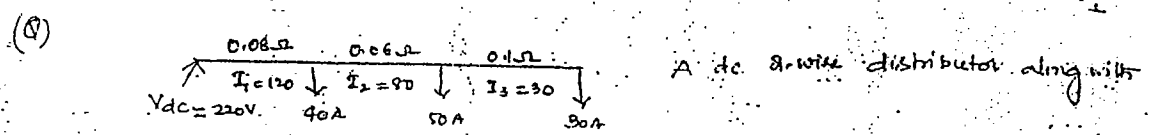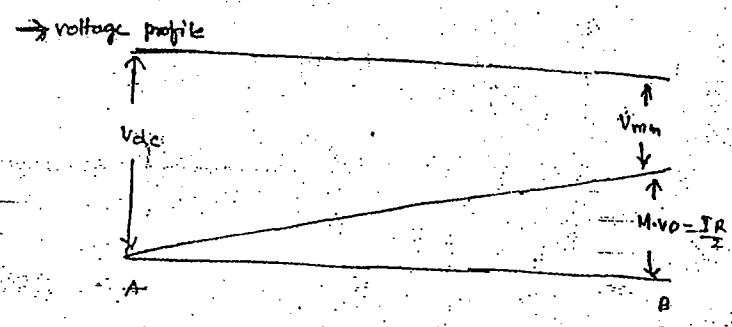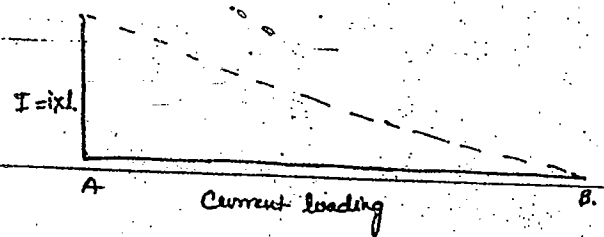
$$\text{Total power loss} = \frac{I^2 R}{3}$$




Concentrated loading is as shown above. The minimum voltage drop of the distributor in volts is

Sol

$$V_{min} = V_{dc} - (I_1 R_1 + I_2 R_2 + I_3 R_3)$$

$$= 220 - (120 \times 0.08 + 90 \times 0.06 + 30 \times 0.1)$$


$$= 202.6 \text{ volts}$$

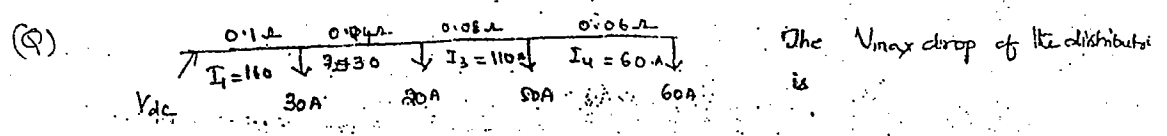

$$V_{max \text{ Drop}} = 160 \times 0.1 + 130 \times 0.04 + 110 \times 0.07 + 60 \times 0.06$$

$$= 33.6 \text{ volts}$$

(Q)

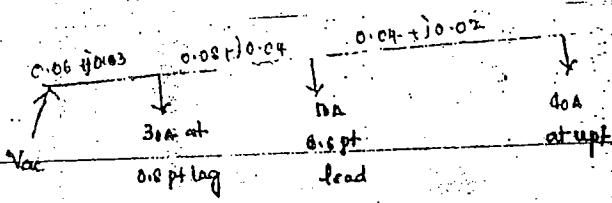

Calculate MVD of a 2-wire distributor

So

$$\text{Max Voltage drop} = I_1 \tau_1 + I_2 \tau_2 + I_3 \tau_3$$

$$I_1 = (30 \times 0.8 - j30 \times 0.6) + 50(0.6 + j50 \times 0.8 + 40)$$

$$= 24 - 18j + 30 + 40j + 40$$

$$= 94 + j22$$

$$I_2 = 30 + 40j + 40$$

$$= 70 + 40j$$


$$I_3 = 40$$

$$\text{MVD}_{ae} = (0.06 + j0.03)(94 + j22) + (70 + 40j)(0.08 + j0.04) + 40(0.04 + j0.02)$$

$$= 4.79 - j4.14 + 4 + 6j + 3.2 + j1.6$$

$$\text{MVD}_{ae} = 12.18 + j11.74$$

(Q)

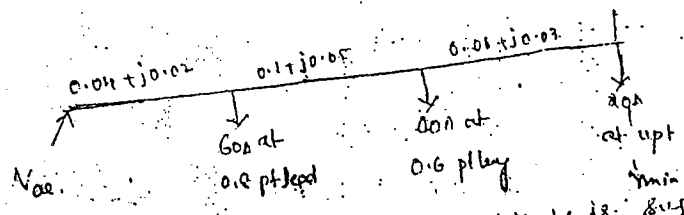

The min voltage of distributor is 220V

The voltage at which the distributor is supplying

So

$$V_{ac} = 220 + (I_1 \tau_1 + I_2 \tau_2 + I_3 \tau_3)$$

$$I_1 = (60 \times 0.8 + j60 \times 0.6) + (40 \times 0.6 - j40 \times 0.8)$$

$$= (48 + j36) + 24 - j32 + 20$$

$$I_1 = 48 + 24 + 20 + j(36 - 32)$$

Ⓠ A DC 2 WIRE DISTRIBUTOR IS HAVING A LENGTH OF 1200m. The resistance of the distributor is 0.2 Ω/km. The uniform loading of the distributor is 0.1 A/m. The max voltage drop of the distributor.

Sol

$$\begin{aligned} \text{MVD} &= \frac{I \cdot R}{2} \\ &= \frac{0.1 \times 1200 \times 0.2 \times 1.2}{2} \\ &= \frac{28.8}{2} = 14.4 \text{ V} \end{aligned}$$

Ⓠ A radial dc-wire distributor is having a uniform loading of 0.1 A/m. The length of the distributor is 800m. The resistance of each wire is $10^{-4} \Omega/\text{m}$. The distributor is fed at 220V. The min. voltage on the distributor is

Sol


$$V_{\text{min}} = V_{\text{dc}} - \text{MVD}$$

resistance of distributor = 2×10^{-4}

$$\begin{aligned} \text{MVD} &= \frac{I \cdot R}{2} \\ &= \frac{(0.1 \times 800) (2 \times 10^{-4} \times 800)}{2} \\ &= \frac{12.8}{2} = 6.4 \text{ V} \end{aligned}$$

$$V_{\text{min}} = 220 - \text{MVD}$$

$$= 220 - 6.4$$

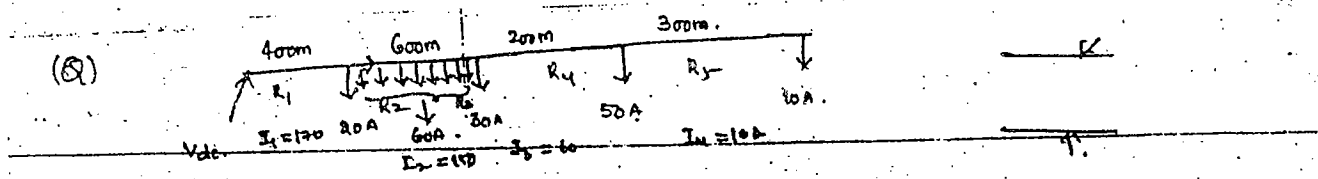

$$i = 0.1 \text{ A/m}$$

The resistance of the each wire is $1.5 \times 10^{-4} \Omega/\text{m}$. The max voltage drop of the distributor is.

Sol

$$I_1 = 20 + 30 + 50 + 10 + 60 = 170$$

$$R_1 = 2 \times 1.5 \times 10^{-4} \times 400 = 0.12$$

$$R_2 = 2 \times 1.5 \times 10^{-4} \times 600 = 0.09$$

$$R_3 = 0.09$$


$$R_4 = 2 \times 1.5 \times 10^{-4} \times 200 = 0.06$$

$$R_5 = 2 \times 10^{-4} \times 1.5 \times 300 = 0.09$$

$$\text{MVD} = 170 \times 0.12 + 150 \times 0.09 + 60 \times 0.09 + 10 \times 0.09$$

$$= 48.3 \text{ V}$$

(Q)

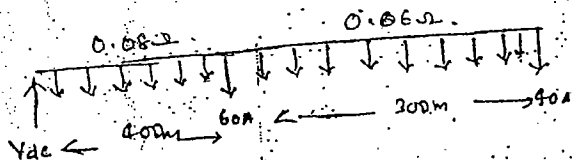

$$\text{uniform loading} = 0.1 \text{ A/m}$$

$$\text{Resistance of the distributor} = 2 \times 10^{-4} \Omega/\text{m}$$

$$\text{The length of the distributor} = 700 \text{ m}$$

MVD = ?

Sol

$$\text{MVD} = I_1 R_1 + I_2 R_2 + \frac{IR}{2}$$

$$= \frac{(170 \times 0.12) + (150 \times 0.09) + (0.1 \times 700 \times 1.5 \times 10^{-4})}{2}$$

$$= \frac{100 \times 0.08 + 40 \times 0.06 + (0.1 \times 700 \times 1.5 \times 10^{-4})}{2}$$

$$= 10.4 + 70.14$$


$$= \underline{80.54}$$

→ Disadvantages of Radial distributor fed from one end.

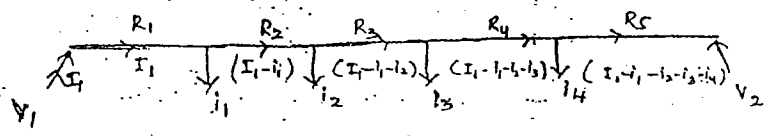- (1) It will provide low voltages for the consumers who will be far away from the source.
- (2) As it is fed from only one supply, the reliability of the scheme is less.
- (3) In effective utilization of the size of the conductor over a given length.

→ In order to overcome the disadvantages it is proposed that the distributor can be fed from both ends.

→ RADIAL DISTRIBUTOR FED FROM BOTH ENDS WITH CONCENTRATED LOADS: (DC-2 wire)



→ The minimum voltage will occur at one of the load point to which the current can be supplied by both the sources

→ To locate the minimum potential point it is required to calculate the magnitude of any one of the source current.


$$V_2 = V_1 - D_{\text{drop}}$$

$$V_2 = V_1 - [I_1 R_1 + (I_1 - I_2) R_2 + (I_1 - I_2 - I_3) R_3 + (I_1 - I_2 - I_3 - I_4) R_4 + (I_1 - I_2 - I_3 - I_4 - I_5) R_5]$$

$$V_1 [R_1 + R_2 + R_3 + R_4 + R_5] = V_1 - V_2 + I_1 R_1 + (I_1 + I_2) R_2 + (I_1 + I_2 + I_3) R_3 + (I_1 + I_2 + I_3 + I_4) R_4 + (I_1 + I_2 + I_3 + I_4) R_5$$

$$I_1 = \frac{V_1 - V_2 + I_1 R_1 + (I_1 + I_2) R_2 + (I_1 + I_2 + I_3) R_3 + (I_1 + I_2 + I_3 + I_4) R_4 + (I_1 + I_2 + I_3 + I_4) R_5}{R_1 + R_2 + R_3 + R_4 + R_5} \rightarrow \textcircled{1}$$

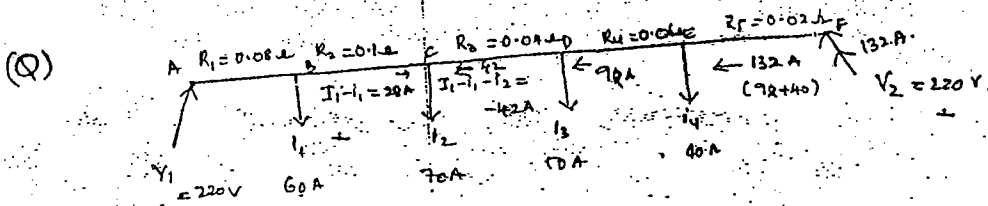eq (1) hold good for both equal & unequal voltage



The V_{min} in distributor in volts is

Sol

$$R_1 + R_2 + R_3 + R_4 + R_5 = 0.3 \Omega$$

$$I_1 = \frac{0 + 60 \times (0.1) + (80)(0.04) + (180)(0.06) + 220 \times 0.02}{0.3}$$

$$= \frac{26.4}{0.3} = 88 \text{ A}$$

$$I_1 = 88 \text{ A}$$

$$I_2 = 132 \text{ A (from fig.)}$$

$$\therefore V_{min} = V_1 - I_1 R_1$$


$$= V_2 - I_2 R_2$$

$$V_{min} = 220 - (88 \times 0.08 - 28 \times 0.1) = 210.16 \text{ V}$$


$$= 220 - (132 \times 0.06 - 92 \times 0.06 - 42 \times 0.04) = 210.16 \text{ V}$$

$$V_{min} = 210.16 \text{ V}$$


→ Current diagram

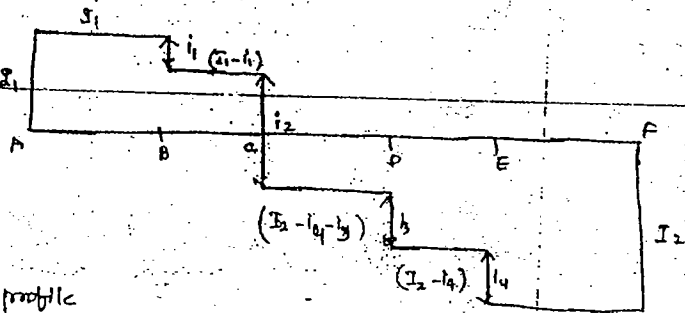

→ Voltage profile

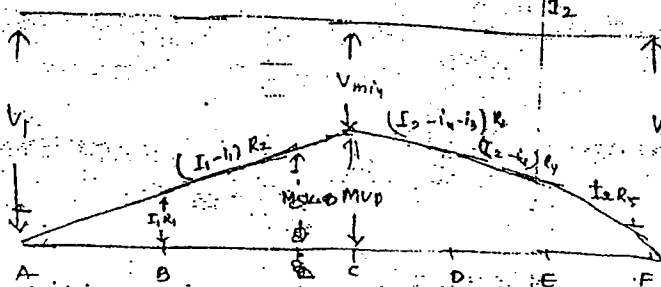

(Q)

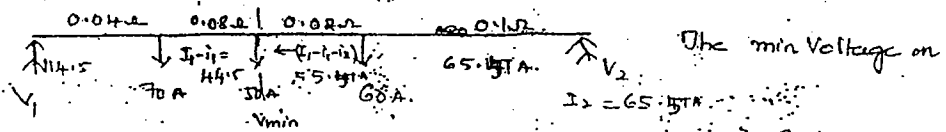

The min Voltage on the distributor is 218.5V. The distributor is fed in such way that $V_1 - V_2 = 1.5V$. The magnitude of the same voltages of the distributor i.e. $V_1 = ?$, $V_2 = ?$

Sol

$$I_1 = \frac{V_1 - V_2 + I_1 R_2 + (I_1 + i_2) R_3 + (i_1 + i_2) R_4}{R_1 + R_2 + R_3 + R_4}$$

$$= \frac{1.5 + 70(0.08) + (120 \times 0.02) + (180 \times 0.6)}{0.04 + 0.08 + 0.02}$$

$$= \frac{27.5}{0.14}$$

$$= 114.58 A$$

$$I_2 = 65.5 A$$

$$V_{min} = 218.5 = V_1 - M.V.D$$



$$V_2 = V_{min} + V.P$$

$$V_1 = 218.5 + (114.5 \times 0.04) + (44.5 \times 0.08)$$

$$= \underline{226.64 \text{ V}}$$

$$V_2 = 218.5 + (65.5 \times 0.1) + (5.5 \times 0.02)$$

$$= \underline{225.14 \text{ V}}$$

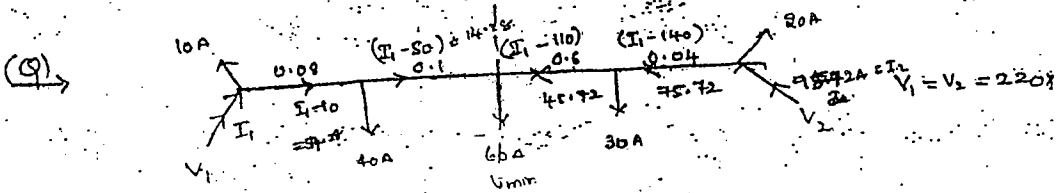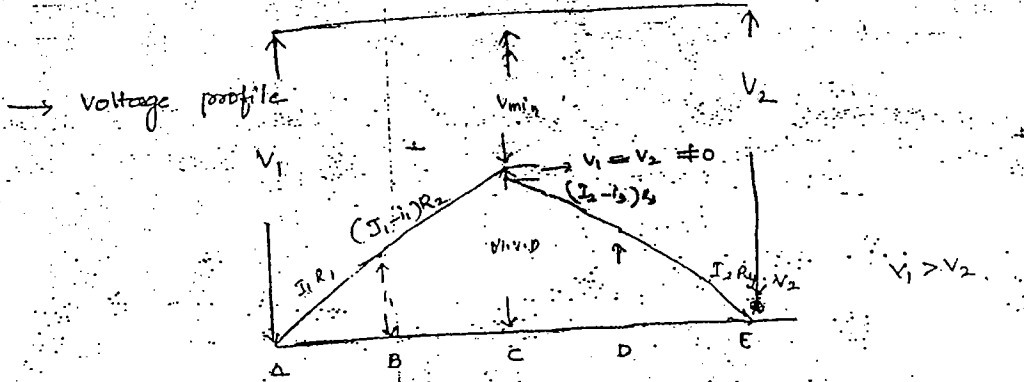

The min voltage of the distributor is

Sol

$$V_1 - V_2 = \text{Drop}$$

$$(I_1 - 10) \times 0.08 + (I_1 - 50) \times 0.1 + (I_1 - 110) \times 0.06 + (I_1 - 140) \times 0.04 = 0$$

$$\Rightarrow I_1 [0.08 + 0.1 + 0.06 + 0.04] = 10 \times 0.08 + 50 \times 0.1 + 110 \times 0.06 + 140 \times 0.04$$

$$\Rightarrow I_1 = \frac{18}{0.28}$$


$$I_1 = 64.28 \text{ A}$$

$$V_{min} = 220 - \frac{(1-10)}{(54.28 \times 0.08 + 14.28 \times 0.1)}$$

$$= 220 - \frac{(1-10)}{(75.22 \times 0.04 + 14.28 \times 0.06)}$$

$$= 214.42 \text{ V}$$

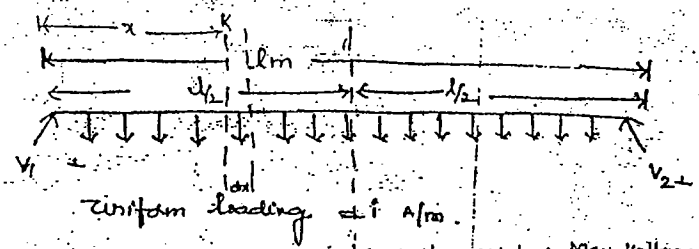→ DC-WIRE RADIAL DISTRIBUTOR FED FROM BOTH ENDS WITH UNIFORM LOADING



Resistance of the distributor = $\pi \Omega/m$ l = distance of wire in m.
 Min voltage point Max voltage drop = $\frac{IR}{8}$

Case (i) Equal voltages

→ If $V_1 = V_2$ then the minimum potential will get exactly at the middle of the distributor. So that the distributor is symmetric on both sides with respect to the middle of the distributor.

Drop in the 'dx' = $(i \cdot x \cdot \frac{1}{2}) - (i \cdot x) \cdot \pi dx$

Drop up to 'x' = $\int_0^x (i \cdot \frac{1}{2} - i \cdot \pi) \pi dx$

$$= i \pi \int_0^x (\frac{1}{2} - x) dx$$

$$= i \pi \left[\frac{1}{2}x - \frac{x^2}{2} \right]_0^x$$

$$= i \pi \left[\frac{1}{2}x - \frac{x^2}{2} \right]$$

Max Voltage drop will be at $x = \frac{1}{2}$

$$= i \pi \left[\frac{1}{2} \cdot \frac{1}{2} - \frac{1}{2} \left(\frac{1}{2} \right)^2 \right]$$

$$= i \pi \left[\frac{1}{4} - \frac{1}{8} \right]$$

Max Voltage drop = $i \pi \left[\frac{1}{8} \right] = \frac{(i \pi) (\pi x l)}{8} = \frac{I \cdot R}{8}$

$$\text{Total power loss} = \frac{I^2 R}{2}$$

→ The maximum voltage drop and the total power loss of a radial distributor fed from both the ends having uniform loading will be $\frac{1}{4}$ th to that of the max. voltage drop and the total power loss of a radial distributor fed from one end.

$$M.V.D = \frac{1}{4} \left(\frac{I \cdot R}{2} \right), \quad P. \text{ loss} = \frac{1}{4} \left(\frac{I^2 R}{2} \right)$$

(Q) A dc 2 wire radial distributor fed from both ends with equal voltages of 220V. The uniform loading is 0.1 A/m and resistance of each wire is 0.1 Ω /km. The length of the distributor is 1600m. The min voltage of the distributor is.

Sol

$$V_{\min} = V_1 - \text{Drop} \\ = V_2 - \text{Drop}$$

$$V_{\min} = 220 - \frac{(I \cdot R)}{8}$$

$$= 220 - \frac{(0.1 \times 1600) (2 \times 0.1 \times 1.6)}{8}$$

(Q) The max voltage drop and the total power loss of a radial distributor fed from both the ends having uniform loading is 2.5V and 5W. The max voltage drop and the total power loss of radial distributor fed from one end with uniform loading is.

Sol

$$\frac{I R}{8} = 2.5V$$

$$\frac{I^2 R}{16} = 5W$$


→ both ends

$$\rightarrow \frac{IA}{2} = 2.5 \times 4 = 10V$$

$$\rightarrow \frac{IA^2}{2} = 5 \times 4 = 20W$$

} on = end.

Calc (ii) Unequal voltages:

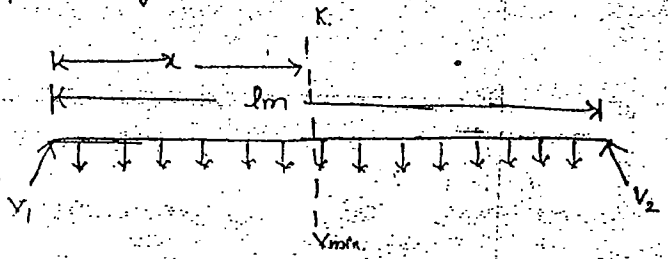

uniform loading = i A/m

Resistance of distributor = r Ω /m

$$V_1 \neq V_2$$

→ In order to locate the minimum potential point can be assumed at point K' having a distance x' from any one of the source.

$$V_{min} = V_1 - \text{Drop}$$

(or)

$$V_{min} = V_2 - \text{Drop}$$

$$V_1 - i r \frac{x^2}{2} = V_2 - i r \frac{(l-x)^2}{2}$$

$$= V_2 - i r \frac{(l^2 + x^2 - 2lx)}{2}$$

$$V_1 - \frac{i r x^2}{2} = V_2 - \frac{i r l^2}{2} - \frac{i r x^2}{2} + i r l x$$

$$V_1 = V_2 - \frac{i r l^2}{2} + i r l x$$

$$i r l x = V_1 - V_2 + \frac{i r l^2}{2}$$

$$x = \frac{V_1 - V_2}{i r l} + \frac{l}{2}$$



$$x = \frac{V_1 - V_2}{i r l} + \frac{l}{2}$$

9/2/2019

RING MAIN DISTRIBUTOR:

It consists of one or more sources and form a closed circuit(s) loop

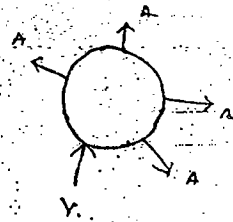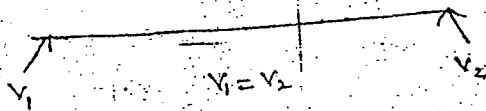- Radial distributor fed from both ends with equal voltages can also be treated as ring main distributor with single equivalent source.




(Q) The minimum voltage of the distributor is 215 V. The magnitude of the source voltage.

Sol

In order to locate the minimum voltage point consider the sum

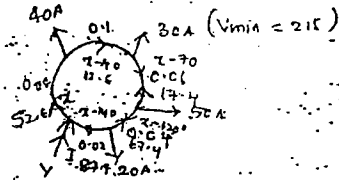of the voltage drop in the distributor will be zero.



$$x \times 0.08 + (x - 40) \times 0.1 + (x - 70) \times 0.06 + (x - 120) \times 0.04 + (x - 140) \times 0.02 = 0$$


$$x = \frac{40 \times 0.1 + 70 \times 0.06 + 120 \times 0.04 + 140 \times 0.02}{0.08 + 0.1 + 0.06 + 0.04 + 0.02}$$

$$= \frac{132}{0.3} = 52.6A$$


$$V = 215 + 12.6 \times 0.1 + 52.6 \times 0.08$$

$$= 215 + 5.468$$

$$= 220.468V$$

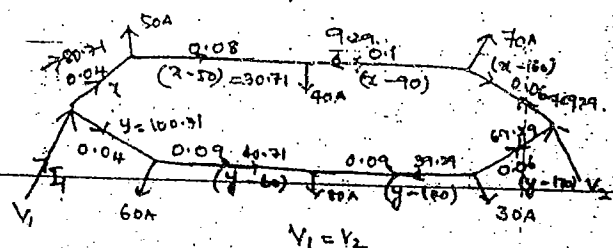

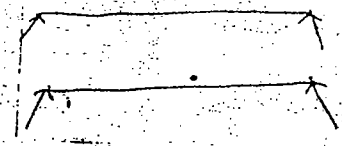(Q) $V_1 = V_2 = 220V$
 Calculate the minimum voltage of the distributor.



→ If the ring main distributor is fed from n sources then it will be resolved as n -radial distributors fed from both ends so that it consists of n minimum voltages.

$$x \times 0.04 + (x-50) \times 0.08 + (x-90) \times 0.1 + (x-160) \times 0.06 = 0$$

$$x = \frac{50 \times 0.08 + 90 \times 0.1 + 160 \times 0.06}{0.04 + 0.08 + 0.1 + 0.06} = \frac{22.6}{0.28} = 80.71A$$


$$y \times 0.04 + (y-60) \times 0.09 + (y-140) \times 0.09 + (y-190) \times 0.05 = 0$$

$$y = \frac{60 \times 0.09 + 140 \times 0.09 + 190 \times 0.05}{0.04 + 0.09 + 0.09 + 0.05} = \frac{28.2}{0.27} = 104.44A$$

$$V_{min} = 220 - 80.71 \times 0.04 - 30.71 \times 0.08 = 214.32V$$

$$220 - 104.44 \times 0.04 - 40.71 \times 0.09 = 212.307V$$

(Q)

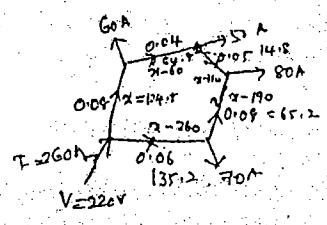

The new voltage of the distributor

So


$$x = \frac{60 \times 0.04 + 110 \times 0.05 + 190 \times 0.05 + 260 \times 0.06}{0.04 + 0.05 + 0.05 + 0.06} = \frac{47}{0.2} = 235A$$

$$V_{min} = 220 - 135.2 \times 0.06 - 65.2 \times 0.08$$

$$= 206.67 \text{ V}$$

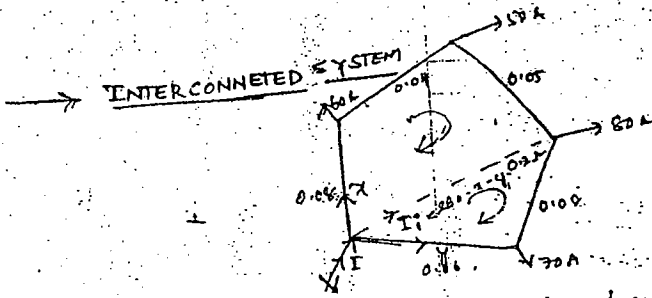(6)

$$V_{min} = 220 - (124.8 \times 0.08 + 64.8 \times 0.04 + 14.8 \times 0.05)$$



If a ring main distributor is having only one source then there is a possibility to have a low voltage at the minimum potential and in order to increase the min. potential voltage, it is proposed to have an interconnector between the source and the minimum potential point so that certain amount of current will be carried out by the interconnector directly to the min. potential point which will reduce the magnitude of the current in the distributor so that the voltage drops will be reduced.


→ In general the size of the interconnector will be 50% to that of the size of the original distributor.

$$= 2 \times 0.08 - (x-60) \times 0.04 + (x-110) \times 0.05 - (260-x-y) \times 0.05$$

$$x(0.08 + 0.04 + 0.05 + 0.05) = \frac{60 \times 0.04}{2.14} + \frac{110 \times 0.05}{50} - 50 + 0.2y$$

$$0.37x - 0.2y + 97.1 = 0$$

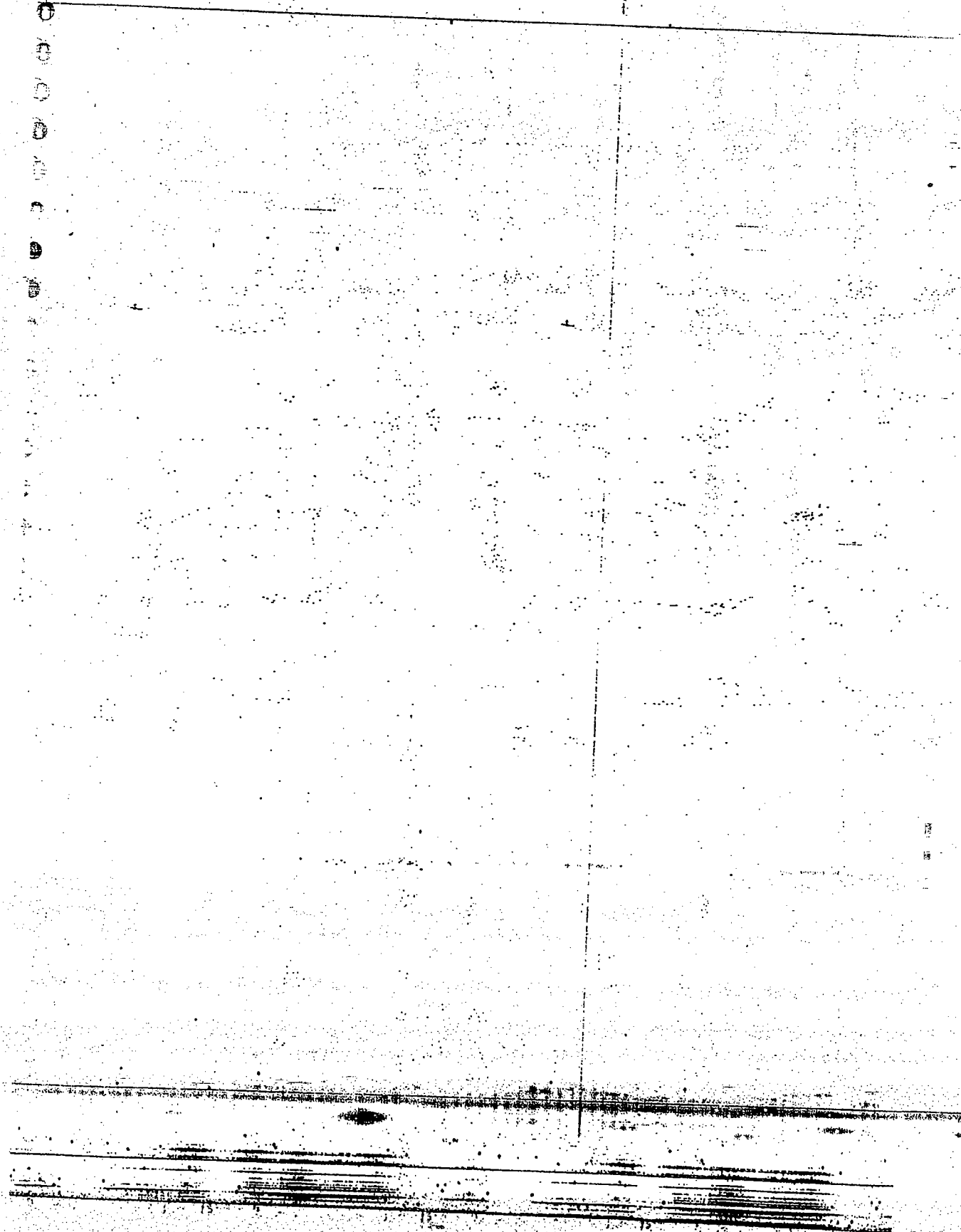
$$260 - x - y - (y - 70) 0.08 - y \times 0.06 = 0.$$



→ PER UNIT SYSTEM, SYMMETRICAL COMPONENTS AND FAULT ANALYSIS.

→ The fault analysis on the existing system can be carried out by using symmetrical components and they are expressed in per-unit values.

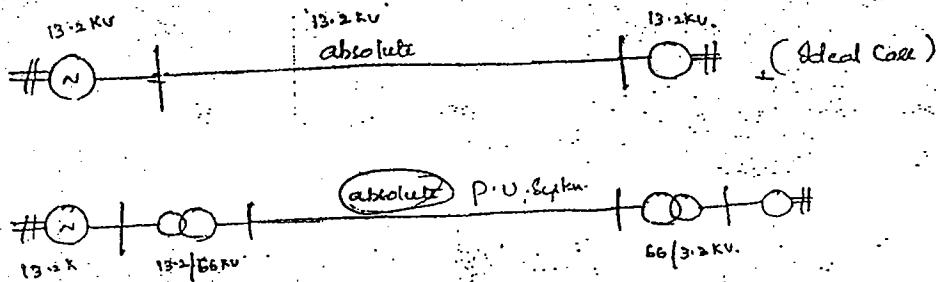→ Electrical quantities
 / absolute — associated with units
 / per-unit — doesn't associated with units



ABSOLUTE SYSTEM


1. If the given single line diagram is dealing with more than one operating voltage then the above single line diagram can be represented electrically with more than one electrical n/w so that there are more than one n/w equation to be solved. Hence the time taking is high, in order to analyse the performance of the single line diagram.

2. The absolute impedance of the t/t in primary and secondary are not same so that it will be represented electrically as two elements.

PER UNIT SYSTEM

1. The given single line diagram is dealing with more than one operating voltage then the above single line diagram can be represented electrically with only one network. Hence there is only one n/w equation to be solved. Hence the time taking is less in order to analyse the performance of the given single line diagram.

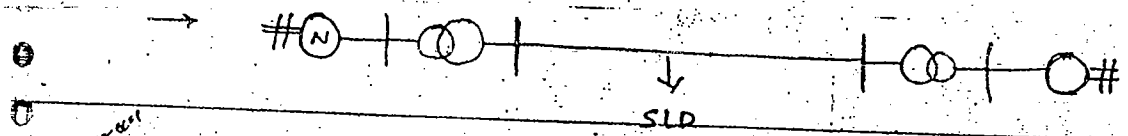2. In the per-unit system the impedance of the transformer will be same either on primary or secondary. So it can be represented electrically as a single element only.








SLD
 ↓
 Electrical Simulation
 (or)
 Machine Modelling (Electrically)






→ In the p.u. system, the given single line diagram can be represented as an electrical simulation diagram in a phase manner under the assumption of the load is balanced.


Ex: Syn machine → Voltage source in series with Impedance [Reactance]
 T/f, Tr-line and Induction motors → Imp [Reactance]

SLD

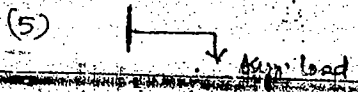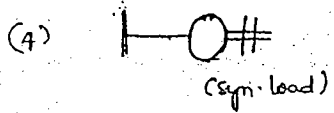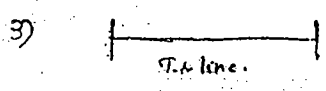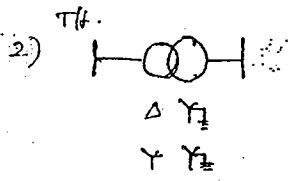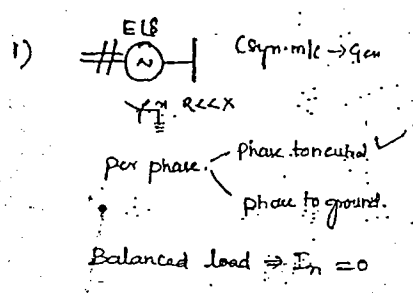

SIMULATION

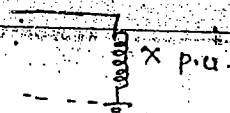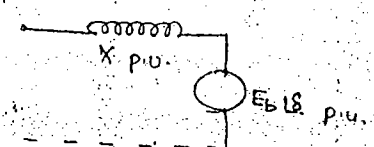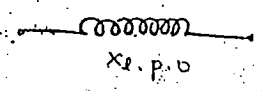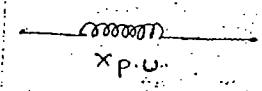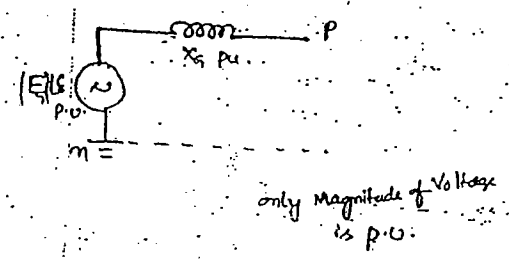

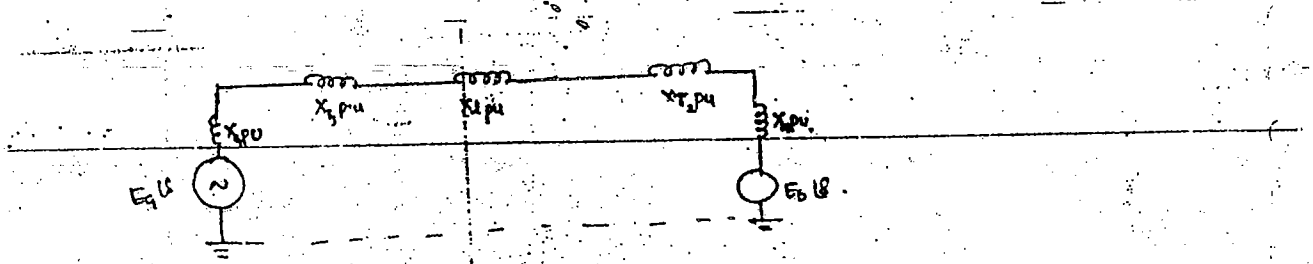

Simulation diagram for SLD

The above simulation diagram is having the voltage and the reactances. These values need to be represented in p.u. manner. It is very easy to represent the voltage in p.u. because the voltage is one of the ratings, however a mathematical equation to be developed to represent the reactance in per cent in terms of the ratings of the equipment i.e.

- (1) Voltage & Current (or) Voltage and its capacity in V.A.

→ PER UNIT QUANTITY (OR) VALUE:

$$\text{P.U. Value} = \frac{\text{Actual (or) absolute quantity in the unit}}{\text{Base or reference quantity in the same unit}}$$

→ The magnitude of the p.u. quantity does depend on the Base value and the selection of the Base value is optional.

Ex:		absolute	P.U.	absolute	P.U.
Gen-1		V_1	$V_1 \text{ p.u.} = \frac{V_1}{V_{sb}}$	I_1	$I_1 \text{ p.u.} = \frac{I_1}{I_{sb}}$
Gen-2		$(V_2)_b$	$V_2 \text{ p.u.} = \frac{V_2}{V_{sb}}$	$(I_2)_b$	$I_2 \text{ p.u.} = \frac{I_2}{I_{sb}}$

← same m/c →

In addition to the voltage, if the equipment is rated internally of current

select the current base from the same m/c if it is dealing with more than one electrical quantity at the rating.

absolute

P.U

$$X_1 = \frac{V_1}{I_1}$$

$$X_{1 P.U} = \frac{X_{1 \Omega}}{X_{2b}} = \frac{X_{1 \Omega}}{\frac{V_{2b}}{I_{2b}}} = X_{1 \Omega} \cdot \frac{I_{2b}}{V_{2b}} \quad \left| \frac{V_{2b}}{I_{2b}} = X_{2 \Omega} \right.$$

$$X_2 = \frac{V_2}{I_2}$$

$$X_{2 P.U} = \frac{X_{2 \Omega}}{X_{2b}} = \frac{X_{2 \Omega}}{\frac{V_{2b}}{I_{2b}}} = X_{2 \Omega} \cdot \frac{I_{2b}}{V_{2b}}$$

The ratio of two base values will give another base value but it will have a different unit.

∴ In general,
$$X_{P.U.} = X_{\Omega} \frac{I_b}{V_b} \quad \text{--- (1)}$$

if the equipment is having the rating in terms of the voltage and current.

However most of the equipments have their rating in terms of voltage and its capacity in volt Amperic rather than voltage & current

absolute

P.U. (X)

$$\frac{VA_1}{(VA_2)_b}$$

$$X_{1 P.U} = X_{1 \Omega} \cdot \frac{I_{2b}}{V_{2b}} = X_{1 \Omega} \cdot \frac{VA_{2b}}{V_{2b}^2} = X_{1 \Omega} \cdot \frac{VA_{2b}}{(V_b)^2} \quad \left| \frac{VA_{2b}}{V_{2b}^2} = \frac{VA_{2b}}{(V_b)^2} \right. = I_2(b) A$$

$$X_{2 P.U} = X_{2 \Omega} \cdot \frac{I_{2b}}{V_{2b}} = X_{2 \Omega} \cdot \frac{VA_{2b}}{V_{2b}^2} = X_{2 \Omega} \cdot \frac{VA_{2b}}{(V_b)^2}$$

∴ In General.

$$X_{P.U} = X_{\Omega} \frac{VA_b}{(V_b)^2} = X_{\Omega} \cdot \frac{VA_b}{10^6 \left(\frac{V_b}{10^3}\right)^2}$$

$$X_{P.U} = X_{\Omega} \frac{MVA_b}{(KV_b)^2} \quad \text{--- (2)}$$

illy

$$Z_{P.U} = Z_{\Omega} \frac{MVA_b}{(KV_b)^2}$$

The p.u. Impedance/reactance is directly proportional to its capacity and inversely proportional to square of the operating voltage.

Phase Value: $X_{p.u} \times 100 = \%$
 $X_{p.u} \times 100 = \%$

3- ϕ 3-W
 MVA - 3- ϕ but "X" in phase
 KV - 1- ϕ

(Q) Alternator rated at 6.6 KV, 5 MVA and $X = 5 \Omega$

$$X_{p.u} = 5 \times \frac{5}{(6.6)^2}$$

(Q) Alternator rated at 11 KV, 100 MVA having $X = 2.0 p.u.$ The p.u reactance of the alternator for the rating of 200 MVA, 13.2 KV is

$$X_{p.u. New} = X_{p.u. old} \times \frac{MVA_{new}}{MVA_{old}} \times \left(\frac{KV_{old}}{KV_{new}} \right)^2$$

$$= 2 \times \frac{200}{100} \times \left(\frac{11}{13.2} \right)^2$$

$$= 2$$

lly

$$X_{p.u. New} = X_{p.u. old} \times \frac{MVA_{new}}{MVA_{old}} \times \left(\frac{KV_{old}}{KV_{new}} \right)^2$$

(Q) What is the p.u reactance if the capacity & voltage are double.

$$X_{p.u. (new)} = 1 \times \frac{2}{1} \left(\frac{1}{2} \right)^2 = \frac{1}{2}$$


(Q) capacity $\frac{1}{2}$, voltage $= \frac{1}{2}$ $X_{p.u} = ?$

$$X_{p.u. (new)} = 1 \times \frac{1/2}{1} \times \left(\frac{1/2}{1} \right)^2 = 2 p.u. \text{ or } 200\%$$


(Q) Capacity $= \frac{1}{4}$ Voltage $= 4$ times $X_{p.u} = ?$

$$X_{p.u. (new)} = 1 \times \frac{1/4}{1} \times \left(\frac{4}{1} \right)^2 = 4 p.u. = 400\%$$


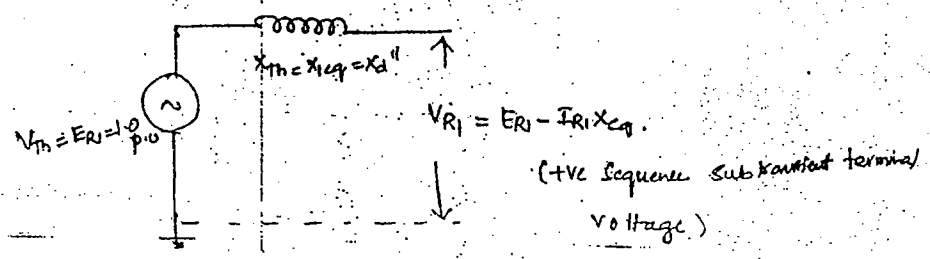
to loaded alternator. Hence, the fault analysis can be carried out generally on a no load system rather than loaded system.




+ve Sequence sub-transient network.

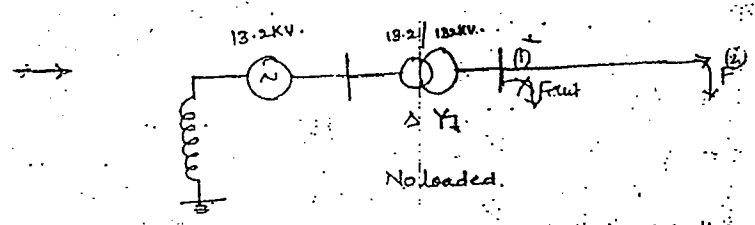

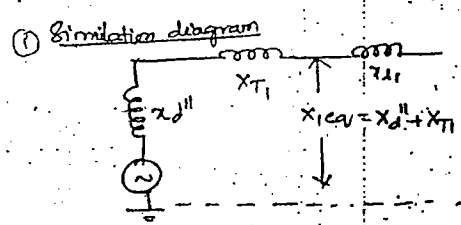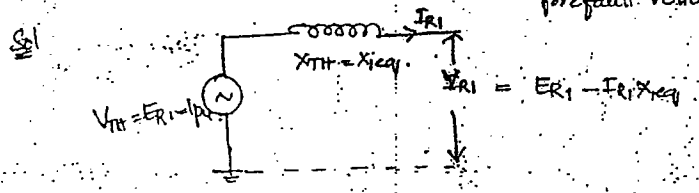
prefault voltage $V_{th} = E_{R1} = 1.0 \rightarrow \left(\frac{132 \text{ k}}{132 \text{ F}} \right)$






② $X_{eq} = X_{d''} + X_{T1} + X_{L1}$




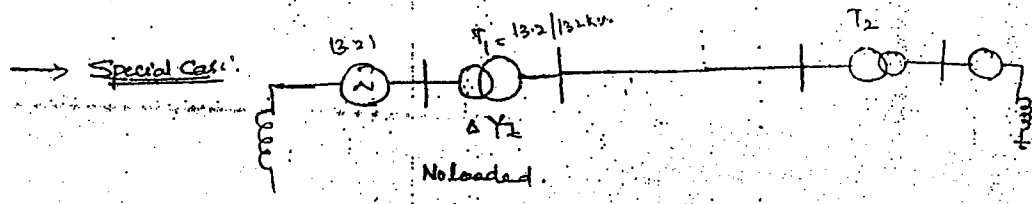


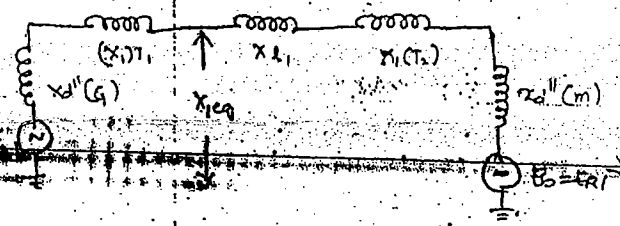Since, two active sources are both sides.



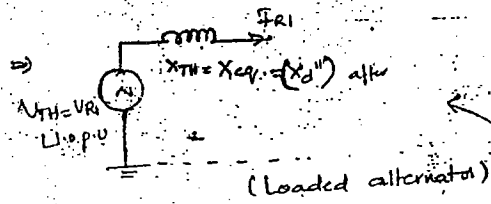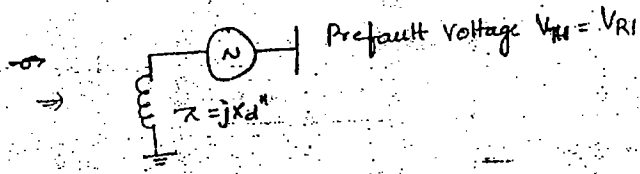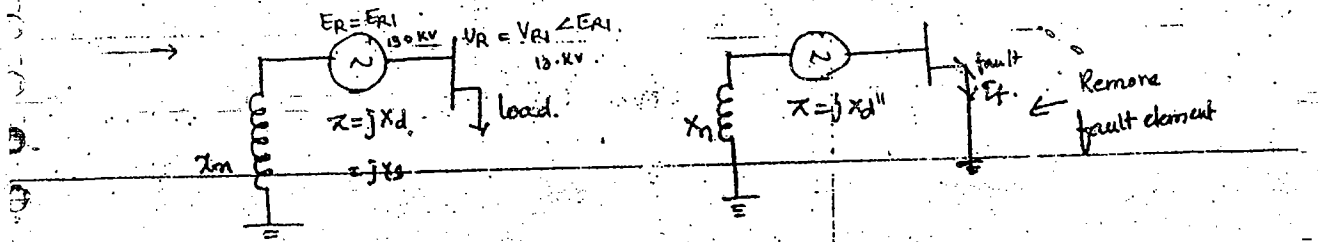

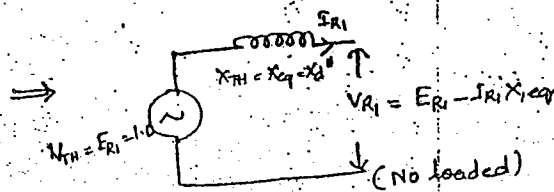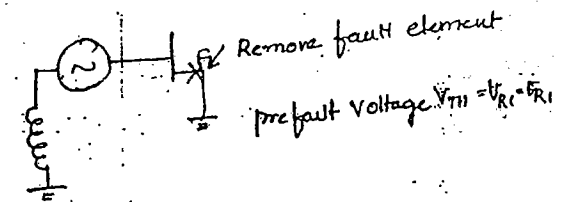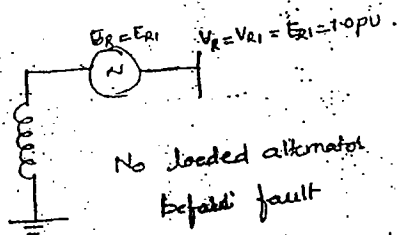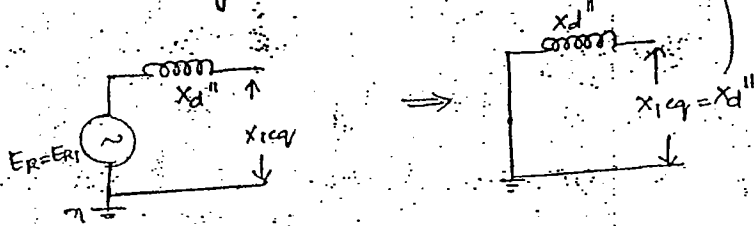→ In order to evaluate reactance w.r.t. fault point, draw the simulation diagram for the given SLD



There is no change in the equivalent reactance if the alternator is working under no load condition (or) loaded condition, however pre-fault voltages are different. In case of no loaded alternator the +ve sequence subtransient current delivered will be high compared

→ The Sequence Components are associated with their Sequence Networks!



(*) Subtransient Imp/Reactance m/w's

Balanced Components → per-phase.

→ In case of +ve and -ve sequence m/w's the reference is neutral where as in case of Zero sequence m/w's the reference is ground.

So include the neutral grounding effect ^{while} by drawing the Zero Sequence

and ignore the neutral grounding effect while drawing +ve & -ve sequence m/w's

$$I_m = I_R + I_B + I_G = 0 \quad \text{Balanced System}$$

$$\neq 0 \quad \text{Unbalanced System}$$

$$I_m = I_{R0} + I_{R1} + I_{R2} + I_{Y0} + I_{Y1} + I_{Y2} + I_{B0} + I_{B1} + I_{B2}$$

$$= I_{R0} + I_{R1} + I_{R2} + I_{R0} + K^2 I_{R1} + K I_{R2} + I_{R0} + K I_{R1} + K^2 I_{R2}$$

$$= 3I_{R0} + I_{R1}(1+K^2+K) + I_{R2}(1+K+K^2)$$

$$= 3I_{R0} + 0 + 0$$

$$\boxed{I_m = 3I_{R0}} \quad \Leftrightarrow \quad \text{So}$$


→ SEQUENCE NETWORKS:

→ Any sequence network consists of prefault voltage at the fault point in series with equivalent subtransient reactance which is evaluated with respect to fault point by replacing all the active sources with their internal reactances.

→ The sequence m/w's are also called as an electrical equivalent of Thevenin's theorem.

→ The single line diagram of the power system m/w may consist of ~~active sources~~ ^{active sources} because of the symmetry and they can be replaced as short circuit while evaluating equivalent reactance.

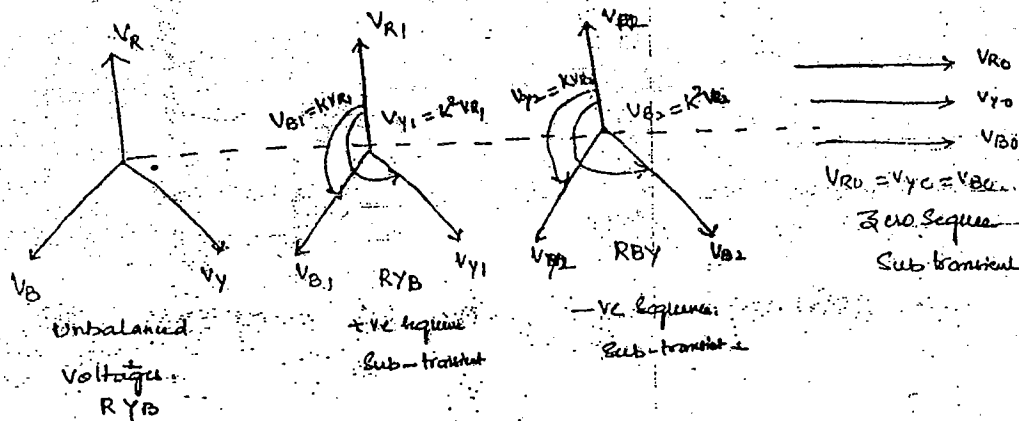→ From the above, we can understand that the $\overset{\ominus}{+ve}$ and $\overset{\ominus}{-ve}$ sequence components are referred to the phase where as the zero sequence components are referred to the ground.



$$\begin{aligned}
 V_R &= V_{R0} + V_{R1} + V_{R2} \\
 V_Y &= V_{R0} + K^2 V_{R1} + K V_{R2} \\
 V_B &= V_{R0} + K V_{R1} + K^2 V_{R2}
 \end{aligned}
 \Rightarrow
 \begin{bmatrix} V_R \\ V_Y \\ V_B \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & K^2 & K \\ 1 & K & K^2 \end{bmatrix} \begin{bmatrix} V_{R0} \\ V_{R1} \\ V_{R2} \end{bmatrix}$$

$$\begin{bmatrix} I_R \\ I_Y \\ I_B \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & K^2 & K \\ 1 & K & K^2 \end{bmatrix} \begin{bmatrix} I_{R0} \\ I_{R1} \\ I_{R2} \end{bmatrix} \Rightarrow \begin{bmatrix} I_{R0} \\ I_{R1} \\ I_{R2} \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & K^2 & K \\ 1 & K & K^2 \end{bmatrix}^{-1} \begin{bmatrix} I_R \\ I_Y \\ I_B \end{bmatrix}$$

Unknown unbalanced

Known balanced Sequence Components

$A^{-1} = \frac{Adj A}{\det A}$

$$\begin{bmatrix} I_{R0} \\ I_{R1} \\ I_{R2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & K & K^2 \\ 1 & K^2 & K \end{bmatrix} \begin{bmatrix} I_R \\ I_Y \\ I_B \end{bmatrix}$$

Unknown

Known

Ex:

Solid



Hollow



Stranded



$m=1$

(Counts Surface)

* $\rightarrow p$ less
 \rightarrow Better Conductor


$m=1$

(Surface)

$\rightarrow p$ is least

m is less than one, $V_d \downarrow$

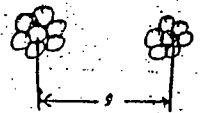\Rightarrow Corona is high.
 $\rightarrow p$ is high



Self GMD

* Coronas

Hollow < Solid < Stranded


$\uparrow V_d \propto \text{Self GMD} \uparrow$

$V_d \propto m \times$

$\therefore p \downarrow$

\rightarrow For the same amount of current, the radius of the hollow conductor will be slightly high when compared to solid, hence V_d is high and Corona loss is less.

DISTRIBUTION SYSTEM

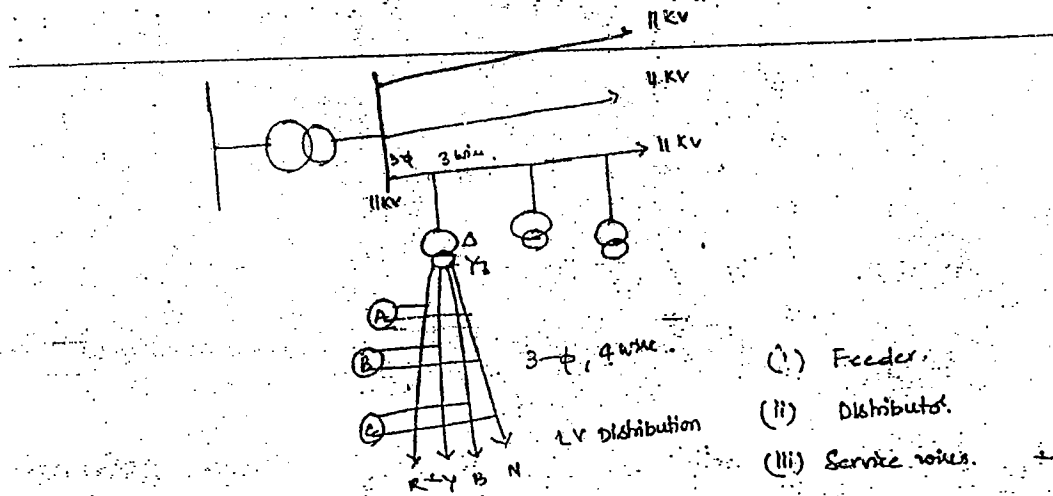

— Feeder is rarely used in distribution.

→ A Feeder is the one in which the magnitude of the current throughout the length is same and in distribution system it is very rarely used.

→ Distributor is an element in which the magnitude of current varies throughout its length and in distribution system it is the most common word.

— The selection of the size of the conductor for distributor is based on voltage drop, and if the operating voltage is increased by n times then the area of c/s of distributor will reduce by $\frac{1}{n^2}$ times.

→ A Service wires are the completely insulated wires and they can connect the distributor to the consumer terminals.

→ The guard ring will protect the string of the insulator against direct lightning stroke in which the peak magnitude of the lightning surge will be discharged to the ground from the guard ring through the cross arm.




CONCEPT OF CORONA


→ The ionisation of insulating material (air) near the surface of the power conductor at certain points is called as CORONA.
(OR)

→ The complete disruption of the dielectric strength of air near the surface of the power conductor at certain point is called as CORONA.

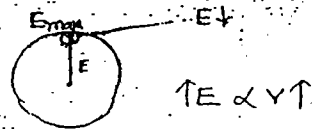→ Because of radioactivity in the space there are certain free electrons which are scattered.



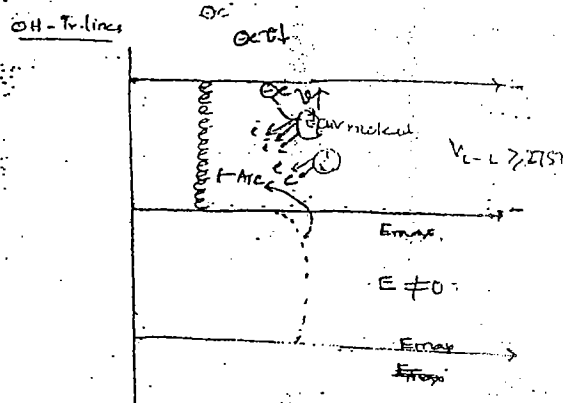$v \rightarrow$ mobility of the electron.



→ As the operating voltage between the two conductors will increase then the electric field intensity at the surface of the conductor will increase which in turn will increase the mobility of the electron near the surface of the conductor.

→ When the operating voltage b/w the two conductor has become $> 275kV$ there will be huge electric field intensity at the surface of the conductor, so that the mobility of electron is very high and it will collide with any air molecules so that some


Electrons can be released from these molecules.
 → The released electrons will further collide with the other air molecules so that few more electrons are released and it will be continuous and after certain time, there will be an electron avalanche will take place i.e., the distance b/w the two conductors is having high electron density and finally it will lead to the occurrence of the arc b/w the two conductors.

— Arc is an ionized body. So that it will be treated as L-L fault.

→ There fore the reliability of the supply is reduced.

→ In order to eliminate the occurrence of the arc at higher and higher operating voltages, then the tr. line is designed in such a way that the $(\frac{d}{r})$ ratio > 15 .
 (d → dia b/w spans, r → rad of conductor)

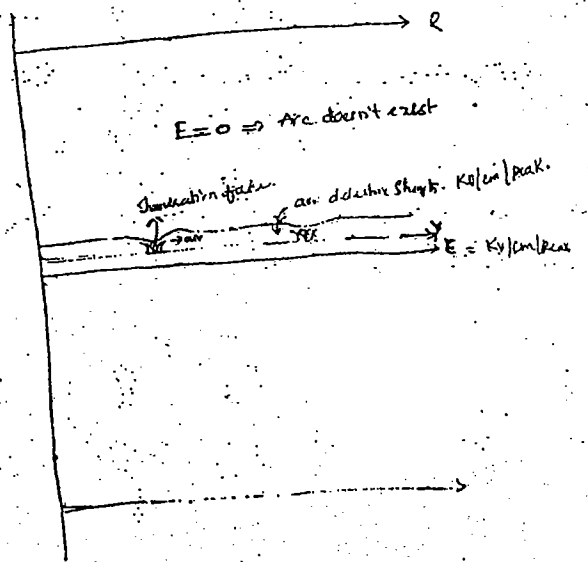
→ Even though the arc can be eliminated but there is a possibility to get the ionization of air near the surface of the power conductor, at certain locations, because in those locations, the electric strength of air is expected to be less than the electric field intensity.



→ The voltage at which the ionization of air takes place is called as CRITICAL DISRUPTIVE VOLTAGE (V_d)

→ The ionisation of the air is the field intensified ionisation at certain locations.

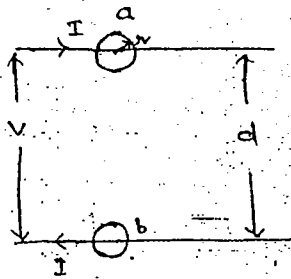→ Critical Disruptive Voltage (V_d): (1- ϕ , 2-wire outl)



$$E_{max} = \frac{V}{\pi \ln(d/r)}$$

$$V = \frac{E_{max} \pi \ln(d/r)}{\sqrt{2}} \text{ KV/rms}$$

g_0 = Dielectric strength of air KV/cm/peak.

$$V_d = g_0 \pi \ln(d/r) \text{ KV/rms}$$

$g_0 = 30 \text{ KV/cm/peak}$ at NTP $\Rightarrow 25^\circ\text{C}$ and 76 cm Hg.

$$\Rightarrow g_0 = \frac{30}{\sqrt{2}} = 21.2 \text{ KV/cm/rms at NTP}$$

$$\therefore V_d = 21.2 \pi \ln(d/r) \text{ KV/rms}$$

→ In a practical case it is difficult to maintain NTP. So at any temperature and pressure the critical disruptive voltage " V_d "

$$V_d = g' \pi \ln(d/r) \text{ KV/rms}$$

g' = dielectric strength of air at any temperature & pressure.

$$g' = g_0 \cdot \delta$$

$\delta \rightarrow$ Air density factor (less than 1)

$$\delta = \frac{3.92 \times h}{273 + t} < 1; \text{ h = actual pressure in cm of Hg.}$$

t = actual temp in $^\circ\text{C}$

$$\Rightarrow g' < g_0$$

$$V_d = 21.1 \delta \pi \ln(d/r) \text{ KV/nms.}$$

Consider the surface irregularity factor m

$$V_d = 21.1 \delta m \pi \ln(d/r) \text{ KV/nms.} \rightarrow \text{Calculated Value.}$$

$\rightarrow m = 1 \rightarrow$ of surface is smooth (solid conductor)


$\rightarrow m = 0.98 - 0.98 \rightarrow$ For rough surface (stranded conductor)

$\rightarrow m = 0.83 - 0.87 \rightarrow$ Underground Cable

\rightarrow In Underground cables, there is a possibility for the ionisation of the insulating material at higher operating voltage due to the temperature gradient.

$$V_d \propto \delta, m, \pi, \ln(d)$$

\rightarrow In order to avoid the ionisation of the air, then the calculated critical disruptive voltage must be more than the operating voltage of the transmission system, for which the transmission line is designed with maximum distance of separation. However due to bad weather conditions which are prevailed in the atmosphere, the calculated critical disruptive voltage is appears to be less than the operating voltage so that the corona will be initiated.

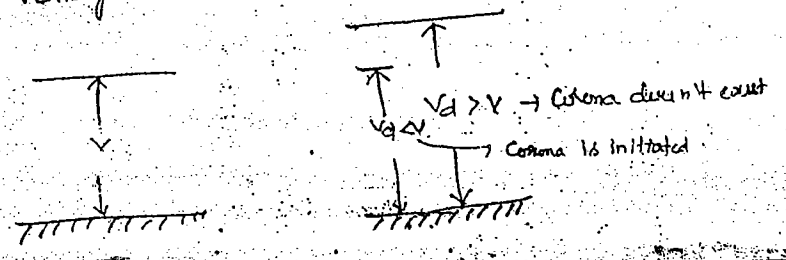

For 3- ϕ OHTL

$$V_d = 21.1 \delta m \pi \ln \left(\frac{GMD}{r} \right) \text{ KV/line/phase}$$

$GMD = \sqrt[3]{x_{12} x_{23} x_{31}}$ \rightarrow Unsymmetrical Configuration


$GMD = d$ \rightarrow Symmetrical Configuration

For Bundle conductors (α) double circuit:

$$V_d = 21.1 \delta m \alpha \pi \ln \left(\frac{GMD}{\text{Self GMD}} \right) \text{ KV/line/phase.}$$


\rightarrow Identification of the initiation of Corona on tr. line:

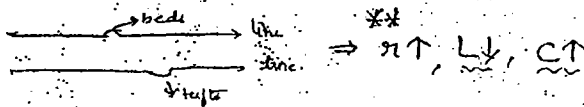- (1) Occurrence of hissing noise
- (2) Releasing of ozone gas
- (3) Occurrence of beads and tufts at certain locations which can be seen through a "stroboscope"



8/2/10

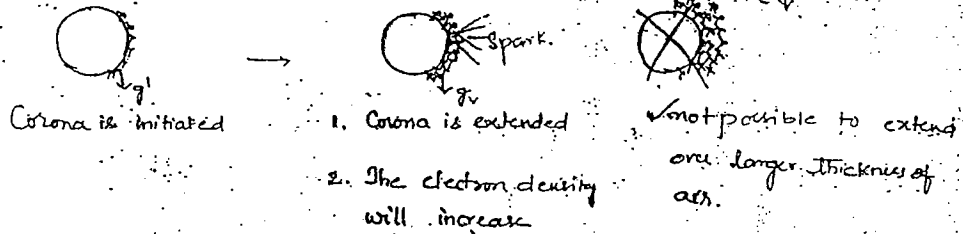\rightarrow VISUAL CRITICAL DISRUPTIVE VOLTAGE:



\rightarrow As the Corona is initiated then it will be extended near the surface of the conductor over a smaller thickness of the air. So that the density will increase. The increased electron density will result as the occurrence of the spark near the surface of the conductor in the form of WHITE BLuish GLOW COLOUR and the voltage which corresponding to the occurrence of the spark is called as VISUAL CRITICAL DISRUPTIVE VOLTAGE.

$$V_v = g_v m \pi \ln(d/r) \text{ KV/rms.}$$

→ The occurrence of the spark will take place if there is a gradient for the dielectric strength of air between the occurrence of the spark and the corona is initiated.

$$g_v = g' \left(1 + \frac{0.3}{\sqrt{rS}}\right)$$

But $g' = g_0 S = \frac{30}{\sqrt{r}} S = 21.1 S \text{ KV/cm}$

$$V_v = 21.1 S m \left(1 + \frac{0.3}{\sqrt{rS}}\right) \pi \ln(d/r) \text{ KV/rms.}$$

and

$$V_d = 21.1 S m \pi \ln(d/r) \text{ KV/rms.}$$

$$V_v > V_d$$

→ For any t/line the occurrence of the spark will take place at higher voltages when compared to the voltage at which the corona is initiated.

→ Result of Corona: When the corona is initiated then there will be certain amount of real power loss which will be converted into heat, so the insulating material will be slowly treated up. The loss due to occurrence of the initiation of corona is a real power loss which will be named as corona loss apart from the ohmic loss of the system.

Empirical form, Corona loss $P = 241 \times 10^{-5} \left(\frac{f+25}{S}\right) \sqrt{\frac{r}{d}} (V_p - V_d)^2 \text{ KW/Phase/Km.}$

\nearrow operating voltage / phase
 \rightarrow critical disruptive voltage / phase

→ The corona may not be initiated in all the three wires at the same time. So that the corona loss will be expressed in phase

(Q) If $f = 50 \text{ Hz}$, $\delta = 0.95$, $r = 2.5 \text{ cm}$, $d = 8 \text{ m}$ $V_p = 292.45 \text{ kV}$, $V_d = 294.65 \text{ kV}$

$p = ?$

Sol

Here $V_p = 292.45 \text{ kV/phase}$

$V_d = 294.65 \text{ kV/phase}$

** If $V_d > V_p \rightarrow$ Corona does not exist.

$\Rightarrow p = 0$

If $V_p = 292.45 \text{ kV/phase}$

$V_d = 290.25 \text{ kV/phase}$

* $V_d < V_p \rightarrow$ Corona exists.

FACTORS INFLUENCING THE CORONA LOSS:

(1) Electrical factor

(i) Supply Frequency

In ac system $p \propto (f+25)$

In dc system $p \propto 25$ ($f=0$)

As the frequency $\uparrow \Rightarrow P_{ac}$ increases.

(Q) A 500kV tr-line $P = 1.2 \text{ kW}$, for 60Hz $P = ?$

$$\frac{P_1}{P_2} = \frac{(f_1+25)}{(f_2+25)} = \frac{1.2}{P_2} = \frac{75}{85}$$

$$P_2 = \frac{85}{75} \times 1.2 =$$

- a) 1.2
- b) 1.1
- c) 1.26
- d) 1.36

\rightarrow For the same operating voltage the Corona loss in d.c system is less when compared to a.c system.

(Q) of 400 kv a.c tr. line, $p = 8 \text{ kw}$, 400 kv dc. tr. line. $p = ?$


- a) 3 b) 6 **c) 1** d) 2

$3 \propto 75$


$p \propto 25$

$\Rightarrow p = 1$

(ii) Nature of Supply wave form: (a.c)

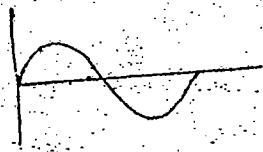

Sinusoidal wave.


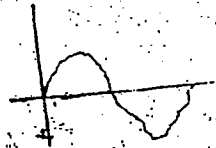


distorted wave of 5th harmonic exhibit

$\downarrow P \propto (f + 25)$

$\uparrow P \propto (f + 5f + 25)$

(iii) Polarity of the Conductors: (d.c)

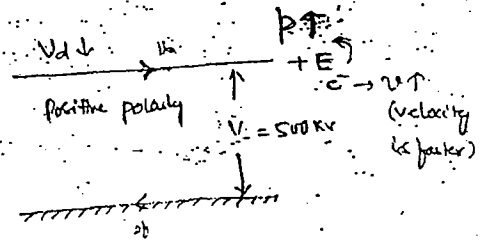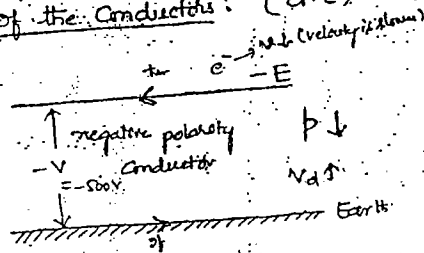

As $P \propto (V_p - V_d)^2$

$\therefore P \propto \frac{1}{V_d} \quad (V_d \uparrow \Rightarrow -ve) \Rightarrow \text{As } V_d \downarrow \Rightarrow P \uparrow$

→ of the voltage at which the Corona occurs will be less than the Corona loss will be high.

→ In HVdc transmission we prefer negative polarity conductors to get less Corona loss.

(iv) Distance of Separation between two Conductors:


(i) $p \propto \frac{1}{\sqrt{d}}$ (from empirical formula for Corona loss)

\Rightarrow As $d \uparrow$ then $p \downarrow$

(or) (ii) $V_d \propto \ln(Cd)$

\therefore As $d \uparrow \Rightarrow V_d \uparrow \Rightarrow p \downarrow$

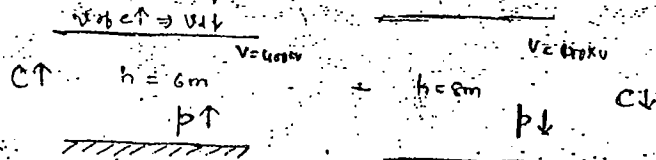(iii) The height of the conductor from the ground



— If the height of the conductor from the ground is less then the capacitance effect is high. So that there will be better voltage profile throughout the length of the conductor which inturn maintain high electric field intensity, so that the mobility of electron is high. The critical disruptive voltage is less and the Corona loss is high.

(v) Configuration of the Conductors:



— In case of unsymmetrical configuration the Corona loss will be high for the middle conductor when compared to outer conductors where as in case of symmetrical configuration the Corona loss will be same for all the three conductors.


(2) ATMOSPHERIC FACTORS

(i) Temperature and Pressure

Air density factor, $\delta = \frac{3.92 \times h}{273 + t}$

$\downarrow P \propto \frac{1}{\delta} \uparrow$ (or) $\uparrow V_d \propto \delta \uparrow \Rightarrow P \downarrow$

(ii)

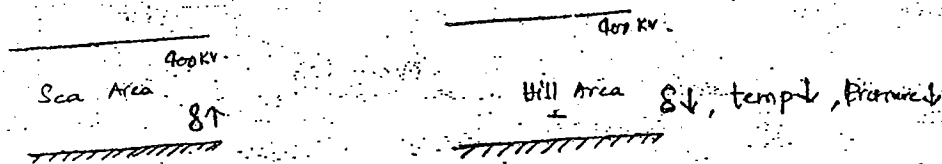

Ans:

- The Corona loss in hill area will be high when compared to the Corona loss in sea area.
- The fall in pressure is predominant when compared to fall in temperature at the hill areas so that the air density factor will be low and the corona loss will be high.

(ii) Deposition of dust, snow, ice and fog on the surface of the conductors

'm' is low (Surface irregularity factor)
Bad weather condition

$\Rightarrow V_d \downarrow \Rightarrow P \uparrow$

(iii) Factors related to the size of the conductors

(1) To reduce the Corona loss, use larger radius of the conductors.

$P \propto 241 \times 10^{-5} \left(\frac{f+25}{\delta} \right) \sqrt{\frac{l}{d}} (V_p - V_d)^2$

As 'r' of conductor \uparrow

$P \propto \sqrt{r}$

How ever $P \propto (V_p - V_d)^2$

We know that $V_d \propto r$

$$\rightarrow \text{as } r \uparrow \Rightarrow V_d \uparrow$$

$$\text{and } V_d \uparrow \Rightarrow (V_p - V_d)^2 \downarrow$$

$$\therefore p \propto (V_p - V_d)^2$$

$$\Rightarrow \text{As } (V_p - V_d)^2 \downarrow \Rightarrow p \downarrow$$

Hence $(V_p - V_d)^2$ is more predominant than \sqrt{r}

$$\text{As the radius } \uparrow \Rightarrow p \downarrow$$

(ii) Employ more than one sub conductor per phase (Bundle conductors)


In Bundle conductors \rightarrow Self GMD

$$\text{As Self GMD } \uparrow \Rightarrow V_d \uparrow$$

$$\Rightarrow p \downarrow$$


(iii) Profile of the conductor (or) Shape of the conductor

Cylindrical conductor

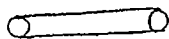

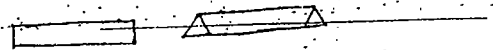1) Uniform distribution of field intensity


$$\Rightarrow V_d \uparrow \Rightarrow p \downarrow$$



$V_d \downarrow$ $p \downarrow$
non-uniform E'

ADVANTAGES OF CORONA


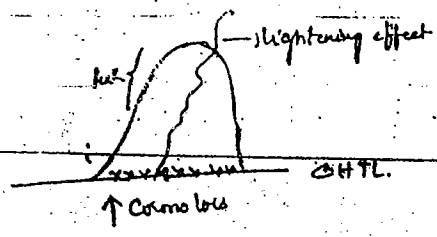
1) The Corona will act as safety valve to the transmission line conductor against direct lightning stroke, in which the peak magnitude of the lightning surge will be dissipated in the form of Corona loss.



* Ground wire to protect the line & to increase insulation level.

→ Disadvantages of Corona:

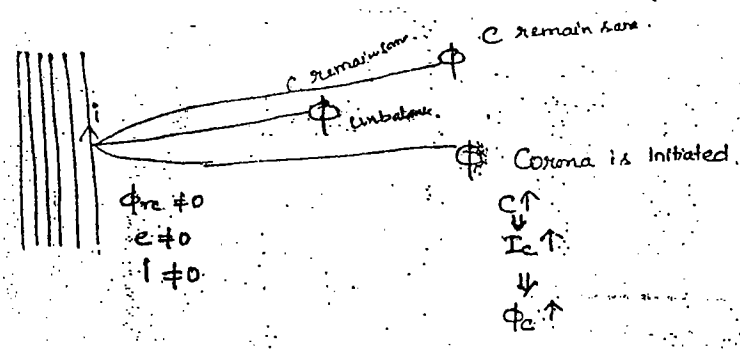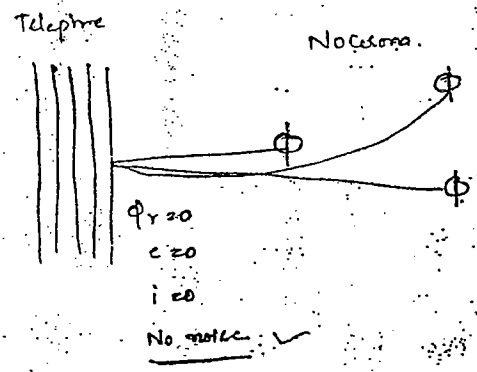- (1) There is certain real power loss in the form of Corona loss.
- (2) The Corona causes an interference with the neighbouring communication line because the net changing flux that can be linked with communication line is not zero.



→ Methods to reduce the Corona loss:

- (1) Use larger size of the conductor
- (2) Use hollow conductor
- (3) Use bundle conductor (most practical)

$$3c' = c'$$

$$c_1' = \frac{c'}{3}$$

$$\rightarrow I_2'' = I_2'$$

$$(V_3 + V_4) \omega c_1' = (V_1 + V_2) \omega c'$$

$$2c_1' = 2c'$$

$$c_2' = c'$$

$$\rightarrow I_3'' = I_3'$$

$$V_4 \omega c_3' = (V_1 + V_2 + V_3) \omega c'$$

$$c_3' = 3c'$$

→ In general, the static capacitance of the required, k^{th} disc

$$C_k' = \frac{Kc'}{n-k}$$

where $K \neq n$ always.

$$c_1' = \frac{c'}{3}$$

$$c_2' = \frac{2c'}{4-2} = \frac{2c'}{2} = c'$$

$$c_3' = \frac{3c'}{4-1} = 3c'$$


→ The 'K' is considered from the cross arm to the power conductor and it is not exactly equal to the no. of discs.

→ Guard ring is partially effective:

if the G.R is not fully effective

$$\% \eta < 100\%$$

$$V_4 = V_3 = V_2 = \dots$$

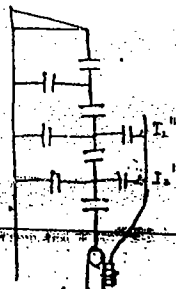

(Q) In a 3-disk string insulator, the Guard ring is effective only for a disk near to the power conductor.

The self capacitance is $\frac{1}{10}$ th of the self capacitance. The peak voltage of the disk is 10kV. Calculate the voltage of the string, string efficiency and the static capacitance.

Sol

$$V_3 = V_2 \neq V_1$$

$$\Rightarrow V_3 = 10 \text{ kV}$$

$$V_2 = 10 \text{ kV}$$

$$V_2 = V_1(1+k)$$

$$\text{Given } V_1 = \frac{10}{1.1}$$

$$V_1 = 9.09 \text{ kV}$$

$$V = V_1 + V_2 + V_3$$

$$= 29.09 \text{ kV}$$

$$\% \eta = \frac{29.09}{3 \times 10} \times 100 = 96.76\%$$


For C_1
 $\rightarrow I_2'' = I_2'$

$$V_3 \omega C_1' = (V_1 + V_2) \omega C_1'$$

$$10 C_2' = 19.09 C_1'$$

$$C_2' = \frac{19.09}{10} C_1'$$

$$\boxed{\frac{C_2'}{C_1'} = 1.909}$$

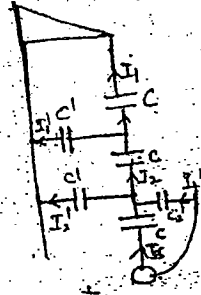

Advantages of Multishell Pin Insulators

(1) Due to the multishells the paths for leakage current will increase so that the magnitude of the leakage current is less.

(2) During bad weather conditions the top shell will become wet and the bottom shells are dry, so that there will be more resistance for leakage current hence the magnitude of leakage current is reduced.

(3) It can withstand the lightning voltage by splitting the lightning magnitude across each shell.


→ Multishells are also called as Rainsheds.

→ The multishell pin insulators will become uneconomical for the voltage 66KV and above so that the String (or) Suspension Insulator is used.


* Cost of insulator $\propto V^{\alpha}$, $\alpha > 2.0$

Slide


(2) SHACKLE INSULATOR

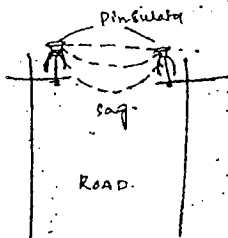

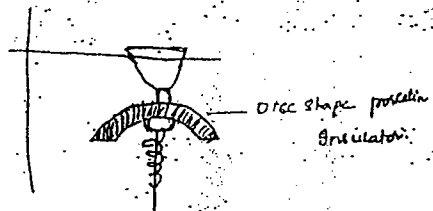As temp \uparrow , sag increases which is unwanted. Hence going for Shackle Insulator.




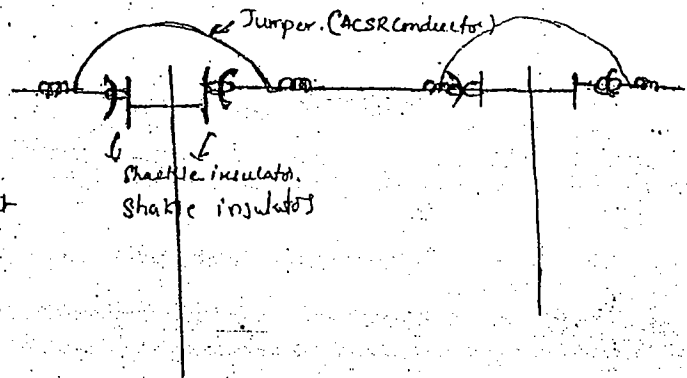
→ The no. of Shackle Insulators which are required are normally "double" that of no. of pin Insulators.



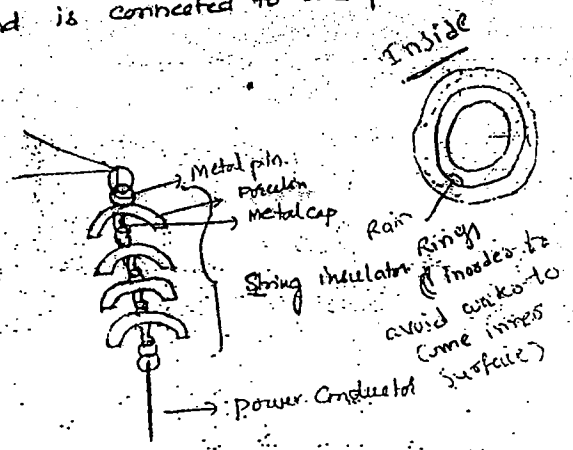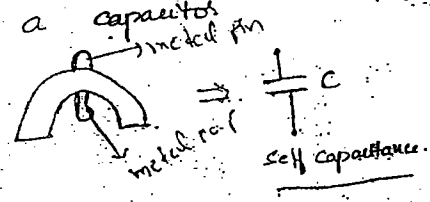(4) STRING OR SUSPENSION INSULATOR:

It consists of two or more larger disc shape porcelain insulators which are connected each other in a feasible manner in order to form a string. One end of the string is connected to the cross arm and the other end is connected to the power conductor.

→ A disc is a mechanical concept can be represented electrically as a capacitor




→

$$V_4 = I_4 \times C$$

$$V_3 = I_3 \times C$$

$$V_2 = I_2 \times C$$

$$V_1 = I_1 \times C$$

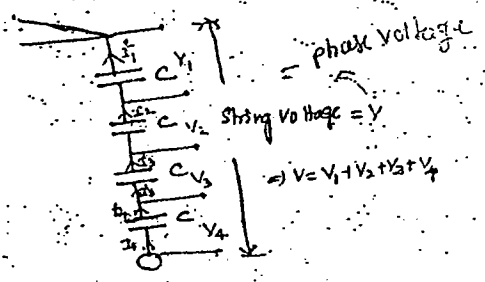

→ In general $V_4 > V_3 > V_2 > V_1$ since $I_4 > I_3 > I_2 > I_1$

→ The utilization of the insulating material of a given string can be analysed by defining the concept of "string efficiency"

→ String efficiency:

$$\% \text{ String efficiency} = \frac{\text{Voltage across the string}}{\text{no. of discs} \times \text{Voltage of a disc near to power conductor}} \times 100$$


$$\% \text{ String efficiency} = \frac{V_1 + V_2 + V_3 + V_4}{4 V_4} \times 100 \quad (\text{Four insulators})$$

In a.c system, the string efficiency is less than 100%, because

(1) The occurrence of shunt capacitance (c')

$$\frac{\text{Shunt cap}}{\text{Self cap}} = \frac{c'}{c} = K \quad (\text{Multiplication factor}) \quad c' \ll c$$

$$K \ll 1$$

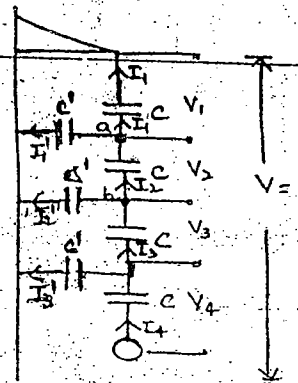

At 'a', $I_2 = I_1 + I_1'$ (All are charging and not capacitive with angle)

$$V_2 \omega c = V_1 \omega c + V_1 \omega c'$$

$$V_2 \omega c = V_1 \omega c + V_1 \omega K c$$

$$V_2 = V_1 (1 + K)$$

voltages across each disc are unequal i.e string efficiency is less than 100% & due to effect of shunt capacitance

At 'b', $I_3 = I_2 + I_2'$

$$V_3 \omega c = V_2 \omega c + (V_1 + V_2) \omega c'$$

$$V_3 \omega c = V_2 \omega c + (V_1 + V_2) \omega K c$$

$$V_3 \omega c = V_2 \omega c + V_1 \omega K c + V_2 \omega K c$$

$$V_3 \omega c = V_2 \omega c (1 + K) + V_1 \omega K c$$

$$V_3 \omega c = \omega c (V_1 (1 + K) (1 + K) + V_1 \omega K c)$$

$$V_3 \omega c = V_1 (1 + K)^2 \omega c + V_1 \omega K c$$

$$V_3 = V_1 (1 + 2K + K^2) + V_1 K$$

$$V_3 = V_1 (1 + 3K + K^2)$$

At 'c'

$$I_4 = I_3 + I_3'$$


$$V_4 \omega c = V_3 \omega c + V_3 \omega c' (V_1 + V_2 + V_3) \omega c'$$

$$V_4 \omega c = V_3 \omega c + V_3 \omega K c = V_1 \omega c + V_2 \omega c + V_3 \omega c$$

$$= V_3 \omega c$$

$$V_4 = V_1 (1 + 6K + 5K^2 + K^3)$$

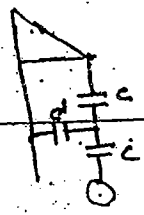(Q) What is the string efficiency of the system if $c' = \frac{1}{2} c$



Sol

$$\% \eta = \frac{V_1 + V_2}{2V_2} \times 100$$

$$= \frac{V_1 + V_1(1+k)}{2(1+k)V_1} \times 100$$

$$k = \frac{c'}{c} = 0.5$$


$$= \frac{V_1(1 + 1(1+k))}{V_1(2(1+k))} \times 100$$

$$= \frac{1 + 1(1+0.5)}{2(1+0.5)}$$

$$\% \eta = \frac{1 + 1.5}{2(1.5)} = \frac{2.5}{3} \times 100 = 83.3\%$$

(Q)

$\% \eta = ?$

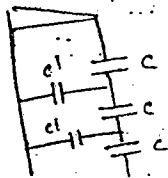

$$c' = \frac{1}{10} c$$

Sol

$$\% \eta = \frac{V_1 + V_2 + V_3}{3V_3} \times 100$$

$$= \frac{V_1 + V_1(1+k) + V_1(1+3k+k^2)}{3(1+3k+k^2)} \times 100$$

$$k = \frac{c'}{c} = \frac{1}{10} = 0.1$$

$$= \frac{3 + 4k + k^2}{3(1 + 3k + k^2)} \times 100$$

$$= \frac{3 + 4(0.1) + (0.1)^2}{3(1 + 3(0.1) + (0.1)^2)} \times 100$$

$$= \frac{3 + 0.4 + 0.01}{3(1.3 + 0.01)} \times 100$$

$$\% \eta = 86.76\%$$

(Q) A 3- ϕ , 3-wire 33 kV system is having ^{string of 3 disc insulators.} the shunt capacitance is $\frac{1}{10}$ of the self capacitance. What are the voltage drops across each disc

Sol

$$V_1 + V_2 + V_3 = \text{string voltage}$$



$$V_1 + V_2 + V_3 = \frac{33 \times 10^3}{\sqrt{3}}$$

$$V_1 + V_1(1+k) + V_1(1+3k+k^2) = \frac{33 \times 10^3}{\sqrt{3}}$$

$$V_1(3+4k+k^2) = \frac{33 \times 10^3}{\sqrt{3}}$$

$$V_1 = \frac{33 \times 10^3}{\sqrt{3}(3+4k+k^2)}$$

$$V_1 = \frac{33 \text{ k}}{\sqrt{3}(3+0.4+0.01)}$$

$$k = \frac{1}{10} = 0.1$$

$$V_1 = 5.56 \text{ kV}$$

$$\begin{aligned} V_2 &= V_1(1+k) \\ &= 5.56(1+0.1) \\ &= 5.1654 \end{aligned}$$

$$\begin{aligned} V_3 &= V_1(1+3k+k^2) \\ &= 5.56(1+3(0.1)+(0.01)) \\ &= 7.2836 \text{ kV} \end{aligned}$$

(Q) In a 3-disc string insulator, the peak voltage of the disc is 9 kV. The shunt capacitance of the string is $\frac{1}{10}$ of self capacitance. The voltage across the string in KV is _____

Sol

Given $V_3 = 9 \text{ kV}$

$$\frac{C'}{C} = k = \frac{1}{10} = 0.1$$

$$V_3 = V_1(1+3k+k^2)$$

$$V_1 = \frac{V_3}{1+3k+k^2} = \frac{9}{1+3(0.1)+(0.01)} = 6.87 \text{ kV}$$

$$V_2 = V_1(1+k)$$

$$= 6.87(1+0.1)$$

$$= 7.55 \text{ KV.}$$

Voltage across string, $V = V_1 + V_2 + V_3$

$$= 6.87 + 7.55 + 9$$

$$= \underline{\underline{23.42 \text{ KV}}}$$

(Q) In a 2-disc string insulator, the voltage across the disc are 40KV and 8KV. The ratio of the self capacitance the shunt capacity is.

Sol

$$V_2 = 10$$

$$V_1 = 8$$

$$V_2 = V_1(1+k)$$

$$\frac{10}{8} = \frac{1}{8}(1+k)$$

$$4+4k = 5$$

$$4k = 1$$

$$k = \frac{1}{4} = \frac{C'}{C}$$

$$\therefore \frac{C}{C'} = \frac{1}{k} = 4$$

(Q) In a 4-disc string insulator the peak voltage of the disc is 30% to that of string voltage. The string efficiency of the system is

Sol

$$\% \eta = \frac{V}{n V_4}$$


$$= \frac{V}{4 \times 0.3 V} \times 100$$

$$= \frac{100}{1.2}$$

$$\% \eta = \underline{\underline{83.33\%}}$$

** For the same operating voltage the string efficiency for the dc system is 100% because the shunt capacitance effect can be ignored. (little less than 100% for practical case)

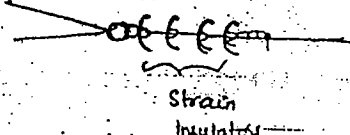→ When ever the road crossing, we have Strain (or) tension Insulator



The efficiency of Strain (or) tension Insulator = 100%. Since there is no shunt capacitance effect.


→ Advantages of String (or) Suspension Insulator:

- (1) Each disc is normally rated for 11KV, so that the operating voltage can be increased by adding the extra required no. of discs only.

→ For 66KV → $\frac{66}{\sqrt{3}} = \frac{38.105}{11} = 3.46 \approx 4$ 5

→ but no. of disc required are 5 ✓ since of unequal voltage across each disc.

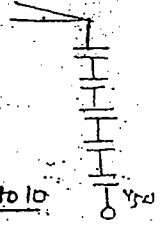* The extra disc is for the safety purpose.



→ For 132KV → $\frac{132}{\sqrt{3}} = \frac{76.21}{11} = 6.9 \approx 7+1 = 8$ to 10

→ For 220KV = $\frac{220}{\sqrt{3}} = \frac{127.9}{11} = 11.5 \approx 12+1 = 13$ to 16

→ For 400KV = $\frac{400}{\sqrt{3}} = \frac{230.9}{11} \approx 20.9 \approx 21+1 = 23$ to 29

S. cut

66 → $\frac{66}{11} = 6 - 1 =$

132 → $\frac{132}{11} = 12 - 2 =$

220 → $\frac{220}{11} = 20 - 4 =$

400 → $\frac{400}{11} = 36 - 8 =$

(2) It requires the replacement of failed disc only.

(2) The string is flexibly connected so that it can make the oscillations horizontally. In order to suppress the wind effect however it requires the longer length of cross arms.

→ METHODS TO IMPROVE STRING EFFICIENCY:

The method which suggests to make equal voltage drop across each disc so that the efficiency will almost 100%.

- (1) Selection of 'k' values → Similar discs: (Most practical one) ≈ 100%
- (2) Grading of insulators → Dissimilar discs = 100%
- (3) Static shielding or Ground ring → Similar discs = 100%

(1) Selection of 'k' values: (longer cross arm)


$$k = \frac{c_l}{c}$$

$$V_0 \neq V_2 \neq V_1$$

$$I_0 \neq I_2 \neq I_1$$

$$I_2' = I_1' = 0 \text{ On practical}$$

because the l

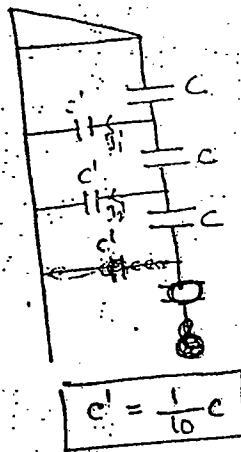

→ If the length of the cross arm is reduced then the shunt capacitance will increase so that the charging current of the shunt capacitor which will reduce the current in self capacitance.

So that the string efficiency is reduced.

→ In order to make the voltage drops almost equal, there should be optimum length of cross arm. So that $c' = \frac{1}{10} c$ can be recommended.

$$K = \frac{c'}{c} = \frac{1}{10}$$

(ii) Grading of the Insulators: (Dissimilar disc) (Equal voltage) = 100% efficiency

→ In the capacitance grading of the insulator, the disc which is having less capacitance will be placed near to the cross arm and the disc which is having highest capacitance will be placed near to the power conductor.


$$V_4 = V_3 = V_2 = V_1$$

$$I_4 \times X_4 = I_3 \times X_3 = I_2 \times X_2 = I_1 \times X_1$$

$$I_4 > I_3 > I_2 > I_1$$

$$X_4 < X_3 < X_2 < X_1$$

$$C_4 > C_3 > C_2 > C_1$$

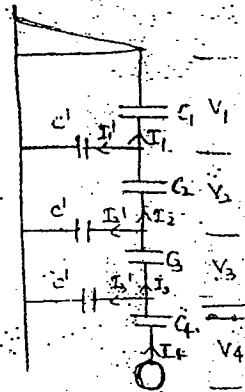

→ The calculation of the capacitance of the disc if c' & C_1 are given.

$$\rightarrow I_2 = I_1 + I_1'$$

$$V_2 \omega C_2 = V_1 \omega C_1 + V_1 \omega c'$$

$$C_2 = C_1 + c'$$

$$(\because V_2 = V_1)$$

$$\rightarrow I_3 = I_2 + I_2'$$

$$V_3 \omega C_3 = V_2 \omega C_2 + (V_1 + V_2) \omega c'$$

$$C_3 = C_2 + 2c'$$

$$C_3 = C_1 + 2c'$$

$\rightarrow I_4 = I_2 + I_3'$

$V_4 \omega C_4 = V_2 \omega C_2 + (V_1 + V_2 + V_3) \omega C'$

$C_4 = C_2 + 3C'$

is ~~extra~~

*
 \rightarrow For n-disc, with disc placed at cross arm

$C_n = C_{n-1} + (n-1)C'$


(3) Guard Ring (a) Static shielding method:

$V_4 = V_3 = V_2 = V_1$

$I_4 = I_3 = I_2 = I_1$

$I_4 X_C = I_3 X_C = I_2 X_C = I_1 X_C$

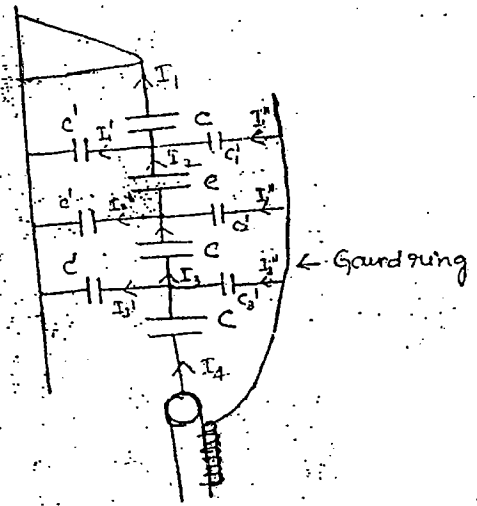\rightarrow Due to Guard ring the static capacitance is formed between the insulator disc and the guard ring



\rightarrow The charging current of the shunt capacitance will be supplied by the charging current of the static capacitance, so that there will be equal currents in each disc, which will result as equal voltage drops.

$\% \eta = 100\%$

\rightarrow Calculation of static capacitance:


$V_1 = V_2 = V_3 = V_4$

$(V_1 + V_2 + V_3) \omega C' = V_1 \omega C'$

that the efficiency of runoff river without pondage will improve.

(iii) Reservoir type: In the reservoir type huge volume of water can be stored by constructing dam across the river during floods and the stored water can be utilized to generate the power over a specified period.

(iv) PUMPED STORAGE PLANT:

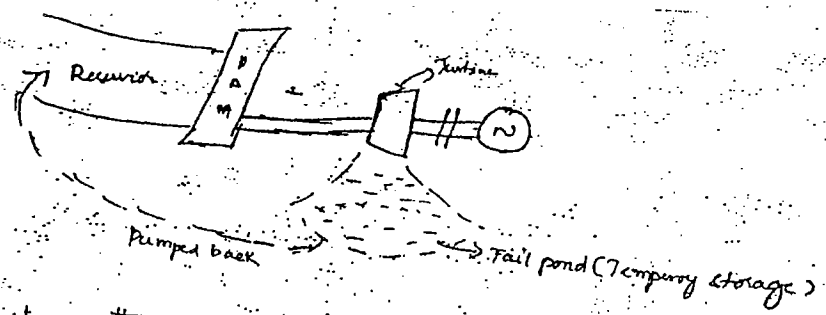

In this type the water is drawn from the dam for the generation purpose and the utilized water will be stored temporarily at the tail pond and during light load condition on the network the stored water will be fed back to the reservoir.

→ **Efficiency is only of 60% because some of the units are seutilized for pump mode.

→ The turbine which is used in pumped storage plant is Reversible turbine.

(4) BASED ON APPLICATION

- 1) Base load plant
- 2) Peak load plant

→ CLASSIFICATION OF TURBINES:

(1) BASED ON HEAD:

- (i) 2-15m → Propeller (or) Kaplan turbine
- (ii) 15-70m → Kaplan (or) Francis
- (iii) 70-500m → Francis or Pelton wheel
- * (iv) above 500m → Pelton wheel
- ** (v) up to 300m → Deriaz turbine

(2) DIRECTION OF FLOW:

- (i) Tangential flow → Pelton wheel
- (ii) Mixed flow (Radial inflow + Axial outflow) → Francis turbine
- (iii) Axial flow → Kaplan (or) propeller
- * (iv) Diagonal flow → Deriaz turbine → up to 200m

→ The preferable turbine used for reversible mode of operation is Deriaz turbine

(3) BASED ON SPECIFIC SPEEDS:

Specific speed: It is the speed of the turbine which is working with a head of 1m and 1 metre horse power

$$** \quad N_s = \frac{N(P)^{1/2}}{h^{5/4}}$$

$$\Rightarrow N \propto \sqrt{P}$$

$$\Rightarrow N_s = \frac{1.15 N P^{1/2}}{h^{5/4}}$$

P is in kW

→ SPECIFIC SPEEDS!

- discharge
- (i) Low speed \rightarrow 4 - 70 rpm \rightarrow Pelton wheel
 - (ii) Medium speed \rightarrow 70 - 420 rpm \rightarrow Francis
 - (iii) High speed \rightarrow 350 - 900 rpm \rightarrow Kaplan (or) Propeller


** Francis turbine can give maximum power with available head and discharge

$\checkmark F \rightarrow P \propto (Qh)$ Medium

$\checkmark P \rightarrow P \propto Q h^2$

$\checkmark K \rightarrow P \propto Q h^3$

→ HIGH HEAD PLANTS!

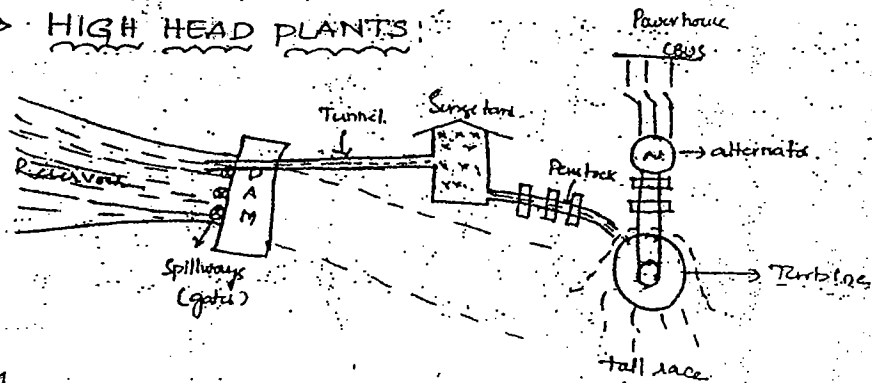

In case of high head plants the power house is normally located away from the dam to reduce the pressure of water

Dam: It is the big R.C.C structure developed b/w the two natural hills in order to develop an amount of head as well as to provide storage facility

Reservoir: It is the catchment area of the dam in which the water is stored.

Spillways (gates): The spillways acting as safety devices to the dam in order to discharge the excess amount of water directly into the low place during the floods.

→ TUNNEL: The power house is away from the main dam. So the required water is first taken from the dam to the surge tank by a closed canal or open canal which is known as tunnel. It is also made by R.C.C.


→ Surge tank: It is located near the turbine and the purpose of this is to store the water temporarily from which the water is allowed to the turbine. It will act as temporarily regulating reservoir also.

→ Penstock: The turbine runner and the surge tank is connected through a steel pipes in case of medium and high head plants which are known as penstocks. The purpose of the penstock is to supply the water to the turbine from a surge tank.

→ If any sudden increase in the load on the alternator then the nozzle of the penstock will be open widely in order to admit -ve pressure, so that the water should be sent to the penstock.

→ If the load on the alternator is suddenly reduced the nozzle is closed, so that the excess should be sent back from the penstocks where the penstock are developed with +ve pressure. The development of +ve and -ve pressure in the penstock is called "Water hammer effect".

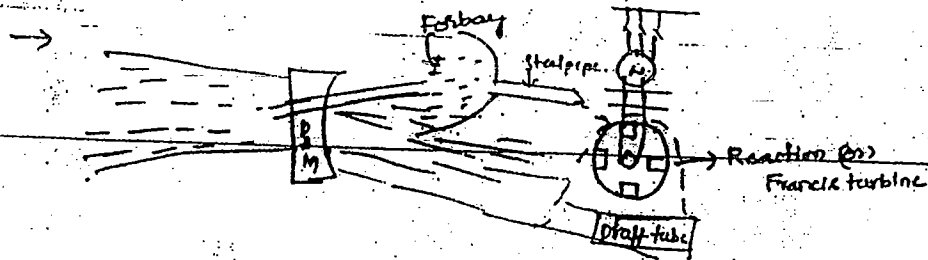
→ The purpose of the surge tank is to suppress the



→ Surge tank is also a temporary water storage device from which the water is supplied to the turbine through penstocks. However from FORBAY, it can plan with more no. of penstocks.

→ The Draft tube is associate with reaction turbines, which will connect the runner outlet to the tail race with a gradually increased in diameter of the tube.

→ LOW HEAD PLANTS:

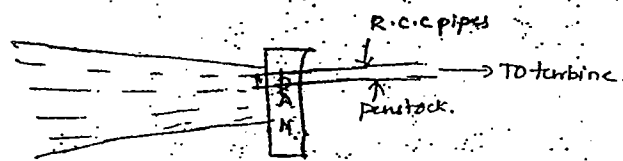

→ In case of low head plants the powerhouse is located near the dam, so that the water is directly taken from the tank through penstocks which are made by R.C.C pipes

→ The velocity of water in penstocks is of


- 1) low head → 2 m/sec
- 2) Medium head → 4 m/sec
- 3) High head → 8 m/sec.

3) NUCLEAR PLANTS

The high pressure and temperature steam is

Converted into Electrical energy

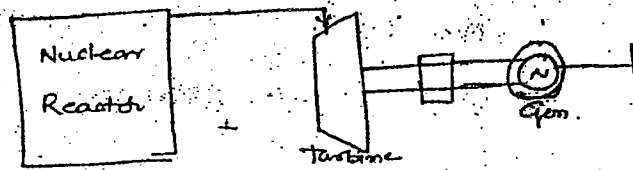→ High temperature and pressure steam can be obtained by the heat released from radioactive materials



* 1.2 Kg of Uranium is sufficient to generate 1 MW for 4 year

→ Selection of site:

1. Availability of water
2. It should be near to load centres but away from populated areas.
3. Facility to dispose the waste material
4. Easy accessible to road and Rail.

→ Plants in India:

(i) Tarapur → Trombay → 2 x 210 MW (Maharashtra)

✓ FUEL: U^{238} → called as Enriched Uranium
→ 99.3% of Uranium

✓ TYPE OF REACTOR: Boiling water Reactor (BWR)

(ii) Rana Pratap Sagar → Rajasthan → 2 x 220 MW

✓ FUEL: U^{235} → natural Uranium → 0.7%

✓ TYPE OF REACTOR: CANDU reactor

(ii) Kalpakkam → 2 X 235 MW (Tamil Nadu)

FUEL: U^{235} → Natural Uranium (0.7%)

TYPE OF REACTOR: CANDU TYPE

(iv) NARORA → 2 X 235 MW (Uttar Pradesh)

FUEL: U^{235}

REACTOR: CANDU

(v) KAKRA → 2 X 235 MW (Gujarat)

FUEL: U^{235}


REACTOR: CANDU

(vi) KAIGA → 2 X 235 (Karnataka)

FUEL: U^{235}

REACTOR: CANDU




→ NUCLEAR REACTOR

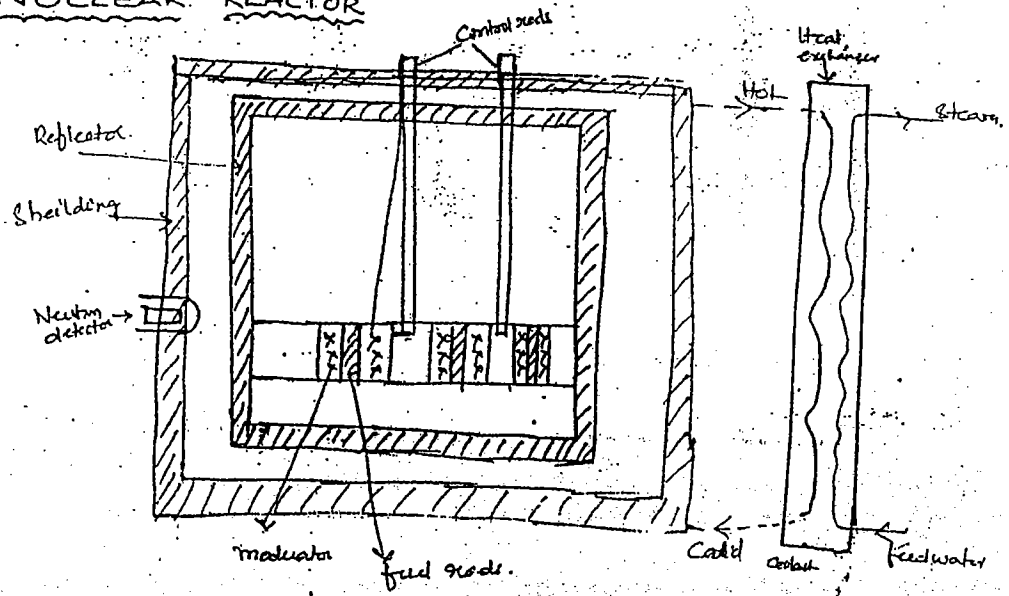

→ Reactors are classified based on the speed of Neutrons

(i) Thermal Reactors → speed less than 2000 m/sec

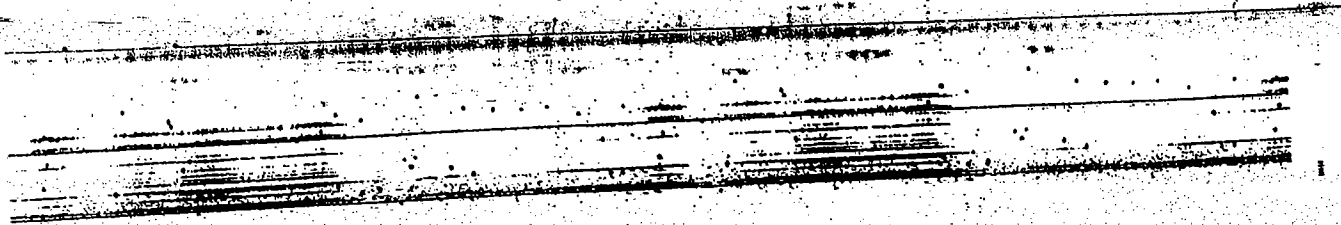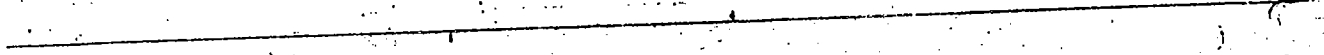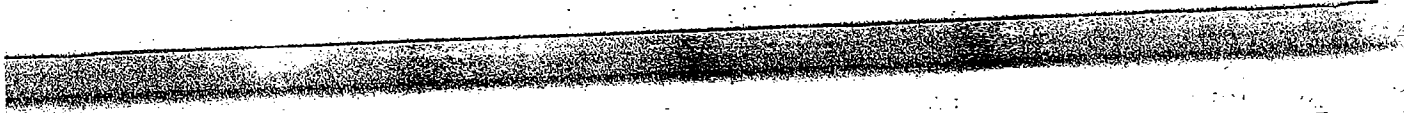(ii) Fast Breeder Reactors → speed more than 2000 m/sec




∴ Charging current, $I_c / \text{phase} = V_{\text{phase}} \omega C / \text{phase}$

$$V_{\text{phase}} = \frac{V_{L-L}}{\sqrt{3}}$$


→ CAPACITANCE OF A 1-φ 2-WIRE TRANSLINE - FINITE EARTH PLANE

↳ By using Kelvin's Images law.

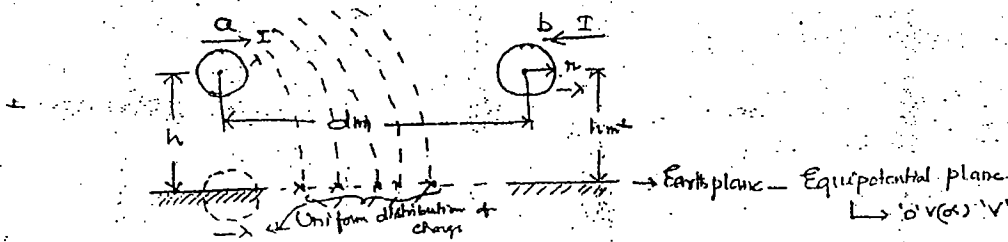

→ The No. of electric flux lines that can be generated from the surface of the conductor are equal to the amount of charge deposited on the surface of the conductor.

No. of flux lines = λ

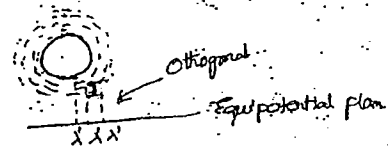

- Electric flux lines are orthogonal to equipotential plane

- Each flux will induce an amount of charge depending upon no. of flux lines.

Eg: $\lambda \rightarrow -\lambda$

$\lambda \rightarrow -\lambda/2$ for '2' flux line.

$\lambda \rightarrow -\lambda/3$ for '3' "

→ Due to more no. of electric flux lines which can cut the equipotential plane in an orthogonal manner, there will be uniform distribution of charges throughout the equipotential plane.

→ It is very difficult to calculate the capacitance b/w charge λ and the uniform distribution of charges. So that the charges

The Earth plane is also running in parallel to the tri-line conductors.


This is an effect of Earth on Capacitor Calculations and

the effect of the earth is not considered for inductance and resistance calculations.

→ By Assuming Earth as isolated i.e. infinite plane.

→ 1-φ 2-wire - Isolated Earth
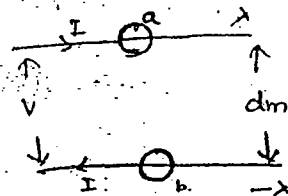
$$C_{ab} = \frac{\lambda}{V} = \frac{\pi \epsilon_0 \epsilon_r}{\ln(d/\lambda)} \text{ F/m.}$$



$$\therefore C_{ab} = \frac{\pi \epsilon_0}{\ln(d/\lambda)} \text{ F/m} \quad (\because \epsilon_r = 1.0)$$

$$\Rightarrow C_{ab} = \frac{3.14 \times 8.854 \times 10^{-12}}{\ln(d/\lambda)} \text{ F/m}$$

$$= \frac{3.14 \times 8.854 \times 10^{-9}}{\ln(d/\lambda)} \text{ F/km}$$

$$C_{ab} = \frac{3.14 \times 8.854 \times 10^{-3}}{\ln(d/\lambda)} \text{ μF/km}$$

$$\Rightarrow C_{ab} \propto \frac{1}{\ln(d/\lambda)}$$

As d is metres, and λ is cm.

$$C_{ab} \propto \frac{1}{\ln(d)}$$

As the $d \uparrow \Rightarrow C_{ab} \downarrow$

→ For Bundle conductors (or) Double circuit lines


The Inductance

$$L_{\text{phase}} = 0.2 \ln \left(\frac{\text{GMD}}{\text{self-GMD}} \right)$$

⇒ CAPACITANCE:

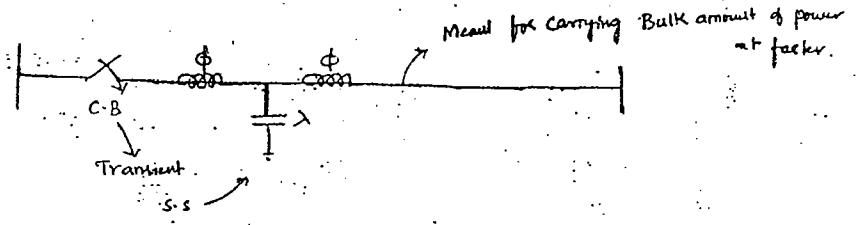1) 1-φ 2 wire


→ A 1-φ 2 wire overhead transmission line will act as a capacitor and the value of the capacitance will be increases as the lengths of the tr. line increases.



→ The Shunt capacitance of the tr. line will be useful for

- (1) Bulk amount of power carrier at a faster rate when the switch is closed
- (2) In order to compensate the voltage drop of the inductive reactance

→ 1-φ-2 wire

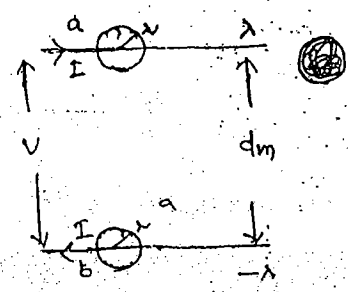


$$\text{Capacitance} = \frac{\text{Charge}}{\text{Voltage}}$$

- It will build up the static field.
- The instantaneous energy that can be

stored (or) discharged by the capacitor = $\frac{1}{2} CV^2$ KVAR or MVAR

INDUCTANCE - 3-PHASE - 3 WIRE

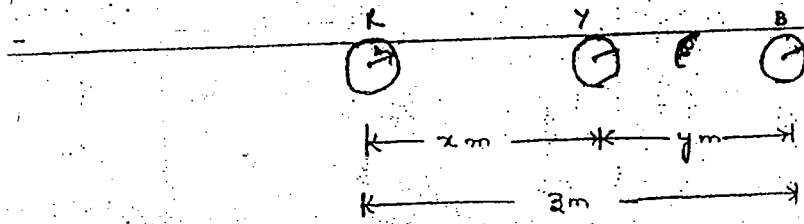

Use the transposition of transmission line to get the equal inductance per phase.

We know $L_a = 0.2 \ln(d/r')$

$$\therefore L/\text{phase} = 0.2 \ln\left(\frac{\text{GMD}}{\text{GMR}}\right) \text{ mH/Km}$$

where $\text{GMD} = \sqrt[3]{xyz}$

$$\text{GMR} = r'$$

If $x = y = z = d \Rightarrow$ Symmetrical Configuration.

$$L/\text{phase} = 0.2 \ln\left(\frac{\text{GMD}}{\text{GMR}}\right) \text{ mH/Km}$$

where $\text{GMD} = d$

$$\text{GMR} = r'$$

Since GMD in metres

& GMR in cm.

$$L \propto \ln(\text{GMD})$$

\rightarrow The inductance/Km in an unsymmetrical configuration will be slightly high when compared to the inductance/Km of a symmetrical configuration.


distance of separation

43

$$\frac{X}{R} < 1.0$$

→ For distribution system.

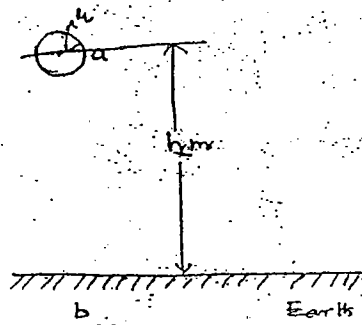⇒ Resistance is predominant in distribution system where as Inductive Reactance is predominant in Transmission system.




$$L_{ab} = L_a + L_b \approx L_a$$

$$L_a = 0.2 \ln\left(\frac{h}{a}\right) \text{ mH/Km.}$$

For all Copper strands
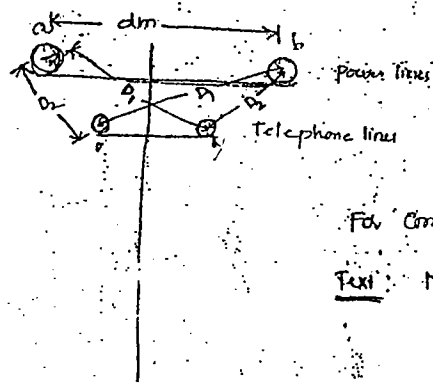
$$L_a = 0.05 \mu r + 0.2 \ln\left(\frac{h}{r}\right) \text{ mH/Km.}$$



For complete derivation go for Text: Nagrath & Kotari

$$M_c + M_d = 2M_c$$

$$= 2 \times 0.2 \ln\left(\frac{D_1}{D_2}\right)$$

→ max dist
→ min dist

$$M_c + M_d = 0.4 \ln\left(\frac{D_1}{D_2}\right) \text{ mH/Km.}$$

$$\Rightarrow L_a = 2 \times 10^{-7} \left[\ln \epsilon^{1/4} + \ln(d/r) \right] \quad \left(\because \ln \epsilon^{1/4} = \frac{1}{4} \right)$$

$$= 2 \times 10^{-7} \left[\ln \left(\frac{d \epsilon^{1/4}}{r} \right) \right]$$

$$= 2 \times 10^{-7} \ln \left(\frac{d}{\epsilon^{3/4} r} \right)$$

$$= 2 \times 10^{-7} \ln \left(\frac{d}{0.7788 r} \right)$$

$$L_a = 2 \times 10^{-7} \ln \left[\frac{d}{r'} \right]$$

Where $r' = \text{imaginary radius} = 0.7788 r$ because of internal flux linkages

$$L_a = 2 \times 10^{-4} \ln(d/r) \quad \text{H/Km.}$$

$$L_a = 2 \times 10^{-7} \ln(d/r) \quad \text{mH/Km.}$$

$$L_a = 0.2 \ln(d/r) \quad \text{mH/Km.}$$


and

$$L_{ab} = 2L_a = 0.4 \ln(d/r) \quad \text{mH/Km.}$$

$$\Rightarrow L \propto \ln \left(\frac{d}{r'} \right) \quad \begin{matrix} d \rightarrow \text{metres} \\ r' \rightarrow \text{cm.} \end{matrix}$$

$$L \propto \ln(d)$$
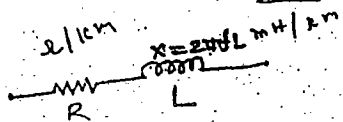
$$\Rightarrow \text{As } d \uparrow \rightarrow L \uparrow$$



$\uparrow x = 200L \uparrow$ of the conductor is small fit is in (m) so we can neglect it

$$\downarrow R \propto \frac{1}{a}, \quad \uparrow L \propto \ln(d)$$

\Rightarrow If distance of separation is high i.e.

d is high x will be high so

$$x > R$$

$$\frac{x}{R} > 1$$

\Rightarrow if area of cross section of loop is high (i.e. d) then inductance of the conductor will be high

From (2)

$$R_{ab} = R_a + R_b$$

$$\neq 2R_a$$


$$R_{ab} \approx R_a$$

if earth is one of the conductor then weight of conductor is reduced


conductor is reduced

→ In case of a.c. trans. system, Earth is not preferred as one of the conductor because it can produce an interference with the any other grounding system. Whereas it can be recommended as one of the conductor for H.V.D.C. transmission because there is no concept of interference (noise due to flux) ^{alternate} _{in phase}

→ Bulk power 3-phase-3wire

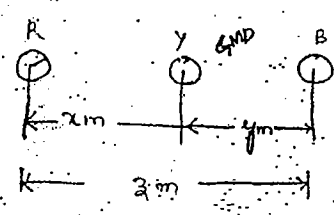

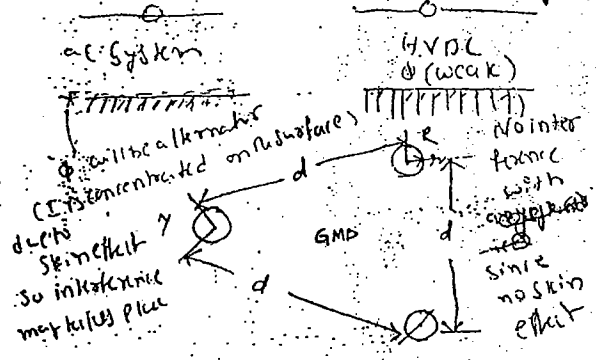Unsymmetrical, $R_{phase} = \frac{Pl}{a} \Omega/km$



Symmetrical.

$$R_{ph} = \frac{Pl}{a} \Omega/km$$

→ The current will be carried out by each phase for 120°

Phase displacement

→ The vector sum of the currents at any point of time will be zero so that there will not be any separate return ^{path} for each phase and the transline constants are calculated in a phase manner having a reference of neutral.

→ For the same operating voltage the resistance/km in both the configurations will be same because it does not depend


up on GND

23-01-19


→ RESISTANCE CALCULATION 1- PHASE 2 WIRE

Transmission lines are normally of 'km' length

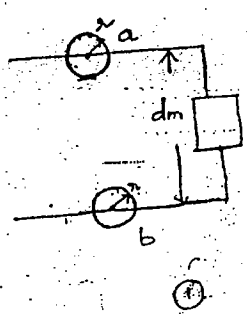All the line constants are evaluated based on per-unit-length i.e. per km



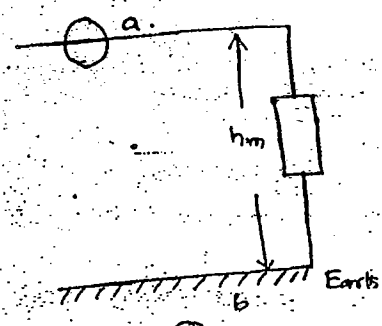$R_{ab} = R_a + R_b$
 $= 2R_a$
 $R_a = \text{Resistance/Conductor}$



(2)
 $R_{ab} = R_a + R_b$
 $\neq 2R_a$

→ The Purpose of the second wire

- (1) To show the potential difference
- (2) To provide the closed path for the Load current

(1) Circuit Resistance = (a) Loop Resistance $R_{ab} = R_a + R_b$
 $R_{ab} = 2R_a$

$R_a = \text{Resistance/Conductor}$

$R_a = \frac{\rho l}{a} \Omega / \text{km}$

$\rho = \text{Specific Resistance } \Omega\text{-km}$

$l = \text{length of one km}$

$a = \text{Area of c/s in } \text{km}^2$


In transmission lines the distance of separation between the two conductors is high and also the size of the conductor is larger. However the resistance does only depend on the size of the conductor and it will be less in tr. lines when compared to the distribution system.

→ INDUCTANCE OF 1-phase 2 Wire Tr-line

Inductance = $\frac{\text{Flux Linkages}}{\text{Current}}$

- It will build up the magnetic field i.e. called Flux.
- The instantaneous energy that can be stored or discharge by the inductor at any point of time is

$E = \frac{1}{2} LI^2$ KVAR (or) MVAR.

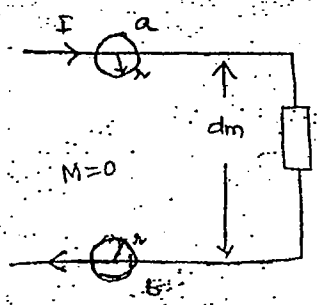

According to skin effect
 $L_{ab} = L_a + L_b \rightarrow$ Circuit (or) Loop inductance

$L_{ab} = 2L_a$

$L_a =$ Inductance / conductor

$\Rightarrow L_a = L_{int} + L_{ext}$

→ In overhead Trans. line the value of Mutual Inductance is XERO since the distance of separation of conductor is very high

→ L_{int} and L_{ext} are to be called as the self inductances of the conductor due to internal flux linkage of inner strands and external flux linkage of outer strands.

$\therefore L_a = L_{int} + L_{ext} \Rightarrow$ self inductance

$L_a = \frac{\mu_0 \mu_r}{8\pi} + \frac{\mu_0 \mu_r}{2\pi} \ln \frac{d}{r}$ H/m.

$= \frac{\mu_0 \mu_r}{8\pi} + \frac{\mu_0 \cdot 1}{2\pi} \ln \frac{d}{r}$

$\mu_r > 1.0$ $\mu_r = 1$ air

inductance that can be offered due to internal flux
~~also depend~~ depends on the distance of separation and
 the radius. Where as the self inductance that could
 be offered due to external flux linkage depends on the
 distance of separation and radius.

$$\therefore L_a = \frac{4\pi \times 10^{-7} \mu_r}{8\pi} + \frac{4\pi \times 10^{-7}}{2\pi} \ln(d/r) \quad \text{H/m}$$

$$= \frac{10^{-7}}{2} \mu_r + 2 \times 10^{-7} \ln(d/r) \quad \text{H/m}$$

$$= \frac{10^{-4}}{2} \mu_r + 2 \times 10^{-4} \ln(d/r) \quad \text{H/km}$$

$$= \frac{10^{-1}}{2} \mu_r + 2 \times 10^{-7} \ln(d/r) \quad \text{mH/km}$$

$$L_a = 0.05 \mu_r + 0.2 \ln(d/r) \quad \text{mH/km}$$

and $L_{ab} = 2L_a = 0.1 \mu_r + 0.4 \ln(d/r) \quad \text{mH/km}$

→ If all the strands are made of Copper

$$L_a = \frac{\mu_r \mu_0}{8\pi} + \frac{\mu_0 \mu_r}{2\pi} \ln(d/r)$$

(if μ_r is not given we should take $\mu_r = 1$)

$$= \frac{\mu_0}{8\pi} + \frac{\mu_0}{2\pi} \ln(d/r) \quad (\because \mu_r = 1.0)$$

$$L_a = \frac{4\pi \times 10^{-7}}{8\pi} + \frac{4\pi \times 10^{-7}}{2\pi} \ln(d/r)$$

$$= \frac{10^{-7}}{2} + 2 \times 10^{-7} \ln(d/r) \quad \text{H/m}$$


$$= 2 \times 10^{-7} \left[\frac{1}{4} + \ln(d/r) \right] \quad \text{H/m}$$

→ $\phi \quad \phi \Rightarrow$ Performance of the line is in phase manner.

$\phi \quad \phi \quad \phi \Rightarrow$ per phase under the assumption that the inductance and capacitance are almost equal.

→ The Inductance & Capacitance per phase can be equal under the assumption of the transposition of tr. line or the average inductance or capacitance.

→ TRANSMISSION LINE CONSTANTS:

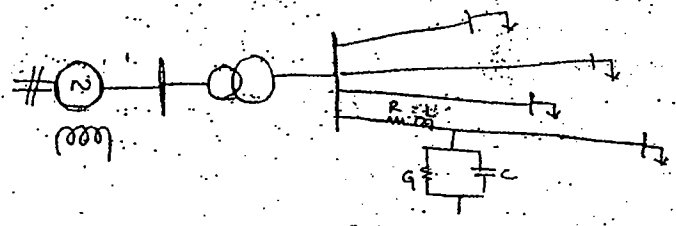



- A Tr. line is a bulk amount of power carrier between the remote generating station to the load.

- It will be represented electrically as

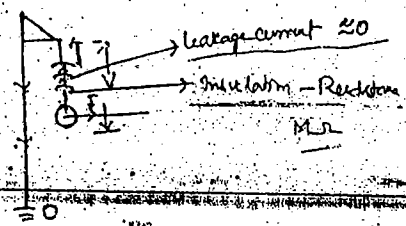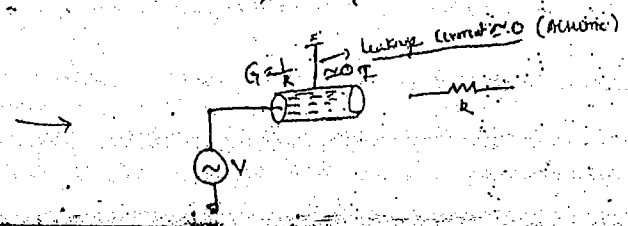- (1) A series combination of resistance & Inductance
- (2) A parallel combination of Conductance & capacitance


However the conductance of tr. line is assumed as ZERO ($G=0$)

$\Rightarrow G=0 \Rightarrow$ Current is '0'



To eliminate the communication interference the Transposition of Tr. lines is employed:

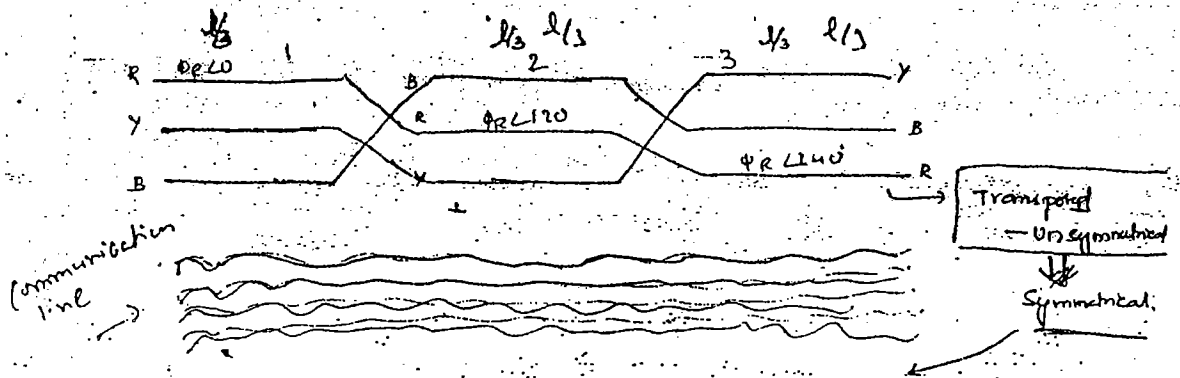Change the position of power conductor at regular intervals by maintaining equal distances so that the position of the original phase conductor will be replaced by its successive phase conductor



$$GMD_R = \sqrt[3]{GMD_{R1} GMD_{R2} GMD_{R3}}$$

$$GMD_{R1} = \sqrt{G \times l_2} = \sqrt{G \times l}$$

$$GMD_{R2} = \sqrt{G \times l}$$

$$GMD_{R3} = \sqrt{G \times l_2}$$

$$(\phi_R l_1 \omega + \phi_R l_1 \omega + \phi_2 l_1 \omega + \phi_2 l_1 \omega + \phi_3 l_1 \omega + \phi_3 l_1 \omega + \phi_4 l_1 \omega + \phi_4 l_1 \omega + \phi_5 l_1 \omega + \phi_5 l_1 \omega)$$

$$\therefore GMD_R = \sqrt[3]{6\sqrt{2} \times G \times 6\sqrt{2}}$$

$$GMD_Y = GMD_B = GMD_R$$

GMD is equal.

4pt is equal.

1/pt is equal.

phi/pt is equal.

phi_r = 0

Voltage drop/phase

is equal.

Balanced Receiving end

Voltage

→ There are certain difficulties that are experienced to do the transposition of H-lines in a modern p.s. because it is a very thick m/w. However the transposition of tr. lines can be recommended in older days because the m/w is a thin m/w.

→ The interference can be avoided either by having max distance by the two sets or by employing the insulated system.

Self GMD = $\sqrt[3]{\text{Self GMD}_R, \text{Self GMD}_Y, \text{Self GMD}_B} = 5.50 \text{ cm}$

$GMD = \sqrt[3]{GMD_R, GMD_Y, GMD_B}$

$GMD_R = \sqrt{GMD_{R1}, GMD_{R2}} = GMD_{R1}$

$= \sqrt{6.08 \times 12 \times 10.8 \times 14.4} = 10.32$


$GMD_B = GMD_R$

$GMD_Y = \sqrt[4]{6.08 \times 6.08 \times 10.8 \times 10.8} = \sqrt{6.08 \times 10.8} = 8.1$


$GMD = \sqrt[3]{10.32 \times 10.32 \times 8.1}$

→ TRANSPOSITION OF TRANSMISSION LINES:

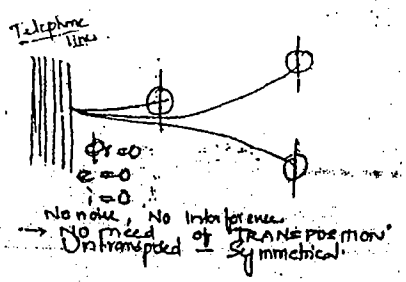Whenever an unsymmetrical transmission line is running neighbour to the communication line then the transmission line will produce an interference in the communication line. In order to eliminate the communication interference the transposition of transmission lines are employed.



GMD is equal | Voltage drop/phase is equal.
 L/ph is equal | Balanced Receiving end Voltage
 I/ph is equal
 phi is equal

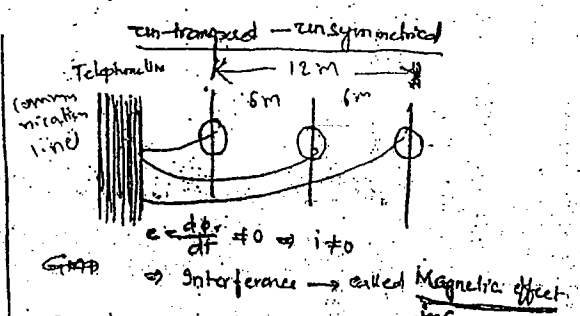

GMD is unequal | Voltage drop/phase is unequal.
 L/ph is unequal | Unbalanced Receiving end Voltage.
 I/ph is unequal
 phi is unequal

The double ckt configuration is more preferred to enhance the power transfer capacity at a given voltage, when compared to a single ckt with larger radius of the conductor, because the double ckt line will have self GMD which is more than GMR, so that \angle phase is reduced.


$$\begin{aligned} \text{(P.T.0)} \rightarrow \therefore GMD_R &= \sqrt{GMD_{R1} GMD_{R2}} \\ &= GMD_{R1} = \sqrt{6 \times 12 \times 10 \times 14.42} \\ &= 10.09 \text{ m} = GMD_{R2} \quad (\text{since both are same}) \end{aligned}$$

$$\begin{aligned} GMD_B &= \sqrt{GMD_{B1} GMD_{B2}} \\ &= GMD_{B1} = 10.09 \text{ m} \end{aligned}$$

$$\begin{aligned} GMD_Y &= \sqrt{GMD_{Y1} GMD_{Y2}} \\ &= GMD_{Y1} = \sqrt{6 \times 6 \times 10 \times 10} \\ &= \sqrt{60} = 7.74 \text{ m} \end{aligned}$$

$$\therefore GMD = \sqrt[3]{10.09 \times 7.74 \times 10.09} = 9.23 \text{ m}$$

→ Eq:

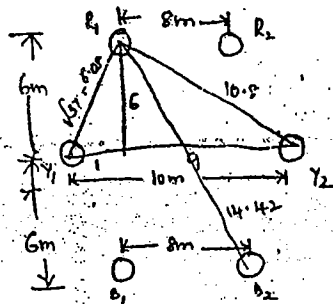

$$\text{Self GMD} = \sqrt[3]{\text{self GMD}_R \text{ self GMD}_Y \text{ self GMD}_B}$$

$$\begin{aligned} \text{self GMD}_R &= \text{self GMD}_R \\ &= \sqrt{0.778 \times 11.5 \times 200} = 39.57 \end{aligned}$$

$$\begin{aligned} \text{self GMD}_B &= \text{self GMD}_B \\ &= \sqrt{0.778 \times 11.5 \times 200} = 39.57 \end{aligned}$$

$$\begin{aligned} \text{self GMD}_Y &= \text{self GMD}_Y \\ &= \sqrt{0.778 \times 11.5 \times 1000} = 24.12 \end{aligned}$$

Q) There are 3 sub conductors in each phase and they are touching each other. The radius of each sub conductor, the self GMD of sub conductor configuration is

Self GMD = self GMD_r

$$= \sqrt{0.7788 \times r \times 2.2 \times 2.2}$$



$$= 1(0.7788)^{1/3} \cdot 2^{2/3} = \sqrt[3]{D_s \times d \times d \times \pi r d}$$

Self GMD = self GMD_r

$(D_s)^{1/3} \cdot d^{3/4} \cdot \pi^{1/8}$


DOUBLE Ckt TR LINE

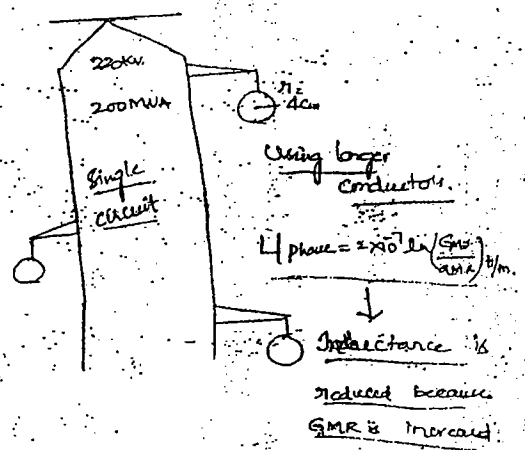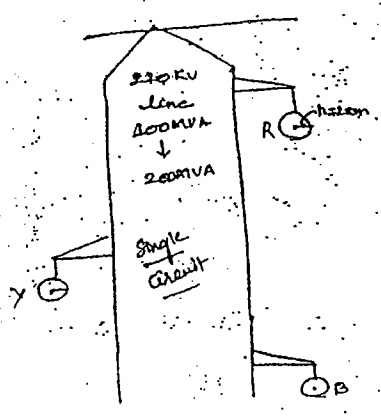ENHANCEMENT OF POWER TRANSFER CAPACITY AT A GIVEN VOLTAGE



The inductance is further reduced by using 'double circuit line'

Double circuit line double ckt

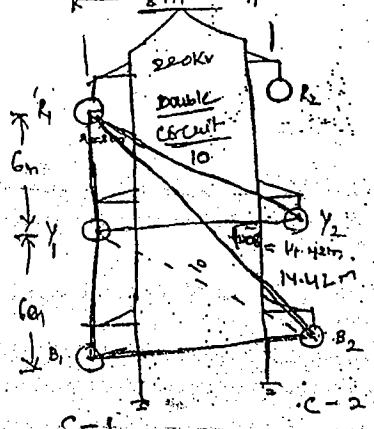

$$L_{\text{phase}} = 2 \times 10^{-7} \ln \left(\frac{GMD}{\text{Self GMD}} \right) \text{ H/m}$$

$$\text{Self GMD} = \text{Self GMD}_R = \text{Self GMD}_1$$



$$\sqrt{1 \times 16} = \sqrt{0.7788 \times 2 \times 800} \text{ cm}$$

$$= 35.297 \text{ cm}$$

$$GMD = \sqrt[3]{GMD_x GMD_y GMD_z}$$

→ (P.T.O.)

Eq:

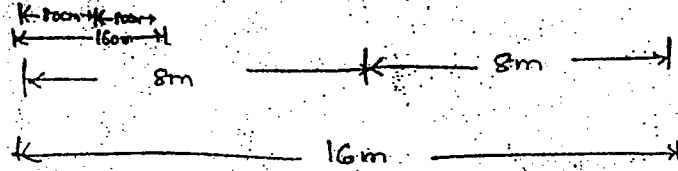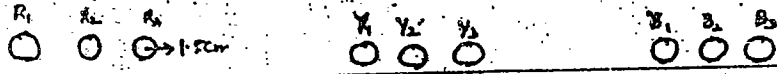

$$\text{Self GMD} = \sqrt[3]{\text{Self GMD}_1 \cdot \text{Self GMD}_2 \cdot \text{Self GMD}_3}$$

$$\text{Self GMD}_1 = \sqrt[3]{0.7788 \times 1.5 \times 80 \times 160}$$

$$\text{Self GMD}_2 = \text{Self GMD}_1$$

$$\text{Self GMD}_3 = \sqrt[3]{0.7788 \times 1.5 \times 80 \times 80}$$

$$\text{Self GMD} = \text{Self GMD}_1 = \sqrt[3]{\text{Self GMD}_1 \cdot \text{Self GMD}_2 \cdot \text{Self GMD}_3}$$

Since the subconductors are unsymmetric

$$\therefore \text{Self GMD}_1 = \sqrt[3]{0.7788 \times 1.5 \times 80 \times 160}$$

$$\text{Self GMD}_3 = \text{Self GMD}_1$$




$$\text{Self GMD}_2 = \sqrt[3]{0.7788 \times 1.5 \times 80 \times 80}$$

$$\text{Self GMD}_1 = \sqrt[3]{0.7788 \times 1.5 \times 80 \times 160}$$

$$\text{Self GMD}_2 = \sqrt[3]{0.7788 \times 1.5 \times 80 \times 80}$$

Q) * The self distance of each subconductor (D_s) and the adjacent distance between any two subconductors (d). The subconductors are arranged as shown below. The self GMD of the subconductor configuration is

Sol

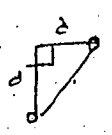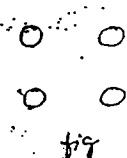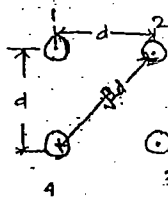

$$\therefore \text{Self GMD} = \text{Self GMD}_1 \text{ (Symmetric Sub Conductors)}$$

$$= \sqrt[4]{D_s \times d \times d \times \sqrt{2}d}$$

$$= \sqrt[4]{(D_s)^4 \cdot d^3 \cdot 2^{1/2}}$$

$\therefore \text{GMD} = \sqrt[4]{(D_s)^4 \cdot d^3 \cdot 2^{1/2}}$

(C)




$$\Rightarrow \text{Self GMD} = \text{Self GMD}_1$$

$$\sqrt[4]{0.7788 \times 1.5 \times 80 \times 160} = \sqrt[4]{(0.7788)^4 \cdot 2^{1/2}}$$

In case of bundle conductors consider the sub-conductor effect for calculation of Self GMD and ignore the sub conductor effect for calculation of GMD.

→ Eq:

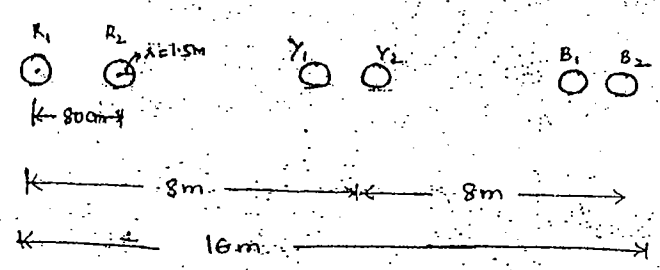


$$\text{Self GMD} = \text{Self GMD}_{R_1}$$

$$= \sqrt{0.7788 \times 1.5 \times 80}$$

$$\therefore \text{GMD} = \sqrt[3]{xy^2} = \sqrt[3]{8 \times 8 \times 16} \text{ m. (Unsymmetric)}$$

→ Eq:

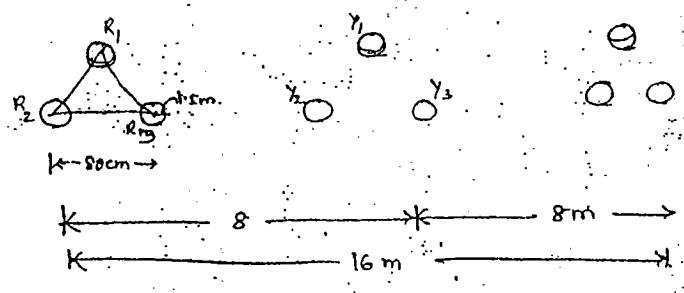

$$\text{Self GMD} = \text{Self GMD}_{R_1}$$

$$= \sqrt[3]{0.7788 \times 1.5 \times 80 \times 80} \quad (\text{Equilateral spacing})$$

$$\text{GMD} = \sqrt[3]{8 \times 8 \times 16} \text{ m.}$$

(6) If the tr. line is a long line then the impedance of the line is represented as characteristic impedance.

$$\Rightarrow \downarrow Z_c = \sqrt{\frac{L}{C}}$$

→ The Relation b/w r_1 and r_1' is

By considering the same aggregate cross sectional area.

$$\Rightarrow \pi r^2 = 2\pi r_1'^2$$

$$r_1' = \frac{r}{\sqrt{2}}$$

For three sub conductors

$$r_1' = \frac{r}{\sqrt{3}}$$

For n sub conductors

$$r_1' = \frac{r}{\sqrt{n}}$$

Self GMD

Self GMD = ?

$$GMR = GMR_R$$


$$\Rightarrow \text{Self GMD} = \text{Self GMD}_R$$

$$= \sqrt{\text{Self GMD}_1 \cdot \text{Self GMD}_2}$$


$$\boxed{\text{Self GMD} = \text{Self GMD}_R} \quad (\text{since, sub conductors are symmetric})$$

$$\therefore \text{Self GMD} = \text{Self GMD}_R = \sqrt{0.7788 \times 1.5 \times 80}$$
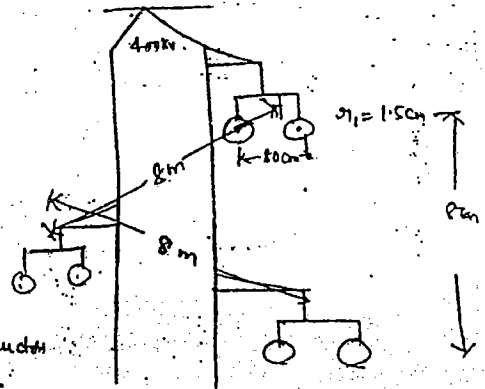
$$\therefore GMD = d = 8m \quad (\text{since voltage is same})$$



Eg:

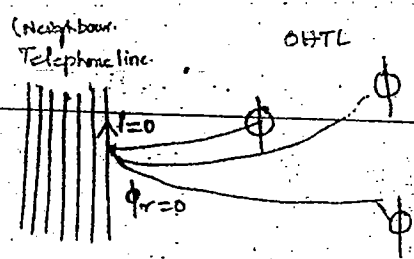


$$\frac{d\phi_r}{dt} = e = 0$$

Since $\phi_r = 0, e = 0, i = 0 \Rightarrow$ No noise in the communication

System \Rightarrow No interference

Eg: of corona discharge

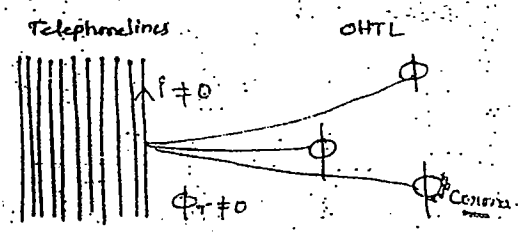

\Rightarrow Noise $\leftarrow \frac{d\phi}{dt} = e \neq 0$ Corona may not take place in every conductor at the same time.

(5) Radio interference.


(4) $L/\text{phase} = 2 \times 10^{-7} \ln \left(\frac{GMD}{r} \right) \text{ H/m}$ Bundle, is reduced, so that the inductive per phase is also reduced ($X = 2\pi fL$).

$$L/\text{phase} = 2 \times 10^{-7} \ln \left(\frac{GMD}{GMR} \right) \text{ H/m} \rightarrow \text{Normal cond.}$$

and $C/\text{phase} = \frac{2\pi\epsilon_0}{\ln \left(\frac{GMD}{r} \right)}$ is increased.

(5) The power system stability will increase because a.c transmission is synchronous transmission and by using bundle conductors the reactance per phase is reduced

$$P = \frac{E_1 V}{X} \sin \delta$$

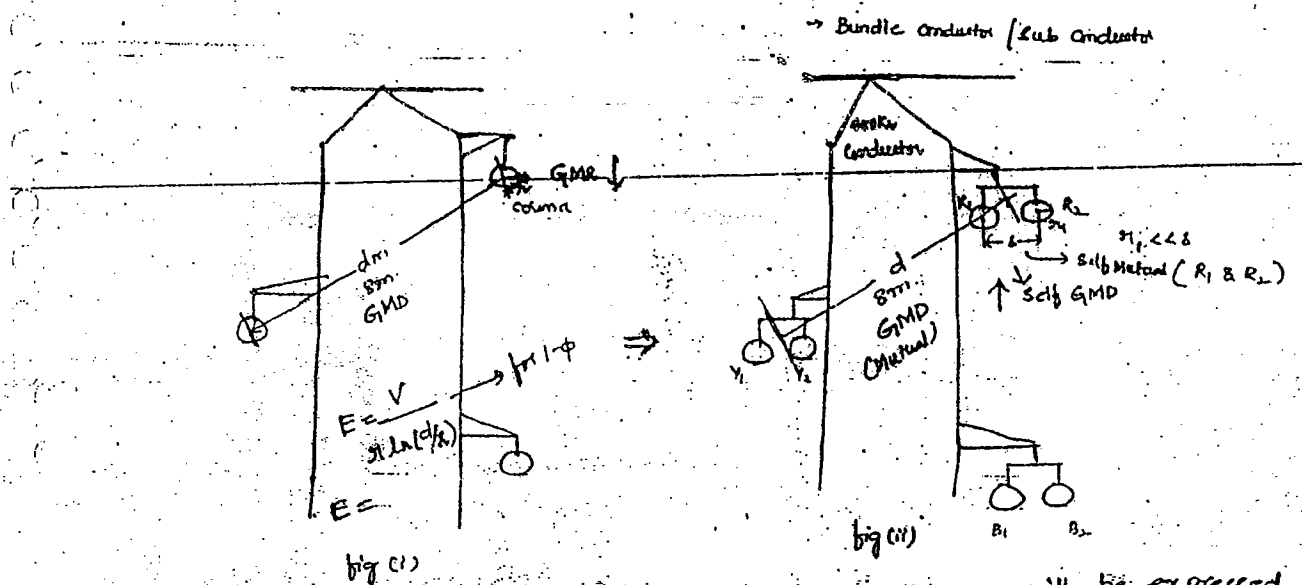

→ In case of Bundle conductors, the self distance will be expressed mathematically as "SELF GMD"

From fig (ii)

$$\text{Self GMD}_{R1} = \sqrt{r_1^2 \times 3}$$

The Bundle Conductor will result as increased self GMD without changing GMD. Since the voltages are same in either case.

$$E = \frac{V}{2.3 \ln(d/n)} \rightarrow 1-\phi$$

$$E = \frac{V}{GMR \ln\left(\frac{GMD}{GMR}\right)}$$

$$E = \frac{V}{\left\{ \text{Self GMD} \ln\left(\frac{GMD}{\text{Self GMD}}\right) \right\}^m}$$

Advantages of B.C:

- 1) The electric field intensity at the surface of each sub conductor is reduced
- 2) The corona loss is reduced because $E \downarrow$ and ionisation of air \downarrow
- 3) The communication interference with the neighbouring communication line is reduced.

57
The GMD depends upon the configuration of the conductors

→ The selection of size of the conductor for EHV line - C. Capacity
① Distributor - Voltage drop

(iii) Modern EHV line - Based on the concept of Corona.

(iv) UHV - Based on the concept of Corona

→ The selection of the insulation level for Modern EHV line is

"Switching Voltage"

→ BUNDLE CONDUCTORS

As the operating voltages are increasing, the electric field intensity at the surface of the conductor will also increase which will be difficult as the ionisation of air near the surface of the conductor and it is known as the concept of CORONA

The result of the CORONA is in the form of Corona loss which is a real power loss apart from I^2R loss. In order to avoid the concept of CORONA at higher operating voltage the BUNDLE CONDUCTORS are employed.

→ Bundle conductor consists of two or more sub conductors

per phase where the sub conductor spacing is more than the radius of each sub conductor and the sub conductors are running in parallel in order to ↑ the current capacity

→ In order to increase the

→ Each sub conductor is once again a combination of steel

2. A) in stranded manner

(1) Symmetrical Configuration

(i) GMR

$$GMR_R = r'$$

$$GMR_Y = r'$$


$$GMR_B = r'$$

$$GMR = \sqrt[3]{GMR_R GMR_Y GMR_B}$$

$$= GMR_R \quad (\because \text{radii same})$$

$$\Rightarrow \boxed{GMR = GMR_R} \quad (\because \text{self distance of all conductors is same})$$

$$= 0.7788 \times 2.0 \text{ cm}$$

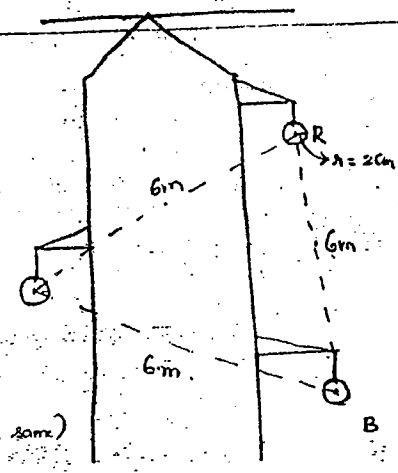

(ii) GMD

$$GMD_R = \sqrt{6 \times 6} = 6, \quad GMD_Y = \sqrt{6 \times 6} = 6, \quad GMD_B = \sqrt{6 \times 6} = 6$$

$$GMD = \sqrt[3]{GMD_R GMD_Y GMD_B} = \sqrt[3]{6 \times 6 \times 6} = 6 \text{ m}$$


$$\boxed{GMD = d} \Rightarrow \text{Equilateral Spacing}$$

(2) Unsymmetrical Configuration

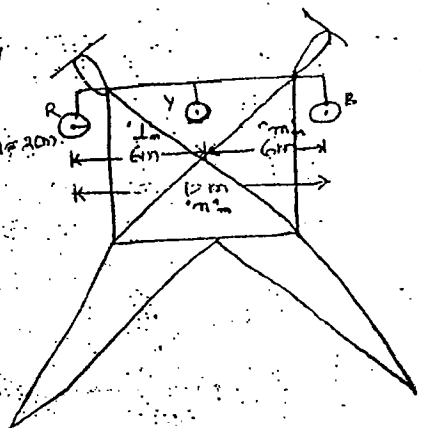(i) GMR

$$GMR_A = GMR_R = GMR_Y = GMR_B = r'$$

$$\Rightarrow GMR = GMR_R = 0.7788 \times 2.0 \text{ cm} \quad r' = 20 \text{ cm}$$



(ii) GMD

$$GMD_R = \sqrt{6 \times 12} = 6\sqrt{2}$$

$$GMD_Y = \sqrt{6 \times 6} = 6$$

$$GMD_B = \sqrt{6 \times 12} = 6\sqrt{2}$$

$$\therefore GMD = \sqrt[3]{6\sqrt{2} \times 6 \times 6\sqrt{2}}$$



$$= \sqrt[3]{6 \times 6 \times 12}$$

$$= \sqrt[3]{xy^2z} = \sqrt[3]{1mn}$$

$$\Rightarrow \boxed{GMD = \sqrt[3]{xy^2z}}$$

* The GMR only depends on the radius of conductor and it is independent of line to line distance.

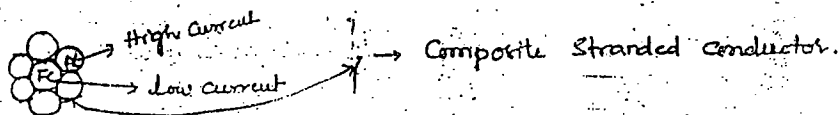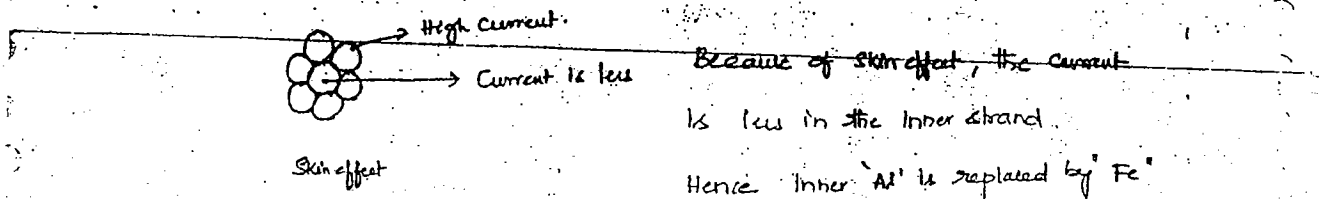→ To reduce the sag, the mechanical strength should increase



→ The purpose of the steel is to increase the mechanical strength and the purpose of 'Al' is to carry more amount of current

→ Example for composite stranded conductor is ACSR Conductor.

→ The No. of steel strands $<$ No. of 'Al' strands.

Arranging of strands for different layers $1 + 6 + 12 + 18 + 24 + 30$

→ In case of comp. stranded conductor the skin effect is further reduced because the effective area that could be utilized will be high in composite stranded conductor.

→ In case of comp. stranded conductor, the conductivity of the steel as well as the conductivity of 'Al' are properly utilized so that the total area is considered for calculation of a.c resistance.

→ ACSR → 'Al' conductor and steel reinforced (or) steel reinforced 'Al' conductor

→ ACSR is represented mathematically as $\frac{x}{y}$ ratio

x → either 'Al' (or) Fe strands.
 y → either 'Al' or Fe strands.

Ex: An ACSR conductor consisting of 30 Al and 7 Fe strands then it

is represented by $\frac{30}{7}$

→ As the skin effect is high, then Rac is high because d is less.

→ skin effect


$$L_{in} \uparrow, L_{ext} \downarrow$$

$$\uparrow L = L_{in} + L_{ext}$$

→ As the area of c/s of conductor increases for same amount of current then, the effective area utilized is less then skin effect is high.


As a \uparrow \Rightarrow a' \downarrow \Rightarrow Rac according to skin effect

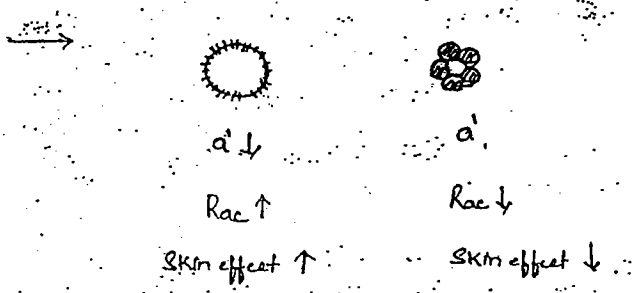
~~Rac $\propto a$~~
 Skin effect $\propto a$ $a \rightarrow$ Area
 Skin effect $\propto d^2$ $d -$ diameter




→ Hence Stranded conductors are preferred than Solid Conductors.

→ And the stranded conductors are replaced by Composite Stranded Conductor

 Copper Stranded Conductor \rightarrow Cost is high \rightarrow UnEconomical.


 \rightarrow Al Str. Conductor \rightarrow Cost is less but \rightarrow Mechanical Strengths is less

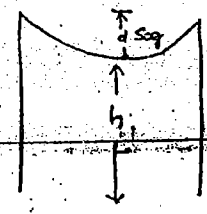As Mech. strength is less \rightarrow Sag \uparrow and ground clearance decreases.



which is an external wire so that the magnitude of the lightning wave is directed to the ground.

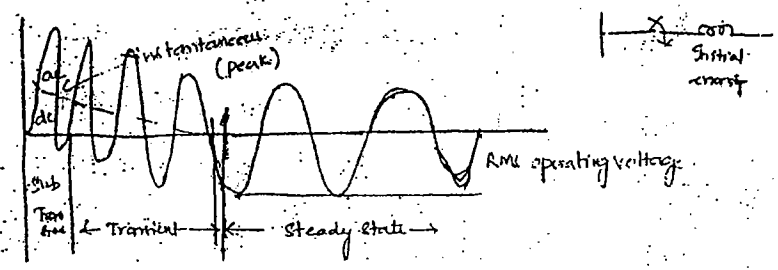- Ground wire is normally made up of Galvanized steel material.
- The lightning voltage can be divated by using Surge diversion Technique.
- When the switch is closed, because of inductance effect of the Hence the wave form is as below.




→ Hence the insulation level selection is based on the Peak values of the switching voltage.

→ DIFFERENT TYPES OF CONDUCTORS


- Solid conductors
- Stranded conductors
- Composite stranded conductors → for $V \leq 220kV$
- Bundle conductors → for $V \geq 275KV$.

SOLID CONDUCTOR (Copper)

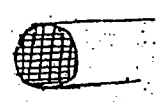

→ It made of a solid copper.

STRANDED CONDUCTOR (Copper)

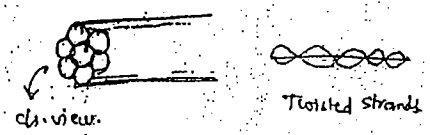

→ It consists of two or more smaller c/s strands and they are twisted.

→ High electrical conductivity.

→ The selection of Insulation level for EHV line (or) Distributor → Switching Voltage

— The selection of Insulation level for EHV line (or) Distributor is based

on the switching voltage (or) switching surge (or) Internal Voltage.

(or) Internal surge


→ The operating voltage of a 3- ϕ , 3-wire tr. line will be Line to Line RMS

Power is 3- ϕ always.

$$\Rightarrow S = \sqrt{3} V_L I_L \Rightarrow 3-\phi$$

→ Operating voltage: A voltage at which the system is working stable and

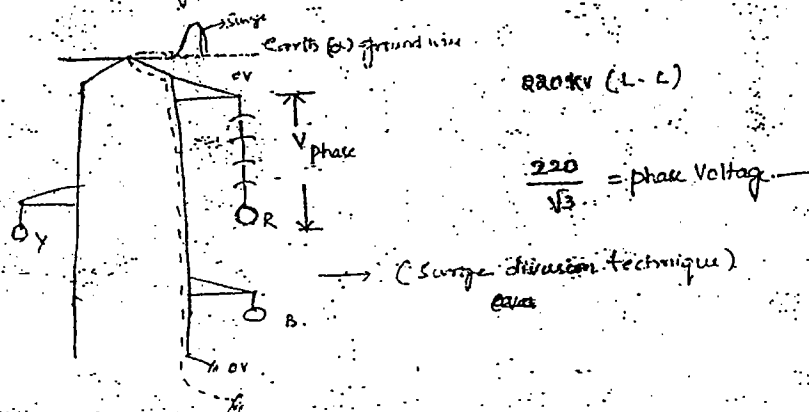the generator working in synchronous speed.



→ Overvoltages on the tr. line because of (1) Direct lightning effect (External)
(2) Switching effect (Internal), these are called as "Surge"


— Any uneven wave form is called "Surge"

— For any given tr. line the magnitude of the lightning voltages are high when compared to the magnitude of switching voltages.

If the lightning is allowed the insulation can be selected for lightning voltages, so that amount of insulation is high, cost of it is high

→ In order to reduce cost of insulation the lightning voltage can be diverted by running a ground (or) earth wire on the top of the tower

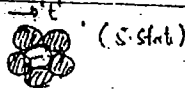— Hence most of the current is concentrated on the outer surface of the stranded conductor.



$$R_{a.c} = \frac{\rho l}{a'} \quad (\text{Rms Resistance})$$

where $a' \rightarrow$ Effective area that is utilized.

$$a' < a$$

$$R_{a.c} > R_{d.c}$$

$$R_{a.c} = K \cdot R_{d.c}$$

$$K = 1.6$$

SKIN effect.

→ When the switch is closed, then the instantaneous currents in the strands will produce the corresponding fluxes. The flux produced by the outer strand will link with inner strand in addition to its own strand. The flux produced by inner strand does only link with its own strand, so that the total flux linkages for inner strands is high and for outer strands is less. The amount of ϕ linkages produced will offer an inductance to the strands.

→ As the internal flux linkages are high, then the inductance offered for inner strands is high, whereas as for outer strands is less.


— The inductance is the one which can oppose initially the flow of current through the strands, so that most of the current is concentrated on the outer strands. If the current can carry in such manner for a period of 't', then the resistance which is offered is called as a.c. resistance.

$$R_{a.c} = \frac{\rho l}{a'} \quad \text{where } a' \rightarrow \text{effective area that is utilized.}$$


$R_{a.c}$ & SKIN effect

→ High Mechanical Strength

→ They are in the form of rods (small)

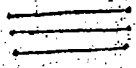

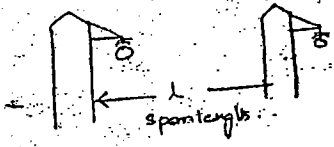
→ It is difficult to connect continuously by stringing solid conductors and difficult to transport



- $l = 300\text{m} \rightarrow$ for 132KV.
- $l = 350\text{m} \rightarrow$ for 220KV.
- $l = 400\text{m} \rightarrow$ for 400KV.

→ In ac system it deals with high skin effect

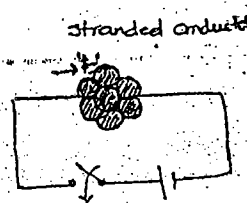→ SKIN EFFECT: If the conductor carries an alternating current then most of the current will be concentrated through an outer surface of the conductor, hence the current distribution is non-uniform in the conductor, because of the non-uniform distribution of flux linkages



DC resistance (ohmic resistance)

$$R_{dc} = \frac{\rho l}{a}$$

$a = \text{total area of cs}$

→ All the strands are strung in parallel in order to increase the current carrying capacity

→ High electrical conductivity


→ Required mechanical strength

→ It can wound like a spring



→ It is easy to transport and stringing of the conductor

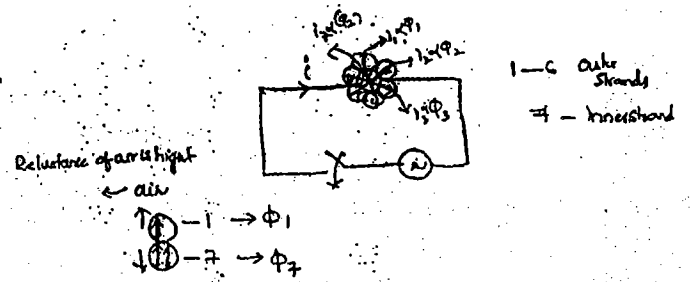→ In ac system it will offer a low skin effect.



Reluctance of air is high

$$\uparrow \text{air} \rightarrow \phi_1$$

$$\downarrow \text{air} \rightarrow \phi_2$$

$\phi_2 \rightarrow$ flux linkages are high

since flux linkages are high then

the inductance is high

The tr. line having one conductor in each phase with the radius of 'r'. The self distance of the conductor w.r.t the same conductor is 'radius' 'r' and the mean of which is also called as "radius".




$$GMR = r' = r^n$$

$r' \rightarrow$ Imaginary radius

$r' = 0.7788 r$ because of skin effect of the conductor.

$$GMR = r'$$

GMD:

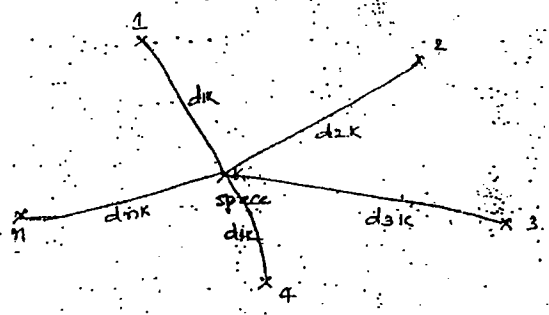

A point 'K' in the space is surrounded by 'n' other points. The Equivalent distance of 'K' w.r.t 'n' other points will be the Geometric mean of the individual distances between the reference point and each individual point.

$$GMD_K = \sqrt[n]{d_{1k} d_{2k} d_{3k} \dots d_{nk}}$$

The tr. line will be two configurations physically as

(1) Symmetrical Configuration \rightarrow Equilateral spacing


(2) Asymmetrical Configuration \rightarrow Flat horizontal spacing

EX: If conductor (ACSR) consists of 7 'Steel and 30 'Al' then it

is represented as $\frac{7}{30}$

→ ACSR represented as $\frac{54}{7}$ then, 54 — Al
7 — Fe.

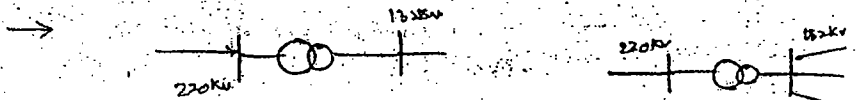→ $\frac{7}{30}$ Al → 132 kV, $\frac{7}{54}$ Al → 220 kV.



power handling is same.

power handling is not same.

→ Hence for all practical purposes the size of the conductor increases as the power handling capacity increases.

22/01/10

→ MATHEMATICAL CONCEPTS

GMR — Geometric Mean Radius → self distance

GMD — Geometric Mean (of) Mutual Distance → mutual distance.

— Transmission lines are normally 3- ϕ , 3-wire and it requires the calculation of the line constants in a phase manner, the GMR & GMD are useful to calculate the inductance per phase and capacitance per phase at a faster rate.

→ Arithmetic Mean → plane co-ordinates

→ Geometric Mean — Space Co-ordinate

GMR: The self distance of a point is the distance from the centre towards the circumference w.r.t same point in the space.

$$a \propto \frac{1}{V^2 \cos^2 \phi}$$

if p.f. is constant.

$$a = \frac{k'}{V^2}$$

$$\frac{a_1}{a_2} = \frac{V_2^2}{V_1^2} = \frac{\eta^2 V_1^2}{V_1^2}$$

$$\Rightarrow \frac{a_1}{a_2} = \frac{\eta^2}{1}$$

$$\Rightarrow \boxed{a_2 = \frac{1}{\eta^2} a_1} \quad \checkmark \quad (\text{for same efficiency also})$$

→ For the same power, same material, and same length if the operating voltage of a distributor increased by 'n' times, the area of c.s. of distributor

is $a_2 = \frac{1}{\eta^2} a_1$

* The selection of size of conductor in Distribution System is "Voltage drop"

ie "1% Voltage drop" criteria.

V_1 , I_1 and R_1

$$\frac{I_1 R_1}{V_1} \times 100$$

$$\frac{I_1 R_1}{V_1} \times 100$$

V_2 , I_2 and R_2

$$\frac{I_2 R_2}{V_2} \times 100$$

$$= \frac{I_1 R_2}{\eta V_1} \times 100$$

$$V_2 = \eta V_1$$

$$I_2 = I_1 / \eta$$

$$\Rightarrow \boxed{R_2 = \eta^2 R_1}$$

$$\boxed{a_2 = \frac{1}{\eta^2} a_1}$$

→ For same material, same length, same power, same power loss, if the voltage is increased by n times then area of c/s of conductor is

Power loss:

$$P_2 = \frac{1}{n} P_1$$

$$P_1 = I_1^2 R_1$$

$$P_2 = I_2^2 R_2 = \left(\frac{I_1}{n}\right)^2 \cdot n R_1 = \frac{I_1^2}{n} R_1 = \frac{P_1}{n} = \frac{P}{n}$$

As Loss is reduced, the efficiency is increased.

Since $\uparrow \eta = 1 - \frac{K}{V \cos \phi}$

$\left\{ \begin{array}{l} \text{K} \leftarrow \text{Constant} \\ \downarrow \\ V \cos \phi \end{array} \right.$

$$\% \eta = \left(1 - \frac{K}{V \cos \phi}\right) \times 100$$

→ As the operating voltage and the power factor are high, then the η is high.

→ For same power, same length, same material, same loss of the operating voltage of EHV is increased by n times then the area of c/s of the conductor is

$$a_2 = \frac{1}{n^2} a_1$$

$$P = VI \cos \phi$$

$$I = \frac{P}{V \cos \phi}$$

$$\text{Loss } p = I^2 R = \frac{I^2 \rho l}{a} \Rightarrow a = \frac{I^2 \rho l}{p}$$

$$\Rightarrow a = \left(\frac{P}{V \cos \phi}\right)^2 \frac{\rho l}{p}$$

$$= \frac{P^2}{V^2 \cos^2 \phi} \frac{\rho l}{p} = \frac{K}{V^2 \cos^2 \phi}$$

→ In an element where the magnitude of the current varies

through out its length is called electrically a DISTRIBUTOR, where

the current density is variable

→ The selection of size of the conductor for EHV line:

→ The selection of size of the conductor for EHV line is based

on the CURRENT CARRYING CAPACITY ($\because V = \text{const}, P = V \cdot I$)

→ Current carrying capacity is nothing but "const. current density"

For distributor:

→ The selection of size of the conductor for distributor is based on "voltage drop"

→ For same power, same material and same length, if the operating voltage of EHV line (OR) feeder is increased by 'n' times then area of the c/s of the conductor is $a_2 = \frac{1}{n^2} a_1$

Exp

$$P = V_1 I_1 \cos \phi$$

$$P = V_2 I_2 \cos \phi$$

$$\Rightarrow = \eta \sqrt{a} \cdot \frac{I}{\eta} \cos \phi$$

$$P = VI \cos \phi$$

$$V_2 = n V_1$$

$$I_2 = I_1 / n$$

→ The selection of size of conductor in EHV line is based on Current Carrying Capacity

$$\Rightarrow I \propto a$$

$$I_1 \propto a_1$$

$$I_2 \propto a_2$$

$$I_2 = \frac{I_1}{n}$$

$$\Rightarrow a_2 = \frac{1}{n^2} a_1$$

→ As the line side of tff is always STAR with Neutral grounding so that the tr-lines are always electrically 3-φ Y. So, that




$$V_{\text{phase}} = \frac{V_L}{\sqrt{3}} \quad \text{and} \quad I_{\text{ph}} = I_L$$

→ For the lengths of the line $> 500 \text{ km}$ we prefer HVDC transmission

→ In India, max HVDC transmission is $\pm 500 \text{ kV DC}$.

→ For the lengths of the line $< 500 \text{ km}$, A.C transmission is preferred for economical reasons.

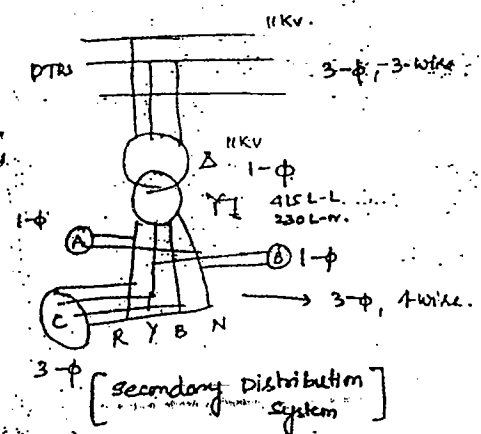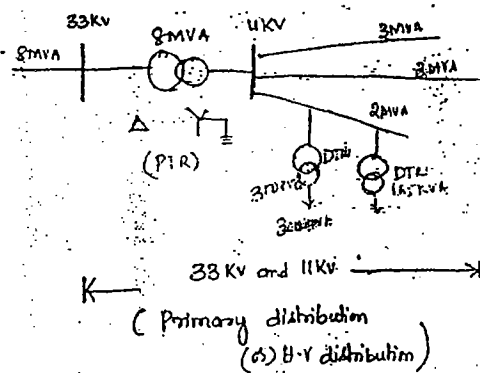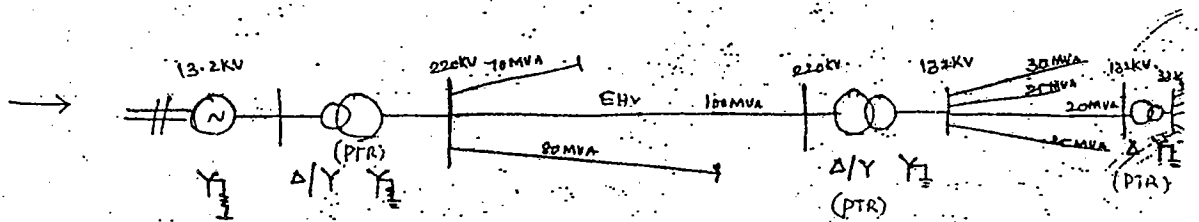→ According to protection system, the source end of the tr-line will be provided with neutral grounding



→ If the magnitude of the current that could be carried out throughout its length is same then such a current carrying element is called FEEDER, hence EHV lines are called FEEDERS.

I of a

$$I = J \cdot a$$

$$J = I/a \rightarrow$$

A Feeder is also called

a

constant current density element

→ If there is any 3-φ fault in a single str. line then

$$P = P_s - P_c$$

$$P = P_s - 0$$

$$P = P_s$$

= (accelerated because of +ve power) ↑

lly if there is any 3-φ fault in any one of the parallel tr. line

then

$$P = P_s - P_c \downarrow$$


$$= +ve$$

= acceleration ↓

→ The a.c power transmission from the syn. m/c to the load is asynchronous transmission. i.e. it is associated with 180° stability.

→ In order to maintain the s. state stability and also the transient stability, the tr. lines are proposed with parallel lines.

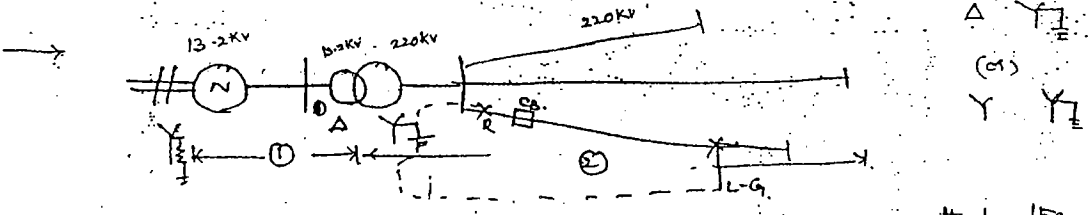→ By using parallel lines the net reactance of the system is reduced and also the acceleration property is reduced during the fault condition.




→ While selecting the t/t wdg it should ensure that the fault in one electrical m/w should not reflect in another electrical m/w so that the line side of the t/t must be star with grounding whereas the source side of the t/t is isolated grounding.

H.V. \rightarrow Modern EHV \rightarrow 400kv. (AP Transco) --

H.V. \rightarrow UHV \rightarrow 765kv and above. (PGCIL)

\rightarrow Maximum transmission in India is 765KV (PGCIL)

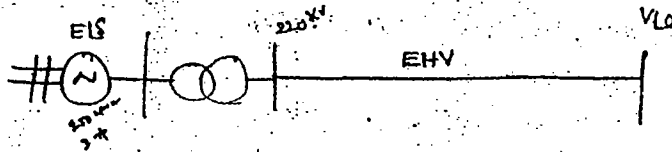\rightarrow Based on the distance of transmission, the selection of the transmission voltage is considered.



$$S = \sqrt{3} V_L I_L$$

$$I_L = \frac{250 \times 10^6}{\sqrt{3} \times 220 \times 10^3}$$

$I_{phase} \downarrow \Rightarrow I_L \downarrow \Rightarrow a \downarrow \Rightarrow w \downarrow$


Therefore:

(i) Cost is less.

(ii) $P_L = 3I^2R \downarrow$

(iii) $\% \eta \uparrow$

12/01/10

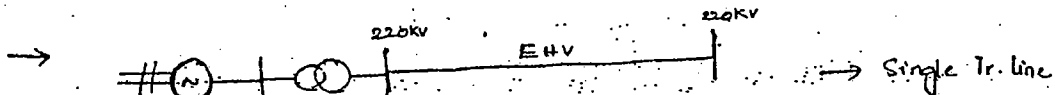

250MVA
3- ϕ
SOTH.
PF=0.8


\rightarrow P.V.
 \rightarrow Q.

$$P_L = \frac{E_V \sin \delta T}{X_{eq} \uparrow} \quad \delta T$$

($R \ll X$) [loss less]

$$= 250 \times 0.8$$

\rightarrow Parallel line:

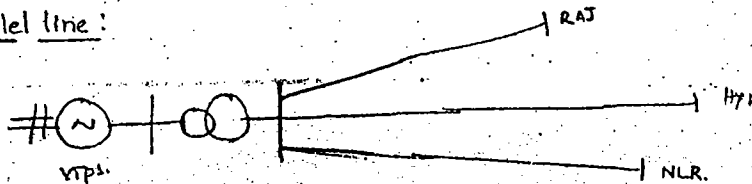


$$P = 250 \times 0.8$$

$$P = \frac{E_V \sin \delta \downarrow}{X_{eq} \downarrow} \Rightarrow \delta \downarrow \leq 70^\circ$$

The Reactance X_{eq} reduce in parallel tr. line decreases. Hence

the power transmission is same.

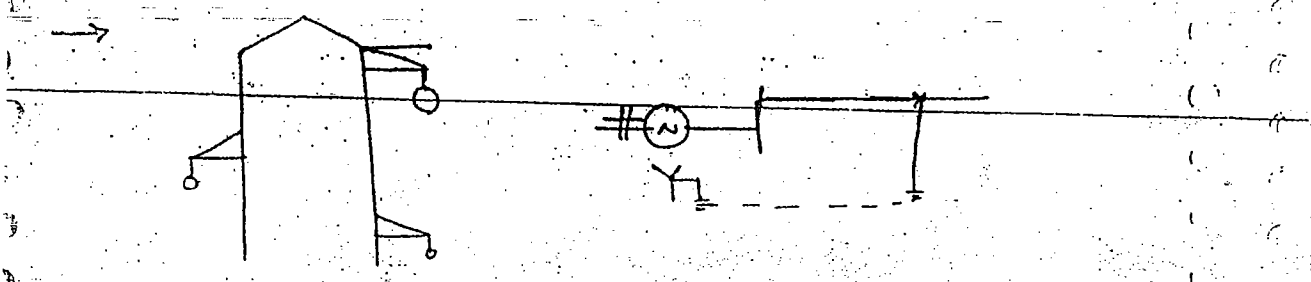


→ The H-lines are not having any neutral grounding but the grounded fault in H-lines will be closed through the neutral grounding of the generator. Hence if gen - Y_1 then H.L. is also "Y"

Disadvantages of HV TX system

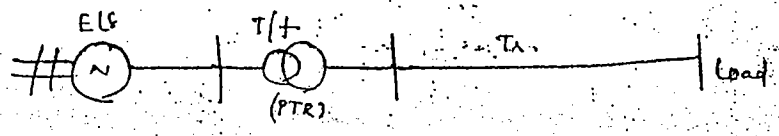- (i) $I_{phase} = I_L$
 - ⇒ $I \propto a$
 - ⇒ $a \uparrow \rightarrow \text{weight} \uparrow \Rightarrow \text{ax l.}$
 - ⇒ Cost \uparrow
- (ii) Power loss = $3 I^2 R \uparrow$
- (iii) % $\eta \downarrow$

→ In order to overcome all the disadvantages, we have to change the electrical quantities V, I without changing power. Hence a t/t is connected.



- Power transformers (PTR) → 1 MVA and above
- Distribution t/t → $\leq 500 \text{ KVA}$

→ To change electrical characteristics H.V $\begin{cases} 66 \text{ Kv} \\ 132 \text{ Kv} \\ 220 \text{ Kv} \end{cases}$

~~A syn m/c is a diversity character note~~

→ A syn m/c → Speed Regulation

→ For a system to be stable the angle is $0 \leq \delta \leq 90^\circ$

As δ changes → Speed changes → Frequency changes.


→ "Y grounding" is required because of Grounded faults taken

into considered.

→ L-G faults are frequently occurring faults in the system.


→ The system is dealing with grounded faults and also with isolated grounded faults, in order to provide a closed path for fault current in case of ground faults, it is necessary to employ neutral grounding.

(Resistance grounding)

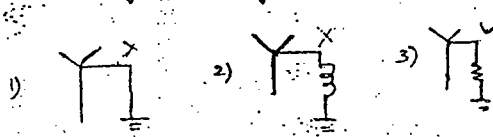

→ It improves the stability of the syn m/c during fault condition and also provide closed paths

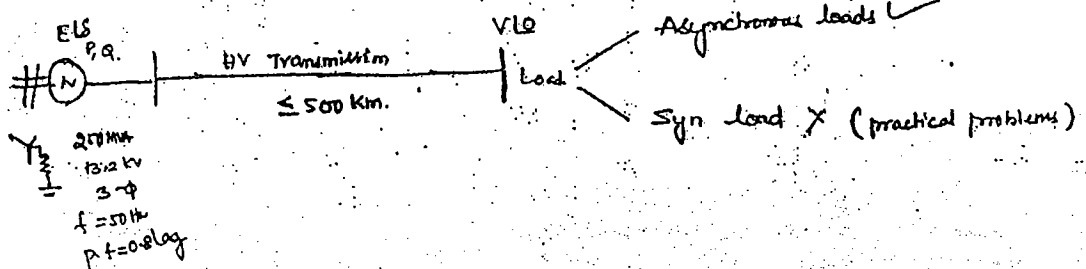→ The Resistance grounding can be employed to provide the closed paths and also to improve the stability of the system.




→ Disadvantages of HV transmission

$$(1) S = \sqrt{3} V_L I_L$$

$$I_L = \frac{250 \times 10^6}{\sqrt{3} \times 270 \times 10^3}$$

$$I_{ph} = I_L \text{ (Y system)}$$

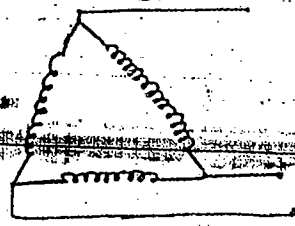

3-φ Δ (or) closed (or) Shunt wdg


→ Voltage and current are per phase values and
 Power is always a 3-φ since, size of conductor & insulation is decided.

$S = \sqrt{3} V_L I_L$ 'Y' → $V_{phase} = \frac{V_L}{\sqrt{3}}$, $I_{ph} = I_L$ ⇒ More weight of conductor is required.

$S = \sqrt{3} V_L I_L$ Δ → $V_{phase} = V_L$, $I_{ph} = \frac{I_L}{\sqrt{3}}$ ⇒ More amount of insulation is required.

→ Cost of the equipment = Conductor^{cost} + Insulation cost


→ Single Line Diagram (SLD)

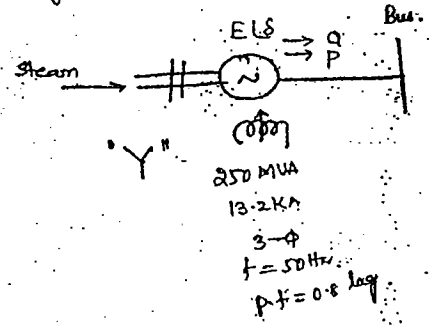

→ When there is unbalance in the load because of faults, the electrical quantities become more than the rated values. Hence there are chances of failure of insulation and results in damage of equipment which can

→ To employ effective protection system in a phase manner, the alternator star wdg is preferred as a 3-φ Y-winding

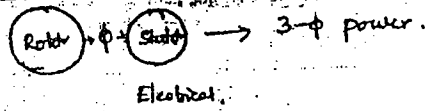→ Power Generation — Electrically $\begin{cases} 1\text{-phase} \\ 3\text{-phase (Bulk amount of power)} \end{cases}$



→ Three phase is nothing but '3- Single phases' are suitable. Connected as \underline{Y} or $\underline{\Delta}$

→ The physical appearance of electric equipment

(i) Conductor → Carry the current

(ii) Insulation → To provide electrical isolation with other surfaces, so that the leakage current is prevented.

→ The selection of the size of the current conductor is based on current carrying capacity ⇒ $I \propto a$ ✓

→ The insulation is based on the voltage. ~~through~~

⇒ $\text{Insulation} \propto \text{voltage}$ ✓


⇒ $E \propto V \propto \text{Insulation} \rightarrow \text{dielectric strength (KV/cm)}$

Dielectric strength \uparrow ⇒ thickness of insulation \uparrow

⇒ Voltage \uparrow ⇒ thickness of insulation \uparrow


→ Voltage and Current are called Basic electrical quantities which are crucial to design the electrical equipment.

→ For a 3- ϕ phase system.

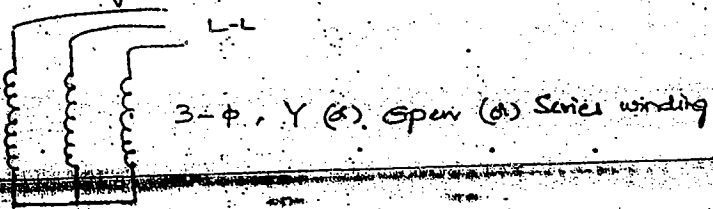

→ The Nature of Current in MHD is dc current

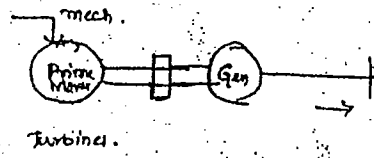→ Most of the power is generated based on Rotational principles



→ Normally for generation, synchronous generator (or) alternators are used.

→ For Non-Conventional Sources: Generators used are

1) Asynchronous Generators

Ex: Induction generator.

→ Most of the Conventional plants are located at Remote places by fulfilling the geographical conditions.

→ Where as for N.C plants are located near the load points.

→ Application:

Conventional

- Except gas plants, the remaining are suitable for base loads plants.

→ Generation — Transmission
↓
Distribution.

→ The Bulk amount of power is generated at remote places and it is needed to be carried over a longer distance through transmission and then


followed by distribution.

N.C.

→ Except Geothermal plants, the remaining are suitable for Peak loads.

→ The amount of power generation is very less so that the available power can only distributed from the generation to the nearer load points by using D.

Ex:

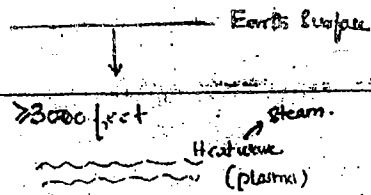


* Heat waves can be identified where there are frequent eruption of volcanoes

→ Wind Mill: pressure of the wind (Mech) is converted into electrical energy

→ Latest Range is 1 MW plant each

→ Started with 20 kW

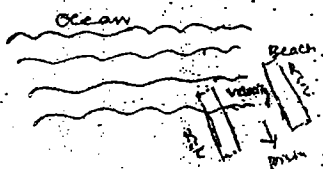
→ TIDAL plant: The velocity of the tide in the ocean (Mech) is converted into electrical energy



Turbine used: "Bulb Turbine" which is Kaplan turbine

→ Solar: Fuel: Sun light

→ MHD:

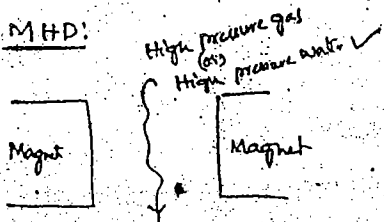

→ If the high temperature is allowed to flow b/w the two magnets the emf is induced in the magnets which is connected to the load (EMI)

1) Steam (or) Thermal: The high pressure and high temperature steam (Mech energy) will be converted into Electrical Energy

- pressure → 100 to 160 kg/cm²

- Temperature → 540°C

For captive plants: 7 kg/cm² (10 MW)


↳ (For self purposes)

(2) Hydel: Most of the Hydel plants are of Reservoir type.

- The potential energy of the stored water is first converted into kinetic energy and then later into electrical energy.


(3) Nuclear: steam (or) thermal plant but in place of boiler, a Nuclear reactor is placed.

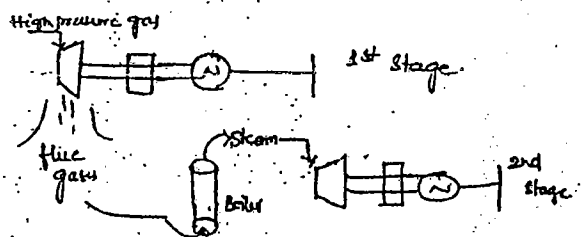(4) Gas: The high pressure gas is converted into electrical energy → 1st stage



Called as combined cycle (or) two stage

5) NO atmospheric pollution

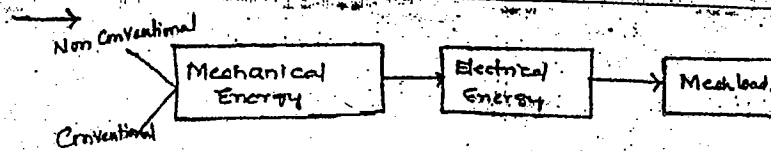

Mechanical energy can be obtained by (1) Conv (2) Non-Conv.

Non Conventional

1) Small Capacity power generation for a short interval of time

EX: Solar, wind, Tidal, Biomass, Geothermal and Magneto Hydro Dynamo generator. (MHD)

→ KW - Few (MW) with Voltage of 230V, 650V and 11KV.

→ Hence low voltage category.

→ Biomass plants: generation is based on steam

→ Grass Fuel: pulp of the sugar - Cane, waste material of paddy, ground nut. e.t.c

→ Recently huge no. of plants are in demand

→ Geothermal: It is also based on steam plants principle

Fuel: No fuel (Fuel less)

CONVENTIONAL

1. Bulk amount of power generation over a longer period

EX: Steam (or) Thermal, Hydel, Nuclear and Gas.

→ With Few MW to 500 MW with range of voltage 33KV, 66KV


11KV, 13.2KV, and 22KV. Hence

comes under high voltage upto 33KV

→ Max voltage generation levels in India is 22KV

$$\uparrow E \propto N \uparrow \Phi \uparrow$$

EX: (1) For 15 MW

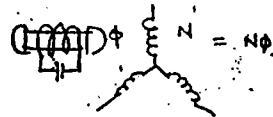

(2) For 100 MW the size of rotor field and stator increases.

→ 62% of power is by Steam
33% from Hydel.

5% from Nuclear, Gas and

→ POWER SYSTEM: It is the system which deals with the almost

all electrical equipment which are placed at different locations

depends on the requirement and they are all working together
to deliver electrical energy to the consumer on Economical basis




— Electrical Energy: Electrical power over a period of time.

The need of Electrical energy is—

1) To have an artificial illumination in order to see the
objects very clearly (10%).

2) To drive the mechanical loads (90%).

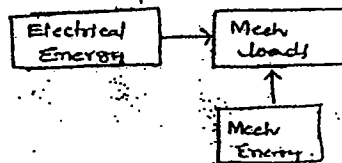

EX: Traction system

→ (1) The transformation of electrical energy into a mechanical ^{energy} ~~load~~ will be more effective so that the energy loss in the system is less and finally the efficiency is high.

(2) If the power can be generated in a bulk manner then it is more economical.


(3) By employing effective monitoring system then the interruptions to the system are less so that the reliability of the supply is high.

(4) Easy control over the electrical energy in the form of switches.

distribution of charge can be replaced by single equivalent charge for the calculation of capacitance.

- Zero potential plane means → potential is "ZERO" always.
- Equipotential plane can be zero potential but converse is not true.
- For the safety of the electrical system it is preferred to consider the earth as ZERO potential plane.

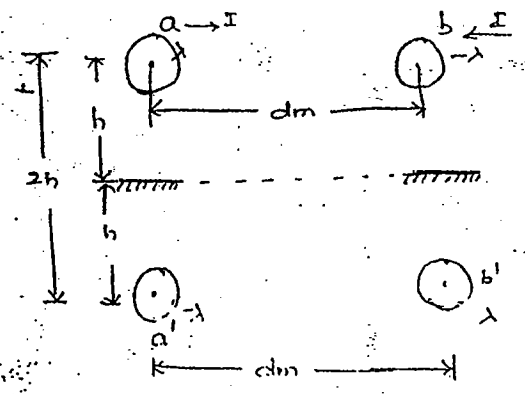By considering a conductor at a depth of 'h' from earth to calculate the earth effect.





$C_{ab} = \frac{\pi \epsilon_0}{\ln \left[\frac{d}{2 \left(1 + \frac{d^2}{4h^2} \right)^{1/2}} \right]}$ F/m → Effect of Earth

$C_{ab} = \frac{\pi \epsilon_0}{\ln \left(\frac{d}{r} \right)}$ F/m → Isolated Earth


→ of the effect of earth is considered the value of capacitance will increase when compared to isolated earth

Eg:

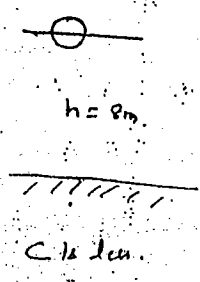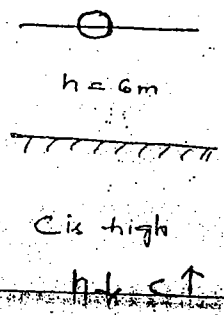

→ In General, in all practical cases, the calculation of Capacitance is by Isolated Earth Concept

Reason:

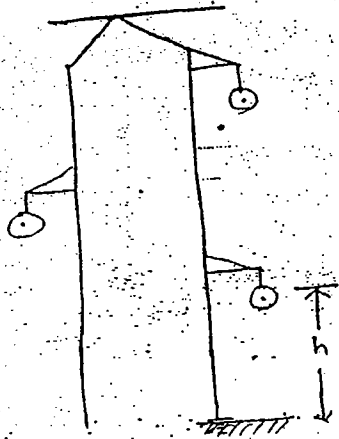

* The electric flux cannot reach the earth for such ~~large~~ ^{more} heights. Hence isolated earth is considered.

= 6.1 m for 132 KV
 = 7.1 m for 220 KV
 = 8.5 m for 400 KV.

⇒ R L X_L C B_s ($X_c = \frac{1}{B}$)

lengths ↑ ↑ ↑ ↑ ↑ ↑, X_c ↓ ($X_c \propto \frac{1}{L}$)

Eq: A 100km tr-line having a charging reactance of 50Ω. What is the charging reactance if the length of the line is 200 km.

$$X_c \propto \frac{1}{L}$$

$$\frac{x_{c1}}{L_1} = \frac{x_{c2}}{L_2} \Rightarrow \frac{50}{100} = \frac{x_{c2}}{200}$$

$$x_{c2} = \underline{\underline{25}}$$

24/11/10


64

→ PERFORMANCE OF TRANSMISSION LINES:

→ The performance of any electrical equipment can be analysed by using efficiency and Regulation of that equipment.

Regulation $\left\{ \begin{array}{l} \text{Speed (Rotating equipment)} \\ \text{Voltage (Static equipment)} \end{array} \right.$

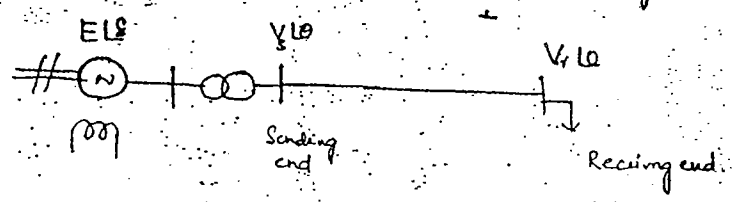
→ Hence for Transmission lines $\left\{ \begin{array}{l} \text{Efficiency} \\ \text{Voltage Regulation} \end{array} \right.$



$\theta \approx 0$

Since $Z_T \ll Z_L$

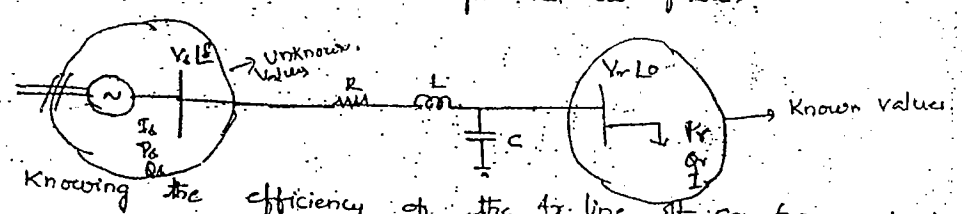Trans. line can be represented as follows



By knowing the efficiency of the tr. line, it can be understood the amount of energy loss in the form of heat which is not recovered

→ If the efficiency of the tr. line is high then the energy loss is less so that the performance of the tr. line will be satisfactory.


$$\% \eta = \frac{P_r}{P_s + 3I^2R} \times 100$$

→ The trans. line η as well as the voltage Regulation can be calculated by knowing the sending end voltage & sending end current with the help of the receiving end voltage and the receiving end current along with tr. line constants.

→ Generally the Tr. lines are more efficient because

$$\eta = \frac{P_r}{P_s + 3I^2R} \rightarrow \text{very less (by default)}$$

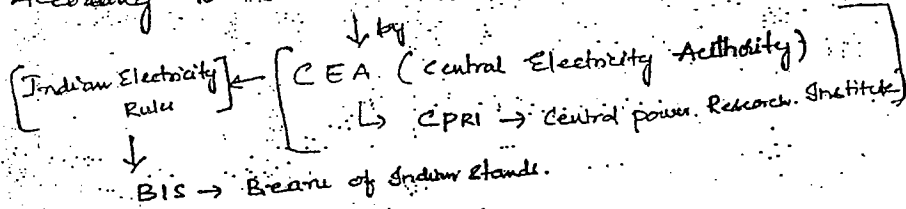→ According to Indian standards the power loss is (2-5)%



→ The loss in the distribution network is (8-10)%

→ The Tr. & Dr loss is (10-15)% i.e. Ohmic loss (Tech loss) (I²R + Mech)

In addition to that Commercial loss

$$\text{loss} = \text{Tech loss} + \text{Commercial loss}$$

Commercial loss includes:
 ① Meter loss, i.e. meter which is not working
 ② Unauthorized tapping of energy

→ VOLTAGE REGULATION:

It is the change in the voltage of the receiving end from no load to full load while keeping the sending end voltage constant and also the supply frequency is made as constant

$$|V_{r0}| = \text{No load Voltage}$$

$$|V_r| = \text{Full load Voltage}$$

$$P = P_m - P_e$$

$$= 0$$

$$N = N_s \rightarrow f = 50 \text{ Hz}$$

by keeping excitation constant

$$\% \text{ Regulation } \%E = \frac{|V_{r0}| - |V_r|}{|V_r|} \times 100 \quad \text{volts (or) K.V.}$$

→ Regulation is expressed in 1-φ where as the efficiency in 3-φ


Since power is in 3-φ and voltage is in 1-φ.

→ If the Regulation of tr. line is low then there will be a better voltage at the load point so that the performance of the load is satisfactory, which in turn the performance of the tr. line is satisfactory.

→ Quality of the supply to the consumer is in the form of VOLTAGE

→ The Regulation of a tr. line is decided by L & C of the line.

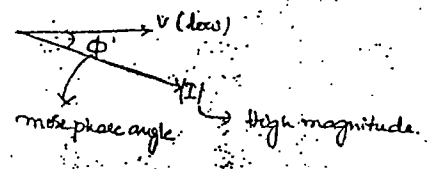→ Eq. 8 If the magnitude of voltage is low.




$$S = VI \cos \phi + jVI \sin \phi$$

$$P + jQ$$

$P \downarrow \Rightarrow$ poor quality.

② If voltage is high

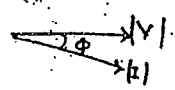

$$S = VI \cos \phi + jVI \sin \phi$$


$$= P + jQ$$

\hookrightarrow high quality.


In General

→ Regulation of the tr. line is not exactly same as the voltage drop of the tr. line

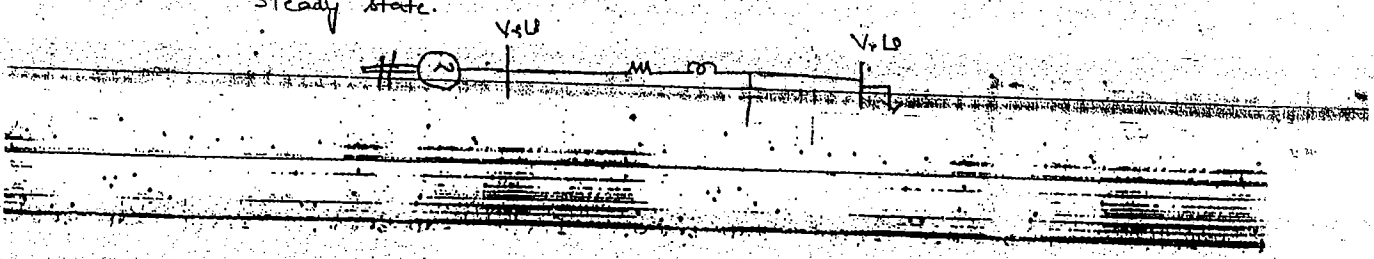For all the above cases the tr. line is considered as Steady state.




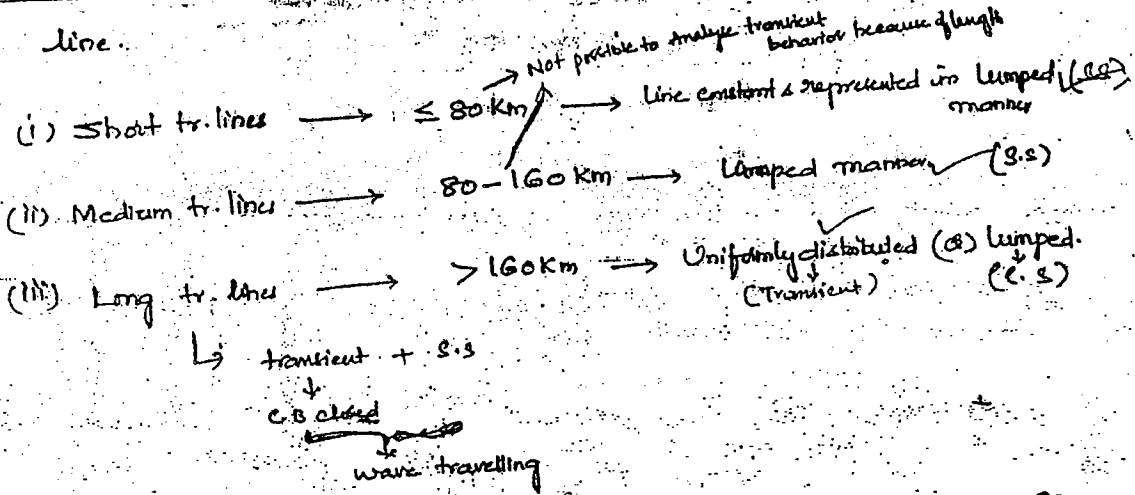→ The performance of the tr. lines can be analysed by representing the line electrically based on the physical length of the line.



→ If the lines are represented in lumped manner → then we can use KCL and KVL for analysis

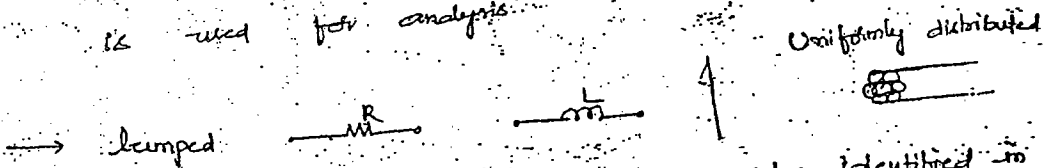→ If the line is distributed uniformly the mathematical approach is used for analysis



→ A lumped element is one which can be identified in physical manner and also separated electrically.

→ Uniformly distributed is the one which cannot be identified physically and also not possible to separate electrically.

→ In general any tr. line consisting of a stranded conductor and it is represented in a uniformly distributed manner.


- Regulation of lines & efficiency
- 1) STL → %E = ± 6%, $\eta = 95\%$
 - 2) MIL → %E = ± 9%, $\eta = 97\%$
 - 3) LTL → %E = ± 12%, $\eta = 98\%$

→ In STE, $C \approx 0$ since Cap/Km is negligible (ZERO Assumed) because of length is short. ($\therefore R$ & L are considered)

→ As the length of the line is short, so that the shunt capacitance can be assumed as ZERO ($C \approx 0$)

→ For medium line, R, L & C
 → For long line, R, L & C } are considered.

→ SHORT LINE:

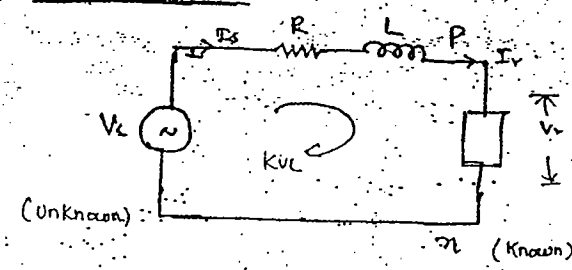

→ Medium Line: This is of '4' network models based on the shunt capacitance placement

Most commonly employed because these are of symmetrical representation


1) Nominal - T: → shunt capacitance is at the middle of the line

2) Nominal - Π : → shunt capacitance is placed on both sides of the line with equal magnitude

3) Load End Capacitance: Shunt cap is placed at load end.

4) Sending End Capacitance: Shunt Cap is placed at source end.


1) Nominal - T:

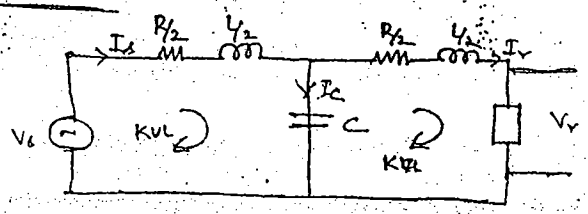

3 equations to solve for V_s & I_c .

I_c is upto middle of the line.


(2) Nominal- π

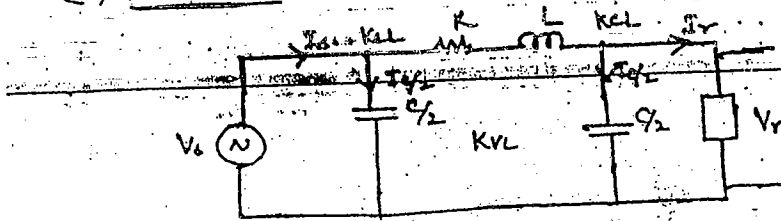

③ equations to solve for V_s & I_s


I_c is half at S.E. & L.E

(3) LEC

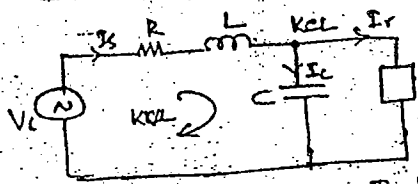

Unsymmetrical
② equations for V_s & I_s

(4) SEC

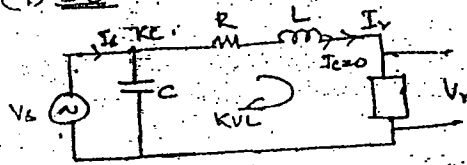


Unsymmetrical
② equations for V_s & I_s

→ For a given rated voltage & stated current at the receiving end, the voltage & current which is calculated at the sending end are called as Nominal Voltage & Nominal Current

∴ why we call Nominal- π & Nominal-T

→ In order to reduce the no. of the network equations, so that the time taking will be less to calculate V_s and I_s is by representing the tr. line in a two-port m/w model rather than RLC model

3) Long line:

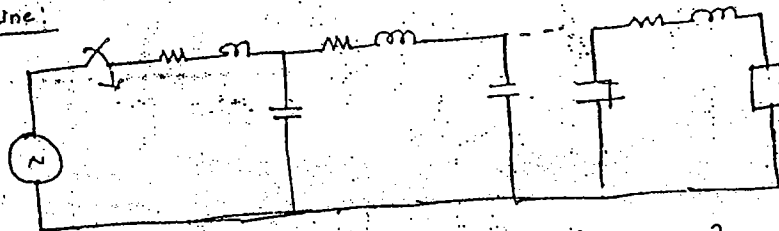


✓ Mathematical approach (transient)

✓ Steady state → Lumped { Equivalent-T, Equivalent- π } models

for analysis by using KCL & KVL

→ TWO PORT NETWORK MODEL

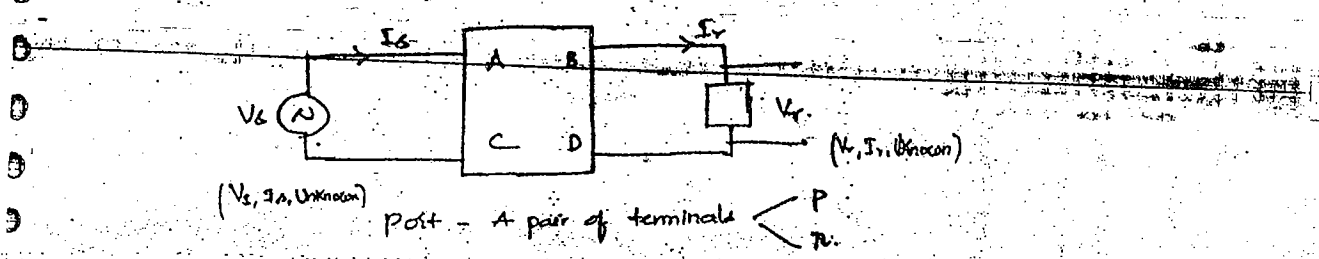

Two ports < Sending end
Receiving end

→ The unknown electrical quantities are evaluated by using the known electrical quantities along with certain parameters. These parameters are called ABCD parameters (or) Transmission parameters.

$$V_s = AV_r + BI_r \rightarrow \textcircled{1} \quad \text{KV/phase}$$

$$I_s = CV_r + DI_r \rightarrow \textcircled{2} \quad \text{KA/phase}$$


$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix} \quad \begin{bmatrix} V_s \\ I_s \end{bmatrix} = \frac{1}{AD-BC} \begin{bmatrix} D & -B \\ -C & A \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix}$$

If $A = D \Rightarrow$ Symmetric network model.

and

If $AD - BC = 1 \Rightarrow$ A Reciprocal network model.

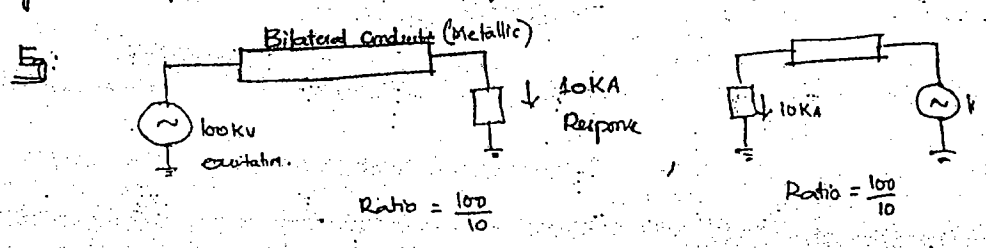
Reciprocal network: The ratio of excitation to the response is same even though the positions are interchanged.



Electronic element \rightarrow hybrid parameters
Electronic metallic \rightarrow ABCD parameters

→ Any electrical netw may or may not symmetric but always Reciprocal.

→ Units of ABCD values:

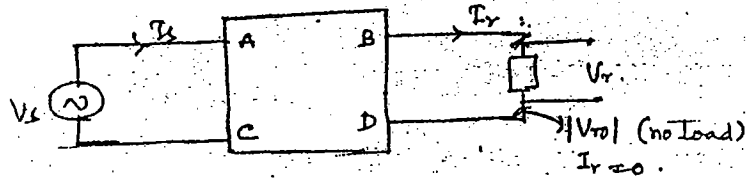

Case (i) No load condition at receiving end

$$V_s = A V_{r0} \rightarrow \textcircled{3}$$

$$I_s = C V_{r0} \rightarrow \textcircled{4}$$

$$\frac{V_s}{I_s} = \frac{A}{C} \rightarrow \textcircled{5}$$

$$\% \epsilon = \frac{|V_{r0}| - |V_r|}{|V_r|} \times 100$$


$$\% \epsilon = \frac{\frac{V_s}{A} - |V_r|}{|V_r|} \times 100$$

$$A = \frac{V_s}{V_{r0}} \Big|_{I_r=0} \text{ Unitless}$$

$$C = \frac{I_s}{V_{r0}} \Big|_{I_r=0} \text{ O.C admittance}$$

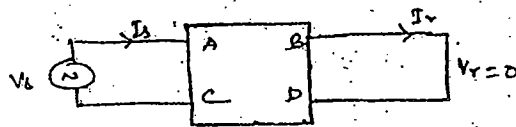(a) Mhos
(b) Siemens

Case (ii) Assuming short circuit at the receiving end.



$$V_s = B \cdot I_r \rightarrow \textcircled{6}$$

$$I_s = D \cdot I_r \rightarrow \textcircled{7}$$

$$\frac{V_s}{I_s} = \frac{B}{D} \rightarrow \textcircled{8}$$

$$B = \frac{V_s}{I_r} \Big|_{V_r=0} \text{ ohms S.C Impedance - ohms}$$

$$D = \frac{I_s}{I_r} \Big|_{V_r=0} \text{ Unitless}$$


From eqn $\textcircled{5}$ & $\textcircled{8}$

$$(B \neq 0 \neq 0)$$

$$\frac{V_s}{I_s} = \frac{V_r}{I_r} = \frac{A}{C} = \frac{B}{D}$$

$$\Rightarrow \frac{V_s}{I_s} = \sqrt{\frac{A \cdot B}{C \cdot D}} = \sqrt{\frac{B}{C}} = \sqrt{\frac{Z_{oc}}{Y_{oc}}}$$
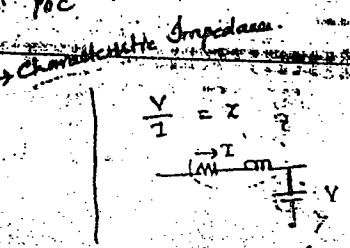
$$\frac{V_c}{I_s} = \sqrt{Z_{oc} Z_{sc}} = Z_c$$



→ A tr. line is having a series representation of Impedance and parallel representation of admittance, the ratio of Voltage to the current anywhere in the line is called as the "CHARACTERISTIC IMPEDANCE" of the line.

→ ABCD values with magnitude & Angle.


- A = |A| ∠ α
- B = |B| ∠ β
- C = |C| ∠ γ
- D = |D| ∠ δ

Max value of A is Δ

⇒ generally long lines are assumed as lossless since R is very less

STL	MTL	LTL
C ≠ 0	C ≠ 0	C ≠ 0
A = 1.0	A = 0.95 - 0.98	A = 0.9 - 0.95
α = 0	α = 1 - 2°	α = 2 - 5°
B = √(R² + X²)	B = √(R² + X²)	B = √(R² + X²)
depends on the length of the line	depends on line length	depends on length of the line
β = Impedance angle	β = tan⁻¹(X/R)	β = tan⁻¹(X/R)
β = 60°	β = 70°	β = 87°
C = ωC = 0	C = ωC	C = ωC
γ = 0	γ = 90° (g=0)	γ = 90° (g=0)
D = A	D = A	D = A

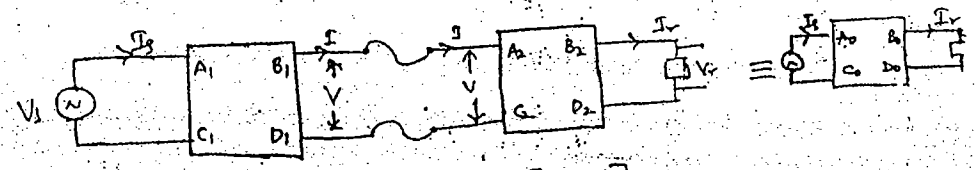→ Two trans. lines are connected in Cascade (or) Tandem



$$\begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix}$$

→ If two tr. lines are connected in cascade then the equivalent tr. line matrix is nothing but the matrix multiplication of the individual tr. line matrices.

$$\Rightarrow \begin{bmatrix} A_0 & B_0 \\ C_0 & D_0 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix}$$

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} V \\ I \end{bmatrix}, \quad \begin{bmatrix} V \\ I \end{bmatrix} = \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix}$$


$$\Rightarrow \begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} A_0 & B_0 \\ C_0 & D_0 \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix}$$


→ For two similar lines

$$\begin{aligned} A_1 = A_2 = A \\ B_1 = B_2 = B \\ C_1 = C_2 = C \\ D_1 = D_2 = D \end{aligned} \Rightarrow \begin{bmatrix} A_0 & B_0 \\ C_0 & D_0 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

→ Two Transmission lines in parallel:

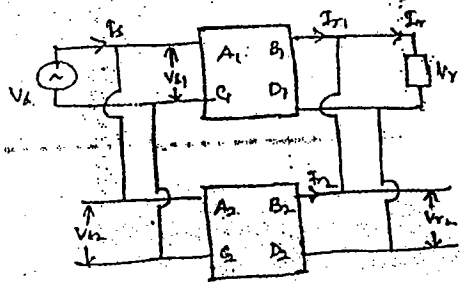
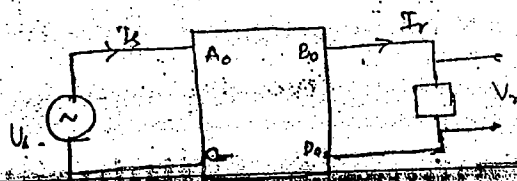
$$\begin{aligned} V_1 &= V_2 = V \\ V_1 &= V_2 = V_r \\ I_s &= I_{s1} + I_{s2} \end{aligned}$$



$$A_0 = \frac{A_1 B_2 + A_2 B_1}{B_1 + B_2}$$

$$B_0 = \frac{B_1 B_2}{B_1 + B_2}$$

$$C_0 = C_1 + C_2 + \frac{(A_1 - A_2)(D_2 - D_1)}{B_1 + B_2}$$

$$D_0 = \frac{D_1 B_2 + D_2 B_1}{B_1 + B_2}$$

For similar lines

$$A_1 = A_2 = A$$

$$A_0 = A$$

$$B_1 = B_2 = B$$

$$B_0 = B/2 \text{ (Impedance)}$$

$$C_1 = C_2 = C$$

$$C_0 = 2C \text{ (Admittance)}$$

$$D_1 = D_2 = D$$

$$D_0 = D$$

1st line

$$V_s \textcircled{1} = A \textcircled{V_r} + B_1 I_{r1} \rightarrow \textcircled{1}$$

$$I_{s1} = C_1 V_{r1} + D_1 I_{r1} \rightarrow \textcircled{2}$$

2nd line

$$V_s \textcircled{2} = A_2 \textcircled{V_{r2}} + B_2 I_{r2} \rightarrow \textcircled{3}$$

$$I_{s2} = C_2 V_{r2} + D_2 I_{r2} \rightarrow \textcircled{4}$$

$$\textcircled{1} \times B_2 \neq \textcircled{3} \times B_1$$

$$V_s (B_1 + B_2) = (A_1 B_2 + A_2 B_1) V_r + B_1 B_2 \underbrace{(I_{r1} + I_{r2})}_{I_r}$$

$$\therefore V_s = \left(\frac{A_1 B_2 + A_2 B_1}{B_1 + B_2} \right) V_r + \left(\frac{B_1 B_2}{B_1 + B_2} \right) I_r \rightarrow \textcircled{5}$$

$$V_s = A_0 V_r + B_0 I_r \rightarrow \textcircled{6}$$

Comparing Eq's $\textcircled{5}$ and $\textcircled{6}$

we get B_0 and $A_0 = D_0$


and C_0 can be calculated by $A_0 D_0 - B_0 C_0 = 1.0$

$$\Rightarrow C_0 = \frac{A_0 D_0}{B_0}$$

$$C_0 = 1 - \frac{(A_1 B_2 + A_2 B_1)}{B_1 + B_2} \left(\frac{D_1 B_2 + D_2 B_1}{B_1 + B_2} \right)$$

$$C_0 = 1 - \frac{B_1 B_2}{B_1 + B_2}$$

SHORT TRANSMISSION LINES:

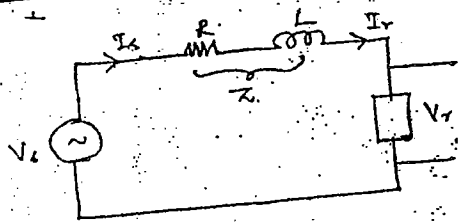

$$V_s = A V_r + B I_r \rightarrow \textcircled{1}$$

$$I_s = C V_r + D I_r \rightarrow \textcircled{2}$$

$$V_s = 1.0 \times V_r + \tau \times I_r \rightarrow \textcircled{3}$$

$$I_s = 0 \times V_r + 1.0 \times I_r \rightarrow \textcircled{4}$$

Comparing $\textcircled{1}, \textcircled{2}$ with $\textcircled{3}$ & $\textcircled{4}$

$$A = 1.0, B = \tau, C = 0, D = 1.0$$

$$A = D \text{ and } AD - BC = 1.0$$

Regulation of the line

$$\% \epsilon = \frac{|V_{r0}| - |V_r|}{|V_r|} \times 100 \rightarrow \text{Any line.}$$

FOS No load

$$|V_{r0}| = V_s$$

$$C \neq 0$$

$$I_s = I_r$$

$$\% \epsilon = \frac{|V_s| - |V_r|}{|V_r|} \times 100$$

STL

Regulation of the line is equal to VOLTAGE DROP

On STL

$$\therefore \% \epsilon = \frac{V_r + I_r \cdot X - V_r}{V_r} \times 100$$

$$\% \epsilon = \frac{I_r \cdot X}{V_r} \times 100$$

Another method

$$\% \epsilon = \frac{|V_{noL}| - |V_r|}{|V_r|} \times 100$$


$$\% \epsilon = \frac{\left| \frac{V_s}{A} \right| - |V_r|}{|V_r|} \times 100$$

$$\% \epsilon = \frac{|V_s| - |V_r|}{|V_r|} \times 100$$


$$\% \epsilon = \frac{V_s + I_r \cdot X - V_r}{V_r} \times 100$$

$$\% \epsilon = \frac{I_r \cdot X}{V_r} \times 100$$

→ Alternative method

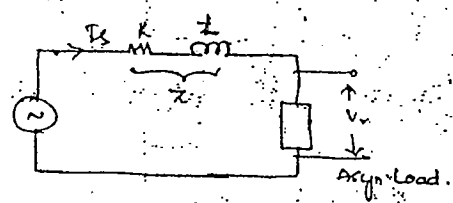

Use the vector diagram

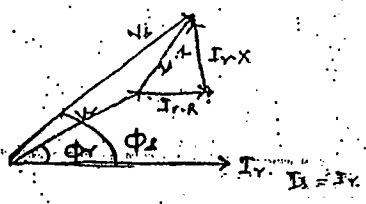

$$\cos \phi_s = \frac{V_r \cos \phi_r + I_r R}{V_s}$$


$$V_s \cos \phi_s = V_r \cos \phi_r + I_r R \rightarrow (1)$$

$$V_s \sin \phi_s = V_r \sin \phi_r + I_r X \rightarrow (2)$$

Square and Add eq's (1) & (2)

$$V_s \approx V_r \cos \phi_s + I_r R \cos \phi_s \pm I_r X \sin \phi_s$$

$$I_s = I_r$$

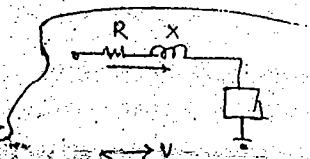

+ for lagging load
- for leading load

$$\% \epsilon = \frac{|V_{ro}| - |V_{rs}|}{|V_r|} \times 100$$

For No load

$$|V_{ro}| = |V_s|$$

$$\% \epsilon = \frac{|V_s| - |V_r|}{|V_r|} \times 100$$

$$\% \epsilon = \frac{V_r + I_r R \cos \phi_r \pm I_r X \sin \phi_r - V_r}{-V_r} \times 100$$

$$\% \epsilon = \frac{I_r R}{V_r} \times 100 \cos \phi_r \pm \frac{I_r X}{V_r} \times 100 \sin \phi_r$$


$$\% \epsilon = \% V_r \cos \phi_r \pm \% V_x \sin \phi_r$$

$$\% V_r = \% \text{ resistance drop} = \frac{I_r R}{V_r} \times 100$$

$$\% V_x = \% \text{ Reactance drop} = \frac{I_r X}{V_r} \times 100$$

$\% \epsilon$ will be maximum, if the load is Inductive load.

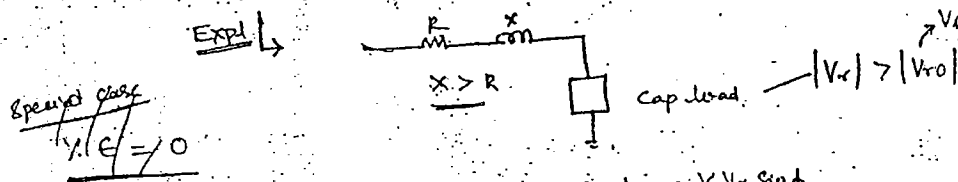$\% \epsilon$ will be negative, if the load is Capacitive load.



$$\% \epsilon = \% V_r \cos \phi_r - \% V_x \sin \phi_r$$

since $(X > R)$

Drop in 'X' is more than drop in 'R'

\rightarrow Under loaded condition $|V_{ro}|$ is less than $|V_r|$

Hence Negative Regulation and more voltage at receiving end

\rightarrow Special case

$$\% \epsilon = 0 \quad \boxed{X=R} \quad \text{and } 0.707 \text{ p.f. load}$$

(Practically not possible)



→ The phase angle at which the regulation is maximum

$$\% E = \% V_1 \cos \phi_r + \% V_2 \sin \phi_r$$

$$\frac{d \% E}{d \phi_r} = - \% V_2 \sin \phi_r + \% V_1 \cos \phi_r = 0$$

$$\tan \phi_r = \frac{\% V_1}{\% V_2} = \frac{I_r \cdot X}{I_r \cdot R} = \frac{X}{R}$$
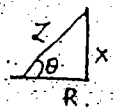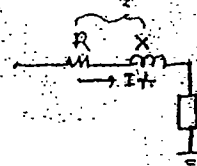
$$\phi_r = \tan^{-1} \left(\frac{X}{R} \right)$$



$$\tan \theta = \frac{X}{R}$$

$$\Rightarrow \tan \phi_r = \frac{X}{R} = \tan \theta$$

$$\phi_r = \theta$$

→ The phase angle at which the regulation is zero.

$$\% E = \% V_1 \cos \phi_r - \% V_2 \sin \phi_r = 0$$

$$\tan \phi_r = \frac{\% V_1}{\% V_2} = \frac{I_r \cdot R}{I_r \cdot X} = \frac{R}{X}$$


$$\tan \phi_r = \frac{R}{X}$$

$$\phi_r = \tan^{-1} \left(\frac{R}{X} \right)$$

$$\tan \phi_r = \cot \theta = \tan \left(\frac{\pi}{2} - \theta \right)$$

$$\phi_r = \frac{\pi}{2} - \theta$$

$$\phi_r + \theta = \frac{\pi}{2}$$

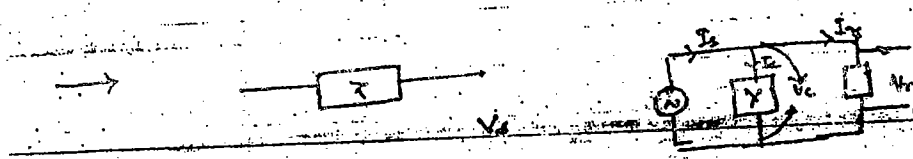

$$\begin{matrix} A = 1.0 \\ B = Z \\ C = 0 \\ D = 1.0 \end{matrix}$$

$$\begin{matrix} A = 1.0 \\ B = 0 \\ C = Y \\ D = 1.0 \end{matrix}$$

$$V_s = V_c = V_r + 0 \cdot I_r$$

$$V_s = A V_r + B I_r$$

$$\begin{matrix} A = 1.0 \\ B = 0 \end{matrix}$$

$$\begin{matrix} I_s = I_c + I_r \\ = V_c Y + I_r \end{matrix}$$

$$\begin{matrix} I_s = C V_r + D I_r \\ C = Y \\ D = 1.0 \end{matrix}$$

→ MEDIUM TRANSMISSION LINES

→ Nominal-T

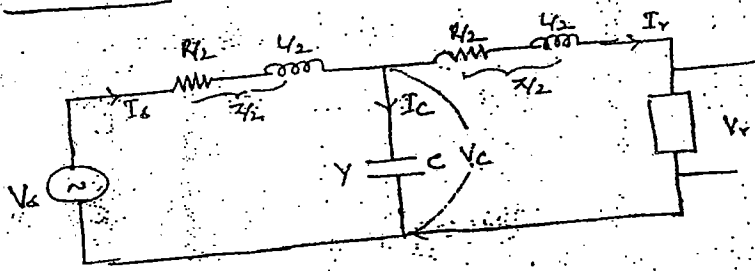


fig (c)

$$V_s = A V_r + B I_r$$

$$I_s = C V_r + D I_r$$

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & Z/2 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} \begin{bmatrix} 1 & Z/2 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix}$$

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 + \frac{ZY}{2} & Z(1 + \frac{ZY}{4}) \\ Y & 1 + \frac{ZY}{2} \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix}$$

$$A = 1 + \frac{ZY}{2}$$

$$B = Z(1 + \frac{ZY}{4})$$


$$C = Y$$

$$D = 1 + \frac{ZY}{2}$$

$$A = D \text{ and } AD - BC = 1.0$$

Symmetric and Reciprocal.

NOMINAL-T

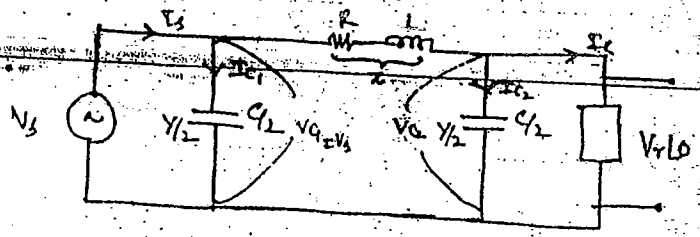

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ Y/2 & 1 \end{bmatrix} \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ Y/2 & 1 \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix}$$

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 + \frac{ZY}{2} & Z \\ Y(1 + \frac{ZY}{4}) & 1 + \frac{ZY}{2} \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix}$$

A = $1 + \frac{ZY}{2}$

B = Z

C = $Y(1 + \frac{ZY}{4})$

D = $1 + \frac{ZY}{2}$

A = D and AD - BC = 1, Symmetrical & Reciprocal

→ Nominal-T
 → Regulation, % = $\frac{|V_{no}| - |V_r|}{|V_r|} \times 100$
 for fig (a)

$|V_{no}| = \frac{|V_s| \left| \frac{1}{j\omega C} \right|}{\left| R/2 + \frac{j\omega L}{2} + \frac{1}{j\omega C} \right|}$ (By potential divider rule)


Under No Load Condition
 $V_r = |V_{no}| = \frac{|V_s|}{\beta}$
 $I_r = 0$

$|V_{no}| > |V_s| \rightarrow$ Ferranti effect

F.E: If the line is working at no load or light load condition then the receiving end voltage is more than the sending end voltage which is known as the FERRANTI EFFECT.

Where ~~is the Ferranti effect~~ will be much severe in LTL when compared MTL

Vector diagram

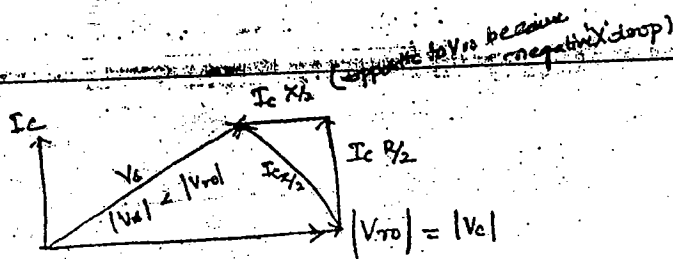

Another method

$$|V_{ro}| = \left| \frac{V_c}{A} \right|$$

$$|V_{ro}| > |V_c|$$

$|A| < 1.0$ because of shunt capacitance

$$A = 1 + \frac{ZY}{2}$$

$$|A| = \left| 1 + \frac{ZY}{2} \right|$$

$$= \left| 1 + \frac{|Z||Y|}{2} \right|$$

$$= \left| 1 + \frac{|Z||Y|}{2} \cos(\theta + \gamma) + j \frac{|Z||Y|}{2} \sin(\theta + \gamma) \right|$$

$(\theta + \gamma)$ $(\theta + \gamma)$
 MTL (90 + \gamma)

-ve. ↑ then ↓
(vector addition)

$$= |a + jb|$$

$$< \underline{1.0}$$

→ Nominal-π

$$\% \text{e} = \frac{|V_{ro}| - |V_r|}{|V_r|} \times 100$$

For no load condition

$$|V_{ro}| = |V_c| = \frac{|V_c| \cdot \left| \frac{1}{j\omega C} \right|}{\left| R + j\omega L + \frac{1}{j\omega C} \right|}$$

$$\frac{|V_{ro}|}{|V_c|} > 1$$

$$|V_{s0}| = \left| \frac{V_0}{A} \right|$$

$$|A| < 1.0$$

$$\Rightarrow |V_{s0}| > |V_0|$$


→ For a given receiving end voltage, the sending end voltage which is calculated will be slightly high for nominal-π configuration, so that the regulation will be slightly high.

known in Nominal-π when compared to nominal-T (since series capacitance is on load end side)

Q) Which is the most practical network model in Medium line.

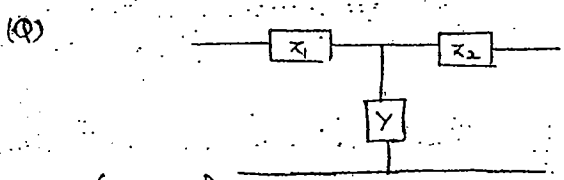- (i) N-T (ii) N-π (iii) either N-T or N-π (iv) None

Expt: In a practical case there is a better voltage at the load point, for a fixed sending end voltage if the transmission line is modelled in the nominal-π configuration rather than nominal-T.




($Z_1 \neq Z_2$) Asymmetric But Reciprocal.

↓
Y is not placed exactly at the middle of the line

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & Z_1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} \begin{bmatrix} 1 & Z_2 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix}$$


$$A \neq D, \text{ But } AD - BC = 1.$$

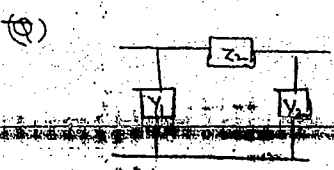

$Y_1 \neq Y_2$, Asymmetric but Reciprocal

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ Y_1 & 1 \end{bmatrix} \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ Y_2 & 1 \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix}$$

(3) Load end capacitance!

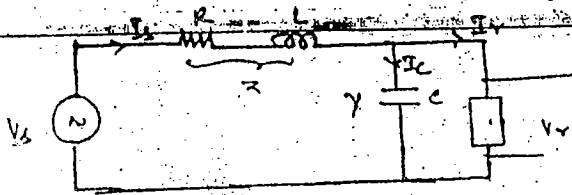

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix}$$

$A = 1 + ZY$

$B = Z$


$C = Y$

$D = 1 - 0$

Unsymmetrical

$A \neq D$, But $AD - BC = 1 - 0$

(4) Source End Capacitance!

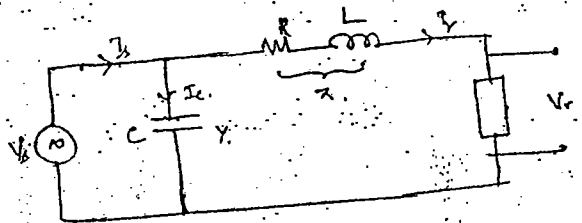

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ Y & 0 \end{bmatrix} \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix}$$

$A = 1 - 0$

$B = Z$

$C = Y$

$D = 1 + YZ$

Unsymmetrical but Reciprocal

	A	B	C	D
1) Distance between Conductors increases	Remain Same	↑	↓	Remain Same
2) Radius increases	Remain Same	↓	↑	Remain Same
3) Lengths increase	↓	↑	↑	↓

Eq: Nominal-T (for above, Expt)

$$A = 1 + \frac{ZY}{2} \Rightarrow \text{Remain same}$$


$$B = \pi \left(1 + \frac{ZY}{4} \right) \Rightarrow \uparrow$$

$$C = Y \Rightarrow \downarrow$$

$$D = 1 + \frac{ZY}{2} \Rightarrow \text{Remain same}$$


As $d \uparrow \Rightarrow L \uparrow, \pi \uparrow$
 $C \downarrow, Y \downarrow$

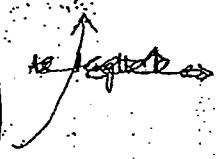As $r \uparrow \Rightarrow L \downarrow, \pi \downarrow$
 $C \uparrow, Y \uparrow$



28/10/10

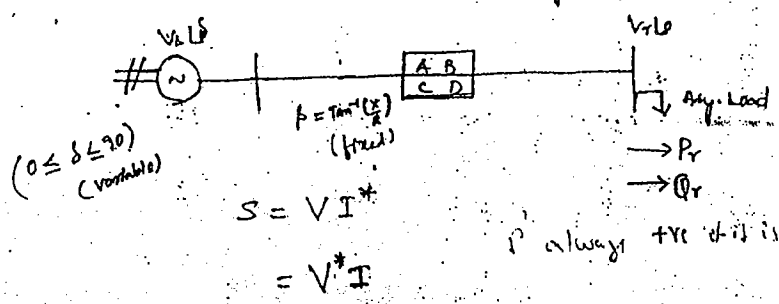→ POWER TRANSFER EQUATIONS: (Receiving end)



The purpose of the conjugate is to ensure that the real power is always positive and also to provide the sign for the reactive power.

In AC system (Conjugate requirement explanation)



$$S = VI$$

$$S = |V| |I| \angle \alpha + \beta$$

$$= |V| |I| \angle \alpha + \beta$$

$$S = |V| |I| \cos(\alpha + \beta) + j |V| |I| \sin(\alpha + \beta)$$

$$\alpha + \beta > 90$$

\Rightarrow P will be -ve (no meaning for -ve Real power)

Conjugate

$$S = VI^*$$

$$= |V| |I| \angle -\beta$$

$$= |V| |I| \angle \alpha - \beta$$

$$S = |V| |I| \cos(\alpha - \beta) + j |V| |I| \sin(\alpha - \beta)$$

If $\alpha > \beta \Rightarrow$ Voltage leading w.r.t Current.

$$\alpha - \beta < 90 \text{ (+ve)}$$

$$S = P + jQ$$

For Inductive load $P > 0, Q > 0$

If $\alpha < \beta \Rightarrow$ Voltage is lagging w.r.t Current

$$\alpha - \beta < 90 \text{ (-ve)}$$

$$S = P - jQ$$

For Capacitive load $P > 0, Q < 0$

* Hence the Real power is always positive

$$S_r = V_r I_r^*$$

$$S_r = |V_r| |I_r| \left[\frac{|V_s| |I_s| \cos(\alpha - \beta)}{|V_s| |I_s|} \right]^*$$

$$\left\{ \begin{array}{l} \text{Since} \\ V_s = AV_r + BI_s \\ I_r = \frac{V_s - AV_r}{B} \end{array} \right.$$

$$S_r = \frac{|V_s| |V_r|}{|B|} \cos(\beta - \delta) - \frac{|A|}{|B|} |V_r|^2 \cos(\beta - \alpha)$$

$$\therefore P_r = \frac{|V_s| |V_r|}{|B|} \cos(\beta - \delta) - \left[\frac{A}{B} \right] |V_r|^2 \cos(\beta - \alpha) \rightarrow (1)$$

$$Q_r = \frac{|V_s| |V_r|}{|B|} \sin(\beta - \delta) - \left[\frac{A}{B} \right] |V_r|^2 \sin(\beta - \alpha) \rightarrow (2)$$

$P_r = P_{max}$ = Steady state stability limit

$\alpha \rightarrow$ stability angle

$\delta \neq 90^\circ$ because there is some resistance


in the line

Hence $\delta = 85^\circ - 87^\circ$ to deliver max power at ' α '

$$\rightarrow \delta = \beta$$

$$P_{max} = \frac{|V_s| |V_r|}{|B|} - \frac{|A|}{|B|} |V_r|^2 \cos(\beta - \alpha) \text{ MW. } \left. \begin{array}{l} \text{power-angle curve} \\ \text{operating angle for stability} \end{array} \right\}$$


$$Q_r = - \frac{|A|}{|B|} |V_r|^2 \sin(\beta - \alpha) \text{ MVAR } \left. \begin{array}{l} \text{Capacitive Load (C)} \\ \text{Synchronous load} \end{array} \right\} \text{ electrically}$$

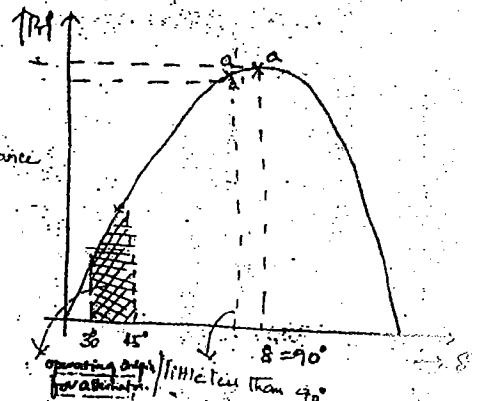

→ To deliver the max amount of real power to the load, then the load at the load end must be a synchronous load


→ Due to practical limitations of the synchronous motor, it is not preferable to replace the induction motor with synchronous motor if the load at the load end is induction motor then the real power to be +ve and also the reactive power to be "+ve" which can possible by allowing the alternator to deliver the required real power and reactive power with the operating angles rather than stability angle i.e. 30 to 45

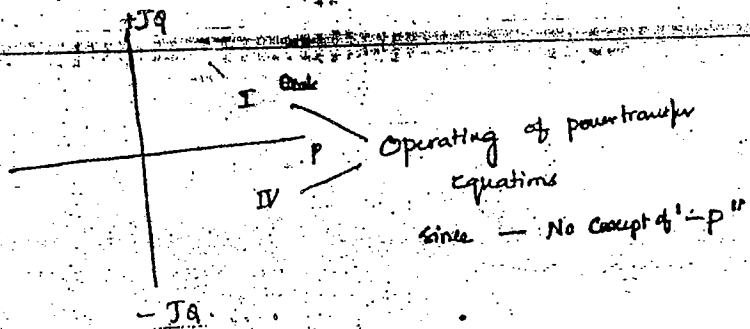→ The locus of the power transfer equations is a CIRCLE.



To prove
 In the given transmission line the amount of real power transfer does depends upon the difference of the angle b/w two ends of the trans line and the amount of reactive power transfer does depends upon the difference in the magnitude of the voltage on both ends of the transmission line.

→ Special case (1)

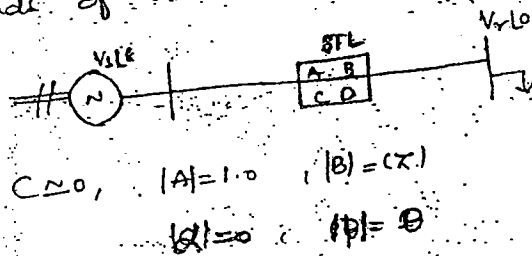

$$P_r = \frac{|V_2||V_1|}{|Z|} \cos(\theta - \delta) = \frac{1.0}{|Z|} |V_1|^2 \cos \theta \rightarrow \text{①}$$

$$Q_r = \frac{|V_2||V_1|}{|Z|} \sin(\theta - \delta) = \frac{1.0}{|Z|} |V_1|^2 \sin \theta \rightarrow \text{②}$$

$P_r = P_{max} = \text{Steady state stability}$

$$\Rightarrow \delta = 0$$

$$P_{max} = \frac{|V_2||V_1|}{|Z|} = \frac{1.0}{|Z|} |V_1|^2 \cos 0$$

$$Q_r = \frac{1.0}{|Z|} |V_1|^2 \sin 0$$

For Synchronous Load.

→ The maximum power transfer is possible provided that the load at the load end must be a synchronous load irrespective of transmission line. However it is more preferred to have ~~motors~~ motors at the load and the alternator is able to operate with operating angle of 5° to 10° only if it is connected to short line.

→ ② STL and loss less

$$C \approx 0, R \approx 0.$$

$$|A| = 1.0, \alpha = 0.$$

$$|B| = |X|$$

$$\beta = 0 = 90^\circ$$

From eq (1) & (2)

$$P_r = \frac{|V_s||V_r|}{|X|} \sin \delta \quad (\because \cos 90^\circ = 0)$$

$$Q_r = \frac{|V_s||V_r|}{|X|} \cos \delta - \frac{1.0}{|X|} |V_s|^2 (\sin 90^\circ - 0)$$

Loss less short line

$$\text{If } \delta = \beta = 90^\circ$$

$$P_r = P_{max} = \frac{|V_s||V_r|}{|X|}$$

$$Q_r = \frac{-1.0}{|X|} |V_s|^2 \rightarrow (-ve) \Rightarrow \text{Syn Load.}$$

∴ Even for loss less line the P_{max} will be possible for syn load only

$$P_r = \frac{|V_s||V_r|}{|X|} \sin \delta$$

$$P_r = P_{max} \sin \delta$$

$$P_r = K \sin \delta \quad (\because K = P_{max} = \frac{|V_s||V_r|}{|X|})$$

$$\Rightarrow P_r \propto \sin \delta$$

$$\Rightarrow P_r \propto \sin \delta \quad (\delta < 90^\circ)$$

$$\Rightarrow P_r \propto (\delta - 0) \quad (\text{Real power transfer depends on angle})$$

$$Q_r = \frac{|V_s||V_r|}{|X|} \cos \delta - \frac{1.0}{|X|} |V_s|^2$$

$$Q_r = \frac{|V_r|}{|X|} [|V_s| \cos \delta - |V_r|]$$

δ is small as δ 5° to 10°

$$\cos \delta \approx 1.0$$

$$Q_r = \frac{|V_r|}{|X|} [|V_s| - |V_r|]$$


$$= \frac{|V_r|}{|X|} [\text{Line Voltage drop}]$$

$Q_r \propto$ (line voltage drop) [Hence Reactive power depends on line voltages.]

→ POWER TRANSFER EQUATIONS (Sending end)

$$S_s = V_s I_s^* \quad (\text{Refer Text book})$$

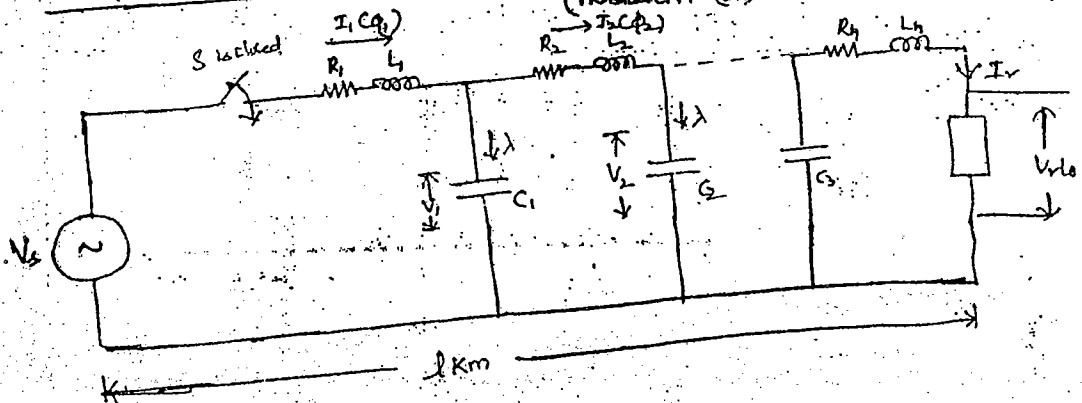
→ LONG TRANSMISSION LINE CONSTANTS (Uniformly distributed Line Constants)
(TRANSIENT OR SWITCHING WAVE TRAVELLING)



$$R_1 = R_2 = R \quad \Omega / \text{Km}$$

$$L_1 = L_2 = L \quad \text{H} / \text{Km}$$
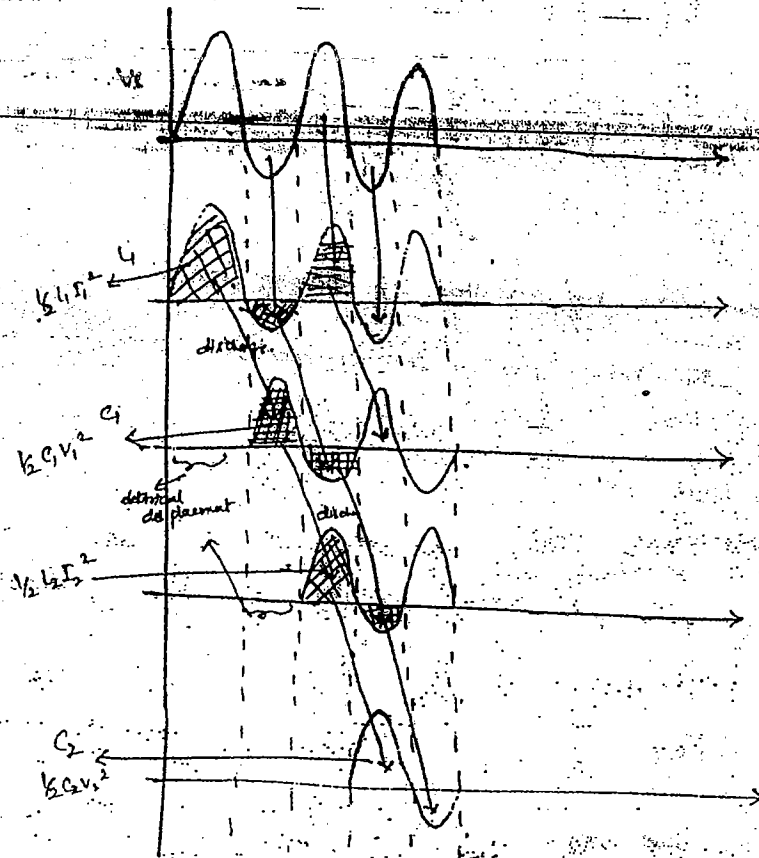
$$C_1 = C_2 = C_3 = C \quad \text{F} / \text{Km}$$



- The transmission line is represented with uniformly distributed line constants so that the time constants of these elements are negligible.
- When the switch is closed then the switching voltage will be opposed by the resistance and inductance which are in series.
- The time constant of these elements is negligible so that the current will be allowed to flow immediately through the inductor and it can develop the magnetic field.
- The magnitude of the switching voltage will be converted into the current and it will be stored in the inductor in an instantaneous manner.
- The switching voltage waveform is a continuous so that the inductor has to discharge the energy stored previously.

The stored energy of the inductor will discharge to the capacitor so that the capacitor will be slowly charging and it can develop the static field. The energy stored in the static field is $\frac{1}{2} C_1 V_1^2$

The switching waveform will be travelled by having an electrical displacement between the inductor and the capacitor.

At the end of first Km.

Energy balance

$$\frac{1}{2} L_1 I_1^2 = \frac{1}{2} C_1 V_1^2 \quad \text{--- (1)}$$

$$P_{net} = 0$$

$$\Rightarrow \boxed{V_1 = V_s} \quad (R = 0)$$

\Rightarrow The travelling wave does not have any attenuation.

\rightarrow of $P_{net} = 0$, but $R \neq 0$

$$\Rightarrow \boxed{V_1 \neq V_s}$$

\Rightarrow The travelling wave does experience an attenuation

From eq (1) $\frac{V_1}{I_1} = \sqrt{\frac{L_1}{C_1}} = \sqrt{\frac{L}{C}} = Z_c$ Char. Impedance
Surge Impedance

The ratio of voltage to the current at any distance is called as the characteristic impedance (Z_c) The Surge impedance.

When the switch is closed the line will experience high frequency surges so that the impedance offered is called a Surge impedance.

\rightarrow At the end of 2nd Km, Energy balance

$$\frac{1}{2} L_1 I_1^2 = \frac{1}{2} C_1 V_1^2$$

$$P_{net} = 0$$

$$V_2 = V_1 \quad (R \approx 0)$$

→ The travelling wave does not having any attenuation

of $Q_{net} = 0$ but $R \neq 0$.

$$\rightarrow (V_2 \neq V_1)$$

∴ The travelling wave does experience any attenuation

From eq (5)

$$\frac{V_2}{I_2} = \sqrt{\frac{L_2}{C_2}} = \sqrt{\frac{L}{C}} = X_C \text{ (or) } X_S$$

From the above, it can be understood that the switching wave will be travelled by gradually building up of the magnetic field in the inductor and the static field across the capacitor. So that the concept of wave travelling is in terms of the reactive power balance.


— The ratio of voltage to the current at any distance is called as Characteristic Impedance or Surge Impedance. If the resistance is assumed as zero, the travelling wave form does not experience any attenuation.

→ In case of OHTL the switching wave form will be travelled exactly at light velocity is: 3×10^8 m/s or 3×10^5 km/sec.

→ The tr. line is represented with uniformly distributed line constants so that consider the mathematical solution to know the velocity of wave travelling

→ Mathematical Approach is:

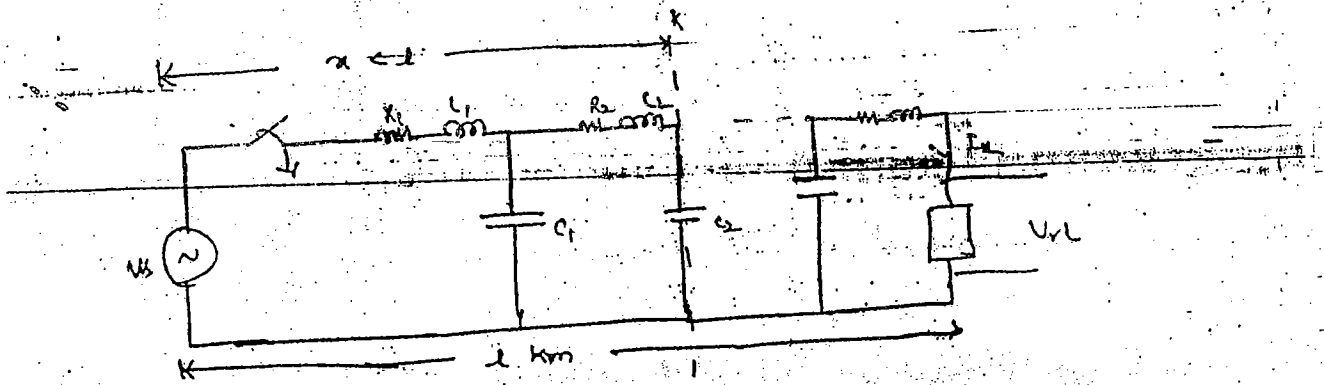Consider point 'x' at a distance of 'x' where $(x < l)$ from the source.



The total magnetic field deposited upto 'x'

$$\phi = Lx \cdot I \quad [I_1 = I_2 = I, R \approx 0]$$

$$\frac{d\phi}{dt} = V = LI \cdot \frac{dx}{dt} = LIv \rightarrow (1)$$

$v \rightarrow$ Velocity of wave travelling.

The total static field upto 'x'

$$\lambda = c \cdot x \cdot V$$

$$\frac{dx}{dt} = I = cV \cdot \frac{dv}{dt} = cVv \rightarrow (2)$$

Multiplying (1) & (2)

$$VI = VI LCV^2$$

$$V = \frac{1}{\sqrt{LC}}$$

\rightarrow velocity of wave travelling

$$V = \frac{1}{\sqrt{2 \times 10^{-4} \ln\left(\frac{2h}{a}\right) \times 2 \times 3.14 \times 8.85 \times 10^{-12} \times \epsilon_r}}$$

$\frac{h}{a}$ (unitless)
 $\frac{1}{\text{km}}$ (unitless)
 km (unitless)
 F/km

For OHTL

$$\epsilon_r = 1$$

$$V = 3 \times 10^5 \text{ km/sec.}$$

$$V = 3 \times 10^8 \text{ m/sec}$$

($R=0$)

} light velocity.


→ If Resistance is considered then the velocity of wave is

~~$V = 2.5 \times 10^8 - 2.8 \times 10^8 \text{ m/sec } (R \neq 0)$~~

$V \rightarrow$ Attenuation velocity

Resistance can provide the attenuation for the velocity of the wave form and also the magnitude of the wave form

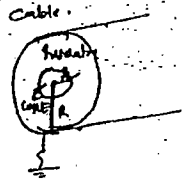
→ For underground cable, the velocity of wave travelling is




$$V = \frac{1}{\sqrt{2 \times 10^4 \ln(R/r) \times \frac{2 \times 3.14 \times 8.85 \times 10^{-12} \times (6.7)}{\ln(R/r)}}} = \frac{3 \times 10^8 \text{ m/s}}{\sqrt{\epsilon_r}}$$

The velocity of wave travelling in underground cable will be less than light velocity.

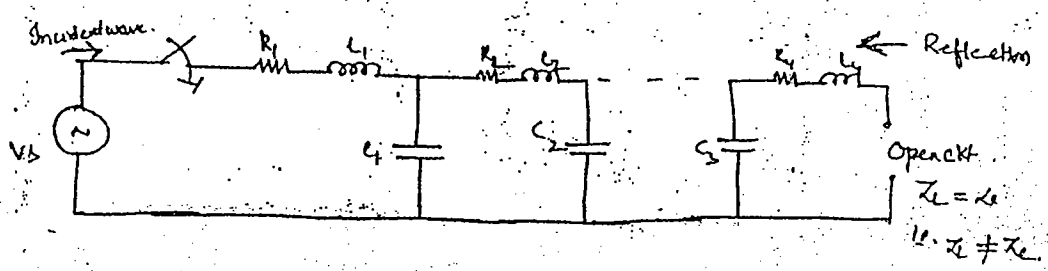
→ The damped inductive load will become open circuit when the switching wave reaches the load end. So that the load impedance is not matched with the characteristic impedance.



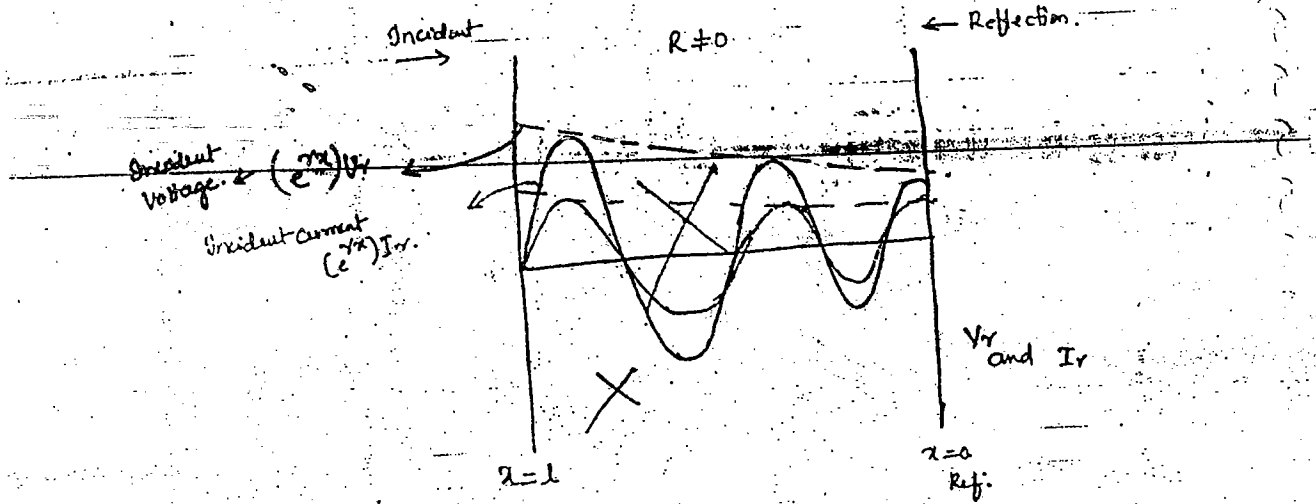When the $Z_L \neq Z_0$, then there will be a reflection wave form which is travelled in the transmission line by offering the characteristic impedance. Hence the line will experience the incident waveform and also the reflected wave form and they have expressed their magnitude in terms of receiving end voltage and receiving end current (because V_r, I_r are always known values)



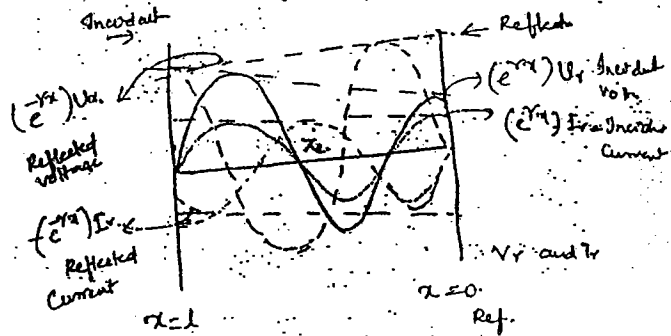The sign of the incident current will be same as that of the sign of incident voltage



The average of these two waveforms at any distance in the transmission line are called transmitted voltage and transmitted current

$$V_x = \left(\frac{e^{\gamma x} + e^{-\gamma x}}{2} \right) V_r + Z_c \left(\frac{e^{\gamma x} - e^{-\gamma x}}{2} \right) I_r$$

$$I_x = \frac{1}{Z_c} \left(\frac{e^{\gamma x} + e^{-\gamma x}}{2} \right) V_r + \left(\frac{e^{\gamma x} - e^{-\gamma x}}{2} \right) I_r$$

If $x=l$

$$V_s = \left(\frac{e^{\gamma l} + e^{-\gamma l}}{2} \right) V_r + Z_c \left(\frac{e^{\gamma l} - e^{-\gamma l}}{2} \right) I_r$$

$$I_s = \frac{1}{Z_c} \left(\frac{e^{\gamma l} + e^{-\gamma l}}{2} \right) V_r + \left(\frac{e^{\gamma l} - e^{-\gamma l}}{2} \right) I_r$$

$$\Rightarrow V_s = \cosh \gamma l V_r + Z_c \sinh \gamma l I_r$$

$$I_s = \frac{1}{Z_c} \sinh \gamma l V_r + \cosh \gamma l I_r$$

Comparing with

$$V_s = A V_r + B I_r$$

$$I_s = C V_r + D I_r$$

$$A = \cosh \gamma l, \quad B = Z_c \sinh \gamma l$$

$$C = \frac{1}{Z_c} \sinh \gamma l, \quad D = \cosh \gamma l$$

$$A = D \quad \& \quad AD - BC = 1.0 \Rightarrow \text{Symmetric \& Reciprocal.}$$

Whenever a line constants are represented T and Π sections then the line is said to be symmetric and reciprocal.

29/10/10:

$$V_s = \cosh \gamma l V_r + Z_c \sinh \gamma l I_r$$

$$I_s = \frac{1}{Z_c} \sinh \gamma l V_r + \cosh \gamma l I_r$$

Where


$$\gamma = \text{propagation constant} = \sqrt{ZY} = \sqrt{G_p/Km \cdot A_d/Km}$$

$$= \sqrt{(R + j\omega L)(G + j\omega C)} = \alpha + j\beta$$

Where

α = Real part = Attenuation Constant (Nepers / Km)

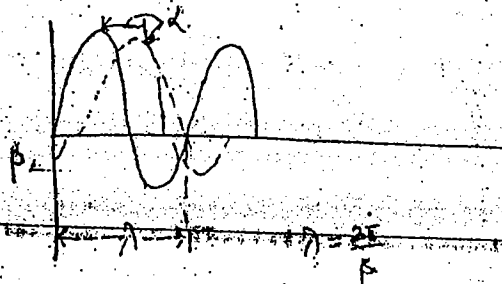β = phase component (or) quadrature component (rad / Km)



A travelling wave is having a propagation constant

$$\gamma = \alpha + j\beta$$

For one complete sinusoidal variation, the wavelength in which the wave is travelled,

For lossless line, $R=0$ & $G=0$

$$\rightarrow \gamma = \sqrt{(j\omega L)(j\omega C)} = j\omega\sqrt{LC} = j\beta$$

(Q) A 300km, Tr. line is having quadrature component of 0.0027 rad/km. What is the % of the physical length of a Tr. line to be wavelength of the line?

Phy length $l = 300\text{km}$

Wave length $\lambda = \frac{2\pi}{\beta}$


$$\therefore \frac{l}{\lambda} = \left(\frac{300}{\frac{2\pi}{0.027}} \times 100 \right) \text{ Ans}$$

$$\rightarrow Z_c \text{ (or) } Z_0 = \sqrt{\frac{B}{C}} = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{R + j\omega L}{G + j\omega C}} \rightarrow 400 \angle 0^\circ \Omega$$

(It is -ve) why $G \approx 0$

For long Tr. line $R=0, G=0$
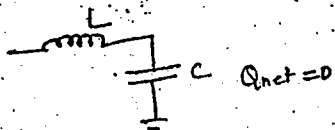
$$Z_c \text{ (or) } Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{\text{Ind/Km}}{\text{Adm/Km}}} = 400 \angle 0^\circ \Omega = 400 \Omega$$



⇒ In a lossless Tr. line, the net reactive power of seg is zero so that the Tr. line can be neither inductor or capacitor hence it will be a resistive nature. It is independent on line length

for 300km $Z_c = 400 \Omega$
for 400km $Z_c = 400 \Omega$ (same since) of loss

~~At a~~

At a frequency of 50 Hz, $X_L = 400 \Omega$, of $f = 100$ Hz then

$X_L = 400 \Omega$


→ For 132KV, 220KV, 400KV, 765KV the X_L is same but for 400KV and 765KV will be less but about $\approx 380 \Omega$ (for 400KV)

→ SURGE IMPEDANCE LOADING / CHARACTERISTIC IMPEDANCE LOADING

In a loss less transmission line it is the loading of the transmission line where the load impedance is equal the characteristic impedance of the transmission line.

(OR)

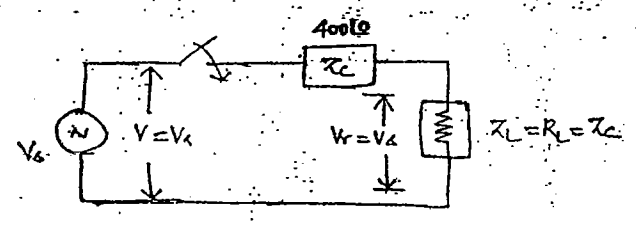Whenever the transmission line is terminated by a load having the load impedance is equal to the characteristic impedance of the line then such loading on the transmission line is called as characteristic impedance loading



→ If the line is operating with SLK then such a trans line is called a FLAT LINE. A Flat line is the one in which the magnitude of voltage throughout its length will be same

→ A transmission line is a Flat line provided that it is of an infinite line length
 $R=0$

→ If the tr. line is of infinite length then the travelling wave does not experience any attenuation

$$SIL = \frac{V_s V_r}{Z_c}$$

$$SIL = \frac{V^2}{Z_c} \quad [\because V_s = V_r = V] \text{ MW}$$

Units of SIL = MW (∵ system is working under unity pf)

$$\therefore SIL \propto V^2$$

$$\propto \frac{1}{Z_c}$$


Eg: A 400KV tr. line SIL = ?

$$\begin{aligned} \Rightarrow SIL &= \frac{V^2}{Z_c} \\ &= \frac{400 \times 400}{400} \\ &= 400 \text{ MW} \end{aligned}$$

For a 220KV tr. line, then SIL = ?

$$\Rightarrow SIL = \frac{220 \times 220}{400} = \frac{22 \times 22}{4} = 121 \text{ MW}$$

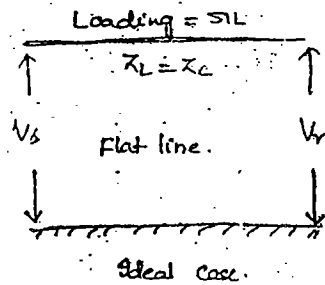→ SIL is also known as Ideal Capacity (or) No-load Capacity




(1) Loading > SIL (MVA Capacity)

$$\Rightarrow Z_L < Z_c \quad (\because \text{loads are parallel, } X_{eq} \downarrow)$$

Since the current is more, $|I| \uparrow$

$$k \cdot |I|^2 > k \cdot C V^2$$


∴ Net = Inductive nature

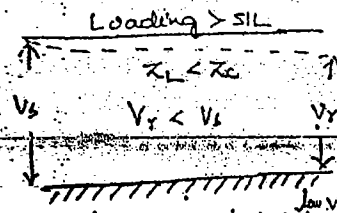

→ In parallel trans. network it is impractical to work with full load conditions by all the lines at the same point of time.

→ In order to improve the voltage at any one of the load point by increasing the excitation of the alternator then it will also increase the voltage at other parallel loads, which is not required. Hence the excitation is not recommended

(2) External method:

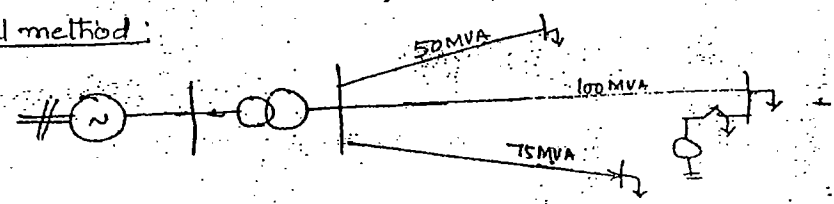

— In external method, install a suitable voltage control device and control the voltage at that particular point without effecting the voltage of other parallel transmission line. Hence the location for the voltage control device is the Receiving end.

— The various device that can be used for voltage control are

- (1) Shunt Capacitor
- (2) Shunt Inductor
- (3) Series Capacitor
- (4) Synchronous Capacitor
- (5) Synchronous Inductor
- (6) Synchronous phase modifier

— All most all voltage control devices are of purely Capacitive nature or Inductive nature and the rating of those devices are expressed in terms of reactive power

$$S = \sqrt{P^2 + Q^2}$$

$$= Q \quad [P=0]$$

KVA (or) MVAR

$$Q_r = \frac{V_r}{|X|} [|V_s| - |V_r|]$$

→ For a fixed sending end voltage, the voltage at the receiving end will be controlled, by controlling the net reactive power at the load point i.e. either by injecting the reactive power or by absorbing the reactive power hence the concept of voltage control is also called as the concept of reactive power control

→ Some times we call the voltage control device as Compensating devices

$$\text{Rating of voltage control / compensating device} = \text{MVAR (Reactive power)}$$

→ The amount of the reactive power of the system is

$$Q_r + Q_c = Q_d$$


$$(or) Q_c = Q_d - Q_r$$

Q_r → Reactive power to line.

Q_d → load reactive.

Q_c → Compensative reactive power

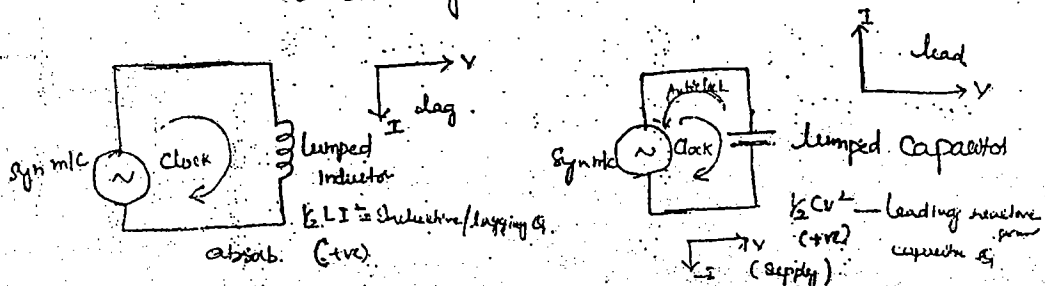
→ The sign property for the reactive powers of the lumped elements and also the synchronous machines.



→ In the above m/w the synchronous m/c will deliver the required

reactive power ^{required} by the lumped elements.

→ In order to get the conventional sign:

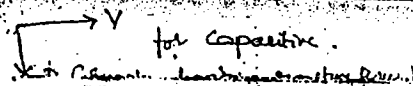

(ii) Loading < SIL (MVA Capacity)
 $\Rightarrow Z_L > Z_C$ (\because light loads)


$\Rightarrow |I| \downarrow$

$\Rightarrow \frac{1}{2} LI^2 < \frac{1}{2} CV^2$

$\rightarrow Q_{net} = \text{Capacitive reactive}$

\rightarrow leading power factor

i.e. $V_R > V_S$ i.e. Ferranti effect

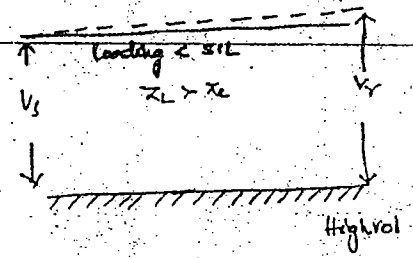


\rightarrow Whenever the actual receiving end voltage has become divergent with its limits of the voltages then it will be declared as either low voltage or high voltage. The result of low voltage is the poor performance of the system, the result of high voltage will be failure of the insulation suddenly.

$(V \pm \% E) \rightarrow$ poor performance [Low voltage]

High voltage \rightarrow Failure of insulation

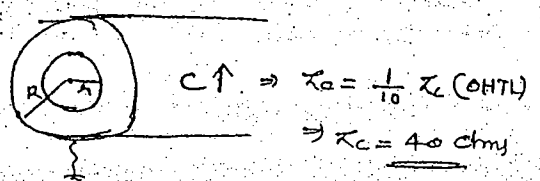\rightarrow In order to improve the performance of the system or to prevent the failure of the insulation it is necessary to have a suitable control over the load voltage which is known as the concept of voltage control.



\rightarrow The most economical loading on overhead tr. line is the loading more than SIL

→ The most economical loading in an underground cable is

the loading $< SIL$


because

Sheath (heat) = 0

Cable (heat) is high.

⇒ High temperature gradient

⇒ Insulation life decrease.

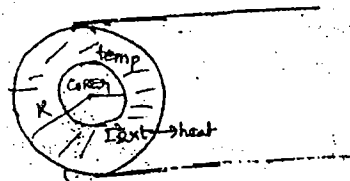

Ineffective heat dissipation.

→ Due to the improper heat dissipation there will be a temperature gradient at the surface of the cable and it will increase if the loading is more than SIL, so that the insulation failure will take place.

→ If the loading is $< SIL$, the cable will experience severe over voltage if the length of the cable is high because the capacitance / km is high. In order to limit the over voltage the cables are not recommended beyond 50 km to transmit the bulk amount of power.


⇒ VOLTAGE CONTROL

Voltage Control can be done by 2 methods



(1) Internal method — Excitation Control

(2) External method — Install any suitable device

(1) Internal method!

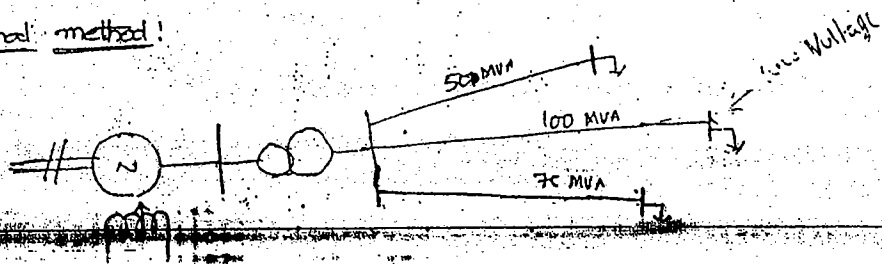


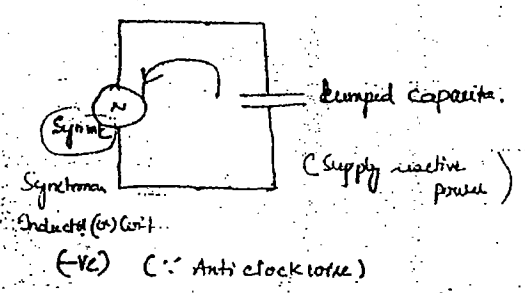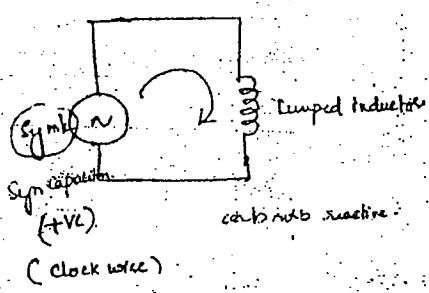$\Rightarrow \frac{1}{2} LI^2 \rightarrow +ve$ (absorbing the reactive power) (C.W. Convent direction)
 $\frac{1}{2} CV^2 \rightarrow -ve$ (supply the reactive power) (C.C.W. Convent direction)



\rightarrow The sign of the reactive power of the lumped elements are opposite to that of the sign of the reactive power of synchronous elements.

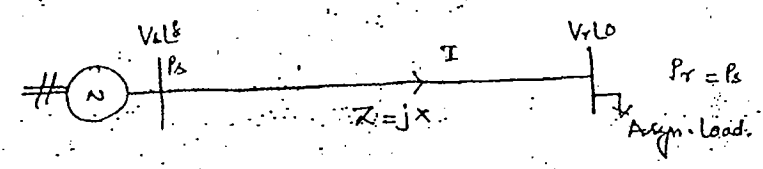APPROXIMATE MATHEMATICAL RELATION FOR LUMPED ELEMENTS.



$$|V_r| = |V_s| - jX I \rightarrow \text{①}$$

The voltage control device does not change the real power

$$P_s = P_r$$


$$V_r I^* = V_s I^* = P + jQ$$

$$I^* = \frac{P + jQ}{|V_s|}$$

$$(I^*)^* = I = \frac{P - jQ}{|V_s|^*} = \frac{P - jQ}{|V_s|}$$

$$|V_r| = |V_s| - jX \left[\frac{P - jQ}{|V_s|} \right]$$

$$|V_r| = |V_s| \left[1 - \frac{X}{|V_s|} \frac{P}{|V_s|} - \frac{X}{|V_s|} \frac{Q}{|V_s|} \right]$$

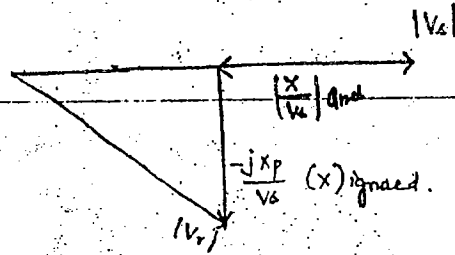


$$|V_r| \approx |V_s| - \frac{|X|}{|V_s|} Q_{net}$$

→ In case of the shunt capacitor and shunt inductor, the voltage is controlled by controlling the net reactive power at the load point for fixed sending voltage & fixed line reactance

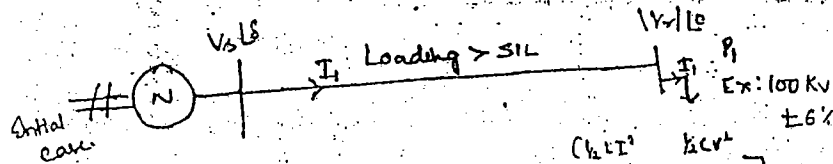(1) SHUNT CAPACITOR: (power factor improvement / correction device)

If the transmission line is experiencing the loading more than surge impedance loading, then the inductive reactive power of the system is more than the capacitive reactive power so that the receiving end voltage is less than V_s and if it is a low voltage, a suitable shunt capacitor is placed at the load end in order to inject capacitive reactive power to compensate the excess inductive reactive power of the system so that the voltage at the receiving end will be improved.



$$|V_{r1}| = |V_s| - \frac{X}{V_s} [Q_{ab} - Q_{gen}] \rightarrow (1)$$

$$\Rightarrow |V_{r1}| < |V_s|$$


if it is low voltage then it needs to improve

$$|V_{r1}| < (V - \% \epsilon)$$

85

for ex: 100KV $\pm 6V$, = Regulation limit (94 - 106 KV)

low voltage ←

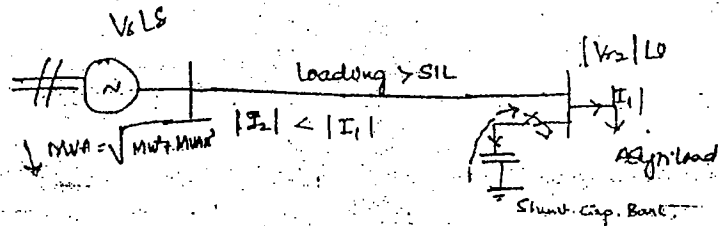

$$|V_{r2}| = |V_s| - \frac{X}{|V_s|} [Q_{ab} - Q_{Gen} - Q_{sh. Cap}]$$

$$|V_{r2}| = |V_s| - \frac{X}{|V_s|} [Q_{ab} - (Q_{Gen} + Q_{sh. Cap})] \rightarrow (2)$$

$$\therefore |V_{r2}| < |V_s|, \text{ But } |V_{r2}| > |V_{r1}| \Rightarrow |V_{r2}| > (V - \% \epsilon)$$

∴ Voltage of the system is improved


→ if $|V_{r2}| = |V_s| \rightarrow$ Flat voltage

$$Q_{net} = 0$$

$$Q_{sh. cap} = Q_{ab} - Q_{Gen}$$

∴ The rating of the shunt capacitor is high so that the extra cost of the shunt capacitor is also high. Hence the supply system is uneconomical.

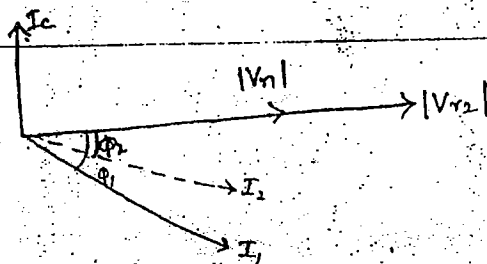→ if the voltage is improved the rating of the capacitor required is less so that the extra cost of capacitor is less and finally the total cost of the supply system is economical.



$|V_{r2}| > |V_{r1}|$ — Improvement in voltage.

$$Q_2 < Q_1$$

$\cos \phi_2 > \cos \phi_1$ — Improvement in p.f. of the load.

$$S_1 = \frac{P_1}{\cos \phi_1}, \quad S_2 = \frac{P_2}{\cos \phi_2} \quad (P_2 = P_1)$$

→ In case of shunt capacitor, the improvement in the power factor of the load is predominant compared to the improvement in voltage because the improvement in the power factor of the load will result as there is saving in annual bill paid by the consumer.

→ Consumers are

- 1) Domestic
- 2) Non-domestic
- 3) Industrial

Flat rate tariff
Two part tariff

$$\text{Bill} = \underbrace{Rs. \times \text{kVA}}_{F.c} + \underbrace{\text{Paise} \times \text{kWhr}}_{R.c}$$

→ Some of the voltage control devices are preferred as power factor correction devices rather than voltage control devices because the existing power system will experience low power factors due to the following reasons and it is necessary to improve the p.f. of the


system
→ Reasons for low power factor.

(1) Most of the loads are driven by induction motors.

→ (ii) The Heating and welding in the industry is done by using induction principle.

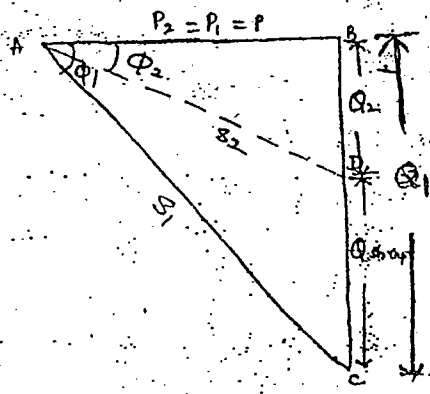(iii) Due to no load current of the transformer, the power factor at the full load will also be reduced.

→ The amount of reactive power supplied by the Shunt Capacitor by using the power triangle can be obtained.



$$Q_{sh. Cap} = Q_1 - Q_2$$

$$= S_1 \sin \phi_1 - S_2 \sin \phi_2$$

$$= \frac{P_1 \sin \phi_1}{\cos \phi_1} - \frac{P_2 \sin \phi_2}{\cos \phi_2}$$

$$Q_{sh. Cap} = P (\tan \phi_1 - \tan \phi_2) \rightarrow 3 \phi$$


$$Q_{sh. Cap/ph} = \frac{P (\tan \phi_1 - \tan \phi_2)}{3}$$

$$Q_{sh. Cap} \propto \sqrt{f}$$

$$Q_{sh. Cap/ph} = V_{phase} \cdot I_{c/ph} \sin 90^\circ$$

$$= V_{phase} \cdot \frac{V_{phase}}{X_c} = V_{phase}^2 \omega C / phase$$
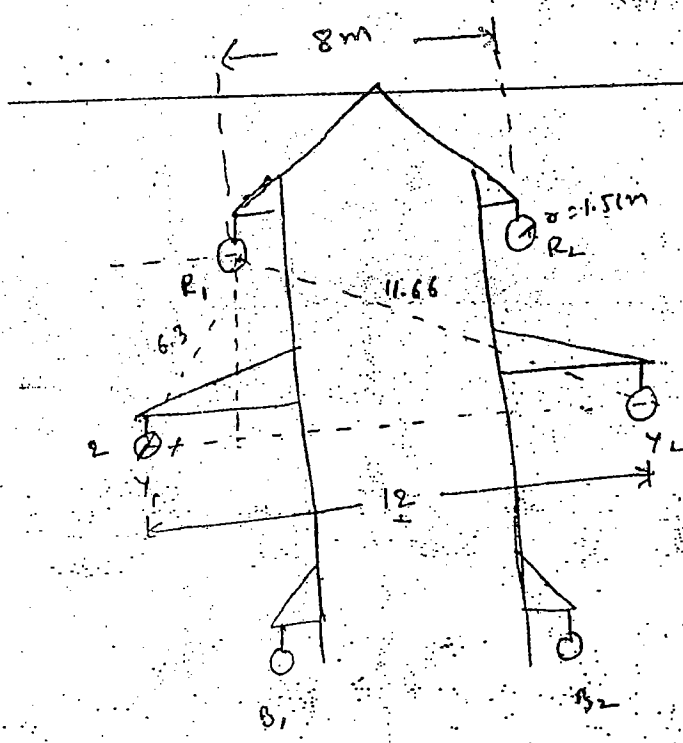
$$C / phase = \frac{Q_{sh. Cap/ph}}{V_{phase}^2 \omega} \quad F(\phi) \mu F$$



$$= \sqrt[3]{\text{self } GMD_R \text{ self } GMD_y \text{ self } GMD_z}$$

$$\text{self } GMD_R = \sqrt{\text{self } GMD_{R_x} \text{ self } GMD_{R_z}}$$

$$= \text{self } GMD_R$$

$$= \sqrt{0.7788 \times 1.5 \times 800 \text{ (m)}}$$

$$\text{self } GMD_B = \text{self } GMD_R$$

$$\text{self } GMD_y = \text{self } GMD_{y_1}$$

$$= \sqrt{0.7788 \times 1.5 \times 2 \times 1200}$$

$$GMD = \sqrt[3]{GMD_R \ GMD_y \ GMD_B}$$

$$GMD_R = GMD_{R_1} = \sqrt[4]{6.3 \times 12 \times 11.66 \times 14.4}$$


$$GMD_B = GMD_R = GMD_{R_1}$$

$$GMD_y = GMD_{y_1} = \sqrt[4]{6.3 \times 6.3 \times 11.66}$$

11 Feb 2010

→ SHUNT INDUCTOR: Whenever the tr-line is experiencing the loading less than SIL then the capacitive reactive power of the system is more than inductor reactive power. So that the receiving end voltage is more than sending end. If it is a high voltage a suitable shunt inductor is placed in a receiving end in order to absorb the excess capacitive reactive power so that the receiving end voltage will reduce which will prevent the failure of insulation.

Initial case:

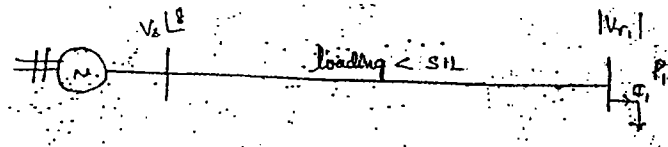


$$|V_{r1}| = |V_s| - \frac{X}{|V_s|} [Q_{ab} - Q_{gen}]$$

$|V_{r1}| > |V_s|$ → If it is a high voltage

$$\therefore |V_{r1}| > (V + \%E)$$

It requires to reduce the voltage.

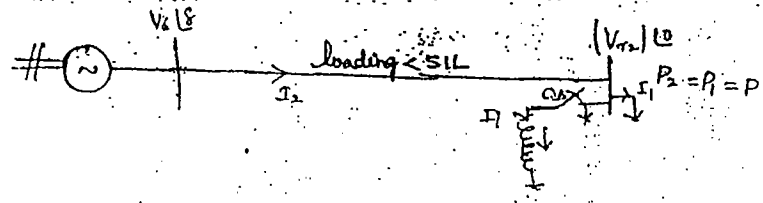

$$|V_{r2}| = |V_s| - \frac{X}{|V_s|} [Q_{ab} + Q_{sh. Ind} - Q_{gen}]$$

$$|V_{r2}| > |V_s|$$

$$\text{But } |V_{r2}| < |V_{r1}|$$

$$\Rightarrow |V_{r2}| < |V_{r1}|$$

— The shunt inductors are ^{inducted} when the loading on the tr. line is a light load in order to limit the Ferranti effect of the tr. line rather than the power factor of the load. Hence it will be treated as the voltage control device rather than power factor correction device.

— As similar to that of the shunt capacitor, the amount of reactive power absorbed will be calculated by using the power triangle.

$$Q_{sh. Ind} = P(\tan \phi_1 - \tan \phi_2) \quad (3-9)$$

$$Q_{sh. Ind / phase} = \frac{P(\tan \phi_1 - \tan \phi_2)}{3.0}$$

$$= V_{phase} \cdot I_{i / phase} \sin 90^\circ$$

$$Q_{sh. Ind / phase} = V_{phase} \cdot \frac{V_{phase}}{X_L} = \frac{V_{phase}^2}{\omega L / phase}$$

$$L_{phase} = \frac{V_{phase}^2}{\omega Q_{sh. Ind / phase}}$$

$$\Rightarrow Q_{sh. Ind / phase} \propto \frac{V^2}{f}$$

(Q) What are the percentage increases in the reactive power of the shunt capacitor and the shunt inductor if the operating voltage and frequency are increased by 10%.


Sol

$$Q_{sh. Cap} \propto V^2 f$$

$$Q_1 \propto V_1^2 f_1$$

$$Q_2 \propto V_2^2 f_2$$
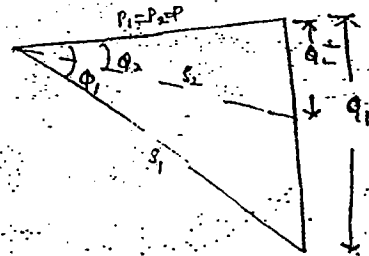
$$\therefore Q_2 \propto (1.1V_1) \times (1.1f_1)$$



$$Q_2 \propto 1.331 V_1^2 f_1$$

$$\rightarrow \frac{Q_2 - Q_1}{Q_1} \times 100 = 33\%$$

(ii) $Q_{sh} \text{ Indu} \propto \frac{V_1^2}{f}$

$$Q_1 \propto \frac{V_1^2}{f_1}$$



$$Q_2 \propto \frac{V_2^2}{f_2}$$

$$\rightarrow Q_2 = \frac{(1.1V_1)^2}{(1.1)f_1}$$

$$Q_2 = \frac{1.21V_1^2}{1.1f_1} = \frac{1.1V_1^2}{f_1}$$

$$Q_2 - Q_1 = 0.1 \rightarrow 10\%$$

→ System Study

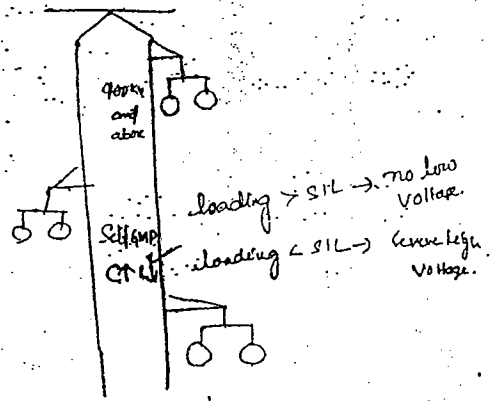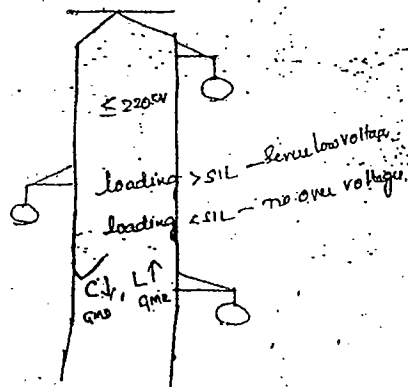


→ In EHV line the shunt compensation is Shunt capacitor, resulting powerfactor correction

→ In modern EHV line the shunt compensation is Shunt Inductor resulting in reduction of voltage.

→ The shunt compensation doesnot affect the power system stability since the reactance of the line is not affected by shunt cap & shunt ind.

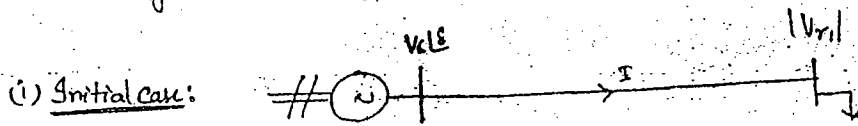
→ SERIES CAPACITOR: In this case the voltage at the end of the tr. line will be embolled by controlling the product of the reactance and the net reactive power of the line is. Controlling the voltage drop



$$|V_{r1}| = |V_s| - |\Delta V_1|$$

$$|\Delta V_1| = |IR \cos \phi_r + IX_L \sin \phi_r|$$

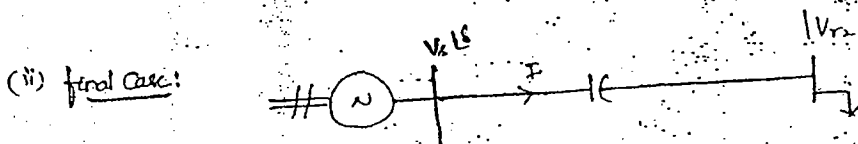$\phi_r \rightarrow$ phase angle of the load.



$$\uparrow |V_{r2}| = |V_s| - |\Delta V_2|$$

$$\downarrow |\Delta V_2| = |IR \cos \phi_r + I(X_L - X_C) \sin \phi_r|$$

$|V_{r2}| > |V_{r1}| \rightarrow$ improvement in voltage.

The improvement in the voltage by the series capacitor will be

$$|\Delta V_c| = |IX_C \sin \phi_r| \Rightarrow \text{Booster in the voltage}$$

Hence the series capacitors are also called as BOOSTER.

→ As the capacitor is connected in series, the % Compensation given

$$\text{to the line reactance} = \frac{X_C}{X_L} \times 100$$

→ In tr. line

$$P_{\max 1} = \frac{V_s V_r}{X_L}$$

$$\uparrow P_{\max 2} = \frac{V_s V_r}{(X_L - X_C)}$$

steady state stability limit

$$\Rightarrow \frac{Q_{sh \text{ cap}}}{Q_{re \text{ cap}}} = \frac{\sin \phi_r \cdot V}{IX} = \frac{\sin \phi_r}{\frac{IX}{V}} = \frac{\sin \phi_r}{\epsilon}$$


Since p.f. of the load $\cos \phi_r = 0.8$ (generally)
 $\sin \phi_r = 0.6$

$$\therefore \frac{Q_{sh \text{ cap}}}{Q_{re \text{ cap}}} = \frac{0.6}{\epsilon} > 1.0$$

- For STL — $\epsilon = 0.06$
- MIL — $\epsilon = 0.09$
- LTL — $\epsilon = 0.12$

Hence $Q_{sh \text{ cap}} > Q_{re \text{ cap}}$ for the same voltage.

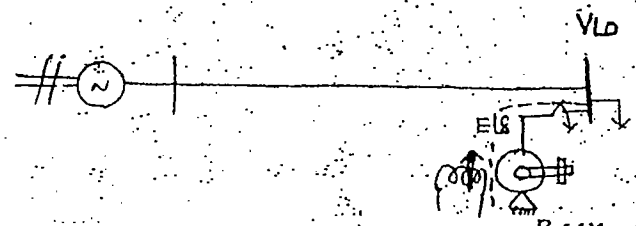→ SYNCHRONOUS CAPACITOR & SYNCHRONOUS MOTOR



Reactive power of trans. line is.

$$Q_r = \frac{|V_s||V_r|}{|B|} \sin(\beta - \delta) - \frac{|A|}{|B|} |V_r|^2 \sin(\beta - \delta)$$

$$Q = \frac{|E||V|}{|X|} \cos \delta - \frac{1.0}{|X|} |V|^2$$

→ No loaded ($\delta = 0$) (∵ SFC not connected to any load and also not meant any thing to drive)

$$\Rightarrow Q = \frac{|E||V|}{|X|} - \frac{1.0}{|X|} |V|^2$$

$$Q = \frac{|V|}{|X|} [|E| - |V|]$$

$R \ll X \Rightarrow |X| = |X|$
 (Syn. motor) $\Rightarrow \theta = 90^\circ$

$\delta =$ Torque angle (or) load angle.

Assume $C \approx 0$ (No shunt element connected)
 ↓
 Short link.

$\Rightarrow A = 1.0$
 $\alpha = 0$

Case (1): If $Q > 0$ provided $|E| > |V| \Rightarrow$
(1/3)

\Rightarrow Reactive power flowing from load to Bus.

\Rightarrow Synchronous Capacitor (or) Condenser.

\rightarrow A No loaded syn. m/c working with over excitation is called Syn. Capacitor / Condenser.

\rightarrow Since loading $>$ SIL Hence the Syn. Capacitor is called

as power factor correction device rather than Voltage control device.

\rightarrow Hydel plants can be operated as Syn. Capacitor / Condenser. due to dry season has to increase p.f (or) voltage control by supplying reactive power. (in addw days)

Case (2): $Q < 0$, $|E| < |V| \rightarrow$ Syn. Inductor (or) Syn. coil.

- A no loaded syn. m/c. working with under excitation is called as Syn. Inductor (or) Syn. coil.

\rightarrow Syn m/c can be worked as Syn. Inductor provided that

$$\boxed{\text{loading} < \text{SIL}}$$


\rightarrow The syn m/c having a specific design. that is it has the voltage rating at same as that of the bus voltage and the size of the rotor is smaller because it is working under no load condition.

\rightarrow In modern p.s system m/c the shunt capacitors are more preferred when compared to syn. m/c, due to the following comparisons.

SHUNT CAPACITOR

(i) The Control of voltage (or) Reactive

Power is in step nature

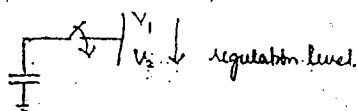


(ii) $P_2 = P_1 = P$

(iii) There is no starting method

(iv) For the same operating voltage the cost of the capacitor is less

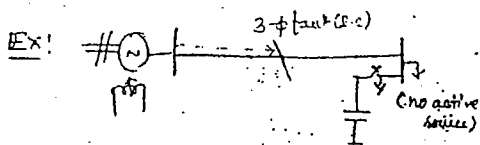(v) It will not raise the fault level during fault conditions



$I_f = I_g$ (Since, cap (or) SMC doesn't supply any current to the fault)

(vi) It doesn't associated with stability

SYNCHRONOUS CAPACITOR

(i) The Control of voltage (or) reactive power


smooths over a wide range due to change of excitation.

(ii) P_2 is slightly more than P_1 due to mechanical losses of Synchronous motor

(iii) It requires certain starting methods

(iv) For the same operating voltage the cost of the m/c is high.

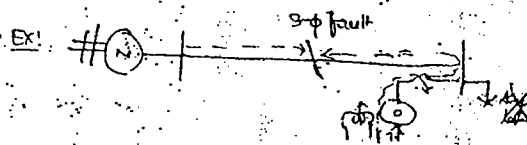(v) It will raise the fault level during the fault conditions.




$I_f = I_g + I_{sync}$

(vi) It is associated with stability since it is of Synchronous motor with some excitation.

2/2/10

→ SYNCHRONOUS PHASE MODIFIER (Power factor Correction device)

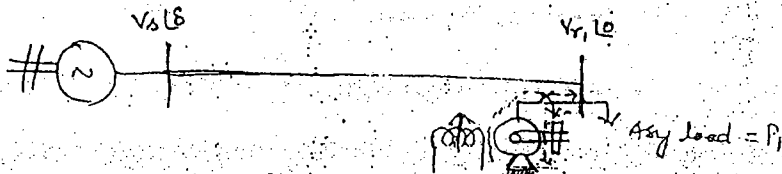Any loaded synchronous machine working with over excitation is called as Synchronous phase modifier.




local load = $p \ll P_1$

Overall load $P_2 = P_1 + p$

$$Q = \frac{V}{X} [E \cos \delta - V]$$

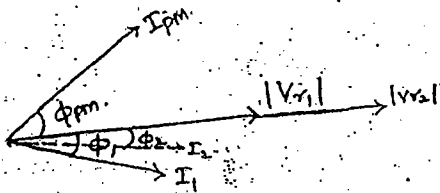$Q > 0$, $E \cos \delta > V \rightarrow$ Synchronous phase modifier



$$|V_{s2}| > |V_{s1}|$$

$$\phi_2 < \phi_1$$

$\cos \phi_2 > \cos \phi_1 \Rightarrow$ power factor correction device.

3-09

(Q) Match the following

A. Shunt capacitor (4):

B. Shunt Inductor (3)

C. Series capacitor (2)

D. Series Inductor (1)

1. Do reduce fault level

2. Do improve the stability

3. Do limit the Ferranti effect

4. Do improve p.f of the load.

\rightarrow Rating of the synchronous phase modifier = $\sqrt{P^2 + Q_{pm}^2}$ KVA

$$\cos \phi_{pm} = \frac{P}{S} \text{ leading}$$


\rightarrow The amount of reactive power supplied by the synchronous phase modifier

$$Q_{pm} = Q_1 - Q_2$$

$$= S_1 \sin \phi_1 - S_2 \sin \phi_2$$

$$= \frac{P_1 \tan \phi_1}{\cos \phi_1} - \frac{P_2 \tan \phi_2}{\cos \phi_2}$$
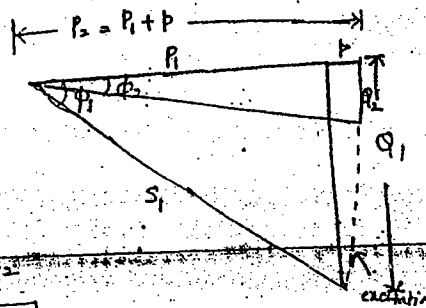
$$Q_{pm} = P_1 \tan \phi_1 - P_2 \tan \phi_2$$




→ TAP CHANGING TRANSFORMER

→ The voltage of the load can

also be controlled either
by increasing the no. of

turns or decreasing the
no. of turns by providing

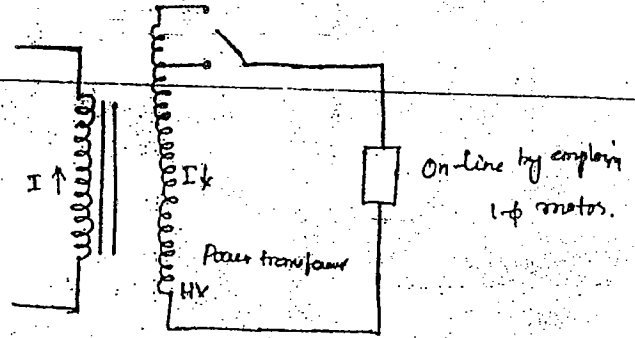the tap changer of the transformer which is known as tap changing transformer



→ The tap changing can be done on online mechanism by employing single phase motor.


→ For all power transformers the facility of tap changing is provided.

→ In addition As the loads are the most inductive loads then the improvement in voltage given by the tap changing transformer will not bring the voltage into the regulation level so the other voltage control device which are discussed are also to be installed along with tap changing of the transformer.

→ In high voltage side the magnitude of the current is less so that the intensity of the spark that could be taken by place while changing the tapping is less.

→ WAVE TRAVELLING - UNIFORMLY DISTRIBUTED LINE CONSTANTS ($R=0$)

Case (i) Line is open circuited

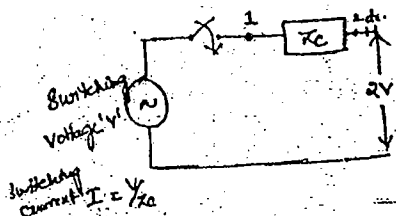

This can be understood by (i) Energy balance (ii) Wave stacking

(i) Energy Balance

At '1'

$$\frac{1}{2} LI^2 = \frac{1}{2} CV^2$$

$$\frac{V}{I} = \sqrt{\frac{L}{C}} = Z_c$$

$$V = I \cdot Z_c$$

At '2'

$$\frac{1}{2} LI^2 = \frac{1}{2} CV^2$$

$$\frac{V}{I} = \sqrt{\frac{L}{C}} = Z_c$$

$$V = I \cdot Z_c$$

In dx

$$\frac{1}{2} L dx I^2 = \frac{1}{2} C dx V^2$$

$$\frac{V}{I} = \sqrt{\frac{L}{C}} = Z_c$$

$$V = I \cdot Z_c$$

→ At the end of the tr. line the energy stored in the Inductor will give away an instantaneous voltage to the capacitor where as the capacitor is unable to discharge the previous energy that was stored.

$$\therefore \frac{1}{2} LI^2 dx = \frac{1}{2} C e^2 dx \quad e = \text{Inst. Voltage}$$

$$\frac{e}{I} = \sqrt{\frac{L}{C}} = Z_c$$

$$e = I \cdot Z_c = V$$




$$V_c = V + e = V + V = 2V$$

$$V_c = 2V$$

→ When the switch is closed then there will be current waveform and the voltage waveform that will be travelled in the tr. line. However at the end of the line the current has to become zero and according to energy balance principle, the energy cannot be destroyed but it can be converted into another form i.e. static field so that the voltage across the capacitor become $2V$.

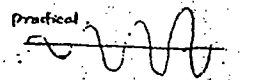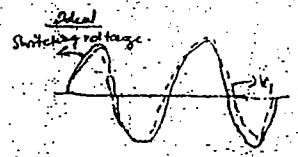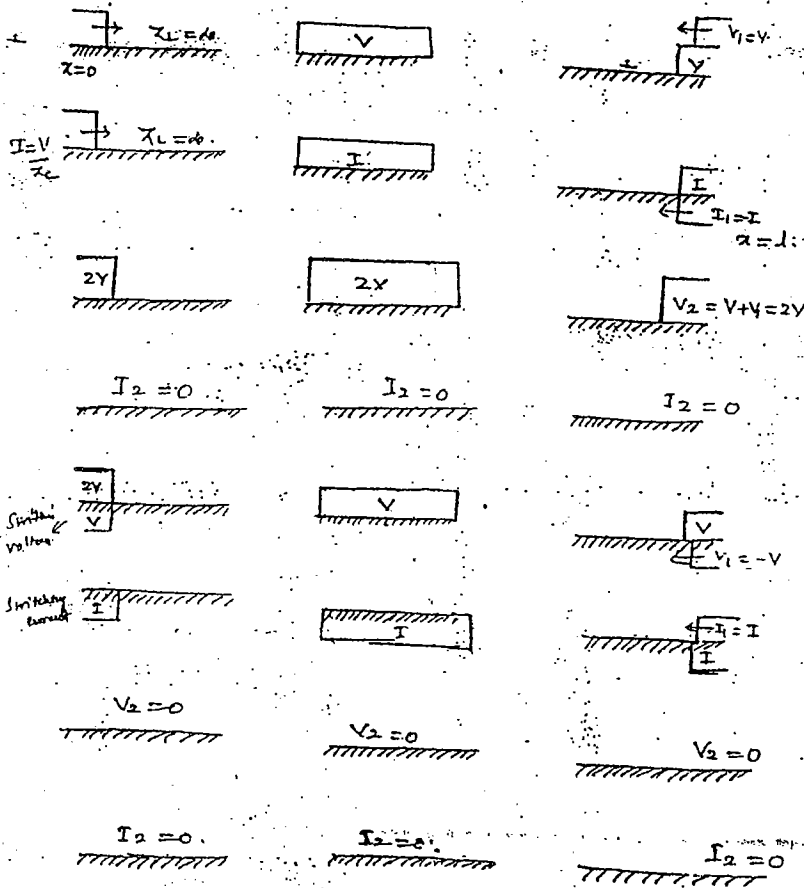(ii) Wave Shaping:

The sign of the switching voltage and switching current are assumed as zero.



$V_1 = 0$, Due to attenuation (R ≠ 0)

$V_1 = V =$ Reflected Voltage.

$I_1 = -I =$ Reflected Current

$\frac{V_1}{V} = 1.0$ Coefficient of reflection for voltage of o.c line.

$\frac{I_1}{I} = -1.0$ C. of reflectn of o.c line

→ (P.T.O) for Explanation.

→ At the end of the tr. line the load impedance is not matched with the characteristic impedance. there will be a concept of reflection to the switching wave form.

- The reflection current can be chosen in opposite to that of switching current because at the end of the line the current has to become zero.

$$V_1 = V = \text{reflected voltage.}$$

$$I_1 = -I = \text{reflected current.}$$

$$\rightarrow \frac{V_1}{V} = 1.0 \quad \text{Coefficient of reflection for voltage of o.c line.}$$

$$\rightarrow \frac{I_1}{I} = -1.0 \quad \text{Coefficient of reflection for current of o.c line}$$

$$V_2 = 2V \quad \text{Refracted voltage.}$$

$$\rightarrow \frac{V_2}{V} = 2 \quad \text{Coefficient of refraction for voltage of o.c line}$$

$$I_2 = 0 \quad \text{Reflected current}$$

$$\rightarrow \frac{I_2}{I} = 0 \quad \text{Coefficient of refraction for current of o.c line.}$$

→ The voltage has become $2V$ at the source point which is an ideal case where as in a practical case voltage is not more than V however under any circumstances the voltage at source should not be more than V .

→ In order to make the voltage V at the source point, the wave travelling can be continued further under the assumption that the supply terminals are interchanged. So the switching voltage & switching current have

become negative.

Subsequent wave travelling (from left)

(Interchanging of supply terminals)

$$V_1 = -V$$

$$I_1 = I$$

$$\frac{V_1}{V} = -1, \quad \frac{I_1}{I} = 1,$$

$$V_2 = 0$$


$$\frac{V_2}{V} = 0,$$

$$I_2 = 0,$$

$$\frac{I_2}{I} = 0.$$

→ As the voltage has become zero and in order to maintain the wave travelling can be continued in a repetition manner.

Case (ii) Line is short circuited.

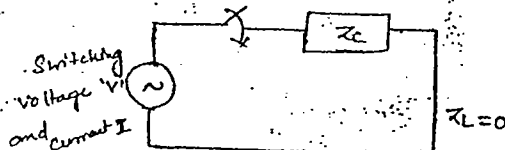

→ At the end of the line the load impedance is not matched with the characteristic impedance so that there will be a reflection wave form and in order to make the voltage zero in a s.c line. It can be assumed that the voltage reflection is negative.

$$V_1 = -V \text{ Reflected Voltage.}$$

$$I_1 = I \text{ Reflected Current}$$

$$\frac{V_1}{V} = -1.0 \text{ Coefficient of reflected voltage for s.c line}$$


$$\frac{I_1}{I} = 1.0 \text{ " " " Current for s.c line.}$$

$$V_2 = 0 \rightarrow \text{Refracted voltage}$$

$$\frac{V_2}{V} = 0 \text{ Coefficient of Refracted } V \text{ for s.c}$$

$$I_2 = 2I \text{ Refracted Current}$$
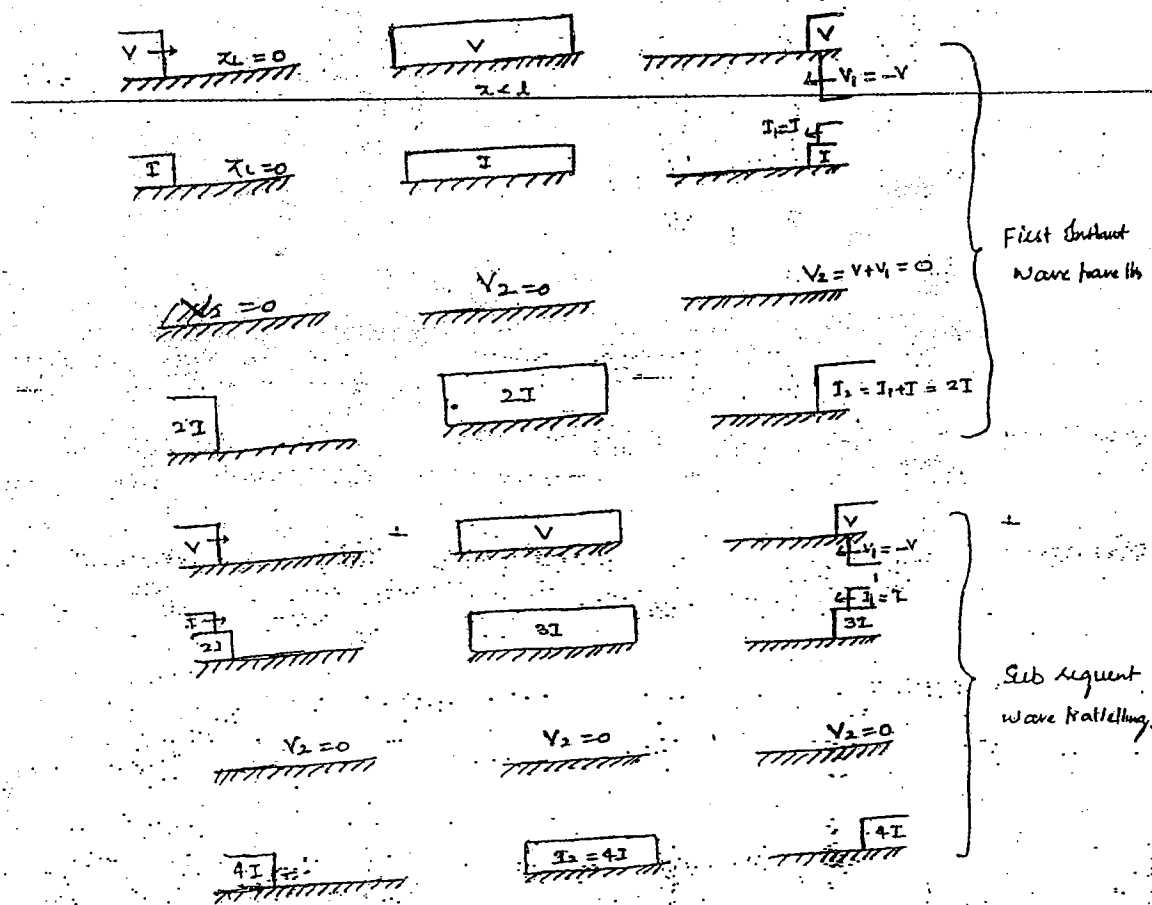
$$\frac{I_2}{I} = 2 \text{ Coef. of Refracted Current of s.c line.}$$



→ Due to the reactance of tr. line the reflected current will be gradually attenuated and become zero over a long tr. line. So that the current is not more than I but the voltage has become zero.


— It is necessary to maintain voltage ' V ' at the source point so that the switching wave travelling is carried out further

→ Subsequent wave travelling.

$$V_1 = -V, \quad I_1 = I, \quad \frac{V_1}{V} = 1.0, \quad \frac{I_1}{I} = 1.0$$

$$V_2 = 0, \quad I_2 = 4I, \quad \frac{V_2}{V} = 0, \quad \frac{I_2}{I} = 4.0$$

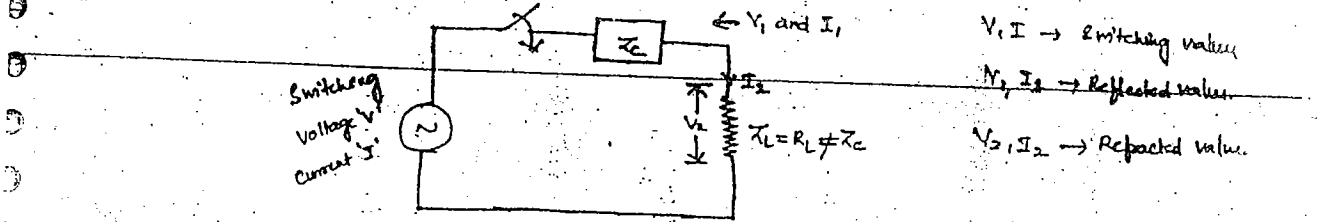Case (iii) Line terminated by an impedance



According to open circuit behavior,

$$V_2 = V + V_1 \rightarrow (1)$$

According to s.c. behavior

$$I_2 = I + I_1 \rightarrow (2)$$

$$\Rightarrow \frac{V_2}{Z_L} = \frac{V}{Z_C} - \frac{V_1}{Z_C} \rightarrow (3)$$

Know V_2 , replace, $V_1 = V_2 - V$

$$\frac{V_2}{Z_L} = \frac{V}{Z_C} - \frac{V_2 - V}{Z_C}$$

$$V_2 = \frac{2V Z_L}{Z_L + Z_C} \quad \text{KV}$$

$$\frac{V_2}{V} = \frac{2 Z_L}{Z_L + Z_C} \quad \text{Coefficient of reflection for Voltage.}$$

$$\frac{V_2}{V} = \frac{2 Z_L}{Z_L + Z_C} \quad \text{Steady state nature of wave.}$$

$$I_2 = \frac{V_2}{Z_L} = \frac{2V Z_L}{Z_L + Z_C} \cdot \frac{1}{Z_L}$$

$$I_2 = \frac{2I Z_C}{Z_L + Z_C} \quad \text{KA}$$

$$\frac{I_2}{I} = \frac{2 Z_C}{Z_L + Z_C} \quad \text{Coefficient of reflection for Current}$$

Do know V_1 , Replace $V_2 = V + V_1$

$$\frac{V_1 + V}{Z_L} = \frac{V}{Z_C} - \frac{V_1}{Z_C}$$

$$V_1 = V \left[\frac{Z_L - Z_C}{Z_L + Z_C} \right] \text{KV}$$


$$\frac{V_1}{V} = \left[\frac{Z_L - Z_C}{Z_L + Z_C} \right] \text{ coefficient of reflection for Voltage.}$$

$$I_1 = \frac{-V_1}{Z_C} = \frac{-V \left[\frac{Z_L - Z_C}{Z_L + Z_C} \right]}{Z_C} = -I \left[\frac{Z_L - Z_C}{Z_L + Z_C} \right]$$

$$I_1 = -I \left[\frac{Z_L - Z_C}{Z_L + Z_C} \right] \text{KA}$$

$$\frac{I_1}{I} = - \left[\frac{Z_L - Z_C}{Z_L + Z_C} \right] \rightarrow \text{Coefficient of reflection for Current}$$

Case (iv) Bifurcated lines - T-network

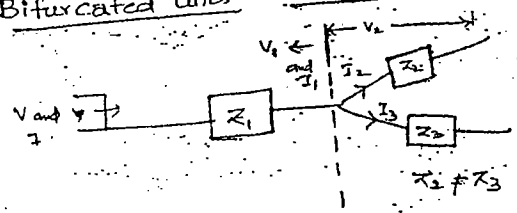

$$V_2 = V + V_1 \rightarrow \textcircled{1}$$

$$I_2 + I_3 = I + I_1 \rightarrow \textcircled{2}$$

$$\frac{V_2}{Z_2} + \frac{V_3}{Z_3} = \frac{V}{Z_1} - \frac{V_1}{Z_1} \rightarrow \textcircled{3}$$

Do know V_2 , Replace $V_1 = V_2 - V$

$$\frac{V_2}{Z_2} + \frac{V_3}{Z_3} = \frac{V}{Z_1} - \frac{V_2 - V}{Z_1}$$

$$V_2 = \frac{-2Y_1 \cdot X_2 X_3}{X_1 X_2 + X_2 X_3 + X_3 X_1}$$

$$\boxed{\frac{V_2}{Y} = \frac{2 \cdot X_2 X_3}{X_1 X_2 + X_2 X_3 + X_3 X_1}}$$

$$I_2 = \frac{V_2}{X_2} = \frac{2Y \cdot \cancel{X_2} X_3}{X_1 \cancel{X_2} + X_2 X_3 + X_3 X_1}$$

$$\boxed{I_2 = \frac{2 I X_1 X_3}{X_1 X_2 + X_2 X_3 + X_3 X_1}} \quad \text{KA}$$

$$I_3 = \frac{V_2}{X_3}$$

$$= \frac{2Y \cdot X_2 \cancel{X_3}}{X_1 X_2 + X_2 \cancel{X_3} + X_3 X_1}$$

$$\boxed{I_3 = \frac{2 I X_1 X_2}{X_1 X_2 + X_2 X_3 + X_3 X_1}}$$

So know V_1 replace $V_2 = V + X_1$

$$V + Y_1 \left[\frac{1}{X_2} + \frac{1}{X_3} \right] = \frac{V}{X_1} - \frac{V}{Y_1}$$

$$Y_1 = V \left[\frac{X_2 X_3 - X_1 X_2 - X_1 X_3}{X_1 X_2 + X_2 X_3 + X_3 X_1} \right]$$

$$\boxed{\frac{V_1}{V} = \left[\frac{X_2 X_3 - X_1 X_2 - X_1 X_3}{X_1 X_2 + X_2 X_3 + X_3 X_1} \right]}$$


→ UNDER GROUND CABLES

OHTL

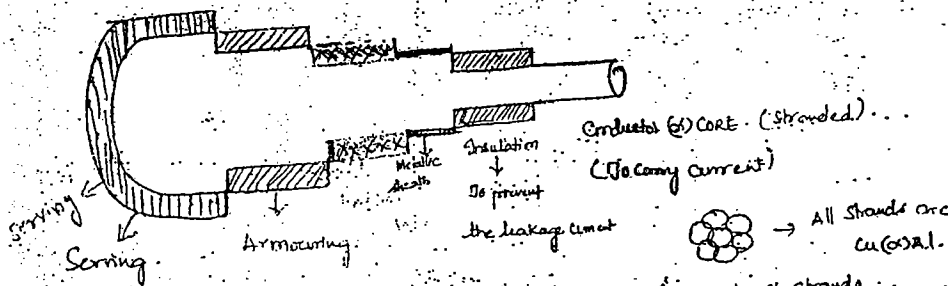- (i) Conductor
- (ii) Line supports
(Galvanized steel structure)
- (iii) Insulation at line supports
(Porcelain)

UGC

- electrical characteristics
- (i) Conductor
 - (ii) Insulation throughout the length
 - (iii) Metallic sheath
- Mechanical characteristics
- (iv) Bedding
 - (v) Armouring
 - (vi) Sealing



- Heavy duty cable → Copper
- In general UGC → of Aluminium

$$\frac{D}{d} = \frac{\text{No. of strands}}{\text{Size of each strand in mm}^2 \text{ of dia}}$$

Ex: $\frac{7}{1.25}, \frac{19}{1.5}$

→ Insulation prevents the leakage current from the surface of the conductor to the ground or earth surface.

Ex: Vulcanized rubber, Impregnated paper, PVC (Poly vinyl chloride), Polyethylene → XLPE (Cross linked polyethylene)

→ used for Multistaged building for distribution as the operating voltage are increased, & power handling capability increases due to the thickness of insulation is high

→ $\leq 1.1 \text{ KV}$ (low voltage)

→ 33KV, 66KV and above

→ KV/cm temp withstanding (i.e. PVC, polythene)

→ Basic Characteristics:

- (i) High dielectric strength

so that the thickness of insulation required for a given voltage.

(2) High insulation resistance: It prevents the leakage current.
It is also MSL.

(3) Non hygroscopic → Do prevent corrosion due to moisture.
(not to absorb moisture from earth)

(4) Free from impurities

(5) It should not be chemically or electrically active.

→ Metallic sheath: To prevent the entry of moisture from the earth surface into the insulating material

Metals used → Aluminium or Lead foils (Pb foils)

→ Bedding: To prevent the mechanical stress from electrical field in the core.

EX: Jute

It is a low grade insulating material.

→ ARMOURING: To prevent the damage of bedding or insulation of the cable while laying or transporting.

It is for the protection against mechanical damage.

EX: Galvanized steel foils.

→ SERVING:

The purpose of the serving is to prevent the occurrence of the corrosion on the armouring. Normally Fiber materials are employed as serving.

→ Normally the cable represented as



r = radius of conductor of core

d = dia

t = thickness of insulation

R = radius of the cable = $r + t$
= $r + t$

→ Classification of Cables:

1. Based on operating voltage.

for the same amount of power, same operating voltage the area of cross section of the conductor of cable is

- (i) Low voltage → 1 KV
- (ii) High voltage → 11 KV
- (iii) Super voltage → 22 KV - 33 KV
- (iv) Extra high voltage → 66 KV
- (v) Extra super voltage → 132 KV and above


→ H.V and above called as power cables } Field nomenclature
 → L.V cables called Distribution cables

2. Based on the insulating material.


- (i) Vulcanised Rubber.
- (ii) Impregnated paper
- (iii) PVC
- (iv) XLPE

3. Based on no. of Cores

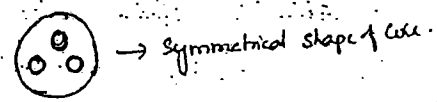- (i) Single core ≥ 66KV
- (ii) Three core ≤ 33KV



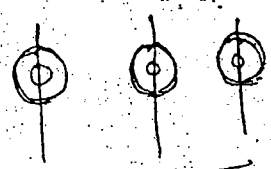↳ Since the insulation requires high for high voltages the cables become bulky.



⇒ 3 - Single core cable ⇒ for high voltages

On symmetrical.

(iii) Three and half → for L.V distribution system.

* Size of neutral = 50% etc of any phase.




→ bulky

3/2/2020


→ 3-Core Cables

- (i) Belted cables → 11KV
- (ii) Screened cables → 22KV - 66KV
- (iii) oil (or) Gas filled cables → 132KV and above.

(i) Belted Cable

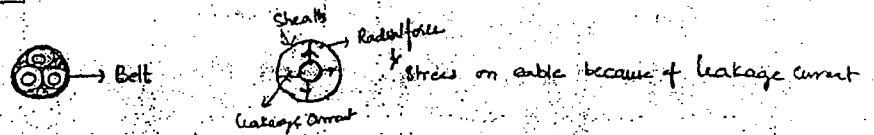


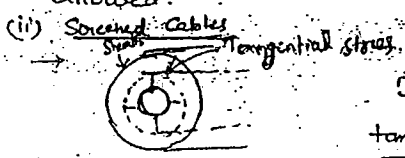→ If there will be a radial stress in the insulating material then the insulating material may not damage. So the radial stress can be allowed.




The insulating material will get damaged because of tangential stress.

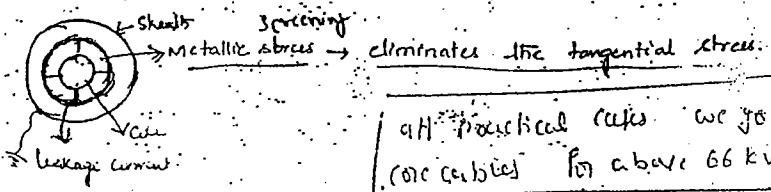to avoid this one inner metallic screen b/w core and sheath



All practical cables we go for 3 single core cables for above 66 KV

(iii) Oil (or) Gas filled Cables

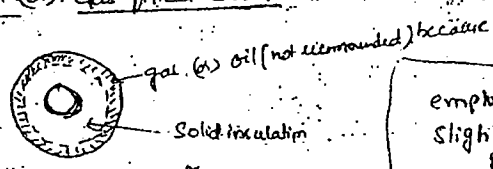

a 3-core cable can also be employed for voltage 66 KV & above with a slight change in the cable insulation but the cost of the cable is high hence single core cables are preferred rather than 3 core cables.

Gas - SF₆ - $\rho = 14 \text{ Kg/cm}^3$ (in c.s. also)

→ FAULTS IN CABLES:

- (i) Open circuit Fault → of cable joints fail the o.c. problem occur
- (ii) Short circuit Fault → Measurement for insulation resistance b/w core & core sheath to identify the o.c. fault



→ (i) if the insulation b/w core and sheath fails then it called Core - Sheath.



(ii) Core - sheath, Core - core fault.

we can identify core-core fault by insulation test of core to core-sheath to identify s.c. fault.

→ To detect the open circuit faults, the insulation resistance

is calculated or measured by using Megger.

→ To detect the s.c faults, by using the measurement of capacitance by using bridges. (H.W. Core - Core, Core - Sheath)

→ Limitations:

(1) For the same power, same operating voltage the area of cross section of the conductor of the cable will be larger when compared to the area of c/s of the conductor of the OHTL so, that the cost of conductor of cable increases.

$$a = \frac{1.5}{v^2 \cos^2 \phi} k \rightarrow \text{for } 3\text{-}\phi \text{ cable}$$

$$a = \frac{0.5}{v^2 \cos^2 \phi} k \rightarrow 3\text{-}\phi \text{ 3-w OHTL}$$

k → Area of c/s of the DC-source supply which is the reference supply.

(2) The amount of insulation required through out the length of the conductor hence the total amount of insulation required will be high. Hence the cost of insulation is high.

(3) Due to the nearness of the two plates the capacitance per km is high hence the charging current per km is high. If the length of the cable increases, the total charging current increases which will result as severe over voltage in the cable. In order to limit the over voltage the cable is not

Recommended beyond 50 km


(*) As the cable is placed in the ground then it is very difficult to locate the location of the fault.

Advantages of Cable:


- 1) The frequency of occurrence of faults are less hence the reliability of the supply is high.
- 2) As the fixed cost of cable is high then the maintenance cost is less compared to O.H.L.

Applications of UGC:

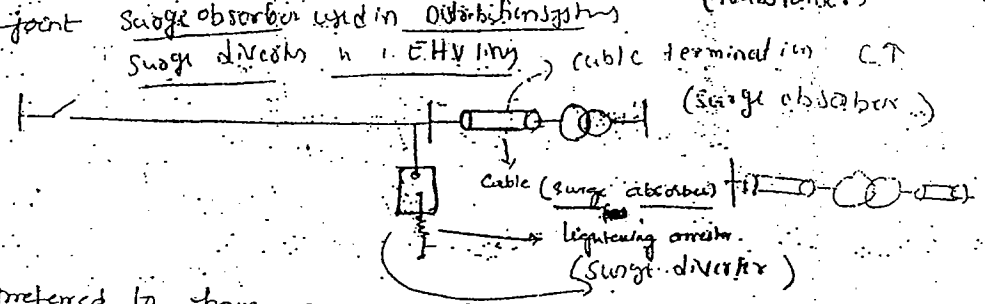- 1) It is well suited for a distributed system in a high populated area so that area will become electrically more beautiful.
- 2) The dead end of OHTL will be connected to the substation through a cable joint surge absorber used in distribution system (Transformer)



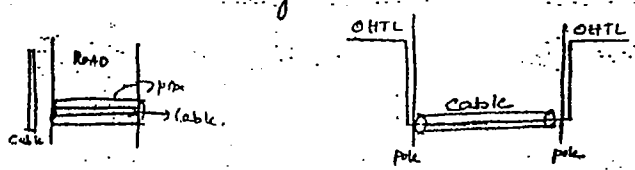3) It is preferred to have a cable joint at road crossing or railway crossing or river crossing.



(4) For all submarine applications the cables are preferred.



CALCULATION OF INSULATION RESISTANCE OF THE CABLE: (1-core cable)

⇒ The electrical characteristics of the cable can be analyzed in single core cable because the bulk amount of power in longer distance can be done at 66 kV & above.

Resistance of the conductor

(a)

$$R_{\text{Cable}} = \frac{\rho l}{a}$$

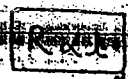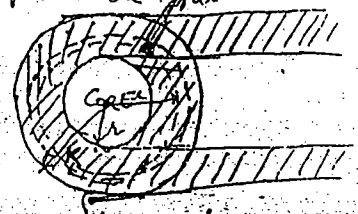

The insulating material is distributed more uniformly from the surfaces of the core towards the sheath and in order to know the insulation resistance use the mathematical solution.

Consider a point 'r' a distance from the centre.

Consider 'x' in the insulation and an elementary length dx

$$\therefore dR_{in} = \frac{\rho dx}{2\pi r l} \quad (\text{circum of cylinder})$$

$$R_{in} = \int \frac{\rho dx}{2\pi r l}$$

$$R_{in} = \frac{\rho}{2\pi l} \ln\left(\frac{R_2}{R_1}\right) M\Omega$$

$$\Rightarrow R_{in} \propto \frac{1}{l}$$

**

(Q) A 20 km length of cable having a insulation resistance of 20 M Ω . What is the insulation resistance of a cable having a length of 5 km.


Sol

$$\frac{R_1}{R_2} = \frac{l_2}{l_1} \Rightarrow \frac{20}{R_2} = \frac{5}{20}$$

$$R_2 = 40 M\Omega$$

→ As temperature $\uparrow \Rightarrow R \uparrow$ further \uparrow of Temp $\Rightarrow R \downarrow$

→ ELECTROSTATIC STRESSES IN THE CABLE:

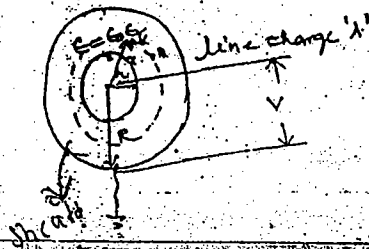

To know the electrostatic stress consider point 'x' at distance of 'x' from the centre.

The electrostatic stress at a distance of 'x' will be

$$E_x = \frac{\lambda}{2\pi\epsilon x}$$

Replace the line charge ' λ ' in terms of the operating voltage of the cable.

$$\begin{aligned} \text{Operating voltage } V &= - \int_R^r E_x dx \\ &= \int_r^R E_x dx \\ &= \int_r^R \frac{\lambda}{2\pi\epsilon x} dx \end{aligned}$$

$$V = \frac{\lambda}{2\pi\epsilon} \ln\left(\frac{R}{r}\right)$$

$$\lambda = \frac{V \cdot 2\pi\epsilon}{\ln(R/r)}$$

$$E_x = \frac{\lambda}{2\pi\epsilon x}$$

$$= \frac{V \cdot 2\pi\epsilon}{\ln(R/r)} \cdot \frac{1}{2\pi\epsilon x}$$

$$E_x = \frac{V \times \sqrt{2}}{x \ln(R/a)} \quad \text{KV/cm/peak}$$

If $x = r$, then

$$E_x = E_{\text{max}} = \frac{V}{r \ln(R/a)} \quad \text{KV/cm/peak}$$

If $x = R$ then

$$E_x = E_{\text{min}} = \frac{V}{R \ln(R/a)} \quad \text{KV/cm/peak}$$

$$r < R$$

→ In a given single core cable, the electrostatic stress is maximum at the surface of the core and it will be minimum at the surface of the sheath.

→ For a 3-core cable

$$E_{max} = \frac{V}{\pi \ln(R/a)} \text{ kV/cm/peak/phase}$$

For 1-core

$$V = \frac{V}{\sqrt{3}} \times \sqrt{2}$$

$$V = \sqrt{2} V$$

Ex: for 33 kV

$$V = \frac{33}{\sqrt{3}} \times \sqrt{2}$$

→ In order to increase the life of cable, then the electrostatic stress at the surface of the core should be reduced for the same operating voltage and also the same size of the cable is 'R'

$$E_x = \frac{V}{\pi \ln(R/a)} \text{ kV/cm/peak}$$

$$f(x) = \pi \ln(R/a) \rightarrow \text{Maximize}$$

$$\frac{df(x)}{dx} = 0 \Rightarrow \frac{R}{\pi} = e \left(\frac{D}{d} \right) = e \quad \text{--- 2.71}$$

Most economical size of the cable so that the stress at the surface of the core is minimized.

$$\frac{R}{\pi} = \frac{1}{e} = \frac{1}{2.71}$$

→ For stability operation of the cable.

$$\frac{R}{\pi} > 0$$

$$\frac{R}{\pi} < \frac{1}{e}$$


$$\frac{R}{\pi} < 0.369$$

Apart from the electrostatic stress the insulating material of the cable will also experience the thermal stress due to small and gradual variation of the load which is known as the steady state stability of the cable.

Variation of Electrostatic stress. Correct selection of size of cable:


Case (i) Initially the cable is selected as
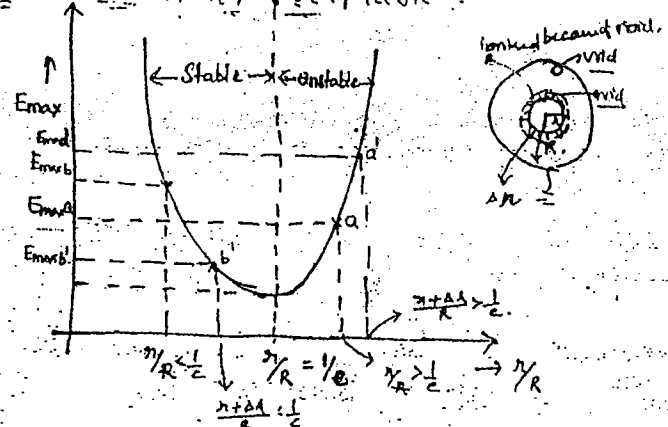
$$\frac{\sigma}{R} > \frac{1}{2} \downarrow$$



Most of the reasons for the failure of the cable is the occurrence of the void in the insulating material.
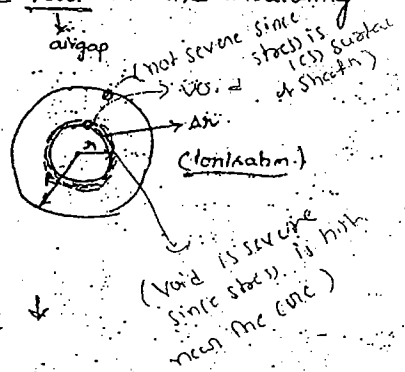
$$\frac{\sigma + \Delta\sigma}{R} > \frac{1}{2} \uparrow$$



Case (ii) Initially the cable is selected as $\frac{\sigma}{R} < \frac{1}{2} \downarrow$

$$\frac{\sigma + \Delta\sigma}{R} < \frac{1}{2} \uparrow$$


Case (iii) is the more suitable for the stable operation of the cable.

→ CAPACITANCE OF SINGLE CORE CABLE:

A single core cable will physically act as a capacitor.

$$C = \frac{\lambda}{V} = \frac{2\pi\epsilon\epsilon_0 x}{\ln(R/x)}$$
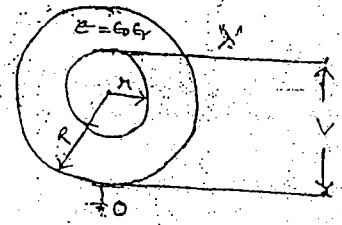
$$\Rightarrow C = \frac{2\pi\epsilon_0\epsilon_r}{\ln(R/x)}$$



$\ln \frac{R}{x} = \ln \frac{R}{d/2} = \ln \frac{2R}{d}$

But in cable, (i) $\epsilon_r > 1.0$

(ii) R is distance between the two plates $\propto \text{cm}$.


So the capacitance in UGC is high as compared to 'C' in OHTL.
 due to $\epsilon_r > 1.8$ (due to presence of the plates)

Char. Impedance, $Z_c = \sqrt{\frac{L}{C}} = 40 \text{ ohms} \rightarrow$ For cable
 (Z_c for UGC is less it is $\frac{1}{10}$ of Z_c in OHTL since 'C' is more)

It is independent of cable length

Charging current $I_c = V \omega C \text{ A/m}$


CAPACITANCE OF 3-CORE CABLE:

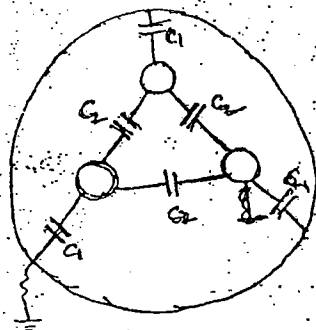

C_1 = Core to sheath capacitance \rightarrow Sheath Capacitor

C_2 = Core to Core capacitance \rightarrow Core Cap.

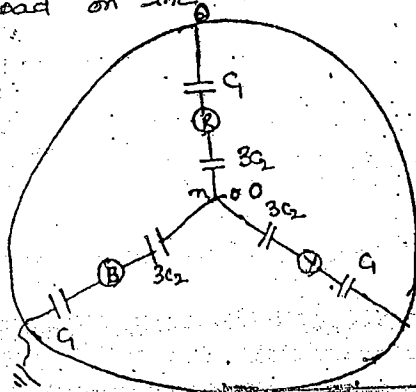To get the capacitance / phase convert the Δ -connected core configuration into an equivalent of Y-configuration, and assuming that the potential of the neutral is zero because the load on the cable is balanced.




Δ	Y
R	$\frac{R}{3}$
X	$\frac{X}{2}$
L	$\frac{L}{3}$
C	$3C$ ($\because X \times \frac{1}{2}$)

$C_{\text{phase}} = C_1 + 3C_2$

$I_c / \text{phase} = V_{\text{phase}} \omega C_{\text{phase}} \text{ Amplitude}$

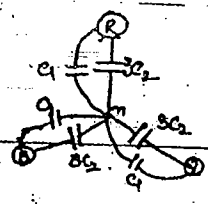$V_{\text{phase}} = \frac{V_{L-L}}{\sqrt{3}}$



∴ potential of neutral = 0
Potential of sheath = 0

Q) In a 3-φ core cable the sheath capacitance 0.1 μF and Core capacitance 0.3 μF. The cable is operated at 11 kV, 3-φ, 50 Hz. The charging current / phase in ampere is

Sol

$C_{\text{phase}} = C_1 + 3C_2$

$= 0.1 + 3(0.3)$



$C_{\text{ph}} = 0.1 + 0.9 = 1.0 \mu\text{F}$

$I_c / \text{phase} = \frac{11 \times 10^3}{\sqrt{3}} \times 314 \times 10^6$

$= 1.995 \text{ A}$

→ If C_1, C_2 are not directly given then the following assumptions are made to calculate C_1 and C_2

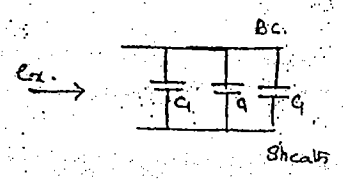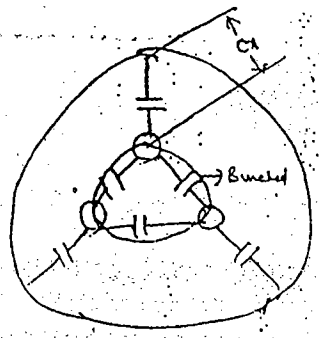(i) Bunch all the 3-cores and measure the capacitance between bunched core and the sheath




$C_x = 3C_1$

$C_1 = \frac{C_x}{3}$

(ii) Connect any two cores to the sheath and measure the capacitance

between the core and the sheath

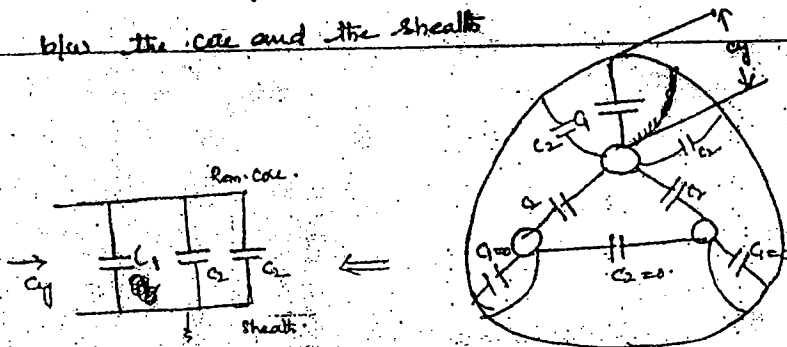

$$C_y = C_1 + 2C_2$$

$$C_2 = \frac{C_y - C_1}{2}$$

$$C_2 = \frac{C_y - \frac{C_x}{3}}{2}$$

$$\therefore C_2 = \frac{3C_y - C_x}{6}$$


$$C_{ph} = C_1 + 3C_2$$


$$= \frac{C_x}{3} + 3 \left[\frac{3C_y - C_x}{6} \right]$$

$$= \frac{3}{2} C_y + \frac{C_x}{3} - \frac{C_x}{2}$$

$$C_{ph} = \frac{3}{2} C_y - \frac{C_x}{6}$$

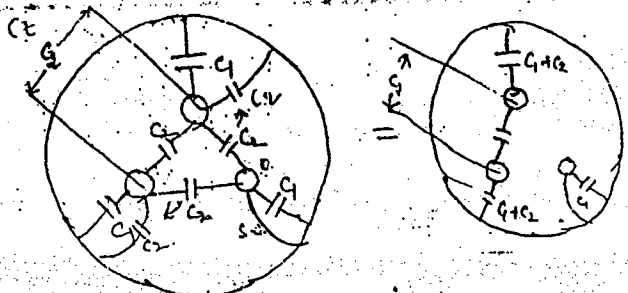(iii) Connect any one of the core to sheath and measure the capacitance between the two cores.



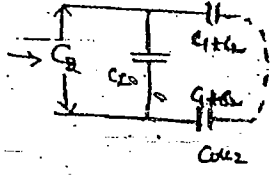

$$C_{eq} = C_2 + \frac{C_1 + C_2}{2}$$

$$= \frac{2C_2 + C_1 + C_2}{2}$$

$$C_2 = \frac{C_1 + 3C_2}{2}$$

$$C_2 = \frac{C_n}{2}$$

$$C_n = 2C_2$$



Q In a 8-Core cable the capacitance b/w the two cores is 0.25 μF when the other core is connected to sheath. The capacitance to neutral in μF is

Sol

$$C_2 = 0.25 \mu F$$


$$C_n = 2 \times 0.25 = 0.5 \mu F$$

→ GRADING OF THE CABLES: The grading of the cable means reduce the difference between the maximum electrostatic stress to the minimum electrostatic stress by way of reducing the maximum stress so that the same size of the cable can be employed at higher voltages, which will increase the power handling capacity (or) for the same operating voltage, the size of the cable will reduced so that the cost of the cable will be reduced.

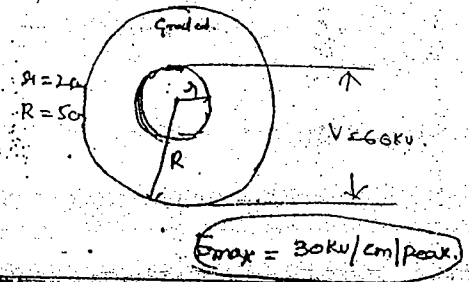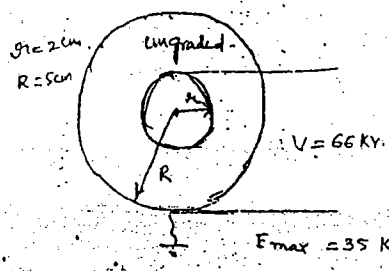

$$E_{max} = 35 \text{ kV/cm peak}$$

$$E_{max} = 30 \text{ kV/cm peak}$$

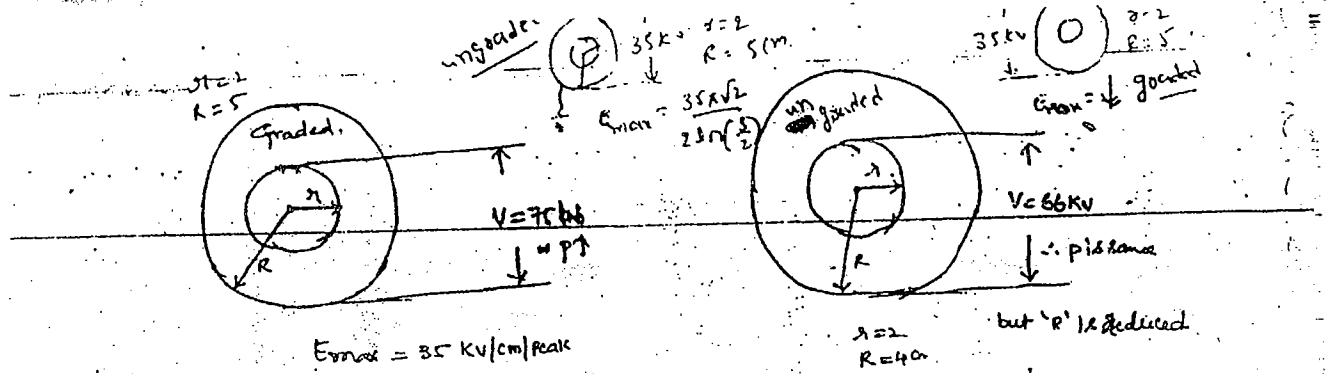

The grading principle can be obtained by using


- (i) Capacitance grading \rightarrow Use more than one insulating material.
- (ii) Intersheath grading \rightarrow Use more than one intersheaths, but same insulating material.

(i) Capacitance grading:

Use more than one insulating material.

Three materials of permittivity ϵ_1, ϵ_2 and ϵ_3

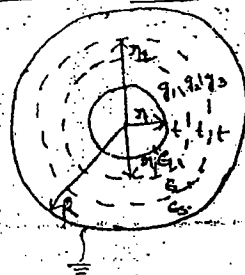Case (i) If the cable is operating with non uniform maximum electrostatic stresses then the insulating material which is having the highest product of the dielectric strength and the permittivity is placed near the core where as the lowest product will be placed near the sheath.



$g_1 =$ dielectric strength kV/cm

$g_2 =$ kV/cm

$g_3 =$ kV/cm

$g_1 \neq g_2 \neq g_3$

$$G_1 = g_1 \times t$$

$$G_2 = g_2 \times t$$

$$G_3 = g_3 \times t$$

$\Rightarrow G_1 \neq G_2 \neq G_3 \Rightarrow$ Ultimate dielectric strengths.

Max

Working stress,

$$E_{max1} = \frac{\lambda}{2\pi\epsilon_1 r_1}$$

$$E_{max2} = \frac{\lambda}{2\pi\epsilon_2 r_2}$$

$$E_{max3} = \frac{\lambda}{2\pi\epsilon_3 r_3}$$

Working stress on insulation = $\frac{\text{Ultimate stress}}{\text{Factor of safety}}$ \rightarrow is same for all dielectric material.

$$E_{\max 1} = \frac{\lambda}{2\pi\epsilon_1 r_1} = \frac{Q_1}{f}$$

$$E_{\max 2} = \frac{\lambda}{2\pi\epsilon_2 r_2} = \frac{Q_2}{f}$$

$$E_{\max 3} = \frac{\lambda}{2\pi\epsilon_3 r_3} = \frac{Q_3}{f}$$

$$\therefore \lambda = 2\pi\epsilon_1 r_1 \frac{Q_1}{f} = 2\pi\epsilon_2 r_2 \frac{Q_2}{f} = 2\pi\epsilon_3 r_3 \frac{Q_3}{f}$$

$$\epsilon_1 r_1 Q_1 = \epsilon_2 r_2 Q_2 = \epsilon_3 r_3 Q_3$$

$$r_1 < r_2 < r_3$$

$$\epsilon_1 Q_1 > \epsilon_2 Q_2 > \epsilon_3 Q_3$$

(Q) A Capacitance grading is employed in cable by using 3 materials 3 insulating materials having the permittivities of 2, 3 and 4. The dielectric strengths of the materials are 20 kV/cm, 30 kV/cm and 15 kV/cm. The materials which are arranged w.r.t the core of the cable is

Sol

$$\epsilon_1 = 2, \quad \epsilon_2 = 3, \quad \epsilon_3 = 4$$

$$Q_1 = 20, \quad Q_2 = 30, \quad Q_3 = 15$$

$$\epsilon_1 Q_1 = 2 \times 20 = 40, \quad \epsilon_2 Q_2 = 3 \times 30 = 90, \quad \epsilon_3 Q_3 = 4 \times 15 = 60$$

\therefore Arrangement is 3, 4, 2. (Core)

** Arrangement w.r.t sheath; 2, 4, 3

\rightarrow The operating voltage of the cable if the stress is given.

$$E_{\max} = \frac{V}{r \ln(r_2/r_1)}$$

$$V = \frac{E_{\max} \times r \ln(r_2/r_1)}{\ln(r_2/r_1)} \quad \text{or} \quad V = \frac{E_{\max} \times r \ln(r_2/r_1)}{\ln(r_2/r_1)} \text{ kV/cm}$$

operating Voltage

$$V = \frac{E_{max1}}{\sqrt{2}} \pi \ln\left(\frac{r_2}{r_1}\right) + \frac{E_{max2}}{\sqrt{2}} \pi_1 \ln\left(\frac{r_3}{r_1}\right) + \frac{E_{max3}}{\sqrt{2}} \pi_2 \ln\left(\frac{r_3}{r_2}\right)$$

KV/cm.
KV/rms

Case (i) The cable is working with uniform working stress then the material which is having highest permittivity will be placed near the core and the material which is having lowest permittivity will be placed near the sheath.

$$q_1 = kv/cm.$$

$$q_2 = kv/cm$$

$$q_3 = kv/cm$$

$$q_1 \neq q_2 \neq q_3$$

$$G_1 = q_1 \times t_1, \quad G_2 = q_2 \times t_2, \quad G_3 = q_3 \times t_3$$

$$\Rightarrow G_1 = G_2 = G_3 = G$$

$$E_{max} = \frac{\lambda}{2\pi \epsilon_1 r_1}$$

$$E_{max} = \frac{\lambda}{2\pi \epsilon_2 r_1}$$


$$E_{max} = \frac{\lambda}{2\pi \epsilon_3 r_2}$$

$$\lambda = 2\pi \epsilon_1 r_1 = 2\pi \epsilon_2 r_1 = 2\pi \epsilon_3 r_2$$

$$\epsilon_1 r_1 = \epsilon_2 r_1 = \epsilon_3 r_2$$

$$r_1 < r_2 < r_3$$

$$\epsilon_1 > \epsilon_2 > \epsilon_3$$

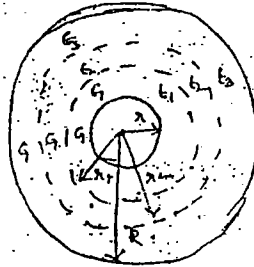


Since the stress are same the operating voltage is

$$V = \frac{E_{max}}{\sqrt{2}} \left[r \ln\left(\frac{r_1}{r}\right) + r_1 \ln\left(\frac{r_2}{r_1}\right) + r_2 \ln\left(\frac{R}{r_2}\right) \right] \quad \text{KV/rms}$$

(Q) The C-grading is employed in a 1-core cable having the permittivities of 1, 2, and 3 and they are working with uniform stress of 30KV/cm. The arranging of the material w.r.t to core is 3, 2, 1

4/02/2020

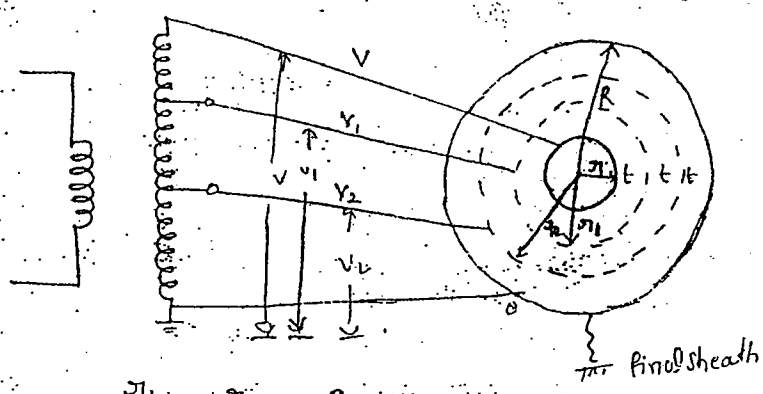INTER SHEATH GRADING: More than one sheath



$$\frac{r_1}{r} = \frac{r_2}{r_1} = \frac{R}{r_2} = K$$

Maximum electrostatic stress without grading

$$\uparrow E_{max1} = \frac{V}{r \ln(r_1/r)} = \frac{V}{r \ln\left(\frac{R}{r_2} \frac{r_2}{r_1} \frac{r_1}{r}\right)} = \frac{V}{r \ln(K^3)} = \frac{V}{3r \ln(K)}$$

The grading principle can be obtained by maintaining the surfaces of the core and intersheaths are at different potentials with the help of a transformer having tappings on cable side so that there will be uniform electric field intensity throughout the cable

$$\downarrow E_{max2} = \frac{V-V_1}{r \ln(r_1/r)} = \frac{V_1-V_2}{r_1 \ln\left(\frac{r_2}{r_1}\right)} = \frac{V_2-0}{r_2 \ln\left(\frac{R}{r_2}\right)}$$

For the same operating voltage, $E_{max 2} \downarrow$

$$\frac{V_1 - V_2}{\sigma_1 \ln(K)} = \frac{V_2}{\sigma_2 \ln(K)}$$

$$V_2 = V_1 \frac{K}{1+K}$$

$$\frac{V - V_1}{\sigma_1 \ln(K)} = \frac{V_1 - V_2}{\sigma_1 \ln(K)} \Rightarrow V_1 = \frac{V K(1+K)}{1+K+K^2}$$

$$\therefore E_{max 2} = \frac{V - \frac{V K(1+K)}{1+K+K^2}}{\sigma_1 \ln(K)} = \frac{V}{\sigma_1 \ln(K) (1+K+K^2)}$$

For the same size of the cable and operating voltage, then maximum electrostatic stress (E_{max}) of graded cable is less than that of ungraded cable ($E_{max 1}$).

→ The same size of the cable can be operated at the same voltage (V) to operate at the same voltage the size of the cable can be reduced in order to get equal stress.

$$\frac{E_{max 1}}{E_{max 2}} = \frac{1+K+K^2}{3}$$

$$\frac{\sigma_1}{\sigma_2} = \frac{\sigma_2}{\sigma_1} = \frac{R}{R_2} = e$$

$$\frac{E_{max 1}}{E_{max 2}} = \frac{1+e+e^2}{3}$$

→ For most economical size of the cable for inter sheath grading.

→ if only one intersheath is there

$$\frac{E_{max 1}}{E_{max 2}} = \frac{1+K}{2} = \frac{1+e}{2}$$



$$\frac{\sigma_1}{\sigma_2} = \frac{R}{R_1} = K$$

→ For most economical size.


→ ~~most commonly employed grading in the cable is the capacitance grading~~ which can be easily employed and also

the cost of grading will be less. (since for inhomogeneous grading transform is rev so cost is more)

→ LOSSES IN THE CABLE

- (i) Core loss
↓
Copper loss
↓ because of
Core current
- (ii) Dielectric loss
↓
Leakage current
in the insulating
material
- (iii) Sheath loss
↓
Induced sheath
current

(1) Core loss:

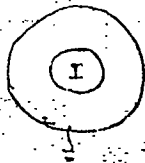

Core loss = $I^2 R$
 $3-\phi \Rightarrow 3 I^2 R$, I = Core Current
 R = Core resistance.


→ For the same amount of current the core loss will increase if the temperature at the surface of the core will increase because of improper heat dissipation, so that the resistance of core will increase.

(2) Dielectric loss:

For 1-core: Dielectric loss = $\frac{V^2}{R_{in}} = V \left(\frac{V}{R_{in}} \right)$, $R_{in} \rightarrow$ insulator resistance.

For 3-core-3 ϕ : Dielectric loss = $\frac{3V^2}{R_{in}}$

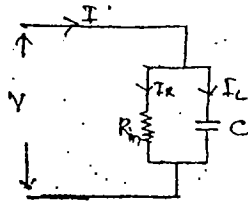Representation of dielectric material electrically as:



$V \left(\frac{V}{R_{in}} \right) = V \cdot V \omega C \tan \delta$


$= V^2 \omega C \tan \delta$

$\delta =$ dielectric angle

$\tan \delta =$ loss (s) dielectric tangent.

Dielectric loss $\propto V^2 f$

Dielectric heat $\propto V^2 f$

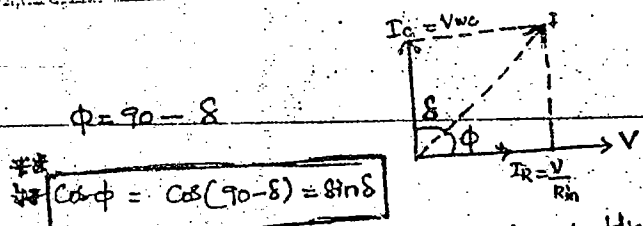

$\phi = 90 - \delta$

$\cos \phi = \cos(90 - \delta) = \sin \delta$

→ Power factor of the cable = sine of dielectric angle.

③ → If $\delta = 30^\circ$, P.f. ⇒ $\cos \phi = \sin 30^\circ = \frac{1}{2} = 0.5$ leading.

∴ $\tan \delta = \frac{I_R}{I_C} = \frac{V/R_{in}}{V\omega C}$

$\frac{V}{R_{in}} = V\omega C \tan \delta$


$\tan \delta = \frac{1}{\omega C R_{in}}$

(3) SHEATH LOSS: It is because of the induced sheath currents (Ac cables)

→ Sheath is near to core.

Rate of change of flux (mutual) which link with sheath.

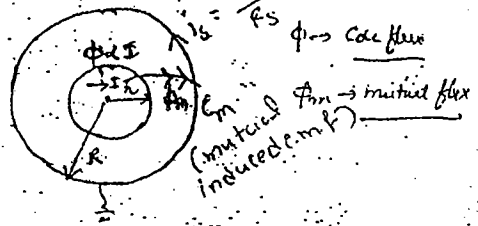$\epsilon_m = \frac{d\phi_m}{dt} = \omega M I$



Sheath current, i_s , by ϵ_m .

M → Mutual inductance b/w core & sheath
 I → Core current

Sheath loss = $i_s^2 R_s(\text{m})$


$R_s(\text{m})$ → mean resistance of the sheath beam
sheath is a foil of rectangular shape

The amount of sheath loss main depends on core current

⇒ If the core current is high then the sheath loss is high because

i_s depends on M , depends on $\phi_m \rightarrow \epsilon_m \rightarrow I$.

→ For a 3-core cable

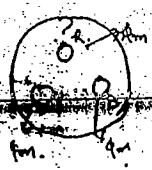

Sheath loss = 0 (because of balanced load because each ϕ_m is 120° apart and resultant $\phi_m = 0 \rightarrow \epsilon_m = 0 \rightarrow i_s = 0 \rightarrow$ No sheath loss)

→ In order to transmit the bulk amount of power, the single core cables are employed rather than 3-core cables, so that the sheath loss can be considered.

→ If the sheath loss is included, then the equivalent resistance of the cable will increase

i.e. $R_{eq} = R(1 + \lambda)$


$R \rightarrow$ Core resistance

$\lambda = \frac{\text{Sheath loss}}{\text{Core loss}}$

→ The induced sheath currents that are produced are classified as

- 1) Sheath eddy currents: These are the currents which are flowing in only one particular sheath of the cable. (Because of un-bonding of the sheath).
- 2) Sheath circulating currents: These are the currents which are flowing from the sheath of one cable to the sheath of another cable. (bonding of the sheaths)

3-core cables running parallel.

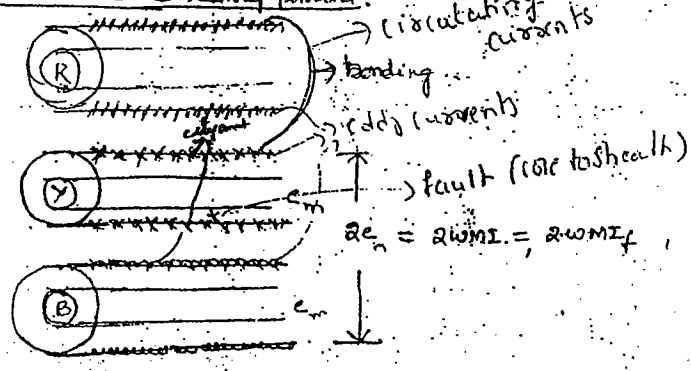

$e_m = 2\omega MI = 2\omega MI_f$, where $I_f =$ fault current due to fault
 $I_f > I$, $I =$ load current


→ There will be puncture of sheath due to excessive voltage that can be developed b/w the two outer sheaths, during the fault condition if the sheath eddy current are allowed. In order to prevent the puncture of the sheaths, sheath circulating currents are allowed rather than eddy currents.

→ If the sheaths circulating currents are allowed by making bonding of the sheaths, then there will be a sheath loss, Due to the sheath loss, the equivalent resistance of the cable will increase and the equivalent inductance will be reduced.

→ To prove $R_{eq} \uparrow$ and $L_{eq} \downarrow$

Consider 1- ϕ cable \Leftrightarrow 1- ϕ transformer, where the sheath is shorted.

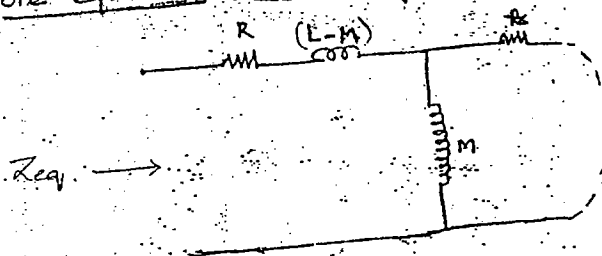The equivalent circuit diagram (electrical equivalent of 1- ϕ cable \Rightarrow 1- ϕ HT)




$$Z_{eq} = R + j\omega(L-M) + \frac{R_s j\omega M}{R_s + j\omega M} \times \frac{R_s - j\omega M}{R_s - j\omega M}$$

$$\Rightarrow Z_{eq} = \left[R + R_s \frac{\omega^2 M^2}{R_s^2 + \omega^2 M^2} \right] + j\omega \left[L - M \frac{\omega^2 M^2}{R_s^2 + \omega^2 M^2} \right]$$

$R_{eq} \uparrow$ $L_{eq} \downarrow$

Hence proved $R_{eq} = R + () \Rightarrow R_{eq} \uparrow$
 $L_{eq} = L - () \Rightarrow L_{eq} \downarrow$ } in sheath loss

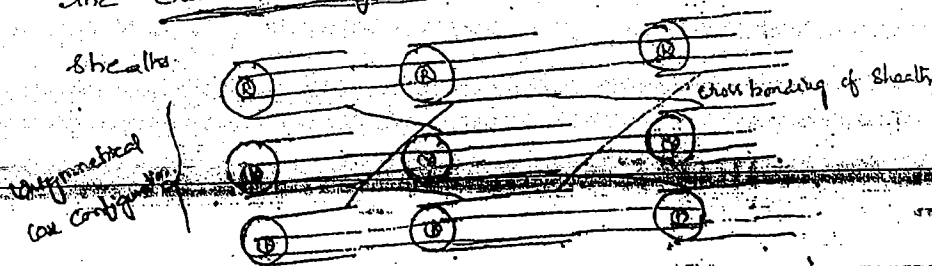→ In order to eliminate the sheath loss it is preferred to have the cross bonding of the sheaths rather than bonding of the sheaths.



→ Due to unsymmetrical core configuration, the sheath loss cannot be eliminated completely. even though the cross bonding of the sheaths are employed

→ In order to eliminate the sheath loss completely, the cross bonding of the sheaths can be done along with transposition of the core.


→ OVER HEAD LINE INSULATORS

— Due to economical reasons, it is preferred to transmit the bulk amount of power over a longer distance. the over-head system is preferred rather than UGC.

— In order to provide the ground clearance between the current carrying element and the ground the line supports are employed. and in order to provide the line to line clearance, the line support is employed with cross arms. In order to provide the electrical isolation between the cross arm and the power conductor a suitable insulation is preferred which is known as the "over-head line insulator".

→ Basic characteristics of the insulating material.

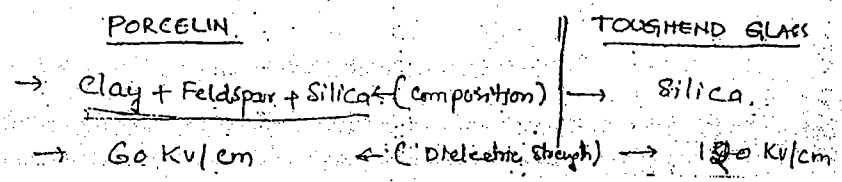- (i) High dielectric strength
- (ii) High insulation resistance
- (iii) Free from impurities.
- (iv) Non-hygroscopic.
- (v) High mechanical strength → to meet wind effect & carry current element




→ Non hygroscopic → As the age of insulator ↑ it will become slowly hygroscopic. Hence frequent replacement is required.

Porcelain Toughest Glass

→ 415V - 3φ to 765 KV (Capacitor) → ≤ 33KV. (For distribution)
 and for HVDC lines.
 ⇒ Porcelain preferred

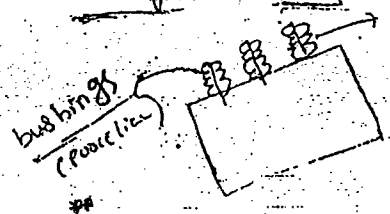→ The Porcelain material is also used as Bushings or Covers for all most all electrical equipments.
 ex: C.O, Transformo. C.P, P.T, etc




→ PORCELIN INSULATIONS:

- (i) Pin Insulators → ≤ 33KV (distribution) [Most Common]
- (ii) Shackle Insulator → ≤ 33KV
 - (1) sudden deviation of the line more than 2°
 - (ii) Road crossing (U) Canal crossings/Rail crossing
 - (iii) Dead end of the line.
- (iii) Stray (or) Guy Insulator → In the dis. op. a mech. support is required at junction poles in order to withstand unequal weights.
- (iv) String (or) Suspension Insulator → (EHV i.e 66KV and above.) (Most Common) #1 in transmission
- (v) Strain (or) Tension Insulator → The application of the shackle insulators at EHV level can be employed with strain (or) tension insulators



→ The insulators which can be employed at the middle of the stray wire in order to prevent the leakage current not to allow to the ground.

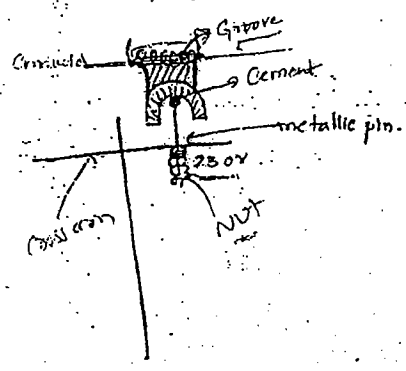(1) PIN INSULATOR:

→ Purpose of the Groove is to house the conductor properly so that the position of the conductor is not disturbed due to wind effect.



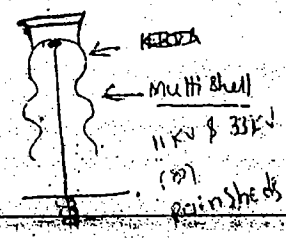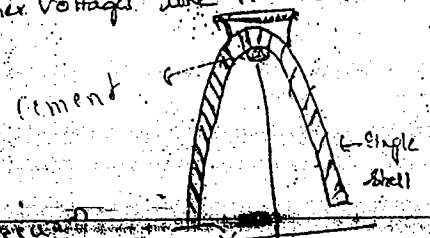→ For higher voltages like 11KV and 33KV in distribution



(Comparison) ... Recommended.


→ Physical Significance of -ve Sequence Component:

The field produced by the -ve sequence component current is opposite to that of the field produced by +ve sequence component current in the stator but it has a relative speed of double the syn. speed w.r.t stator so that an emf is induced in the rotor wdg due to negative sequence flux, which in turn produces the induced current (or) it can be also called as eddy current at double the frequency. ~~So~~ that hence the rotor wdg will get overheated.

→ Zero Sequence Component: Zero sequence component does exist provided

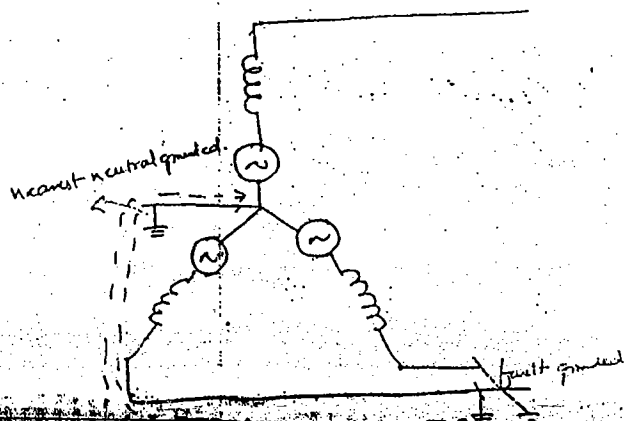- (1) The fault must be grounded fault and
- (2) The nearest neutral must be grounded.

→ If the fault is associated with the ground then the fault current is expected to be flowing from the fault point through ground and enter into the system through nearest neutral grounding. The earth can provide the magnitude without any phase displacement.



Term of the +ve sequence 2.s component.

✓ Ex: In case of Overcurrent protection: $I_{min} = 110\% \text{ of } I$

↓
depends on requirement.

During any type of fault, the +ve sequence subtransient current exists which is always more than the +ve sequence steady state current so that the relay will pick up.

→ The Relay can protect the existing electrical equipment for all types of faults however for line to ground fault the intensity of fault current is less and for 3-φ fault the intensity of the fault current is high hence the relays are ~~set~~ ^{set} with their minimum pick up values by considering the line to ground fault.

→ Negative Sequence Components: There is no induced voltage in the stator winding due to rotor flux, however there will be a terminal voltage at the fault point so that the corresponding current is expected to be flowing from the fault point towards the stator wdg which is having opposite direction to that of the +ve sequence component current so that such components are called the "Negative Sequence components" and they have a sequence of "RBY"

→ Practically the -ve sequence current cannot flow from fault point to source and it is same as +ve sequence current

Since $E_{R2} = 0$, $V_{R2} \Rightarrow$ drop.

$E_{R2} =$ drop = terminal voltage


$0 =$ drop = terminal voltage

-ve terminal voltage.

0 is greater than +ve terminal voltage hence

-ve sequence current flows from source to load.

During the fault: (Refer fig (i))

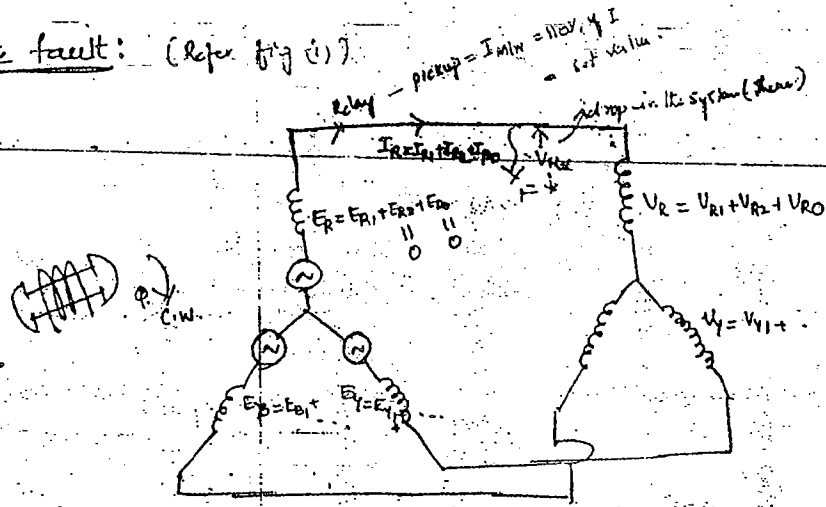

→ Even though the fault is in the stator wdg of the alternator, but there is no change in the rotation of rotor flux i.e. It will continue to rotate in the c.w direction only and the corresponding voltages are induced in the stator wdg with a sequence of RYB. The induced voltages will deliver the corresponding currents to the fault point which in turn produce the corresponding field.


→ The direction of rotation of this fld in the stator wdg is having the same direction of rotation of rotor field so that the corresponding components in phase are called as the +ve sequence sub-transient components and the Reactance (s) impedance is called as +ve sequence sub-transient reactance or impedance.

→ Physical significance of +ve sequence components:

→ Before fault occurs the existing system is dealing with +ve sequence components in a steady state manner and during any type of fault, the +ve sequence components will exist in a sub-transient manner.


→ In order to protect the electrical equipment against the faults the suitable relays are employed having the set value in

→ Do the sequence before fault occurs!

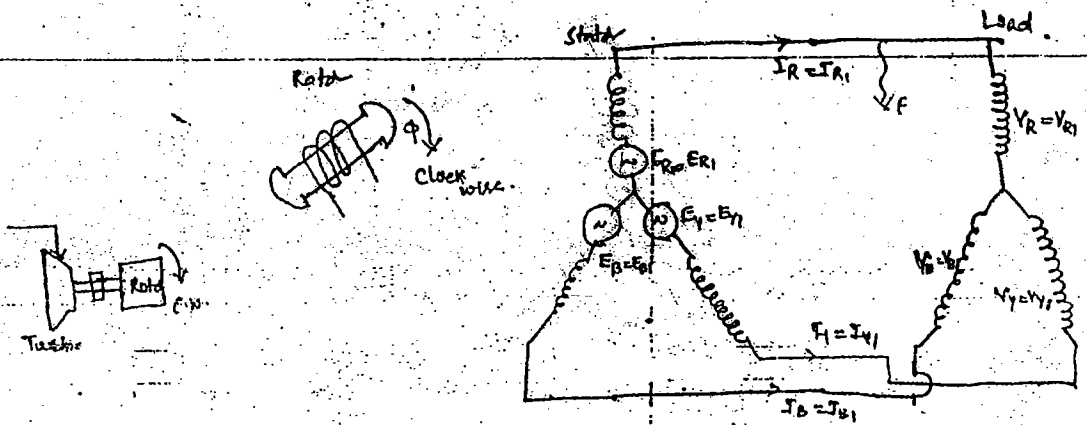

→ It can be assumed as the air gap flux of the stator is rotating in a clockwise direction so that the voltages are induced in the stator having a 3- ϕ winding with sequence of RYB which will be able to deliver the corresponding currents to the load. Based on the magnitude of stator current there will be corresponding stator flux which can be also assumed as the direction of its rotation in clock wise with respect to the rotor of the alternator.

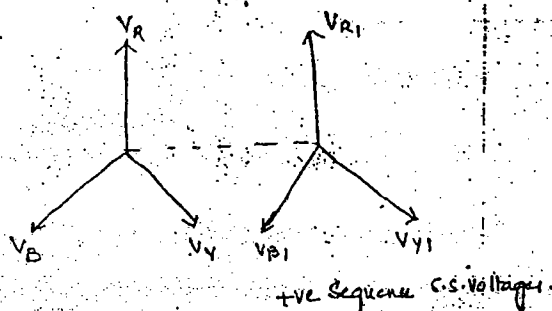→ If the direction of the rotation of the stator field is same as that of the direction of the rotation of rotor field then such electrical quantities in the phasor are called as +ve sequence steady state components and the impedance or reactance that could be offered is called as +ve sequence steady state impedance or reactance.



Will reduce the demagnetisation effect.

Refer during fault condition & Next instances.

**	Fault	* Frequency of occurrence	* Intensity of the fault current (I _f)
Unsymmetrical fault (or) Unbalanced.	L - G	70% → most common	Less severe.
	L - L	15%	
	L - L - G	10%	
Symmetrical (or) Balanced.	L - L - L	5% → least frequent	most severe.
	L - L - L - G		

11/4/10 → L-L-G is more severe compared to L-L (since current is more due to zero potential i.e ground)


→ POSITIVE SEQUENCE COMPONENTS: These are the components having equal in magnitude and 120° phase displacement. These components having the sequence as same as that of the original phase sequence of the network

→ NEGATIVE SEQUENCE COMPONENTS: These are the components having equal in magnitude and 120° phase displacement. The phase sequence of these components is opposite to that of the original phase sequence of the network

→ ZERO SEQUENCE COMPONENTS: These are the components having equal in magnitude without any phase displacement. If there is no phase displacement then there is no phase sequence to compare.

→ Sequence → Order → The direction of rotation in a 3-φ rotating equipment


Before fault:

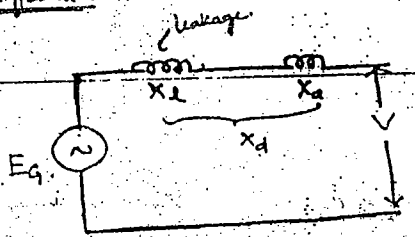


$X_d \rightarrow$ Steady state reactance.

Because of steady state the wave form

is Symmetrical.

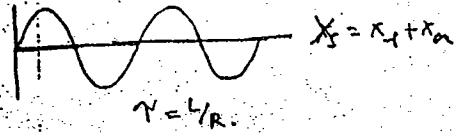


During fault condition

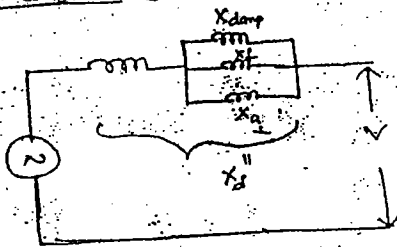

\rightarrow During 1st cycle $\Rightarrow X_d'' = X_l + (X_{damp}) \parallel (X_f) \parallel X_a$

\hookrightarrow Sub-transient period.

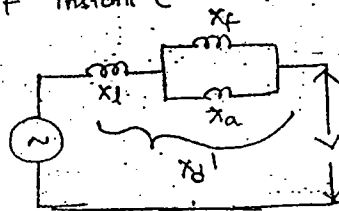\rightarrow For the next instant (2-5 cycles)



X_{damp} will disappear since R is more in damper winding i.e. time constant is 1/s

$$X_d' = X_l + (X_f) \parallel (X_a)$$

\hookrightarrow Transient Reactance (2-5 cycles)

For a given generator, $X_d'' \leftrightarrow X_d' \leftrightarrow X_d$

\Rightarrow Subtransient current are very high than s.s. current

Expt

of a s.c. fault occurs, the armature reaction will result as lesser demagnetization of air gap flux due to dc current apart from the steady state current in the phase.

\rightarrow It is required to maintain the air gap flux so that the counter emf's are produced in the damper and field wdg. when

To get maximum of asymmetrical fault current $\Rightarrow \alpha = 0$:

i.e. $V = 0$, \Rightarrow dc effect high because the inductance stored energy from previous cycle

$$i_m = \frac{\sqrt{2}V}{X} + \frac{\sqrt{2}V}{X}$$

$$i_m = 2 \frac{\sqrt{2}V}{X} \rightarrow \text{Maximum double effect. } \Rightarrow \text{at natural zero crossings}$$



Expl \rightarrow of a short circuit fault occurs, the current in the phases will increase whereas the voltage in the phases ~~is~~ reduces. further the pf of the system will reduce and also the frequency of the system will ~~also~~ slightly reduce. It is interested to calculate the fault current in the phases, because the increase in fault current will increase the heat that can be experience by the winding.



The increase in heat may also result as the failure of the insulation.

\rightarrow it is required to calculate the fault current of the phases & the subtransient currents and they are expressed in terms of rms value because the amount of heat that can be produced does depends upon the rms current.

$$i_p = i_s (\text{rms})$$

\rightarrow S.C Fault on Alternator:

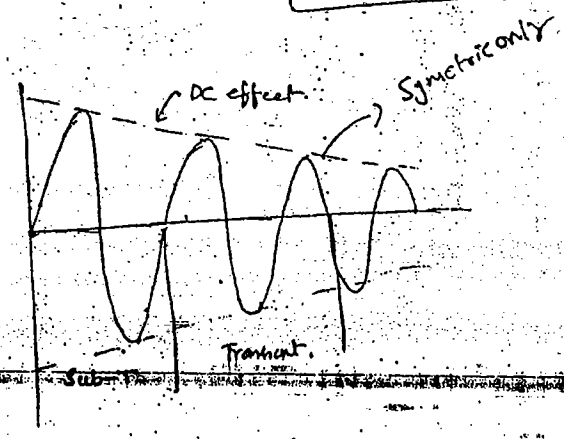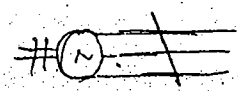

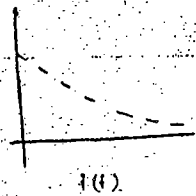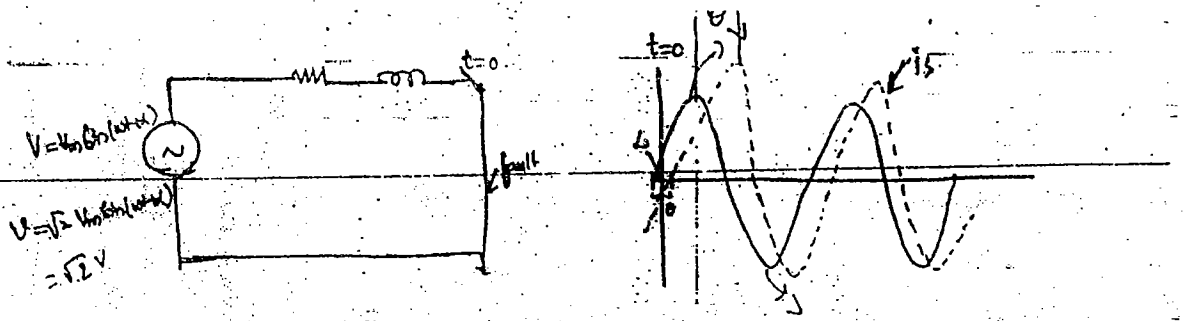

$$i = i_s + i_t$$

$$i_s = \frac{\sqrt{2}V}{Z} \sin(\omega t + \alpha - \theta)$$

$i_s \rightarrow$ steady state current

$i_t \rightarrow$ transient current

$$i(t) = i(0) = i_s(0) + i_t(0)$$

$$= i_t(0) = \frac{\sqrt{2}V}{Z} \sin\left(\frac{\pi}{2} - \theta\right) e^{-t/\tau}$$

\rightarrow Inductor discharging

$$\theta = \tan^{-1}\left(\frac{L}{R}\right)$$

$V \downarrow \quad I \uparrow \quad P \downarrow \quad f \downarrow$

For S.C fault = $\frac{\sqrt{2}V}{Z} \sin(\theta - \alpha) e^{-t/\tau} \rightarrow$ DC effect.

\rightarrow When $i_s(t)$ and $i_t(t)$ are superimposed, then we will get an unsymmetrical wave form. Refer fig (i) (DC effect + i_s)

$$i = \frac{\sqrt{2}V}{Z} \sin(\omega t + \alpha - \theta) + \frac{\sqrt{2}V}{Z} \sin(\theta - \alpha) e^{-t/\tau}$$

During the 1st cycle the maximum effect of dc current will be there.

~~$$i_{max} = \frac{\sqrt{2}V}{Z} \sin(\omega t + \alpha - \theta)$$~~

~~At the instant of fault~~

$$i_{max} = \frac{\sqrt{2}V}{Z} \sin(\omega t + \alpha - \theta) + \frac{\sqrt{2}V}{Z}$$

When fault occurs at $t=0$

$$i_{max} = \frac{\sqrt{2}V}{Z} \sin(\theta - \alpha) + \frac{\sqrt{2}V}{Z}$$

When $\theta = 90^\circ$ ($R \approx 0$)

$$i_{max} = \frac{\sqrt{2}V}{Z} \sin(90 - \alpha) + \frac{\sqrt{2}V}{Z}$$

$$= \frac{\sqrt{2}V}{Z} \cos \alpha + \frac{\sqrt{2}V}{Z}$$

the currents in the phases are reduced.

→ The same thing can also be understood w.r.t to line i.e.

the actual currents in the to line will be reduced so that the inductive reactive power of the system is less than the Capacitive reactive power which will increase the voltage of the phase.

Hence the open ckt fault will be characterized as




- 1) Increase in Voltage
- 2) Reduce in Currents
- 3) Slightly increase in frequency of supply
- 4) Slight improvement in the p.f because of Capacitors dominates

$V \uparrow, I \downarrow, P.F \uparrow, P.T \uparrow$

O.C Fault

→ The increase in voltage of phases will increase the field intensity so that there is a possibility of insulation failure because the dielectric strength of insulation may not be sufficient to withstand the field intensity. It is required to calculate the voltage of the phases and they are expressed in peak value because the system is under subtransient (or) transient period

→ SHORT CIRCUIT FAULT;

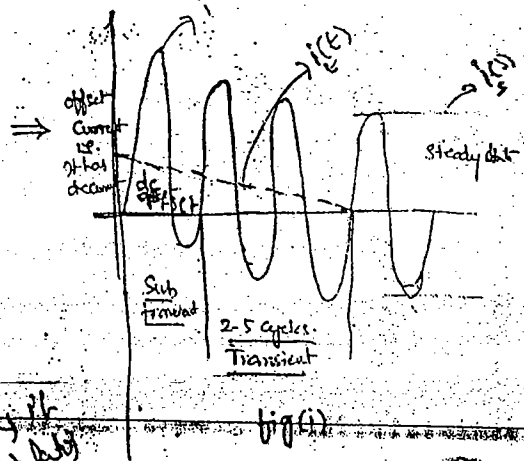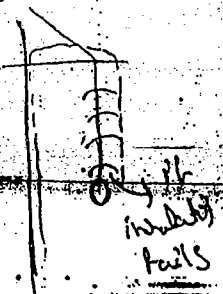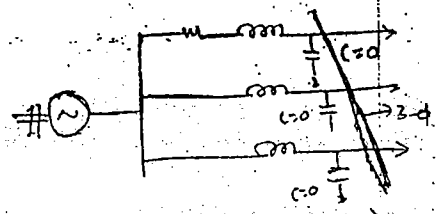

K

→ FAULTS

FAULT

Open ckt (or)
Series fault

Short ckt (or)
Shunt fault.

1. Melting of a fuse or conductor in one phase
 2. Melting of a fuse or conductor in two phases.
- } Unsymmetrical
(or)
unbalanced.

1. The Sic faults does exist due to falling of the tree branches on the wires (or)

(2) failure of the disc insulator in the string (or) failure of the mechanical fittings of the conductor with the string of the insulator.



Based on above condition fault


- are (1) line-ground (L-G)
(2) Line-Line (L-L)
(3) line-line-ground (L-L-G)
(4) line-line-line (L-L-L)
(5) line-line-line-ground (L-L-L-G)

Most or
symmetrical

Symmetrical
(or)
balanced

→ If the conductor will get melt in all the 3 phases then the system is working under no load condition where the no load voltage will be slightly more than rated voltage so that the H will not be treated as fault

→ Open circuit fault:

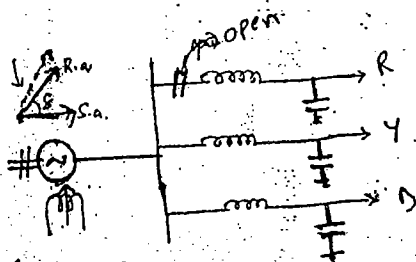

→ Before fault occurs the line is working in a balanced manner and the electrical quantities in the phases are expressed in terms of r.m.s values.

(Steady state)

$$P = P_s - P_r$$

$$= 0$$

$$\Rightarrow N = N_s$$

→ If one of the phase gets melted then the actual loading on the alternator is reduced where as the mechanical IP is same which will result as the symple will experience an acceleration so that the actual speed is slightly more than synchronous speed. The over speed of the alternator will result as the over voltage in the phases, where as

→ The advantage of the Symmetrical Components.

1) If the unbalanced electrical quantity is expressed in terms of balanced electrical components then the mathematical calculations are simple. Hence the time taking to evaluate the unbalanced electrical quantities is less.

$$I_R = I_{R0} + I_{R1} + I_{R2}$$

$$I_Y = I_{Y0} + I_{Y1} + I_{Y2}$$

$$I_B = I_{B0} + I_{B1} + I_{B2}$$

$$Z_R = Z_{R0} + Z_{R1} + Z_{R2}$$

$$Z_Y = Z_{Y0} + Z_{Y1} + Z_{Y2}$$

$$Z_B = Z_{B0} + Z_{B1} + Z_{B2}$$

NOTE:

$$P_R = P_{R0} + P_{R1} + P_{R2}$$

$$P_Y = P_{Y1} + P_{Y2} + P_{Y3}$$

$$P_B = P_{B1} + P_{B2} + P_{B3}$$

* Since power is 3- ϕ , there is no meaning for per phase power. And power never be calculated per phase.


→ The Symmetrical components are balanced components so the Y-phase and B-phase components can be expressed in terms of R-phase by using a suitable notation (vector notation) which is denoted by ' K '.

→ ' K ' is defined as ^{vector} having unity magnitude and 120° phase displacement in an anti clock wise direction.

$$\rightarrow K = 1 \angle 120^\circ = -0.5 + j0.8667 \quad (\text{II})$$

$$\rightarrow K^2 = K \cdot K = 1 \angle 120^\circ \times 1 \angle 120^\circ = 1 \angle 240^\circ = -0.5 - j0.8667 \quad (\text{III})$$
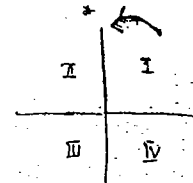
$$\rightarrow K^3 = K \cdot K \cdot K = 1 \angle 120^\circ \cdot 1 \angle 120^\circ \cdot 1 \angle 120^\circ = 1 \angle 360^\circ = 1 \angle 0^\circ = 1.0 + j0.0$$



$$\rightarrow K + K^2 + K^3 = 0$$

$$\Rightarrow 1 + K + K^2 = 0 \quad (\because K^3 = 1)$$


$$K^4 = K^3 \cdot K = K$$

$$K^5 = K^3 \cdot K^2 = K^2$$

→ External Unbalance: \odot

→ If the existing system will experience severe unbalance due to the occurrence of the fault then the electrical quantities in the phases will get severely unbalanced. The unbalanced load voltages are to be evaluated by having individual phase representations. Hence there are three electrical eqns which will provide 3 unbalanced voltages.

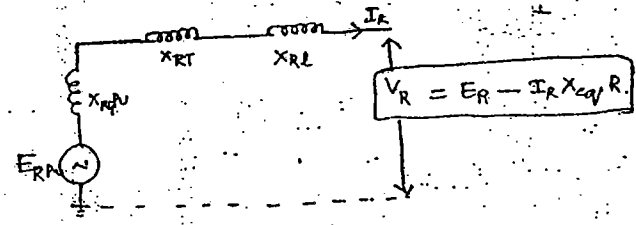→ The time taking is high to evaluate these unbalanced voltages.




Similarly for Y-phase and B-phase.

→ In order to reduce the time taking while evaluating the unbalanced electrical quantities of the phases it is proposed to express the unbalanced phase electrical quantity by a set of 3-balanced electrical quantities.

→ The set of '3' balanced electrical quantities are called as "SYMMETRICAL QUANTITIES (OR) SYMMETRICAL COMPONENTS" which


- are namely:
- 1) Positive Sequence Component — '1'
 - 2) Negative Sequence Component — '2'
 - 3) Zero Sequence Component — '0'
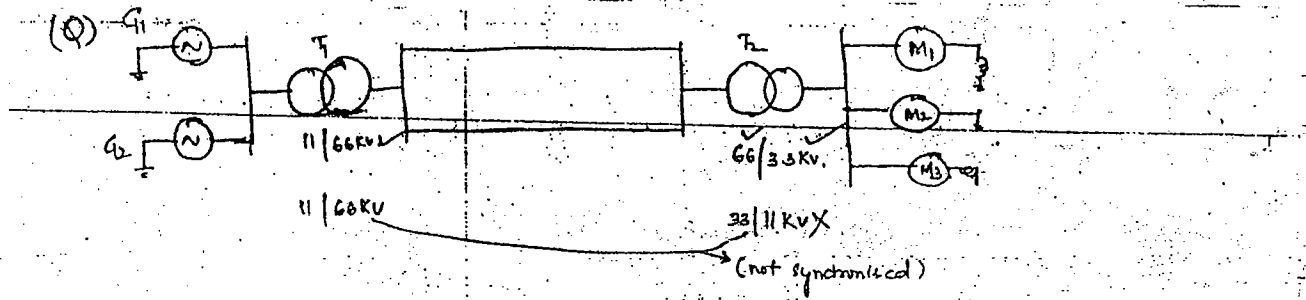
$$\left. \begin{aligned}
 V_R &= V_{R0} + V_{R1} + V_{R2} \\
 V_Y &= V_{Y0} + V_{Y1} + V_{Y2} \\
 V_B &= V_{B0} + V_{B1} + V_{B2}
 \end{aligned} \right\} \Rightarrow \text{balanced} \Rightarrow \text{3-balanced}$$




→ For the synchronization purpose it should ensure that the voltage rating on both ends of the tr. line must be same.

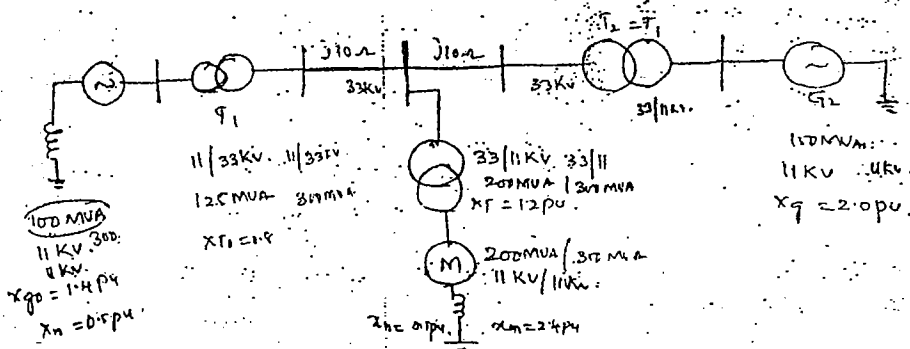(Q) For the SED shown below draw the reactance diagram & indicate the p.u values for voltages & reactance.



Choose base as 300MVA, 11KV.

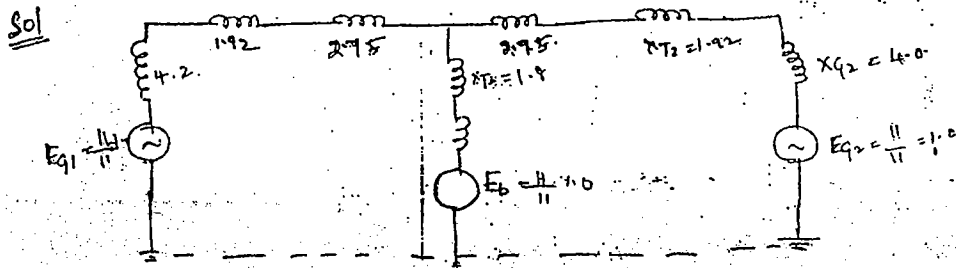


$$X_{G1} \text{ p.u. New} = 1.4 \times \frac{300}{100} \left(\frac{11}{11} \right)^2 = 4.2$$

$$X_{T1} \text{ p.u. New (p)} = 0.8 \times \frac{300}{185} \left(\frac{11}{11} \right)^2 = 1.92$$

$$X_{T2} \text{ p.u. New (s)} = 0.8 \times \left(\frac{300}{20} \right) \left(\frac{33}{33} \right)^2 = 1.92$$
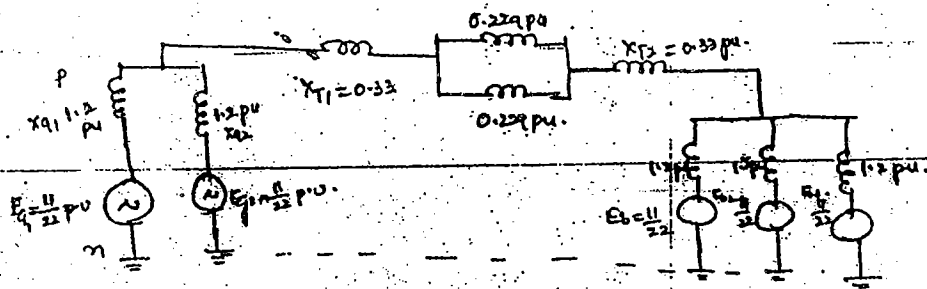
$$X_{L1} = 10 \times \left(\frac{300}{35} \right) = 2.75$$



Given

$$X_{G1} = 1.2 \text{ pu}$$

$$X_{m1} = 1.2 \text{ pu}$$

$$X_{G2} = 2.4 \text{ pu}$$

$$X_{m2} = 1.8 \text{ pu}$$

$$X_n = 0.5 \text{ pu}$$

$$X_{n2} = 2.4 \text{ pu}$$

$$T_2 = T_1$$

$$X_n = 0.5 \text{ pu}$$

$$X_{T1} = X_{T2} = 1.0$$

$$X_n = 0.2$$

$$X_{G1}(\text{new}) = X_{G1}(\text{old}) \times \left(\frac{MVA_{\text{new}}}{MVA_{\text{old}}} \right) \left(\frac{K_{\text{old}}}{K_{\text{new}}} \right)^2$$

$$= 1.2 \times \left(\frac{200}{50} \right) \left(\frac{11}{22} \right)^2$$

$$= 1.2 \text{ pu}$$

$$X_{G2}(\text{new}) = 2.4 \times \left(\frac{200}{100} \right) \left(\frac{11}{22} \right)^2$$

$$= 1.2 \text{ pu}$$

$$X_{T1}(\text{pu})_{\text{new}} = 1.0 \times \left(\frac{200}{150} \right) \left(\frac{11}{22} \right)^2 = 0.33$$

$$X_{T1}(\text{pu})_{\text{old}} = 1.0 \times \left(\frac{200}{150} \right) \left(\frac{66}{132} \right)^2 = 0.33 \text{ pu}$$

$$X_{p.u.}(1) = X_{(2)} \text{ pu} = 20 \times \left(\frac{200}{132} \right)^2 = 0.229 \text{ pu}$$

$$X_{T2}(\text{pu})_{\text{new}} = 1.0 \times \left(\frac{200}{150} \right) \left(\frac{66}{132} \right)^2 = 0.33 \text{ pu}$$

$$X_{T2}(\text{pu})_{\text{old}} = 1.0 \times \left(\frac{200}{150} \right) \left(\frac{11}{22} \right)^2 = 0.33 \text{ pu}$$

$$X_{m1}(\text{pu})_{\text{new}} = 1.2 \times \left(\frac{200}{50} \right) \left(\frac{11}{22} \right)^2 = 1.2 \text{ pu}$$

$$X_{m2}(\text{pu})_{\text{new}} = 1.8 \times \left(\frac{200}{75} \right) \left(\frac{11}{22} \right)^2 = 1.2 \text{ pu}$$

$$X_{m3}(\text{pu})_{\text{new}} = 2.4 \times \left(\frac{200}{100} \right) \left(\frac{11}{22} \right)^2 = 1.2 \text{ pu}$$

$$X_{G2} \text{ pu (new)} = 2.0 \times \frac{300}{150} \left(\frac{11}{11}\right)^2 = 4.0$$

$$X_{T2} \text{ pu (new)}_p = 0.8 \times \left(\frac{300}{125}\right) \left(\frac{11}{11}\right)^2 = 1.92$$

$$X_{T2} \text{ pu (new)}_s = 0.8 \times \left(\frac{300}{125}\right) \left(\frac{33}{33}\right)^2 = 1.92$$

$$X_{L2} = 10 \times \frac{300}{(33)^2} = 2.75$$

$$X_{T3} \text{ pu (new)}_p = 1.2 \times \frac{300}{200} \left(\frac{33}{33}\right)^2 = 1.92$$


$$X_{T3} \text{ pu (new)}_s = 1.2 \times \frac{300}{200} \left(\frac{11}{11}\right)^2 = 1.92$$

$$X_m \text{ pu (new)} = 2.4 \times \frac{300}{20} \left(\frac{11}{11}\right)^2 = 3.6$$

Gate-06 (GM)

Q) A syn. generator connected to the transmission line through a step up transformer having a rating of 13.8/138 KV, 20MVA. At the end of the tr. line the load is connected through a stepdown transformer having a rating of 138/69 KV, 10MVA. The load reactance of 0.72 pu which is evaluated based on the load side transformer ratings. For a system base of 10MVA, 69 KV then the P.U reactance in the generator ckt will be

So

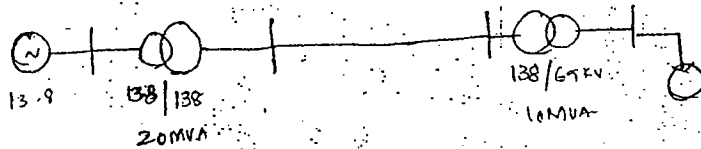


Base of 10MVA, 69 KV

$$X_{pu \text{ new}} = 0.72 \times \frac{20}{10} \left(\frac{69}{13.8}\right)^2$$

$$= 36$$

→ SYMMETRICAL COMPONENTS

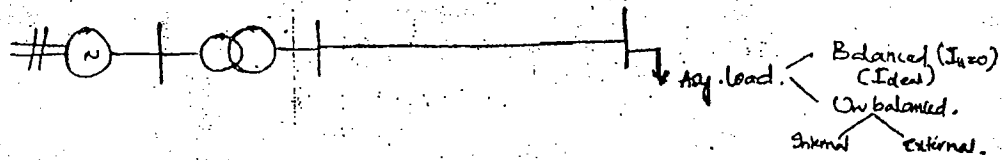


→ When the existing system is working in a balanced load condition

then the performance of the system can be evaluated by knowing the load voltage at load point for which the per phase reactance diagram along with P.U values, can be recommended.

→ There is only one m/w equation to be solved, so that the time taking will be less.

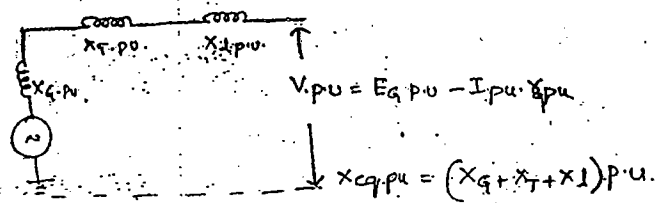→ Whenever the load is balanced, neutral is taken as reference. (Ideal case)



→ Unbalanced load
 Internal (less severe) (1- ϕ loads) $\left[\begin{matrix} I_n \leq 10\% \text{ Full load} \\ \text{current} \end{matrix} \right]$
 External (more severe) (3- ϕ loads) (faults)
 $\left(I_n > 10\% \text{ of Full load current} \right)$

→ Even though the system is working with internal unbalance but the load voltages at the load point are within the allowable regulation so that the per phase reactance diagram is sufficient along with p.u values in order to evaluate the load voltages.

→ There is only one m/w equation to be solved, so that the time taking will be less.

→ Faulty resistance by
 Substation $\leq 1 \Omega$
 Tr. line $\leq 2 \Omega$
 Distribution $\leq 5 \Omega$

Q) Alternator rated as 11 KV, 100 MVA, $X = 8 \Omega$, what is the p.u. reactance for the rating of 150 MVA, 13.2 KV

Sol

$$X_{pu} = X_r \times \left(\frac{MVA}{(KV)^2} \right)$$

$$= 8 \times \left(\frac{150}{(13.2)^2} \right)$$

$$= 6.88 \text{ pu}$$

$$X_{pu} = 8 \times \frac{100}{(11)^2}$$


$$= \frac{800}{121}$$

$$= 6.61 \rightarrow \text{old}$$


$$X_{pu_{new}} = 6.61 \times \left(\frac{150}{100} \right) \times \left(\frac{11}{13.2} \right)^2$$

$$= 6.61 \times 1.5 \times 0.69$$

$$= 6.84 \text{ pu}$$

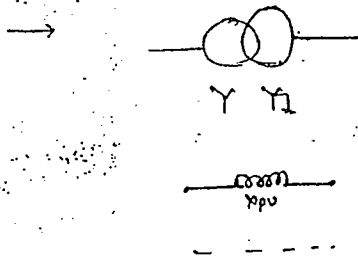


Per-phase

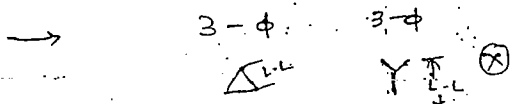


but

1-φ Y equivalent

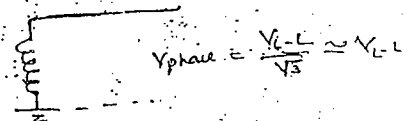


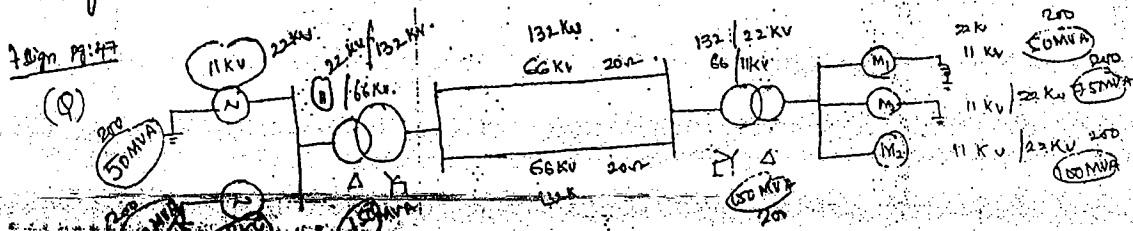Expl: The p.u. Reactance of both sides of t/t will be same if it can be assumed as the phase voltage of the single phase Y equivalent will be same as V_{LL} of the original Δ -connected system.



Choose a base of 22KV, 200 MVA, Draw the reactance diagram and indicate p.u. values.

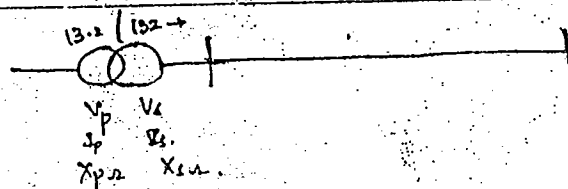The pu reactance of the transformer on both sides will be same:



$$X_p \text{ pu} = \frac{X_{p.a}}{X_b}$$

While calculating the primary reactance in pu consider, the primary ratings of the transformer as the base values.

$$X_p \text{ pu} = \frac{X_{p.a}}{X_b} = \frac{X_{p.a}}{\frac{V_p}{I_p}} = X_{p.a} \cdot \frac{I_p}{V_p} = \frac{X_{s.a}}{k^2} \cdot \frac{I_p}{V_p}$$

$$= \frac{X_{s.a}}{\frac{V_s^2}{V_p^2}} \cdot \frac{I_p}{V_p} \quad (\because k = \frac{V_s}{V_p})$$

$$= X_{s.a} \cdot \frac{V_p^2}{V_s^2} \cdot \frac{I_p}{V_p}$$

$$= X_{s.a} \cdot \frac{V_p I_p}{V_s^2}$$

$$= X_{s.a} \cdot \frac{V_p I_p}{V_s^2}$$

(\because The product of $V \cdot I$ on either side of a t/f is same)

$$= X_{s.a} \cdot \frac{I_s}{V_s}$$

$$= \frac{X_{s.a}}{\frac{V_s}{I_s}}$$




$$= \frac{X_{s.a}}{X_b} = X_s \text{ pu}$$

\rightarrow In case of t/f, the base voltage of the system changes where as the capacity of the t/f is same on both sides.




\rightarrow The t/f rating can be assumed as the transformer capacity and also the line side voltage of the transformer.



$$X_{2eq} = [X_d''(G) + (X_1)T_1] \parallel [X_{L1} + (X_1)T_2 + X_d''(M)]$$

→ Negative Sequence Networks

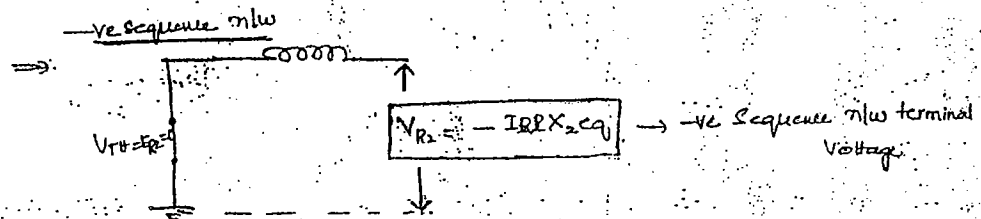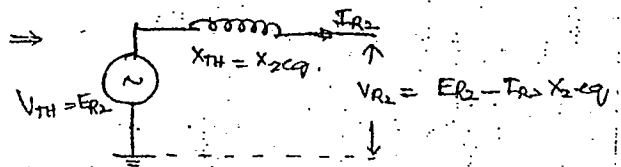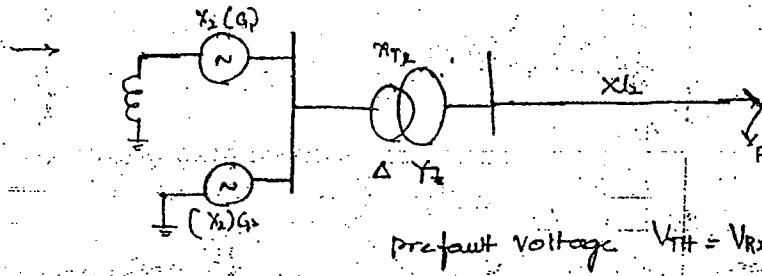

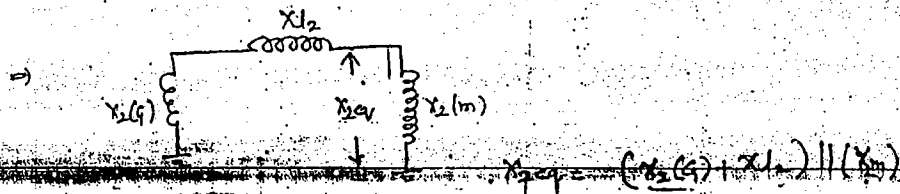
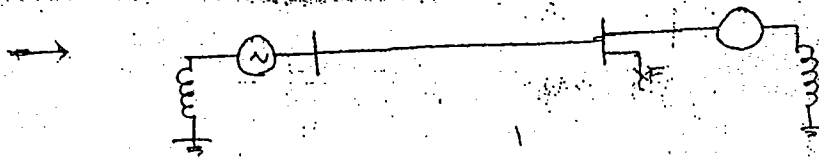
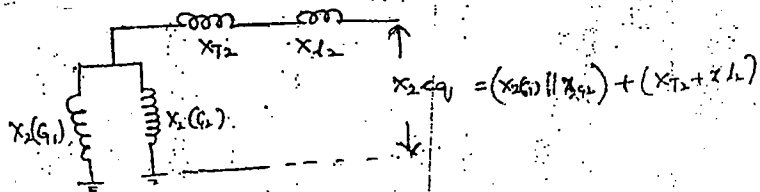
Use the Simulation diagram to calculate X_{2eq} .



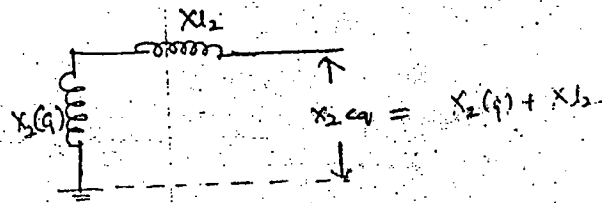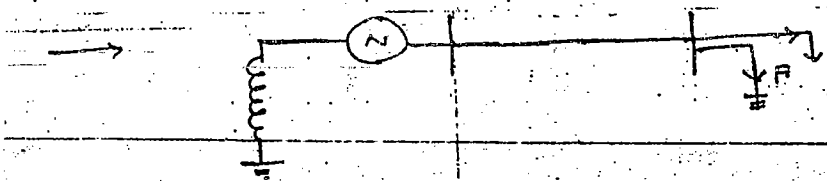

→ The -ve sequence n/w is similar to that of +ve sequence n/w except there is no prefault voltage.

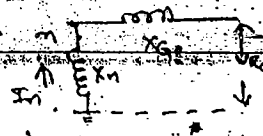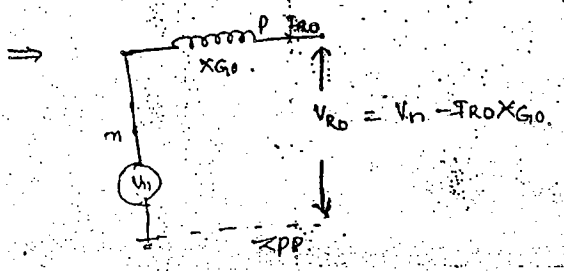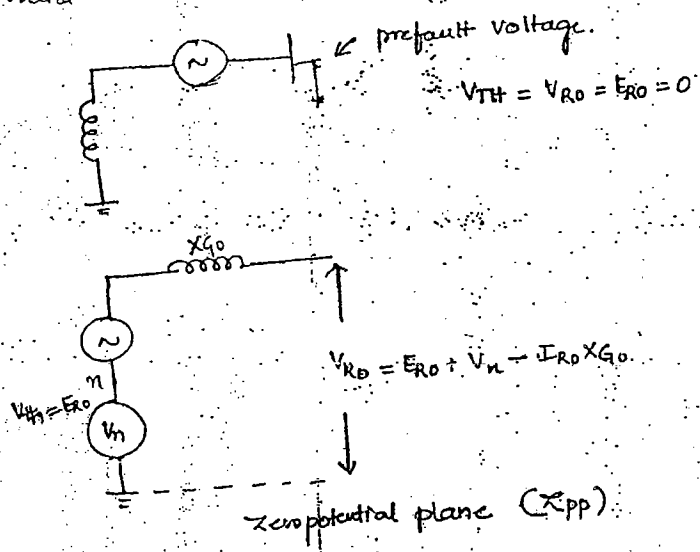→ Zero Sequence Network: While drawing the zero sequence n/w include the neutral grounding effect because the reference is the ground.



$$I_n = -3I_{f0}$$

$$V_n = -V_c$$

$$I_n = 3I_{f0}$$


$$V_n = +V_c$$

(possible only under identical balance condition)

∴ Under fault condition.

$$I_n = -3I_{f0}$$

$$V_{R0} = -3I_{f0}X_n - I_{f0}X_{G0}$$

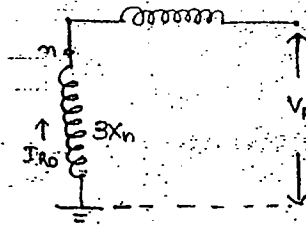

$$V_{R0} = -3I_{f0}X_n - I_{f0}X_{G0}$$

$$= -I_{f0}(3X_n + X_{G0})$$


$$= -I_{f0}X_{ocq}$$

To ensure the current through the series is same i.e. I_{f0}

$$X_{ocq} = X_{G0} + 3X_n$$




$$V_{R0} = -I_{f0} \cdot X_{ocq} \quad (\text{Zero sequence } \eta/\omega \text{ terminal voltage})$$
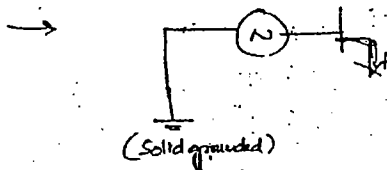
$$\begin{bmatrix} V_{R0} \\ V_{R1} \\ V_{R2} \end{bmatrix} = \begin{bmatrix} 0 \\ E_{R1} \\ 0 \end{bmatrix} - \begin{bmatrix} X_{ocq} & 0 & 0 \\ 0 & X_{ocq} & 0 \\ 0 & 0 & X_{ocq} \end{bmatrix} \begin{bmatrix} I_{R0} \\ I_{R1} \\ I_{R2} \end{bmatrix}$$




$$X_{ocq} = X_{G0} + 3X_n$$

$$= X_{G0} + 0 = X_{G0}$$

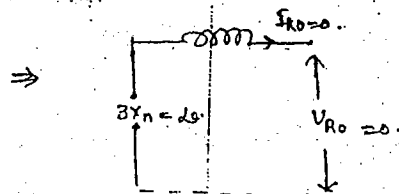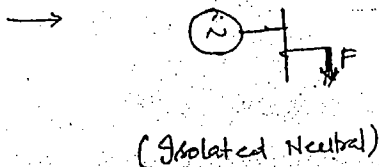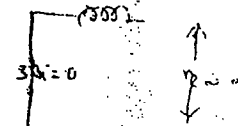


$$X_{ocq} = X_{G0} + \infty = \infty$$

→ If the Alternator is Delta Connected

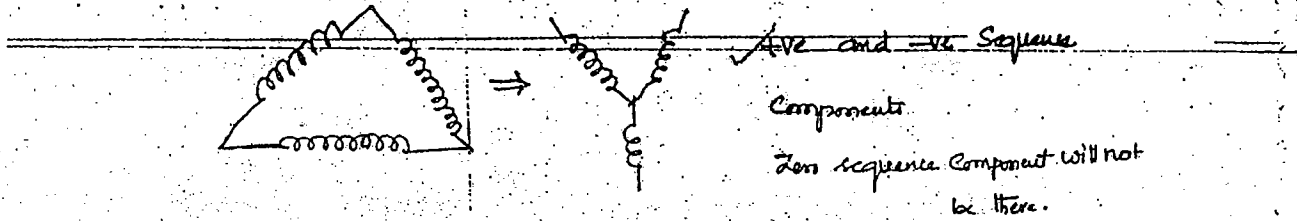


17/02/2010

→ ZERO SEQUENCE NETWORKS OF TRANSFORMER:

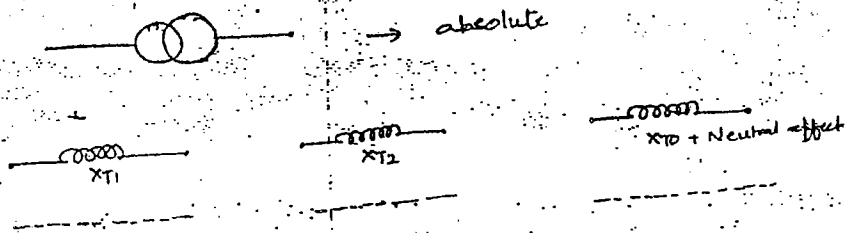

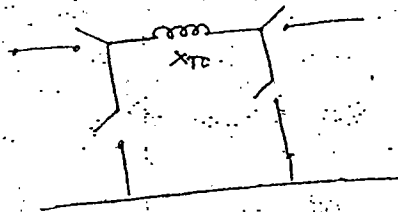
→ To include the neutral effect represent the X_0 as a mechanical equivalent i.e. series parallel switches






- If the winding is Y on either side → operate series switch.
- If the winding is Δ → operate the parallel switch
- There is Y -related neutral — there is no closed path — then
 ✓ open the switch. ($3X_n = \infty$)
- Y → Solid neutral → Close the switch. ($3X_n = 0$)
- Y → Radiane neutral → Close the switch ($3X_n$)
- Δ → Closed winding → Close the parallel switch ($3X_n = \infty$)

7/4 Connection








Zero sequence x_{0eq}

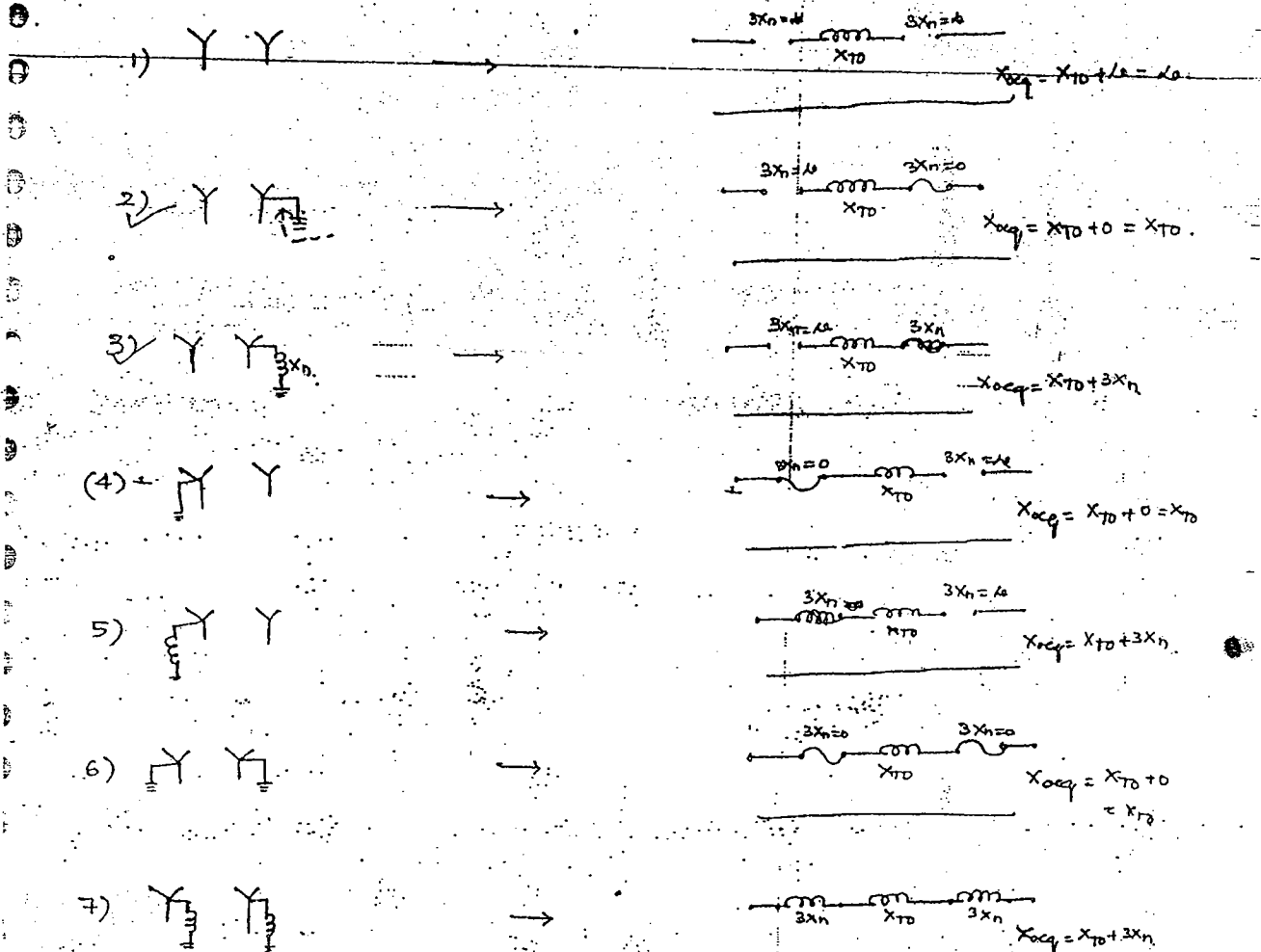


② & ③ are practical cases.

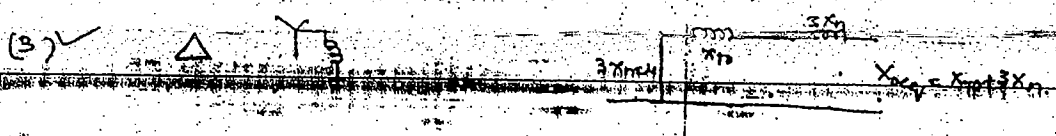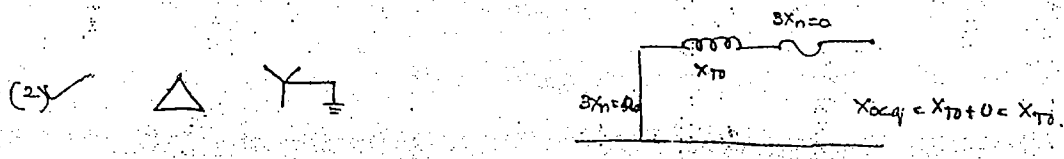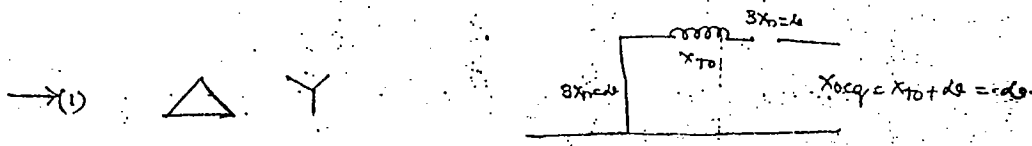

(primary & secondary are same)

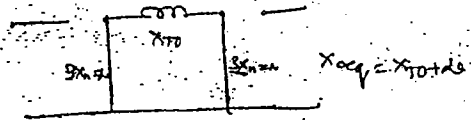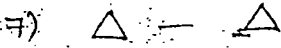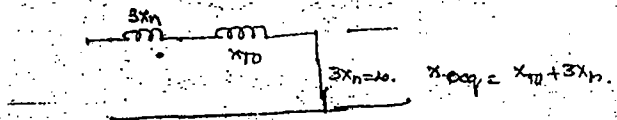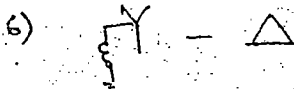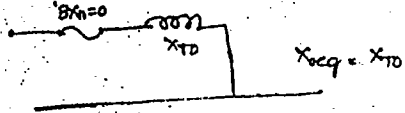
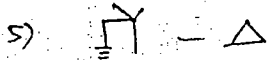
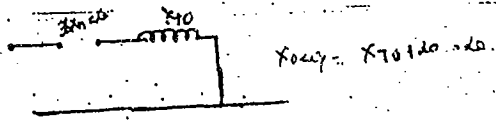


(Q)

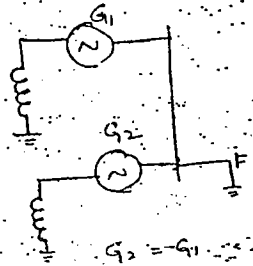


$G_2 = -G_1$
 $X_{d''} = 0.2$
 $X_2 = 0.2$
 $X_{eq} = 0.1$
 $X_n = 0.05$

Sol

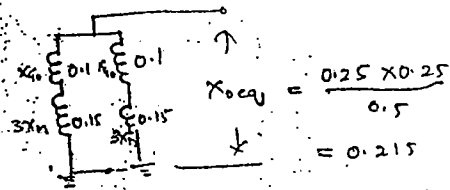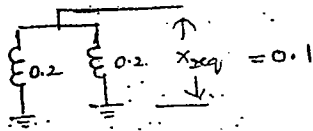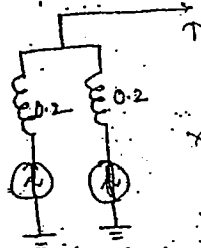


(Q)





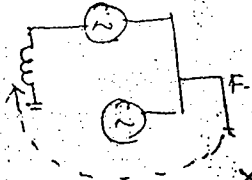



$X_{1eq} = 0.1$

$X_{2eq} = 0.1$





$X_{ocq} = 0.25$





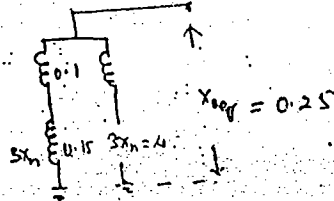


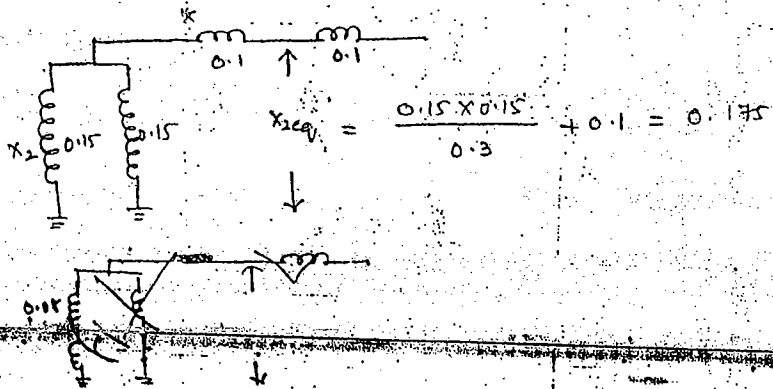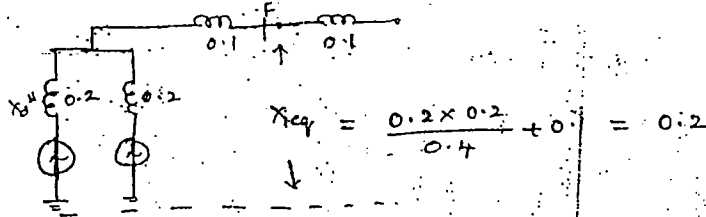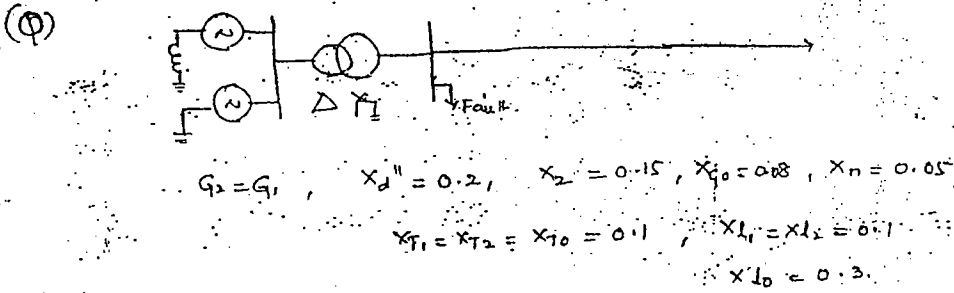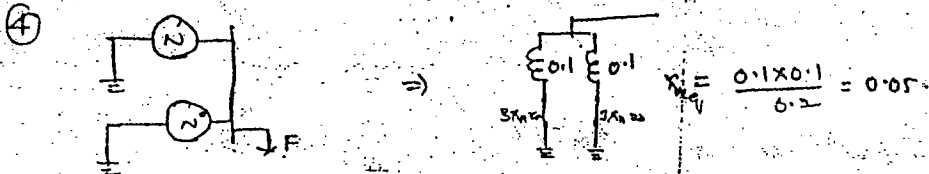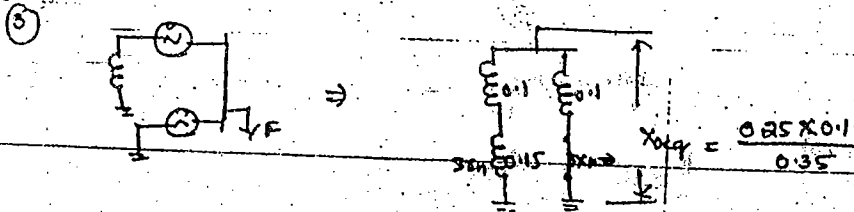


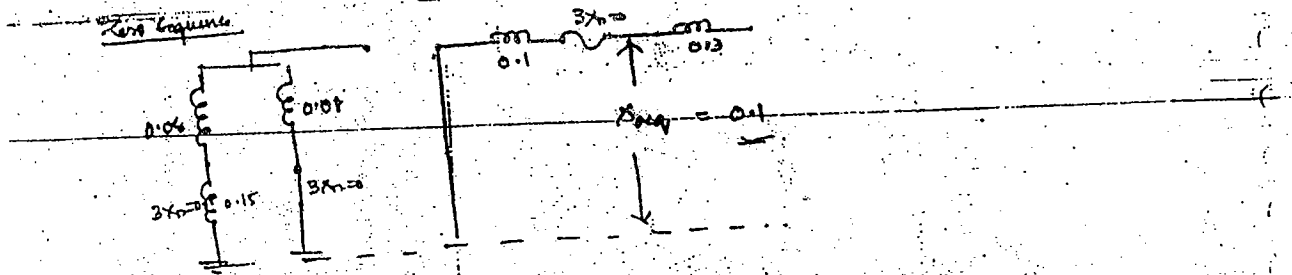


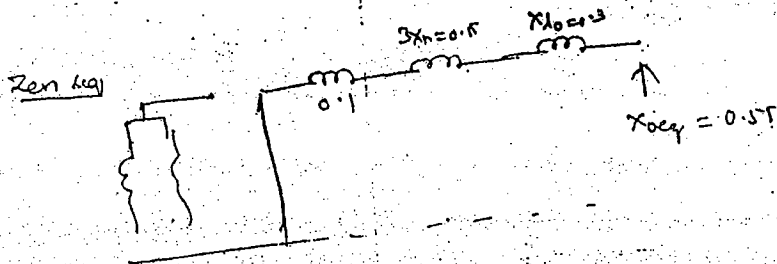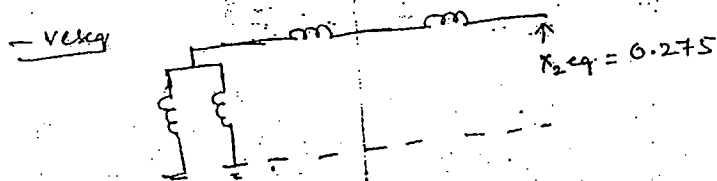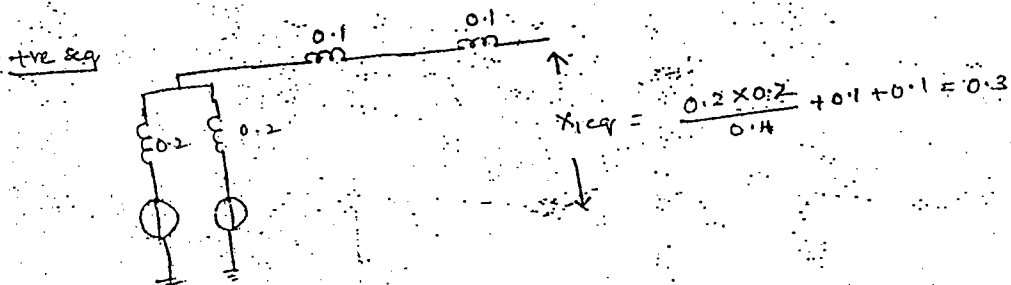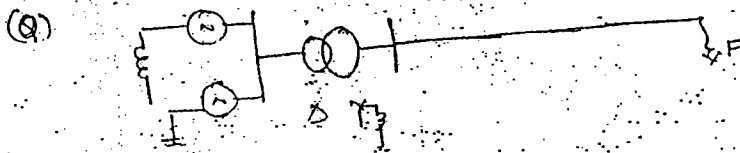of $3X_p = 0.15$ in above calc.
 $\therefore X_{req} = 0.1 + 0.15 = 0.25$




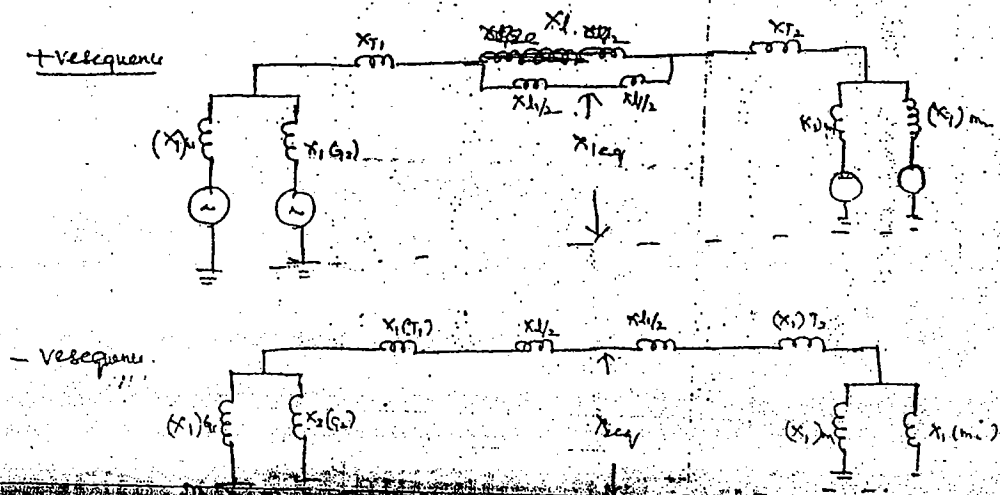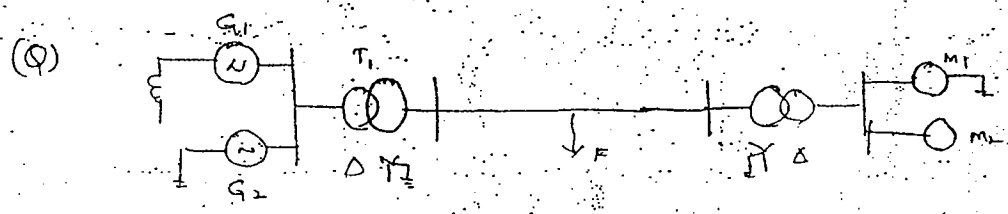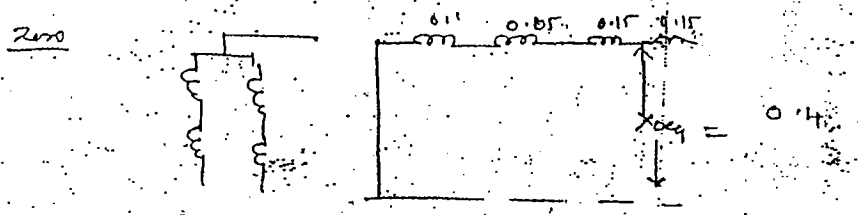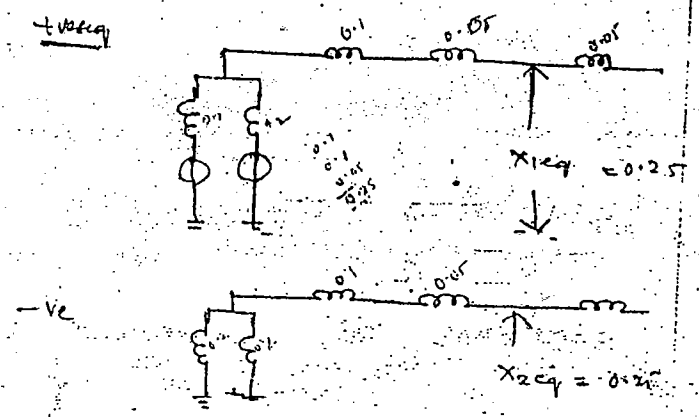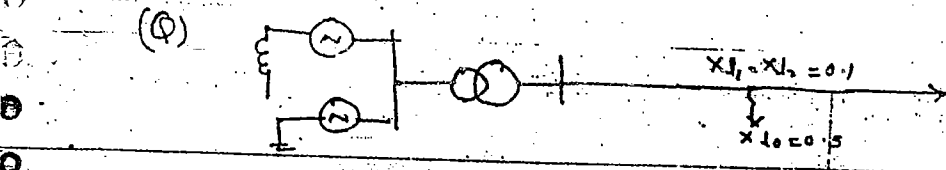


Zur Seite 2

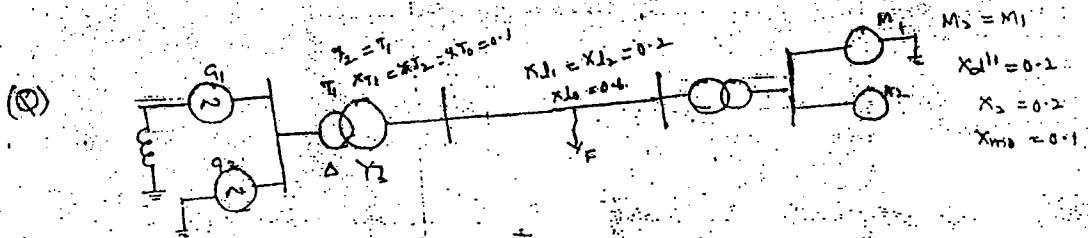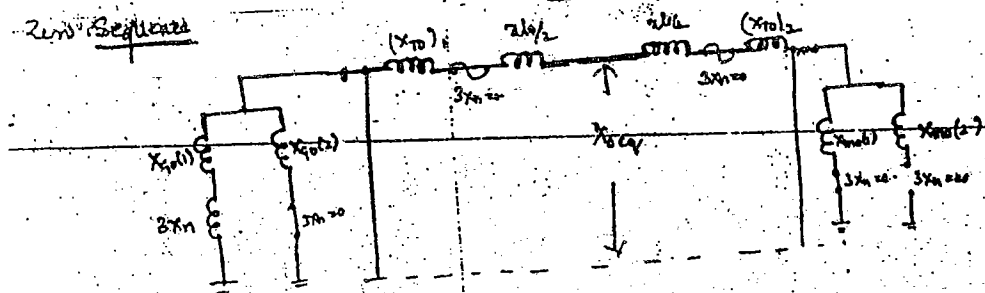


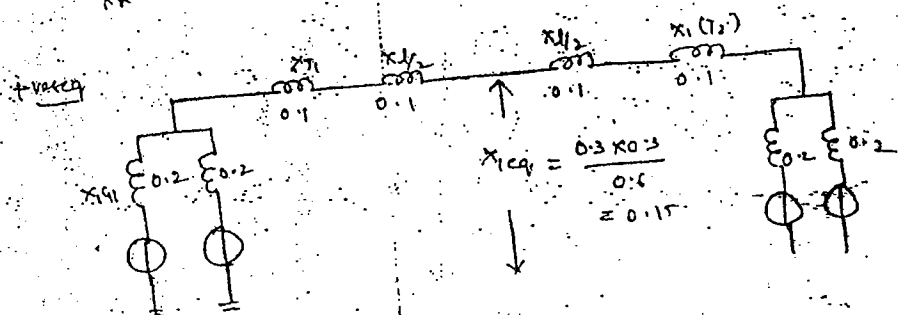$G_2 = G_1$
 $X_d'' = 0.2$
 $X_2 = 0.2$
 $X_q = 0.1$
 $X_n = 0.05$




-ve seq
 $X_{2eq} = 0.15$

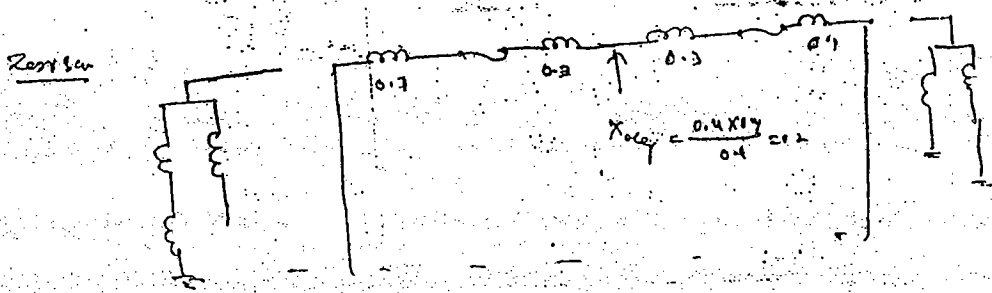

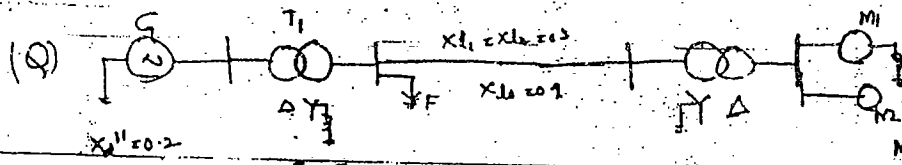


$X_{11} = 0.2$
 $X_2 = 0.15$
 $X_{q0} = 0.08$
 $T_2 = T_1$
 $X_{T1} = X_{T2} = X_{T0} = 0.1$
 $X_n = 0.05$
 $M_1 = M_2 = 9$
 $X_{d1} = 0.2$
 $X_2 = 0.15$
 $X_{m1} = 0.08$
 $X_n = 0.05$


Sol.

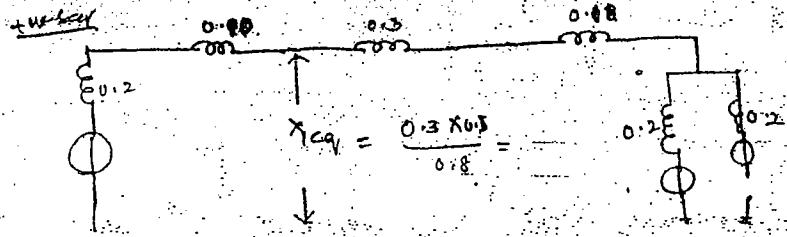

Zero seq

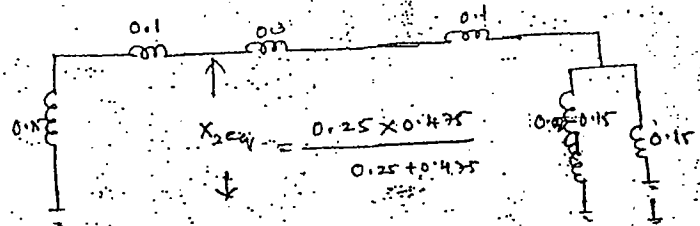

Zero seq

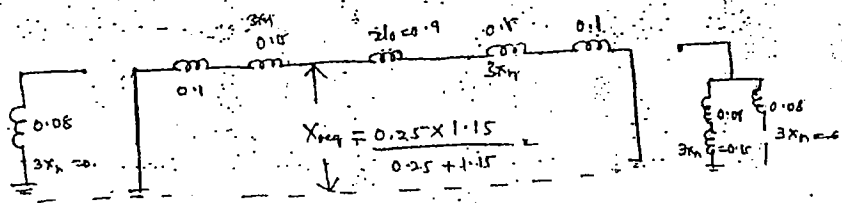

→ RELATIONS AMONG THE SEQUENCE REACTANCES


	+ve Sequence Sub-T (1 st cycle)	-ve Sequence Sub-T	Zero Sequence Sub-T
1) Turbo gen	X_d''	$X_d'' = X_d''$ (Uniform air gap flux)	$X_{G0} < X_d''$
2) Salient pole	X_d''	$X_2 < X_d''$ (Non-uniform air gap flux)	$X_{G0} < X_d''$
3) Transfr	X_{T1}	$X_{T2} = X_{T1}$	$X_{T0} = X_{T1}$
4) Tr. line	X_{L1}	$X_{L2} = X_{L1}$	* $X_{L0} = 3X_{L1}$

} Leakage reactance

→ X_d'' (Turbo) > X_d'' (Salient)
 $I_{sc} \downarrow$ $I_{sc} \uparrow$

→ The tft and tr. line are the static devices and they are made up of bilateral elements so that the conductivity will be same in both the directions hence the negative sequence reactances are equal to +ve sequence reactance.

→ Salient pole Machine:

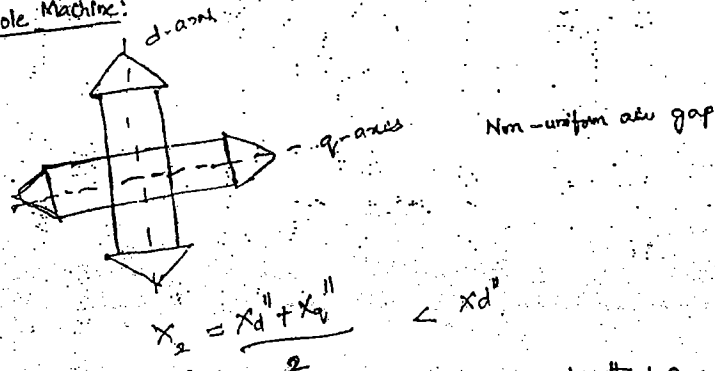


→ In case of salient pole machine the currents that are induced due to negative sequence component flux in the stator wdg will be alternatively maxima in the direct axis and in the quadrature axis.

Hence the -ve sequence reactance is the average reactance of both the axes.

$$X_2 = \frac{X_d'' + X_q''}{2} < X_d''$$

→ In case of turbo alternator there are no quadrature axis hence



$$X_2 = X_d''$$

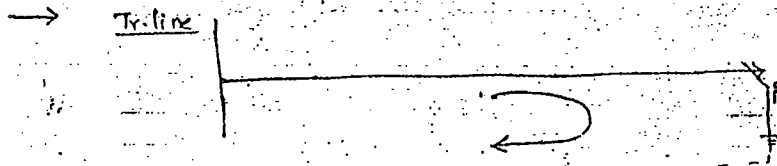

Include Earth(0) ground effect

$$2.5 X_{01} = 3.5 X_{01}$$


$$X_{00} = 3 X_{01}$$

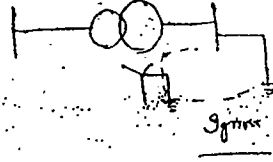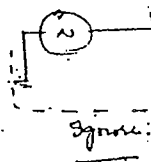

* X_{00} → The zero sequence component exists if the fault is associated with the ground. The fault current is expected to flow from the fault point through the ground and enters into the system from neutral grounding. In case of tr. line include the earth effect while calculating the zero sequence reactance offered and in case of alternator as well as t/f ignore the earth effect. The impedance (or) Reactance offered by the earth will change from time to time due to dissimilar soils throughout the length and different moisture levels. Hence the total zero sequence reactance to the tr. line is a variable value due to inclusion of the earth and it can vary $2.5 X_1$ to $3.5 X_1$.

average of this is "3X₁" * * *

(or)

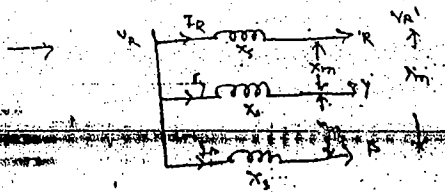

$$\begin{aligned} X_{1eq} &= X_2 - X_m \\ X_{2eq} &= X_2 - X_m \\ X_{0eq} &= X_2 + 2X_m \end{aligned}$$

$$\begin{aligned} Z_{1eq} &= Z_s - Z_m \\ Z_{2eq} &= Z_s - Z_m \\ Z_{0eq} &= Z_s + 2Z_m \end{aligned}$$

⊙ Before fault

$$V_R = V_R' + I_R X_s + I_y X_m + I_B X_m$$


$$= V_R' + I_R X_s + K^2 I_R X_m + K I_R X_m$$

$$= V_R' + I_R X_s + I_R X_m (K^2 + K)$$

$$= V_R' + I_R X_s + I_R X_m (-1)$$

$$V_R = V_R' + I_R (X_s - X_m) \quad (\text{Steady state})$$

⊙ fault occurs!

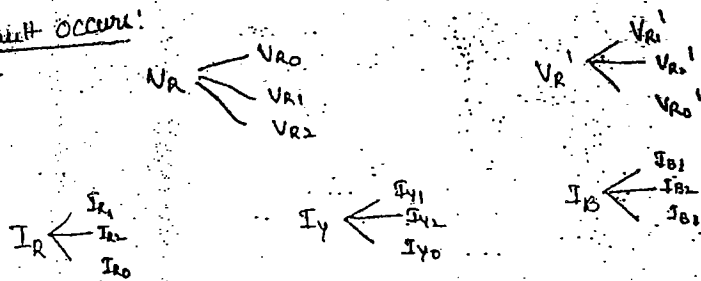

$$V_{R1} = V_{R1}' + I_{R1} X_s + I_{Y1} X_m + I_{B1} X_m$$

$$= V_{R1}' + I_{R1} X_s + K^2 I_{R1} X_m + K I_{R1} X_m$$

$$= V_{R1}' + I_{R1} X_s + I_{R1} X_m (K^2 + K)$$

$$= V_{R1}' + I_{R1} X_s + I_{R1} X_m (-1)$$

$$= V_{R1}' + I_{R1} \underbrace{(X_s - X_m)}_{X_{1eq}}$$

$$V_{R2} = V_{R2}' + I_{R2} X_s + I_{Y2} X_m + I_{B2} X_m$$

$$= V_{R2}' + I_{R2} X_s + K^2 I_{R2} X_m + K I_{R2} X_m$$


$$= V_{R2}' + I_{R2} X_s + I_{R2} X_m (K^2 + K)$$

$$= V_{R2}' + I_{R2} X_s + I_{R2} X_m (-1)$$

$$= V_{R2}' + I_{R2} \underbrace{(X_s - X_m)}_{X_{2eq}}$$

$$\begin{aligned}
 V_{R0} &= V_{R0}^i + I_{R0} X_s + I_{Y0} X_m + I_{B0} X_m \\
 &= V_{R0}^i + I_{R0} X_s + I_{R0} X_m + I_{R0} X_m \\
 &= V_{R0}^i + I_{R0} \underbrace{(X_s + 2X_m)}_{X_{0q}}
 \end{aligned}$$

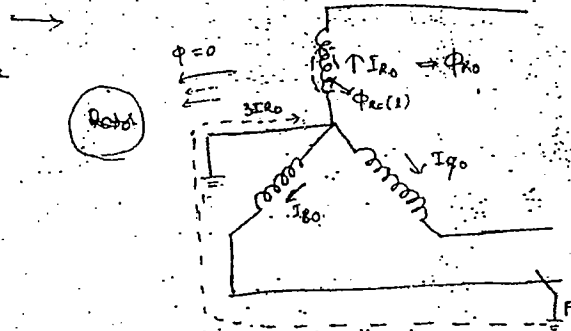→ In case of transformer, $X_{T0} = X_{T1}$ ($X_{m0} = +ve X$) because it is a static device and also there is no ground effect. hence



Expt → The field produced by the zero sequence component is having zero phase displacement w.r.t. ground and 120° phase displacement in the space w.r.t. air gap. So the net zero sequence flux which can be linked with rotor wdg. will be zero and there is no effect of zero sequence component on the rotor provided that if the stator's wdg. is a symmetrical wdg. (i.e. completely distributed or full length wdg.) However the alternator designed with an asymmetrical wdg. i.e. short pitch wdg.

In case of asymmetrical wdg. there will be certain leakage flux out of the total zero sequence flux produced and the reactance offered to the leakage flux is treated as zero sequence flux which is less than the +ve sequence reactance.


18/2/2010

FAULT ANALYSIS

- 1) In any type of SC faults the +ve sequence subtransient current exists
- 2) If the fault is associated with ground then it will be treated as unbalanced fault. The fault current will be expressed in terms of zero sequence currents however there should be a relation b/w the zero sequence current and the +ve sequence current.
- 3) If the fault is not associated with ground but unbalance then the fault current will be expressed in terms of -ve sequence current. There should be a relation b/w negative sequence current and also the +ve sequence current.
- 4) If the fault is not associated with ground but a balanced fault then the fault current is same as +ve sequence current.

1) Line to Ground fault (L-G): Consider alternator working at no load, rated voltage solid neutral $\Rightarrow I_f$ is high, and solid fault (phase to ground without reactor)

$(X_f = 0)$

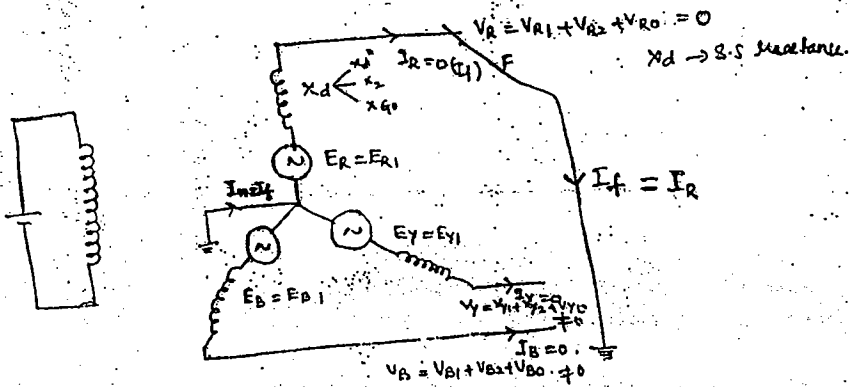

During fault

$$I_f = I_a$$

$$V_r = 0, \quad I_y = I_b = 0$$

Using the Symmetrical Components

$$I_{R0} = \frac{1}{3} (I_{R1} + I_{R2} + I_{R3}) = I_{R/3}$$

$$I_{R1} = \frac{1}{3} (I_{R1} + KI_{R2} + K^2 I_{R3}) = I_{R/3}$$

$$I_{R2} = \frac{1}{3} (I_{R1} + K^2 I_{R2} + KI_{R3}) = I_{R/3}$$

$$\therefore I_{R0} = I_{R1} = I_{R2} = \frac{I_R}{3}$$

* In L-G fault all the sequence currents are same

$$I_R = I_f = 3I_{R0} = 3I_{R1} \text{ p.u. (r.m.s.)}$$

Actual fault current, $I_f \text{ pu} = \frac{I_f \text{ (actual)}}{I_{\text{base}}}$

$$I_f \text{ (actual)} = I_f \text{ (p.u.)} \cdot I_{\text{base}} \text{ A (or) KA}$$

In a 3- ϕ system

$$S = \sqrt{3} V_L I_L$$

$$I_L = \frac{S}{\sqrt{3} V_L} \quad \text{For } Y\text{-system}$$

$$I_{\text{phase}} = I_L = \frac{S}{\sqrt{3} V_L} = I_{\text{base}}$$

→ Calculation of I_{R1} :

$$V_R = V_{R1} + V_{R2} + V_{R0} = 0$$

$$= E_{R1} - I_{R1} X_{1eq} - I_{R2} X_{2eq} - I_{R0} X_{0eq} = 0$$

$$E_{R1} = I_{R1} (X_{1eq} + X_{2eq} + X_{0eq}) = 0$$


$$I_{R1} = \frac{E_{R1}}{X_{1eq} + X_{2eq} + X_{0eq}} \text{ p.u.}$$

$$I_f = \frac{3 \cdot E_{R1}}{X_{1eq} + X_{2eq} + X_{0eq}} \text{ p.u.}$$


Where

$$X_{1eq} = X_1, X_{2eq} = X_2, X_{0eq} = X_0$$

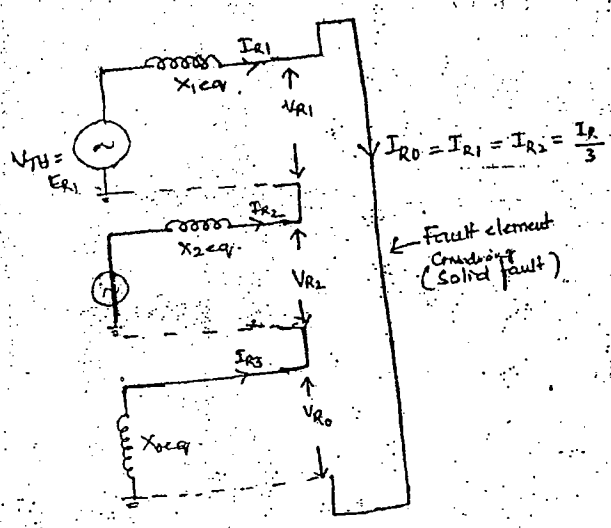* If the fault is associated with the ground so that the three sequence components are excited. The associated sequence networks are connected in series because the sequence currents are same.



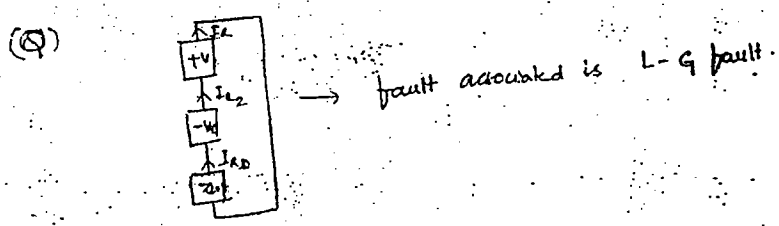* The theorem equivalent have to be closed by the fault element.



⇒ Potential of the Neutral during fault:

$$\begin{aligned}
 V_n &= I_n X_n \\
 &= I_f X_n \\
 &= 3I_{R0} X_n \quad (\text{ie } I_{R0} \cdot 3X_n)
 \end{aligned}$$

1) $V_n = 0$ (if it is solid neutral) since $3X_n = 0$

2) $V_n = 3I_{R0} X_n$ (Reactance neutral)

$$V_n(\text{actual}) = V_n - p.u \times V_{base}$$

⇒ Calculation of s.c. MVA of the fault:

$$\frac{V_b}{X_{pu}} = \frac{F}{V_b}$$

In fault condition

$$X_d'' \text{ p.u.} = X_d'' \cdot \frac{I_b}{V_b}$$

$$X_d'' \text{ p.u.} = \frac{I_b}{\frac{V_b}{X_d''}} = \frac{I_b}{I_{sc}} \rightarrow \text{s.c. Current}$$

(X_{d''})⁻¹ → s.c. reactance in Ohm.

(Q) The alternator is having p.u. (or) s.c. reactance = 0.2, what is s.c. current

$$I_{sc} = \frac{I_b}{X_d''} = \frac{1.0}{0.2} = 5 \text{ p.u.}$$

(Q) of the

$$X_d'' \text{ p.u.} = \frac{I_b}{I_{sc}} \times \frac{3V_b}{3V_b} = \frac{\text{Base MVA}}{\text{s.c. MVA}}$$

$$\Rightarrow \boxed{\text{s.c. MVA} = \frac{\text{Base MVA}}{X_d'' \text{ p.u.}} \text{ P}}$$

For L-G fault

$$\boxed{\text{s.c. MVA} = \frac{\text{Base MVA}}{X_{1eq} + X_{2eq} + X_{0eq}} \text{ P.u.}}$$

→ If the neutral is grounded with a reactance of "X_n" then,

$$X_{1eq} = X_d''$$

$$X_{2eq} = X_2$$

$$X_{0eq} = X_{G0} + 3X_n$$

$$\boxed{I_f = \frac{3 \cdot E_{R1}}{X_{1eq} + X_{2eq} + X_{G0} + 3X_n}}$$

→ If the neutral is isolated, then

$$X_{1eq} = X_d'', \quad X_{2eq} = X_2, \quad X_{0eq} = X_{G0} + \infty = \infty$$

$$\boxed{\frac{3 \cdot E_{R1}}{X_{1eq} + X_{2eq} + \infty} = 0 \text{ p.u.}}$$

$$\left. \begin{matrix} X_{1eq} + X_{2eq} \\ 3X_n = \infty \end{matrix} \right\} X_{G0} + \infty = \infty (X_{0eq})$$


→ If the alternator is connected to long tr. lines with isolated neutral

then the fault current is ZERO. However, the voltage in the healthy phases will become " $\sqrt{3}$ " times of the rated voltage which is known as "arching grounds" = $(\sqrt{3} \times V_{rated})$. The result of the arching grounds will make the failure of insulation of healthy phase called "FLASH OVER OF INSULATION".


→ If the alternator is connected to solid then there are no arching grounds because the voltages of healthy phases is same as that of rated voltage.

→ In a practical case the alternators are normally connected with long lines and it requires to eliminate the arching grounds. In order to eliminate the arching grounds the neutral of the alternator is connected to the ground through a COIL and the type of grounding is called Resonant grounding. The value of inductance of the coil,
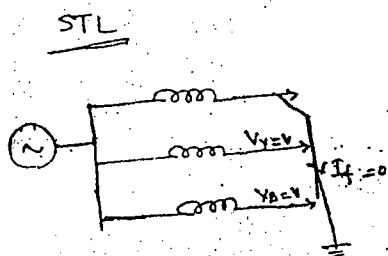
$$L = \frac{1}{3\omega^2 C} \quad (\text{Peterson Coil})$$



No. Shunt Capacitance.

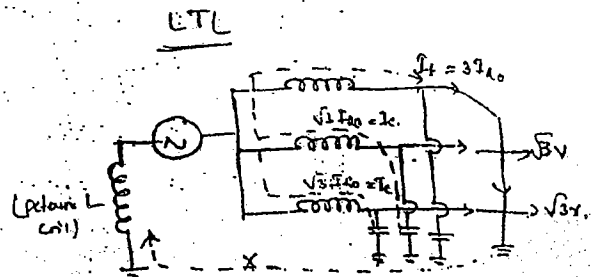

Shunt capacitance effect.

Hence Shunt capacitance is responsible for "arching grounds".
Hence the shunt capacitance effect is nullified by connecting a

Peter coil as shown in fig (blackpu) and the charging currents are compensated.


$$I_n = 3I_{R0}$$

$$\frac{X_L}{X_C} = 3 \frac{X_L}{X_C}$$

$$\frac{1}{\omega L} = 3 \times \frac{1}{\omega C}$$


$$\Rightarrow L = \frac{1}{3\omega^2 C}$$

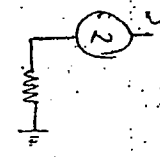→ Generally alternators are connected with resistance grounding in all practical cases for the purpose of stability.




$$Z_{ocq} = 3R_n + jX_{q0}$$

or

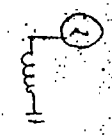

$$X_{ocq} = X_{q0} + 3X_n$$

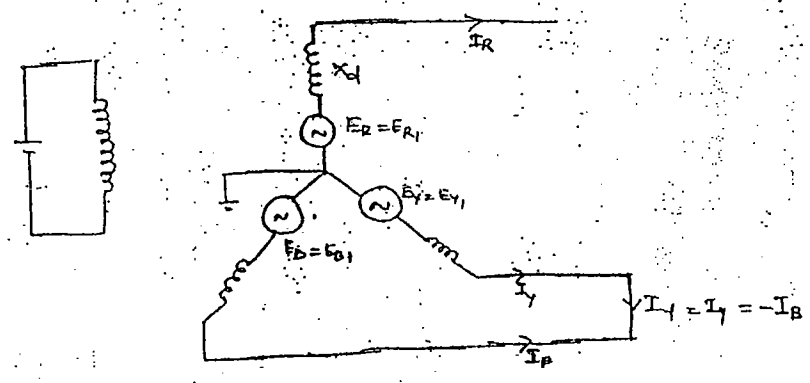(2) Line-to-Line Fault (L-L fault): Consider alternator with no load, rated voltage, solid neutral & solid fault.



During fault

$$I_f = I_y = -I_B$$

$$I_R = 0, \quad I_y + I_B = 0$$

$$V_y = V_B$$

} Unbalance Condition.

Retaining by using Symmetrical Components

$$I_{R0} = \frac{1}{3} [I_{R1} + I_{R2} + I_{R3}] = 0$$

$$I_{R1} = \frac{1}{3} [I_{R1} + K I_{R2} + K^2 I_{R3}] = \frac{I_{R2}}{3} [K - K^2]$$

$$I_{R2} = \frac{1}{3} [I_{R1} + K^2 I_{R2} + K I_{R3}] = \frac{I_{R1}}{3} [K^2 - K]$$

$$\Rightarrow I_{R2} = -\frac{I_{R1}}{3} [K - K^2] = -I_{R1} \rightarrow \textcircled{1}$$

$$V_Y = V_B$$


$$V_{Y0} + V_{Y1} + V_{Y2} = V_{B0} + V_{B1} + V_{B2}$$

$$K^2 V_{R1} + K V_{R2} = K V_{R1} + K^2 V_{R2}$$


$$(K^2 - K) V_{R1} = (K^2 - K) V_{R2}$$

$$V_{R1} = V_{R2} \rightarrow \textcircled{2}$$

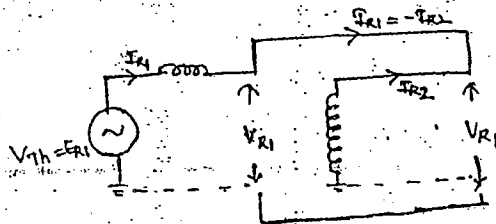The fault is not associated with ground but unbalance. So it consists of +ve and -ve sequence components; the associated sequence mlw are connected in anti parallel according to eq (1) & (2)



Ex:

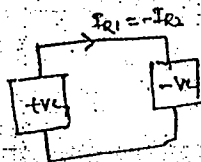

From eq (2)

$$V_{R1} = V_{R2}$$

$$E_{R1} - I_{R1} X_{1eq} = -I_{R2} X_{2eq}$$

$$E_{R1} = I_{R1} X_{1eq} + I_{R1} X_{2eq}$$

$$I_{R1} = \frac{E_{R1}}{X_{1eq} + X_{2eq}} \quad \text{P.U.} \rightarrow \text{+ve sequence Sub-T Current}$$

$$I_f = I_y = I_{y0} + I_{y1} + I_{y2}$$

$$= 0 + k I_{R1} + k I_{R2}$$

$$I_f = I_y = (k^2 - k) I_{R1}$$

$$I_f = I_y = \left[(-0.5 - j0.8667) - (-0.5 + j0.8667) \right] I_{R1}$$

$$I_f = I_y = -j1.732 I_{R1} = j1.732 I_{R2}$$

$$I_f = \sqrt{3} I_{R1} \quad \left(\begin{array}{l} \text{90}^\circ \\ \text{-ve sign is neglected} \end{array} \right)$$

→ In case of L-G fault the unbalanced line current is 3-times the balanced phase current where as in L-L fault the unbalanced line current is $\sqrt{3}$ times the balanced phase current

$$I_{f \text{ actual}} = I_f \cdot \text{p.u.} \times I_{\text{base}} \quad \text{A or KA}$$

$$\text{S.C. MVA} = \frac{\text{Base MVA}}{X_{1eq} + X_{2eq}}$$


→ potential of the Neutral during fault

$$V_n = I_n X_n = 0 \rightarrow \text{For Solid Neutral \& also reactance Neutral}$$

of the neutral will be ZERO even in case of Reactance Neutral.


→ In case of Reactance neutral (or) Isolated Neutral, the fault current remains same because the +ve sequence and -ve sequence m/f's doesn't depends on neutral grounding.

(Repeated)
Q) W.P

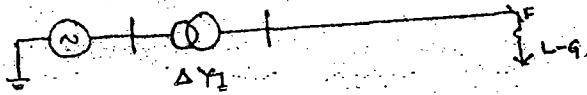

Ans: If of the line-ground fault is referred towards the alternator side of the transformer then it will be treated as L-L fault.

3) Line to Line to Ground Fault:

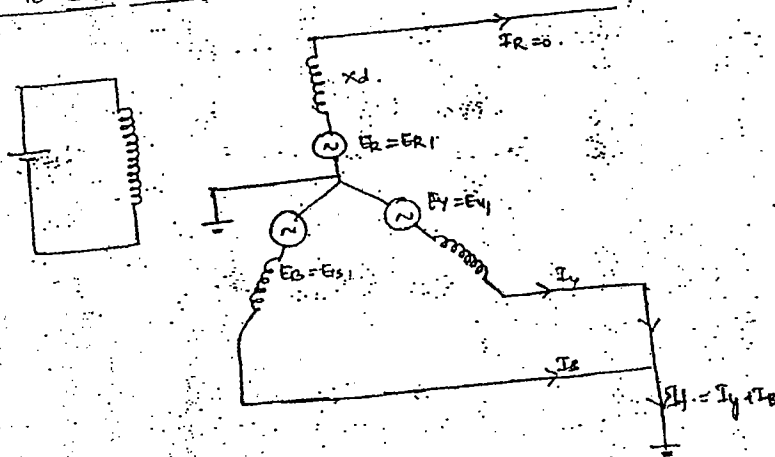

During fault

$$\left. \begin{aligned} I_f &= I_y + I_B \\ I_R &= 0 \\ V_Y &= V_B = 0 \end{aligned} \right\}$$

Unbalanced.

$$I_R = I_{R0} + I_{R1} + I_{R2} = 0$$

$$I_{R0} = -I_{R1} - I_{R2}$$


Resolving by using Symmetrical Components

$$V_{R0} = \frac{1}{3} [V_R + V_Y + V_B] = \frac{V_R}{3}$$

$$V_{R1} = \frac{1}{3} [V_R + K V_Y + K^2 V_B] = \frac{V_R}{3}$$

$$V_{R2} = \frac{1}{3} [V_R + K^2 V_Y + K V_B] = \frac{V_R}{3}$$

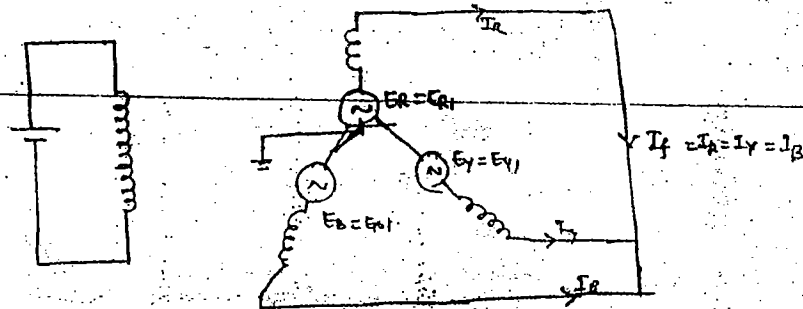→ Line to Line to Line Fault - (Balanced Fault) Symmetrical Fault:



During Fault:

Fault Current $I_f = I_R = I_Y = I_B$

But $I_R + I_Y + I_B = 0$

$V_R = V_Y = V_B$


Balanced Fault.

Resolving by using Symmetrical Components:

$I_{R0} = \frac{1}{3} [I_R + I_Y + I_B] = 0$

$I_{R1} = \frac{1}{3} [I_R + K I_Y + K^2 I_B] = I_R$

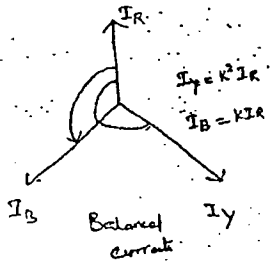$I_{R2} = \frac{1}{3} [I_R + K^2 I_Y + K I_B] = 0$



$I_{R2} = \frac{1}{3} [I_R + K^2 K I_R + K K I_R] = 0$

$= \frac{1}{3} [I_R + K^2 K I_R + K^2 I_R] = 0$

$= \frac{1}{3} I_R [1 + K^2 + K] = 0$

$\Rightarrow I_{R2} = 0$

$\Rightarrow I_f = I_R = I_{R1}$ P.U.

$I_{R0} = 0, V_{R0} = 0$

$I_{R2} = 0, V_{R2} = 0$

$V_{R1} = \frac{1}{3} [V_R + K V_Y + K^2 V_B]$

$= \frac{V_R}{3} [1 + K + K^2]$

$= 0$

$\Rightarrow V_{R1} = 0$

\rightarrow In a 3- ϕ S.C. Fault the +ve sequence n/w terminal voltage is ZERO i.e. $V_{R1} = 0$

$$E_{R1} - I_{R1} X_{1eq} = 0$$

$$I_{R1} = \frac{E_{R1}}{X_{1eq}} \text{ p.u.} \rightarrow \text{+ve Sequence Subtransient Current}$$


$$I_f = I_{R1} = \frac{E_{R1}}{X_{1eq}} \text{ p.u.}$$

$$I_f (\text{actual}) = I_f \text{ p.u.} \cdot I_{\text{base}}$$

$$\text{S.C. MVA} = \frac{\text{Base MVA}}{X_{1eq}}$$


Potential of the Neutral during fault
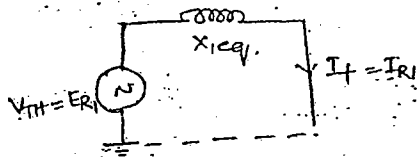
$$V_n = I_n X_n = 0 \text{ (for Solid and Reactance neutral grounding)}$$



\rightarrow In case of Isolated Neutral (or) Reactance neutral, then the fault current remains same because the +ve sequence n/w does not depend on neutral grounding.

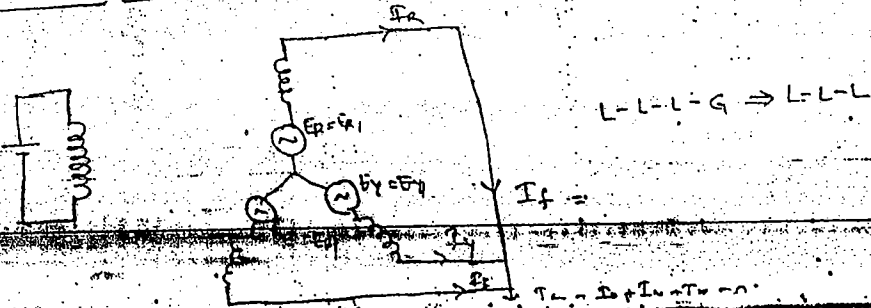\rightarrow L-L-L-G Fault: (3- ϕ to Ground Fault)



$$V_{R0} = V_{R1} = V_{R2} = V_{Rf/3} \rightarrow \textcircled{1}$$

The fault is accounted with the ground so that all the three sequence components exists.

$$I_f = I_A + I_B = I_{Y0} + I_{Y1} + I_{Y2} + I_{B0} + I_{B1} + I_{B2}$$

$$I_f = I_{R0} + K I_{R1} + K I_{R2} + I_{R0} + K I_{R1} + K^2 I_{R2}$$

$$= 2 I_{R0} + (K^2 + K) I_{R1} + I_{R2} (K^2 + K)$$

$$I_f = 2 I_{R0} - I_{R1} - I_{R2}$$

$$I_f = 2 I_{R0} + I_{R0} = 3 I_{R0} \text{ p.u. } \quad (\because I_{R0} = -I_{R1} - I_{R2})$$

→ Calculation of I_{R1}

$$I_{R0} + I_{R1} + I_{R2} = 0$$

Replace I_{R0} and I_{R2} in terms of I_{R1}

$$V_{R0} = V_{R1}$$

$$-I_{R0} x_{0eq} = E_{R1} - I_{R1} x_{1eq}$$

$$I_{R0} = - \left[\frac{E_{R1} - I_{R1} x_{1eq}}{x_{0eq}} \right]$$

$$V_{R1} = V_{R2}$$

$$E_{R1} - I_{R1} x_{1eq} = -I_{R2} x_{2eq}$$


$$I_{R2} = - \left[\frac{E_{R1} - I_{R1} x_{1eq}}{x_{2eq}} \right]$$

$$I_{R0} + I_{R1} + I_{R2} = 0$$

$$I_{R1} = \frac{E_{R1}}{x_{1eq} + \frac{x_{2eq} x_{0eq}}{x_{2eq} + x_{0eq}}} \rightarrow \textcircled{2}$$

1st V_e sequence sub-transient current

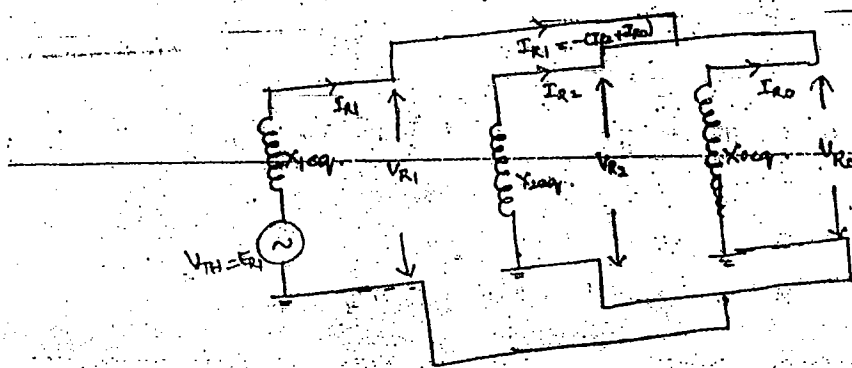From eq's $\textcircled{1}$ and $\textcircled{2}$ it can be observed that the parallel combination of -ve sequence and zero sequence impedances connected in series with +ve sequence imped.



$$I_f = 3 I_{r0} \text{ p.u.}$$

$$I_{r0} = -I_{r1} \frac{X_{2eq}}{X_{2eq} + X_{0eq}}$$

$$SC \text{ MVA} = \frac{\text{Base MVA}}{X_{1eq} + \frac{X_{2eq} X_{0eq}}{X_{2eq} + X_{0eq}}}$$

→ potential of the neutral during the fault:

$$V_n = I_n X_n = 0 \rightarrow \text{Solid neutral grounding}$$

$$= I_n X_n \text{ p.u.} \rightarrow \text{Resistance neutral grounding}$$


** ⇒ whenever there is Reactance Neutral

$$X_{0eq} = X_{G0} + 3X_n$$

** ⇒ whenever there is Isolated Neutral

$$X_{0eq} = X_{G0} + \infty = \infty$$

$$(\because 3X_n = \infty)$$

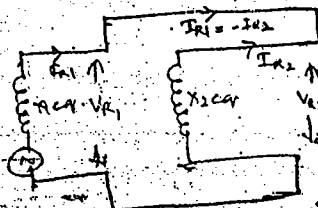


$$L-L-G \Rightarrow L-L$$

(No zero sequence component exists)

A L-L-L-G fault can be resolved as L-L-L fault.

$$I_{R1} = \frac{E_{R1}}{X_{1eq}}$$

(Q)

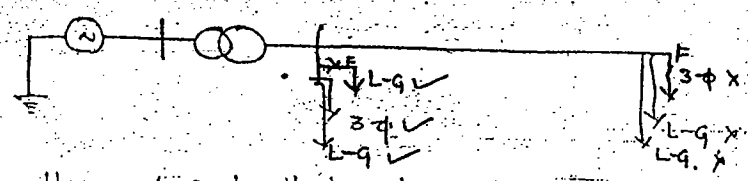


Here L-G fault is only considered. Since L-G is near to source compared to 3-φ fault.

- * Hence 3-φ fault is treated as fault in the system.
- * Here only L-G fault near to the source is considered.

→ We know that the sub-transient reactance offered is very low so that the sub-transient currents are high which will also increase the breaking of the circuit breaker so, that the rating of the c.b is high. The rating of c.b is chosen by considering a 3-φ s.c fault on the existing system. In order to reduce the SC MVA of the breaker it is proposed to have a Series REACTOR in the existing system. So that the net reactance offered will increase which will reduce the sub-transient current as well as the SC-MVA of the breaker.


→ Another application of Reactor is

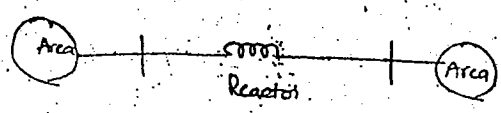

→ REACTORS


(1) Construction

(1) Iron Core

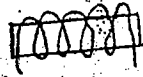

(Saturation problem) X

(2) Air Core


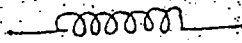


✓

Air core reactors are more preferred than that of Iron core because the iron core reactor is having a core saturation problem.

(2) Application

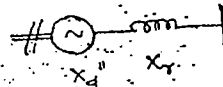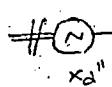(1) Generator Reactor / Alternator reactor



$$S.C. MVA = \frac{\text{Base MVA}}{X_d''}$$


$$S.C. MVA = \frac{\text{Base MVA}}{X_d'' + X_r}$$

** → The Modern Turbo alternator do not require any series reactor because it has inherently high reactance i.e. 2.0 pu.

$$\begin{aligned} \rightarrow \text{SCR} = S.C. MVA &= \frac{\text{Base MVA}}{X_{pu}} \\ &= \frac{1.0}{2.0} = \frac{1}{2} = \underline{0.5 \text{ pu}} \end{aligned}$$

→ The salient pole generators and also the small capacity turbo alternators require the series reactors.

(2) Feeder Reactor:

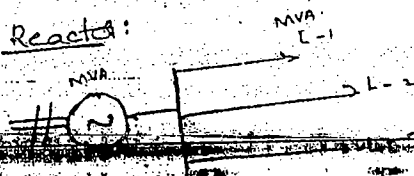



The p.u. reactance of the feeder w.r.t its own rating is very less however w.r.t generator capacity it is very high.

hence there is no need of series reactor in feeders. Sometimes

the fault may take place near to bus bar in the line and

it is considered as Bus-Fault so there is a possibility

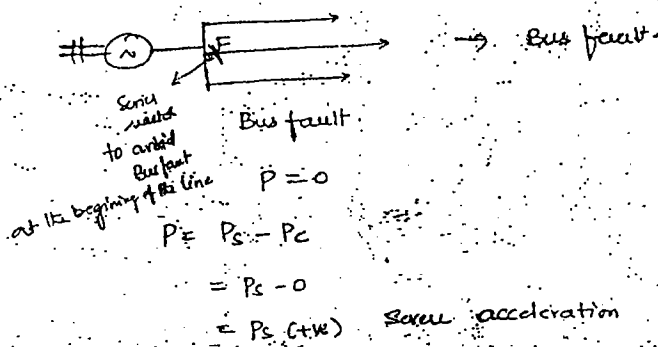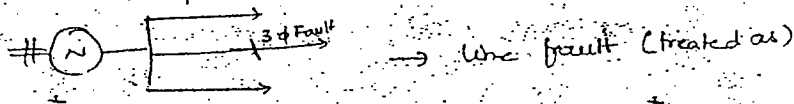to lose the synchronism by the syn. machine.




→ In order to prevent the stability problem a series reactor is proposed having a small reactance and it is preferred to place at the beginning of the tr. line.


17/02/10

→ FAULTS (ASSIGNMENT)

(01)

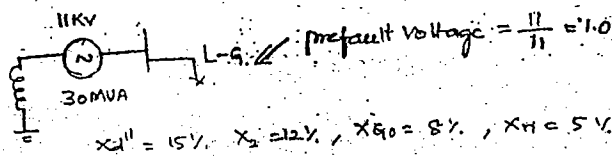

V_n (p.u), V_n (KV)

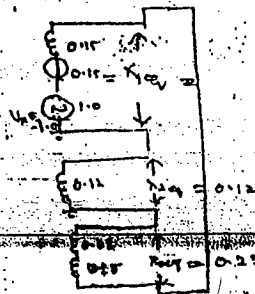

$$I_f = \frac{E - V_n}{X_{1eq} + X_{2eq} + X_{0eq}}$$

$$= \frac{3 \times 1.0}{0.15 + 0.12 + 0.08}$$

$$= 3 \times 1.0$$

$$= 3.0 \text{ p.u. } \Rightarrow 30 \text{ MVA}$$

$$I_f (a) = \frac{G \times \frac{30}{\sqrt{3} \times 11} \text{ KA}}{\left(\frac{\text{MVA}}{\text{KV}} \right)}$$

$$V_n = I_n \cdot X_n$$

$$= I_f \cdot X_n$$

$$V_n = 6.0 \times 0.05 = \underline{0.3 \text{ pu}}$$

$$V_n = \frac{0.3 \times 11}{\sqrt{3}} \text{ KV}$$

$$\text{S.C. MVA} = \frac{+30}{0.15 + 0.12 + 0.23}$$

$$= \frac{30}{0.5} = 60 \text{ MVA}$$

0.15
0.12
0.23

→ +ve Sequence S-T current. $\Rightarrow I_{R1} = \frac{I_f}{3} = \frac{6.0}{3} = 2.0 \text{ p.u.} \left(\frac{E_{R1}}{3} \right)$

→ Voltages of the phases during the fault

$$V_R = V_{R1} + V_{R2} + V_{R0}$$

$$V_{R1} = E_{R1} - I_{R1} X_{1eq}$$

$$= 1.0 - 2.0 \times 0.15 \angle 90^\circ$$

$$= 1.0 - 2.0 \times 0.15$$

$$= \underline{0.7 \angle 0^\circ}$$

$$V_{R2} = -I_{R2} X_{2eq}$$

$$= -2 \angle 90^\circ \times 0.12 \angle 90^\circ = \underline{-0.24 \angle 0^\circ}$$

$$V_{R0} = -I_{R0} X_{0eq}$$

$$= -2 \angle 90^\circ \times 0.23 \angle 90^\circ = \underline{-0.46 \angle 0^\circ}$$

$$V_R = V_{R1} + V_{R2} + V_{R0}$$

$$= 0.7 \angle 0^\circ + -0.24 \angle 0^\circ + -0.46 \angle 0^\circ$$

$$= \underline{0}$$

$$V_y = -V_{y0} + V_{y1} + V_{y2}$$

$$= V_{R0} + K^2 V_{R1} + K V_{R2}$$

$$= -0.46 \angle 0^\circ + 0.7 \angle 240^\circ + 0.24 \angle 120^\circ$$

$$= -0.46 + \cos^{0^\circ} 240 + j0.7 \sin 240 - 0.24 \cos 120 - j0.24 \sin(120)$$

$$= -0.69 - j0.814$$

$$= 1.06 \angle -130^\circ$$

$$V_B = V_{B0} + V_{B1} + V_{B2}$$

$$= V_{R0} + K V_{R1} + K^2 V_{R2}$$

$$= -0.46 \angle 0^\circ + 0.7 \cos(120) + j0.7 \sin 120 - 0.24 \cos 240 - j0.24 \sin 240$$

$$= -0.69 - j0.398$$

$$= 0.796 \angle 150^\circ$$

(10) 3- ϕ 500 MVA, 50 Hz, $V = 22$ kV, $X_1 = X_2 = 0.15$, $X_0 = 0.05$

Find: The subtransient current for 1- ϕ to ground fault in p.u.

$$I_{R1} = I_f = \frac{3 E_{R1}}{X_{1eq} + X_{2eq} + X_{0eq}}$$

$$= \frac{3 \times 1.0}{0.15 + 0.15 + 0.05}$$


$$= \frac{3}{0.35} = 8.571 \text{ p.u.}$$

$$I_f (\text{KA}) = 8.57 \times \left(\frac{500}{\sqrt{3} \times 22} \right)$$

$$= 112.45 \text{ KA}$$

Neutral solid grounded, $V_n = 0$
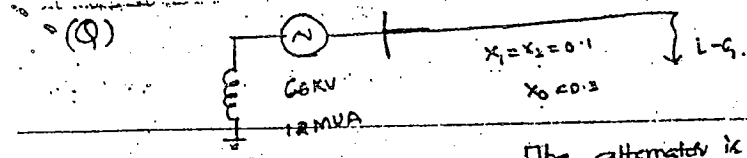
$$S.C. \text{ MVA} = \frac{500}{0.15 + 0.15 + 0.05} = \frac{500}{0.35} = 1428.5 \text{ p.u.}$$




$X_d'' = 0.12$
 $X_2 = 0.1$
 $X_{G0} = 0.02$
 $X_n = 0.05$

The alternator is working under no load at rated voltage. The +v. line is having the same rating as that of alternator. The potential of the neutral to Volt during the fault is.

Sol

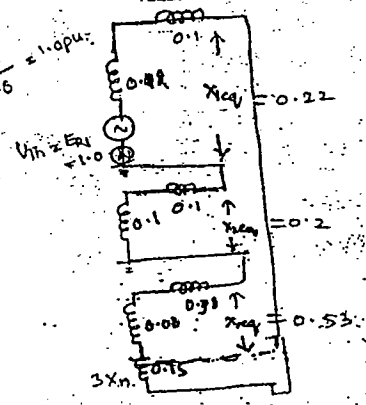Pre-fault Voltage = $\frac{6.6}{\sqrt{3}} = 3.81 \text{ pu}$



$$V_n = I_n X_n$$

$$= I_f X_n$$

$$I_f = \frac{3 \cdot E R I}{X_{1eq} + X_{2eq} + X_{0eq}}$$

$$= \frac{3 \times 1}{0.22 + 0.2 + 0.53}$$

$$= 3.157 \text{ pu}$$

$$= 3.157 \text{ pu}$$


$$V_n = I_n X_n$$

$$= 3.157 \times 0.05$$

$$= 0.157 \text{ pu}$$


$$V_n (\text{KV}) = 0.157 \times \frac{6.6 \times 10^3}{\sqrt{3}} \text{ Volt}$$

$$= 598.25 \text{ KV}$$

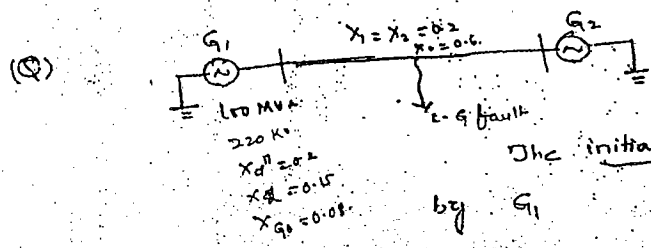


The initial symmetrical RMS current in KA supplied by G1 Sub-transient current.

Sol

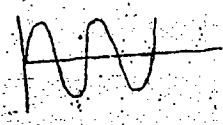

Sub-transient Current = Initial symmetrical RMS current (a.c) component.

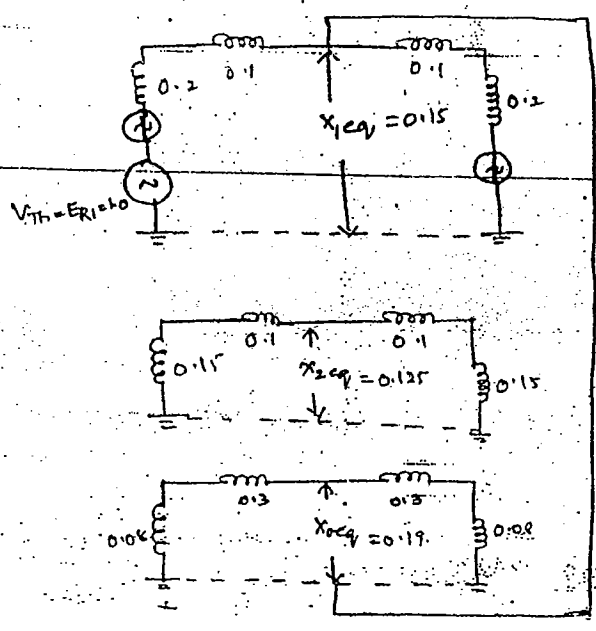Pre-fault Voltage = $\frac{220}{\sqrt{3}} \text{ pu}$



$$I_f = \frac{3 \times 1 \text{ pu}}{0.15 + 0.125 + 0.19} = 6.45 \text{ pu}$$

$$I_f (G) = \frac{6.45}{2} = 3.225 \text{ pu}$$


$$I_f (\text{KA}) = 3.225 \times \frac{100}{\sqrt{3} \times 220} \text{ KA} = 0.846 \text{ KA}$$

→ The momentary fault current to KA (is) the initial symmetrical current in KA.

$$I_m = I_f (\text{KA}) \times 1.6 \quad (\text{Include dc effect})$$

$$= 3.225 \times \frac{100}{\sqrt{3} \times 220} \times 1.6 = 1.35 \text{ KA}$$


(Q2)

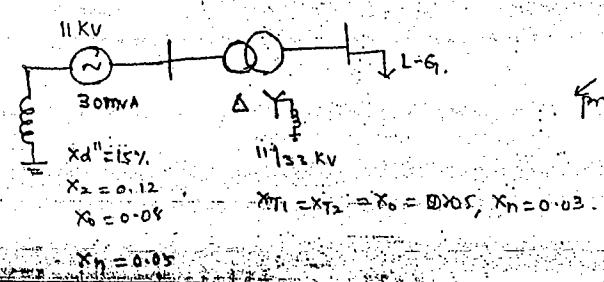

$$V = 31.75 \text{ KV}$$

$$V_{\text{prefault voltage}} = \frac{31.75}{33} = 0.962 \text{ pu}$$
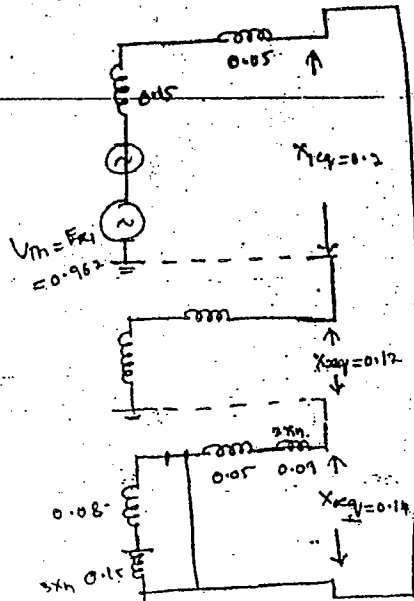
$$X_{T1} = X_{T2} = X_0 = 0.05, X_n = 0.05$$



$$I_f = \frac{3 \times 0.962}{0.2 + 0.17 + 0.14} = 5.66 \text{ p.u.}$$

$$I_f (\text{KA}) = \frac{5.66 \times 30}{\sqrt{3} \times 33} \text{ KA} = 2.970 \text{ KA}$$


$$V_n = I_n X_n = I_f X_n$$

$$V_n = 5.66 \times 0.03 \text{ p.u.}$$


$$= 5.66 \times 0.03 \times \frac{33}{\sqrt{3}} \text{ KV} = 3.235 \text{ KV}$$

$$\text{S.C MVA} = \frac{30}{0.2 + 0.17 + 0.14} = \frac{30}{0.51} = 58.8 \text{ p.u.}$$

(03)

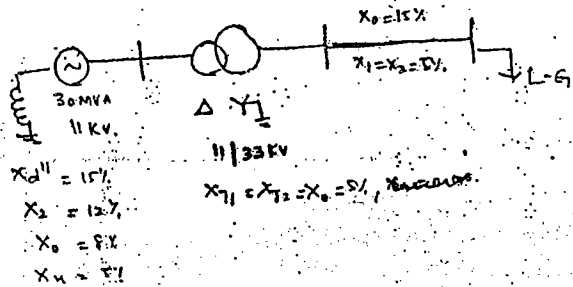
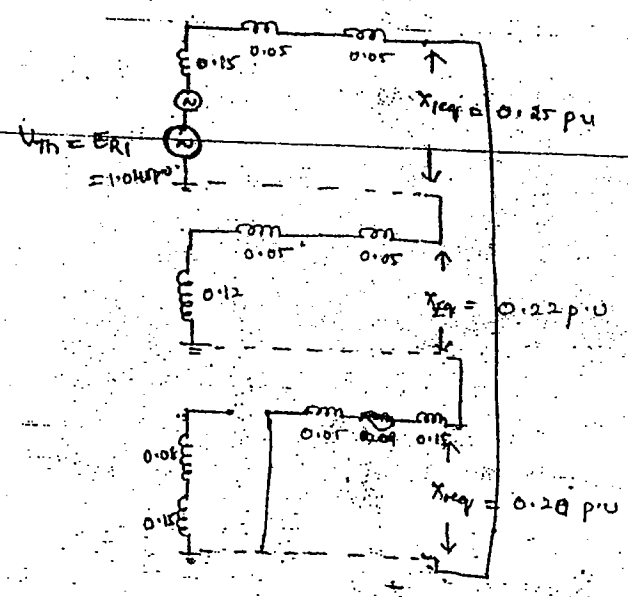
$$\text{Pre fault voltage} = \frac{34.5}{33} = 1.045 \text{ p.u.}$$



$$\begin{array}{r} 0.12 \\ 0.05 \\ \hline 0.17 \\ 0.12 \end{array}$$

$$\begin{array}{r} 0.05 \\ 0.05 \\ \hline 0.10 \\ 0.20 \end{array}$$

$$I_f = \frac{3 \times 1.045}{0.25 + 0.22 + 0.20} = \frac{3.135}{0.67} = 4.67 \text{ p.u.}$$

$$\begin{array}{r} 11 \\ 1045 \times 3 \\ \hline 3135 \\ 0.17 \\ 0.22 \\ 0.20 \\ \hline 0.67 \end{array}$$

~~IC~~ $V_n = 0$

(04)



$$I_{R0} = 1.2 \text{ p.u.} \Rightarrow I_f = 3I_{R0} = 7.2 \text{ p.u.}$$

$$X_n = 5\%$$

$$V_n = I_n X_n = I_f X_n = 7.2 \times 0.05 = 0.36 \text{ p.u.}$$

(06)

(a)

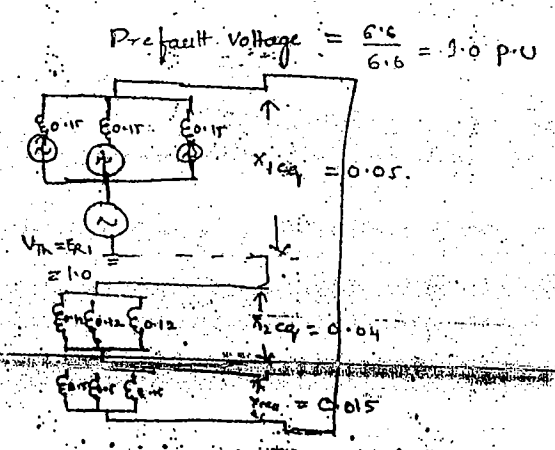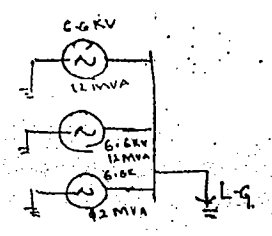


$$I_f = \frac{3 \times 1.0}{0.05 + 0.04 + 0.015}$$

$$= 28.57 \text{ pu.}$$

$$I_f(\text{KA}) = 28.57 \times \left(\frac{12}{\sqrt{3} \times 66} \right) \text{ KA} \approx \underline{30 \text{ KA}}$$

$$V_n = 0$$

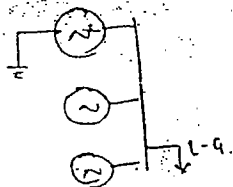(b) One of the neutral is grounded & the other two are isolated




$$I_f = \frac{3 \times 1.0}{0.05 + 0.04 + 0.04}$$



$$= 22.2 \text{ pu}$$

$$= 22.2 \times \frac{12}{\sqrt{3} \times 66} \text{ KA} = 23.30 \text{ KA.}$$

$$V_n = 0.$$

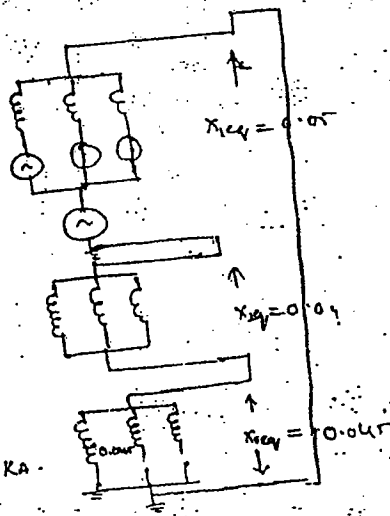

(c)

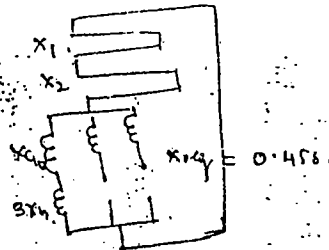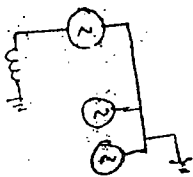

$$X_n \text{ pu} = 0.5 \times \frac{12}{(66)} = 0.137 \text{ pu}$$

$$3X_n = 3 \times 0.137 = 0.41$$

$$I_f = \frac{3 \times 1.0}{0.05 + 0.04 + 0.406}$$

$$= 5.47 \text{ pu} = 5.47 \times \frac{12}{\sqrt{3} \times 66} \text{ KA}$$

$$= 5.742 \text{ KA}$$

$$V_n = I_n \times X_n$$

$$= 5.47 \times 0.137 \text{ pu}$$


$$= 5.47 \times 0.137 \times \frac{66}{\sqrt{3}} \text{ KV}$$

$$= 285.55 \text{ KV}$$

(Q) One of the generator is grounded through a resistance of 2Ω . Calculate

I_f (p.u), I_f (KA), & V_n in Volts.

1811

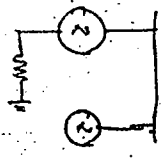

$$R_n = 2 \times \frac{22}{(6.6)^2}$$

$$= 0.55 \text{ p.u.}$$

$$3R_n = 1.65 \text{ p.u.}$$

$$I_f = \frac{3 \times 110}{j0.05 + j0.05 + 1.65 + j1.05}$$

$$= \frac{3 \times 110}{1.65 + j0.135}$$

$$= \frac{3 \times 110}{\sqrt{(1.65)^2 + (0.135)^2}}$$

$$= 1.81 \angle -4.67^\circ \text{ p.u.}$$

$$I_f \text{ (KA)} = \frac{1.81 \times 12}{\sqrt{3} \times 6.6} \text{ KA} = 1.90 \text{ KA}$$


$$V_n = I_n R_n$$

$$= 1.81 \times 0.55 \text{ p.u.}$$


$$V_n = 1.81 \times 0.55 \times \frac{6.6 \times 10^3}{\sqrt{3}} \text{ V} = 3793.36$$

$$S \cdot \text{CMVA} = \frac{12}{1.65 + j0.135} = \frac{12}{\sqrt{(1.65)^2 + (0.135)^2}} = 7.248 \text{ p.u.}$$

(Q8)

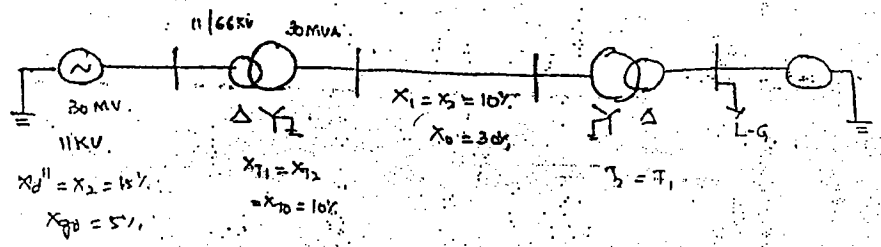
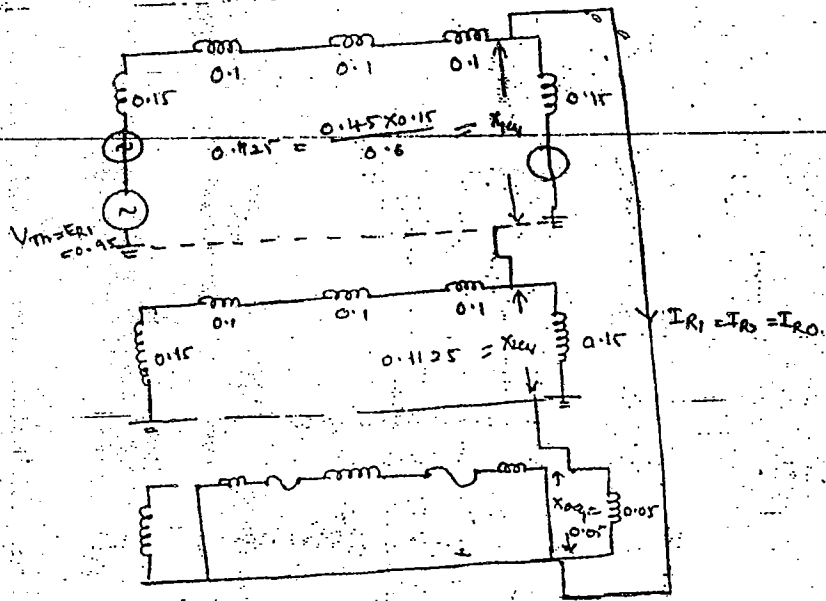
$$\text{Prefault Voltage} = \frac{10.5}{11} = 0.95$$



$$(i) \quad I_{R1} = \frac{E_{R1}}{X_{1eq} + X_{2eq} + X_{0eq}}$$

$$= \frac{0.95}{0.1125 + 0.1125 + 0.05} = 3.45 \text{ pu}$$

$$I_{R1}(G) = 3.45 \times \frac{0.15}{0.15 + 0.45} = 0.8625$$

$$I_{R1}(M) = 3.45 \times \frac{0.45}{0.45 + 0.15} = 0.75 \times 3.45 = 2.5875$$


$$I_{R2}(G) = 3.45 \times \frac{0.15}{0.15 + 0.45} = 0.8625$$

$$I_{R2}(M) = 3.45 \times \frac{0.45}{0.45 + 0.15} = 2.5875$$

$$I_{R0}(G) = 0$$

$$I_{R0}(M) = 3.45$$

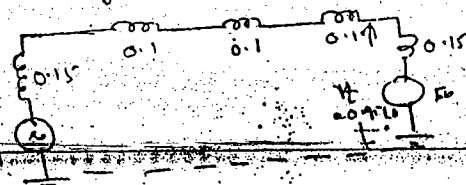(ii) Calculation of voltages behind the reactances of the mlt's



$$E_g = 0.95 \angle 0^\circ + I \cdot pu \times 0.45 \angle 90^\circ$$

$$E_b = 0.95 \angle 0^\circ - I \cdot pu \times 0.15 \angle 90^\circ$$

$$I \cdot pu = \frac{15 \times 10^6}{\sqrt{3} \times 10.5 \times 10^3 \times 0.8} \bigg/ \frac{30 \times 10^6}{\sqrt{3} \times 11 \times 10^3} \quad \begin{matrix} \text{(actual)} \\ \text{(base)} \end{matrix}$$

$$= \frac{15 \times 11}{30 \times 10.5 \times 0.8}$$

$$= 0.655 \angle 36.86^\circ$$

$$E_g = 0.95 \angle 0^\circ + 0.655 \angle 36.86^\circ \times 0.45 \angle 90^\circ$$

$$= 0.95 \angle 0^\circ + 0.655 \times 0.45 \angle 90^\circ + 36.86^\circ$$


$$E_g = 0.808 \angle 16.96^\circ$$

$$E_b = 0.95 \angle 0^\circ - 0.655 \angle 36.86^\circ \times 0.15 \angle 90^\circ$$

$$= 0.95 \angle 0^\circ - 0.655 \times 0.15 \angle 90^\circ + 36.86^\circ$$

$$E_b = 0.894 \angle 5.04^\circ$$


(18)

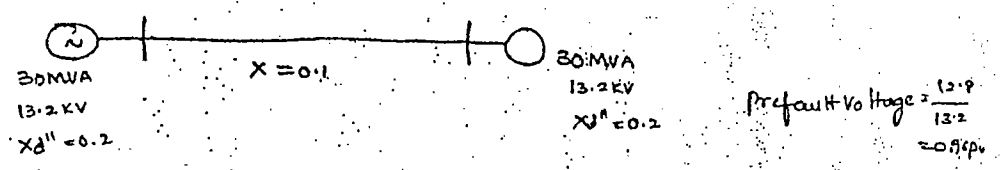

Sol

Fault Analysis is generally based on prefault voltage.

$$V_m = E_{R1} = 0.96 \text{ pu}$$

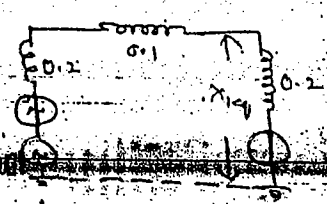


$$I_f = \frac{E_{R1}}{X_{12}} = \frac{0.96}{0.2 + 0.2} = 2.4 \text{ pu}$$

$$I_{ff}(G) = 8.0 \times \frac{0.2}{0.5}$$

$$I_{ff}(M) = 8.0 \times \frac{0.3}{0.5}$$

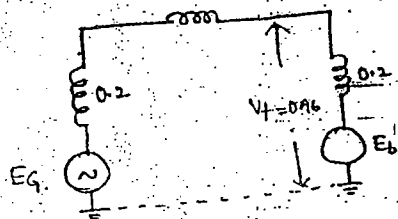But calculate the internal voltages for fault currents



$$E_G = 0.96 \angle 0^\circ + I_{pu} \times 0.3 \angle 90^\circ$$

$$E_B = 0.96 \angle 0^\circ - I_{pu} \times 0.2 \angle 90^\circ$$

$$\text{But } I_{pu} = \frac{20 \times 10^6}{\sqrt{3} \times 12.8 \times 10^3 \times 0.8} \Bigg/ \frac{30 \times 10^6}{\sqrt{3} \times 15.2 \times 10^3}$$

$$= 0.86 \angle 36.86^\circ$$

$$E_G = 0.96 \angle 0^\circ + 0.86 \times 0.3 \angle 126.86^\circ = 0.831 \angle 114.34^\circ$$

$$E_B = 0.96 \angle 0^\circ - 0.86 \times 0.2 \angle 126.86^\circ = 1.07 \angle -73.7^\circ$$

$$I_G = \frac{E_G}{0.3 \angle 90^\circ} = \frac{0.831 \angle 114.34^\circ}{0.3 \angle 90^\circ} = 2.77 \angle -75.62^\circ$$

$$I_M = \frac{E_B}{0.2 \angle 90^\circ} = \frac{1.07 \angle -73.7^\circ}{0.2 \angle 90^\circ} = 5.35 \angle -97.37^\circ$$

$$I_f = I_G + I_M = 7.989 \angle -99.98^\circ$$


(11)

$$\begin{aligned}
 V_n &= I_n X_n \\
 &= 3 I_{R0} X_n \\
 &= 3 I_{R1} X_n \\
 &= 3 \times 2.0 \times 0.05 \\
 &= 0.3 \text{ pu} \\
 V_n &= 0.3 \times \frac{13.2 \times 10^3}{\sqrt{3}} \text{ Volts} = 2286.3 \text{ V.}
 \end{aligned}$$


(12)

$X_d'' = X_2 = 20\%$, 30 MVA, 13.2 KV,
 $V_f = 13.8$

Sol

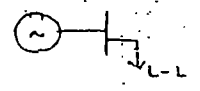


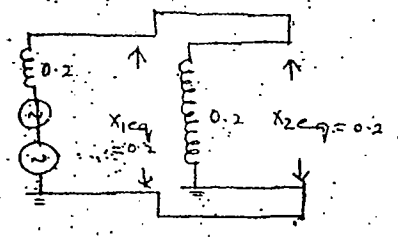Pre-fault Voltage = $\frac{13.8}{13.2} = 1.045$




$$\begin{aligned}
 I_f &= \sqrt{3} I_{R1} \\
 &= 1.732 \times \frac{E_{R1}}{X_{1eq} + X_{2eq}} \\
 &= 1.732 \times \frac{1.045}{0.2 + 0.2} \\
 &= 4.52 \text{ pu} \\
 I_f &= 4.52 \times \frac{30}{\sqrt{3} \times 13.2} \text{ KA} \\
 &= 1033.4 \text{ KA}
 \end{aligned}$$

(14)

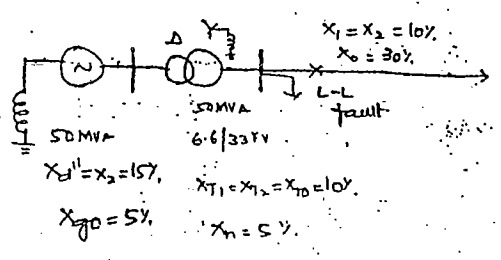

Sol

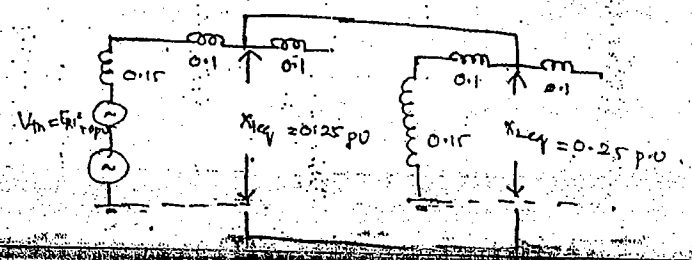Pre-fault Voltage = $\frac{33}{33} = 1.0 \text{ pu}$




$$I_f = 1.732 \times \frac{1}{0.25 + j0.25} = 3.464 \text{ pu}$$

$$I_f(\text{KA}) = \frac{3.464 \times 50}{\sqrt{3} \times 33} \text{ KA} = 3299.7 \text{ KA}$$

$$\text{S.C. MVA} = \frac{50}{0.25 + j0.25} = \frac{50}{0.5} = \frac{500}{5} = 100$$

(20)

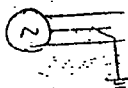

LLG \Rightarrow L-L

15 MVA, 13.2 kV,

+ve 30%,
-ve 20%,
'0' 0%

$$I_f = \frac{\sqrt{3} \cdot E_{R1}}{X_{1eq} + X_{2eq}}$$

$$= 1.732 \times \frac{1.0}{0.3 + j0.2}$$

$$= 3.464 \text{ pu}$$

$$I_f(\text{A}) = \frac{3.464 \times 15 \times 10^3}{\sqrt{3} \times 13.2 \times 10^3} \text{ A} = 2272.6$$

The limiting values of the currents in the phases is nothing but the max amount of current in the phases which is same as fault current

$$I_y = I_B = I_f$$

$$\Rightarrow I_f = 3.464 \times \frac{15 \times 10^3}{\sqrt{3} \times 13.2 \times 10^3} \text{ A} = 2272.6$$

Repetitive
MP stand
97

(Q) A short ext fault on the alternator has given the following results

$$I_{R1} = -j8.5 \text{ pu}, I_{R2} = j5.5 \text{ pu}, I_{R3} = j3.0 \text{ pu} \text{ and}$$

$$V_{R1} = V_{R2} = V_{R3} = 0.45 \text{ pu} \text{ The fault is}$$

- A) L-G B) L-L-G C) LL-L-G (D) L-L-L


$$I_{R1} = -(I_{R2} + I_{R3})$$

(14) The voltage of healthy phase is _____

$$V_{RO} = V_{RJ} = V_{RD} = V_R/3$$

$$\begin{aligned} V_{R0} &= 3V_{RO} \\ &= 3 \times 0.45 \\ &= \underline{1.35 \text{ p.u.}} \end{aligned}$$

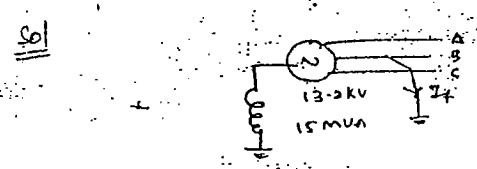(15) A, 50th, 13.2kV, 15MVA, $X_1 = X_2 = 20\%$, $X_{q0} = 8\%$ and $X_n = 0.5\%$
 $V_t = 13.9 \text{ V}$




In grounded faults the current through the ground/neutral will be same as fault current

$$\text{Pre-fault voltage} = \frac{13.9}{13.2} = 1.05 \text{ p.u.}$$

$$E_g = 1.05 \text{ p.u.}$$

$$\begin{aligned} X_n &= 0.5 \times \frac{15}{(13.2)^2} \\ &= 0.043 \end{aligned}$$
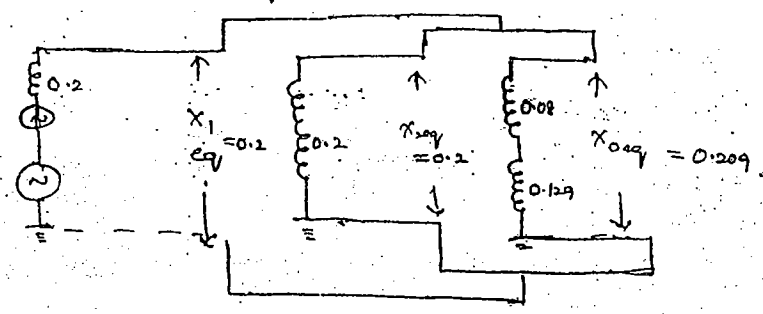
$$\begin{aligned} 3X_n &= 3 \times 0.043 \\ &= 0.129 \text{ p.u.} \end{aligned}$$



$$I_{\text{ground}} = I_f = 3 I_{c0}$$

$$X_{eq} = X_1 + X_2 + X_0 + X_n$$

$$I_{a1} = \frac{1.05}{0.2 + \frac{0.2 \times 0.29}{0.409}}$$

$$= 3.47 \angle -90^\circ$$

$$I_{a0} = -3.47 \angle -90^\circ \times \frac{0.2}{0.409}$$

$$= 1.69 \angle 90^\circ$$

$$I_{a2} = -3.47 \angle -90^\circ \times \frac{0.209}{0.409}$$

$$= 1.77 \angle 90^\circ$$

$$I_{\text{ground}} = 3 \times 1.69 \angle 90^\circ$$

$$= 3 \times 1.69 \times \frac{15}{\sqrt{3} \times 13.2} \text{ KA (rms)} \approx 577.5 \text{ KA}$$

$$V_n = I_n X_n$$

$$= 3 \times 1.69 \times 0.043$$

$$V_n = 3 \times 1.69 \times 0.043 \times \frac{13.2 \times 10^3}{\sqrt{3}} \text{ Volt} = 1661.45$$

$$\text{SC MVA} = \frac{15}{0.2 + \frac{0.2 \times 0.29}{0.409}} = \frac{15}{0.302} = 49.63$$

Current in phase B AC:

$$I_B = I_{B0} + I_{B1} + I_{B2}$$

$$= I_{A0} + k^2 I_{A1} + k I_{A2}$$

$$= 1.69 \angle 90^\circ + 3.47 \angle 150^\circ + 1.77 \angle 90^\circ + 120^\circ$$

$$I_B = 5.2 \angle 150^\circ + 6$$

$$5.2 \angle 150^\circ + 6 \times \left(\frac{15 \times 10^6}{13.2 \times 10^3} \right)$$

$$= 5.2 \times 1136.36 \angle 150^\circ + 6$$

$$I_c = I_{c0} + I_{c1} + I_{c2}$$

$$= I_{c0} + KI_{c1} + K^2 I_{c2}$$



$$= 1.69 \angle 90^\circ + 8.47 \angle -90^\circ + 20^\circ + 1.77 \angle 90^\circ + 240^\circ$$

$$= 5.2 \angle 29.2^\circ \text{ p.u.}$$

$$I_c(a) = I_c \text{ p.u.} \times I_{base} = 5.2 \times 1136.36 \angle 29.2^\circ$$

$$= 5909.07 \angle 29.2^\circ$$

(16)

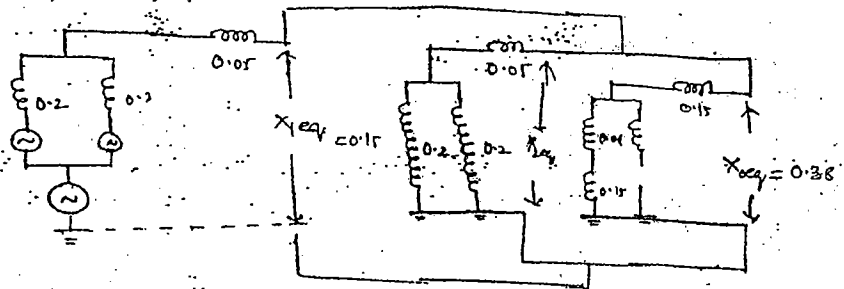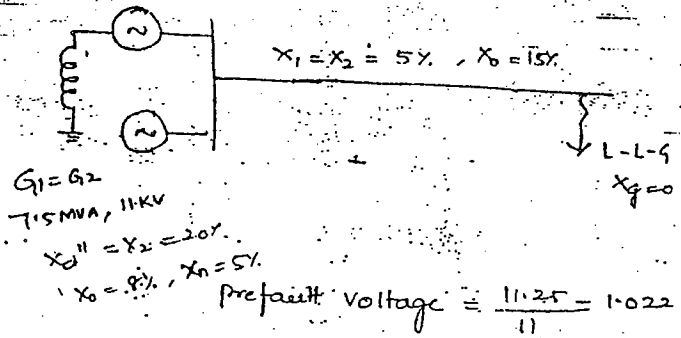

$$I_{ground} = I_f = 3 I_{R0}$$

$$I_{R1} = \frac{1.022}{0.15 + 0.15 \angle 90^\circ} = 3.968 \angle -9^\circ$$

$$I_{R0} = -I_{R1} \frac{X_2 \text{ eq}}{X_2 \text{ eq} + X_0 \text{ eq}}$$

$$= 3.968 \angle 90^\circ \times \frac{0.15}{0.15 + 0.9}$$

$$= 1.12 \text{ p.u.}$$

$$I_{ground} = 3 \times 1.12$$

$$= 3.36 \text{ p.u.}$$

$$= 3.36 \times \frac{7.5}{\sqrt{3} \times 11} \text{ KA} = 160.04 \text{ KA}$$

$$SCMVA = \frac{7.5}{0.15 + \frac{0.15 \times 0.38}{0.15 + 0.38}} = \frac{7.5}{0.15 + \frac{0.057}{0.53}} = 29.12$$

(17) 30 MVA, 11 KV, $X_d'' = 20\%$, $X_d' = 30\%$, $X_d = 100\%$, Balanced fault

$$I_f = I_R = I_{R1} = \frac{E_{R1}}{X_d''} = \frac{1.0}{0.2} = 5.0 \text{ p.u.}$$

$$I_f (\text{KA}) = 5 \times \frac{30}{\sqrt{3} \times 11} \text{ KA} = 952.62 \text{ KA}$$

After 4 cycles

$$I_f = 3.33 \text{ p.u.}$$

$$= 3.33 \times \frac{30}{\sqrt{3} \times 11} \text{ KA} = 634.45$$

(25) A 20 MVA, 33 KV, $I_f 3\phi = 319 \text{ A}$
 $I_f L-G = 659 \text{ A}$
 $I_f L-L = 435 \text{ A}$

Sol

$$I_f(a) = I_f \cdot \text{p.u.} \cdot I_{base}$$

$$I_{base} = \frac{20 \times 10^6}{\sqrt{3} \times 33 \times 10^3} = 350 \text{ A}$$

$$319 = \frac{E_{R1}}{X_{1 \text{ p.u.}}} \times 350$$

$$X_{1 \text{ p.u.}} = \frac{350 \times 350}{319} = 384.33$$

L-L

$$I_f(\text{ca}) = \frac{1.732 \times E_{R1}}{X_{1pu} + X_{2pu}} \cdot I_{base}$$

$$\Rightarrow X_{1pu} + X_{2pu} = \frac{1.732 \times 1.0 \times 350}{435}$$


$$\begin{aligned} \Rightarrow X_{2pu} &= \frac{1.732 \times 350 \times 1.0}{435} - X_{1pu} \\ &= 1.3933 - 1.097 \\ &= 0.2966 \end{aligned}$$

L-G


$$I_f(\text{ca}) = \frac{3 \cdot E_{R1}}{X_{1pu} + X_{2pu} + X_{0pu}} \cdot I_{base}$$

$$X_{1pu} + X_{2pu} + X_{0pu} = \frac{3 \times 1.0 \times 350}{659}$$
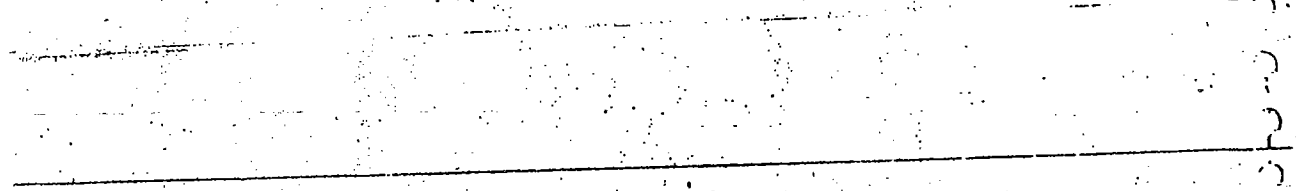
$$\begin{aligned} X_{0pu} &= \frac{3 \times 350}{659} - X_{1pu} - X_{2pu} \\ &= 1.593 - 1.097 - 0.2966 \\ &= 0.1997 \text{ pu} \end{aligned}$$






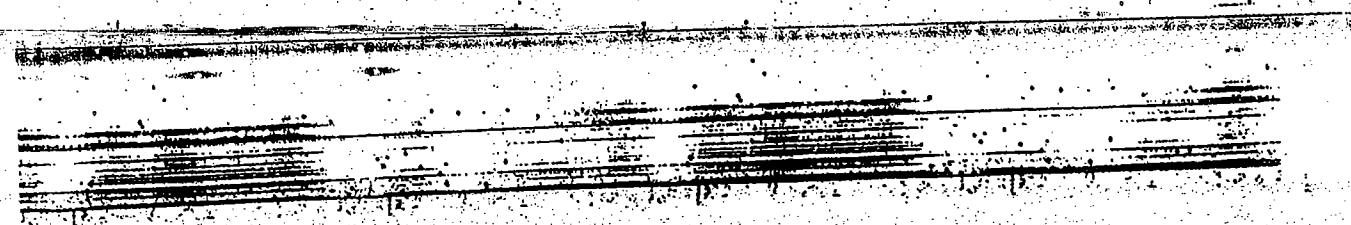
Handwritten marks or characters, possibly a date or initials, located on the right side of the page.





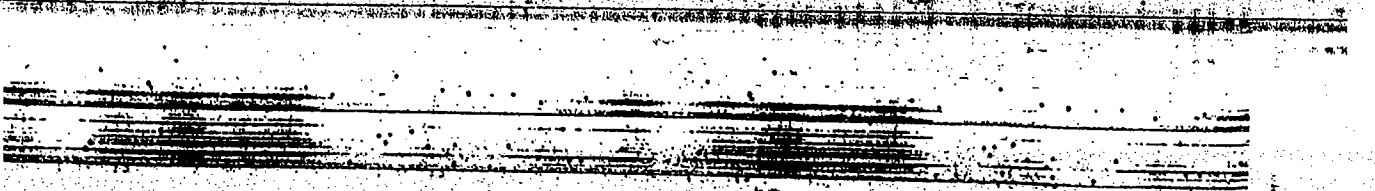The page contains extremely faint and illegible text, likely bleed-through from the reverse side of the paper. The text is scattered across the page and is not readable.




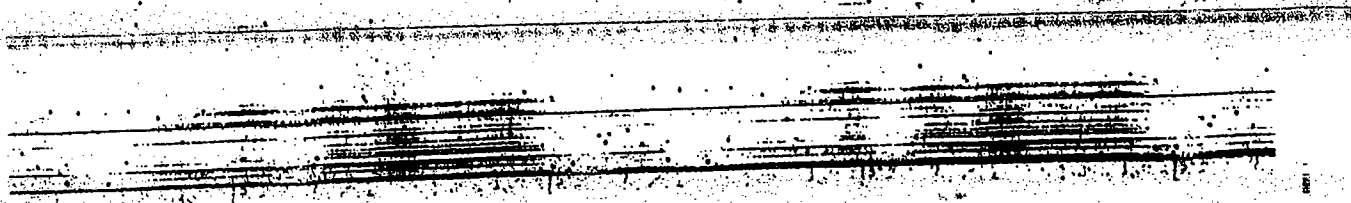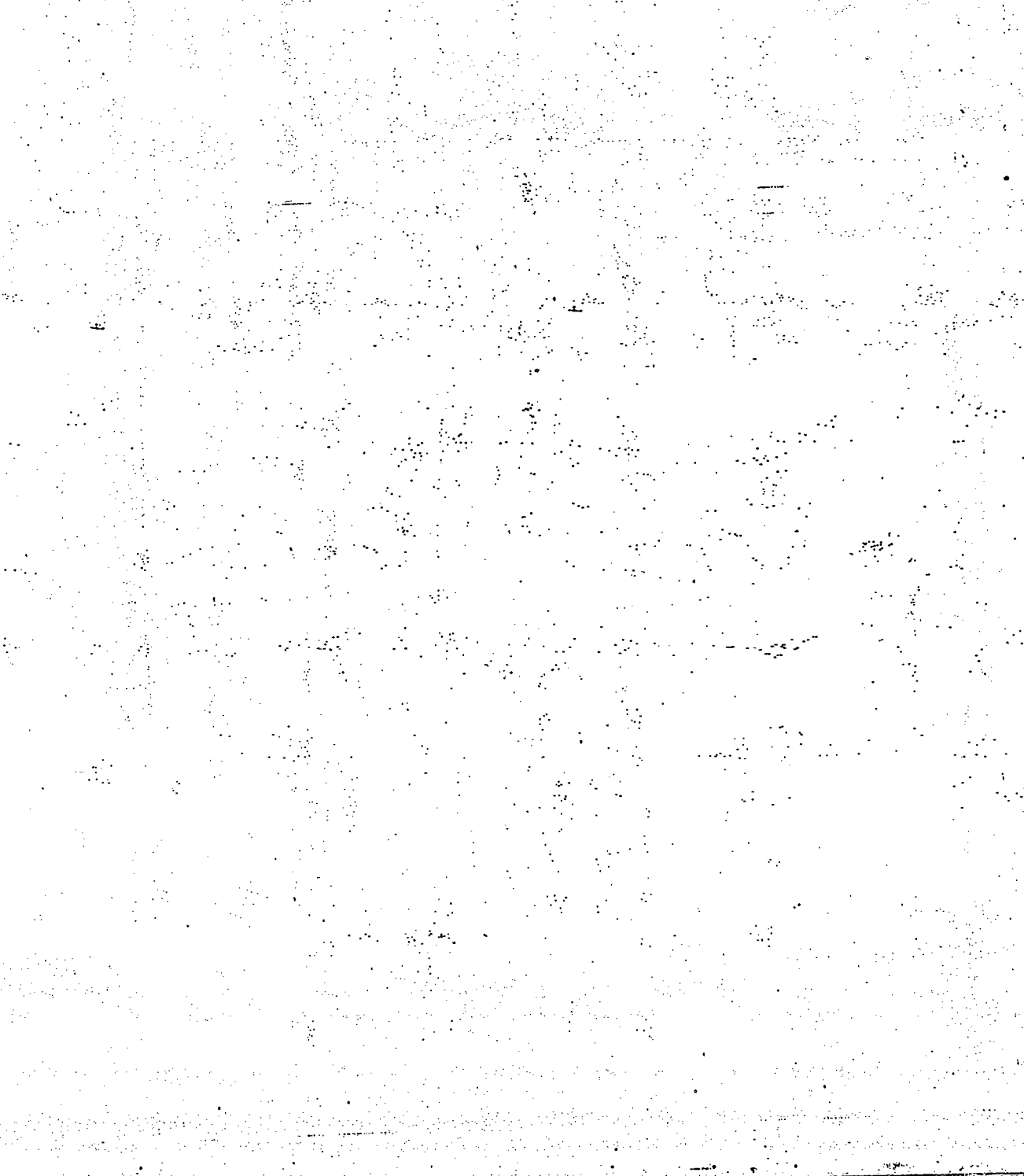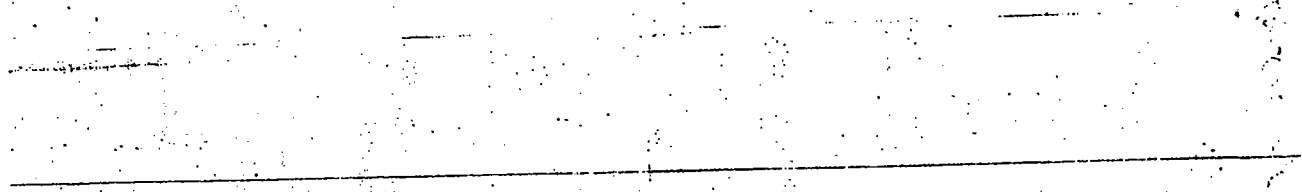


23/03/10

POWER SYSTEM STABILITY

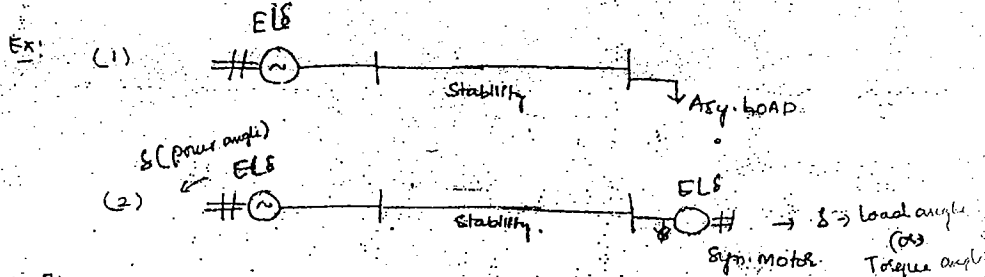→ Stability is associated with synchronous machines while delivering or receiving power from, sym machine can act both as generator and motor



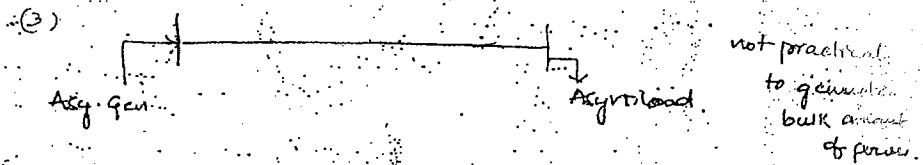The above two cases have associated with stability because sym. m/cs are involved in both cases.





In this case the concept of stability doesn't arise.


The bulk amount of power is generated by using conventional sources with the help of Asy. generators and the load may be asynchronous or synchronous.

STABILITY: It is the ability of the synchronous machine to deliver maximum amount of real power to the load by maintaining the synchronization with the externally connected tie line, i.e. transmission line

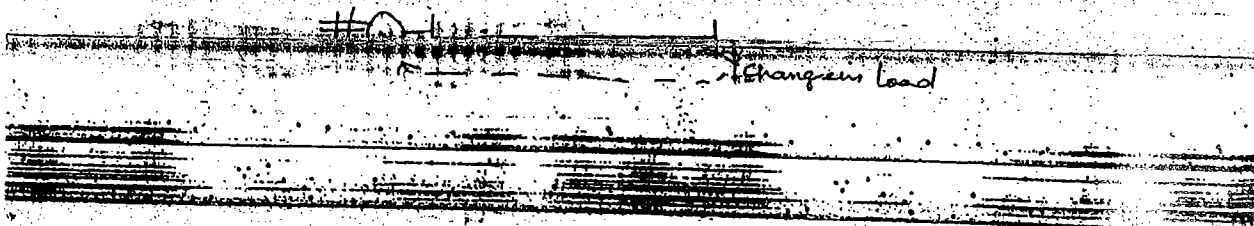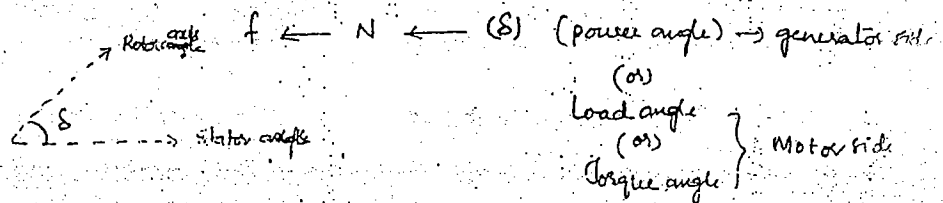SYNCHRONIZATION: It is associated with some parameters in the system like frequency (f) and voltage (V)



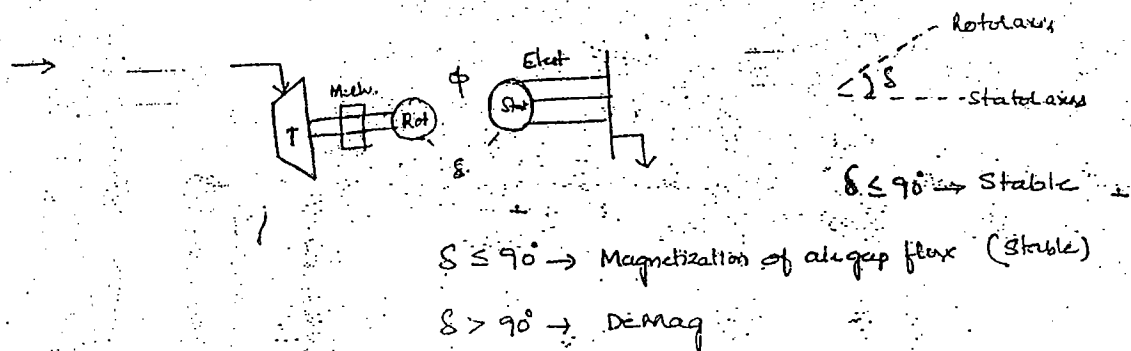→ The power system network is a dynamic network that is it will experience a continuous variation of the load. Any change of load will reflect directly on the source of generation i.e. change in the position of rotor axis with respect to the stator. Which in turn understand in terms of speed or the frequency of the system.




→ The stability of the synchronous machine can also be understood in terms of the magnetization of air gap flux (ϕ). Demagnetization of the air gap flux

→ Change of load on the system is considered as

- 1) Small and gradual change \rightarrow Steady State Stability
- 2) Sudden and large variation \rightarrow Transient Stability

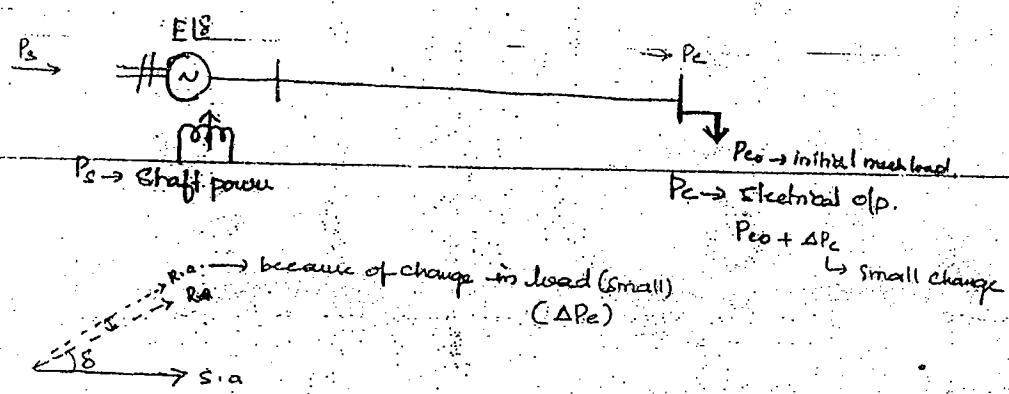1) STEADY STATE STABILITY : It is the ability of a syn. m/c. to deliver maximum amount of real power to the load by a synchronous machine while maintaining the synchronisation with the externally connected to line where the syn. machine is experiencing a small and gradual variation of the load. The small and gradual variation of the load means the rate of change of load is less than the rate of change of excitation (or) the frequency of oscillations made by the rotor are less than natural frequency of the system.




The oscillations of the rotor, i.e. the frequency of the oscillations of rotor is negligible small.

→ As there is no much change in the rotor position for a small and gradual variation of the load then the steady state stability analysis can be analysed by using the static motor model i.e. the power flow equations of the reactance diagram (per phase)

→ The change of load is considered in all the three phases so that the synchronous machine is working in a balanced manner, the current in the neutral is zero and the reference for the reactance diagram is neutral.

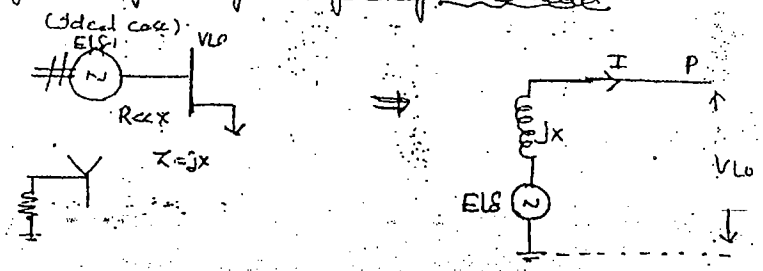→ Steady stability analysis by using static model



The power equation at load point

$$S = VI^*$$

$$= |V| |I_0| \left[\frac{|E|}{|X|} - |V| \right]^*$$

$$\frac{P}{X} = \frac{|V|^2}{|X|} \left[\frac{|E|}{|V|} - 1 \right]$$

Real power transfer, $P_e = \frac{|E||V|}{X} \sin \delta$


($\because \delta'$ is not considered in stability)

$\therefore P_e = P_{max} = \text{Steady state stability limit } (\delta = 90^\circ)$

$\therefore P_{max} = \frac{|E||V|}{X} \sin 90^\circ$

$\Rightarrow P_{max} = \frac{|E||V|}{X}$

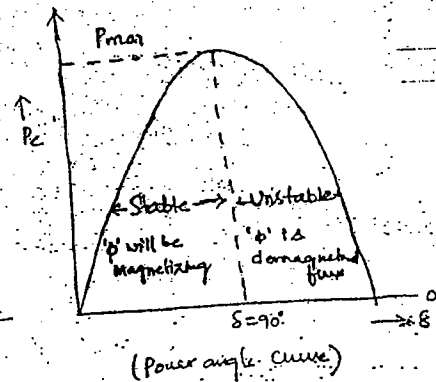→ Due to change of load if $\delta > 90^\circ$ the real power transfer P_e is reduced



→ The S.S. of the Syn. m/c can also be analysed by considering the degree of magnetic coupling (or) the electrical stiffness which can be expressed in terms of synchronizing power i.e. $\frac{dP_e}{d\delta}$

$\therefore \frac{dP_e}{d\delta} = \frac{|E||V|}{X} \cos \delta$

If $\delta > 90^\circ \Rightarrow \frac{dP_e}{d\delta} = -ve. \Rightarrow \text{Demagnetization}$

→ The concept of the steady state stability is the angle stability, i.e. if $\delta \leq 90^\circ$ before change of load, the Syn. m/c is stable, otherwise it is unstable.

Ex: A Syn. m/c is directly connected to the load. The internal voltage of the Syn. m/c is 1.2 p.u. and the load voltage 1.0 p.u. The synchronous reactance of the m/c is 1.5 p.u. The Real power transfer, the synchronizing power and the steady state stability limit of the Syn. m/c

for an initial angle of $\delta = 30^\circ$

Sol

$$P_c = \frac{EV}{X} \sin \delta$$


$$= \frac{(1.2)(1.0)}{1.5} \sin 30^\circ$$

$$= \frac{1.2}{1.5} \times 0.5 = 0.4 \text{ p.u.}$$

$$\frac{dP_c}{d\delta} = \frac{EV}{X} \cos \delta = \frac{1.2 \times 1.0}{1.5} \cos 30^\circ = 0.712 \text{ p.u.}$$

$$P_{max} = \frac{EV}{X} = \frac{1.2 \times 1.0}{1.5} = 0.8 \text{ p.u.}$$

→ Practical case:

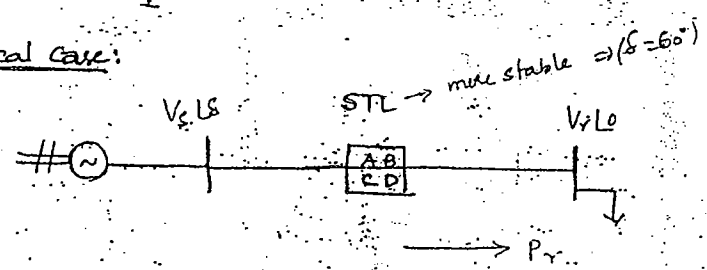

$$P_r = P_c = \frac{|V_s||V_r|}{|B|} \cos(\beta - \delta) - \frac{|A|}{|B|} V_r^2 \cos(\beta - \alpha)$$

$$P_s = \frac{|D|}{|B|} V_s^2 \cos(\beta - \alpha) - \frac{|V_s||V_r|}{|B|} \cos(\beta + \delta)$$

For STL, $C \approx 0$ (shunt cap)

$$|A| = 1.0 \quad \beta = |\alpha|$$

$$\alpha = 0 \quad \beta = 0$$


$$P_c = \frac{|V_s||V_r|}{|Z|} \cos(0 - \delta) - \frac{1.0}{|Z|} V_r^2 \cos(0 - 0^\circ)$$

$P_c = P_{max} = \text{steady state stability limit at } \delta = 0$

(power angle = impedance angle)

→ The stability of the system, if it is connected to the tr. line is influenced by its impedance angle of the tr. line

$$P_{max} = \frac{|V_s| |V_r|}{|Z|} = \frac{1.0 |V_r| \cos \theta}{|Z|}$$

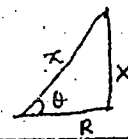

$$P_{max} = \frac{|V_s| |V_r|}{\sqrt{R^2 + X^2}} = \frac{1.0 |V_r|^2 X R}{\sqrt{R^2 + X^2}}$$

In order to maximize the steady state stability limit, the stability equation needs to be differentiated with respect to reactance of the m/w.

$$\frac{dP_{max}}{dx} = 0$$


$$X = \sqrt{3} R$$

$$\Rightarrow \frac{X}{R} = \sqrt{3}$$

$$\Rightarrow \theta = \tan^{-1}\left(\frac{X}{R}\right) = 60^\circ \rightarrow \text{So delivers max power for STL}$$

$$\therefore \theta = \delta = 60^\circ \rightarrow \text{more stable}$$

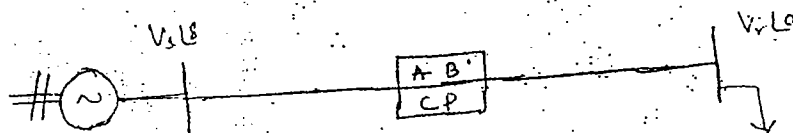→ However the alternators are normally connected with long lines.



$$P_r = P_e = \frac{|V_s| |V_r|}{|B|} \cos(\beta - \delta) - \left(\frac{A}{B}\right) |V_s|^2 \cos(\beta - \alpha)$$

if $\delta = \beta \Rightarrow P_e = P_{max} = \text{Steady state stability limit}$



$$P_{max} = \frac{|V_s| |V_r|}{|B|} - \frac{A}{B} |V_s|^2 \cos(\beta - \alpha)$$

$$\delta = \beta = \tan^{-1}\left(\frac{X}{R}\right) = 60^\circ$$

In long lines $X \uparrow$ and $R \downarrow$ in. $\theta = \tan^{-1}(\frac{X}{R})$

→ In case of long lines the $\frac{X}{R}$ ratio is high when compared to short line so that the impedance angle is almost equal to 90°

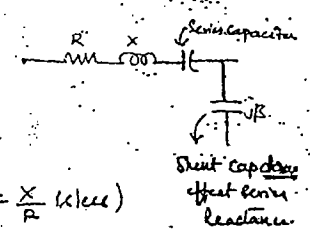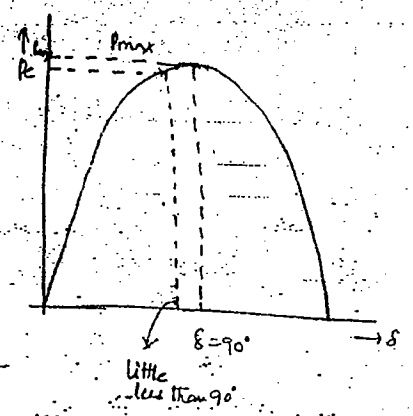→ If the alternator is connected to longline then it will be less stable when compared to STL and in order to improve the stability the $\frac{X}{R}$ ratio of the long line should be reduced by having a compensation to the LTL i.e. employing a suitable series capacitor



→ A LTL is a compensated line for stability purpose where as a STL is a uncompensated line (because $\frac{X}{R}$ is less)

$$P_e = \frac{|E||V|}{|X|} \sin \delta$$

$$= P_{max} \sin \delta$$

$$P_{max} = \text{Steady state stability limit} = \frac{|E||V|}{|X|}$$


→ For the given amount of power delivered if the steady state stability limit is high then the angle of the syn. m/c. will be less

→ Methods to improve the SSSL

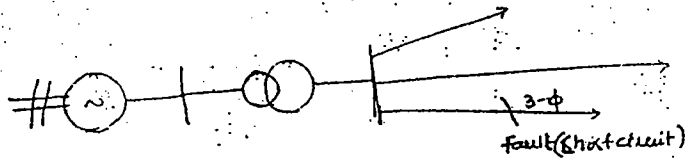- (1) Operate the system at higher operating voltages.
- (2) Reduce the reactance of the system.
 - (a) Parallel transmission lines
 - (b) Double CRT line
 - (c) Parallel capacitor
 - (d) Series capacitance

→ TRANSIENT STABILITY: It is the ability of the synchronous machine to deliver the maximum amount of real power to the load by the synchronous machine while maintaining the synchronization with the transmission line where the synchronous machine will experience a sudden and large variation of the load due to the occurrence of 3- ϕ short circuit fault on the transmission line for few cycles only.

∴ if the fault that can exist for more no. of cycles then there are chances to lose the synchronization by the synchronous machine.



Few cycles \Rightarrow Fault clearing time
 \downarrow
 (Relay time + C.B time) \leq 5 cycles

→ Assume

$$P_{e1} = \text{power transfer before fault} = P_{m1} \sin \delta_0$$

$$P_{e2} = \text{power transfer during fault} = P_{m2} \sin \delta$$



∴ In general $\boxed{P_{e2} < P_{e1}} \Rightarrow \underline{P_{m2} < P_{m1}}$

∴ \Rightarrow $\boxed{\text{Transient Stability Limit} < \text{Steady State Stability Limit}}$

SPECIAL CASES:


$$P_{e2} = 0, P_{m2} = 0$$

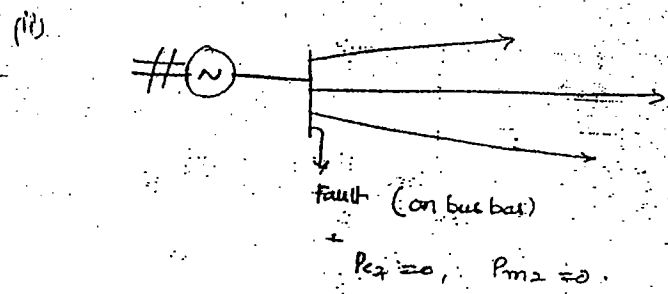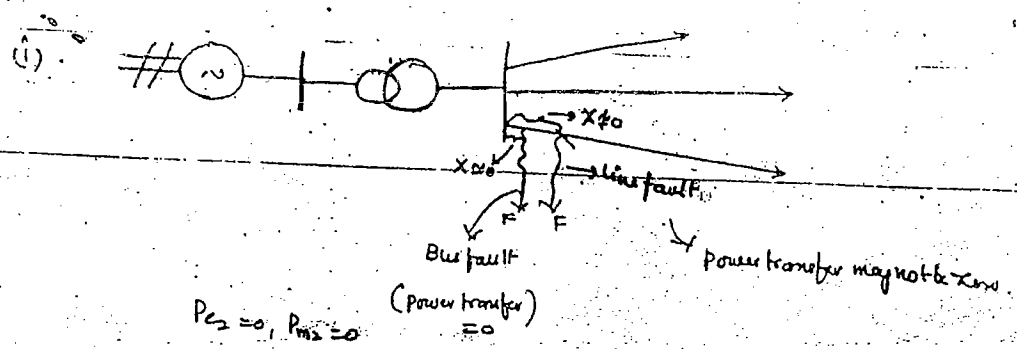(1) Fault occurs on a line near to bus bar



→ As the change of load is a sudden and large variation and it will reflect directly in changing the position of the rotor. The transient stability analysis can be made by considering the dynamic model of the rotating body i.e. the mechanical equivalent of the synchronous machine.

∴ Dynamic model: (Mechi equivalent)

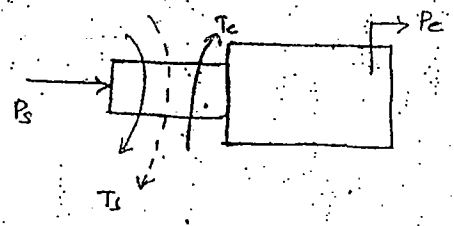

$\omega = \text{angular velocity rad/sec}$

Before fault

$$P = P_s - P_c = 0$$

$$\omega = \omega_s$$

The rotor neither accelerate nor decelerate but stability with some angle.

of a fault occurs

$$P = P_s - P_c$$

$$= +ve \Rightarrow \text{Acceleration (Rotor)}$$

$$\Rightarrow P_{acc} = P_s - P_r$$

$$\Rightarrow P_{acc} = T \omega \quad (\text{Torque} \times \text{angular velocity})$$

and $\omega \neq \omega_s$

$$\omega = \frac{2\pi N}{60}, \text{ where } N \text{ is speed in rpm.}$$

$$P_{acc} = I \alpha \omega \quad (T_d = I \alpha)$$

where $I = \text{Inertia } \text{kg-m}^2$

$\alpha = \text{Angular acceleration} = \text{rad/sec}^2$

$$P_{acc} = M \alpha$$

where $M = \text{Moment of Inertia (or) Angular momentum}$

\downarrow
J sec / Mech rad (Units)

But most of alternators are MVA capacity, so units of

$$M = \text{MJ-sec} / \text{Mech. rad.}$$

$$M = \text{MJ-sec} / \left(\frac{P}{2} \times \text{Mech. deg.} \right)$$


$$= \text{MJ-sec} / \text{Elec. rad.}$$

$$= \text{MJ-sec} / (57.11 \times \text{Elec. deg.})$$

$$M = \text{MJ-sec} / \text{Elec. degree}$$

$$\text{and } \alpha = \frac{d\omega}{dt} = \frac{d^2\theta}{dt^2} = \frac{d^2\delta}{dt^2}$$

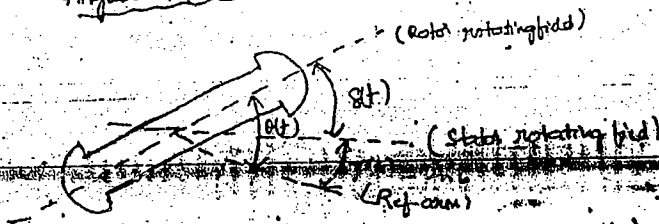But Angular displacement must be equal to Power angle




$$\theta(t) = \delta(t) + \omega_r t$$

$$\frac{d\theta(t)}{dt} = \frac{d\delta(t)}{dt} + \omega_r$$

$$\alpha = \frac{d^2\theta(t)}{dt^2} = \frac{d^2\delta(t)}{dt^2} + 0$$

→ The change of load will result as the change in the position of the rotor w.r.t stator, where as the position of the stator remains same w.r.t reference axis. hence the relative speed is zero.

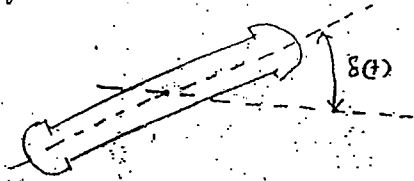∴ No separate reference axis is required, as stator axis itself is a reference axis.



$$M \alpha = P_s - P_e$$


$$M \frac{d^2\delta(t)}{dt^2} = P_s - P_e$$

$$\Rightarrow \frac{M d^2\delta(t)}{dt^2} = P_s - \frac{E V}{X} \sin \delta$$

→ Swing equation of the rotating body

- The swing equation is a non-linear differential equation.
- The swing equation describes the position of the rotor w.r.t stator having the function of time for specified no. of cycles in which the sy. m/c is experiencing a disturbance.

(P.T.O)

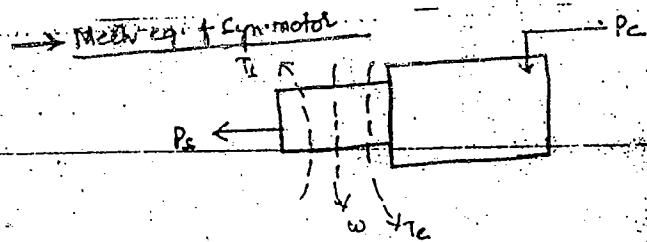


$$M \frac{d^2\theta}{dt^2} = P_e - P_s$$

$$\Rightarrow \boxed{M \frac{d^2\theta}{dt^2} = \frac{E V}{X} \sin\delta - P_s}$$

*+ Consider to know the frequency of oscillations made by the rotor for a small and gradual variation of the load, the solution of the swing equation is required.

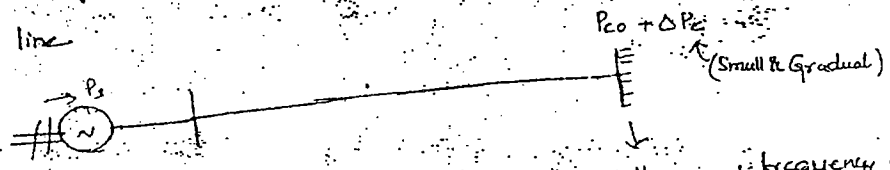Application: Synchronous Generator is connected to an infinite bus through a lossless line



An infinite bus is the one at which the voltage and frequency are constant.

Convert the non-linear differential equation into a linear differential equation by using the Taylor series expansion.


At 'a', $P_s = P_{e0} = P_m \sin\delta_0$

$$\delta_0 = \sin^{-1}\left(\frac{P_s}{P_m}\right)$$

$$M \frac{d^2\delta}{dt^2} = P_a$$

$$M \frac{d^2(\delta_0 + \Delta\delta)}{dt^2} = P_s - (P_{e0} + \Delta P_e)$$

↓ linear differential equation

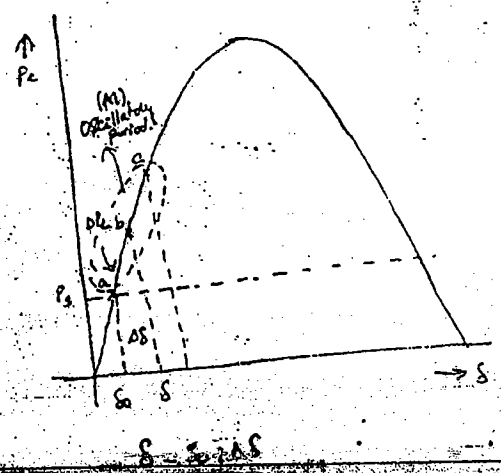

$$M \frac{d^2}{dt^2} \Delta \delta = -\Delta P_e = -\left. \frac{\partial P_e}{\partial \delta} \right|_{\delta_0} \Delta \delta$$

$$\Rightarrow M \frac{d^2}{dt^2} \Delta \delta + \left. \frac{\partial P_e}{\partial \delta} \right|_{\delta_0} \Delta \delta = 0$$

Let $\frac{d}{dt} = k$


$$\left[Mk^2 + \left. \frac{\partial P_e}{\partial \delta} \right|_{\delta_0} \right] = 0$$

$$k = \pm \left[\frac{1}{M} \left(-\left. \frac{\partial P_e}{\partial \delta} \right|_{\delta_0} \right) \right]^{1/2} \text{ rad/sec}$$

Case 1: $\frac{\partial P_e}{\partial \delta} = \frac{EV \cos \delta}{x} = +ve$; when $\delta_0 < \pi/2$


The nature of the roots of the equation are imaginary but undamped oscillations.

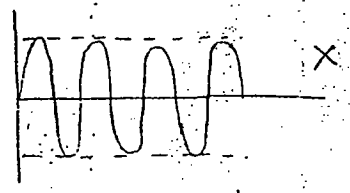The moment of inertia of the system is very high and the change of load is very small



and the magnitude of the oscillations are very less

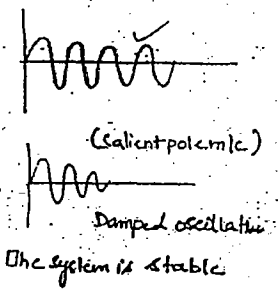→ In case of salient pole alternator because of damper winding the ^{magnitude} frequency of oscillations tend to decrease after few cycles.



→ But in Turbo alternator, because of its large size the oscillations are negligible

The system is stable.


∴ The frequency of oscillations in Hz is given by

$$k = \pm \frac{\left(\frac{1}{M} \left(-\left. \frac{\partial P_e}{\partial \delta} \right|_{\delta_0} \right) \right)^{1/2}}{2\pi} \text{ Hz}$$

Case (2): $\frac{\partial P_e}{\partial \delta} = \frac{EV}{X} \cos \delta = -ve$ when $\delta_0 > \frac{\pi}{2}$

$K = \text{Real roots} \rightarrow$ The s.p.m.c is unstable

(Q) 4) Pg. 63 material:

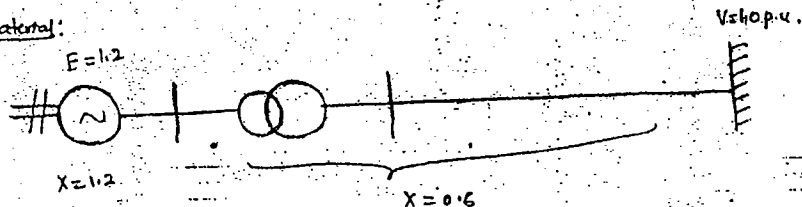

$$H = 4 \text{ MW-sec/MVA}$$

$$= 4 \text{ MJ/MVA}$$

$$P_s = P_e = P_m \sin \delta_0$$

$$0.8 P_m = P_m \sin \delta_0$$

$$\delta_0 = \sin^{-1}(0.8)$$

$$= 53.13$$

$$\frac{\partial P_e}{\partial \delta} = \frac{EV}{X} \cos \delta$$

$$\left. \frac{\partial P_e}{\partial \delta} \right|_{\delta_0} = \frac{1.2 \times 1.0}{1.8} \times \cos(53.13)$$

$$= 0.4$$

(Roots are imaginary)


$$K = \left[\frac{1}{M} \left(-\left. \frac{\partial P_e}{\partial \delta} \right|_{\delta_0} \right) \right]^{1/2}$$

$$= \left[\frac{1}{\frac{5H}{\pi f}} (0.4) \right]^{1/2}$$

$$= \left[\frac{1}{\frac{1.0 \times 4}{3.14 \times 50}} \times 0.4 \right]^{1/2}$$

$$= 3.96 \text{ rad/sec}$$

$$= 0.63 \text{ Hz}$$

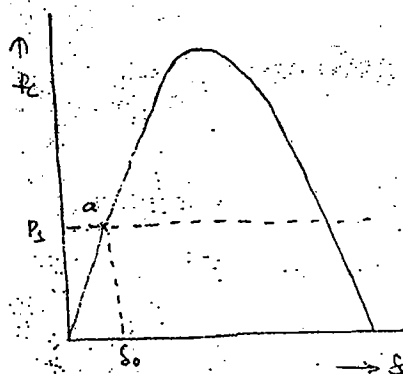


→ TRANSIENT STABILITY: The stability concept can be analyzed by knowing the solution for the swing equation

$$M \frac{d^2 \delta}{dt^2} = P_a$$


The solution for swing equation depends on no. of Syn. m/c. present

- (1) Single machine system
- (2) Two machine system
- (3) Multimachine system.

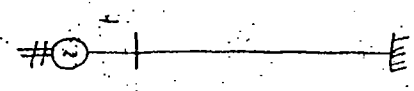
(1) Single machine system: A syn generator connected to infinite bus is called single m/c system.



(2) Two machine system:

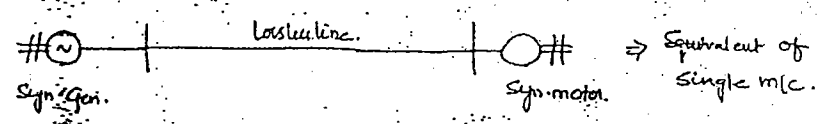

(3) Multimachine system:

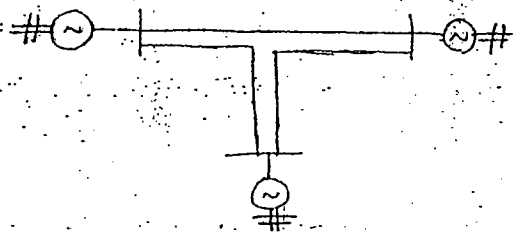

→ For single machine system, the solution can be obtained by Elliptical Integral.


→ For two machine system, the graphical solution, called EQUAL AREA CRITERIA

→ For Multimachine system, the solution can be obtained by "Point by Point" or "Step by step" method.

→ In a two machine system the synchronous generator is connected to the synchronous motor through a lossless line and for the stability point

of view it is equivalent to a single machine because for the

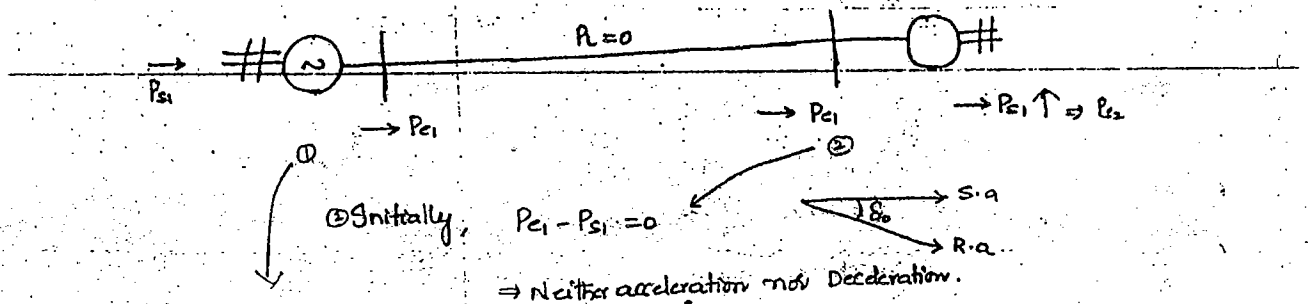
machines are stable (or) unstable at any point of time.



① Initially


$$P_{s1} - P_{c1} = 0$$

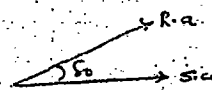Neither acceleration nor deceleration. \Rightarrow



(2) $P_c = P_{s1} - 0$

\Rightarrow accelerated.

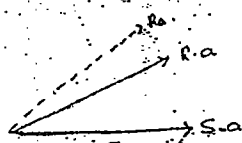


\rightarrow Due to the acceleration of syn/gen the frequency of oscillations are more than the natural frequency of the system, so that the syn generator will also be pulled out.

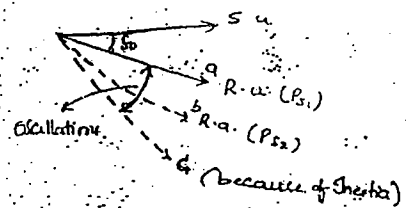(2) If there is sudden and large variation

$$P = P_{c1} - P_{s2}$$

$$= -V_c \cdot (\text{Deceleration of rotor})$$



\rightarrow If the frequency of the oscillations made by syn motor are much more than that of natural frequency due to sudden and large variation of load, then the syn motor will be pulled out from the synchronization.

\rightarrow If the motor is desynchronized then the electrical output delivered by syn/gen is zero. So that the generator will get accelerated.

\rightarrow The Equal area Criteria is also applicable for the synchronous generator connected to infinite bus.

→ We know that


$$M \frac{d^2\delta}{dt^2} = P_e - \frac{P_m \sin \delta}{P_e}$$

→ Calculation of the maximum power transfer (Transient stability limit)

Which is constant during the fault condition even though the real power transfer varies

→ Consider the +ve sequence reactance n/w for the given single line diagram with the following assumptions.

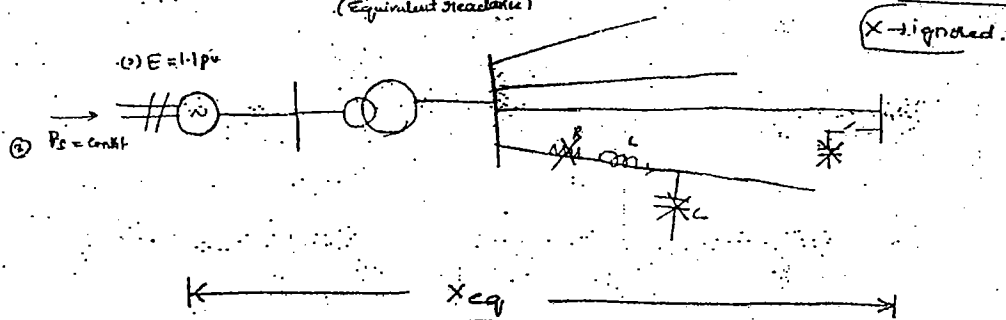- (1) $R \ll X$, line shunt capacitance can be ignored and any external shunt elements can also be ignored, then the exciting network can be modelled as the transfer reactance b/w the source and the load (Equivalent reactance)




- (2) The voltages behind the reactances of the system are assumed as constant because the amount of power transfer does influence severely by the transfer reactance of the system rather than voltages.

- (3) The mechanical i/p of the sy/mic is mechanical same & constant.

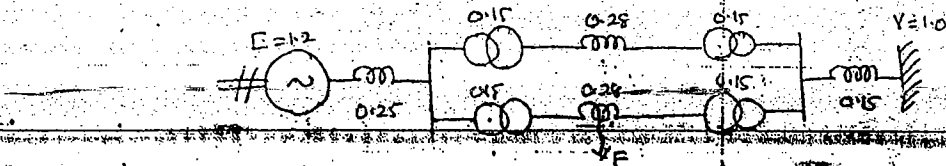- (4) The force produced by the damper wdg on the rotor can be ignored

→ Q(5) Pg: 67. Calculate the P_{max} before fault, during fault & after the fault.



Sol/tet $P_{e1} = \text{power transfer before fault} = \frac{EV}{X_{1eq}} \sin \delta_0 = P_{m1} \sin \delta_0$

$P_{e2} = \text{power transfer during fault} = \frac{EV}{X_{2eq}} \sin \delta = P_{m2} \sin \delta$

$P_{e3} = \text{power transfer after fault} = \frac{EV}{X_{3eq}} \sin \delta = P_{m3} \sin \delta$

where

$P_{m1} = \text{Max. power transfer before fault}$

$P_{m2} = \text{Max. power transfer during fault}$

$P_{m3} = \text{Max. power transfer after fault}$

and: $X_{1eq} = \text{transfer reactance before fault occurs}$

$X_{2eq} = \text{transfer reactance during fault}$

$X_{3eq} = \text{transfer reactance after fault}$

But $\rightarrow P_{m2} = \frac{EV}{X_{2eq}} = \frac{EV}{X_{1eq}} \cdot \frac{X_{1eq}}{X_{2eq}} = \gamma_1 P_{m1}$

where $\gamma_1 = \frac{X_{1eq}}{X_{2eq}} < 1.0$

$P_{m3} = \frac{EV}{X_{3eq}} = \frac{EV}{X_{1eq}} \cdot \frac{X_{1eq}}{X_{3eq}} = \gamma_2 P_{m1}$

where $\gamma_2 = \frac{X_{1eq}}{X_{3eq}} < 1.0$

But $\gamma_2 > \gamma_1$

\rightarrow If the fault is considered in the line at any line length, then the relation is Middle 20% (b) 50% (c) 80%...

is $P_{m2} < P_{m3} < P_{m1}$


$\therefore P_{m1} = \frac{EV}{X_{1eq}} = \frac{1.2 \times 1.0}{0.25 + \frac{0.58}{2} + 0.15} = 1.739 \text{ P.U.}$

$P_{m2} = \frac{EV}{X_{2eq}} = \frac{1.2 \times 1.0}{X_{2eq}} = ?$


$$P_{m3} = \frac{EV}{X_{2eq}} = \frac{1.2 \times 1.0}{0.25 + \frac{0.58}{2} + 0.15} = 1.224 \text{ p.u.}$$

→ Calculation of X_{2eq} :

(3) 'F' is at middle)

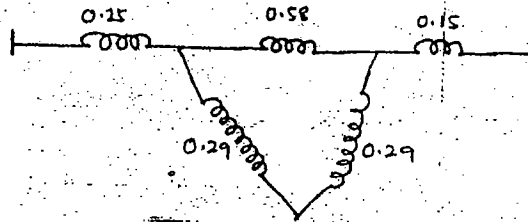




Convert Δ in. to Y

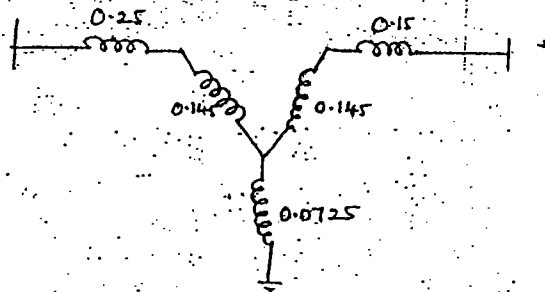

$$\Delta - Y$$

$$\frac{0.58 \times 0.29}{0.58 + 0.29 + 0.29}$$

$$= 0.145$$

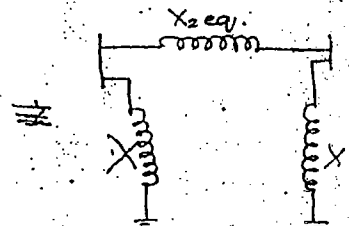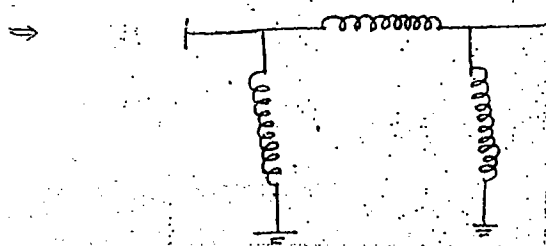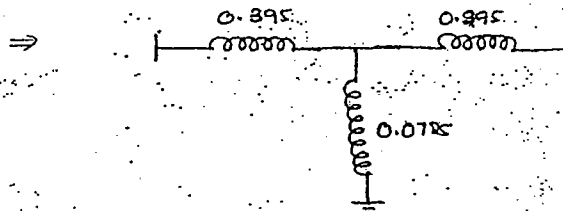

X (signed according to assumptions)

$$X_{2eq} = 0.395 + 0.295 + \frac{0.395 \times 0.295}{0.0725}$$

$$= 2.29 \text{ p.u.}$$

$$P_{m2} = \frac{EV}{X_{2eq}} = \frac{1.2 \times 1.0}{2.29} = 0.52 \text{ p.u.}$$

Special Case (1) Fault occurs on a line near to Bus bar.

$$P_{m1} = \frac{E_V}{X_{1eq}} = \frac{1.2 \times 1.0}{0.25 + \frac{0.58}{2} + 0.15} = 1.739 \text{ p.u.}$$

$$P_{m2} = 0 \quad (\text{during fault max power transfer to load} = 0)$$

$$P_{m3} = \frac{E_V}{X_{3eq}} = \frac{1.2 \times 1.0}{0.25 + 0.58 + 0.15} = 1.224 \text{ p.u.}$$

(2) Fault occurs on bus bar.

$$P_{m1} = \frac{E_V}{X_{1eq}} = \frac{1.2 \times 1.0}{0.25 + \frac{0.58}{2} + 0.15} = 1.739 \text{ p.u.}$$

$$P_{m2} = 0, \quad (\text{since } P_{e2} = 0)$$

$$P_{m3} = P_{m1} = \frac{1.2 \times 1.0}{0.25 + \frac{0.58}{2} + 0.15} = 1.739 \text{ p.u.}$$


In the above two cases, the alternator is considered to be working under no load condition, which is not acceptable for more no. of cycles. Hence the C.B. should be closed at faster rate.

$$\therefore P_{m3} = P_{m1} \quad \text{but} \quad P_{e3} \neq P_{e1} \quad (\because \delta \text{ is not same})$$

→ If a fault occurs on bus bar then the alternator is isolated from the parallel to lines which will result as the no load operation of the alternator.

→ In order to avoid the no load operation of the alternator for more no. of cycles, it can be assumed that the breaker is closed at faster rate the entire m/w will be restored. Hence $P_{m2} = P_{m1}$

Ideal Case

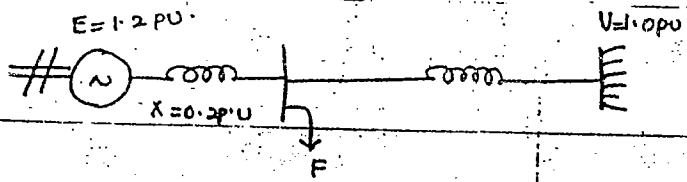

$$P_{m1} = \frac{1.2 \times 1.0}{0.5} \text{ pu} = 2.4 \text{ pu}$$


$$P_{m2} = 0 \quad P_{e2} = 0$$

$$P_{m3} = P_{m1} = \frac{1.2 \times 1.0}{0.5} = \frac{1.2 \times 1.0}{0.5} \text{ pu} = 2.4 \text{ pu}$$

SWINGING OF THE TWO MACHINES

For any change of load, if it reflect in changing the position of rotor axes of both the machines then the two machines are swinging together.

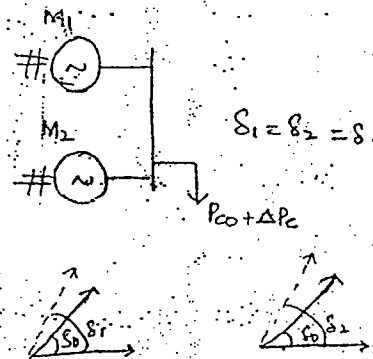(or) For any change of load, if it will be shared by both the machines then the two machines are swinging together.



$$P_{eq} = P_{e1} + P_{e2}$$



$$= M_1 \frac{d^2 \delta_1}{dt^2} + M_2 \frac{d^2 \delta_2}{dt^2}$$

$$M_{eq} \frac{d^2 \delta}{dt^2} = (M_1 + M_2) \frac{d^2 \delta}{dt^2}$$

$$M_{eq} = M_1 + M_2$$

For n-machine system, $M_{eq} = M_1 + M_2 + \dots + M_n$

→ TWO MACHINES DONOT SWINGING TOGETHER!

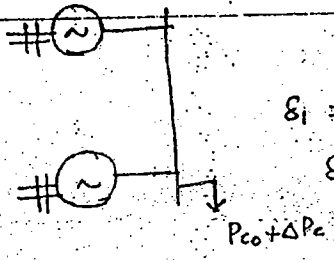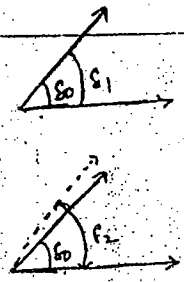

$$\delta_1 \neq \delta_2$$

$$\delta = \delta_2 - \delta_1$$

For any change of load, if it reflects in changing the position of the rotor axis of any one of the machine, then the two machines are donot swinging together. (x)

If the change of load can only shared by only one of the machine then the two machines are donot swinging together

$$\therefore \delta = \delta_2 - \delta_1$$

$$\frac{d^2\delta}{dt^2} = \frac{d^2\delta_2}{dt^2} - \frac{d^2\delta_1}{dt^2}$$

$$= \frac{P_{s2} - P_{e2}}{M_2} - \frac{P_{s1} - P_{e1}}{M_1}$$

$$\frac{d^2\delta}{dt^2} = \frac{P_{s2} - P_{e2}}{M_2} - \frac{P_{s1} - P_{e1}}{M_1} \rightarrow (1)$$

Eq (1) has to become

$$P_{aeq} = P_{seq} - P_{eeq}$$

Multiply on both sides of equation by $\frac{M_1 M_2}{M_1 + M_2}$

$$\frac{M_1 M_2}{M_1 + M_2} \frac{d^2\delta}{dt^2} = \frac{M_1 M_2}{M_1 + M_2} \left[\frac{P_{s2} - P_{e2}}{M_2} - \frac{P_{s1} - P_{e1}}{M_1} \right]$$

$$\frac{M_1 M_2}{M_1 + M_2} \frac{d^2\delta}{dt^2} = \left[\frac{M_1 P_{s2} - M_2 P_{e1}}{M_1 + M_2} \right] - \left[\frac{M_1 P_{e2} - M_2 P_{s1}}{M_1 + M_2} \right]$$

$$P_{aeq} = M_{eq} \frac{d^2\delta}{dt^2}$$

$$\therefore M_{eq} = \frac{M_1 M_2}{M_1 + M_2}$$

$$\frac{1}{M_{eq}} = \frac{1}{M_1} + \frac{1}{M_2}$$

For n-machine system.

$$\frac{1}{M_{eq}} = \frac{1}{M_1} + \frac{1}{M_2} + \dots + \frac{1}{M_n}$$

- In order to maintain the transient stability on a common bus bar where more than one synchronous machine is connected then it is preferred to allow the swinging of the two machines.
- For a given accelerating power, there will be a slow rate of change of rotor angle if the moment of inertia will be high.

$$M \frac{d^2\delta}{dt^2} = P_a$$


$$\frac{d^2\delta}{dt^2} = \frac{P_a}{M}$$

- The swinging of the machines can be possible provided that the machines which are connected to common bus are of identical rating. Else inert.

- The inertia of the synchronous machine can also be expressed in the form of Inertia Constant.

$$\begin{aligned} \text{Inertia Constant (H)} &= \frac{\text{K.E. Stored in rotor}}{\text{Rating of the machine}} \quad \text{MJ/MVA} \\ &= \frac{\frac{1}{2} I \omega^2}{S} = \frac{\frac{1}{2} I \omega \cdot \omega}{S} = \frac{\frac{1}{2} M \times \omega^2}{S} \end{aligned}$$

$$M = \frac{SH}{180f} \text{ degree.}$$

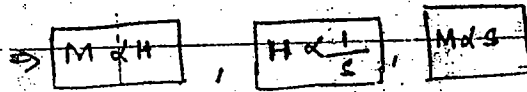

$$\propto H_{eq} = H_1 + H_2 + \dots + H_n \rightarrow \text{Swinging together}$$

$$\frac{1}{H_{eq}} = \frac{1}{H_1} + \frac{1}{H_2} + \dots + \frac{1}{H_n} \rightarrow \text{Don't swinging together}$$

Ex: Gen-1, \rightarrow Capacity S_1 and H_1 Inertia Constant = ?
 Gen-2 \rightarrow Capacity S_2 and H_2

Sol: In order to maintain the swinging of the two machines, then the two machines will brought to a common base.

Let Common base $\rightarrow S_b$

$$H_{1 \text{ new}} = \frac{H_{1 \text{ old}} S_b}{S_1}$$

$$H_{2 \text{ new}} = \frac{H_{2 \text{ old}} S_b}{S_2}$$

$$H_{eq} = H_{1 \text{ New}} + H_{2 \text{ New}}$$

EQUAL AREA CRITERIA

(i) It gives the solution for swing equation; in a graphical manner

(ii) The Net area covered by the synchronous m/c during the first swing b/w the two swinging points will be ZERO (cs).

The area covered during acceleration by the syn m/c will be same as the area covered during deceleration of the first swing.

Reference equation to prove (ii) is

$$M \frac{d^2\delta}{dt^2} = P_a$$

Multiply both sides with $2 \frac{d\delta}{dt}$ and integrate w.r.t dt

$$\int M \frac{d^2\delta}{dt^2} \cdot 2 \frac{d\delta}{dt} dt = \int P_a \cdot 2 \frac{d\delta}{dt} dt$$



Mathematically



$$\int \frac{d}{dt} M \left(\frac{d\delta}{dt} \right)^2 = 2 \int P_a \frac{d\delta}{dt} \times dt \quad \left(\because P_a = P_e - P_m \right)$$

$$= \underbrace{P_e - P_m}_{\text{center}} \int d\delta$$

$$\frac{d\delta}{dt} = \left[\frac{2}{M} \int P_a d\delta \right]^{1/2}$$

The above expression should be proved, equal to ZERO

For a m/c

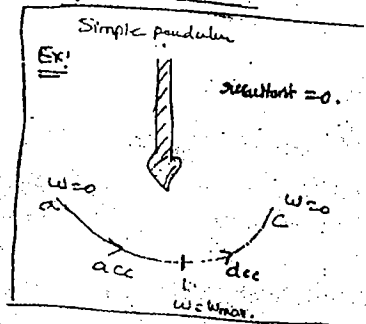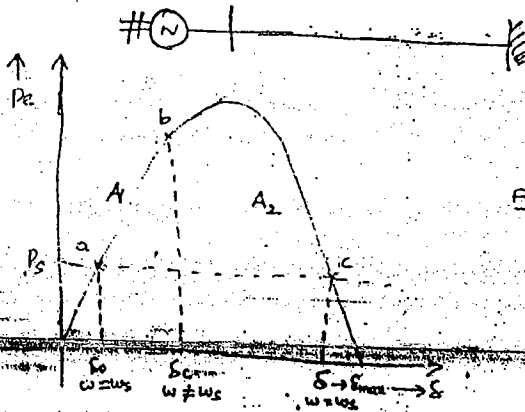

From above eq

$$\left(\frac{d\delta}{dt} \right) \Big|_{\delta_0} = 0$$

$$\left(\frac{d\delta}{dt} \right) \Big|_{\delta} = 0$$

$$\therefore \frac{d\delta}{dt} = \left[\frac{2}{M} \int_{\delta_0}^{\delta} P_a d\delta \right]^{1/2}$$

$$\Rightarrow \int_{\delta_0}^{\delta} P_a d\delta = 0$$

(iii) The equal area criteria provides the critical clearing angle made by the syn m/c at the time of fault cleared by circuit breaker.

(iv) Consider the first swing for the stability analysis

(a) if $A_1 < A_2 \rightarrow$ Stable.

(b) if $A_1 = A_2 \rightarrow$ Critically Stable

(c) if $A_1 > A_2 \rightarrow$ Unstable

A_1, A_2 (from power angle curve)

(v) Even though δ_{max} is more than 90° , in order to get $\omega = \omega_s$ during the first swing but there are chances to maintain the stability because it is the area comparison but not the angle comparison.

(vi) If the synchronous m/c is stable during the first swing it could be also stable during the subsequent swings.

(vii) In Equal Area criteria it is unable to convert the critical clearing angle

(δ_c) made by the breaker into critical clearing time

\rightarrow Applications:

(1) A sudden increased mechanical i/p to the synchronous generator

(2) A sudden increased mechanical o/p on synchronous motor

(3) Fault occurs at the middle of the tr. line in a parallel transmission system

(4) Fault occurs on a line near to busbar, in a parallel transmission system

(5) Fault occurs on a bus bar in a parallel transmission system

(6) Fault occurs on an alternator connected to infinite bus through a lossless line

(7) Removal of one of the parallel tr. line by using fault acting circuit breaker forcibly

→ ASSUMPTIONS FOR EQUAL AREA CRITERIA:


(i) $P_a = 0$ and $\omega = \omega_s$ then there is no change in the rotor angle at that position

(ii) $P_a \neq 0$ but $\omega = \omega_s$ (or) $P_a = 0$ but $\omega \neq \omega_s$, then the rotor angle will change (\uparrow or \downarrow)

(iii) Consider the effect of moment of inertia while explaining the Equal Area Criteria


Applications

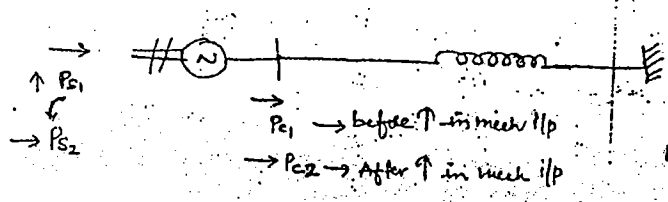1) A sudden increase in mechanical ip to the synchronous m/c.




$$P_{e1} = \frac{EV}{X_{eq}} \sin \delta_0$$
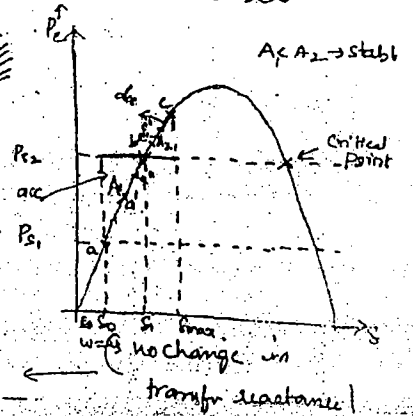
$$P_{e2} = \frac{EV}{X_{eq}} \sin \delta = \frac{EV}{X_{eq}} \sin \delta$$



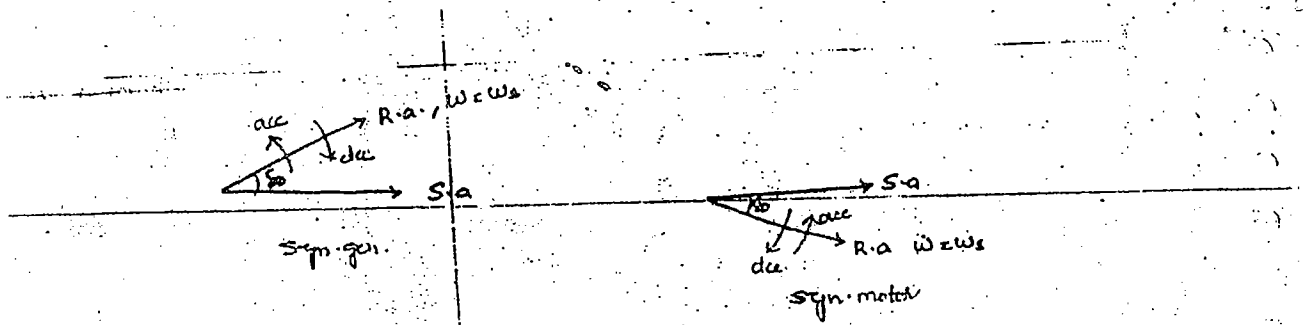$\omega = \omega_s$
 $\omega_{max} = \omega_s$
 $\omega_{min} = \omega_s$



→ Initially the syn. generator is supplied with a mech. i/p of P_{s1} and electrical o/p of P_{e1} . It is represented by point 'a' on power angle curve.

→ If the mechanical i/p is suddenly increased from P_{s1} to P_{s2} where P_{e1} there is no change in electrical o/p because the reactance of the system is same and due to large moment of inertia there is no sudden change in the rotor angle.

$$\begin{aligned} \text{Hence } P &= P_{s2} - P_{e1} \quad (\because \text{Angle not changing, } X \text{ not changing}) \\ &= +ve \\ &= \text{acceleration} \Rightarrow \underline{W > W_s} \end{aligned}$$

→ Due to the relative speed of the synchronous m/c b/w the actual speed and the syn. speed there is change in rotor position.

⇒ Rotor angle will increase slowly.

→ The excess mech. i/p will be stored in the rotor in the form of kinetic energy.

→ The angle will ↑ beyond 'b' in order to get $W = W_s$ in a condition

that the electrical o/p must be more than mech. i/p. Further it should also fulfill that the area which is covered beyond 'b' should be equal to the area which is already covered from 'a' to 'b'.

→ The limiting point can be assumed as 'c'.

→ The K.E. stored in the rotor will be converted into electrical i/p.

	Power	Property	Speed	Remarks/obs
→ At 'a'	$P = P_{s1} - P_{c1}$ $= 0$	Neither acceleration nor deceleration	$\omega = \omega_s$	δ doesn't change
→ 'a' to 'b'	$P = P_{s2} - P_{c2}$ $= P_{s2} - \frac{EV}{X_{2eq}} \sin \delta$ $X_{2eq} = X_{1eq}$ and $(\delta > \delta_0)$ $= +ve$	Acceleration	$\omega > \omega_s$	δ will ↑ slowly
→ At 'b'	$P = P_{s2} - P_{c2}$ $= P_{s2} - \frac{EV}{X_{2eq}} \sin \delta_1$ $= 0$	Neither Acc (at) Deceleration	$\omega = \omega_{max} > \omega_s$	According to (i) & (ii) assumption of equal area criteria the angle will ↑
→ 'b' to 'c'	$P = P_{s2} - P_{c2}$ $= P_{s2} - \frac{EV}{X_{2eq}} \sin \delta$ $\delta > \delta_1$	Deceleration	$\omega < \omega_{max}$ phase but $\omega > \omega_s$	δ will further ↓
→ At 'c'	$P = P_{s2} - P_{c2}$ $= P_{s2} - \frac{EV}{X_{2eq}} \sin \delta_{max}$	deceleration	$\omega = \omega_s$	The angle δ starts decreasing
→ 'c' to 'b'	$P = P_{s2} - P_{c2}$ $= P_{s2} - \frac{EV}{X_{2eq}} \sin \delta$ $(\delta < \delta_{max})$	deceleration	$\omega < \omega_s$	The δ ↓
→ At 'b'	$= -ve$ $P = P_{s2} - P_{c2}$ $= P_{s2} - \frac{EV}{X_{2eq}} \sin \delta$ $= 0$	Neither deceleration nor acceleration	$\omega = \omega_{min} < \omega_s$	Due to 2nd & 3rd assumption of E.A.C the initial angle will continue ↓
→ 'b' to 'a'	$P = P_{s2} - P_{c2}$ $= P_{s2} - \frac{EV}{X_{2eq}} \sin \delta$ $+ve (\delta < \delta_1)$	Acceleration	$\omega > \omega_s$	δ further ↓

⇒ Even though the synchronous m/c is swinging, there will be relatively change in rotor angle after completing each swinging.


For first swing taken into consideration

$$A_1 < A_2 \rightarrow \text{Stable}$$


$$= +V_c \quad \uparrow$$

→ If $\omega = \omega_s$ is obtained before the critical point of the curve then the synchronous machine is stable

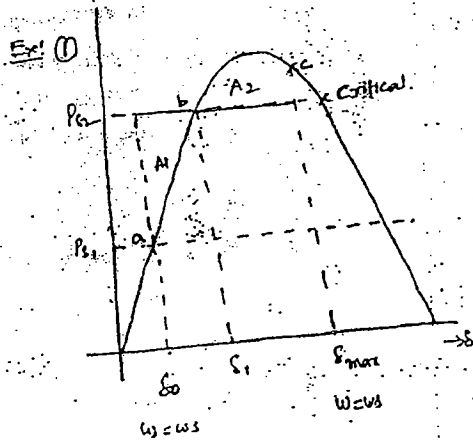
→ ** After completing the first swing the point is at 'b' the $\omega = \omega_s$


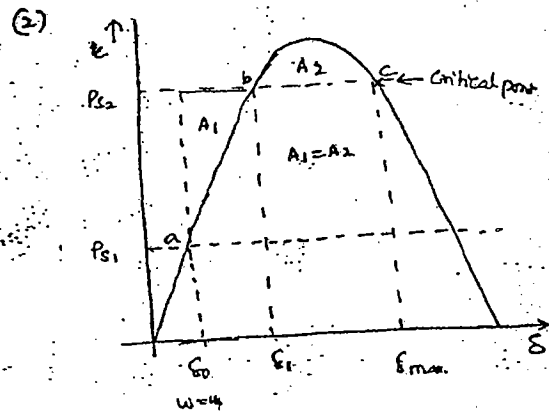
$$\Rightarrow A_1 < A_2 \rightarrow \text{Stable}$$


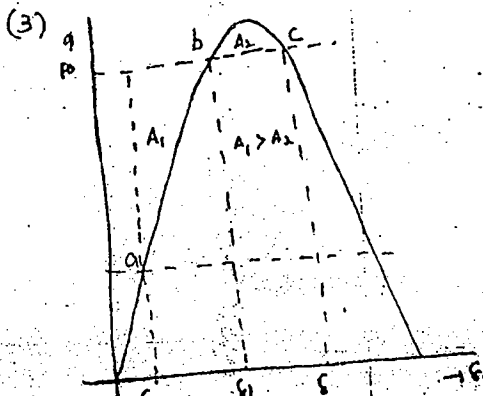
$$\Rightarrow A_1 = A_2 \rightarrow \text{Critically Stable}$$




$$A_1 > A_2 \Rightarrow \text{Unstable}$$


→ The purpose of the equal area criteria is to calculate critical clearing angle made by rotor at the time of fault cleared by CB by considering critically stable condition.

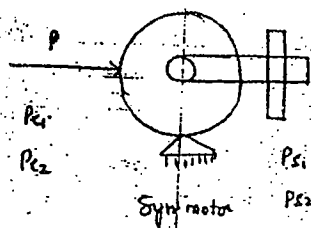(ii) Sudden increase in the mechanical input of the syn. motor.

The Equal Area Criteria of a synchronous motor is a mirror image to that of generator.



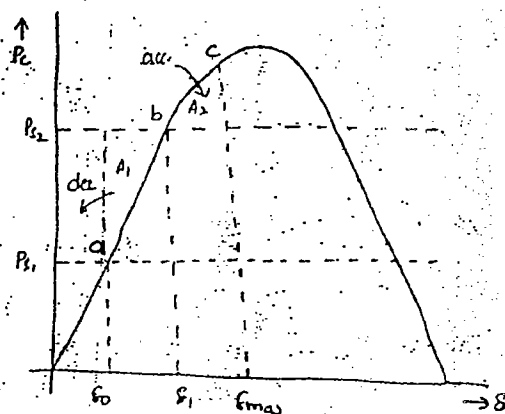→ Initially the syn. motor is supplied with an electrical input P_{e1} and the corresponding mech. input P_{s1} . It is represented by point 'a'.



→ The mech. input on the motor is suddenly ↑

where as there is no change in the electrical input because the reactance of the motor is same and there is no sudden change in the rotor angle due to large moment of inertia.

$$P = P_{e1} - P_{s1}$$

$$F = -V_e$$

deceleration

$$\omega < \omega_s$$

→ Due to relative speed of syn. motor the rotor angle will slowly increase.

At 'a' $P = P_{e1} - P_{s1}$
 $= \frac{EV \sin \delta_0}{X_{eq}} - P_c$
 Neither Acc nor decelerate $\omega = \omega_s$ & does not change

'd to 'b' $P = P_{e1} - P_{s1}$
 $= -V_c$
 Deceleration $\omega < \omega_s$


b
 b to c

c to b

b

b to a

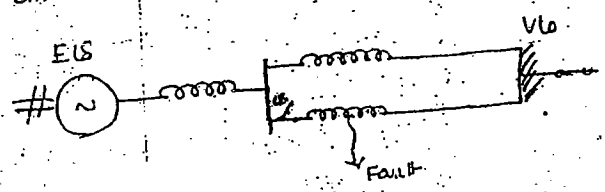(3) Fault occurs in the middle of the tr. line in parallel Tr. System.



$$P_{e1} = P_{m1} \sin \delta$$


$$P_{e2} = P_{m2} \sin \delta$$

$$P_{e3} = P_{m3} \sin \delta$$

$$P_{m2} < P_{m3} < P_{m1}$$

Initially the Syp. generator is supplied with mech llp of P_s and the corresponding obj of P_{e1} .
 It is represented by point 'a' on P_e curve.

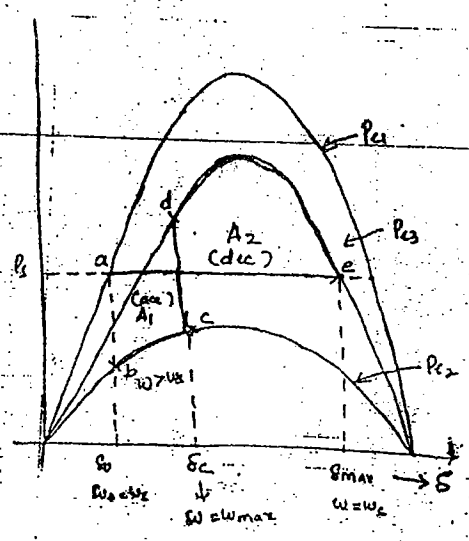A B-C fault has taken place at the middle of the tr. line so that the electrical otp is reduced suddenly due to change in the reactance of the m/w even though there is no sudden change in the rotor angle. It is represented by point 'b' on P_{e2} curve. However the mech. ip remain same. Hence



$$P = P_s - P_{e2}$$

$$= P_s - \frac{EV}{X_{2eq}} \sin \delta_0$$

$$= +ve \rightarrow \text{acceleration of rotating body. and } \omega > \omega_s$$

At 'a'

$$P = P_s - P_{e1}$$

$$= P_s - \frac{EV}{X_{2eq}} \sin \delta_0$$

$$= +ve$$

Acceleration $\omega = \omega_s$ & does not change

'b' to 'c'

$$P = P_s - P_{e2}$$

$$= P_s - \frac{EV}{X_{2eq}} \sin \delta$$

$$\Rightarrow (\delta > \delta_0)$$

$$= +ve$$

Acceleration $\omega > \omega_s$ & will slowly

'd' to 'e'

$$P = P_s - P_{e1}$$

$$= P_s - \frac{EV}{X_{2eq}} \sin \delta$$

$$(\delta > \delta_c)$$

$$= -ve$$

Deceleration $\omega < \omega_{max}$ but $\omega > \omega_s$ & will further increase

Calculation of δ_c

$$\int_{\delta_0}^{\delta_{max}} P_a d\delta = 0 = \int_{\delta_0}^{\delta_c} P_a d\delta + \int_{\delta_c}^{\delta_{max}} P_a d\delta = 0$$

$$= \int_{\delta_0}^{\delta_c} (P_s - P_{m2}) d\delta + \int_{\delta_c}^{\delta_{max}} (P_s - P_{m3}) d\delta = 0$$

$$= \int_{\delta_0}^{\delta_c} (P_s - P_{m2} \sin\delta) d\delta + \int_{\delta_c}^{\delta_{max}} (P_{m3} \sin\delta - P_s) d\delta \quad \rightarrow \text{(Critical angle theory)}$$

→ Due to relative speed the rotor angle will slowly increase
 → It can be assumed that the angle will ↑ slowly till the fault is cleared by the breaker after few cycles.

→ It can be assumed that the fault is cleared at 'c' and the angle corresponding to that is called " δ_c (Critical clear angle)"

→ When the fault is cleared by the breaker, the faulty line is isolated and the alternator will deliver the electrical o/p with another healthy line. The electrical o/p is suddenly increased due to change in the reactance of the m/w even though the rotor angle is same.

- It is represented by point 'd' on P_{s3} curve where as the mech i/p to the system is same. Due to moment of inertia of the rotating body the angle will ↑ further in order to get $\omega = \omega_c$ in a critical stable manner.

$$\int_{\delta_0}^{\delta_{max}} P_a d\delta = \int_{\delta_0}^{\delta_c} (P_s - P_{m2} \sin\delta) d\delta = \int_{\delta_c}^{\delta_{max}} (P_{m3} \sin\delta - P_s) d\delta$$

$$\Rightarrow \left[P_s \delta + P_{m2} \cos\delta \right]_{\delta_0}^{\delta_c} = \left[-P_{m3} \cos\delta - P_s \delta \right]_{\delta_c}^{\delta_{max}}$$

$$\Rightarrow P_s \delta_c - P_s \delta_0 + P_{m2} \cos\delta_c - P_{m2} \cos\delta_0 = -P_{m3} \cos\delta_{max} + P_{m3} \cos\delta_c - P_s \delta_{max} + P_s \delta_c$$

$$P_s \sin \delta_{max} - P_s \sin \delta_0 + P_{m3} \cos \delta_{max} - P_{m2} \cos \delta_0 = P_{m3} \cos \delta_c - P_{m2} \cos \delta_c$$

$$P_s (\delta_{max} - \delta_0) + P_{m3} \cos \delta_{max} - P_{m2} \cos \delta_0 = (P_{m3} - P_{m2}) \cos \delta_c$$

$$\delta_c = \cos^{-1} \left[\frac{P_s (\delta_{max} - \delta_0) + P_{m3} \cos \delta_{max} - P_{m2} \cos \delta_0}{P_{m3} - P_{m2}} \right] \text{ elec. deg.}$$

At 'a' $P_s = P_{e1} = P_{m1} \sin \delta_0$

$$\delta_0 = \sin^{-1} \left(\frac{P_s}{P_{m1}} \right) \text{ elec. deg.}$$

$$\delta_0 (\text{rad}) = \delta_0 \times \frac{3.14}{180}$$

At 'b' $P_s = P_{e3} = P_{m3} \sin \delta_{max}$

$$\delta_{max} = \sin^{-1} \left(\frac{P_s}{P_{m3}} \right) \leq 90^\circ$$

→ In a critically stable condition δ_{max} will be expected to be more than 90°

$$P_s = P_{e3} = P_{m3} \sin (180 - \delta_{max})$$


$$180 - \delta_{max} = \sin^{-1} \left(\frac{P_s}{P_{m3}} \right)$$

$$\therefore \delta_{max} = 180 - \sin^{-1} \left(\frac{P_s}{P_{m3}} \right) \text{ elec.}$$


$$\left. \begin{array}{l} \delta_{max} (\text{rad}) \\ = \delta_{max} \times \frac{3.14}{180} \\ \text{elec.} \end{array} \right\}$$

27/02/10

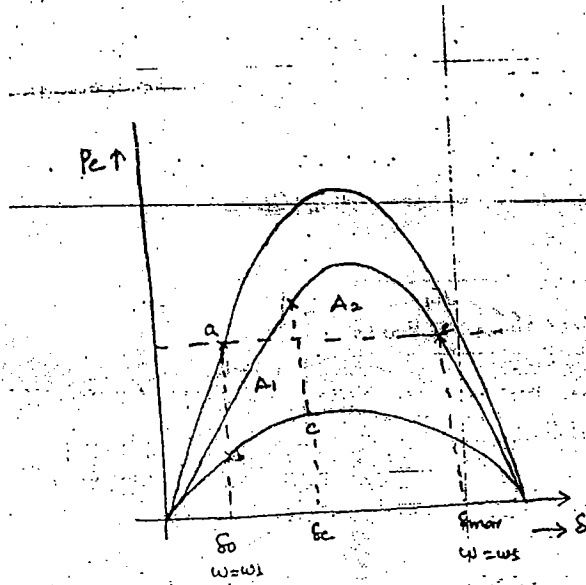→ For any given system there will be a critical clearing angle which can be calculated by using the Equal area criteria. However the actual angle made by the breaker during the fault condition should be less than the critical clearing angle in order to maintain the stability, otherwise



No further swings
(critically stable)

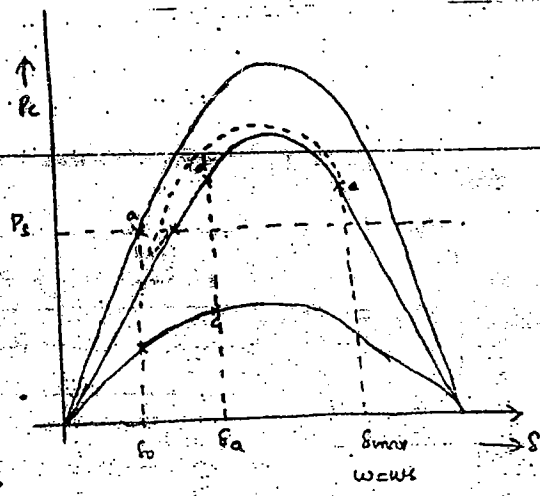

$\delta_a < \delta_c$
Further swings
(stable)

(4) FAULT OCCURS ON A LINE NEAR THE BUSBAR




$$P_{e1} = P_{m1} \sin \delta_0$$

$$P_{e2} = 0, P_{m2} = 0$$

$$P_{e3} = P_{m3} \sin \delta$$

$$P_{m3} > P_{m1}$$

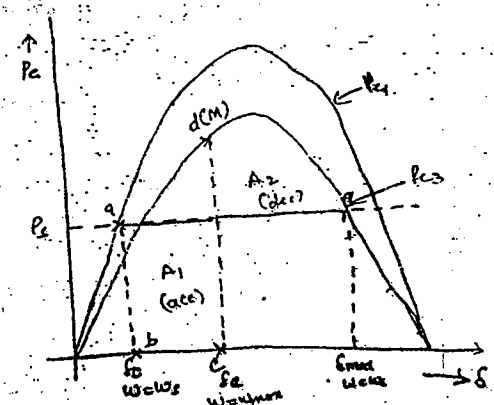

→ Initially the alternator is supplied with mech ip and corresponding o/p of P_{e1} . It is represented by point 'a'

→ A 3- ϕ s.c fault is taken place on one of the parallel line near to busbar and it will be assumed as fault on busbar so that the electrical o/p become zero where as the mech ip remains same. It is represented by point 'b'

Hence $P_e = 0 = P_{e3}$ (acceleration) $w > w_s$ (On)

At 'a' $P = P_s - P_{e1}$
 $= P_s - P_m \sin \delta$
 $= 0$

Neither acc nor decelerate $\omega = \omega_s$ & doesn't change

(c) The rotor angle of the alternator will \uparrow still the fault is cleared. The fault is cleared after few cycles and it can be represented by point 'c'. The angle corresponding to ' δ_c '

'b' to 'c' $P = P_s - P_{e2}$
 $= P_s - 0$
 $= P_s$
 $= +ve$

Acceleration $\omega > \omega_s$ & will slowly increase

\rightarrow If the fault is cleared by the breaker, the faulty line is isolated and the alternator will be able to deliver the electrical o/p through the healthy line which is represented by point 'd' with the same mech i/p. Due to moment of inertia the angle will increase further to get $\omega = \omega_s$ in a critically stable manner. It is represented by point 'e'.

d to e $P = P_s - P_{e3}$
 $= P_s - P_m \sin \delta$
 $\Rightarrow (\delta > \delta_c)$
 $= -ve$

Deceleration $\omega < \omega_s$ but $\omega > \omega_s$ & will also further increase.

Calculation of δ_c

$$\int_{\delta_0}^{\delta_{max}} P_a d\delta = 0 = \int_{\delta_0}^{\delta_c} P_a d\delta + \int_{\delta_c}^{\delta_{max}} P_a d\delta = 0$$

$$= \int_{\delta_0}^{\delta_c} (P_s - P_m \sin \delta) d\delta + \int_{\delta_c}^{\delta_{max}} (P_s - P_m \sin \delta) d\delta = 0$$

$$= \int_{\delta_0}^{\delta_c} (P_s - 0) d\delta = \int_{\delta_c}^{\delta_{max}} (P_m \sin \delta - P_s) d\delta$$

$$\delta_c = \cos^{-1} \left[\frac{P_s (\delta_{max} - \delta_0) + P_m \cos \delta_{max}}{P_m} \right] \text{ c.k. deg.}$$

→ of the accelerating power during the fault is constant for a special fault then the critical clearing angle which is calculated by using equal area criteria can be possible to convert into critical clearing time

$$M \frac{d^2\delta}{dt^2} = P_a = P_s - P_{e2} = P_s \quad (\because \text{during fault } P_{e2} = 0)$$

$$\frac{d^2\delta}{dt^2} = \frac{P_s}{M}$$

$$\frac{d\delta}{dt} = \frac{P_s}{M} t$$

$$\delta = \frac{P_s}{M} \frac{t^2}{2} + A$$

at $t = t_c$

$$\delta_c = \frac{P_s}{M} \frac{t_c^2}{2} + A$$

Use initial condition to get a 'A' value

$t_c = 0$, before fault


$$\delta_c = \delta_0 = 0 + A$$

$$\Rightarrow \delta_c = \frac{P_s}{M} \frac{t_c^2}{2} + \delta_0$$

$$t_c = \sqrt{\frac{2M(\delta_c - \delta_0)}{P_s}}$$

$M \rightarrow \text{rad}$
 $(M \rightarrow \text{rad})$
 $\delta_c - \delta_0 \rightarrow \text{rad}$
 Since P_s is small


(5) Fault on bus bar

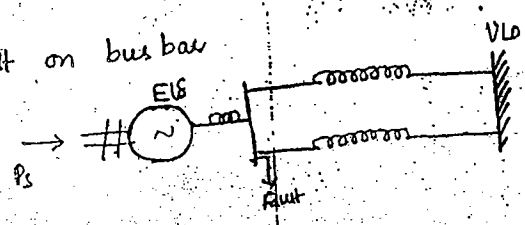

$$P_{e1} = P_{m1} \sin \delta_0$$

$$P_{e2} = 0, P_{m2} = 0$$

$$P_{e3} = P_{m3} \sin \delta$$

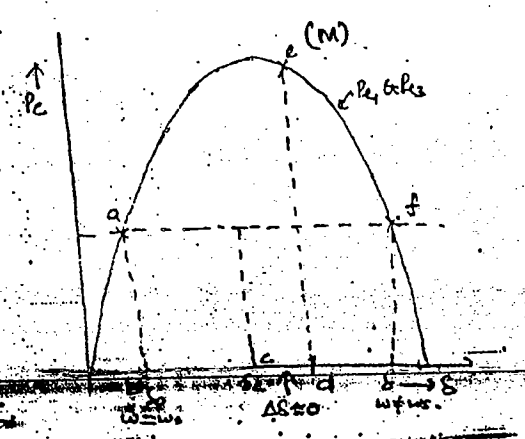

At 'a'

$$P = P_s - P_{e1}$$

$$= P_s - P_m \sin \delta_0$$

$$= 0$$

Neither acceleration
nor deceleration

$$\omega = \omega_s$$

δ doesn't change

→ A 3- ϕ short circuit fault occurs on the busbar so that the electrical o/p has become zero where as the mechanical i/p remains same.

It is represented by point 'b' hence

$$P = P_s - P_{e2}$$

$$= P_s - 0$$

$$= P_s (+ve)$$

acceleration

$$\omega > \omega_s$$

The rotor angle of generator will slowly increase till the fault is cleared. The fault is cleared after few cycles and it can be represented by point 'c'

'b' to 'c'

$$P = P_s - P_{e2}$$

$$= P_s - 0$$

$$= P_s (+ve)$$

Acceleration

$$\omega > \omega_s$$

δ will increase slowly

→ If the fault is cleared by the breaker then the alternator will be isolated from both the parallel lines so that the electrical o/p "Zero". The mechanical i/p remains same. It will result that the alternator is working at no load condition and it behaves as an acceleration period. In order to avoid the no load operation of the alternator it can be assumed that the fault is cleared at a faster rate and CB is closed after few cycles so that the total n/w will be restored

→ It can be assumed that the breaker is closed at point 'd'

'c' to 'd'

$$P = P_s - P_{e3}$$

$$= P_s - 0$$

$$= P_s (+ve)$$

(No load position)

Acceleration

$$\omega > \omega_s$$

δ will increase

→ If the CB is closed, the alternator will deliver the electrical o/p by both the lines

which can be represented by point 'e' and the mechanical i/p remains same. Due

to moment of inertia the angle will increase further to get $\omega > \omega_s$ in a critically full manner

→ However the synchronous machine will become unstable if $A_1 > A_2$ because the no load operation of the alternator will increase the acceleration region.

→ The following assumptions are made to the synchronous machine are critically stable.

- (1) The equal area criteria is a graphical solution and it can give an approximate critical clearing angle.
- (2) The no. of cycles during which the no load operation of the alternator are very few and the moment of inertia of the system is very high so that the change in rotor angle and the change in speed during the no load condition can be assumed as zero. (i.e. $\Delta\delta \approx 0, \Delta\omega \approx 0$)

→ Calculation of δ_c

$$\int_{\delta_0}^{\delta_{max}} P_a \cdot d\delta = 0$$


$$\int_{\delta_0}^{\delta_c} P_a \cdot d\delta + \int_{\delta_c}^{\delta_{max}} P_a \cdot d\delta = 0$$

$$\int_{\delta_0}^{\delta_c} (P_s - P_{m2}) \cdot d\delta = \int_{\delta_c}^{\delta_{max}} (P_{m3} - P_s) \cdot d\delta$$

$$\therefore \delta_c = \cos^{-1} \left[\frac{P_s (\delta_{max} - \delta_0) + P_{m3} \cos \delta_{max}}{P_{m3}} \right] \text{ cleardeg.}$$

$$P_{m3} = P_{m1}$$

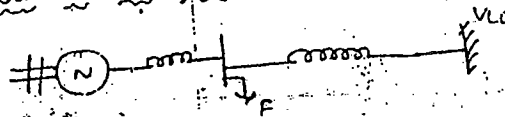(6) Fault occurs on an alternator connected to infinite bus through a line.




The equal area criteria of present application will be similar to that of the equal area criteria of the previous case(s)

$$P_{e1} = P_{m1} \sin \delta_0$$


$$P_{e2} = 0, P_{m2} = 0$$

$$P_{e3} = P_{m3} \sin \delta$$

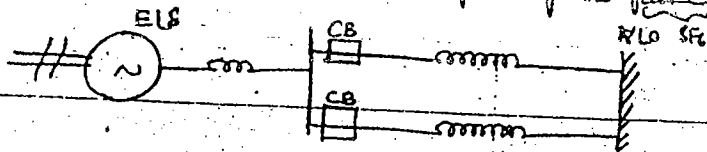(7) Removal of one of the 11kV tr. line by using the fast CB possibility



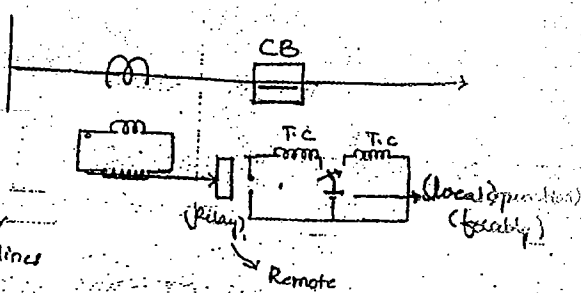$P_d > P_g \Rightarrow f \downarrow$ (by necessity)
up to 48.5 (tolerable)



$P_{c1} = \frac{EV \sin \delta_0}{X_{1eq}}$ Power transfer within two lines

$X_{1eq} = X_g + \frac{X_l}{2}$

$P_{m1} = \frac{EV}{X_{1eq}}$

$P_{c2} = \frac{EV \sin \delta_0}{X_{2eq}}$ → power transfer with one line


$= P_{m2} \sin \delta$

$P_{m2} = \frac{EV}{X_{2eq}}$; $X_{2eq} = X_g + X_l$

$P_{m2} < P_{m1}$

→ Initially the alternator is supplied with a new MP of P_s and a corresponding output of P_{c1} . It is represented by point 'a' on P_{c1} curve

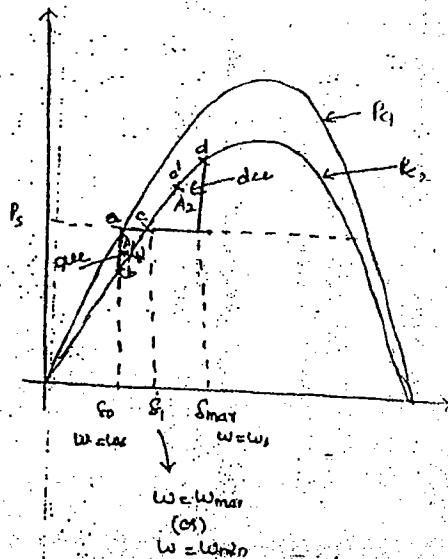→ whenever the existing load on the system is smaller than the available generation which can be identified by the way of falling of the system frequency, it is necessary to remove some of the existing load by way of isolating one of the connected tr. line by using fast acting C.B's



→ At 'a' $P_0 = P_s - P_{c1}$

$= P_s - \frac{EV \sin \delta_0}{X_{1eq}}$
 $= 0$

Not the acc
not dec

↓ don't clear

→ The removal of the tr. line will lead to the transient stability on the system and it can be analyzed by using equal area criteria.

→ The falling of the frequency is an indication for load shedding


→ The raising of the frequency is Backing down

→ If one of the tr. line is removed then the electrical op is reduced suddenly due to change in the reactance of the system where at the mech. op remains same.

$$\begin{aligned}
 P &= P_s - P_e \\
 &= P_s - \frac{EV}{X_{seq}} \sin \delta \\
 &= +ve \\
 &= \text{acceleration} \Rightarrow \omega = \omega_s
 \end{aligned}$$

∴ δ will slowly increase.

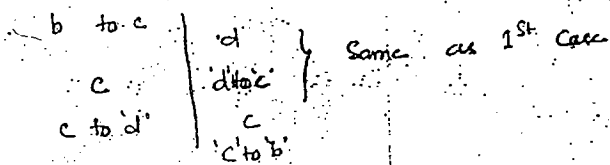→ As the angle will increase the op power also slowly increases.



→ POINT-BY-POINT METHOD : (1) It gives the solution for swing equation

in a mathematical manner

(2) The point by point method provides the change of angle made by the rotor for a smaller interval of time i.e. Δt (0.05 sec by default).

By knowing the change of angle, then the actual angle made by the rotor at the end of the interval will be calculated.

→ The following assumptions are made in order to calculate the change of angle and also the actual angle of the rotor.


(1) The accelerating power which is calculated at the beginning of the interval

is expected to be constant throughout the interval. It is assumed to be constant from the middle of the previous interval to the middle of the present interval.

(2) The angular velocity which is calculated at the middle of the interval is assumed to be constant through out the interval because of large moment of inertia

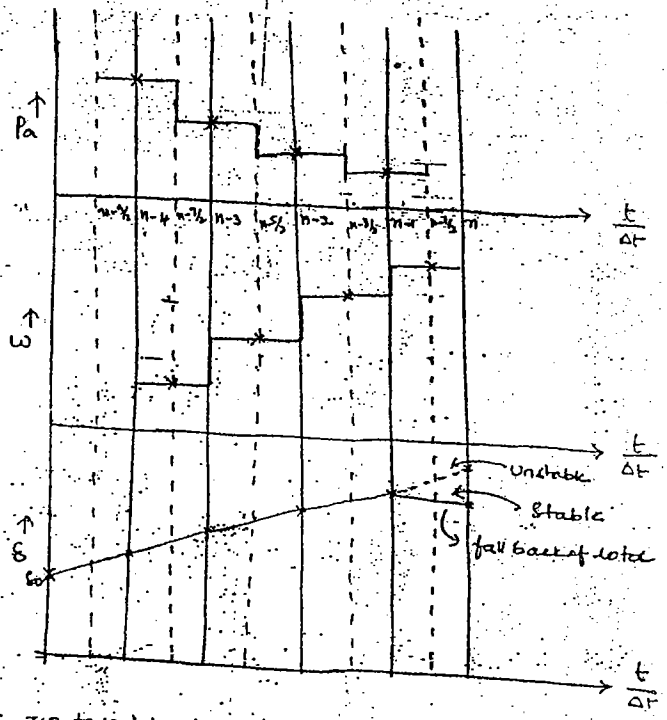(3) The change of angle which is calculated at the beginning of the interval is expected to have a smooth variation till the end of the interval.

→ In p-by-p method, the system is stable provided that the rotor angle is expected to be fall back after certain no. of intervals, then the system is stable otherwise the system is unstable.



Ex: After 5 cycles (2-f-clips)

- 1 - acc → 50 Cych.
- 2 → 5 Cych.

$\frac{t}{T_0} = 0.1 \uparrow 0.25, 0.2 \dots 0.5$ up to 12 intervals to say the system is stable or not. fault cleared, but imbrued.

→ The change in angular velocity during the first interval $\Delta \omega_1 = \alpha \cdot \Delta t$

Where $\alpha = \frac{Pa}{M}$;

→ The actual speed at the end of the interval $\omega_1 = \omega_0 + \Delta \omega_1$
 $\omega_0 \rightarrow$ initial speed i.e. N_s

→ The change of angle during 1st interval $\Delta \delta_1 = \omega_1 \cdot \Delta t$
 $= (\omega_0 + \Delta \omega_1) \Delta t$
 $= \omega_0 \Delta t + \alpha (\Delta t)^2$
 $= \Delta \delta_0 + \alpha (\Delta t)^2$

$$\Delta \delta_1 = \Delta \delta_0 + \alpha (\Delta t)^2$$

→ The actual angle at the end of 1st interval is

$$\delta_1 = \delta_0 + \Delta\delta_1$$

→ The change of angular velocity during 2nd interval is

$$\Delta\omega_2 = \alpha \Delta t \quad \alpha = \frac{P_a}{M}$$

→ The actual speed at the end of interval $\omega_2 = \omega_1 + \Delta\omega_2$

→ The change of angle during 2nd interval $\Delta\delta_2 = \omega_2 \Delta t$
 $= (\omega_1 + \Delta\omega_2) \Delta t$
 $= \omega_1 \Delta t + \alpha (\Delta t)^2$

$$\Delta\delta_2 = \Delta\delta_1 + \alpha (\Delta t)^2$$

→ The present change of angle not only depends on the accelerating power of present angle but also depends on the change of angle of previous intervals.

→ The actual angle at the end of 2nd interval, $\delta_2 = \delta_1 + \Delta\delta_2$

∴ In general $\Delta\delta_n = \Delta\delta_{n-1} + \alpha (\Delta t)^2$

and

$$\delta_n = \delta_{n-1} + \Delta\delta_n$$

→ While calculating the change of angle consider the average accelerating power at the time of fault occur at the time of fault clear in all other intervals consider accelerating power only.

Fault occur


$$P_a(\text{avg}) = \frac{P_{a1} + P_{a2}}{2}$$

Fault cleared

$$P_a(\text{avg}) = \frac{P_{a2} + P_{a3}}{2}$$

⇒ Even though the synchronous motor is stable during the 1st swing but there are chances to fall out of synchronism during the subsequent swing which is called tipping of the synchronous motor.

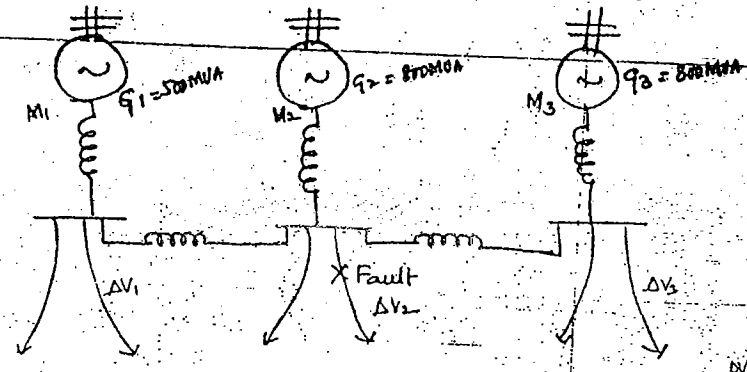Ex: cascade tripping of lines (a) post failure.



ΔV1, ΔV2, ΔV3 are change in voltages.

1st swing
 descending order
 XG2, G3, G1

Moment of inertia of capacity

ΔV2 > ΔV3 > ΔV1


of fault is on G1

1st swing: G1, G3, G2
 2nd swing: G3, G2
 3rd swing: G2

2nd swing
 XG3, G1

3rd swing
 XG1

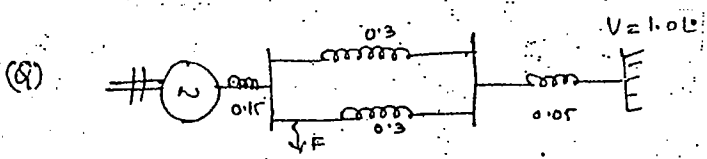* If equal capacities are there, then the G's which is near to the fault will swing 1st.



The alternator is initially supplying 1.0 p.u. to the infinite bus. The fault occurs on a line near to bus bar. The inertia constant is 4 p.u. show the rotor angle by using point by point method for a time of 0.25 sec.

Sol

$$P_{m1} = \frac{EV}{X_{1eq}} = \frac{1.1 \times 1.0}{0.15 + \frac{0.3}{2} + 0.05} = 3.14 \text{ p.u.}$$

$$P_{m2} = 0, P_{m3} = 0$$

$$P_{m3} = \frac{EV}{X_{3eq}} = \frac{1.1 \times 1.0}{0.15 + 0.3 + 0.05} = 2.2 \text{ p.u.}$$

Time	$\Delta \delta$	δ
Initial. 0^-	0	18.57
0.05	2.84	21.4
\rightarrow 0.1	6.23	27.63
0.15	6.1	33.74
0.2	4.83	38.57
0.25	2.75	41.32

δ at 0^-

$$P_s = P_{e1} = P_{m1} \sin \delta_0$$

$$\delta_0 = \sin^{-1} \left(\frac{P_s}{P_{m1}} \right)$$

$$= \sin^{-1} \left(\frac{1.0}{3.14} \right)$$

$$\delta_0 = 18.57$$

$$\Delta \delta_1 = \Delta \delta_0 + \kappa (\Delta t)^2$$

$$= 0 + \frac{P_a}{M} (\Delta t)^2$$

$$= \left(\frac{0.44 \times 10^{-3}}{0.5} \right) (0.05)^2$$

$$\Delta \delta_1 = 2.84$$

$$\delta_1 = \delta_0 + \Delta \delta_1$$

$$= 18.57 + 2.84$$

$$= 21.4$$

$$M = \frac{SH}{180 f}$$

$$= \frac{1.0 \times 4}{180 \times 50}$$

$$= 0.44 \times 10^{-3}$$

$$P_a = P_{avg}$$

$$= \frac{P_{a1} + P_{a2}}{2}$$

$$= \frac{0 + P_1 - P_2}{2}$$

$$= \frac{1.0 - 0}{2}$$

$$= 0.5$$

\rightarrow C.B. time is 5 cycles $\rightarrow \frac{5}{50} = 0.1$

$$\Delta \delta_2 = \Delta \delta_1 + \kappa (\Delta t)^2$$

$$= 2.84 + \frac{P_a (avg)}{M} (\Delta t)^2$$

$$P_a (avg) = \frac{P_{a2} + P_{a3}}{2}$$

$$= \frac{P_2 - P_{e2} + P_3 - P_{e3}}{2}$$

$$= \frac{2P_3 - P_{e3}}{2} = \frac{2P_3 - P_{m3} \sin \delta_1}{2} = \frac{2(1) - P_{m3} \sin(21.4)}{2}$$

$$P_a (avg) = 0.598$$

$$\Delta \delta_2 = 2.84 + \frac{0.598}{0.44 \times 10^{-3}} (0.05)^2$$

$$= 6.23$$

$$\delta_2 = \Delta \delta_2 + \delta_1$$

$$= 6.23 + 21.4$$

$$= 27.63$$

$$\rightarrow \Delta \delta_3 = \Delta \delta_2 + \alpha (\Delta t)^2$$

$$= 6.23 + \frac{Pa}{M} (\Delta t)^2$$

$$= 6.23 + \frac{P_2 - P_1}{0.44 \times 10^3} (0.05)^2$$

$$= 6.23 + \frac{1.0 - 2.2 \sin(27.63)}{0.44 \times 10^3} (0.05)^2$$

$$= 6.1$$

$$\delta_3 = \delta_2 + \Delta \delta_3$$

$$= 27.63 + 6.1 = 33.74$$

$$\rightarrow \Delta \delta_4 = \Delta \delta_3 + \alpha (\Delta t)^2$$

$$= 6.1 + \frac{Pa}{M} (0.05)^2$$

$$= 6.1 + \frac{P_2 - P_1}{M} (0.05)^2$$

$$= 6.1 + \frac{1.0 - 2.2 \sin(33.74)}{0.44 (m)} (0.05)^2$$

$$= 4.83$$

$$\delta_4 = \Delta \delta_4 + \delta_3$$

$$= 4.83 + 33.74 = 38.57$$

$$\rightarrow \Delta \delta_5 = \Delta \delta_4 + \alpha (\Delta t)^2$$

$$= 4.83 + \frac{Pa}{M} (0.05)^2$$


$$= 4.83 + \frac{P_2 - P_1}{M} (0.05)^2$$



$$= 4.83 + \left(\frac{1.0 - 2.2 \sin(38.57)}{0.44 \text{ m}} \right) \times (0.05)^2$$




$$= 2.72$$



$$\delta_5 = 2.72 + 38.57$$

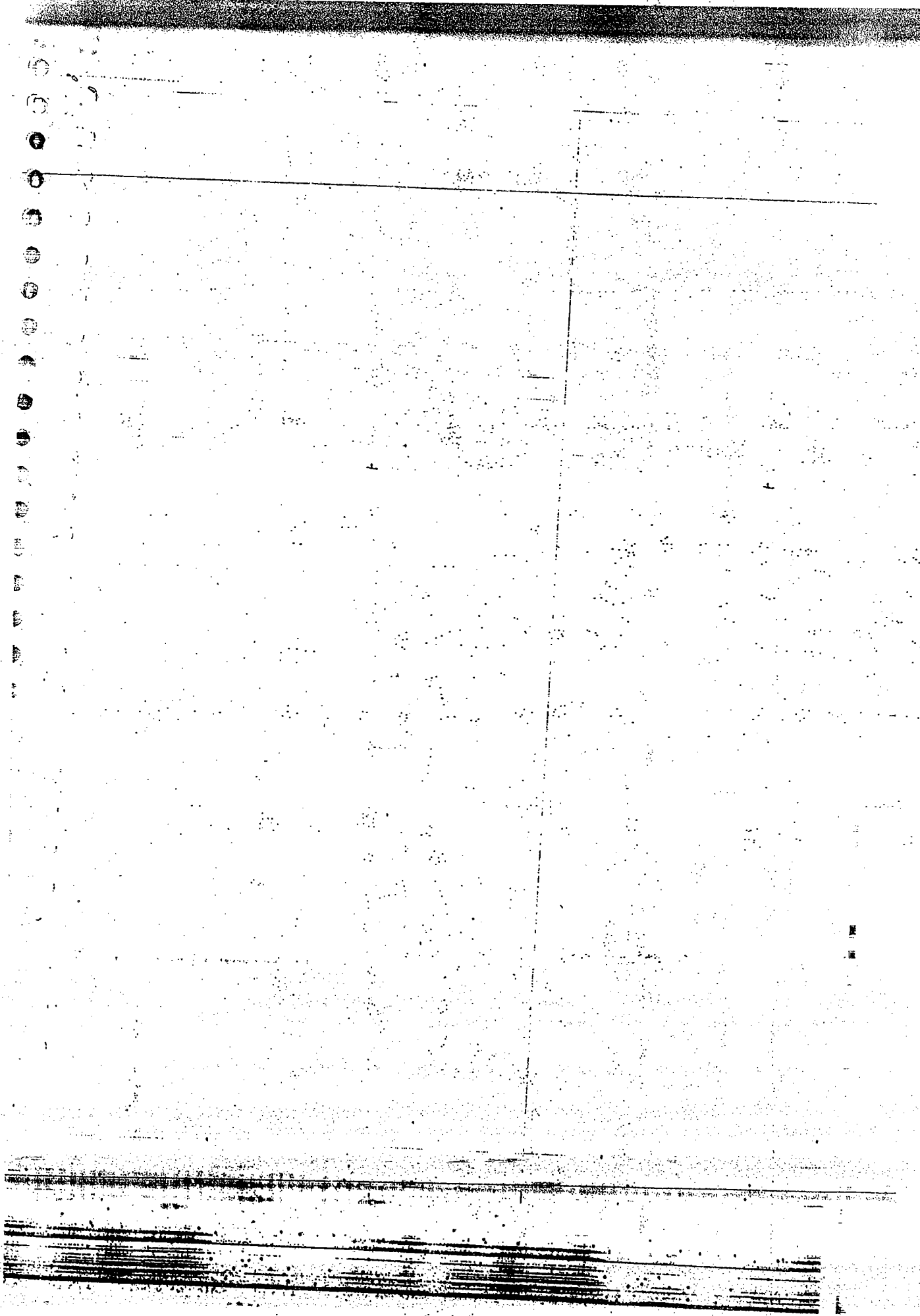After fault condition is
instead of taking Paug.



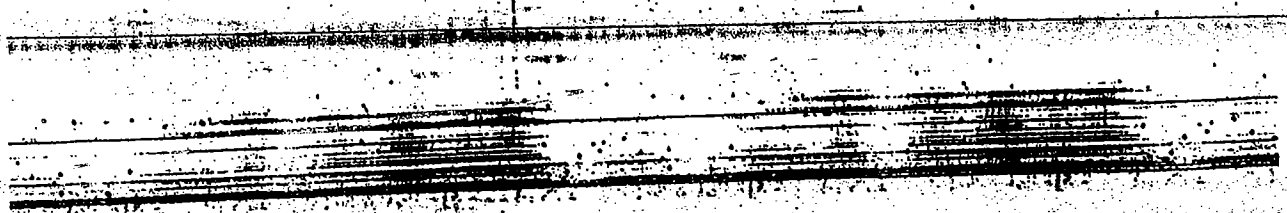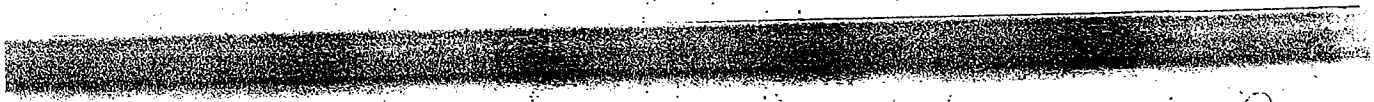

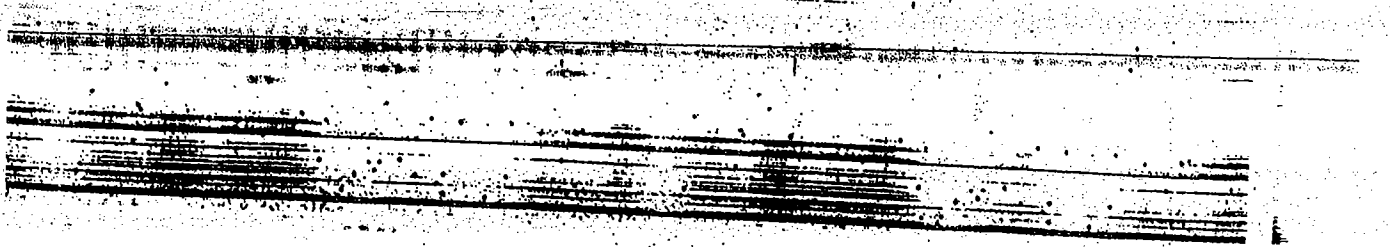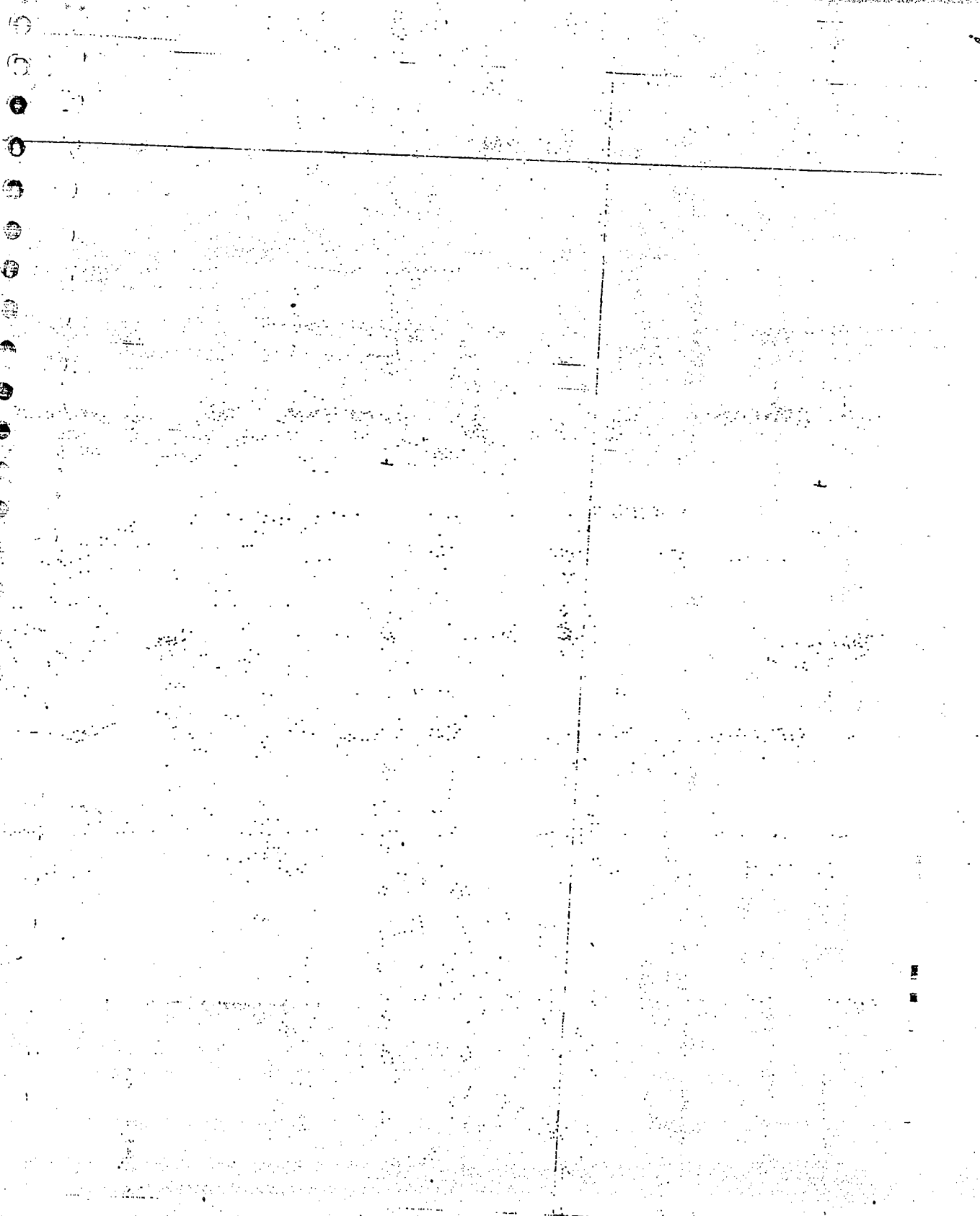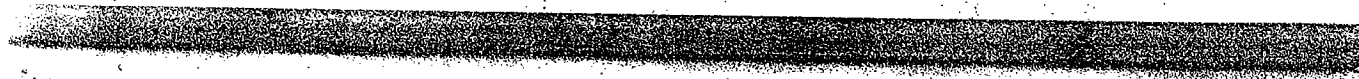

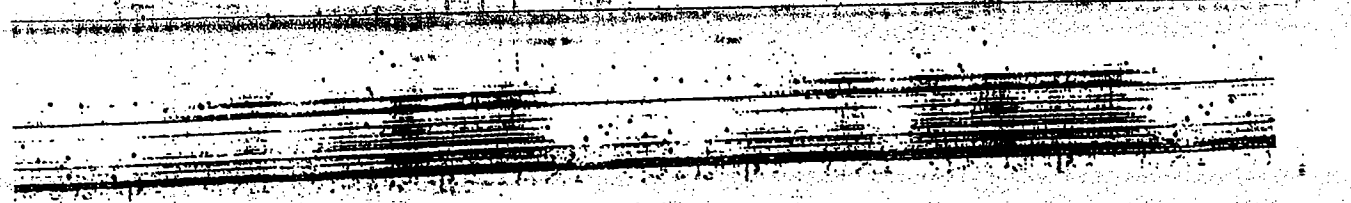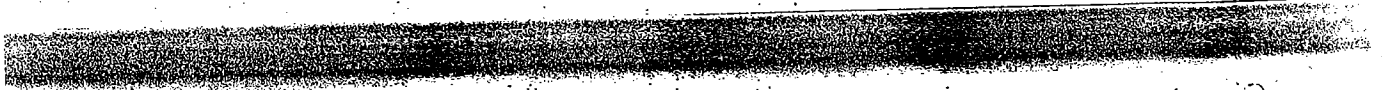


25/01/2010

→ ECONOMIC ASPECTS AND ECONOMIC LOAD DISPATCH

→ ECONOMIC ASPECTS:

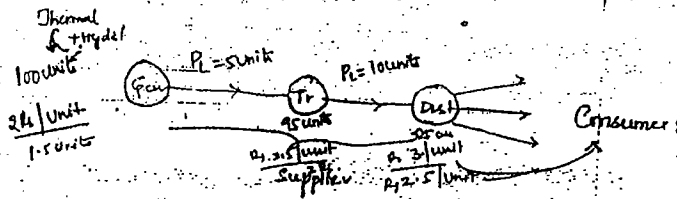Minimize the cost/unit/annum of electrical energy generation so that the cost/unit/annum of electrical energy consumed by the consumer is minimum.



Consumer: Consumer Satisfaction to the supplier. i.e.

- 1) Quality of the supply
- 2) Cost/unit is minimum

→ By proper mixing of Thermal & Hydel the cost of generation can be minimized so that the cost/unit for consumer is minimized.

Unit = 1000 kwhr
 = 1 Kwhr.


→ The cost/unit to the consumer is decided on annual basis

→ Cost: (1) fixed cost & (2) Running Cost

→ Fixed Cost:

Ex: Thermal Station:

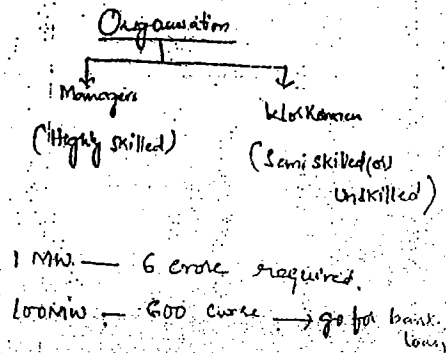- (1) Cost of the land
- (2) Cost of buildings
- (3) Cost of machinery
- (4) Salaries of the Managers
- (5) Interest & Insurance charges
bank loan fire hazard
- (6) Depreciation charges



→ Depreciation: It is the cost in Rs/annum which is wasted, while the equipment is running.

Eq: Fan — Rs. 1000/-

Life = 10 years.

$$\text{Depreciation/annum} = \text{Rs. } 100 \quad \left(\frac{\text{Cost}}{\text{no. of years}} \right)$$

(2) Running Cost:

- (1) Cost of fuel
- (2) wages to workmen
- (3) Maintenance Cost

→ Cost/unit/annum:

$$\text{Cost/unit/annum} = \frac{\text{Fixed Cost/annum} + \text{Running Cost/annum}}{\text{Total no. of units that are generated in a year}}$$

$$\text{Fixed Cost/annum} = \frac{\text{Fixed Cost}}{\text{No. of useful years (ie. life of plant)}}$$

plant	Life
Gas station →	15 years
Thermal →	20 years
Nuclear →	25 years
Hydel →	50 years
X RCC buildings —	100 years.

$$\therefore \text{F.C/annum} = \frac{600 \text{ Crores}}{20 \text{ years}} = 30 \text{ Crores.}$$

$$\text{Running/annum} = 70 \text{ Crores (Assume)}$$

Eq: BIKE
 F.C → 50,000
 R.C/ann → 5,000
 R.C — 365 x 50


$$\text{No. of Unit} = 500 \text{ Million Units}$$

$$\therefore \text{Cost/unit/annum} = \frac{30+70}{500} = \frac{100 \times 10^7}{500 \times 10^6} = 2 \text{ Rs/unit}$$

→ The Cost/unit/annum can be minimized by considering the load factor and the diversity factor.

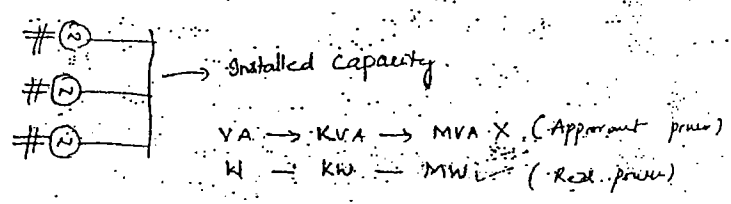1) Connected load (or) Installed Capacity:

→ The Arithmetic sum of the ratings of all the electrical equipments of a consumer (or) The Arithmetic sum of the ratings of the generators which are connected to a common bus is called Connected load (or) Installed Capacity (w.r.t gen station)



→ In the Economic aspects and Economic load dispatch the rating of the equipment is in terms of the real power of the system.

→ The Connected load of the Installed Capacity can be considered remain same over a period of one year.

2) MAXIMUM LOAD: It is the highest amount of power being consumed by consumer or delivered by the generating station for a shorter interval of time over a specified period (24 hours)

→ For smooth functioning of the system without losing the stability the planning is made on daily basis.

→ To maintain the stability of the sync. m/c, the M.L must be less than installed capacity.

$$\boxed{M.L < I.C} \rightarrow \text{Stable}$$

$$M.L = I.C \rightarrow \text{Critically stable}$$

$$M.L > I.C \rightarrow \text{Unstable}$$

$$\rightarrow \text{Reserve Capacity} = \text{Installed Capacity} - \text{Maximum Load}$$

$$\Rightarrow \text{Reserve} = I.C - M.L$$

$$= +ve \rightarrow \text{Stable}$$

$$= 0 \text{ (Critically stable)}$$

$$= -ve \rightarrow \text{Unstable}$$

(3) Maximum Demand: The demand that can be forecasted prior to the day of

(4) Average Load: It is the amount of power being consumed by the consumer or delivered by the generating station for most of the time over a specified period.

$$\text{Average load} = \frac{\text{Connected load of the consumer} \text{ (1 consumer)}}{\text{No. of Equipments}}$$


$$\text{A.L} = \frac{\text{Sum of the connected load of the consumer} \text{ (Consumers > 1)}}{\text{No. of Consumer}}$$

$$\boxed{A.L < M.L < C.L}$$


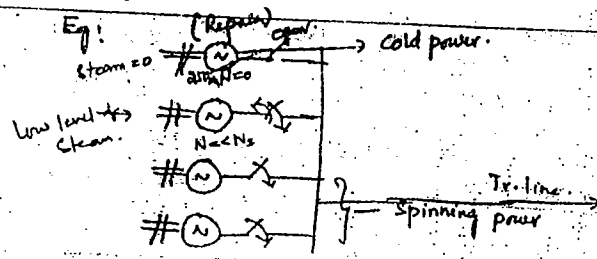
5) FIRM power: It is the amount of power available even during emergency condition

Eg: Diesel generators, Emergency lamps & Battery Banks.

→ COLD POWER (or) COLD RESERVE: It is the amount of power available for service but not operation.
(Repairs)



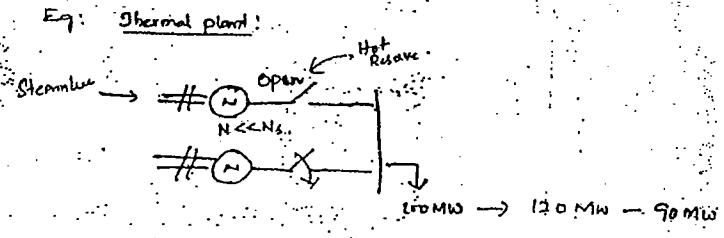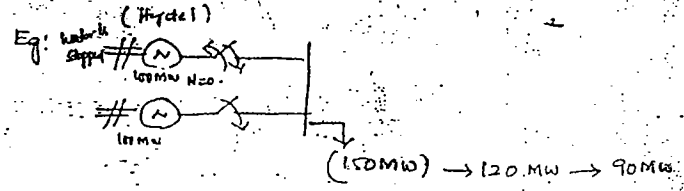→ HOT POWER or HOT RESERVE: It is the amount of power available for operation but not service.



→ The synchronization time of a gas plant for normal startup is 2 minutes.

For Hydel plants — 5 minutes, where as for thermal plant it is 8 hrs. In order to reduce the synchronization time the thermal units are kept under hot reserve.

→ In case of Nuclear plant if they are exists, the variation of the load cannot be normally admitted when compared to other plants because it is very difficult to control the nuclear reaction.

→ Spinning power (or) S^+ is the amount of power available at the busbar due to synchronization of the units and the power is delivered to the load by using transmission lines.

→ LOAD FACTOR (or) PLANT LOAD FACTOR

$$L.F (or) P.L.F = \frac{\text{Average load}}{\text{Maximum load}} < 1.0$$

$$(or) = \frac{\text{Actual no. of units that are generated}}{\text{Maximum load} \times (\text{Total no. of hrs over a specified period})}$$

Daily basis → Daily load factor → 24 (hrs)
 Annual basis → Annual load factor → 8760 (hrs)

Best P.L.F (or) L.F is less than 100%

→ In order to minimize the cost per unit the load factor of the system must be high

Eg. PLF = 50%.
 PLF = 70% → preferred bcoz cost is minimized compared to above.

→ If the load factor is high then the average load on the plant is almost equal to the maximum load so that there will be effective utilization of the steam. The amount of fuel required is less which will reduce the fuel cost, which in turn reduces the running cost and finally the cost/unit is minimized. Hence the L.F of the system will influence the running cost.

Ex: Consumers

- 1) Domestic
- 2) Non-Domestic (or) Commercial
- 3) Industrial \rightarrow Bulk power (influence the simultaneous max load)
- 4) Agriculture
- 5) Public purpose

(Q) Ex:

	CL	M.L	Time	10-12	16-18	8-10
A	300kw	300	10-12 hrs	300	240	220
B	350kw	350	16-18 hrs	280	330	270
C	400kw	390	8-10 hrs	300	340	390
		<u>1020</u>		<u>900</u>	<u>930</u>	<u>880</u>

Simultaneous Max Load
(Installed capacity basis)

$$\text{Diversity Factor} = \frac{1020}{930} > 1$$

The installed capacity is selected based on the simultaneous maximum load on the system which is less so that the fixed cost is reduced and finally the cost/unit is minimized.

\rightarrow In a practical case it is more flexible to minimize the R. cost when compared to the fixed cost of the system.

\rightarrow In a large system which is dealing with more no. of industrial consumers it is very difficult to reduce the installed capacity in order to reduce the fixed cost. Hence the cost/unit

~~can be minimized~~ effectively by ~~reducing~~ the load factor in order to reduce the running cost.

Ex: A 100kW alternator

	P_1	P_2
00 - 3hrs	30kW	50kW
3 - 6hrs	70kW	60kW
6 - 9hrs	95kW	95kW
9 - 12hrs	60kW	70kW

In: D_2 the effective utilization of steam is good.

hence L.F \uparrow since Avg load \approx Max. load.

*** P.L.F = 80% and above in Nuclear plant

P.L.F = 60% - 70% \rightarrow Thermal plants

P.L.F = 30 - 40% \rightarrow Hydel plants

P.L.F = 10 - 20% \rightarrow Gas plants

\rightarrow DIVERSITY FACTOR:

$$\text{Diversity Factor} = \frac{\text{Arithmetic sum of max loads of all the consumers}}{\text{Simultaneous max load on the system}}$$

> 1.0

\rightarrow if the diversity factor of the system is high then the cost/unit is minimize

** \rightarrow In order to minimize the cost/unit, the Load factor & the Diversity factor should be high.

\rightarrow The maximum load of the consumer exists for only few hours and of the installed capacity is chosen based on the arithmetic sum of maximum loads of all the consumers then the installed capacity is high

Hence the fixed cost of the system \Rightarrow the cost per unit is high.

\rightarrow In order to reduce the fixed cost there will be effective

utilization of the installed capacity i.e. select the installed

capacity for a simultaneous max load on the system which is always less than the arithmetic sum of max load of all the consumers

→ PLANT CAPACITY FACTOR:

$$\text{PLANT CAPACITY FACTOR} = \frac{\text{Average Load}}{\text{Installed Capacity}}$$

$$< 1.0 \text{ (or) } < 100\%$$

For a given plant, $\text{PCF} < \text{PLF}$ since

$$\text{PLF} = \frac{\text{Avg. load}}{\text{Max. load}}$$

the installed capacity $>$ Max. load.

If $\text{PCF} = \text{PLF} \Rightarrow \text{M.L} = \text{I.C} \Rightarrow \text{Reserve} = 0$

$$\text{Reserve} = \text{Installed capacity} - \text{Max. load.}$$

(Q) A plant is having a max load of 100 MW having the PCF = 50% and PLF = 70%. The Reserve Capacity of plant in MW is

Sol

$$\text{P.C.F} = 50\% \quad \text{PLF} = 70\%$$

$$\frac{\text{PCF}}{\text{PLF}} = \frac{\text{Max. load}}{\text{Installed Capacity}}$$

$$\frac{0.5}{0.7} = \frac{100}{\text{Inst. Capacity}}$$

$$\text{I.C} = 140 \quad (100 \times \frac{7}{5})$$

$$\text{Reserve} = 140 - 100 = \underline{40 \text{ MW}}$$

→ Plant Capacity Factor = $\frac{\text{Actual no. of units that are generated}}{\text{Max possible no. of units that can be generated based on the installed capacity}}$

$$< 1.0 \text{ (or) } < 100\%$$

For Ex: 100 kW - Generator

00 - 3 hrs - 80 kW

3 - 6 hrs - 50 kW

6 - 9 hrs - 30 kW

12 - 15 hrs - 60 kW

18 - 18 hrs - 70 kW

19 - 21 hrs - 90 kW

22 - 24 hrs - 80 kW

25 - 27 hrs - 60 kW

$$PCF = \frac{80 \times 3 + 150 \times 3 + 80 \times 3 + 40 \times 3 + 60 \times 3 + 70 \times 3 + 90 \times 3 + 20 \times 3}{100 \times 24}$$

< 1 or $< 100\%$

→ PLANT USE FACTOR

$$P.U.F = \frac{\text{Actual No. of units that are generated}}{\text{Installed Capacity} \times (\text{Actual no. of hrs does the plant is working})}$$

For a given plant, $PUF > PCF$

$$P.U.F = \frac{\text{Max. load}}{\text{Installed Capacity}}$$

→ In order to know the max. utilization of plant out of the installed capacity so far, then the above definition is consider.

$$PUF = \frac{\text{Max. load}}{\text{Installed Capacity}} = \frac{\frac{\text{Max. load}}{\text{avg. load}}}{\frac{\text{Installed capacity}}{\text{avg. load}}} = \frac{\frac{1}{PLF}}{\frac{1}{PCF}} = \frac{PCF}{PLF}$$

$$\therefore PUF = \frac{PCF}{PLF}$$

→ PLF } → Add. of capacity
 Diversity Factor } → size of each unit
 } → minimize cost/unit

→ The load on the system is, the Avg load and the max load are increases from year to year and it requires a proper planning of the installed capacity. The PCF and PUF are the basis to

decide the selection of the amount of additional capacity to be added and also the size of each unit of the additional capacity.

Ex: 1000 MW

$1000 \times 1 = 1000 \text{ MW} \rightarrow$ Less reliable & uneconomical at light loads.



$\sqrt{500 \times 2} = 1000 \text{ MW} \rightarrow$ Reliable & easy to maintain synchronisation + Economical

$250 \times 4 = 1000 \text{ MW} \rightarrow$ Difficult to maintain the synchronisation.

Graphical Representations

LOAD CURVE: It gives the variation of the load w.r.t time over a specified period in a graphical manner.

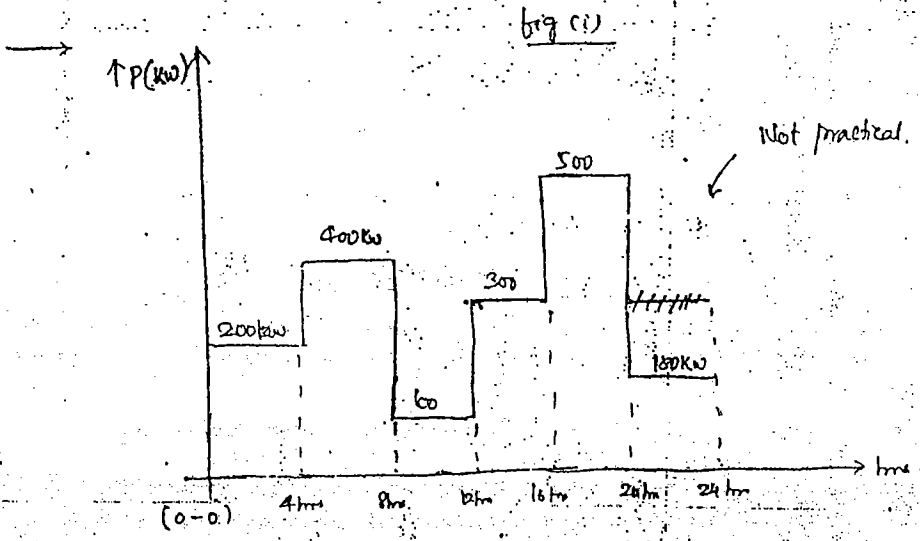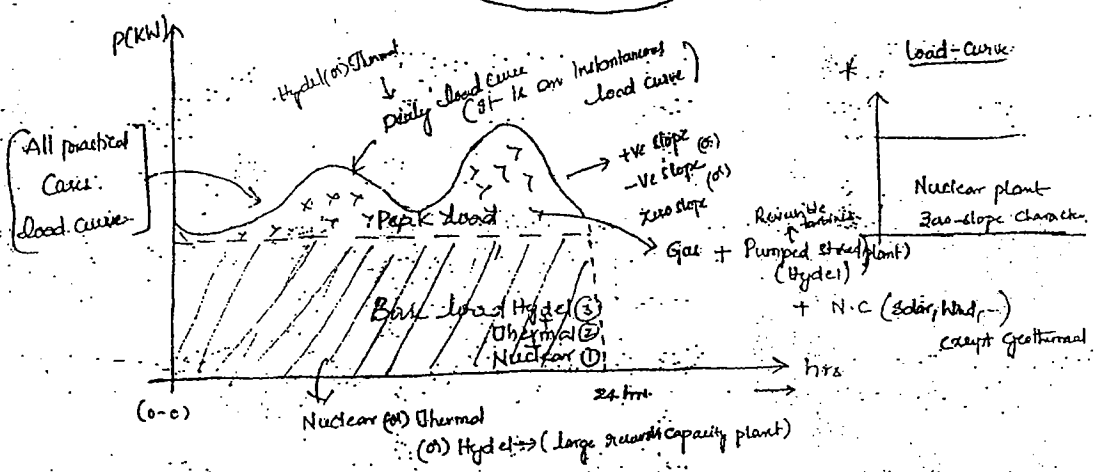It can be Daily load curve (or) Monthly (or) Annual load curve.



big (1)

From load curve

(i) Area = $P \times t =$ No. of units generated (or) consumed

(ii) Peak point = Max. load

(iii) Average load = $\frac{\text{Area}}{\text{no. of hrs}}$

(iv) PLF = $\frac{\text{Average load}}{\text{Max. load}}$

(v) The load curve is the basis for load forecasting

∴ From fig (ii) Calculate the load curve values.

(i) No. of units generated = $4(200 + 400 + 100 + 300 + 500 + 150)$

= $4(1650)$

Peak load = 500 kW

Average load = $\frac{\text{Area}}{\text{No. of hrs}} = \frac{1650 \times 4}{24}$ hrs

PLF = $\frac{1650/6}{500} = \frac{1650}{6 \times 500}$

→ The No. of hours that the peak load plant will operate will be calculated by considering the cost analysis of the plants.

→ Cost Analysis:

1) Two-part

Base load ← Cost $C_1 = R_1 a_1 / \text{kW} + P a_1 b_1 / \text{kWhr}$ → Exp

Peak load ← Cost $C_2 = R_1 a_2 / \text{kW} + P a_2 b_2 / \text{kWhr}$ → Util

⇒ $a_1 > a_2$, $b_1 < b_2$

$$C = C_1 + C_2$$

→ Do get the total no. of time does the peak load plant will operate then the total cost of the system should be minimum

P_1 = Capacity of peak load

P = Total Capacity

$(P - P_1)$ = Capacity of Base load

' x_1 ' be the no. of units of peak load

x be the total no. of units

$(x - x_1)$ → be the no. of units of Base load

$$C = C_1 + C_2 = (P - P_1)a_1 + (x - x_1)b_1 + P_1a_2 + x_1b_2$$


$$\frac{dC}{dP_1} = 0 = -a_1 + \left(-\frac{dx_1}{dP_1} \times b_1\right) + a_2 + \frac{dx_1}{dP_1} b_2$$

$$\Rightarrow \frac{dx_1}{dP_1} (b_2 - b_1) = -(a_2 - a_1)$$

$$\text{No. of hrs} \Rightarrow h = \frac{dx_1}{dP_1} = \left(\frac{a_1 - a_2}{b_2 - b_1}\right) \times 100$$


→ LOAD DURATION CURVE (LDC) It can be obtained from a given load curve. It gives the variation of the load w.r.t percentage of time and the loads are rearranged in a descending order.

From fig (ii) Load curve

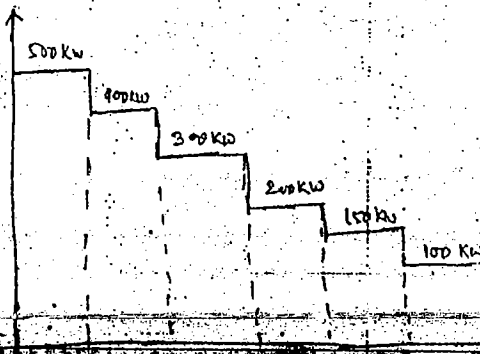

(20 - 10) = 10, 10, 10, 10, 10, 10

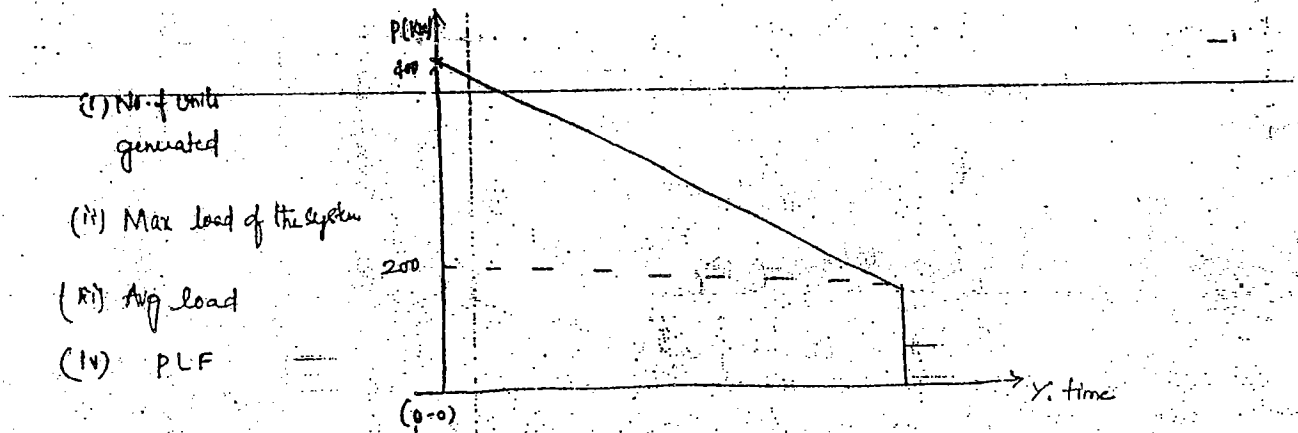(Q) The Annual load duration curve of a system is as shown below.



(i) No. of units generated = $\frac{1}{2} \times b \times h + b \times l$
 $= \frac{1}{2} \times 8760 \times 200 + 8760 \times 200$
 $= 8760 \times 300 \text{ kWh}$

(ii) Max load = 400 kW

(iii) Avg load = $\frac{\text{No. of Units}}{\text{No. of hrs}} = \frac{8760 \times 300}{8760} = 300 \text{ kW}$

(iv) PLF = $\frac{300}{400} = 0.75$

Another method

Avg load = $\frac{1}{2} (400 + 200) = 300 \text{ kW}$

No. of Units = 8760×300 (Avg load \times No. of hrs)

Max load = 400

(Q) The daily load duration curve of the system is as shown below



$\frac{20}{100}$ Avg load = $\frac{1}{2} (300 + 0)$
 $= 150 \text{ kW}$

No. of units = $150 \times 24 \text{ kWh}$

Max load = 300 kW

PLF = $\frac{150}{300} = \frac{1}{2} = 0.5$
 $= 50\%$

26/1/2010


→ ECONOMIC LOAD DISPATCH:

(i) Pre Load Dispatch (a) Unit Commitment

Select optimally the required no. of generating units from the available healthy units in order to meet the demand over a specified period of time with certain reserve capacity. The reserve capacity is necessary in order to meet the load over and above the demand to maintain the stability of the synchronous machines.

(ii) Online Load Dispatch: Allocate the existing load among the optimally selected units in such a way that the total fuel cost is minimized from time to time i.e. hour to hour basis.


Ex (i)

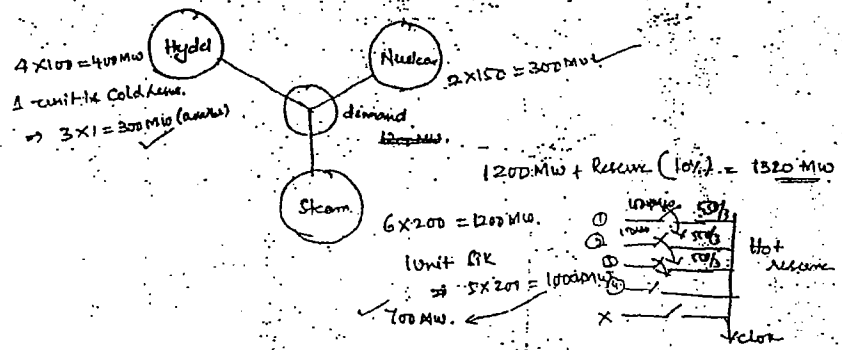

Ex (ii)


Load Cycle.

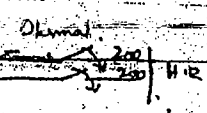- 1) 00 - 3hrs - 750 MW
 $\Rightarrow 300 \text{ Nuclear} + 200 \text{ Hydel} + 150 \text{ Thermal}$
 \therefore Fuel Cost is minimum
- 2) 3hrs - 6hrs - 900 MW
 $\Rightarrow 300 \text{ (N)} + 200 \text{ (H)} + 500 \text{ (Thermal)}$
 \Rightarrow Fuel Cost is minimum
- 3) 6 - 9hrs \Rightarrow 1150 MW
 $\Rightarrow 300 \text{ (N)} + 300 \text{ (H)} + 550 \text{ (Thermal)}$
 $\Rightarrow 300 \text{ (N)} + 300 \text{ (H)} + 400 \text{ (Thermal)}$



→ The unit that is closed (operated) first is to open when the load decreases in the thermal p. station.

→ Fuel Cost Equation:

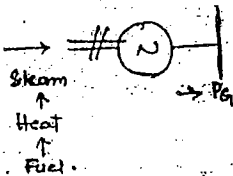


Fuel cost equation

$$F = \frac{1}{2} \alpha P_G^2 + \beta P_G + \gamma \quad \text{Rs/hr.}$$

$$C = \frac{1}{2} \alpha P_G^2 + \beta P_G + \gamma \quad \text{Rs/hr.}$$

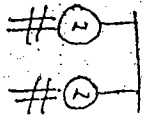If there are n -units connected to the bus, then




$$\text{Fuel cost equation } \Rightarrow F_i = \frac{1}{2} \alpha_i P_{G_i}^2 + \beta_i P_{G_i} + \gamma_i \quad \text{Rs/hr.}$$

$$(i = 1, 2, 3, \dots, n)$$

→ Fuel cost equation is a Non-linear Simultaneous equation.

→ α, β, γ are +ve real co-efficients

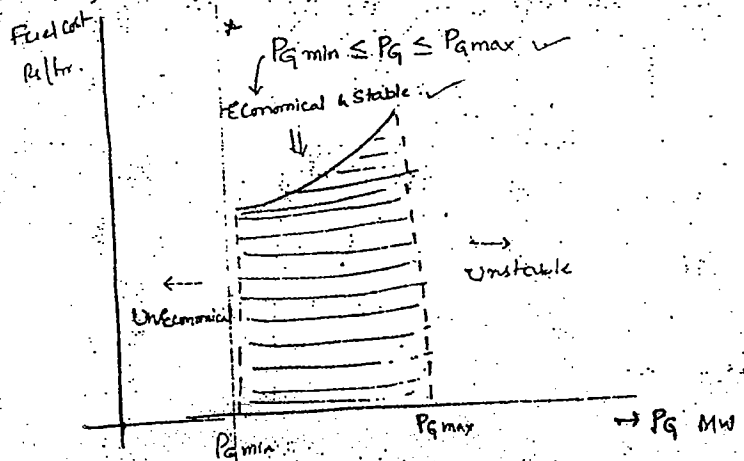

→ Minimize the Fuel cost

$$\frac{dF}{dP_G} = \text{Incremental Fuel cost equation}$$

$$= \alpha P_G + \beta \quad \text{Rs/hr/MW} = \text{Rs/MWhr. (unit for incremental fuel cost)}$$

for n -unit


$$\frac{dF_i}{dP_{gi}} = \alpha_i P_{gi} + \beta_i \quad \text{Rs/Mwhr.}$$

where $i = 1, 2, \dots, n$

α_i is the slope of incremental fuel cost curve

β_i is the interception of the incr. fuel cost curve

→ Graphical Representation

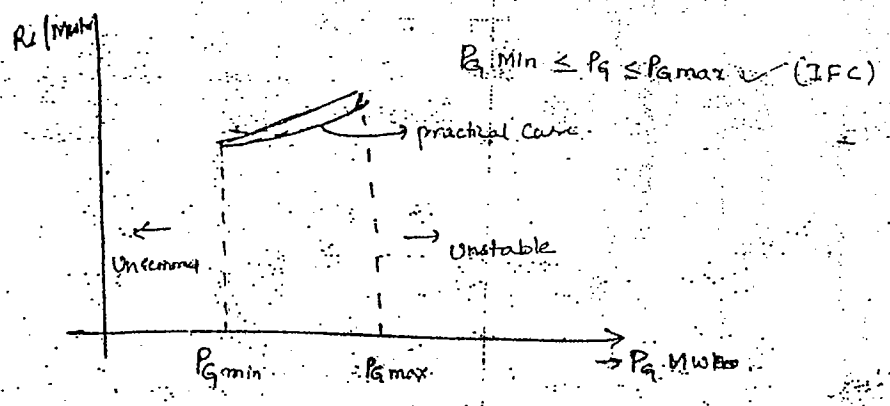

Ex: practical case

For a 200 MW plant

Actual load = 100 MW

Fuel required is 500 Tonnes

If actual load = 200 MW

∴ Fuel required is less than 1000 Tonnes, because of internal efficiency of the system.

→ Two problems in Economic load dispatch.

→ Problem 1: Minimize the total fuel cost of n -generating units which are optimally selected in such a way that the demand on system is equal to the total power generation and the transmission losses are ignored. (loss-less problem)

$$\text{Min } F_T = F_1 + F_2 + \dots + F_n = \sum_{i=1}^n F_i$$

subjected to

$$P_T = P_{g1} + P_{g2} + \dots + P_{gn} = \sum_{i=1}^n P_{gi}$$

} Constrained Minimization

Ex: Design 13.2/220kV power transformer of 100 MVA.

↳ vijay ✓
 CG ✓
 SIEMENS ✓
 L&F X
 Radika X
 VVE X

of 13.2/220kV PTR of 100 MVA with
 No load loss not more than 0.5% of capacity

↳ Conditional manner for design. i.e. Constrained manner.

→ The above problem is having a constraint so that it cannot be solved by using ordinary minimization technique. The solution for the above problem can be obtained by using Simplex method of Optimization technique which says that construct an auxiliary function in terms of the main function along with constraint.

$$\text{Auxiliary function } (F) = \text{Main Function } F_1 + \lambda (\text{constraint})$$

$\lambda \rightarrow$ Lagrangian multiplier of the system.

$$F = \sum_{i=1}^m F_i + \lambda (P_d - \sum_{i=1}^m P_{Ai})$$

↳ Unconstrained Function

→ If the auxiliary function is minimized then the main function will be minimized along with constraints.

$$\therefore \frac{dF}{dP_{Ai}} = \frac{d}{dP_{Ai}} \sum_{i=1}^m F_i + \lambda \left(\frac{dP_d}{dP_{Ai}} - \frac{d}{dP_{Ai}} \sum_{i=1}^m P_{Ai} \right) = 0$$

$$\therefore \frac{d}{dP_{Ai}} (F_1 + F_2 + \dots + F_i + F_m) + \lambda \left(\frac{dP_d}{dP_{Ai}} - \frac{d}{dP_{Ai}} (P_{G1} + P_{G2} + \dots + P_{Gi} + P_{Gn}) \right) = 0$$

$$= \frac{dF_i}{dP_{Ai}} + \lambda (0 - 1) = 0 \quad \left\{ \begin{array}{l} \frac{dF_i}{dP_{Ai}} = 0 \text{ when } i \neq j \\ \frac{dP_{Ai}}{dP_{Ai}} = 1 \text{ when } i = j \end{array} \right.$$

$$\Rightarrow \frac{dF_i}{dP_{Ai}} = \lambda \text{ Rs/MWhr}$$

$$\frac{dF_1}{dP_1} = \frac{dF_2}{dP_2} = \frac{dF_3}{dP_3} = \dots = \frac{dF_n}{dP_n} = \lambda \quad \text{Rs/Mwhr} \rightarrow \textcircled{1}$$

The incremental fuel cost of n -generating units which are optimally selected are same and is equal to the "Lagrangian multiplier" of the system

ASSIGNMENT: (Material Page 69-71)

① Given $F = 0.12 P_G^2 + 20 P_G + 40 \quad \text{Rs/Mwhr}$

$P_G = 200 \text{ MW}$

$\therefore \frac{dF}{dP_G} = 0.24 P_G + 20 \quad \text{Rs/hr}$

$\Rightarrow 75\% \text{ of Capacity} = 150 \quad \left(\frac{75}{100} \times 200 \right)$

$F = 0.12 (150)^2 + 20 (150) + 40 \quad \text{Rs/Mwhr}$

Fuel cost/day = Fuel cost in Rs/hr $\times 24$

$\therefore \frac{dF}{dP_G} = 0.24 (150) + 20 \quad \text{Rs/Mwhr}$

When Full loaded

$F = 0.12 (200)^2 + 20 (200) + 40$

$\frac{dF}{dP_G} =$

② $F_1 = 0.2 P_1^2 + 30 P_1 + 60$

$F_2 = 0.15 P_2^2 + 20 P_2 + 80$

$\lambda = 120$

$\therefore \frac{dF_1}{dP_1} = \frac{dF_2}{dP_2} = \lambda = 120$

~~$P_1 = 200 - 30 / 0.4$~~ ; $P_2 = \frac{120 - 20}{0.3}$

Power received by the load $P_d = P_1 + P_2$ (Assumption: Lossless)

(10) Given $\frac{dF_1}{dP_1} = 0.12P_1 + 16$, $\frac{dF_2}{dP_2} = 0.2P_2 + 24$, $\frac{dF}{dP_2} = 0.15P_2 + 18 = \lambda$

* The Lagrangian multiplier ' λ ' is also called as
 "The cost received for each plant"

(13) $P_1 + P_2 = 150 \rightarrow \textcircled{1}$

$\frac{dF_1}{dP_1} = \frac{dF_2}{dP_2} \Rightarrow 0.1P_1 + 20 = 0.12P_2 + 16$

$\Rightarrow P_1 = \frac{0.12P_2 + 16 - 20}{0.1}$

$P_1 = 1.2P_2 - 40 \rightarrow \textcircled{2}$

From $\textcircled{1}$ $\frac{1.2P_2 - 40 + P_2}{1.2P_2 + P_2 - 40} = 150$

$P_2 = \frac{190}{2.2}$

$= 86.36 \text{ MW}$

$P = 1.2P_2 - 40 = 63.64 \text{ MW}$

$\lambda = 0.1P_1 + 20 = 0.1(63.64) + 20$

$= 0.12P_2 + 16 = 0.12(86.36) + 16$

(Q*) The fuel cost of the 3 units.

$F_1 = 0.1P_{G1}^2 + 20P_{G1} + 40$ A/h $F_2 = 0.15P_{G2}^2 + 16P_{G2} + 20$ R/h


$F_3 = 0.2P_{G3}^2 + 12P_{G3} + 24$ A/h The total load on the system is 600 MW. Neglect the tr. line losses and find the most economical division of the load among the three units.

sol) $P_1 + P_2 + P_3 = 600 \text{ MW}$

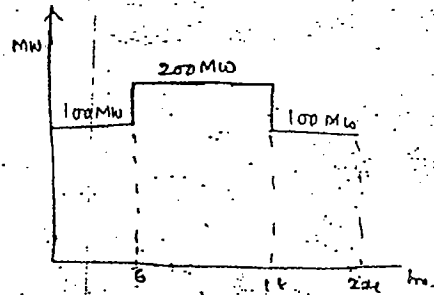(Q4)


$$\left. \begin{aligned} F_1 &= 0.15P_1^2 + 20P_1 + 30 \\ F_2 &= 0.2P_2^2 + 16P_2 + 20 \end{aligned} \right\} \text{Rs/hr.}$$

$$F_T = \underbrace{(F_1 + F_2)}_{100 \text{ MW}} \times 12 + \underbrace{(F_1 + F_2)}_{200 \text{ MW}} \times 12$$



(12) $F_1 = a + bP_1 + cP_1^2$, $F_2 = a + bP_2 + 2cP_2^2$

$$P_1 + P_2 = 300 \text{ MW.}$$

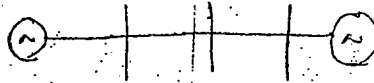

$$\frac{dF_1}{dP_1} = \frac{dF_2}{dP_2} = cP_1 + b = 2cP_2 + b$$

$$P_1 = 2P_2$$

$$2P_2 + P_2 = 300$$

$$P_1 = 200 \text{ MW}, P_2 = 100 \text{ MW}$$

$$(09) \quad \left. \begin{aligned} I_{c1} &= 0.3P_1 + 20, \\ I_{c2} &= 0.4P_2 + 30, \end{aligned} \right\} I_3 = 30 \text{ Rs/Mwhr.}$$

$$50 \leq P_i \leq 800$$

$$I_{c1} = I_{c2} \neq I_{c3}$$

→ The ^{incr. f.c} I_{c3} of unit '3' is 30 Rs/Mwhr, which remain same for any generation of plant '3' hence 300 MW will be assigned for plant '3' and balance 400 MW will be allocated b/w plant 1 and plant 2.

$$I_{c3} = 30 \begin{array}{l} \swarrow 50 \times \\ \searrow 300 \checkmark \end{array}$$

$$\therefore P_{G1} + P_{G2} = 400$$

$$I_{c1} = I_{c2} = 0.3P_1 + 20 = 0.4P_2 + 30$$

$$(07) \quad \begin{aligned} P_{G1} &= -120 + 60I_{c1} - 2.5I_{c1}^2 \\ P_{G2} &= -140 + 40I_{c2} - 2I_{c2}^2 \\ P_{G3} &= -90 + 50I_{c3} - 1.5I_{c3}^2 \end{aligned}$$

$$I_c \rightarrow \text{Rs/Mwhr.}$$

$$P_G = \text{MW.}$$

$$I_{c1} = I_{c2} = I_{c3} = \lambda$$

$$P_{G1} + P_{G2} + P_{G3} = 500$$

$$-120 + 60\lambda - 2.5\lambda^2 - 140 + 40\lambda - 2\lambda^2 - 90 + 50\lambda - 1.5\lambda^2 = 500$$

$$-6\lambda^2 + 150\lambda - 350 = 500$$

$$6\lambda^2 - 150\lambda + 850 = 0$$

$$\lambda = \frac{150 \pm \sqrt{6 \times 850}}{12}$$

$$\lambda = \frac{-150 \pm \sqrt{(150)^2 - 4(-6)(870)}}{2(-6)}$$

$$\lambda = 8.68 \text{ Rs/MWhr } \checkmark \text{ (less)}$$

$$\lambda = 16.31 \text{ Rs/MWhr } \times \text{ (More)}$$

$$P_{G1} = -120 + 60(8.68) - 2.5(8.68)^2 =$$

$$P_{G2} = -140 + 40(8.68) - 2(8.68)^2 =$$

$$P_{G3} = -90 + 50(8.68) - 1.5(8.68)^2 =$$

(22)

$$C_1(P_{G1}) = 0.006 P_{G1}^2 + 8 P_{G1} + 350$$


$$C_2(P_{G2}) = 0.009 P_{G2}^2 + 7 P_{G2} + 400$$

} thousand Rs/hr.

$$100 \text{ MW} \leq P_{G1} < 600 \quad ; \quad 50 \text{ MW} \leq P_{G2} \leq 500.$$

$$\text{Total } P = 600$$

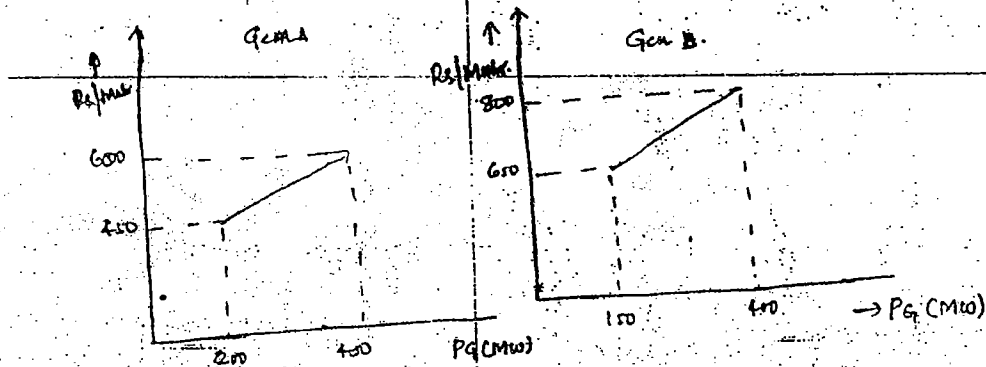Gate-04
 (Q5) The IFC of two generators are as follows.



The most economical division of the load of 700 MW b/w the two units. Neglect the tr. line losses.

Sol

Gen A

Min Gen - 200 - Rs. 450/MWhr.

Max Gen - 400 - Rs. 600/MWhr.

Gen B

Min Gen - 100 MW - Rs. 600/MWhr.

Max Gen - 400 MW - Rs. 800/MWhr.

The incremental fuel cost of a maximum generation for plant 'A' is less than the incremental fuel cost of minimum generation from plant 'B'.

hence $P_{GA} = 450 \text{ MW}$, $P_{GB} = 250 \text{ MW}$

(OG)

$$\frac{dF_1}{dP_1} = 0.1P_1 + 20, \quad \frac{dF_2}{dP_2} = 0.12P_2 + 15$$

Load = 300 MW.
 Capacity of each = 200 MW.

(1) Most economical division

$$P_1 + P_2 = 300 \rightarrow \textcircled{1}$$

$$\frac{dF_1}{dP_1} = \frac{dF_2}{dP_2}$$

$$0.1P_1 + 20 = 0.12P_2 + 15$$

$$\Rightarrow P_1 = \frac{0.12P_2 + 15 - 20}{0.1} = 0.12P_2 - 50 \rightarrow \textcircled{2}$$

$$P_1 = 149.1 \text{ MW}$$

$$P_2 = 150.9 \text{ MW}$$

Total Fuel cost $F = F_1 + F_2 = 0.1 \frac{P_1^2}{2} + 20P_1 + Y_1 + 0.13 \frac{P_2^2}{2} + 15P_2 + Y_2$

~~$F = 0.05(140.9)^2 + 20(140.9) + 0.06(159.1)^2 + 15(159.1) + Y_1 + Y_2$ R/hr.~~

$F =$

(ii) Equal load sharing

$P_1 = P_2 = 150 \text{ Mw}$

Total Fuel cost $F = F_1 + F_2 = 0.05(150)^2 + 20(150) + 0.06(150)^2 + 15(150) + Y_1 + Y_2$ R/hr.

When the load is shared equally the total fuel cost of the system is high so that it is to be called an economical division of the load.

(ii) - (i) = Saving of Fuel cost = R/hr.

Saving / Annum = Saving in R/hr \times 8760

→ Problem 2 (Loss problem)

Minimise the total fuel cost of n generating units which are optimally selected in such a way that the demand on the system and also the transmission line losses are equal to the total power generation.

Min $F_T = \sum_{i=1}^n F_i$

subjected to

$P_d + P_L = \sum_{i=1}^n P_{G_i}$

Constrained
Minimization

$P_L =$ Transmission line loss

→ If the trans. line loss is included for a given demand, then the generation capacity will increase so that fuel cost of the system will increase hence the trans. line loss should be expressed mathematically as a function of generation schedules.

$$P_L = \text{Trans. line loss} = \sum_{i=1}^n \sum_{j=1}^n P_{Gi} B_{ij} P_{Gj} \rightarrow \text{A Non-linear Simultaneous Equation}$$

P_{Gi} = Generation of i^{th} unit

P_{Gj} = Generation of j^{th} unit

B_{ij} = Loss Co-efficient of i^{th} & j^{th} units

n = no. of generating units

* Unit of loss coefficient B_{ij} is MW^{-1} or $\frac{1}{\text{MW}}$

→ To express a trans. line loss.


Ex: 2-bus system.



$$P_L = B_{11} P_{G1}^2 + P_{G1} B_{12} P_{G2} + P_{G2} B_{21} P_{G1} + B_{22} P_{G2}^2$$

⇒ ④ Loss Coefficients

→ For 3-bus system.

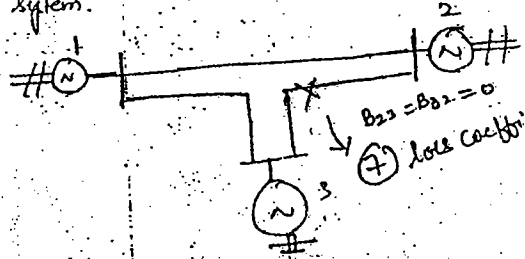

$B_{23} = B_{32} = 0$
 ⇒ ⑦ Loss Coefficients

$$P_L = B_{11} P_{G1}^2 + P_{G1} B_{12} P_{G2} + P_{G1} B_{13} P_{G3} + P_{G2} B_{21} P_{G1} + B_{22} P_{G2}^2 + P_{G2} B_{23} P_{G3} + P_{G3} B_{31} P_{G1} + P_{G3} B_{32} P_{G2} + B_{33} P_{G3}^2$$

⇒ ⑨ Loss Coefficients


→ For 4-bus system

16 Loss Coefficients

For n -Bus system n^2 Loss Coefficients

→ For a given demand if all the loss coefficients are proposed then the total amount of loss will be high so that the generation schedules are high and the total fuel cost of the system is high. However, it is necessary to reduce the transmission loss for a given demand for which some of the loss coefficients must be zero. i.e. by using minimum no. of transmission it should ensure that the power system n/w will be an interconnecting network.

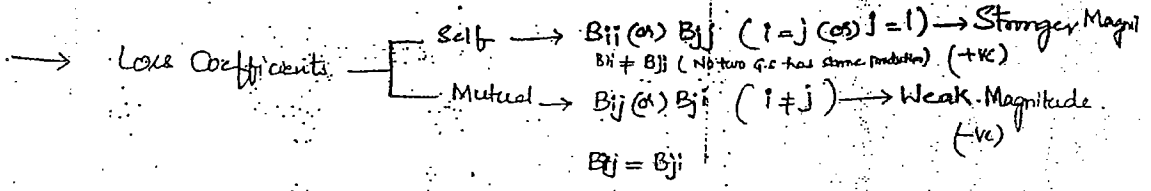→ For a n-bus system the most of the loss coefficients will become zero and there are few loss coefficients which are non-zero's



(Q) Which of the following relations holds good for the loss coefficients

- (i) $B_{11} = B_{12} = 0.008 \therefore B_{21} = B_{22} = 0.006$
- (ii) $B_{11} = 0.008, B_{12} = B_{21} = -0.006, B_{22} = 0.004$
- (iii) $B_{11} = B_{22} = 0.008, B_{12} = B_{21} = +0.004$ ~~$B_{22} = 0.004$~~
- (iv) $B_{11} = 0.006, B_{12} = B_{21} = -0.002, B_{22} = 0.008$ (Magnitude of B_{12}, B_{21} must be less than B_{11}, B_{22})

→ Even though the demand on the system is constant but the connected transmission line loss will change as the generation schedules are changed.

→ Even though the transmission loss changes as the generation changes but the loss coefficient remains same.

Solution:

Auxiliary Function (F) = Main Function $F_r + \lambda$ (constraint)

$$= \sum_{i=1}^n F_i + \lambda (P_d + P_r - \sum_{i=1}^n P_{Gi})$$

Minimize the Aux Function in order to minimize the main function along with constraints.

$$\frac{dF}{dP_{Gi}} = \frac{d}{dP_{Gi}} \left(F_i + \lambda \left(\frac{dP_i}{dP_{Gi}} + \frac{dP_L}{dP_{Gi}} - \frac{d}{dP_{Gi}} \sum_{i=1}^n P_{Gi} \right) \right) = 0$$

$$\frac{dF_i}{dP_{Gi}} + \lambda \left(0 + \frac{dP_L}{dP_{Gi}} - 1 \right) = 0$$

incremental fuel cost

incremental trans. line loss

$$\frac{dF_i}{dP_{Gi}} = \lambda \left(1 - \frac{dP_L}{dP_{Gi}} \right)$$

$$\frac{dF_i}{dP_{Gi}} \times \left(\frac{1}{1 - \frac{dP_L}{dP_{Gi}}} \right) = \lambda$$

$$\frac{dF_i}{dP_{Gi}} \times L_i = \lambda$$

where $L_i =$ Penalty factor of i^{th} unit

$$L_i = \frac{1}{1 - \frac{dP_L}{dP_{Gi}}} \rightarrow \text{Unit loss}$$

$$\frac{dF_i}{dP_{Gi}} L_i = \frac{dF_2}{dP_{G2}} = L_2 = \dots = \frac{dF_n}{dP_{Gn}} L_n = \lambda \rightarrow (2)$$

→ The product of incremental fuel cost & the penalty factor for all the units are same and it is equal to the Lagrangian multiplier of the system.

→ The inclusion of trans. line loss will result as the cost received for each plant (λ) should be more than the received per each plant of a loss less problem. This can understand by multiplying the incremental fuel cost with a penalty factor and the penalty factor are normally slightly more than 1.

$$\frac{dF_i}{dP_{Gi}} = \frac{dF_2}{dP_{G2}} = \frac{dF_3}{dP_{G3}} = \dots = \frac{dF_n}{dP_{Gn}} = \lambda \rightarrow (1)$$


$$\frac{dF_i}{dP_{Gi}} L_i = \frac{dF_2}{dP_{G2}} L_2 = \dots = \frac{dF_n}{dP_{Gn}} L_n = \lambda \rightarrow (2)$$

Eq (2) is the most economical operation of the system since

It is a practical case.

The method for solution above solution is called Penalty Factor Method

→ Special Case:

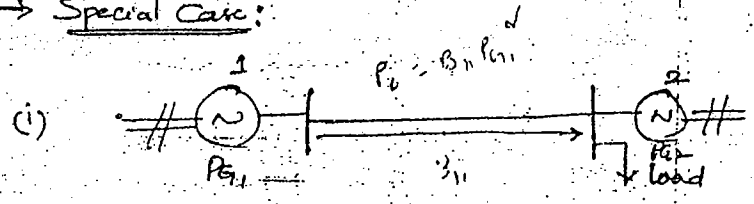

In the above single-line diagram, the total load is placed on station 2. Which of the following relations are holds good for loss coefficient

- (i) $B_{11} \neq B_{12} \neq 0, B_{21} = B_{22} = 0$
- (ii) $B_{11} \neq 0, B_{12} = B_{21} = B_{22} = 0$
- (iii) $B_{11} = B_{12} = B_{21} = 0, B_{22} \neq 0$
- (iv) $B_{11} = B_{22} \neq 0, B_{12} = B_{21} = 0$
- (v) $L_1 = 1.0, L_2 \neq 1.0$
- (vi) $L_1 \neq 0, L_2 = 1.0$
- (vii) $L_1 \neq L_2 \neq 1.0$
- (viii) $L_1 = L_2 = 1.0$

Exp: In the above diagram loss contributed by station '2' is zero. So that the loss coefficients which are associated with station '2' are zero.

Ans: (i)

$$P_L = B_{11} P_{G1}^2$$

(ii)

$$L_2 = \frac{1}{1 - \frac{dL}{dP_{G2}}} = \frac{1}{1 - 0} = 1, L_1 = \frac{1}{1 - \frac{dL}{dP_{G1}}} \neq 1.0$$

$$\frac{dF_1}{dP_{G1}} L_1 = \frac{dF_2}{dP_{G2}} = \lambda$$

↓ loss unit ↓ loss unit

(iii) if load is on station 1 in (i)

Ans: $B_{11} = B_{12} = B_{21} = 0, P_L = B_{22} P_{G2}^2$

$L_1 = 1.0, L_2 \neq 1.0$

$$\frac{dF_1}{dP_{G1}} = \frac{dF_2}{dP_{G2}} (L_2 = \lambda)$$

→ Penalty factor method also applicable for the loss problem, which is defined with Lagrangian Multiplier

$$\frac{dF_1}{dP_{G1}} L_1 = \frac{dF_2}{dP_{G2}} L_2 = \dots = \frac{dF_n}{dP_{Gn}} L_n = \lambda$$

$$P_d = \sum P_G - P_L$$

→ By knowing the Lagrangian multiplier then the corresponding generation schedules are to be calculated. By calculating the generation schedules the connected to line loss will be calculated and finally the power received by the load is also calculated.

However the loss problem is also defined with the demand and in such case the penalty factor method is not suitable.

→ The above problem can be solved by using iterative method but the time taking is high.

→ To reduce the time taking an approximate method is considered which is known as "losses are included but not co-ordinated".

Ex: Two Bus system

$$P_{G1} + P_{G2} - P_L = P_d$$

$$P_{G1} + P_{G2} - [B_{11}P_{G1}^2 + 2B_{12}P_{G1}P_{G2} + B_{22}P_{G2}^2] = P_d \rightarrow \textcircled{1}$$

Eq. ① is non-linear equation with two unknowns (i.e.) P_{G1} & P_{G2}

∴ Replace one with another by considering the entire problem as loss less problem

$$\frac{dF_1}{dP_{G1}} = \frac{dF_2}{dP_{G2}}$$

$$d_1 P_{G1} + B_1 = d_2 P_{G2} + B_2$$

$$P_{G1} = \frac{d_2 P_{G2} + B_2 - B_1}{d_1}$$

Substitute eq (2) in eq (1)

Now equation (1) is non-linear equation with unknown P_{G2} .

$$P_{G2} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

(P_{G2}^I and P_{G2}^{II})


(P_{G1}^I and P_{G1}^I)

(P_{G1}^I, P_{G2}^I), (P_{G1}^{II}, P_{G2}^{II})

$$P_L = \sum P_G = P_d$$

→ The generation schedules which can provide less amount of loss will be considered as the actual generation schedules for a given demand.

→ Special Case

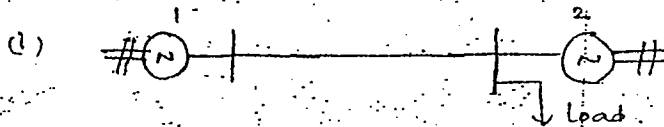

$$P_{G1} + P_{G2} - P_L = P_d$$

$$P_{G1} + P_{G2} - B_{11} P_{G1}^2 = P_d \rightarrow (1)$$

Repeat the above procedure to calculate P_{G1} and P_{G2}

→ Problems (Assignment)

(13) Given $\frac{dF}{dP} = 0.002P + 18$

$$\frac{dL}{dP_G} = 0.2, \quad \lambda = 25$$

$$\frac{dF}{dP_G} \times L = \lambda$$

$$(0.002P + 18) \times \frac{1}{1 - 0.2} = 25$$

$$0.002P + 12 = 25 \times 0.8$$

$$P = 1000 \text{ MW}$$

(15)

$$L_2 = 1.25$$

$$C = 400 \text{ Rs/MWhr}$$

$$\frac{dF}{dP_1} L_1 = \frac{dF_2}{dP_2} L_2 = \lambda$$

$$= 400 \times 1.25 = \lambda$$

$$\Rightarrow 500 \text{ Rs/MWhr}$$

(19)

$$B_{11} = 0.001, B_{22} = 0.002, B_{12} = B_{21} = -0.0008$$


$$P_1 = 150 \text{ MW}, P_2 = 100 \text{ MW}$$

$$P_L = B_{11} P_{G1}^2 + 2B_{12} P_{G1} P_{G2} + B_{22} P_{G2}^2$$

$$= 0.001 \times (150)^2 + 2 \times (-0.0008) \times 150 \times 100 + 0.002 \times (100)^2$$

=

(20)

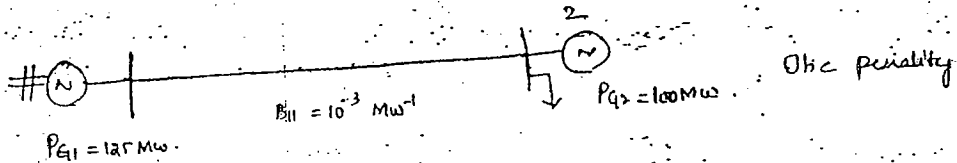

factor of the both the units are

sol

$$L_1 = \frac{1}{1 - \frac{dP_L}{dP_1}} = \frac{1}{1 - 2B_{11}P_{G1}}$$


$$= \frac{1}{1 - 2 \times 10^{-3} \times 125} = 1.33$$

$$P_L = B_{11} P_{G1}^2$$

$$\frac{dP_L}{dP_1} = 2B_{11}P_{G1}$$

$$L_2 = 1.0 \text{ (No loss)}$$

(21)

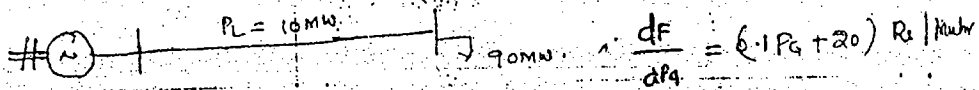

A load of line loss

the penalty factor of the unit and also the Lagrangian multiplier

Sol

pen, fee $L = \frac{1}{1 - \frac{dP_L}{dP_G}}$

$P_G = P_L + P_d$
(10 + 90) MW.

Since $P_L = 10$ MW constant loss since only one unit, we cannot minimize the loss.


→ As the demand is contributed by only one generator so that the loss in the m/w is always constant and the differential loss can be ignored.

$L = \frac{1}{1 - \frac{10}{100}} = \frac{100}{90} = \frac{10}{9}$

$\frac{dF}{dP_G} L = \lambda$

$\Rightarrow (0.1 \times 100 + 20) \times \frac{10}{9} = \lambda$

(16)

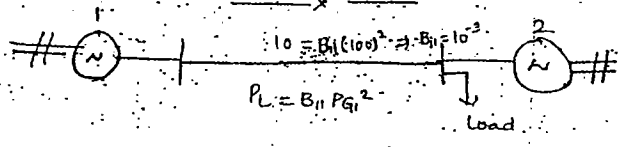

$\lambda = 25 \text{ MW/MW} \quad L_2 = 10$

$\frac{dF_2}{dP_2} = 25$

$0.06 P_{G2} + 19 = 25 \Rightarrow P_{G2} = \frac{25-19}{0.06} \text{ MW}$

$P_{G2} = 100 \text{ MW}$

$\frac{dF_1}{dP_1} L_1 = \lambda = 25$

$(0.02 P_{G1} + 17) \frac{1}{1 - \frac{dP_L}{dP_1}} = 25$

$(0.02 P_{G1} + 17) \frac{1}{1 - 2B_{11} P_{G1}} = 25$

$(0.02 P_{G1} + 17) = 25 (1 - 2B_{11} P_{G1})$

$0.02 P_{G1} + 17 = 25 - 25 \times 2 \times 10^{-3} \times P_{G1}$

$\Rightarrow 0.02 P_{G1} + 25 \times 2 \times 10^{-3} P_{G1} = -17 + 25$

$P_L = B_{11} P_{G1}^2$
 $(P = B_{11} (100)^2)$
 $B_{11} = 10^{-3}$

$$P_{G1} = 114.39 \text{ MW}$$


$$P_{G2} = 100 \text{ MW}$$

$$P_d = P_{G1} + P_{G2} - P_L$$

$$= 114.39 + 100 - \underbrace{10^3 (114.38)^2}_{\text{Numerator}}$$

$$P_d = 214.39$$

(14)

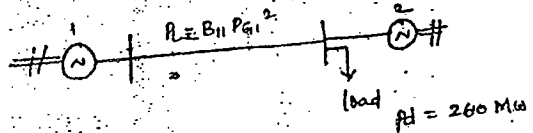

$$P_{G1} + P_{G2} - B_{11} P_{G1}^2 = 260$$

$$P_L = B_{11} P_{G1}^2$$

$$10 = B_{11} (100)^2$$

$$B_{11} = 10^{-3}$$

$$\therefore P_{G1} + P_{G2} - 0.001 P_{G1}^2 = 260 \rightarrow \textcircled{1}$$

Replace P_{G2} in terms of P_{G1}

$$\frac{dP_1}{dP_{G1}} = \frac{dP_2}{dP_{G2}}$$

$$0.02 P_1 + 16 = 0.04 P_2 + 20$$

$$P_{G2} = \frac{0.02 P_{G1} + 16 - 20}{0.04} \rightarrow \textcircled{2}$$

Subst $\textcircled{2}$ in $\textcircled{1}$

$$P_{G1} + 0.5 P_{G1} - 100 - 0.001 P_{G1}^2 = 260$$

$$-0.001 P_{G1}^2 + 1.5 P_{G1} - 360 = 0$$

$$P_{G1} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$P_{G1} = 1200 \text{ MW} \rightarrow P_{G2} = 500 \text{ MW} \quad \times$$

$$P_{G1} = 300 \text{ MW} \rightarrow P_{G2} = 50 \text{ MW} \quad \checkmark \quad (\text{Since load } P_L = 260 \text{ MW})$$

(20)

$$P_L = B_{11}P_{G1} + 2B_{12}P_{G1}P_{G2} + B_{22}P_{G2}^2$$

$$\frac{dR}{dP_{G1}} = 2B_{11}P_{G1} + 2B_{12}P_{G2}$$

$$\frac{dR}{dP_{G2}} = 2B_{12}P_{G1} + 2B_{22}P_{G2}$$

$$\frac{dF_1}{dP_{G1}} L_1 = \lambda = 2.6$$

$$(0.01P_{G1} + 20) \times \frac{1}{1 - \frac{dR}{dP_{G1}}} = (0.01P_{G1} + 2) \times \frac{1}{1 - 2B_{11}P_{G1} - 2B_{12}P_{G2}} = 2.6$$

$$\Rightarrow (0.01P_{G1} + 2) \times \frac{1}{1 - 2 \times 0.0015P_{G1} + 2 \times 0.0005P_{G2}} = 2.6$$

$$= \frac{0.01P_{G1} + 2.6 \times 2 \times 0.0015P_{G1} - 2.6 \times 2 \times 0.0005P_{G2}}{P_{G1}} = 2.6 - 2 = 0.6$$

$$P_{G1} = 0.6$$

114.

$$\frac{dF_2}{dP_{G2}} L_2 = \lambda$$

$$(0.01P_{G2} + 1.5) \times \frac{1}{(1 - 2B_{12}P_{G1} - 2B_{22}P_{G2})} = 2.6$$

$$0.01P_{G2} + 1.5 = 2.6(1 + 2 \times 0.0005P_{G1} - 2 \times 0.0005P_{G2})$$

$$- 2.6 \times 2 \times 0.0005P_{G1} + 0.01P_{G2} + 2.6 \times 0.0005P_{G2} = 2.6 - 1.5 = 1.1 \rightarrow \textcircled{2}$$

From eq's ① & ② $P_{G1} =$

$P_{G2} =$