

# **NETWORK ANALYSIS**

**Theory, Example and Practice**



**GATE GUIDE**

# **NETWORK ANALYSIS**

**Theory, Example and Practice**

**R. K. Kanodia**

**Ashish Murolia**

**JHUNJHUNUWALA**  
**JAIPUR**

**Exclusive Sales Counter & BO:**

**NODIA & COMPANY**

55, Suryalok Complex, Gunfoundry, Abids, Hyderabad – 500001.

Phone : 040 – 64582577

**Network Analysis : Theory, Example & Practice, 1e**

**R. K. Kanodia, Ashish Murolia**

AA1213

Copyright © by Jhunjhunuwala

Information contained in this book has been obtained by author, from sources believes to be reliable. However, neither Jhunjhunuwala nor its author guarantee the accuracy or completeness of any information herein, and Jhunjhunuwala nor its author shall be responsible for any error, omissions, or damages arising out of use of this information. This book is published with the understanding that Jhunjhunuwala and its author are supplying information but are not attempting to render engineering or other professional services.

**JHUNJHUNUWALA**

B-8, Dhanshree Tower Ist, Central Spine, Vidyadhar Nagar, Jaipur – 302023

Ph : +91–141–2101150.

[www.nodia.co.in](http://www.nodia.co.in)

email : [enquiry@nodia.co.in](mailto:enquiry@nodia.co.in)

---

Printed By: Nodia & Company, Jaipur

# The GATE GUIDE

The GATE GUIDE is an exclusive series of books authored by RK Kanodia & Ashish Murolia, published by JHUNJHUNUWALA. GATE GUIDE is intended to provide best content to the students preparing for GATE(Electronics & Communication Engineering). The GATE examination consists of multiple choice problems which are tricky, conceptual and evaluates the fundamental understanding of the subject. As an GATE aspirant your study should be emphasized on the following points all which are incorporated in each GATE GUIDE.

**Brief and Explicit Theory which covers all the Topics:** The syllabus of GATE examination includes all the subjects of under graduation which you have to study in a short span of your preparation. Therefore, theory should be point-to-point and explicit which develops the fundamentals of the subject. Additionally, it should give you the whole coverage of the syllabus.

**Concepts & Formulas:** The questions appeared in GATE are numerical as well as conceptual. Your study must incorporate all the concepts and formulas which should be highlighted for a quick reading.

**Step-by-step Problem Solving Methodology:** For solving different kind of numerical problems, a particular methodology should be followed. Note that for a specific problem alternate methods can be used. The best method is one which is much simpler and less time consuming.

**Well-explained Examples:** Solved examples gives a good understanding of the solution methodologies. They enhance the problem solving skills. Also, it makes you to choose the best solution between alternate methods.

**Practice Exercise:** Only theory is not sufficient for a good score. You need to practice as much questions as you can. Remember that, similar questions do not give the whole breadth of the syllabus. There should be a variety of questions which covers all the topics.

GATE GUIDE is first of its kind ever published for GATE aspirants. GATE GUIDE is available in the following subjects:

- ★ Signals & System
- ★ Network Analysis
- ★ Communication System
- ★ Control System

## *Preface To The First Edition*

The stupendous response for the first title of the series GATE GUIDE Signals & Systems encouraged us to present GATE GUIDE Network Analysis. Over the last few decades, numerous text books have been published on this subject. But, still the students face difficulties when they begin preparing for an competitive examination like GATE. The reason behind is that most texts are too large, tedious and based on universities syllabus. There is no book which has been designed thoroughly for an engineering competitive examination.

This book is intended to provide a complete and straight forward coverage of the subject of Network Analysis for the GATE examination. The book has been categorized into fifteen chapters which covers whole breadth of the syllabus of Network Analysis for GATE Electronics & Communication Engineering. The notable feature of this book is the explicit theory, problem solving methodologies, solved examples and practice exercises given in each chapter. The text is written in very clear and matter-of-fact style. We try to prevent excessive text which hides core concepts of the subject and dissipates a lot of time. Important formulas and concepts are highlighted in the text screen for quick reading.

Problem solving is fundamental to the study of circuit analysis. Each chapter contains step-by-step problem solving methodology, by following which student feels enable to solve almost each variety of problem in circuit analysis. Solved examples are incorporated after each methodology and are solved by using same procedure given in methodology. Solved examples strengthen your problem solving skills and makes you confident in solving problems. We have taken the solved examples in form of multiple choices questions considering the fact that GATE examination is based on multiple choice questions only.

Once you go through text and solved examples the practice exercises become easier to solve. Practice exercises are graded as *exercise A* and *exercise B* on the basis of complexity of questions. Also, exercise A organizes question in particular order of theory, whereas in exercise B questions are ordered randomly. Answer key of each practice exercise is given at the end of the book to enlighten you, if you get a correct answer for the problem. Each question of practice exercise is compiled as exam like as possible.

Although we have put a vigorous effort in preparing this book, some errors may have crept in. We shall appreciate and greatly acknowledge the comments, criticism and suggestion from the users of this book which leads to some improvement. You may write to us at [raj कुमार.kanodia@gmail.com](mailto:raj कुमार.kanodia@gmail.com) and [ashish.murolia@gmail.com](mailto:ashish.murolia@gmail.com)

Wish you all the success in conquering GATE.

Authors

# AT A GLANCE

## 1. Brief Theory

Each chapter comprises brief theory covering all the topics. It is very explicit and provides a clear understanding of the topics.

## 2. Problem Solving Method

a step by step approach for problem solving procedures.

## 3. Solved Example (Multiple Choice)

Each topic is followed by a Multiple choice solved example which has a significant relevance with theory.

Initial current through inductor is  $i_L(0^-) = 2$  A.  
Hence (C) is correct option.

### 14.6 CIRCUIT ANALYSIS IN THE $s$ -DOMAIN

All the circuit analysis techniques that we have studied for pure resistive networks may be used in  $s$ -domain analysis. The node voltage method, mesh current method, source transformations, and Thevenin-Norton equivalents are all valid techniques in the  $s$ -domain. These can be applied using same methodologies as we discussed for resistive networks.

The step-by-step procedure of circuit analysis in the  $s$ -domain is given below.

#### M E T H O D O L O G Y

1. Draw the circuit into  $s$ -domain by substituting an  $s$ -domain equivalent for each circuit element. The inductors and capacitors are replaced by their equivalent discussed in previous section.
2. Apply any circuit analysis technique to obtain the desired voltage or current in the  $s$ -domain.
3. Take inverse Laplace transform to convert the voltages and/or currents back to the time domain.

For transient circuits, first we find initial capacitor voltages and inductor currents. To obtain this, we draw the circuit for  $t < 0$ , by replacing all capacitors with open circuits and all inductors with short circuits. After that follow the steps 1, 2 and 3.

#### ► EXAMPLE

For  $t > 0$ , the voltage  $v_o(t)$  in the following network, will be



- (A)  $v_o(t) = 2(1 - e^{-4t})u(t)$  V
- (B)  $v_o(t) = (-8 + 10e^{-4t})u(t)$  V
- (C)  $v_o(t) = (8 - 10e^{-4t})u(t)$  V
- (D)  $v_o(t) = 2(1 - 5e^{-4t})u(t)$  V

#### SOLUTION :

**Step 1:** Taking zero initial condition and transforming the circuit into  $s$ -domain as shown in figure.

**Step 2:** Applying mesh analysis to the circuit

Mesh 1:  $I_1(s) = -4/s$

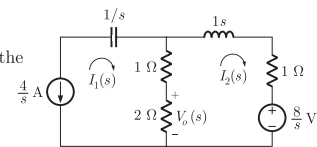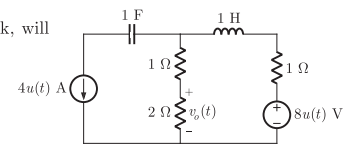

#### 4. Marginal Notes

Marginal notes are extra source of learning. They emphasize useful concepts, summarized text and indicates common mistakes that students need to avoid.

#### 5. Text Screen

Useful concepts, theorems and formulas are highlighted into text screen for a quick reading.

For any linear resistive circuit, any output voltage or current, denoted by the variable  $y$ , is related linearly to the independent sources(inputs), i.e.,

$$y = a_1x_1 + a_2x_2 + \dots + a_nx_n$$

where  $x_1, x_2, \dots, x_n$  are the voltage and current values of the independent sources in the circuit and  $a_1$  through  $a_m$  are properly dimensioned constants.

Thus, a linear circuit is one whose output is linearly related (or directly proportional) to its input. For example, consider the linear circuit shown in figure 5.2.1. It is excited by an input voltage source  $V_s$ , and the current through load  $R$  is taken as output(response).

Suppose  $V_s = 5 \text{ V}$  gives  $I = 1 \text{ A}$ . According to the linearity principle,  $V_s = 10 \text{ V}$  will give  $I = 2 \text{ A}$ . Similarly,  $I = 4 \text{ mA}$  must be due to  $V_s = 20 \text{ mV}$ . Note that ratio  $V_s/I$  remains constant, since the system is linear.

We know that the relationship between power and voltage (or current) is not linear. Therefore, linearity does not applicable to power calculations..


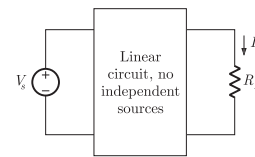


Fig 5.2.1 A linear circuit
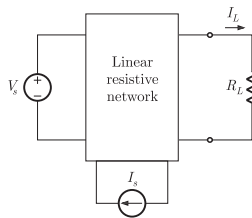
#### ▶ EXAMPLE

For the circuit shown in figure, some measurements are made and listed in the table below.



	$V_s$	$I_s$	$I_L$
1.	7 V	3 A	1 A
2.	9 V	1 A	3 A

If  $V_s = 10 \text{ V}$  and  $I_s = 4 \text{ V}$ , then the value of  $I_L$  will be

- (A) 1.6 A
- (B) 4.4 A
- (C) 3.2 A
- (D) 6.4 A



## 6. Practice Exercise

Practice exercises covers variety of problems from each topic that enhance your confidence level. Practice exercises are divided into two levels on the basis of complexity.

### PRACTICE A

**MCQ 8.1.1** The current in an *RLC* circuit is described by the equation

$$\frac{d^2 i(t)}{dt^2} + 8 \frac{di(t)}{dt} + 16i(t) = 0$$

What is the natural frequency for the circuit ?

- (A)  $-2$  rad/sec                      (B)  $-8$  rad/sec  
(C)  $-4$  rad/sec                      (D)  $-12$  rad/sec

**MCQ 8.1.2** The current in a series *RLC* network is given by

$$i(t) = Ae^{-\alpha t} + Be^{-\beta t}, \quad A \text{ \& B are constants}$$

The damping factor will be equal to

- (A) 2.68                                  (B) 0.6  
(C) 1.2                                    (D) 1.34

**MCQ 8.1.3** A series *RLC* circuit has  $R = 4 \Omega$  and  $C = 2 \text{ F}$ . The value of  $L$  so that the circuit is critically damped, will be

- (A) 4 H                                    (B) 2 H  
(C) 16 H                                 (D) 8 H

**Statement for Questions 4-6 :**

A parallel *RLC* circuit has the following parameters;  $R = 1 \text{ k}\Omega$ ,  $L = 12.5 \text{ H}$ , and  $C = 2 \mu\text{F}$ .

**MCQ 8.1.4** What type of damping does the circuit exhibit ?

- (A) critical damping                      (B) under damping  
(C) over damping                        (D) none of these

**MCQ 8.1.5** What value of  $R$  will cause a damped frequency of 120 rad/sec ?


- (A) 3.12 k $\Omega$                               (B) 1.56 k $\Omega$   
(C) 6.41 k $\Omega$                               (D) 12.82 k $\Omega$

**MCQ 8.1.6** What value of  $R$  will result in a critically damped response ?

- (A) 2 k $\Omega$                                   (B) 2.5 k $\Omega$   
(C) 5 k $\Omega$                                   (D) 1.25 k $\Omega$
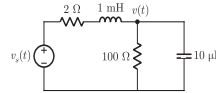
### PRACTICE B

**MCQ 8.2.1** The differential equation for the circuit shown below is



- (A)  $v''(t) + 3000v'(t) + 1.02 \times 10^8 v(t) = 10^8 v_s(t)$   
(B)  $v''(t) + 1000v'(t) + 1.02 \times 10^8 v(t) = 10^8 v_s(t)$   
(C)  $\frac{v''(t)}{10^8} + \frac{2v'(t)}{10^5} + 1.02v(t) = v_s(t)$   
(D)  $\frac{v''(t)}{10^8} + \frac{2v'(t)}{10^5} + 1.98v(t) = v_s(t)$

**MCQ 8.2.2** In a parallel *RLC* circuit the voltage across inductor and current through the capacitor are given as


$$v_L(t) = (20e^{-4t} \cos 2t - 80e^{-4t} \sin 2t) \text{ V}$$

$$i_C(t) = (-6e^{-4t} \cos 2t + 7e^{-4t} \sin 2t) \text{ A}$$

What are the values of parameters  $R$ ,  $L$  and  $C$  ?

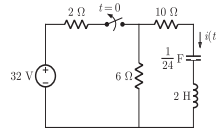- (A)  $R = 10 \Omega$ ,  $L = 1 \text{ H}$ ,  $C = 50 \text{ mF}$   
(B)  $R = 5 \Omega$ ,  $L = 2 \text{ H}$ ,  $C = 25 \text{ mF}$   
(C)  $R = 3.33 \Omega$ ,  $L = 1.33 \text{ mH}$ ,  $C = 37.5 \text{ mF}$   
(D)  $R = 5 \Omega$ ,  $L = 1 \text{ H}$ ,  $C = 50 \text{ mF}$

**MCQ 8.2.3** In the following network, the switch opens instantaneously at  $t = 0$ . The current  $i(t)$  for  $t > 0$  will be



# SYLLABUS

## GATE ELECTRONICS & COMMUNICATION ENGINEERING

### **Networks:**

Network graphs: matrices associated with graphs; incidence, fundamental cut set and fundamental circuit matrices. Solution methods: nodal and mesh analysis. Network theorems: superposition, Thevenin and Norton's maximum power transfer, Wye-Delta transformation. Steady state sinusoidal analysis using phasors. Linear constant coefficient differential equations; time domain analysis of simple RLC circuits, Solution of network equations using Laplace transform: frequency domain analysis of RLC circuits. 2-port network parameters: driving point and transfer functions. State equations for networks.

## IES ELECTRONICS & TELECOMMUNICATION ENGINEERING

### **Networks Theory:**

Network analysis techniques; Network theorems, transient response, steady state sinusoidal response; Network graphs and their applications in network analysis; Tellegen's theorem. Two port networks; Z, Y, h and transmission parameters. Combination of two ports, analysis of common two ports. Network functions : parts of network functions, obtaining a network function from a given part. Transmission criteria : delay and rise time, Elmore's and other definitions effect of cascading. Elements of network synthesis.

# CONTENTS

## CHAPTER 1

### BASIC CONCEPTS

1

1.1	INTRODUCTION TO CIRCUIT ANALYSIS	2
1.2	BASIC ELECTRIC QUANTITIES OR NETWORK VARIABLES	2
1.2.1	Charge	2
1.2.2	Current	3
1.2.3	Voltage	6
1.2.4	Power	8
1.2.5	Energy	11
1.3	CIRCUIT ELEMENTS	12
1.3.1	Active & Passive Elements	12
1.3.2	Bilateral & Unilateral Elements	12
1.3.3	Linear & Non-linear Elements	12
1.3.4	Lumped & Distributed Elements	13
1.4	SOURCES	13
1.4.1	Independent Sources	13
1.4.2	Dependent Sources	15
	Practice A	16
	Practice B	25

## CHAPTER 2

### BASIC LAWS

37

2.1	INTRODUCTION	38
2.2	OHM'S LAW & RESISTANCE	38
2.3	BRANCHES, NODES & LOOPS	41
2.4	KIRCHHOFF'S LAW	42
2.4.1	Kirchhoff's Current Law	42
2.4.2	Kirchhoff's Voltage Law	45
2.5	SERIES RESISTANCES AND VOLTAGE DIVISION	46

2.6	PARALLEL RESISTANCES AND CURRENT DIVISION	48
-----	---	----

2.7	SOURCES IN SERIES OR PARALLEL	51
-----	-------------------------------	----

2.7.1	Series Connection of Voltage Sources	51
2.7.2	Parallel Connection of Identical Voltage Sources	52
2.7.3	Parallel Connection of Current Sources	52
2.7.4	Series Connection of Identical Current Sources	53
2.7.5	Series & Parallel Connection of Voltage & Current Sources	55

2.8	ANALYSIS OF SIMPLE RESISTIVE CIRCUIT WITH A SINGLE SOURCE	55
-----	---	----

2.9	ANALYSIS OF SIMPLE RESISTIVE CIRCUIT WITH A DEPENDENT SOURCE	58
-----	--	----

2.10	DELTA - TO - WYE ( $\Delta$ - Y) TRANSFORMATION	60
------	---	----

2.10.1	Wye To Delta Conversion	61
2.10.2	Delta To Wye Conversion	61

2.11	NON-IDEAL SOURCES	63
------	-------------------	----

	Practice A	64
--	------------	----

	Practice B	86
--	------------	----

## CHAPTER 3

### GRAPH THEORY

105

3.1	INTRODUCTION	106
-----	--------------	-----

3.2	NETWORK GRAPH	107
-----	---------------	-----

3.2.1	Directed and Undirected Graph	106
3.2.2	Planar and Non-planar Graph	107
3.2.3	Subgraph	107
3.2.4	Connected Graphs	108
3.2.5	Degree of Vertex	108

<b>3.3 TREE AND CO-TREE</b>	<b>109</b>
3.3.1 Twigs and Links	111
<b>3.4 INCIDENCE MATRIX</b>	<b>113</b>
3.4.1 Properties of Incidence Matrix	116
3.4.2 Incidence Matrix and KCL	118
<b>3.5 TIE-SET</b>	<b>118</b>
3.5.1 Tie-set Matrix	120
3.5.2 Tie-set Matrix and KVL	121
3.5.3 Tie-set Matrix and Branch Currents	122
<b>3.6 CUT-SET</b>	<b>123</b>
3.6.1 Fundamental Cut-set	125
3.6.2 Fundamental Cut-set Matrix	126
3.6.3 Fundamental Cut-set Matrix and KCL	129
3.6.4 Tree Branch Voltage and Fundamental Cut-set Voltage	130
Practice A	131

## CHAPTER 4

### **NODAL AND LOOP ANALYSIS 141**

4.1 INTRODUCTION	142
4.2 NODAL ANALYSIS	142
4.3 MESH ANALYSIS	149
4.4 COMPARISON BETWEEN NODAL ANALYSIS AND MESH ANALYSIS	154
Practice A	155
Practice B	167

## CHAPTER 5

### **CIRCUIT THEOREMS 179**

5.1 INTRODUCTION	180
5.2 LINEARITY	180
5.3 SUPERPOSITION	184
5.4 SOURCE TRANSFORMATION	188

5.4.1 Source Transformation For Dependent Source	192
--	-----

### **5.5 THEVENIN'S THEOREM 193**

5.5.1 Thevenin's Voltage	194
5.5.2 Thevenin's Resistance	195
5.5.3 Circuit Analysis Using Thevenin's Equivalent	202

### **5.6 NORTON'S THEOREM 203**

5.6.1 Norton's Current	204
5.6.2 Norton's Resistance	205

### **5.7 TRANSFORMATION BETWEEN THEVENIN'S & NORTON'S EQUIVALENT CIRCUIT 208**

### **5.8 MAXIMUM POWER TRANSFER THEOREM 210**

### **5.9 RECIPROCITY THEOREM 214**

### **5.10 SUBSTITUTION THEOREM 218**

### **5.11 MILLMAN'S THEOREM 220**

### **5.12 TELLEGEN'S THEOREM 221**

Practice A	222
------------	-----

Practice B	239
------------	-----

## CHAPTER 6

### **INDUCTOR AND CAPACITOR 253**

#### **6.1 CAPACITOR 254**

6.1.1 Voltage-Current Relationship of a Capacitor	254
6.1.2 Energy Stored In a Capacitor	258
6.1.3 Some Properties of an Ideal Capacitor	260

#### **6.2 SERIES & PARALLEL CAPACITORS 261**

6.2.1 Capacitors in Series	261
6.2.2 Capacitors in Parallel	262

#### **6.3 INDUCTOR 265**

6.3.1 Voltage-Current Relationship of an Inductor	265
6.3.2 Energy Stored in an Inductor	269

6.3.3	Some Properties of an Ideal Inductor	270
<b>6.4</b>	<b>SERIES &amp; PARALLEL INDUCTORS</b>	<b>270</b>
6.4.1	Inductors in Series	270
6.4.2	Inductors in Parallel	271
<b>6.5</b>	<b>DUALITY</b>	<b>273</b>
Practice A		276
Practice B		291

## **CHAPTER 7**

### **FIRST ORDER RL AND RC CIRCUITS 305**

<b>7.1</b>	<b>INTRODUCTION</b>	<b>306</b>
<b>7.2</b>	<b>SOURCE FREE OR ZERO-INPUT RESPONSE</b>	<b>306</b>
7.2.1	Source-Free $RC$ Circuit	306
7.2.2	Source-Free $RL$ Circuit	310
<b>7.3</b>	<b>THE UNIT STEP FUNCTION</b>	<b>312</b>
<b>7.4</b>	<b>DC OR STEP RESPONSE OF FIRST ORDER CIRCUIT</b>	<b>314</b>
<b>7.5</b>	<b>STEP RESPONSE OF AN <math>RC</math> CIRCUIT</b>	<b>314</b>
7.5.1	Complete Response	316
7.5.2	Complete Response in Terms of Initial and Final Conditions	316
<b>7.6</b>	<b>STEP RESPONSE OF AN <math>RL</math> CIRCUIT</b>	<b>317</b>
7.6.1	Complete Response	318
7.6.2	Complete Response in Terms of Initial and Final Condition	319
<b>7.7</b>	<b>STEP BY STEP APPROACH TO SOLVE <math>RL</math> &amp; <math>RC</math> CIRCUITS</b>	<b>319</b>
7.7.1	Solution Using Capacitor Voltage or Inductor Current	319
7.7.2	General Method	328
<b>7.8</b>	<b>STABILITY OF FIRST ORDER CIRCUITS</b>	<b>332</b>
Practice A		334

Practice B	350
------------	-----

## **CHAPTER 8**

### **SECOND ORDER CIRCUITS 365**

<b>8.1</b>	<b>INTRODUCTION</b>	<b>366</b>
<b>8.2</b>	<b>SOURCE FREE SERIES <math>RLC</math> CIRCUIT</b>	<b>366</b>
<b>8.3</b>	<b>SOURCE FREE PARALLEL <math>RLC</math> CIRCUIT</b>	<b>371</b>
<b>8.4</b>	<b>STEP BY STEP APPROACH OF SOLVING SECOND ORDER CIRCUITS</b>	<b>375</b>
<b>8.5</b>	<b>STEP RESPONSE OF SERIES <math>RLC</math> CIRCUIT</b>	<b>379</b>
<b>8.6</b>	<b>STEP RESPONSE OF PARALLEL <math>RLC</math> CIRCUIT</b>	<b>381</b>
<b>8.7</b>	<b>THE LOSSLESS <math>LC</math> CIRCUIT</b>	<b>383</b>
Practice A		386
Practice A		400

## **CHAPTER 9**

### **SINUSOIDAL STEADY STATE ANALYSIS 411**

<b>9.1</b>	<b>INTRODUCTION</b>	<b>412</b>
<b>9.2</b>	<b>CHARACTERISTICS OF SINUSOID</b>	<b>412</b>
<b>9.3</b>	<b>PHASORS</b>	<b>415</b>
<b>9.4</b>	<b>PHASOR RELATIONSHIP FOR CIRCUIT ELEMENTS</b>	<b>417</b>
9.4.1	The Resistor	418
9.4.2	The Inductor	418
9.4.3	The Capacitor	419
<b>9.5</b>	<b>IMPEDANCE &amp; ADMITTANCE</b>	<b>421</b>
9.5.1	Admittance	424
<b>9.6</b>	<b>KIRCHHOFF'S LAWS IN THE PHASOR DOMAIN</b>	<b>425</b>

9.6.1	Kirchhoff's Voltage Law (KVL)	425
9.6.2	Kirchhoff's Current Law (KCL)	426
<b>9.7</b>	<b>IMPEDANCE COMBINATIONS</b>	<b>428</b>
9.7.1	Impedance in Series & Voltage Division	428
9.7.2	Impedance in Parallel & Current Division	429
9.7.3	Delta-to-Wye Transformation	432
<b>9.8</b>	<b>CIRCUIT ANALYSIS IN PHASOR DOMAIN</b>	<b>434</b>
9.8.1	Nodal Analysis	434
9.8.2	Mesh Analysis	435
9.8.3	Superposition Theorem	436
9.8.4	Source Transformation	437
9.8.5	Thevenin & Norton Equivalent Circuits	439
<b>9.9</b>	<b>PHASOR DIAGRAMS</b>	<b>441</b>
	Practice A	445
	Practice B	462

## **CHAPTER 10**

### **AC POWER ANALYSIS 481**

<b>10.1</b>	<b>INTRODUCTION</b>	<b>482</b>
<b>10.2</b>	<b>INSTANTANEOUS POWER</b>	<b>482</b>
<b>10.3</b>	<b>AVERAGE POWER</b>	<b>483</b>
<b>10.4</b>	<b>EFFECTIVE OR RMS VALUE OF PERIODIC WAVEFORM</b>	<b>487</b>
<b>10.5</b>	<b>COMPLEX POWER</b>	<b>489</b>
10.5.1	Alternative Forms for Complex Power	490
<b>10.6</b>	<b>POWER FACTOR</b>	<b>494</b>
<b>10.7</b>	<b>MAXIMUM AVERAGE POWER TRANSFER THEOREM</b>	<b>499</b>
10.7.1	Maximum Average Power Transfer, when $Z$ is Restricted	502
<b>10.8</b>	<b>AC POWER CONSERVATION</b>	<b>503</b>

<b>10.9</b>	<b>POWER FACTOR CORRECTION</b>	<b>503</b>
	Practice A	506
	Practice B	518

## **CHAPTER 11**

### **THREE PHASE CIRCUITS 529**

<b>11.1</b>	<b>INTRODUCTION</b>	<b>530</b>
<b>11.2</b>	<b>BALANCED THREE PHASE VOLTAGE SOURCES</b>	<b>530</b>
11.2.1	Y-connected Three-Phase Voltage Source	530
11.2.2	$\Delta$ -connected Three-Phase Voltage Source	533
<b>11.3</b>	<b>BALANCED THREE-PHASE LOADS</b>	<b>536</b>
11.3.1	Y-connected Load	536
11.3.2	$\Delta$ -connected Load	536
<b>11.4</b>	<b>ANALYSIS OF BALANCED THREE-PHASE CIRCUITS</b>	<b>538</b>
11.4.1	Balanced Y-Y Connection	539
11.4.2	Balanced Y- $\Delta$ Connection	541
11.4.3	Balanced $\Delta$ - $\Delta$ Connection	543
11.4.4	Balanced $\Delta$ -Y Connection	546
<b>11.5</b>	<b>POWER IN A BALANCED THREE-PHASE SYSTEM</b>	<b>548</b>
<b>11.6</b>	<b>TWO-WATTMETER POWER MEASUREMENT</b>	<b>550</b>
	Practice A	553
	Practice B	564

## **CHAPTER 12**

### **MAGNETICALLY COUPLED CIRCUITS 569**

<b>12.1</b>	<b>INTRODUCTION</b>	<b>570</b>
<b>12.2</b>	<b>MUTUAL INDUCTANCE</b>	<b>570</b>
<b>12.3</b>	<b>DOT CONVENTION</b>	<b>571</b>

<b>12.4 ANALYSIS OF CIRCUITS HAVING COUPLED INDUCTORS</b>	<b>574</b>
<b>12.5 SERIES CONNECTION OF COUPLED COILS</b>	<b>577</b>
12.5.1 Series Adding Connection	577
12.5.2 Series Opposing Connection	578
<b>12.6 PARALLEL CONNECTION OF COUPLED COILS</b>	<b>579</b>
<b>12.7 ENERGY STORED IN A COUPLED CIRCUIT</b>	<b>581</b>
12.7.1 Coefficient of Coupling	583
<b>12.8 THE LINEAR TRANSFORMER</b>	<b>584</b>
12.8.1 T-equivalent of a Linear Transformer	585
12.8.2 $\pi$ -equivalent of a Linear Transformer	585
<b>12.9 THE IDEAL TRANSFORMER</b>	<b>587</b>
12.9.1 Reflected Impedance	590
Practice A	592
Practice B	602

## **CHAPTER 13**

### **FREQUENCY RESPONSE 611**

<b>13.1 INTRODUCTION</b>	<b>612</b>
<b>13.2 TRANSFER FUNCTIONS</b>	<b>612</b>
13.2.1 Poles and Zeros	615
<b>13.3 RESONANT CIRCUIT</b>	<b>615</b>
13.3.1 Series Resonance	616
13.3.2 Parallel Resonance	623
<b>13.4 PASSIVE FILTERS</b>	<b>631</b>
13.4.1 Low Pass Filter	631
13.4.2 High Pass Filter	633
13.4.3 Band Pass Filter	635
13.4.4 Band Stop Filter	636
<b>13.5 EQUIVALENT SERIES AND PARALLEL COMBINATION</b>	<b>638</b>

<b>13.6 SCALING</b>	<b>640</b>
13.6.1 Magnitude Scaling	640
13.6.2 Frequency Scaling	640
13.6.3 Magnitude & Frequency Scaling	641
Practice A	643
Practice B	653

## **CHAPTER 14**

### **CIRCUIT ANALYSIS USING LAPLACE TRANSFORM 661**

<b>14.1 INTRODUCTION</b>	<b>662</b>
<b>14.2 DEFINITION OF THE LAPLACE TRANSFORM</b>	<b>662</b>
14.2.1 Laplace Transform of Some Basic Signals	663
14.2.2 Existence of Laplace Transform	665
14.2.3 Poles & Zeros of Rational Laplace Transforms	665
<b>14.3 THE INVERSE LAPLACE TRANSFORM</b>	<b>666</b>
14.3.1 Inverse Laplace Transform Using Partial Fraction Method	666
<b>14.4 PROPERTIES OF THE LAPLACE TRANSFORM</b>	<b>668</b>
14.4.1 Initial Value & Final Value Theorem	668
<b>14.5 CIRCUIT ELEMENTS IN THE <math>s</math>-DOMAIN</b>	<b>670</b>
14.5.1 Resistor in the $s$ -domain	670
14.5.2 Inductor in the $s$ -domain	670
14.5.3 Capacitor in the $s$ -domain	671
<b>14.6 CIRCUIT ANALYSIS IN THE <math>s</math>-DOMAIN</b>	<b>674</b>
<b>14.7 THE TRANSFER FUNCTION</b>	<b>680</b>
14.7.1 Transfer Function and Steady State Response	683
Practice A	685
Practice B	700

## CHAPTER 15

### **TWO PORT NETWORK 707**

#### **15.1 INTRODUCTION 708**

#### **15.2 IMPEDANCE PARAMETERS 708**

15.2.1 Some Equivalent Networks 713

15.2.2 Input Impedance of a Terminated  
Two port Network in Terms of  
Impedance Parameters 715

15.2.3 Thevenin Equivalent Across Output  
Port in Terms of Impedance  
Parameters 716

#### **15.3 ADMITTANCE PARAMETERS 719**

15.3.1 Some Equivalent Networks 722

15.3.2 Input Admittance of a Terminated  
Two-port Networks in Terms of  
Admittance Parameters 724

#### **15.4 HYBRID PARAMETERS 726**

15.4.1 Equivalent Network 729

15.4.2 Input Impedance of a Terminated  
Two-port Networks in Terms of  
Hybrid Parameters 729

15.4.3 Inverse Hybrid Parameters 730

#### **15.5 TRANSMISSION PARAMETERS 730**

15.5.1 Input Impedance of a Terminated  
Two-port Networks in Terms of  
 $ABCD$  parameters 732

#### **15.6 SYMMETRICAL AND RECIPROCAL NETWORK 733**

#### **15.7 RELATIONSHIP BETWEEN TWO-PORT PARAMETERS 735**

#### **15.8 INTERCONNECTION OF TWO-PORT NETWORKS 737**

15.8.1 Series Connection 737

15.8.2 Parallel Connection 739

15.8.3 Cascade Connection 740

Practice A 744

Practice B 755



# **CHAPTER 5**

## **CIRCUIT THEOREMS**

## 5.1 INTRODUCTION

In this chapter we study the methods of simplifying the analysis of more complicated circuits. We shall learn some of the circuit theorems which are used to reduce a complex circuit into a simple equivalent circuit. This includes Thevenin theorem and Norton theorem. These theorems are applicable to linear circuits, so we first discuss the concept of circuit linearity.

## 5.2 LINEARITY

A system is linear if it satisfies the following two properties

### Homogeneity Property :

The homogeneity property requires that if the input (excitation) is multiplied by a constant, then the output (response) is multiplied by the same constant. For a resistor, for example, Ohm's law relates the input  $I$  to the output  $V$ ,

$$V = IR$$

If the current is increased by a constant  $k$ , then the voltage increases correspondingly by  $k$ , that is,

$$kIR = kV$$

### Additivity Property :

The additivity property requires that the response to a sum of inputs is the sum of the responses to each input applied separately. Using the voltage-current relationship of a resistor, if

$$V_1 = I_1 R \quad (\text{Voltage due to current } I_1)$$

and 
$$V_2 = I_2 R \quad (\text{Voltage due to current } I_2)$$

then, by applying current  $(I_1 + I_2)$  gives

$$\begin{aligned} V &= (I_1 + I_2) R = I_1 R + I_2 R \\ &= V_1 + V_2 \end{aligned}$$

These two properties defining a linear system can be combined into a single statement as

For any linear resistive circuit, any output voltage or current, denoted by the variable  $y$ , is related linearly to the independent sources(inputs), i.e.,

$$y = a_1x_1 + a_2x_2 + \dots + a_nx_n$$

where  $x_1, x_2, \dots, x_n$  are the voltage and current values of the independent sources in the circuit and  $a_1$  through  $a_m$  are properly dimensioned constants.

Thus, a linear circuit is one whose output is linearly related (or directly proportional) to its input. For example, consider the linear circuit shown in figure 5.2.1. It is excited by an input voltage source  $V_s$ , and the current through load  $R$  is taken as output(response).

Suppose  $V_s = 5 \text{ V}$  gives  $I = 1 \text{ A}$ . According to the linearity principle,  $V_s = 10 \text{ V}$  will give  $I = 2 \text{ A}$ . Similarly,  $I = 4 \text{ mA}$  must be due to  $V_s = 20 \text{ mV}$ . Note that ratio  $V_s/I$  remains constant, since the system is linear.


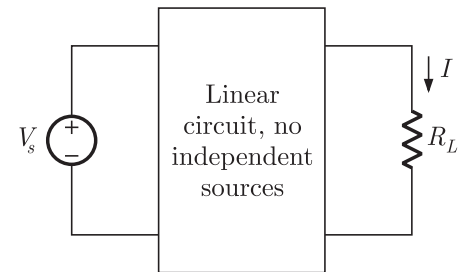


Fig 5.2.1 A linear circuit
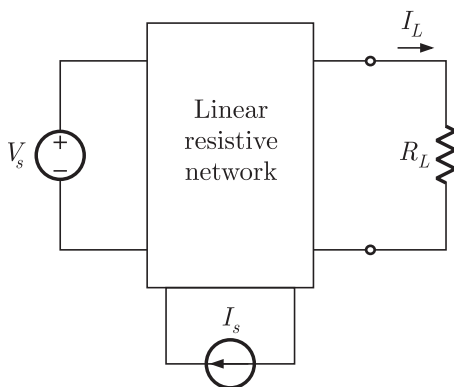
### ► EXAMPLE

For the circuit shown in figure, some measurements are made and listed in the table below.



	$V_s$	$I_s$	$I_L$
1.	7 V	3 A	1 A
2.	9 V	1 A	3 A

If  $V_s = 10 \text{ V}$  and  $I_s = 4 \text{ A}$ , then the value of  $I_L$  will be

- (A) 1.6 A
- (B) 4.4 A
- (C) 3.2 A
- (D) 6.4 A

**SOLUTION :**

Circuit is linear, so the linear equation relating inputs  $V_s$  and  $I_s$  to output  $I_L$  is given by

$$I_L = AV_s + BI_s$$

now, using the values of table

$$1 = 7A + 3B \quad \dots(i)$$

$$3 = 9A + B \quad \dots(ii)$$

Solving equation (i) and (ii)

$$A = 0.4, B = -0.6$$

So,  $I_L = 0.4V_s - 0.6I_s$

For  $V_s = 10 \text{ V}$  and  $I_s = 4 \text{ V}$

$$\begin{aligned} I_L &= 0.4(10) - 0.6(4) \\ &= 4 - 2.4 = 1.6 \text{ A} \end{aligned}$$

Hence (A) is correct option.

**▶ EXAMPLE**

The linear network in the figure contains resistors and dependent sources only. When  $V_s = 10 \text{ V}$ , the power supplied by the voltage source is  $40 \text{ W}$ . What will be the power supplied by the source if  $V_s = 5 \text{ V}$  ?

(A)  $20 \text{ W}$

(B)  $10 \text{ W}$

(C)  $40 \text{ W}$

(D) can not be determined

**SOLUTION :**

For,  $V_s = 10 \text{ V}, P = 40 \text{ W}$

So,  $I_s = \frac{P}{V_s} = \frac{40}{10} = 4 \text{ A}$



Now,  $V'_s = 5 \text{ V}$ , so  $I'_s = 2 \text{ A}$  (From linearity)

New value of the power supplied by source is

$$P'_s = V'_s I'_s = 5 \times 2 = 10 \text{ W}$$


**Note:** Linearity does not apply to power calculations.

Hence (B) is correct option.

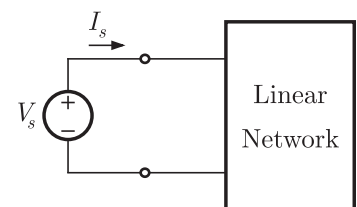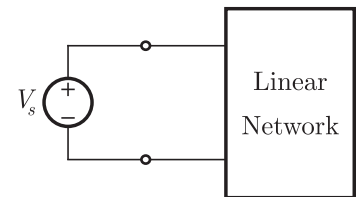
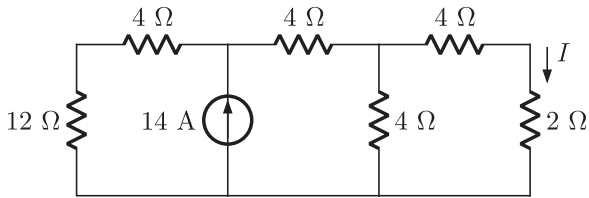
## ► EXAMPLE


In the circuit shown below, the value of current  $I$  will be given by



- (A) 2.5 A  
 (B) 1.5 A  
 (C) 4 A  
 (D) 2 A

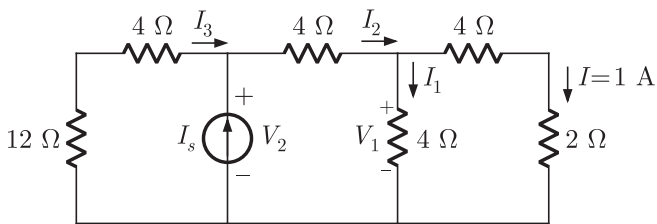**SOLUTION :**

We solve this problem using linearity and assumption that  $I = 1$  A.



$$V_1 = 4I + 2I = 6 \text{ V} \quad (\text{Using KVL})$$

$$I_2 = I_1 + I = \frac{V_1}{4} + I = \frac{6}{4} + 1 = 2.5 \text{ A} \quad (\text{Using KCL})$$

$$V_2 = 4I_2 + V_1 = 4(2.5) + 6 = 16 \text{ V} \quad (\text{Using KVL})$$

$$I_s + I_3 = I_2 \quad (\text{Using KCL})$$

$$I_s - \frac{V_2}{4 + 12} = I_2$$

$$I_s = \frac{16}{16} + 2.5 = 3.5 \text{ A}$$

When  $I_s = 3.5$  A,  $I = 1$  A

But  $I_s = 14$  A, so  $I = \frac{1}{3.5} \times 14 = 4$  A

Hence (C) is correct option.



illustrates the procedure of applying superposition to a given circuit


### **M E T H O D O L O G Y**

1. Consider one independent source (either voltage or current) at a time, short circuit all other voltage sources and open circuit all other current sources.
2. Dependent sources can not be set to zero as they are controlled by other circuit parameters.
3. Calculate the current or voltage due to the single source using any method (KCL, KVL, nodal or mesh analysis).
4. Repeat the above steps for each source.
5. Algebraically add the results obtained by each source to get the total response.

### **▶ EXAMPLE**

In the circuit of figure, the voltage drop across the resistance  $R_2$  will be equal to

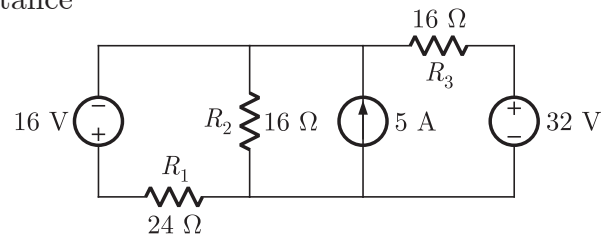- (A) 46 volt  
 (B) 38 volt  
 (C) 22 volt  
 (D) 14 volt




### **SOLUTION :**

The circuit has three independent sources, so we apply superposition theorem to obtain the voltage drop.


**Due to 16 V source only :** (Open circuit 5 A source and Short circuit 32 V source)

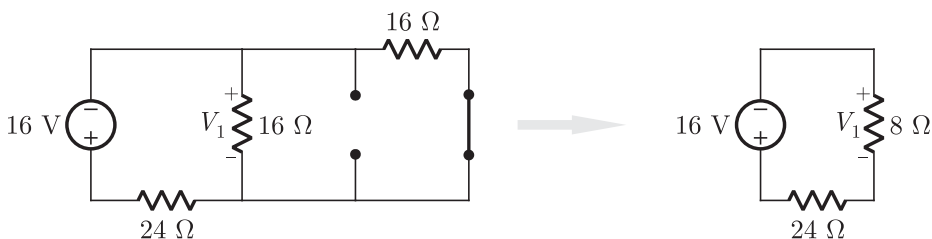Let voltage across  $R_2$  due to 16 V source only is  $V_1$ .








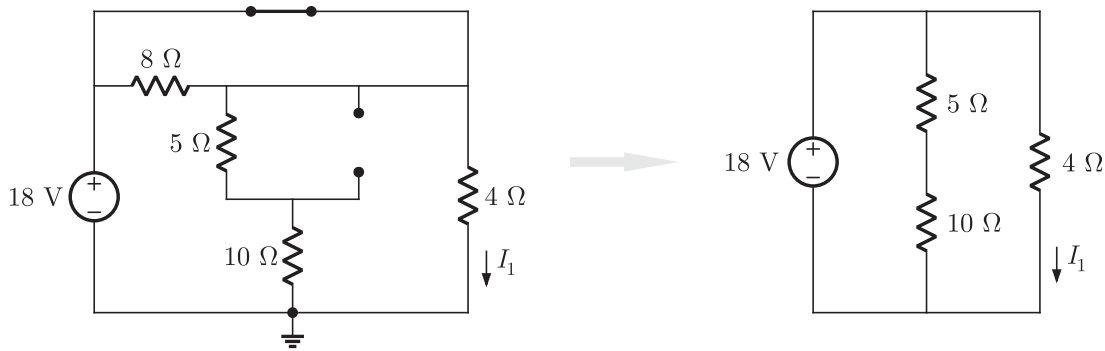


$$I_1 = 18/4 = 4.5 \text{ A}$$

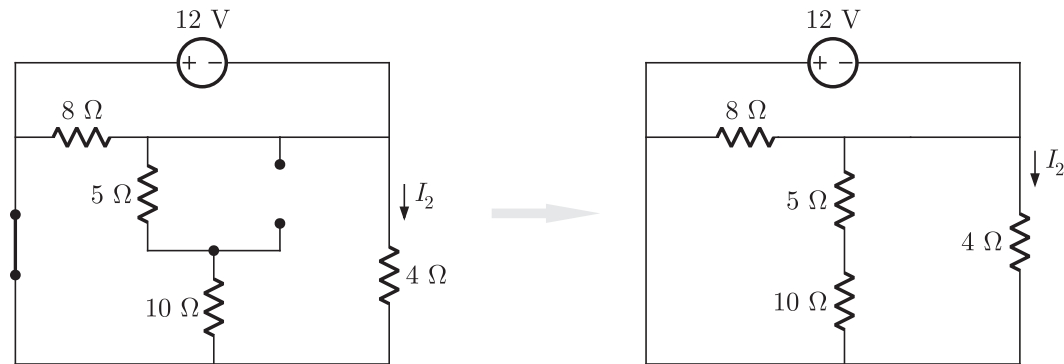**Due to 12 V Source Only :** (Open circuit 4 A and short circuit 18 V source)



$$I_2 = -12/4 = -3 \text{ A}$$

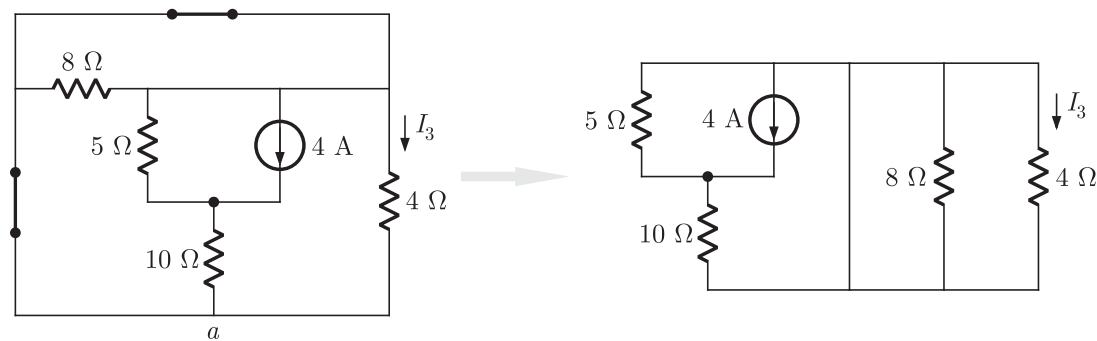**Due to 4 A Source Only :** (Short circuit 12 V and 18 V sources)



$$I_3 = 0 \quad \text{(Due to short circuit)}$$

So,  $I = I_1 + I_2 + I_3 = 4.5 - 3 + 0 = 1.5 \text{ A}$

Power dissipated in 4 Ω resistor

$$P_{4\Omega} = I^2(4) = (1.5)^2 \times 4 = 9 \text{ W}$$

Hence (C) is correct option.

## ► EXAMPLE

For the following circuit, value of current  $I$  is given by

- (A) 0.5 A  
 (B) 3.5 A  
 (C) 1 A  
 (D) 2 A

**SOLUTION :**

We obtain  $I$  using superposition. Note that while applying superposition we do not set dependent source to zero.

**Due to 24 V source only:** (Open circuit 6 A)

Applying KVL

$$24 - 6I_1 - 3I_1 - 3I_1 = 0$$

$$I_1 = \frac{24}{12} = 2 \text{ A}$$

**Due to 6 A source only:** (Short circuit 24 V source)

Applying KVL to supermesh

$$-6I_2 - 3(6 + I_2) - 3I_2 = 0$$

$$6I_2 + 18 + 3I_2 + 3I_2 = 0$$




$$I_2 = -\frac{18}{12} = -\frac{3}{2} \text{ A}$$

From superposition,

$$I = I_1 + I_2$$

$$= 2 - \frac{3}{2} = \frac{1}{2} \text{ A}$$

Hence (A) is correct option.

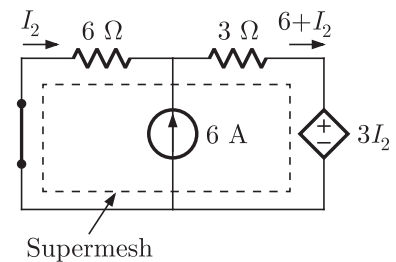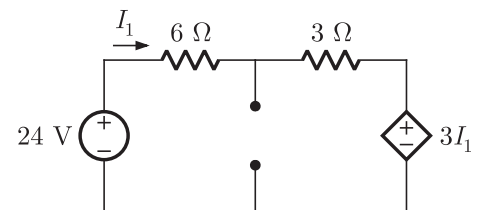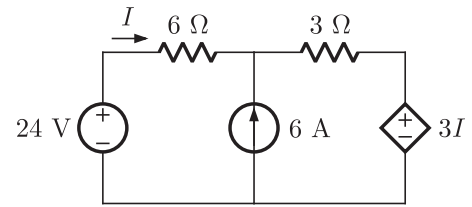**5.4 SOURCE TRANSFORMATION**

It states that an independent voltage source  $V_s$  in series with a resistance  $R$  is equivalent to an independent current source  $I_s = V_s/R$ , in parallel with a resistance  $R$ .

OR

An independent current source  $I_s$  in parallel with a resistance  $R$  is equivalent to an independent voltage source  $V_s = I_s R$ , in series with a resistance  $R$ .

Figure 5.4.1 shows the source transformation of an independent source. The following points are to be noted while applying source transformation.

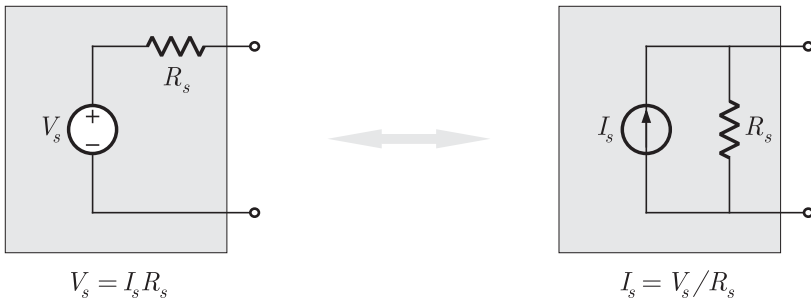


Fig 5.4.1 Source Transformation of independent sources

1. Note that head of the current source arrow corresponds to the +ve terminal of the voltage source. The following figure illustrates this


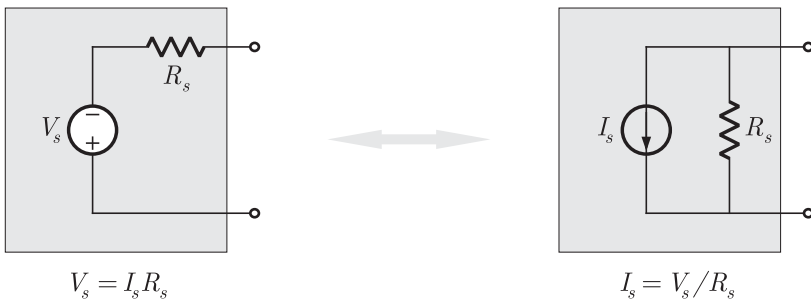


Fig 5.4.2

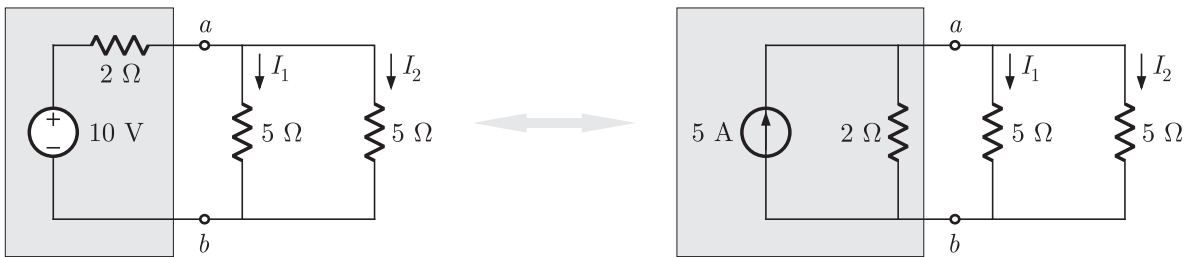2. Source conversion are equivalent at their external terminals only i.e. the voltage-current relationship at their external terminals remains same. The two circuits in figure 5.4.3a and 5.4.3b are equivalent, provided they have the same voltage-current relation at terminals *a-b*



(a) Circuit with a voltage source

(b) Equivalent circuit when the voltage source is transformed into current source

Fig 5.4.3 An example of source transformation


3. Source transformation is not applicable to ideal

voltage sources as  $R_s = 0$  for an ideal voltage source. So, equivalent current source value  $I_s = V_s/R \rightarrow \infty$ . Similarly it is not applicable to ideal current source because for an ideal current source  $R_s = \infty$ , so equivalent voltage source value will not be finite.

### ► EXAMPLE


The value of current  $I$  in the circuit, is equal to

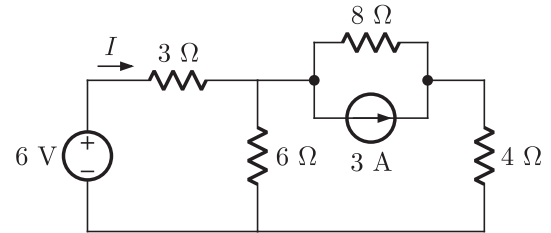- (A)  $2/7$  A
- (B) 1 A
- (C) 2 A
- (D) 4 A


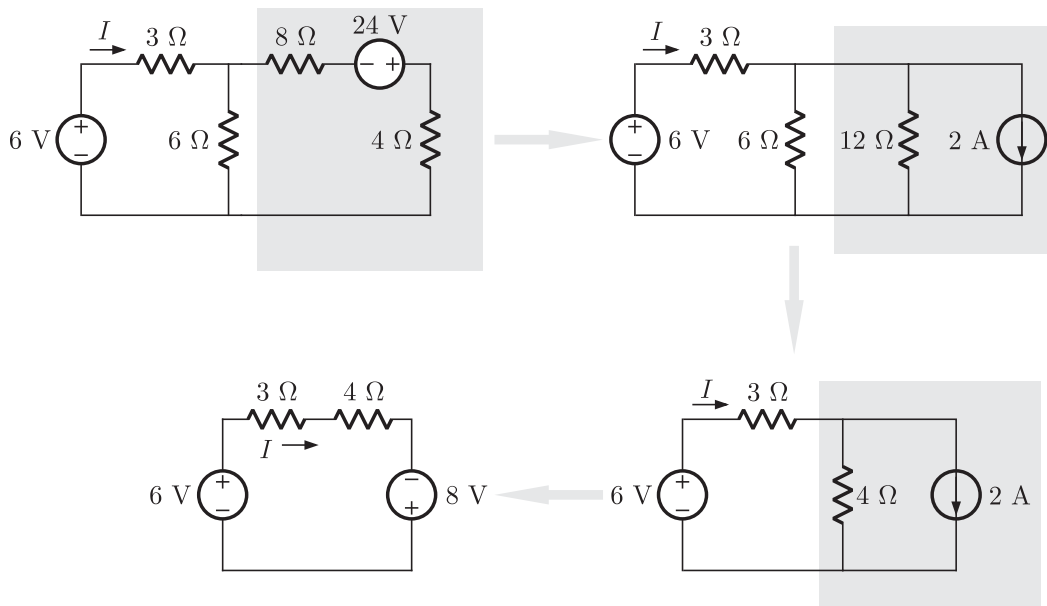
### SOLUTION :

Using source transformation, we can obtain  $I$  in following steps.



$$I = \frac{6 + 8}{3 + 4} = \frac{14}{7} = 2 \text{ A}$$


Hence (C) is correct option.
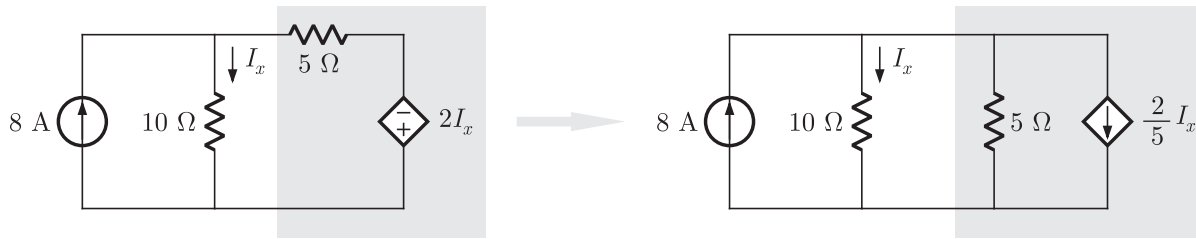
### ► EXAMPLE

What is the value of current  $I$  in the circuit shown below ?







Now using current division

$$I_x = \frac{5}{10 + 5} \left( 8 - \frac{2}{5} I_x \right)$$

$$I_x = \frac{1}{3} \left( 8 - \frac{2}{5} I_x \right)$$

$$3I_x + \frac{2}{5} I_x = 8$$

$$\frac{17}{5} I_x = 8 \Rightarrow I_x = 2.35 \text{ A}$$

## 5.5 THEVENIN'S THEOREM

It states that any network composed of ideal voltage and current sources, and of linear resistors, may be represented by an equivalent circuit consisting of an ideal voltage source,  $V_{Th}$ , in series with an equivalent resistance,  $R_{Th}$  as illustrated in the figure 5.5.1.

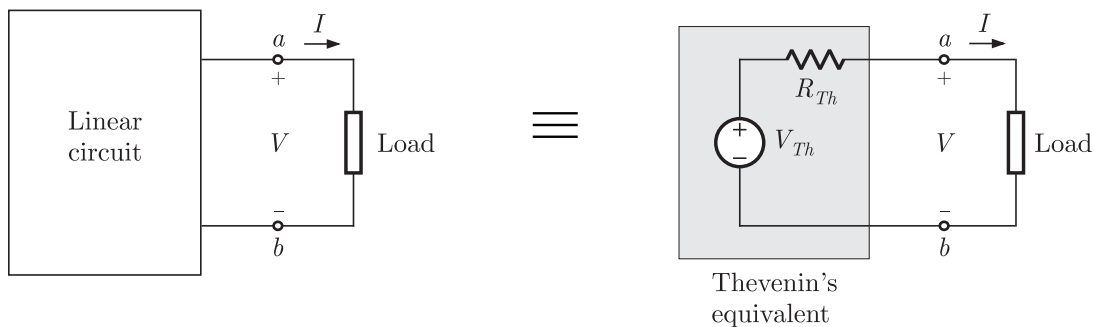


Fig 5.5.1 Illustration of Thevenin theorem

Where  $V_{Th}$  is called Thevenin's equivalent voltage or simply Thevenin voltage and  $R_{Th}$  is called Thevenin's equivalent resistance or simply Thevenin resistance.

The methods of obtaining Thevenin equivalent voltage and resistance are given in the following sections.

### 5.5.1 Thevenin's Voltage

The equivalent Thevenin voltage ( $V_{Th}$ ) is equal to the open-circuit voltage present at the load terminals (with the load removed). Therefore, it is also denoted by  $V_{oc}$ .

For the Thevenin voltage we may use the terms Thevenin voltage or open circuit voltage interchangeably.

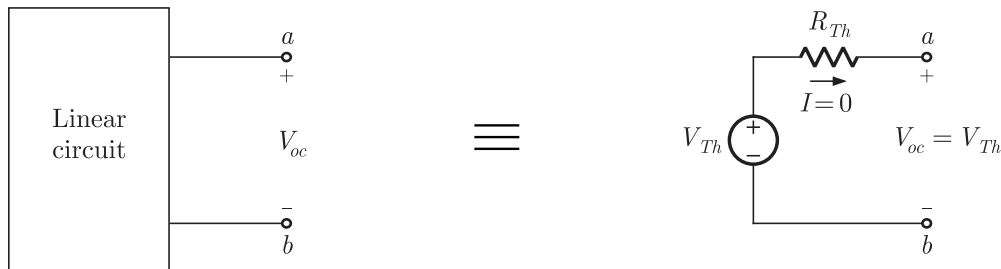


Fig 5.5.2 Equivalence of open circuit and Thevenin voltage

Figure 5.5.2 illustrates that the open-circuit voltage,  $V_{oc}$ , and the Thevenin voltage,  $V_{Th}$ , must be the same because in the circuit consisting of  $V_{Th}$  and  $R_{Th}$ , the voltage  $V_{oc}$  must equal  $V_{Th}$ , since no current flows through  $R_{Th}$  and therefore the voltage across  $R_{Th}$  is zero. Kirchhoff's voltage law confirms that

$$V_{Th} = R_{Th}(0) + V_{oc} = V_{oc}$$

The procedure of obtaining Thevenin voltage is given in the following methodology.

#### **M E T H O D O L O G Y 1**

1. Remove the load i.e open circuit the load terminals.
2. Define the open-circuit voltage  $V_{oc}$  across the open load terminals.
3. Apply any preferred method (KCL, KVL, nodal analysis, mesh analysis etc.) to solve for  $V_{oc}$ .
4. The Thevenin voltage is  $V_{Th} = V_{oc}$ .

Note that this methodology is applicable with the circuits containing both the dependent and independent source.

If a circuit contains dependent sources only, i.e. there is no independent source present in the network then its open circuit voltage or Thevenin voltage will simply be zero.



### 5.5.2 Thevenin's Resistance

Thevenin resistance is the input or equivalent resistance at the open circuit terminals  $a, b$  when all independent sources are set to zero (voltage sources replaced by short circuits and current sources replaced by open circuits).

We consider the following cases where Thevenin resistance  $R_{Th}$  is to be determined.

#### Case 1: Circuit With Independent Sources only

If the network has no dependent sources, we turn off all independent sources.  $R_{Th}$  is the input resistance or equivalent resistance of the network looking between terminals  $a$  and  $b$ , as shown in figure 5.5.3.


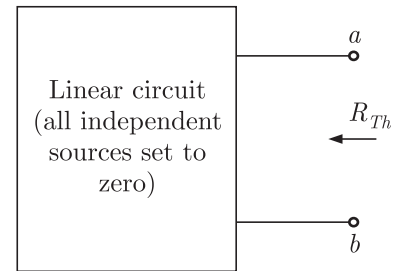


Fig 5.5.3 Circuit for obtaining  $R_{Th}$

#### ▶ EXAMPLE

In the circuit shown below, Thevenin equivalent voltage and resistance seen at load terminal, are equal to

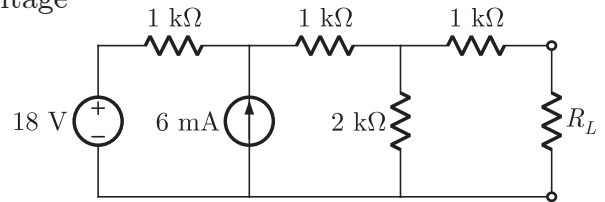- (A) 6 V, 5 kΩ
- (B) 24 V, 5/3 kΩ
- (C) 18 V, 1 kΩ
- (D) 12 V, 2 kΩ




#### SOLUTION :


First we will find Thevenin equivalent across load terminals.
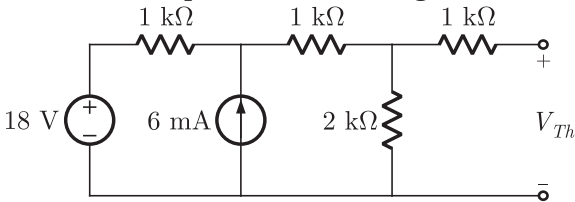
#### Thevenin voltage: (Open circuit voltage)

Remove the load  $R_L$  and open circuit its terminal as shown. Let open circuit voltage or Thevenin voltage is  $V_{Th}$ ,



Using source transformation

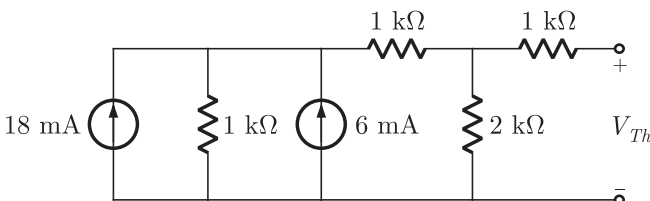



$$3I_1 - 2I_2 = 6 \quad \dots(i)$$

$$\text{Mesh 2: } -24I_2 - 20(I_2 - I_3) - 12(I_2 - I_1) = 0$$

$$-24I_2 - 20I_2 - 12I_2 + 12I_1 = 0 \quad (I_3 = 0)$$

$$14I_2 = 3I_1 \quad \dots(ii)$$

From equation (i) and (ii)

$$I_1 = 7/3 \text{ A, } I_2 = 1/2 \text{ A}$$

Mesh 3:

$$-6(I_3 - I_1) - 20(I_3 - I_2) - V_{Th} = 0$$


$$-6\left[0 - \frac{7}{3}\right] - 20\left[0 - \frac{1}{2}\right] - V_{Th} = 0$$

$$14 + 10 = V_{Th}$$

$$V_{Th} = 24 \text{ volt}$$
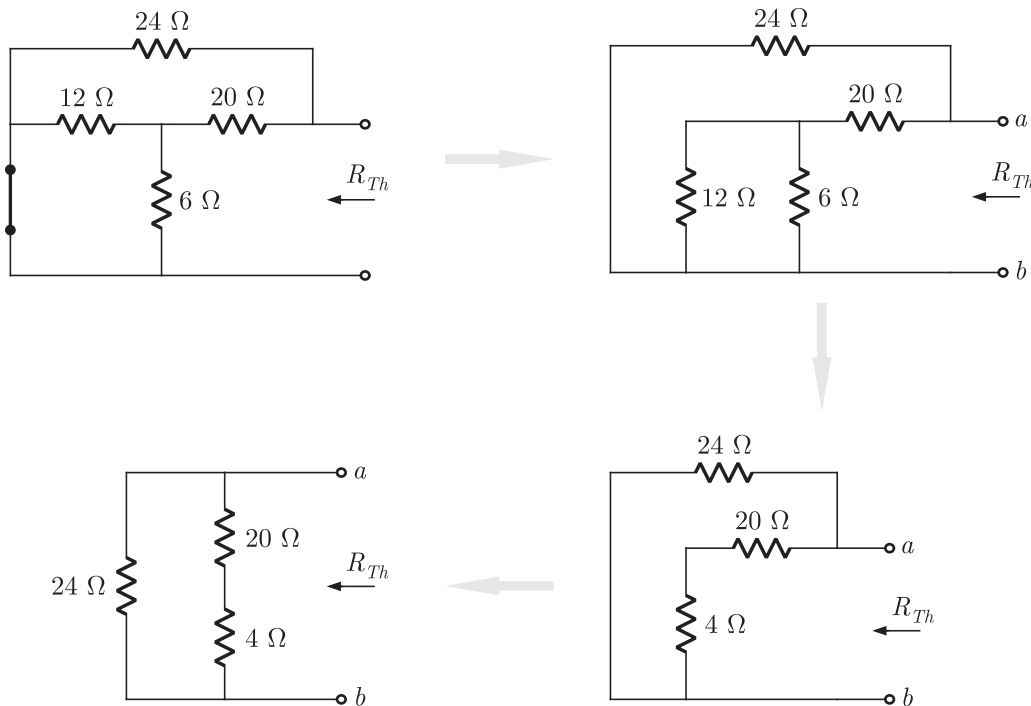
### Thevenin Resistance :

To obtain Thevenin resistance we set independent source to zero i.e. short circuit the 36 V source.



$$R_{Th} = (20 + 4) \parallel 24\Omega$$

$$R_{Th} = 24\Omega \parallel 24\Omega$$

$$R_{Th} = 12\Omega$$

Hence (B) is correct option.

### ► EXAMPLE

What values of  $R_{Th}$  and  $V_{Th}$  will cause the circuit of figure (B) to be the equivalent circuit of figure (A) ?

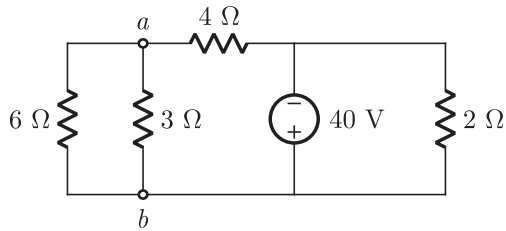


Fig.(A)

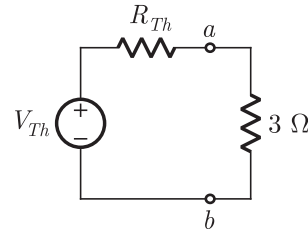


Fig.(B)

- (A)  $2.4 \Omega, -24 \text{ V}$                       (B)  $3 \Omega, 16 \text{ V}$   
 (C)  $10 \Omega, 24 \text{ V}$                         (D)  $10 \Omega, -24 \text{ V}$


### SOLUTION :

#### Thevenin voltage: (Open circuit voltage)

First we remove the load resistance (i.e open circuit the  $3 \Omega$  resistance) and obtain the open circuit voltage across it.


$$V_{Th} = \frac{6}{6+4}(-40) \quad (\text{using voltage division})$$

$$= -24 \text{ volt}$$

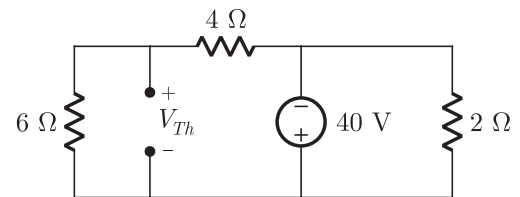
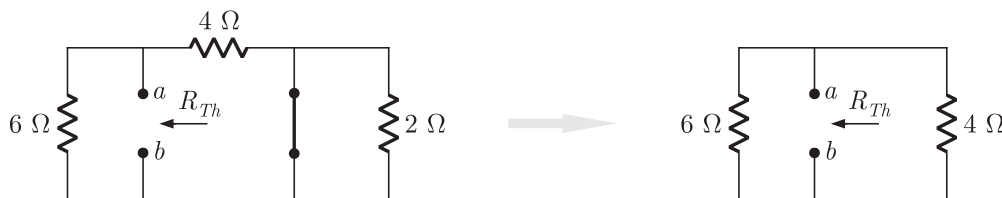
#### Thevenin resistance :

Set all independent source to zero (short circuit 40 V source)



$$R_{Th} = 6 \Omega \parallel 4 \Omega = \frac{6 \times 4}{6+4} = 2.4 \Omega$$

Hence (A) is correct option.

### Case 2: Circuit With Both Dependent and Independent Sources

Different methods can be used to determine Thevenin equivalent resistance of a circuit containing dependent

sources. We may follow the given two methodologies. Both the methods are also applicable to circuit with independent sources only (case 1).

### Using Test Source

#### M E T H O D O L O G Y 2

1. Set all independent sources to zero (Short circuit independent voltage source and open circuit independent current source).
2. Remove the load, and put a test source  $V_{test}$  across its terminals. Let the current through test source is  $I_{test}$ . Alternatively, we can put a test source  $I_{test}$  across load terminals and assume the voltage across it is  $V_{test}$ . Either method would give same result.
3. Thevenin resistance is given by  $R_{Th} = V_{test}/I_{test}$ .

We may use  $V_{test} = 1\text{ V}$  or  $I_{test} = 1\text{ A}$ .

### Using Short Circuit Current

$$R_{Th} = \frac{\text{open circuit voltage}}{\text{short circuit current}} = \frac{V_{oc}}{I_{sc}}$$


#### M E T H O D O L O G Y 3

1. Connect a short circuit between terminal  $a$  and  $b$ .
2. Be careful, do not set independent sources zero in this method because we have to find short circuit current.
3. Now, obtain the short circuit current  $I_{sc}$  through terminals  $a, b$ .
4. Thevenin resistance is given as  $R_{Th} = V_{oc}/I_{sc}$  where  $V_{oc}$  is open circuit voltage or Thevenin voltage across terminal  $a, b$  which can be obtained by same method given previously.

### ► EXAMPLE

The Thevenin equivalent resistance between terminal  $a$  and  $b$  in the following circuit is

- |                  |                  |
|------------------|------------------|
| (A) $22\ \Omega$ | (B) $11\ \Omega$ |
| (C) $17\ \Omega$ | (D) $1\ \Omega$  |

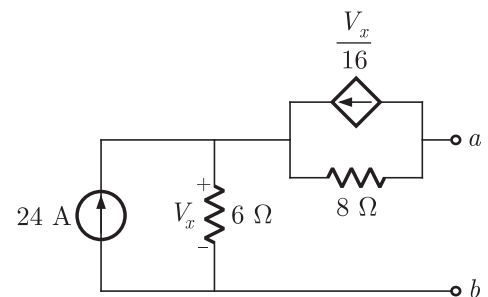

**SOLUTION :**

First we obtain  $R_{Th}$  using the methodology-3 which requires calculation of Thevenin voltage and short circuit current.

$$R_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{\text{Open circuit voltage}}{\text{short circuit current}}$$

**Thevenin voltage: (Open circuit voltage  $V_{oc}$ )**

Using source transformation of the dependent source as shown in figure

Applying KCL at top left node

$$24 = \frac{V_x}{6} \Rightarrow V_x = 144 \text{ V}$$

Using KVL,

$$V_x - 8I - \frac{V_x}{2} - V_{oc} = 0$$

$$144 - 0 - \frac{144}{2} = V_{oc}$$

$$V_{oc} = 72 \text{ V}$$

**Short circuit current ( $I_{sc}$ ):**

Applying KVL in the right mesh

$$V_x - 8I_{sc} - \frac{V_x}{2} = 0$$

$$\frac{V_x}{2} = 8I_{sc}$$

$$V_x = 16I_{sc}$$

KCL at the top left node

$$24 = \frac{V_x}{6} + \frac{V_x - V_x/2}{8}$$

$$24 = \frac{V_x}{6} + \frac{V_x}{16}$$

$$V_x = \frac{1152}{11} \text{ V}$$

$$I_{sc} = \frac{V_x}{16} = \frac{1152}{11 \times 16} = \frac{72}{11} \text{ A}$$



Thevenin resistance,

$$R_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{72}{\left(\frac{72}{11}\right)} = 11 \Omega$$

Hence (B) is correct option.

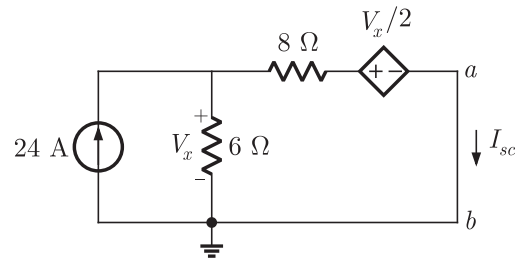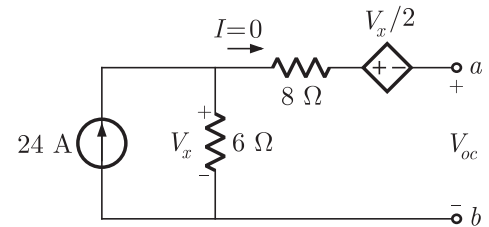
**Alternate method : (Methodology-2)**

We can obtain Thevenin equivalent resistance without calculating the Thevenin voltage (open circuit voltage) as



Here  $V_x$  is different for both the cases because in first case terminals  $a, b$  are open circuit, while in the second case they are short circuited.

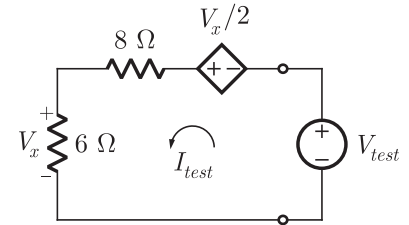given in methodology-2. Set all independent sources to zero (i.e. open circuit current sources and short circuit voltage sources) and put a test source  $V_{test}$  between terminal  $a-b$  as shown



$$R_{Th} = \frac{V_{test}}{I_{test}}$$

$$6I_{test} + 8I_{test} - \frac{V_x}{2} - V_{test} = 0 \quad \text{(KVL)}$$

Thus  $14I - \frac{6I_{test}}{2} - V_{test} = 0 \quad V_x = 6I_{test}$


$$11I_{test} = V_{test}$$

So,  $R_{Th} = \frac{V_{test}}{I_{test}} = 11 \Omega$

**▶ EXAMPLE**

For the circuit shown in the figure, the Thevenin's voltage and resistance looking into  $a-b$  are

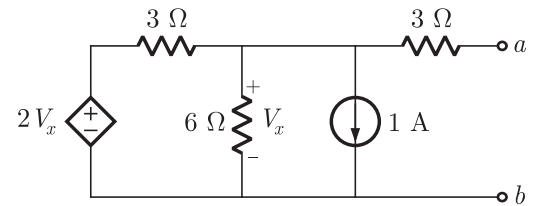- (A) 2 V, 3 Ω
- (B) 2 V, 2 Ω
- (C) 6 V, -9 Ω
- (D) 6 V, -3 Ω



**SOLUTION :**


**Thevenin voltage (Open circuit voltage) :**

Applying KCL at top middle node

$$\frac{V_{Th} - 2V_x}{3} + \frac{V_{Th}}{6} + 1 = 0$$

$$\frac{V_{Th} - 2V_{Th}}{3} + \frac{V_{Th}}{6} + 1 = 0 \quad (V_{Th} = V_x)$$
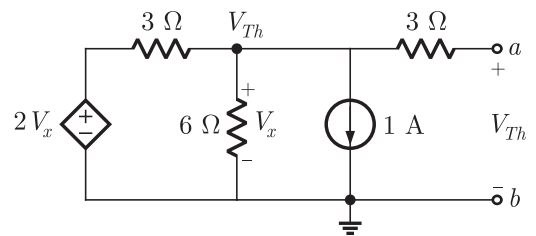
$$-2V_{Th} + V_{Th} + 6 = 0 \Rightarrow V_{Th} = 6 \text{ volt}$$



**Thevenin Resistance :**

To obtain Thevenin resistance we follow the procedure given in methodology-3.

$$R_{Th} = \frac{\text{Open circuit voltage}}{\text{Short circuit current}} = \frac{V_{Th}}{I_{sc}}$$


To obtain Thevenin resistance, first we find short circuit current through  $a-b$

Writing KCL at top middle node

$$\frac{V_x - 2V_x}{3} + \frac{V_x}{6} + 1 + \frac{V_x - 0}{3} = 0$$

$$-2V_x + V_x + 6 + 2V_x = 0$$

$$V_x = -6 \text{ volt}$$

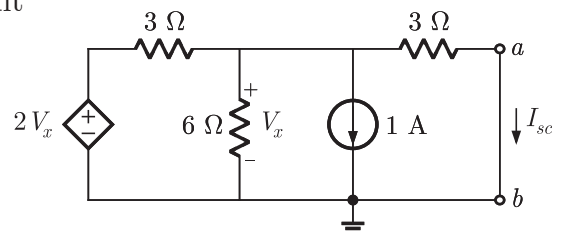





**SOLUTION :**

We obtain Thevenin's equivalent across load terminal.

**Thevenin voltage : (Open circuit voltage)**

Follow the methodology-1 to calculate the Thevenin voltage across load resistance. Using KCL at top left node

$$5 = I_x + 0$$

$$I_x = 5 \text{ A}$$

$$2I_x - 4I_x - V_{Th} = 0 \quad (\text{Using KVL})$$

$$2(5) - 4(5) = V_{Th}$$

$$V_{Th} = -10 \text{ volt}$$

**Thevenin Resistance :**

Follow the methodology-3 to obtain the Thevenin resistance.

First we find short circuit current through  $a-b$

Using KCL at top left node

$$5 = I_x + I_{sc}$$

$$I_x = 5 - I_{sc}$$

Applying KVL in the right mesh

$$2I_x - 4I_x + 0 = 0$$

$$I_x = 0$$

So,  $5 - I_{sc} = 0$  or  $I_{sc} = 5 \text{ A}$

Thevenin resistance,

$$R_{Th} = \frac{V_{Th}}{I_{sc}} = -\frac{10}{5} = -2 \Omega$$




Now, the circuit becomes as shown in figure

$$V = V_{Th} \left( \frac{R_L}{R_{Th} + R_L} \right) \quad (\text{Using voltage division})$$

$$= (-10) \left( \frac{4}{-2+4} \right) \quad R_L = 4 \Omega$$

$$= -20 \text{ V}$$

Hence (C) is correct option.

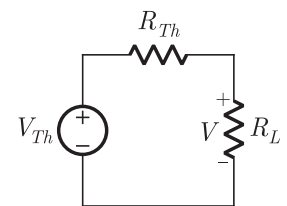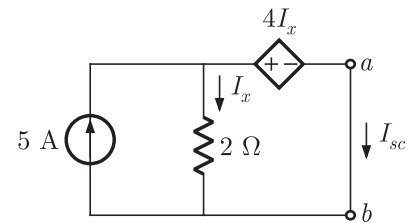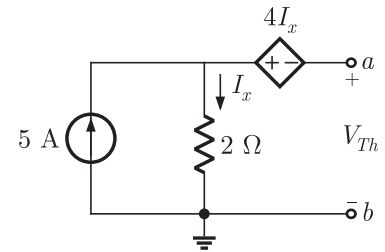**5.6 NORTON'S THEOREM**

Any network composed of ideal voltage and current sources, and of linear resistors, may be represented by an equivalent circuit consisting of an ideal current source,  $I_N$ , in parallel with an equivalent resistance,  $R_N$  as illustrated in figure 5.6.1.

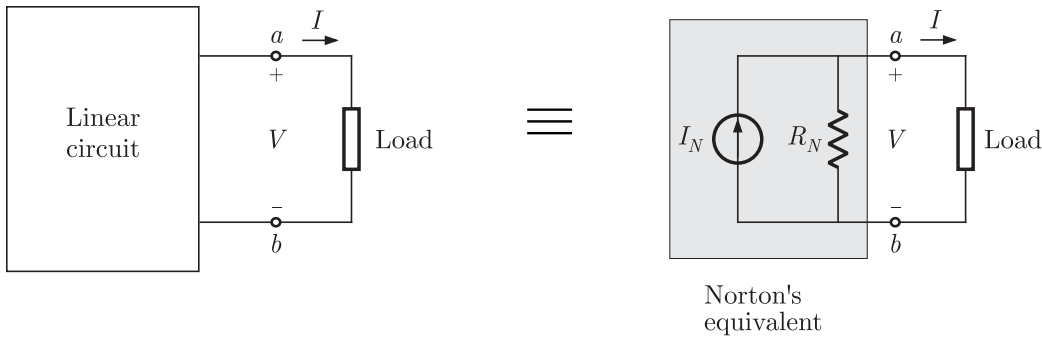


Fig 5.6.1 Illustration of Norton theorem

Where  $I_N$  is called Norton's equivalent current or simply Norton current and  $R_N$  is called Norton's equivalent resistance. The methods of obtaining Norton equivalent current and resistance are given in the following sections.

### 5.6.1 Norton's Current

The Norton equivalent current is equal to the short-circuit current that would flow when the load replaced by a short circuit. Therefore, it is also called short circuit current  $I_{sc}$ .

For the Norton current we may use the term Norton current or short circuit current interchangeably.

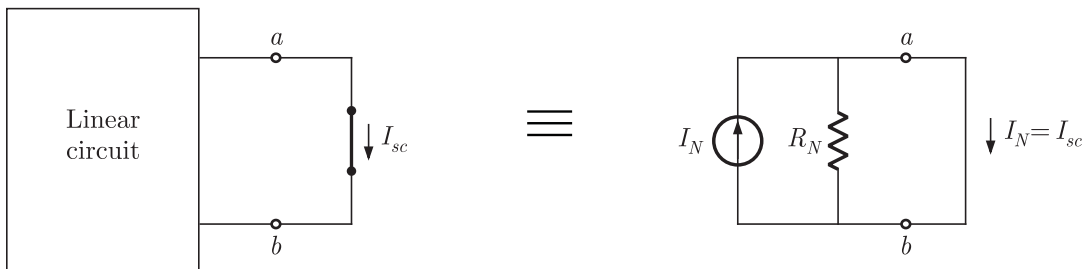


Fig 5.6.2 Equivalence of short circuit current and Norton current

Figure 5.6.2 illustrates that if we replace the load by a short circuit, then current flowing through this short circuit will be same as Norton current  $I_N$

$$I_N = I_{sc}$$

The procedure of obtaining Norton current is given in the following methodology

**M E T H O D O L O G Y**

1. Replace the load with a short circuit.
2. Define the short circuit current,  $I_{sc}$ , through load terminal.
3. Obtain  $I_{sc}$  using any method (KCL, KVL, nodal analysis, loop analysis).
4. The Norton current is  $I_N = I_{sc}$ .

If a circuit contains dependent sources only, i.e. there is no independent source present in the network then the short circuit current or Norton current will simply be zero.

**5.6.2 Norton's Resistance**

Norton resistance is the input or equivalent resistance seen at the load terminals when all independent sources are set to zero (voltage sources replaced by short circuits and current sources replaced by open circuits) i.e. Norton resistance is same as Thevenin's resistance

$$R_N = R_{Th}$$

So, we can obtain Norton resistance using same methodologies as for Thevenin resistance. Dependent and independent sources are treated the same way as in Thevenin's theorem.

**► EXAMPLE**

What are the values of equivalent Norton current source ( $I_N$ ) and equivalent resistance ( $R_N$ ) across the load terminal of the circuit shown in figure ?

	$I_N$	$R_N$
(A)	10 A	$2 \Omega$
(B)	10 A	$9 \Omega$
(C)	3.33 A	$9 \Omega$
(D)	6.66 A	$2 \Omega$



**SOLUTION :**

**Norton Current(short circuit current):**

Short circuit current across terminal  $a-b$  is obtained by

Note that this methodology is applicable with the circuits containing both the dependent and independent source.

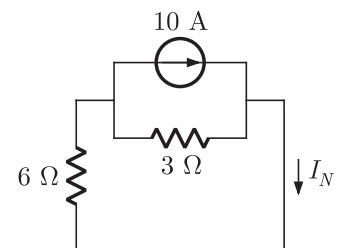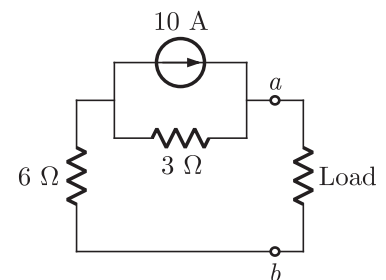We may denote Norton resistance either by  $R_N$  or  $R_{Th}$ .





the network, therefore we put a test source across load terminal and set all independent sources to zero. (Open circuit 6 A source)

$$R_N = R_{Th} = \frac{V_{test}}{I_{test}}$$

By applying KVL


$$V_{test} - 6I_{test} + 4I_x - 10I_x = 0$$

$$V_{test} - 6I_{test} - 6I_x = 0$$

$$V_{test} - 6I_{test} - 6I_{test} = 0 \quad (I_x = I_{test})$$

$$R_{Th} = \frac{V_{test}}{I_{test}} = 12 \Omega$$

Hence (B) is correct option.

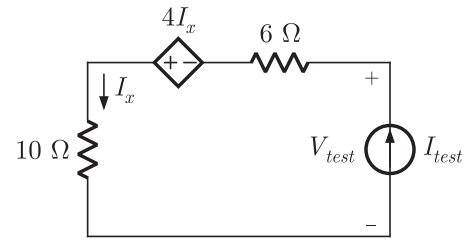

### ► EXAMPLE

In the following circuit value of Norton current ( $I_N$ ) and resistance ( $R_N$ ) with respect to terminals  $a, b$  are

(A)  $I_N = 5 \text{ A}$ ,  $R_N = 50 \Omega$

(B)  $I_N = 3 \text{ A}$ ,  $R_N = 50 \Omega$

(C)  $I_N = 9 \text{ A}$ ,  $R_N = 100 \Omega$

(D)  $I_N = 6 \text{ A}$ ,  $R_N = 150 \Omega$

### SOLUTION :

Norton current (Short circuit current)

By applying KVL

$$-(5 - I_x)40 - 0 + 20I_x + 40I_x = 0$$

$$-200 + 40I_x + 20I_x + 40I_x = 0$$

$$100I_x = 200$$

$$I_x = 2 \text{ A}$$

$$I_{sc} = 5 - I_x = 5 - 2 = 3 \text{ A}$$

### Norton resistance

To obtain Norton resistance we set independent source to zero (open circuit 5 A source) and put a test source across  $a, b$ .




$$R_{Th} = R_N = \frac{V_{test}}{I_{test}}$$

Applying KVL

$$V_{test} - 40I_x - 40I_x - 20I_x = 0$$

$$V_{test} = 100I_x \quad \dots(i)$$

Writing node equation at top right node

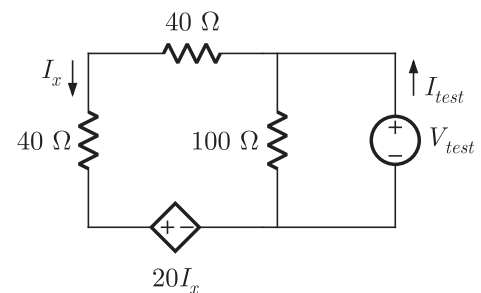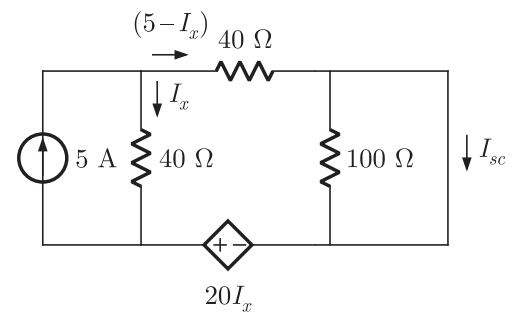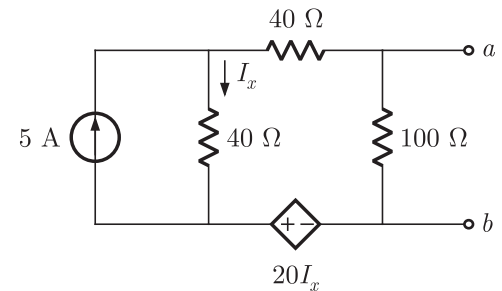

$$I_{test} = \frac{V_{test}}{100} + I_x$$

Substituting  $I_x = V_{test}/100$  from equation (i)

$$I_{test} = \frac{V_{test}}{100} + \frac{V_{test}}{100}$$

$$I_{test} = \frac{V_{test}}{50}$$

$$R_{Th} = R_N = \frac{V_{test}}{I_{test}} = 50 \Omega$$

Hence (B) is correct option.

### Circuit Analysis Using Norton's Equivalent :

As discussed for Thevenin's theorem, Norton equivalent is also useful in circuit analysis. It simplifies a circuit. Consider a linear circuit terminated by a load  $R_L$ , as shown in figure 5.6.4. The current  $I_L$  through the load and the voltage  $V_L$  across the load are easily determined once the Norton equivalent of the circuit at the load's terminals is obtained,

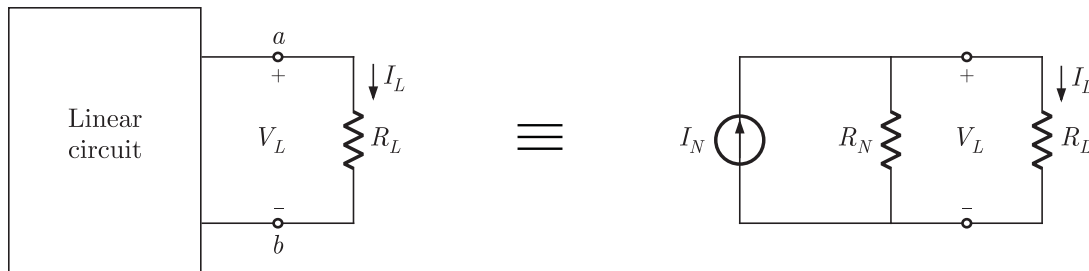


Fig 5.6.4 A circuit with a load and its equivalent Norton circuit

Current through load  $R_L$  is,

$$I_L = \frac{R_N}{R_L + R_N} I_N$$

Voltage across load  $R_L$  is,


$$V_L = R_L I_L = \frac{R_L R_N}{R_N + R_L} I_N$$
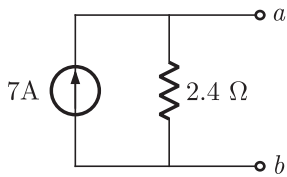
## 5.7 TRANSFORMATION BETWEEN THEVENIN & NORTON'S EQUIVALENT CIRCUITS

From source transformation it is easy to find Norton's and Thevenin's equivalent circuit from one form to another as following



Norton equivalent using source transformation, is



Hence (B) is correct option.

## 5.8 MAXIMUM POWER TRANSFER THEOREM

Maximum power transfer theorem states that a load resistance  $R_L$  will receive maximum power from a circuit when the load resistance is equal to Thevenin's/Norton's resistance seen at load terminals.

i.e.  $R_L = R_{Th}$ , (For maximum power transfer)

In other words a network delivers maximum power to a load resistance  $R_L$  when  $R_L$  is equal to Thevenin equivalent resistance of the network.

### Proof :

Consider the Thevenin equivalent circuit of figure 5.8.1 with Thevenin voltage  $V_{Th}$  and Thevenin resistance  $R_{Th}$ . We assume that we can adjust the load resistance  $R_L$ . The power absorbed by the load,  $P_L$ , is given by the expression

$$P_L = I_L^2 R_L \quad (5.8.1)$$

and that the load current is given as,

$$I_L = \frac{V_{Th}}{R_L + R_{Th}} \quad (5.8.2)$$

Substituting  $I_L$  from equation (5.8.2) into equation (5.8.1)

$$P_L = \frac{V_{Th}^2}{(R_L + R_{Th})^2} R_L \quad (5.8.3)$$

To find the value of  $R_L$  that maximizes the expression for  $P_L$  (assuming that  $V_{Th}$  and  $R_{Th}$  are fixed), we write

$$\frac{dP_L}{dR_L} = 0$$

Computing the derivative, we obtain the following expression :

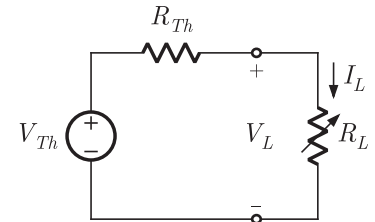


Fig 5.8.1 A circuit used for maximum power transfer



$$\frac{dP_L}{dR_L} = \frac{V_{Th}^2(R_L + R_{Th})^2 - 2V_{Th}^2R_L(R_L + R_{Th})}{(R_L + R_{Th})^4}$$

which leads to the expression

$$(R_L + R_{Th})^2 - 2R_L(R_L + R_{Th}) = 0$$

or  $R_L = R_{Th}$

Thus, in order to transfer maximum power to a load, the equivalent source and load resistances must be matched, that is, equal to each other.

$$R_L = R_{Th}$$

The maximum power transferred is obtained by substituting  $R_L = R_{Th}$  into equation (5.8.3)

$$P_{\max} = \frac{V_{Th}^2 R_{Th}}{(R_{Th} + R_{Th})^2} = \frac{V_{Th}^2}{4R_{Th}} \quad (4.24)$$

or,  $P_{\max} = \frac{V_{Th}^2}{4R_L}$

#### If the Load resistance $R_L$ is fixed :

Now consider a problem where the load resistance  $R_L$  is fixed and Thevenin resistance or source resistance  $R_s$  is being varied, then

$$P_L = \frac{V_{Th}^2}{(R_L + R_s)^2} R_L$$

To obtain maximum  $P_L$  denominator should be minimum or  $R_s = 0$ . This can be solved by differentiating the expression for the load power,  $P_L$ , with respect to  $R_s$  instead of  $R_L$ .

The step-by-step methodology to solve problems based on maximum power transfer is given as following :


#### **M E T H O D O L O G Y**

1. Remove the load  $R_L$  and find the Thevenin equivalent voltage  $V_{Th}$  and resistance  $R_{Th}$  for the remainder of the circuit.
2. Select  $R_L = R_{Th}$ , for maximum power transfer.
3. The maximum average power transfer can be calculated using  $P_{\max} = V_{Th}^2/4R_{Th}$ .

### ► EXAMPLE

In the circuit shown below the maximum power transferred to  $R_L$  is  $P_{\max}$ , then

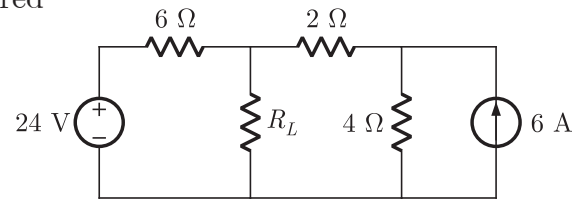
- (A)  $R_L = 12 \Omega$ ,  $P_{\max} = 12 \text{ W}$   
 (B)  $R_L = 3 \Omega$ ,  $P_{\max} = 96 \text{ W}$   
 (C)  $R_L = 3 \Omega$ ,  $P_{\max} = 48 \text{ W}$   
 (D)  $R_L = 12 \Omega$ ,  $P_{\max} = 24 \text{ W}$




### SOLUTION :

Step 1: First, obtain Thevenin equivalent across  $R_L$ .

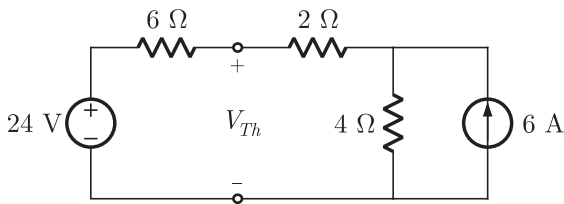**Thevenin voltage : (Open circuit voltage)**



Using source transformation

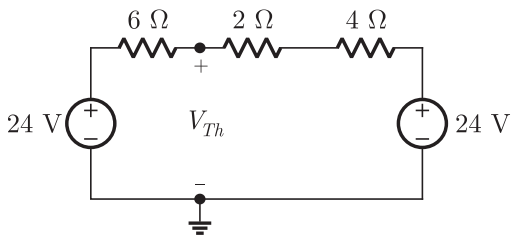


Using nodal analysis

$$\frac{V_{Th} - 24}{6} + \frac{V_{Th} - 24}{2 + 4} = 0$$


$$2V_{Th} - 48 = 0 \Rightarrow V_{Th} = 24 \text{ V}$$

**Thevenin resistance :**

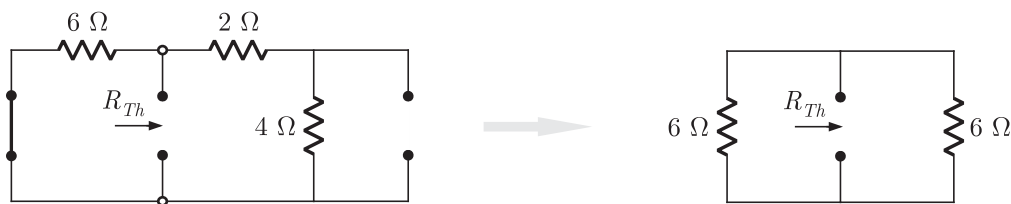

$$R_{Th} = 6 \Omega \parallel 6 \Omega = 3 \Omega$$

Circuit becomes as

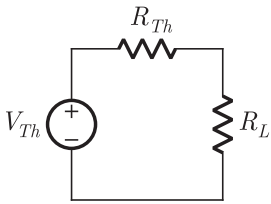

Step 2: For maximum power transfer

$$R_L = R_{Th} = 3 \Omega$$

Step 3: Value of maximum power

$$P_{\max} = \frac{(V_{Th})^2}{4R_L} = \frac{(24)^2}{4 \times 3} = 48 \text{ W}$$

Hence (C) is correct option.

### ► EXAMPLE

In the circuit shown, what value of  $R_L$  maximizes the power delivered to  $R_L$  ?

- (A) 286  $\Omega$  (B) 350  $\Omega$   
 (C) zero (D) 500  $\Omega$

### SOLUTION :

For maximum power transfer  $R_L = R_{Th}$ . To obtain Thevenin resistance set all independent sources to zero and put a test source across load terminals.

$$R_{Th} = \frac{V_{test}}{I_{test}}$$

Writing KCL at the top center node

$$\frac{V_{test}}{2k} + \frac{V_{test} - 2V_x}{1k} = I_{test} \quad \dots(i)$$

Also,  $V_{test} + V_x = 0$  (KVL in left mesh)

So,  $V_x = -V_{test}$



Substituting  $V_x = -V_{test}$  into equation (i)

$$\frac{V_{test}}{2k} + \frac{V_{test} - 2(-V_{test})}{1k} = I_{test}$$

$$V_{test} + 6V_{test} = 2I_{test}$$

$$R_{Th} = \frac{V_{test}}{I_{test}} = \frac{2}{7} \text{ k}\Omega \approx 286 \Omega$$

Hence (A) is correct option.

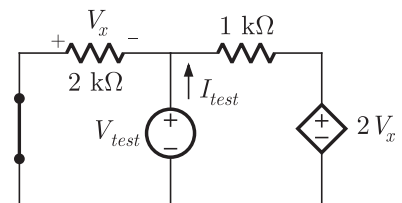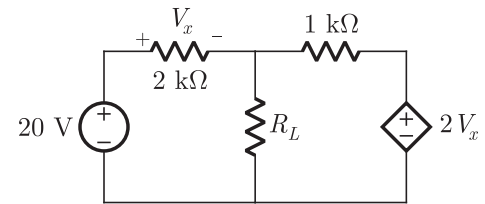

## 5.9 RECIPROcity THEOREM


The reciprocity theorem is a theorem which can only be used with single source circuits (either voltage or current source). The theorem states the following

### Circuit With a Voltage Source

In any linear bilateral network, if a single voltage source  $V_a$  in branch  $a$  produces a current  $I_b$  in another branch  $b$ , then if the voltage source  $V_a$  is removed (i.e. short circuited) and inserted in branch  $b$ , it will produce a current  $I_b$  in branch  $a$ .

In other words, it states that the ratio of response (output) to excitation (input) remains constant if the positions of output and input are interchanged in a reciprocal network. Consider the network shown in figure 5.9.1a and b. Using reciprocity theorem we may write

$$\frac{V_1}{I_1} = \frac{V_2}{I_2} \quad (5.9.1)$$

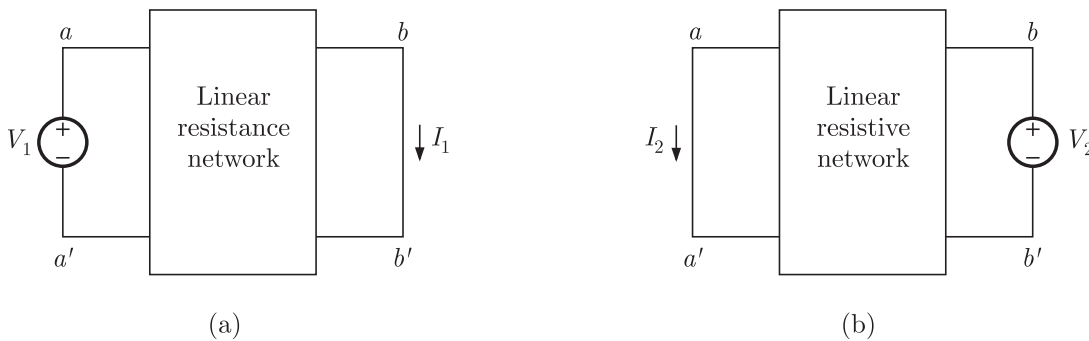

**Fig 5.9.1** Illustration of reciprocity theorem for a voltage source

When applying the reciprocity theorem for a voltage source, the following steps must be followed:

1. The voltage source is replaced by a short circuit in the original location.
2. The polarity of the voltage source in the new location have the same correspondence with branch current, in each position, otherwise a  $-ve$  sign appears in the expression (5.9.1).

This can be explained in a better way through following example.

## ► EXAMPLE

In the circuit of figure (A), if  $I_1 = 20$  mA, then what is the value of current  $I_2$  in the circuit of figure (B) ?

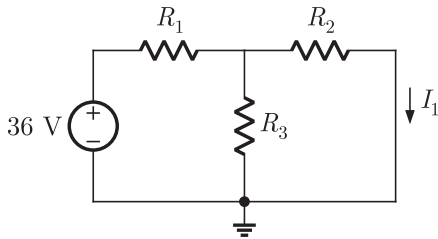


Fig.(A)

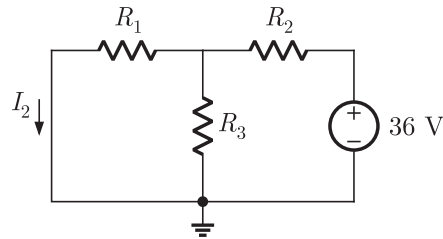


Fig.(B)

- (A) 40 mA  
 (B)  $-20$  mA  
 (C) 20 mA  
 (D)  $R_1$ ,  $R_2$  and  $R_3$  must be known

**SOLUTION :**

In figure (A),  $V_1 = 36$  V,  $I_1 = 20$  mA

In figure (B),  $V_2 = 36$  V,  $I_2 = ?$

Using reciprocity

$$\frac{V_1}{I_1} = \frac{V_2}{I_2}$$

So,  $I_2 = I_1 = 20$  mA

Hence (C) is correct option.

## ► EXAMPLE

In the circuit shown in fig (a) if current  $I_1 = 2.5$  A then current  $I_2$  and  $I_3$  in fig (B) and (C) respectively are

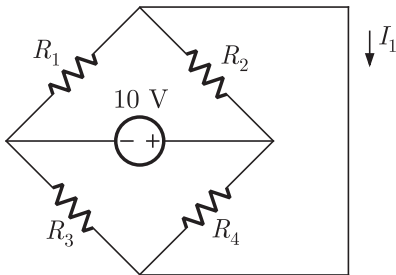


Fig.(A)

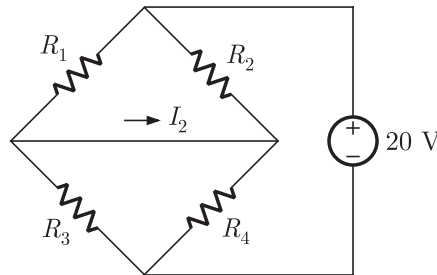


Fig.(B)

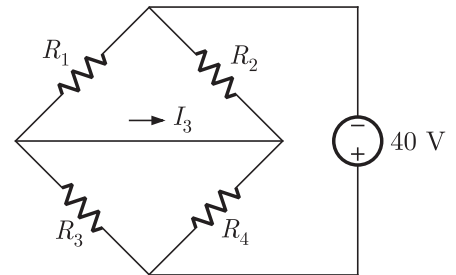


Fig.(C)

(A) 5 A, 10 A

(B) -5 A, 10 A

(C) 5 A, -10 A

(D) -5 A, -10 A

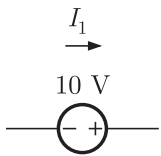
**SOLUTION :**

Fig.(A)

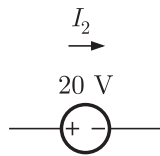


Fig.(B)

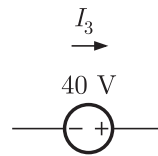


Fig.(C)

It can be solved by reciprocity theorem. Polarity of voltage source should have same correspondence with branch current in each of the circuit. Polarity of voltage source and current direction are shown below

$$\text{So, } \frac{V_1}{I_1} = -\frac{V_2}{I_2} = \frac{V_3}{I_3}$$

$$\frac{10}{2.5} = -\frac{20}{I_2} = \frac{40}{I_3}$$


$$I_2 = -5 \text{ A}$$

$$I_3 = 10 \text{ A}$$

Hence (B) is correct option.

**Circuit With a Current Source**

In any linear bilateral network, if a single current source  $I_a$  in branch  $a$  produces a voltage  $V_b$  in another branch  $b$ , then if the current source  $I_a$  is removed (i.e. open circuited) and inserted in branch  $b$ , it will produce a voltage  $V_b$  in open-circuited branch  $a$ .

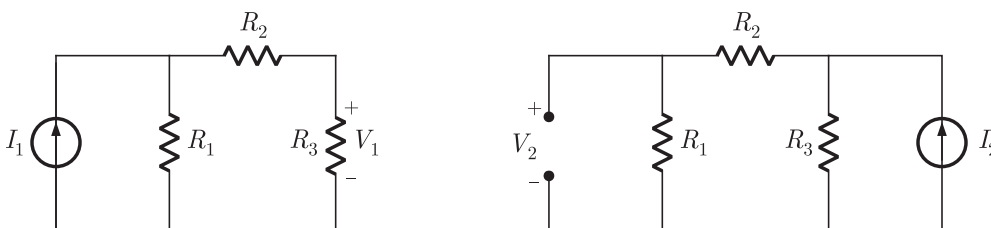

**Fig 5.9.2** Illustration of reciprocity theorem for a current source

Again, the ratio of voltage and current remains

constant. Consider the network shown in figure 5.9.2a and 5.9.2b. Using reciprocity theorem we may write

$$\frac{V_1}{I_1} = \frac{V_2}{I_2} \quad (5.9.2)$$

When applying the reciprocity theorem for a current source, the following conditions must be met:

1. The current source is replaced by an open circuit in the original location.
2. The direction of the current source in the new location have the same correspondence with voltage polarity, in each position, otherwise a -ve sign appears in the expression (5.9.2).

Again the following example illustrated the above concepts using a better approach

### ► EXAMPLE

If  $V_1 = 2\text{ V}$  in the circuit of figure (A), then what is the value of  $V_2$  in the circuit of figure (B) ?

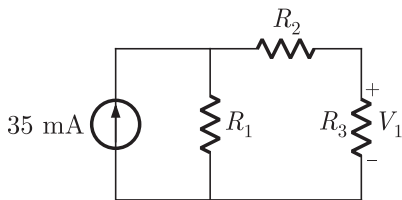


Fig.(A)


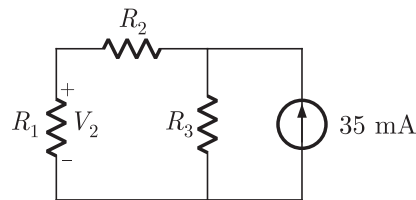


Fig.(B)

- (A) 2 V  
 (B) -2 V  
 (C) 4 V  
 (D)  $R_1$ ,  $R_2$  and  $R_3$  must be known

**SOLUTION :**

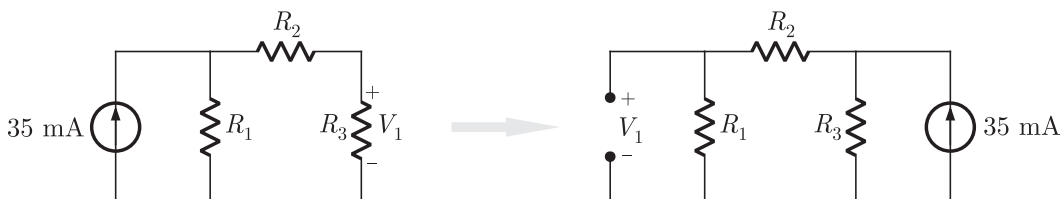

In figure (A),  $I_1 = 35 \text{ mA}$ ,  $V_1 = 2 \text{ V}$

In figure (B),  $I_2 = 35 \text{ mA}$ ,  $V_2 = ?$

Using reciprocity

$$\frac{V_1}{I_1} = \frac{V_2}{I_2}$$

So,  $V_2 = V_1 = 2 \text{ volt}$

Hence (A) is correct option.

## 5.10 SUBSTITUTION THEOREM

If the voltage across and the current through any branch of a dc bilateral network are known, this branch can be replaced by any combination of elements that will maintain the same voltage across and current through the chosen branch.


For example consider the circuit of figure 5.10.1. The voltage  $V_{ab}$  and the current  $I$  in the circuit are given as

$$V_{ab} = \left(\frac{6}{6+4}\right)10 = 6 \text{ V}$$


$$I = \frac{10}{6+4} = 1 \text{ A}$$

The  $6 \Omega$  resistor in branch  $a-b$  may be replaced with any combination of components, provided that the terminal voltage and current must be the same.

We see that the branches of figure 5.10.2a-e are each equivalent to the original branch between terminals  $a$  and  $b$  of the circuit in figure 5.10.1.

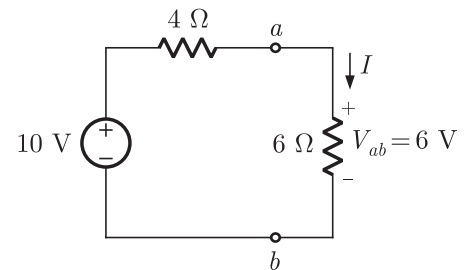

**Fig 5.10.1** A circuit having voltage  $V_{ab} = 6 \text{ V}$  and current  $I = 1 \text{ A}$  in branch  $ab$

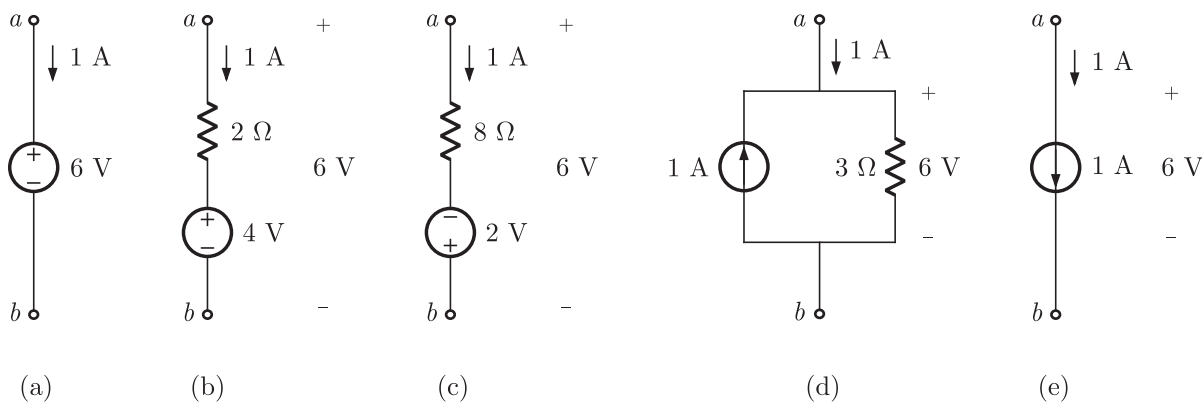

**Fig 5.10.2** Equivalent circuits for branch  $ab$



Also consider that the response of the remainder of the circuit of figure 5.10.1 is unchanged by substituting any one of the equivalent branches.

### ► EXAMPLE

If the  $60\ \Omega$  resistance in the circuit of figure (A) is to be replaced with a current source  $I_s$  and  $240\ \Omega$  shunt resistor as shown in figure (B), then magnitude and direction of required current source would be

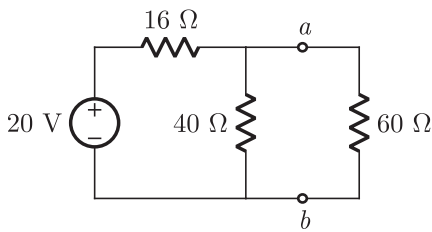


Fig.(A)

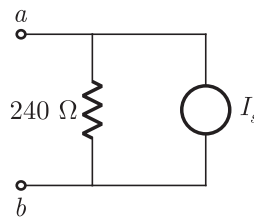


Fig.(B)

- (A) 200 mA, upward                      (B) 150 mA, downward  
 (C) 50 mA, downward                    (D) 150 mA, upward

### SOLUTION :

First we find the voltage and current for the branch  $ab$ , then substitute it with an equivalent.

$$V = \frac{40 \parallel 60}{(40 \parallel 60) + 16} (20) \quad (\text{using voltage division})$$

$$= \frac{24}{40} \times 20 = 12\ \text{V}$$

Current entering terminal  $a$ - $b$  is

$$I = \frac{V}{R} = \frac{12}{60} = 200\ \text{mA}$$

In fig(B), to maintain same voltage  $V = 12\ \text{V}$  current through  $240\ \Omega$  resistor must be

$$I_R = \frac{12}{240} = 50\ \text{mA}$$



Using KCL at terminal  $a$ , as shown

$$I = I_R + I_s$$

$$200 = 50 + I_s$$

$$I_s = 150\ \text{mA}, \quad (\text{downwards})$$

Hence (B) is correct option.

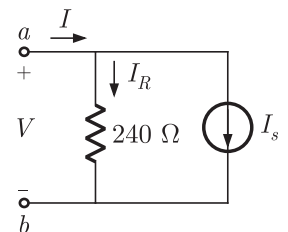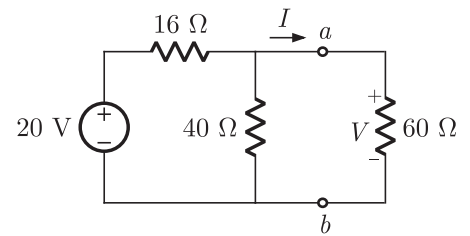



$$= -\frac{144}{5} = -28.8 \text{ V}$$

The equivalent resistance

$$R_{ab} = \frac{1}{\frac{1}{240} + \frac{1}{200} + \frac{1}{800}} = 96 \Omega$$

Now, the circuit is reduced as shown in figure.

$$I = \frac{28.8}{96 + 192} = 100 \text{ mA}$$

Hence (A) is correct option.


## 5.12 TELLEGEN'S THEOREM

Tellegen's theorem states that the sum of the power dissipations in a lumped network at any instant is always zero. This is supported by Kirchhoff's voltage and current laws. Tellegen's theorem is valid for any lumped network which may be linear or non-linear, passive or active, time-varying or time-invariant.

For a network with  $n$  branches, the power summation equation is,

$$\sum_{k=1}^{k=n} V_k I_k = 0$$

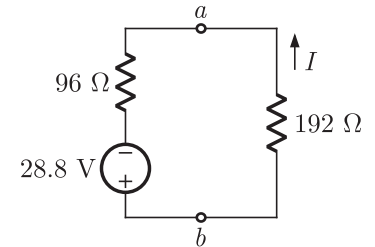One application of Tellegen's theorem is checking the quantities obtained when a circuit is analyzed. If the individual branch power dissipations do not add up to zero, then some of the calculated quantities are incorrect.




\*\*\*\*\*






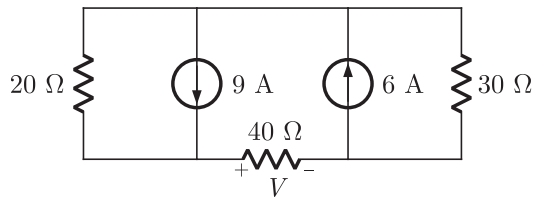**MCQ 5.1.7** In the circuit below, the voltage  $V$  across the  $40\ \Omega$  resistor would be equal to



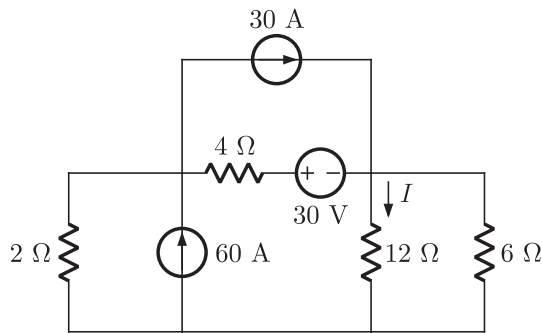
- (A) 80 volt (B) 40 volt  
(C) 160 volt (D) zero

**MCQ 5.1.8** In the circuit below, current  $I = I_1 + I_2 + I_3$ , where  $I_1$ ,  $I_2$  and  $I_3$  are currents due to 60 A, 30 A and 30 V sources acting alone. The values of  $I_1$ ,  $I_2$  and  $I_3$  are respectively



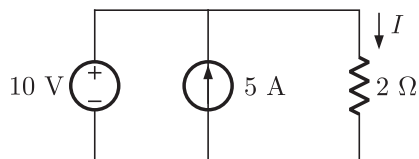
- (A) 8 A, 8 A,  $-4$  A  
(B) 12 A, 12 A,  $-5$  A  
(C) 4 A, 4 A,  $-1$  A  
(D) 2 A, 2 A,  $-4$  A

**MCQ 5.1.9** The value of current  $I$  flowing through  $2\ \Omega$  resistance in the circuit below, equals to



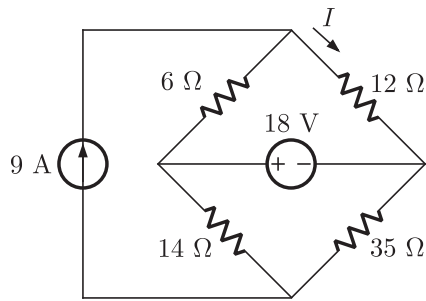- (A) 10 A (B) 5 A  
(C) 4 A (D) zero

**MCQ 5.1.10** In the circuit below, current  $I$  is equal to sum of two currents  $I_1$  and  $I_2$ . What are the values of  $I_1$  and  $I_2$  ?



- (A) 6 A, 1 A
- (B) 9 A, 6 A
- (C) 3 A, 1 A
- (D) 3 A, 4 A


**MCQ 5.1.11** A network consists only of independent current sources and resistors. If the values of all the current sources are doubled, then values of node voltages

- (A) remains same
- (B) will be doubled
- (C) will be halved
- (D) changes in some other way.

**MCQ 5.1.12** Consider a network which consists of resistors and voltage sources only. If the values of all the voltage sources and doubled, then the values of mesh current will be

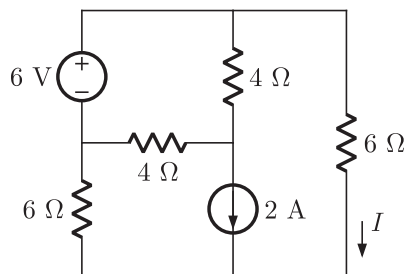
- (A) doubled
- (B) same
- (C) halved
- (D) none of these

**MCQ 5.1.13** In the circuit shown in the figure below, the value of current  $I$  will be given by



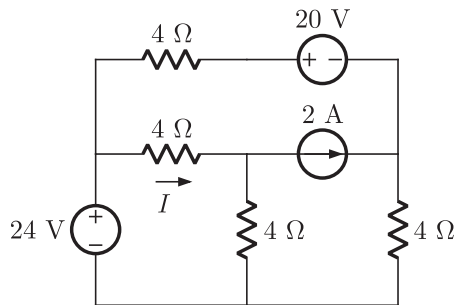
- (A) 1.5 A
- (B) -0.3 A
- (C) 0.05 A
- (D) -0.5 A

**MCQ 5.1.14** What is the value of current  $I$  in the following network ?



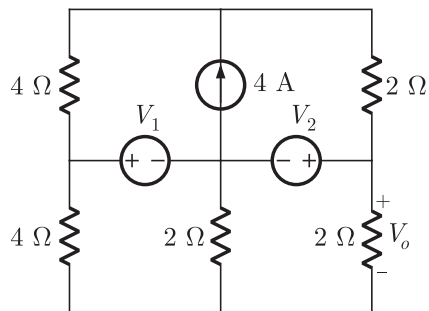
- (A) 4 A (B) 6 A  
(C) 2 A (D) 1 A

**MCQ 5.1.15** In the given network if  $V_1 = V_2 = 0$ , then what is the value of  $V_o$  ?



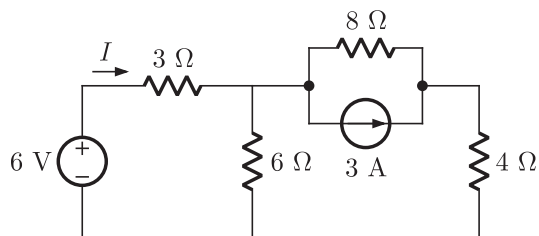- (A) 3.2 V (B) 8 V  
(C) 5.33 V (D) zero


**MCQ 5.1.16** The value of current  $I$  in the circuit below is equal to



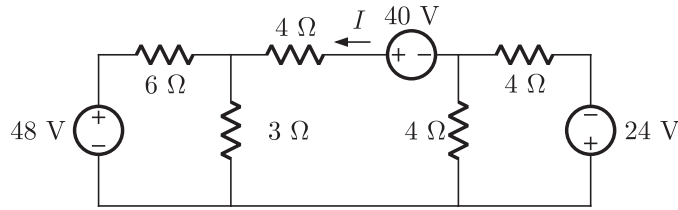- (A)  $\frac{2}{7}$  A (B) 1 A  
(C) 2 A (D) 4 A


**MCQ 5.1.17** What is the value of current  $I$  in the circuit shown below ?








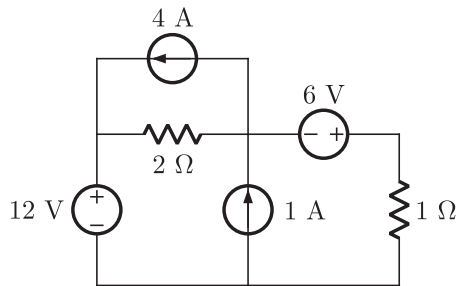
- (A) 8.5 A
- (B) 4.5 A
- (C) 1.5 A
- (D) 5.5 A

**MCQ 5.1.18** In the circuit below, the 12 V source



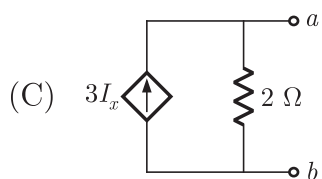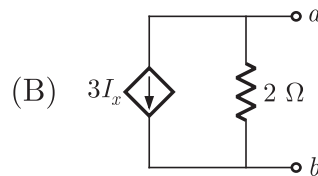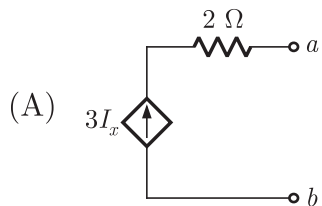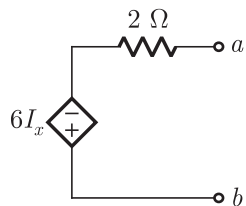
- (A) absorbs 36 W
- (B) delivers 4 W
- (C) absorbs 100 W
- (D) delivers 36 W

**MCQ 5.1.19** Which of the following circuits is equivalent to the circuit shown below ?






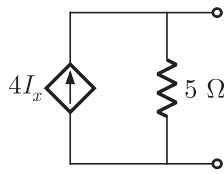(D) None of these

**MCQ 5.1.20** Consider a dependent current source shown in figure below.




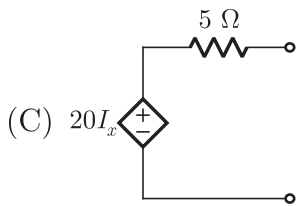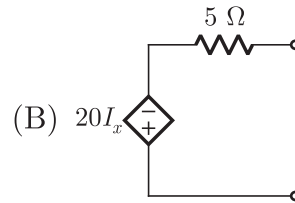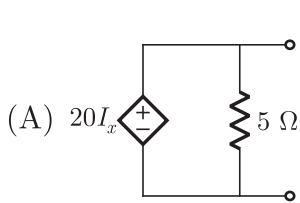The source transformation of above is given by






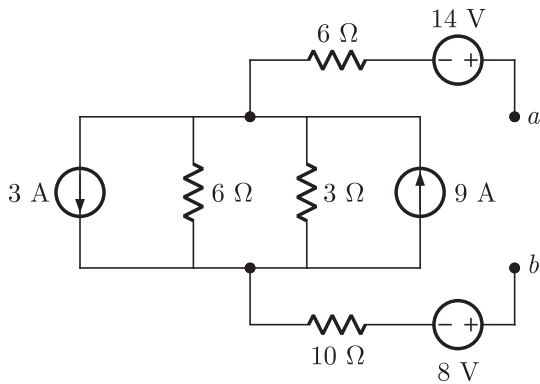
(D) Source transformation does not applicable to dependent sources

**MCQ 5.1.21** Consider a circuit shown in the figure




Which of the following circuit is equivalent to the above circuit ?

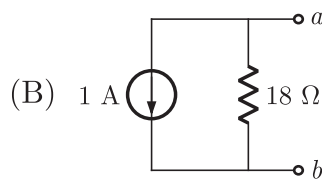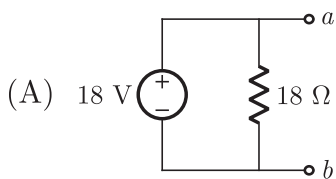

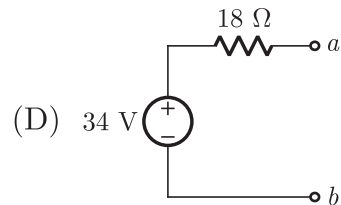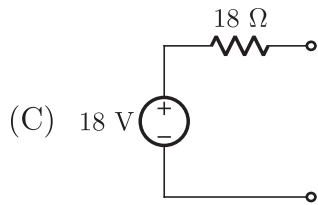

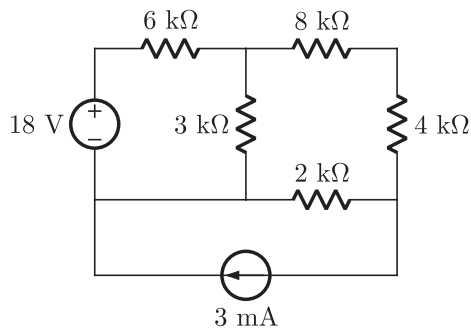**MCQ 5.1.22** How much power is being dissipated by the  $4\text{ k}\Omega$  resistor in the network ?




(A) 0 W

(B) 2.25 mW

(C) 9 mW

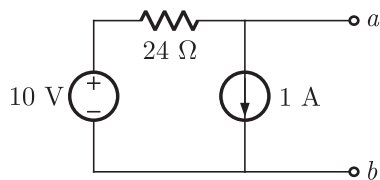(D) 4 mW

**MCQ 5.1.23** For the circuit shown in the figure the Thevenin voltage and resistance seen from the terminal  $a$ - $b$  are respectively




(A) 34 V,  $0\ \Omega$

(B) 20 V,  $24\ \Omega$

(C) 14 V,  $0\ \Omega$

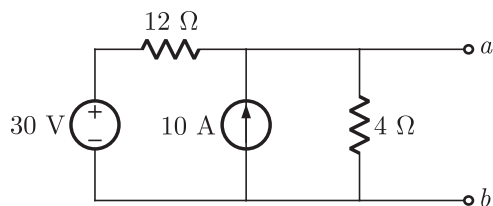(D)  $-14\ \text{V}$ ,  $24\ \Omega$

**MCQ 5.1.24** The Thevenin equivalent resistance  $R_{Th}$  between the nodes  $a$  and  $b$  in the following circuit is



(A)  $3\ \Omega$

(B)  $16\ \Omega$

(C)  $12\ \Omega$

(D)  $4\ \Omega$



**Common Data for Q. 34 to 35 :**

Consider the two circuits shown in figure (A) and figure (B) below

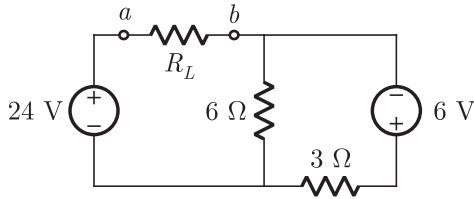


Fig.(A)


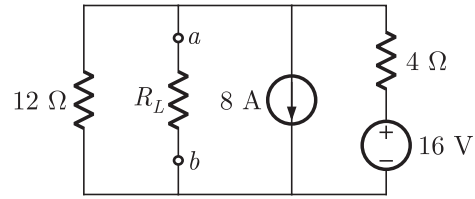


Fig.(B)

- MCQ 5.1.28** The value of Thevenin voltage across terminals  $a$ - $b$  of figure (A) and figure (B) respectively are
- (A) 30 V, 36 V (B) 28 V, -12 V  
 (C) 18 V, 12 V (D) 30 V, -12 V
- MCQ 5.1.29** The value of Thevenin resistance across terminals  $a$ - $b$  of figure (A) and figure (B) respectively are
- (A) zero, 3  $\Omega$  (B) 9  $\Omega$ , 16  $\Omega$   
 (C) 2  $\Omega$ , 3  $\Omega$  (D) zero, 16  $\Omega$

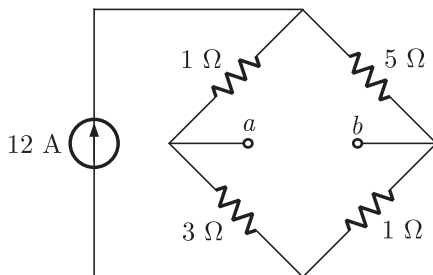**Statement for linked questions**

Consider the circuit shown in the figure.




- MCQ 5.1.30** The equivalent Thevenin voltage across terminal  $a$ - $b$  is
- (A) 31.2 V (B) 19.2 V  
 (C) 16.8 V (D) 24 V
- MCQ 5.1.31** The Norton equivalent current with respect to terminal  $a$ - $b$  is
- (A) 13 A (B) 7 A  
 (C) 8 A (D) 10 A

- MCQ 5.1.32** For a network having resistors and independent sources, it is desired to obtain Thevenin equivalent across the load which is in parallel with an ideal current source. Then which of the following statement is true ?
- (A) The Thevenin equivalent circuit is simply that of a voltage source.
- (B) The Thevenin equivalent circuit consists of a voltage source and a series resistor.
- (C) The Thevenin equivalent circuit does not exist but the Norton equivalent does exist.
- (D) None of these


- MCQ 5.1.33** The Thevenin equivalent circuit of a network consists only of a resistor (Thevenin voltage is zero). Then which of the following elements might be contained in the network ?
- (A) resistor and independent sources
- (B) resistor only
- (C) resistor and dependent sources
- (D) resistor, independent sources and dependent sources.

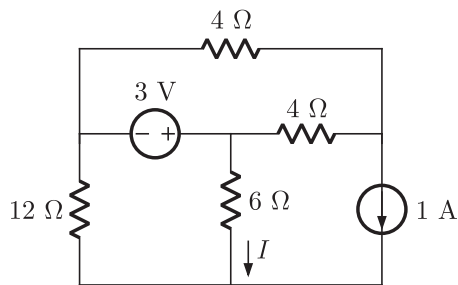- MCQ 5.1.34** In the following network, value of current  $I$  through  $6\ \Omega$  resistor is given by



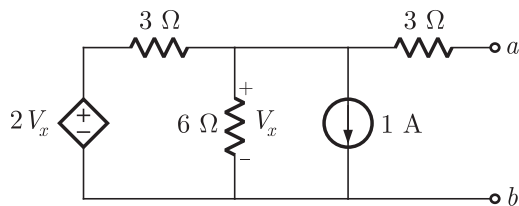
- (A) 0.83 A
- (B) 2 A
- (C) 1 A
- (D)  $-0.5$  A

- MCQ 5.1.35** For the circuit shown in the figure, the Thevenin's voltage and resistance looking into  $a$ - $b$  are



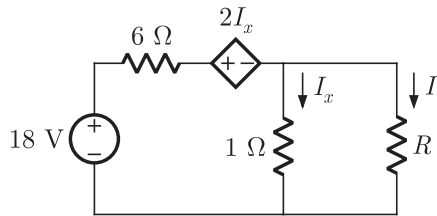
- (A) 2 V,  $3\ \Omega$
- (B) 2 V,  $2\ \Omega$
- (C) 6 V,  $-9\ \Omega$
- (D) 6 V,  $-3\ \Omega$

**MCQ 5.1.36** For the circuit below, what value of  $R$  will cause  $I = 2\text{ A}$  ?



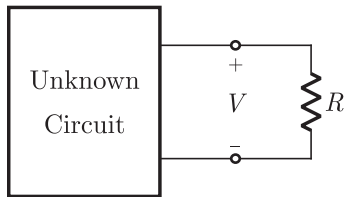- (A)  $2/3\ \Omega$
- (B)  $4\ \Omega$
- (C) zero
- (D) none of these

**MCQ 5.1.37** For the following circuit, values of voltage  $V$  for different values of  $R$  are given in the table.




$R$	$V$
$3\ \Omega$	$6\ \text{V}$
$8\ \Omega$	$8\ \text{V}$

The Thevenin voltage and resistance of the unknown circuit are respectively.





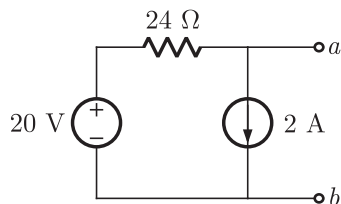
- (A)  $14\ \text{V}$ ,  $4\ \Omega$
- (B)  $4\ \text{V}$ ,  $1\ \Omega$
- (C)  $14\ \text{V}$ ,  $6\ \Omega$
- (D)  $10\ \text{V}$ ,  $2\ \Omega$

**MCQ 5.1.38** In the circuit shown below, the Norton equivalent current and resistance with respect to terminal  $a$ - $b$  is




- (A)  $\frac{17}{6}\ \text{A}$ ,  $0\ \Omega$
- (B)  $2\ \text{A}$ ,  $24\ \Omega$
- (C)  $-\frac{7}{6}\ \text{A}$ ,  $24\ \Omega$
- (D)  $-2\ \text{A}$ ,  $24\ \Omega$

**MCQ 5.1.39** The Norton equivalent circuit for the circuit shown in figure is given by

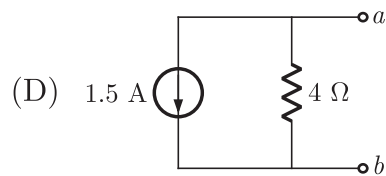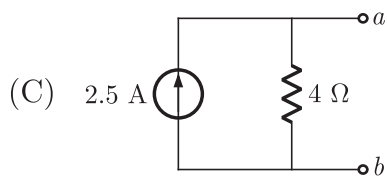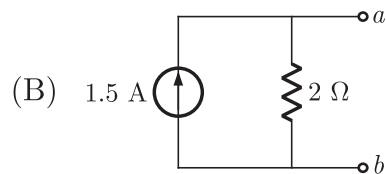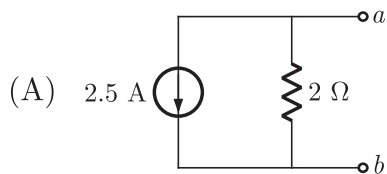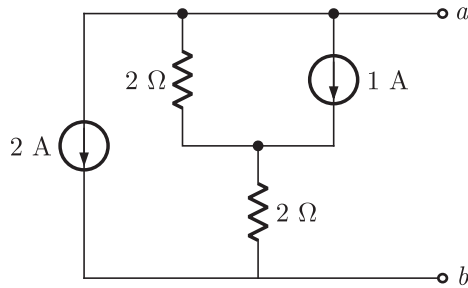

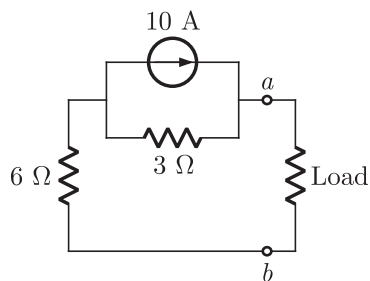**MCQ 5.1.40** What are the values of equivalent Norton current source ( $I_N$ ) and equivalent resistance ( $R_N$ ) across the load terminal of the circuit shown in figure ?



	$I_N$	$R_N$
(A)	10 A	2 Ω
(B)	10 A	9 Ω
(C)	3.33 A	9 Ω
(D)	6.66 A	2 Ω

**MCQ 5.1.41** For a network consisting of resistors and independent sources only, it is desired to obtain Thevenin's or Norton's equivalent across a load which is in series parallel with an ideal voltage sources.


Consider the following statements :

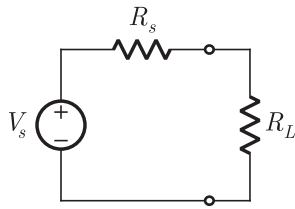1. Thevenin equivalent circuit across this terminal does not exist.
2. The Thevenin equivalent circuit exists and it is simply that of a voltage source.
3. The Norton equivalent circuit for this terminal does not exist.






- MCQ 5.1.45** In the circuit below, if  $R_L$  is fixed and  $R_s$  is variable then for what value of  $R_s$  power dissipated in  $R_L$  will be maximum ?



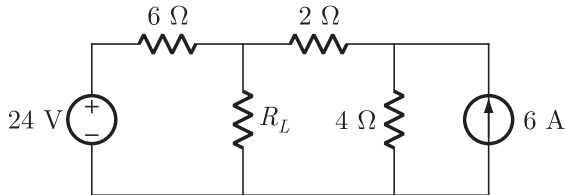- (A)  $R_s = R_L$  (B)  $R_s = 0$   
 (C)  $R_s = R_L/2$  (D)  $R_s = 2R_L$

- MCQ 5.1.46** In the circuit shown below the maximum power transferred to  $R_L$  is  $P_{\max}$ , then



- (A)  $R_L = 12 \Omega$ ,  $P_{\max} = 12 \text{ W}$  (B)  $R_L = 3 \Omega$ ,  $P_{\max} = 96 \text{ W}$   
 (C)  $R_L = 3 \Omega$ ,  $P_{\max} = 48 \text{ W}$  (D)  $R_L = 12 \Omega$ ,  $P_{\max} = 24 \text{ W}$

- MCQ 5.1.47** In the circuit shown in figure (A) if current  $I_1 = 2 \text{ A}$ , then current  $I_2$  and  $I_3$  in figure (B) and figure (C) respectively are

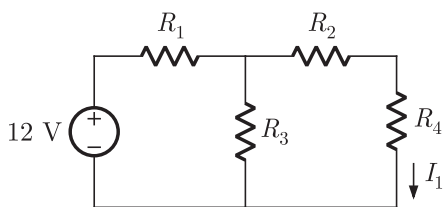


Fig.(A)

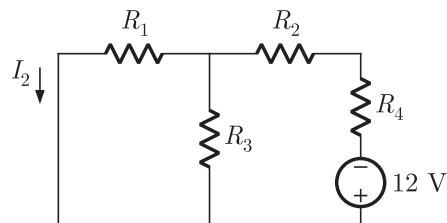


Fig.(B)

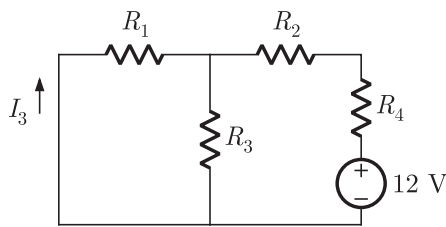


Fig.(C)

(A) 2 A, 2 A

(B) -2 A, 2 A

(C) 2 A, -2 A

(D) -2 A, -2 A

**MCQ 5.1.48** In the circuit of figure (A), if  $I_1 = 20$  mA, then what is the value of current  $I$  in the circuit of figure (B) ?

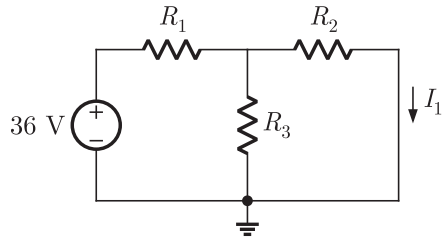


Fig.(A)

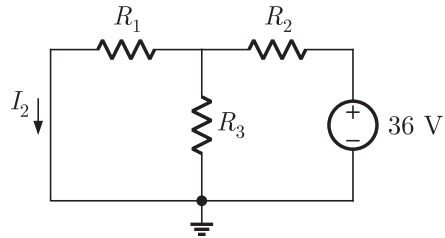


Fig.(B)

(A) 40 mA

(B) -20 mA

(C) 20 mA

(D)  $R_1, R_2$  and  $R_3$  must be known

**MCQ 5.1.49** If  $V_1 = 2$  V in the circuit of figure (A), then what is the value of  $V_2$  in the circuit of figure (B) ?

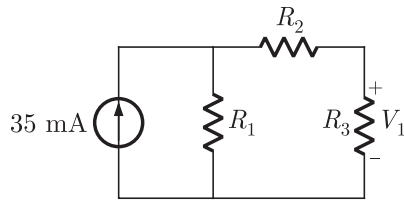


Fig.(A)

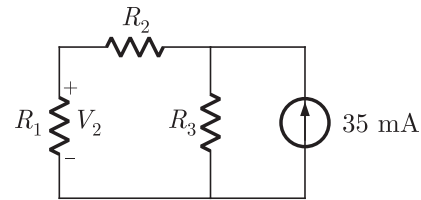


Fig.(B)


(A) 2 V

(B) -2 V

(C) 4 V

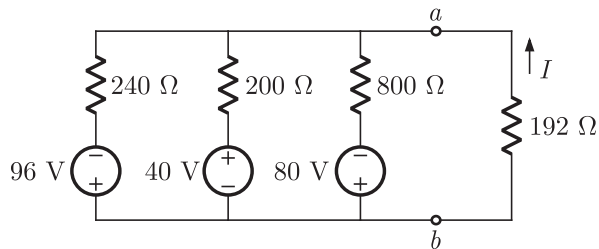(D)  $R_1, R_2$  and  $R_3$  must be known

**MCQ 5.1.50** The value of current  $I$  in the circuit below is equal to




(A) 100 mA

(B) 10 mA

(C) 233.34 mA

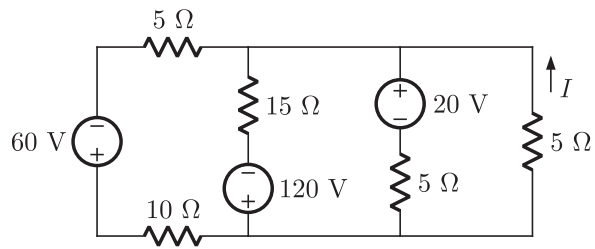(D) none of these

**MCQ 5.1.51** The value of current  $I$  in the following circuit is equal to



(A) 1 A

(B) 6 A






(C) 3 A

(D) 2 A


\*\*\*\*\*

# PRACTICE B

**MCQ 5.2.1** A simple equivalent circuit of the two-terminal network shown in figure is

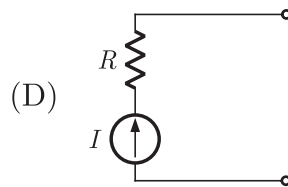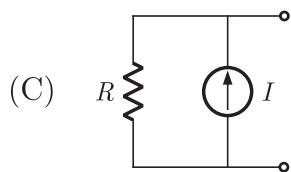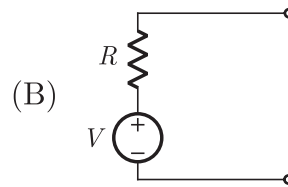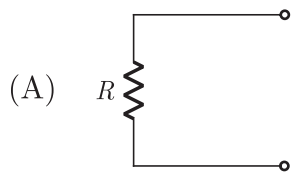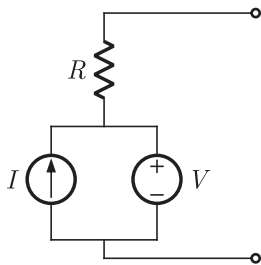

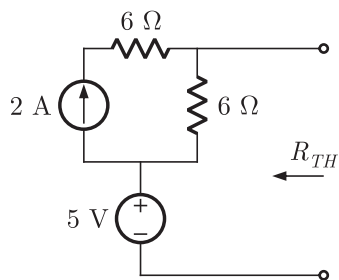**MCQ 5.2.2** For the following circuit the value of  $R_{Th}$  is




(A)  $3 \Omega$

(B)  $12 \Omega$

(C)  $6 \Omega$

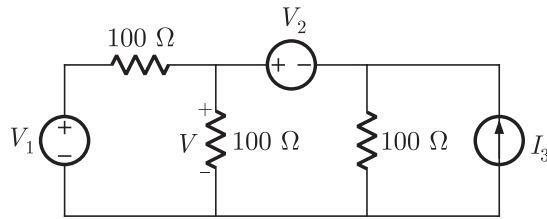
(D)  $\infty$

- MCQ 5.2.3** If  $V = AV_1 + BV_2 + CI_3$  in the following circuit, then values of  $A$ ,  $B$  and  $C$  respectively are



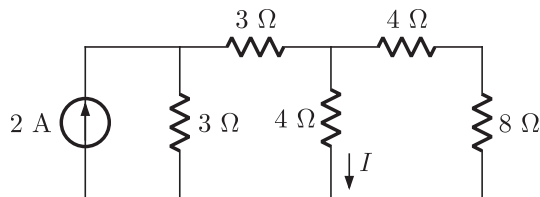
- (A)  $\frac{2}{3}, \frac{2}{3}, \frac{1}{3}$  (B)  $\frac{1}{3}, \frac{1}{3}, \frac{100}{3}$   
 (C)  $\frac{1}{2}, \frac{1}{2}, \frac{1}{3}$  (D)  $\frac{1}{3}, \frac{2}{3}, \frac{100}{3}$

- MCQ 5.2.4** What is the value of current  $I$  in the network of figure ?



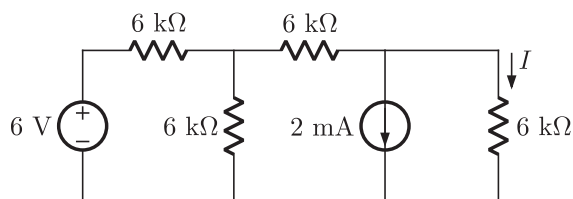
- (A) 0.67 A (B) 2 A  
 (C) 1.34 A (D) 0.5 A

- MCQ 5.2.5** The value of current  $I$  in the figure is



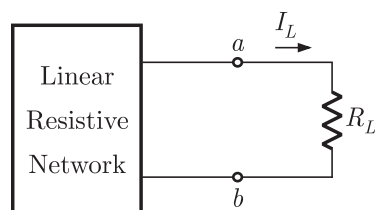- (A)  $-1$  mA (B)  $1.4$  mA  
 (C)  $1.8$  mA (D)  $-1.2$  mA

- MCQ 5.2.6** For the circuit of figure, some measurements were made at the terminals  $a$ - $b$  and given in the table below.




$R_L$	$V_L$
$2 \Omega$	$10 \text{ V}$
$10 \Omega$	$6 \text{ V}$

What is the value of  $I_L$  for  $R_L = 20 \Omega$  ?

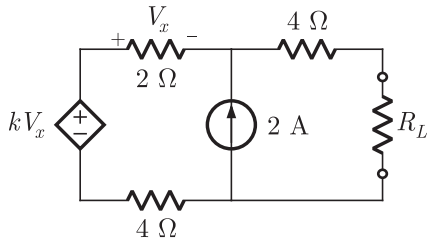
- (A) 3 A
- (B) 12 A
- (C) 2 A
- (D) 4 A

**MCQ 5.2.7** In the circuit below, for what value of  $k$ , load  $R_L = 2 \Omega$  absorbs maximum power ?



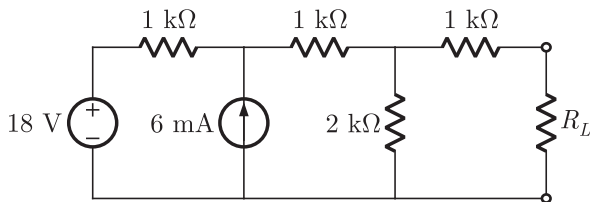
- (A) 4
- (B) 7
- (C) 2
- (D) 6

**MCQ 5.2.8** In the circuit shown below, the maximum power that can be delivered to the load  $R_L$  is equal to



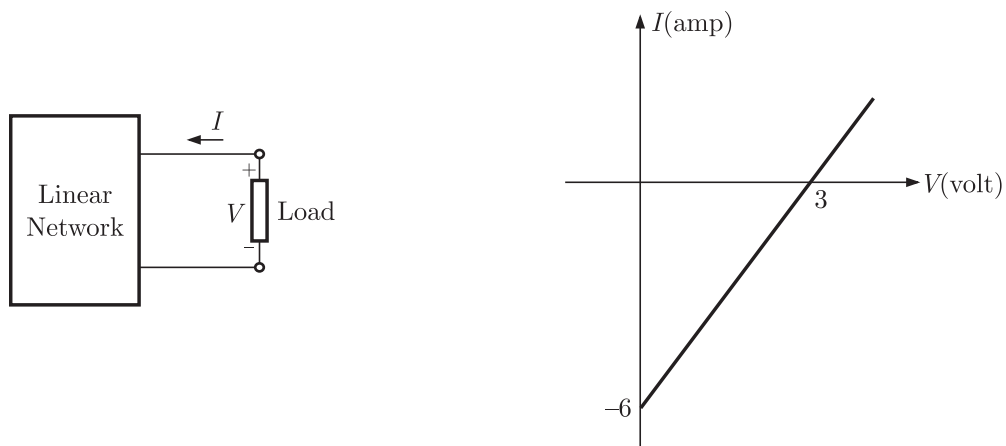
- (A) 72 mW
- (B) 36 mW
- (C) 24 mW
- (D) 18 mW

**MCQ 5.2.9** For the linear network shown below,  $V-I$  characteristic is also given in the figure. The value of Norton equivalent current and resistance respectively are



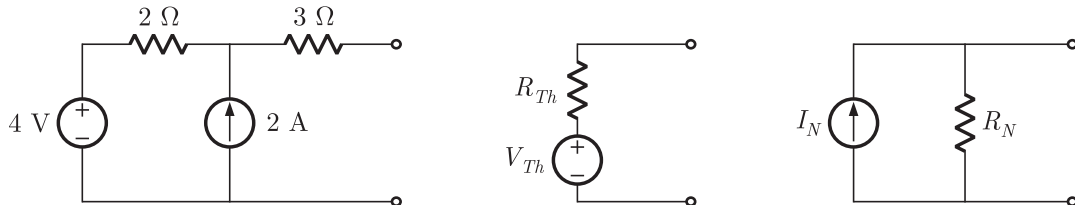- (A) 3 A, 2  $\Omega$  (B) 6  $\Omega$ , 2  $\Omega$   
 (C) 6 A, 0.5  $\Omega$  (D) 3 A, 0.5  $\Omega$


**MCQ 5.2.10** In the following circuit a network and its Thevenin and Norton equivalent are given.



The value of the parameter are

	$V_{Th}$	$R_{Th}$	$I_N$	$R_N$
(A)	4 V	2 $\Omega$	2 A	2 $\Omega$
(B)	4 V	2 $\Omega$	2 A	3 $\Omega$
(C)	8 V	1.2 $\Omega$	$\frac{30}{3}$ A	1.2 $\Omega$
(D)	8 V	5 $\Omega$	$\frac{8}{5}$ A	5 $\Omega$

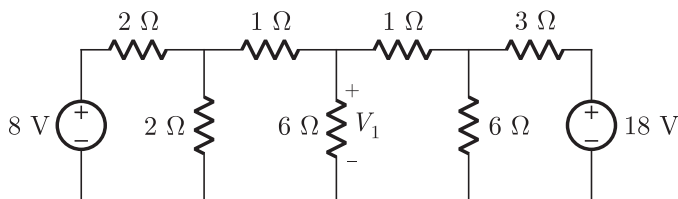**MCQ 5.2.11** In the following circuit the value of voltage  $V_1$  is




- (A) 6 V (B) 7 V  
 (C) 8 V (D) 10 V

**MCQ 5.2.12** A practical DC current source provide 20 kW to a 50  $\Omega$  load and 20 kW to a 200  $\Omega$  load. The maximum power, that can drawn from it, is

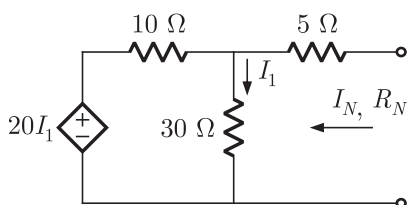- (A) 22.5 kW (B) 45 kW  
 (C) 30.3 kW (D) 40 kW

**MCQ 5.2.13** For the following circuit the value of equivalent Norton current  $I_N$  and resistance  $R_N$  are







(A) 2 A, 20 Ω

(B) 2 A, -20 Ω

(C) 0 A, 20 Ω

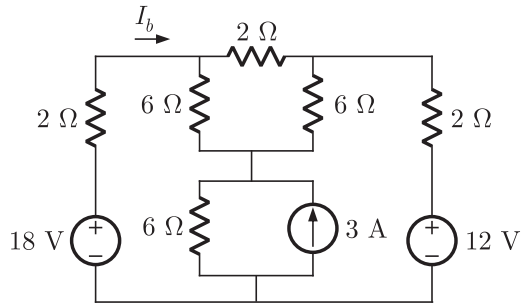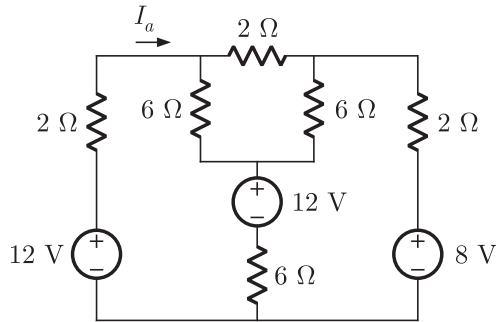(D) 0 A, -20 Ω

**MCQ 5.2.14** Consider the following circuits shown below



The relation between  $I_a$  and  $I_b$  is


(A)  $I_b = I_a + 6$

(B)  $I_b = I_a + 2$

(C)  $I_b = 1.5I_a$

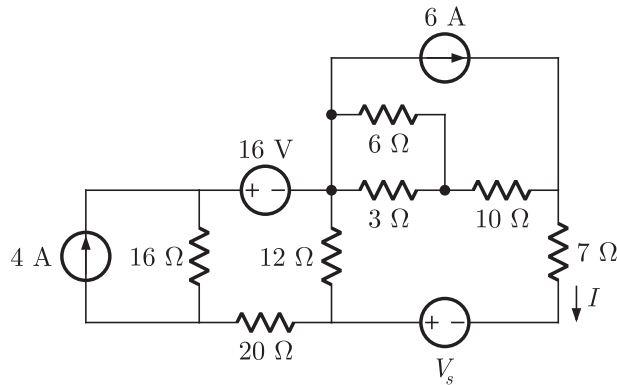(D)  $I_b = I_a$

**MCQ 5.2.15** If  $I = 5$  A in the circuit below, then what is the value of voltage source  $V_s$  ?




(A) 28 V

(B) 56 V

(C) 200 V

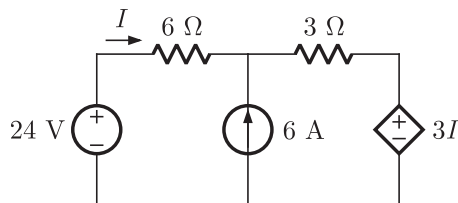(D) 224 V

**MCQ 5.2.16** For the following circuit, value of current  $I$  is given by



(A) 0.5 A


(B) 3.5 A

(C) 1 A

(D) 2 A
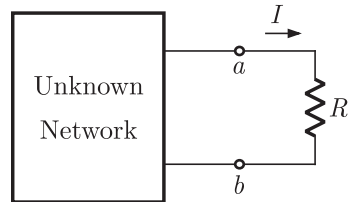
### Statement for Linked Questions

In the following circuit, some measurements were made at the terminals  $a$ ,  $b$  and given in the table below.



$R$	$I$
$3 \Omega$	$2 \text{ A}$
$5 \Omega$	$1.6 \text{ A}$

- MCQ 5.2.17** The Thevenin equivalent of the unknown network across terminal  $a$ - $b$  is  
 (A)  $3 \Omega$ ,  $14 \text{ V}$  (B)  $5 \Omega$ ,  $16 \text{ V}$   
 (C)  $16 \Omega$ ,  $38 \text{ V}$  (D)  $10 \Omega$ ,  $26 \text{ V}$

- MCQ 5.2.18** The value of  $R$  that will cause  $I$  to be  $1 \text{ A}$ , is  
 (A)  $22 \Omega$  (B)  $16 \Omega$   
 (C)  $8 \Omega$  (D)  $11 \Omega$

- MCQ 5.2.19** In the circuit shown in fig (a) if current  $I_1 = 2.5 \text{ A}$  then current  $I_2$  and  $I_3$  in fig (B) and (C) respectively are

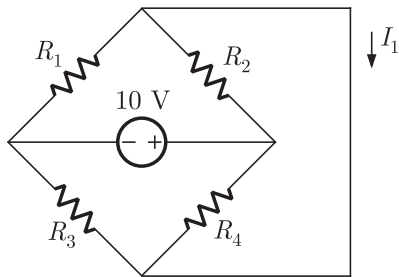


Fig.(A)

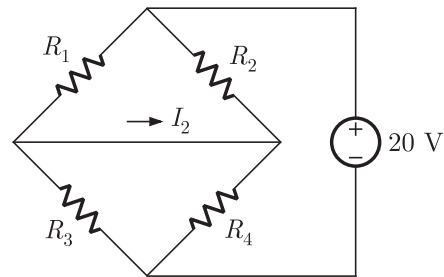


Fig.(B)


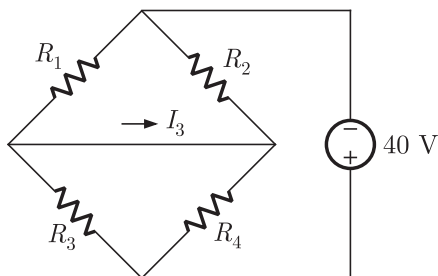


Fig.(C)

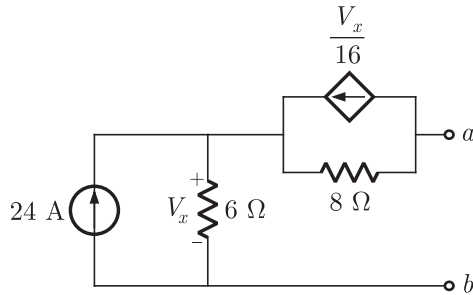
- (A) 5 A, 10 A
- (B) -5 A, 10 A
- (C) 5 A, -10 A
- (D) -5 A, -10 A

**MCQ 5.2.20** The Thevenin equivalent resistance between terminal  $a$  and  $b$  in the following circuit is



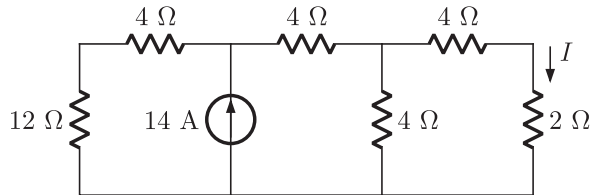
- (A) 22 Ω
- (B) 11 Ω
- (C) 17 Ω
- (D) 1 Ω

**MCQ 5.2.21** In the circuit shown below, the value of current  $I$  will be given by



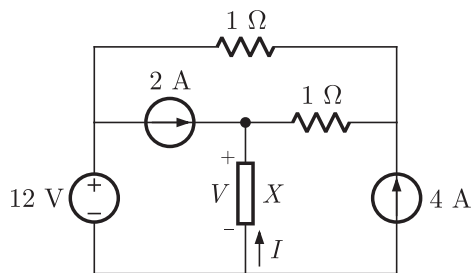- (A) 2.5 A
- (B) 1.5 A
- (C) 4 A
- (D) 2 A


**MCQ 5.2.22** The  $V$ - $I$  relation of the unknown element  $X$  in the given network is  $V = AI + B$ . The value of  $A$  (in ohm) and  $B$  (in volt) respectively are



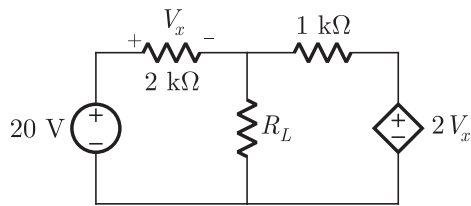- (A) 2, 20
- (B) 2, 8
- (C) 0.5, 4
- (D) 0.5, 16




**MCQ 5.2.25** In the circuit shown, what value of  $R_L$  maximizes the power delivered to  $R_L$  ?



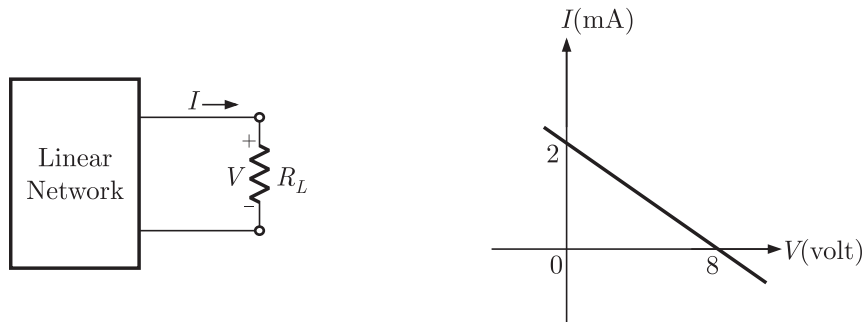
- (A)  $286 \Omega$  (B)  $350 \Omega$   
 (C) zero (D)  $500 \Omega$

**MCQ 5.2.26** The  $V$ - $I$  relation for the circuit below is plotted in the figure. The maximum power that can be transferred to the load  $R_L$  will be



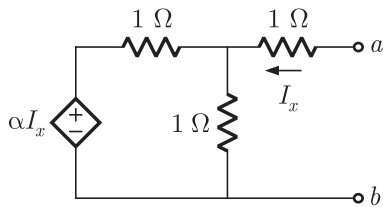
- (A) 4 mW (B) 8 mW  
 (C) 2 mW (D) 16 mW

**MCQ 5.2.27** In the following circuit equivalent Thevenin resistance between nodes  $a$  and  $b$  is  $R_{Th} = 3 \Omega$ . The value of  $\alpha$  is



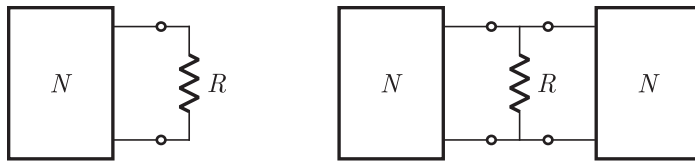- (A) 2 (B) 1  
 (C) 3 (D) 4

**MCQ 5.2.28** A network  $N$  feeds a resistance  $R$  as shown in circuit below. Let the power consumed by  $R$  be  $P$ . If an identical network is added as shown in figure, the power consumed by  $R$  will be



- (A) equal to  $P$  (B) less than  $P$   
 (C) between  $P$  and  $4P$  (D) more than  $4P$

**MCQ 5.2.29** A certain network consists of a large number of ideal linear resistors, one of which is  $R$  and two constant ideal source. The power consumed by  $R$  is  $P_1$  when only the first source is active, and  $P_2$  when only the second source is active. If both sources are active simultaneously, then the power consumed by  $R$  is

- (A)  $P_1 \pm P_2$  (B)  $\sqrt{P_1} \pm \sqrt{P_2}$   
 (C)  $(\sqrt{P_1} \pm \sqrt{P_2})^2$  (D)  $(P_1 \pm P_2)^2$

**MCQ 5.2.30** If the  $60\ \Omega$  resistance in the circuit of figure (A) is to be replaced with a current source  $I_s$  and  $240\ \Omega$  shunt resistor as shown in figure (B), then magnitude and direction of required current source would be

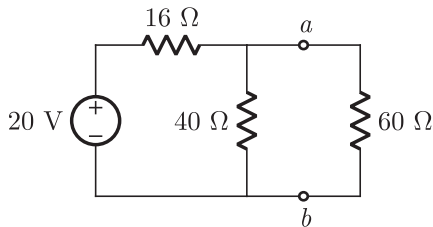


Fig.(A)


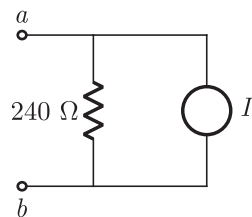


Fig.(B)

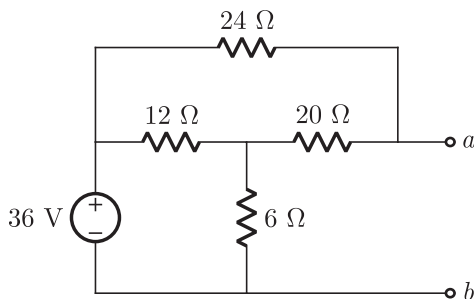- (A) 200 mA, upward (B) 150 mA, downward  
 (C) 50 mA, downward (D) 150 mA, upward

**MCQ 5.2.31** The Thevenin's equivalent of the circuit shown in the figure is




- (A) 4 V,  $48\ \Omega$  (B) 24 V,  $12\ \Omega$   
 (C) 24 V,  $24\ \Omega$  (D) 12 V,  $12\ \Omega$

**MCQ 5.2.32** The voltage  $V_L$  across the load resistance in the figure is given by


$$V_L = V \left( \frac{R_L}{R + R_L} \right)$$

$V$  and  $R$  will be equal to

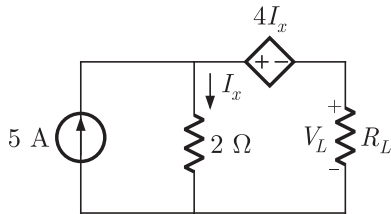

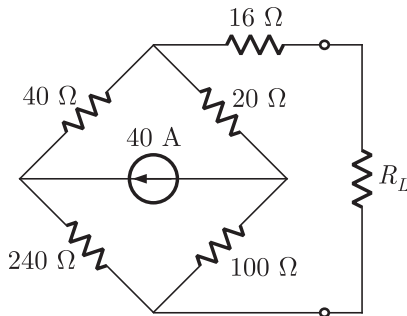- (A)  $-10 \text{ V}, 2 \Omega$  (B)  $10 \text{ V}, 2 \Omega$   
 (C)  $-10 \text{ V}, -2 \Omega$  (D) none of these


**MCQ 5.2.33** The maximum power that can be transferred to the load resistor  $R_L$  from the current source in the figure is



- (A) 4 W (B) 8 W  
 (C) 16 W (D) 2 W

**Common data for Q. 34 to Q. 35**


An electric circuit is fed by two independent sources as shown in figure.

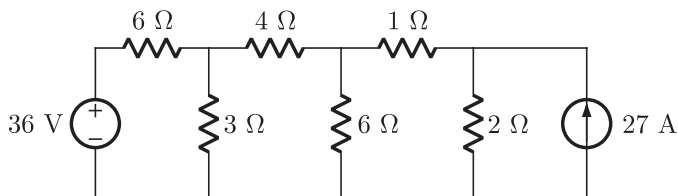

**MCQ 5.2.34** The power supplied by 36 V source will be  
 (A) 108 W (B) 162 W  
 (C) 129.6 W (D) 216 W


- MCQ 5.2.35** The power supplied by 27 A source will be  
 (A) 972 W (B) 1083 W  
 (C) 1458 W (D) 1026 W

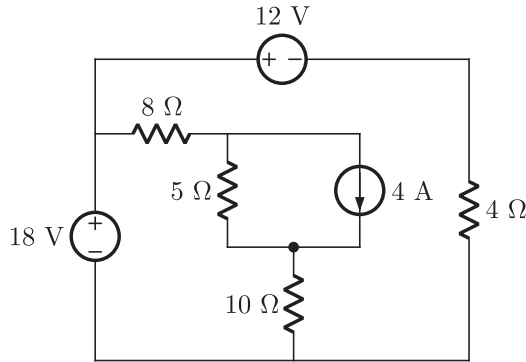- MCQ 5.2.36** In the circuit shown in the given figure, power dissipated in 4 Ω resistor is



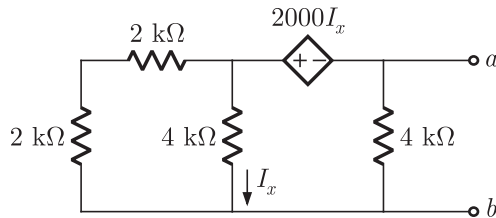
- (A) 225 W (B) 121 W  
 (C) 9 W (D) none of these

- MCQ 5.2.37** In the circuit given below, viewed from  $a$ - $b$ , the circuit can be reduced to an equivalent circuit as



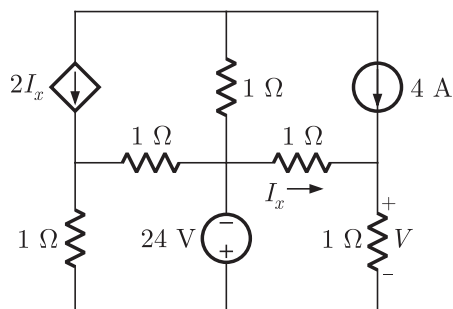- (A) 10 volt source in series with 2 kΩ resistor  
 (B) 1250 Ω resistor only  
 (C) 20 V source in series with 1333.34 Ω resistor  
 (D) 800 Ω resistor only


- MCQ 5.2.38** What is the value of voltage  $V$  in the following network ?





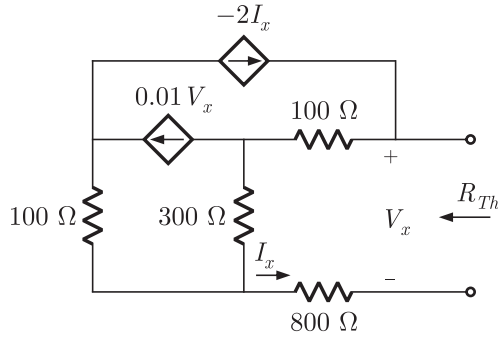
- (A) 14 V
- (B) 28 V
- (C) -10 V
- (D) none of these

**MCQ 5.2.39** For the circuit shown in figure below the value of  $R_{Th}$  is



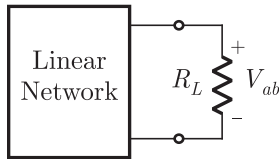- (A) 100 Ω
- (B) 136.4 Ω
- (C) 200 Ω
- (D) 272.8 Ω

**MCQ 5.2.40** Consider the network shown below :




The power absorbed by load resistance  $R_L$  is shown in table :

$R_L$	10 kΩ	30 kΩ
$P$	3.6 MW	1.5 A

The value of  $R_L$ , that would absorb maximum power, is

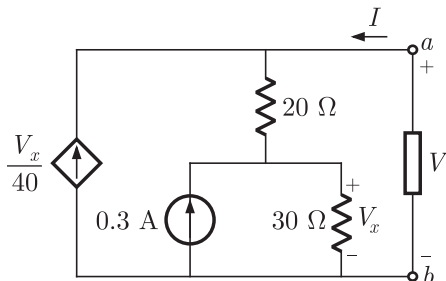- (A) 60 kΩ
- (B) 100 Ω
- (C) 300 Ω
- (D) 30 kΩ

**MCQ 5.2.41** The  $V$ - $I$  equation for the network shown in figure, is given by




(A)  $7V = 200I + 54$

(B)  $V = 100I + 36$

(C)  $V = 200I + 54$

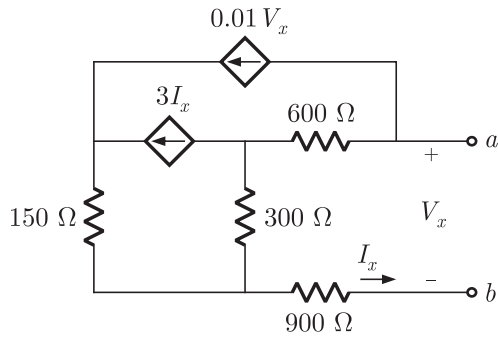(D)  $V = 50I + 54$

**MCQ 5.2.42** In the following circuit the value of open circuit voltage and Thevenin resistance at terminals  $a, b$  are



(A)  $V_{OC} = 100 \text{ V}, R_{Th} = 1800 \text{ } \Omega$

(B)  $V_{OC} = 0 \text{ V}, R_{Th} = 270 \text{ } \Omega$

(C)  $V_{OC} = 100 \text{ V}, R_{Th} = 90 \text{ } \Omega$

(D)  $V_{OC} = 0 \text{ V}, R_{Th} = 90 \text{ } \Omega$

\*\*\*\*\*